

ESE3700: Circuit-Level Modeling, Design and Optimization for Digital Systems

Lec 16: Apr 1, 2024

Synchronous Timing Discipline and
Clocking






Today

- ❑ Managing Timing
- ❑ Latches
- ❑ Registers, clocking

Timing Setup (Preclass 1&2)

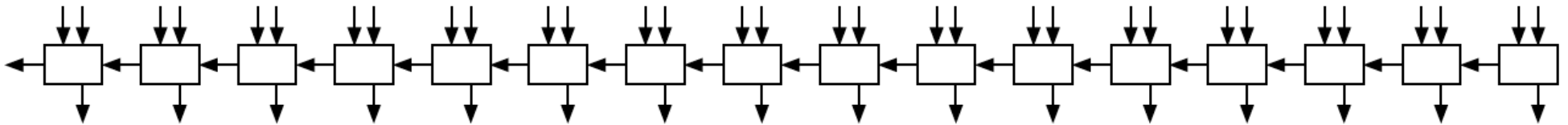
- Delay from 3 adder-inputs to 2 adder-outputbits is T_{bit}
 - i.e single bitslice delay is T_{bit}



- Worst-case delay to output?
- Shortest delay to output?
 - assuming the output switches

Timing Setup (Preclass 3)

 - New set of inputs every $20T_{\text{bit}}$
 - How does it behave?
- bitrev: $\text{Out}[i] = \text{In}[17-i]$
 - Assume delay of bitrev $\ll T_{\text{bit}}$





Challenge

- ❑ Logic paths have different delays
 - E.g. different output bits in an adder
- ❑ Delay of signal is data dependent
 - E.g. length of carry propagation
- ❑ Delay is chip dependent
 - E.g. Threshold Variation
- ❑ Delay is environment dependent
 - E.g. Temperature




Challenge

- ❑ Logic paths have different delays
 - E.g. different output bits in an adder
- ❑ Delay of signal is data dependent
 - E.g. length of carry propagation
- ❑ Delay is chip dependent
 - E.g. Threshold Variation
- ❑ Delay is environment dependent
 - E.g. Temperature
- ❑ Proper behavior depends on inputs being coordinated




Logic Timing

 - How do we fix this?
 - Make it possible to input a new value every $20T_{\text{bit}}$?





Discipline

 - ❑ Add circuit elements to
 - hold values
 - and change at coordinated point
 - Control when changes seen by circuit
- ❑ Only have to make sure to **wait long enough** for all results
- ❑ Decouple outputs and inputs
 - timing of signal change (settling of output change)...
 - ...from timing of signal usage (output used as input)



Synchronous Discipline

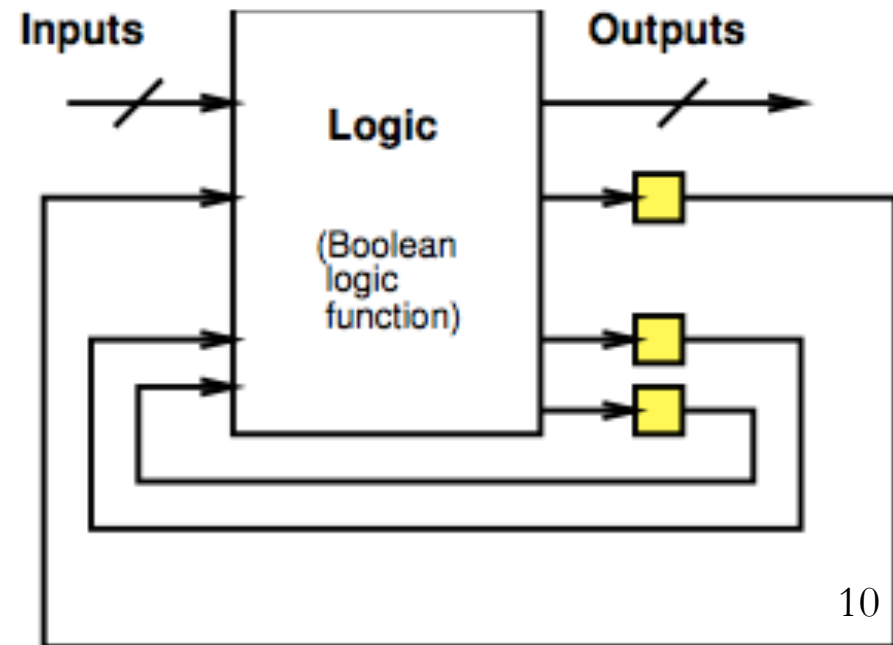 - ❑ Add state elements (registers, latches)
- ❑ Compute
 - From state elements
 - Through combinational logic
 - To new values for state elements





Latch

- ❑ Build with combinational logic
- ❑ Build with pass logic




Latch (Preclass 4a)

- $\phi=1 \rightarrow \text{Out}=\text{In}$
- $\phi=0 \rightarrow \text{Out}=\text{Out}$

- How do we build a latch from combinational logic?
 - At gate level


Multiplexer-based Latch from CMOS Logic

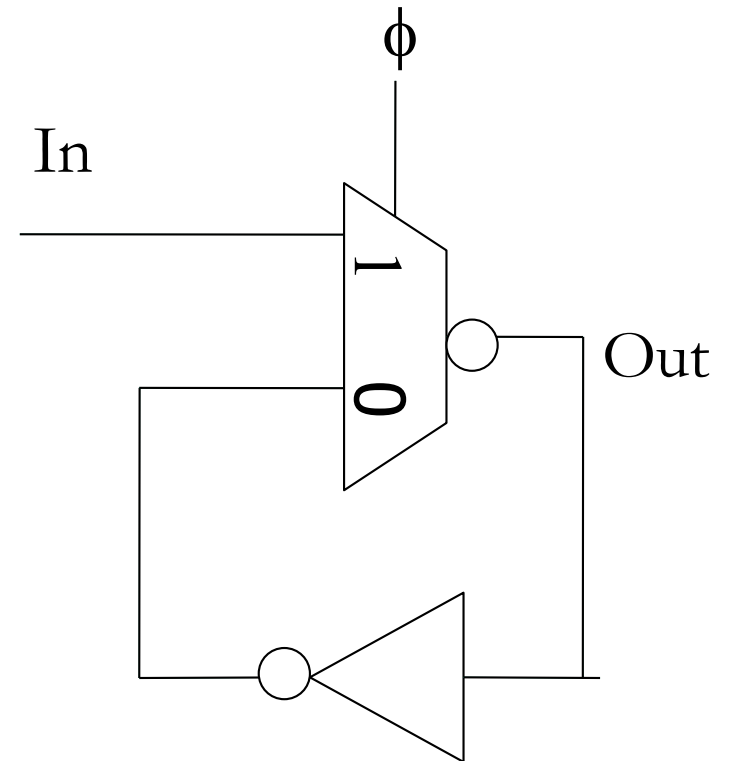- $\phi=1 \rightarrow \text{Out}=\text{In}$
- $\phi=0 \rightarrow \text{Out}=\text{Out}$




How to build the mux with pass logic?

Mux at Transistor Level


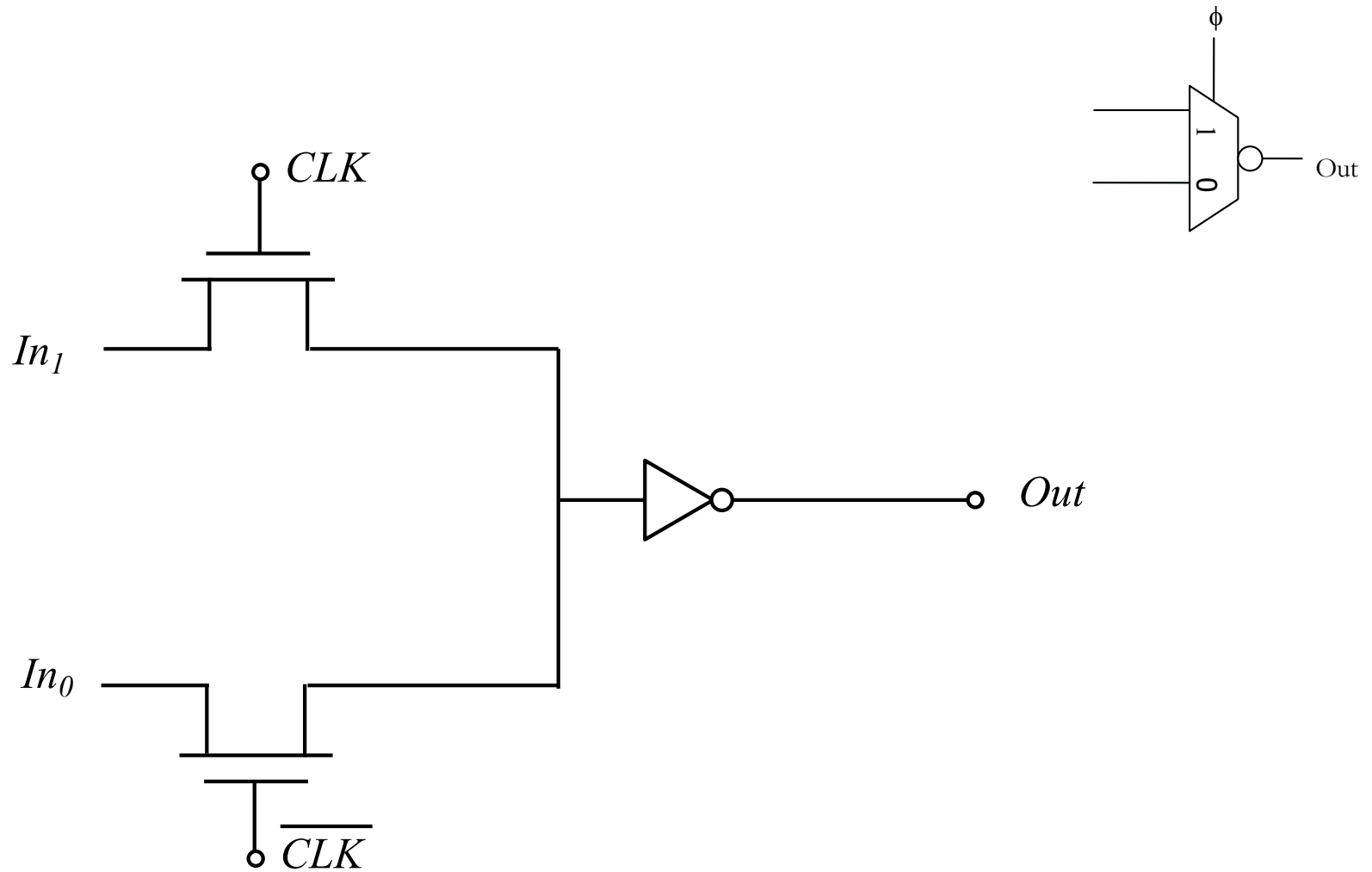





MuxL

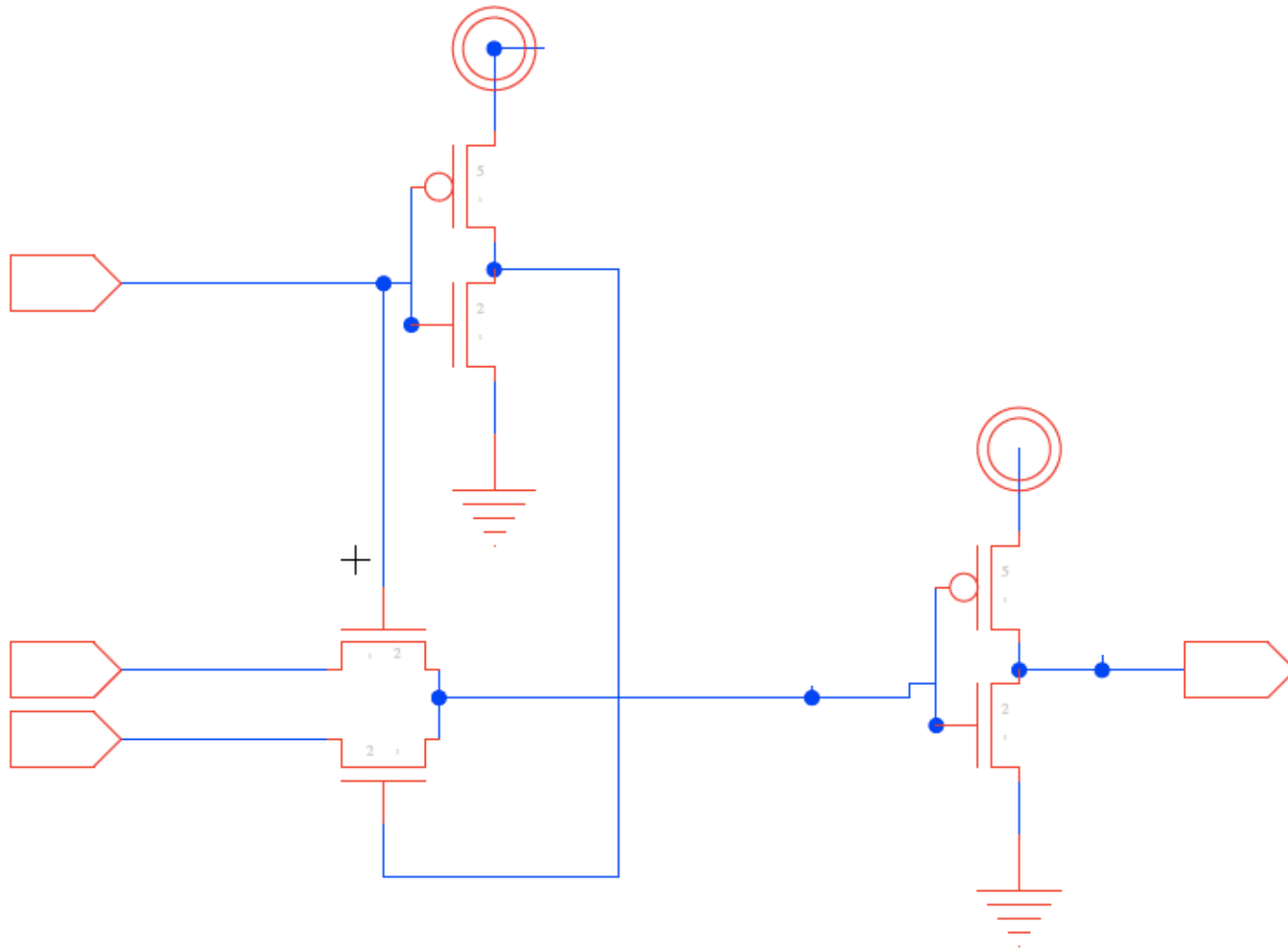



Without level restorer

 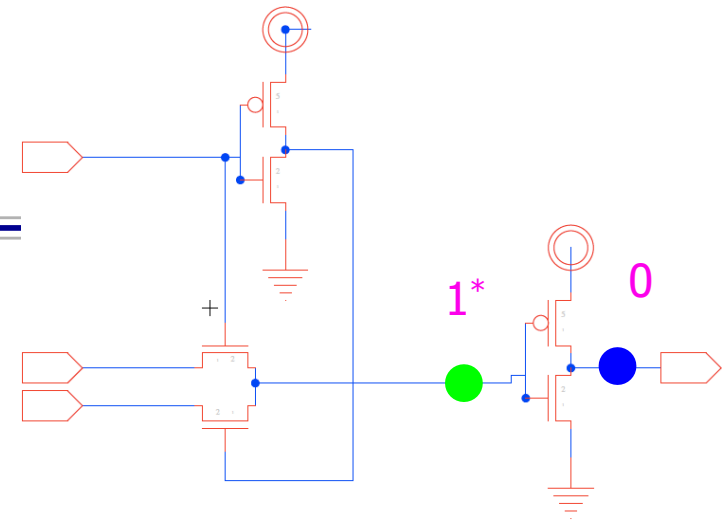

MuxL Level Restorer (“Staticizer”)

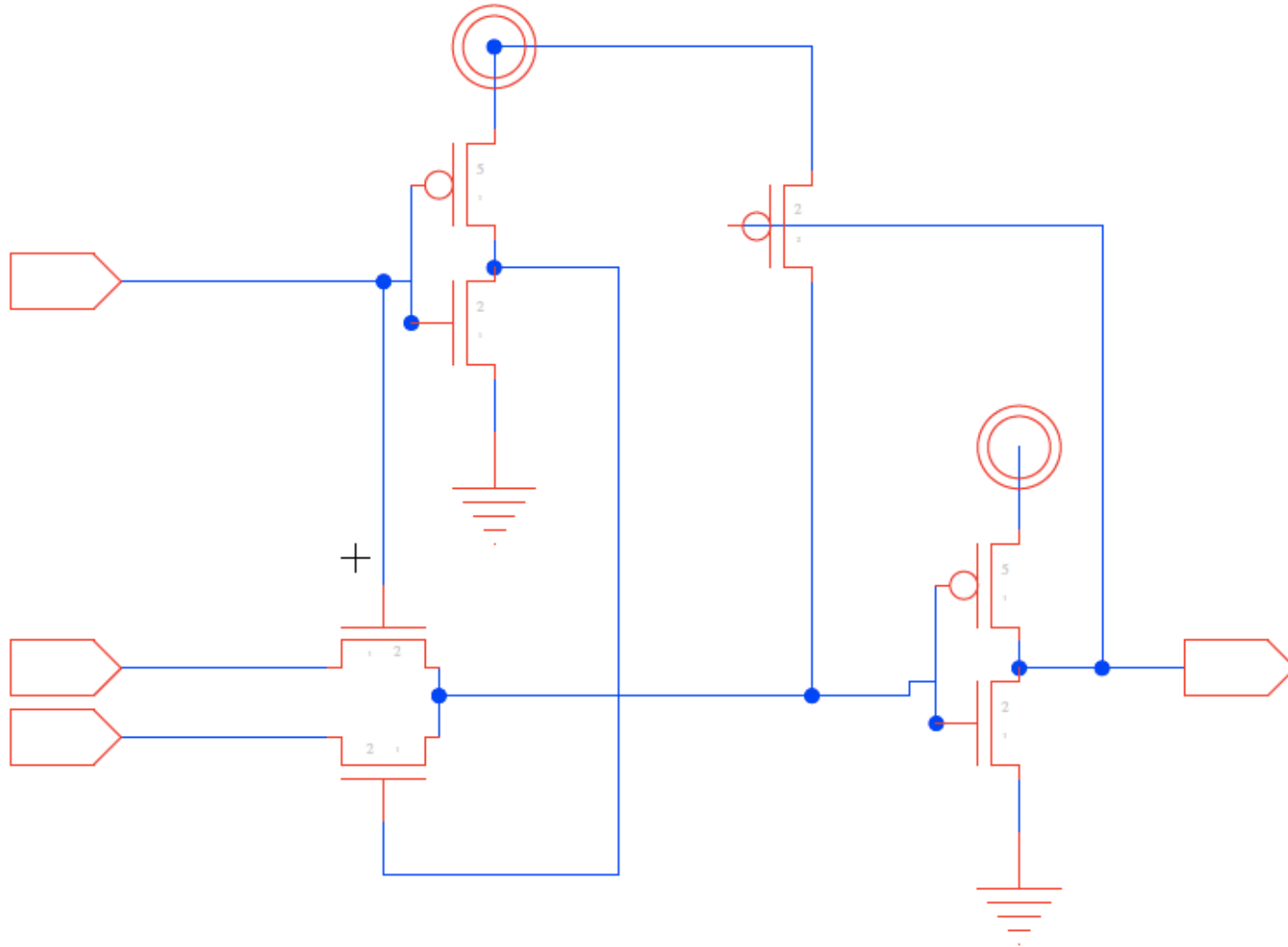

With level restorer

  




Latch (Preclass 4b)

- $\phi=1 \rightarrow \text{Out}=\text{In}$
 - $\phi=0 \rightarrow \text{Out}=\text{Out}$
 - ϕ transitions $1 \rightarrow 0$ Out holds value
-
- How do we build a latch from pass transistors?




Simple Latch

 




Latch with Level Restore

 


What is the difference?

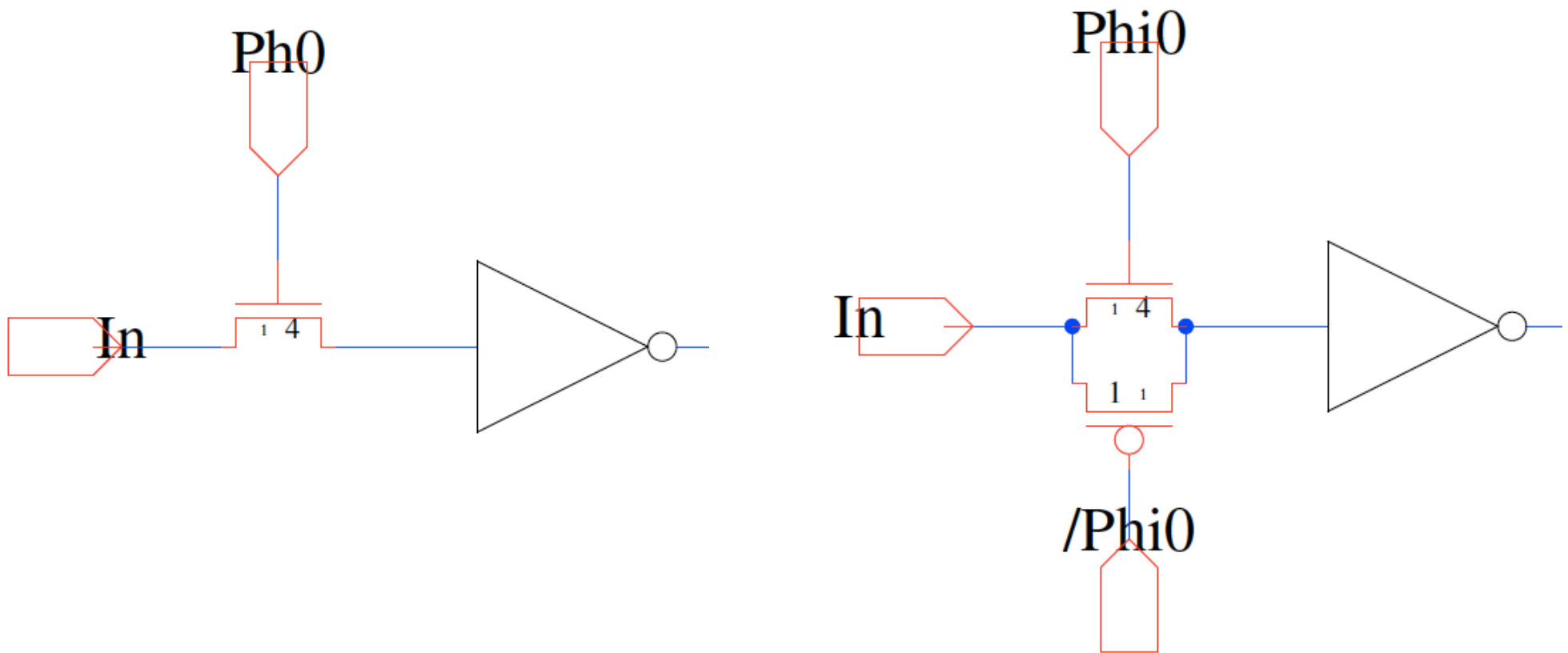

Typical Static Latch

Advantages: VERY ROBUST

- Static
- Full Rail
- Fast (enough)

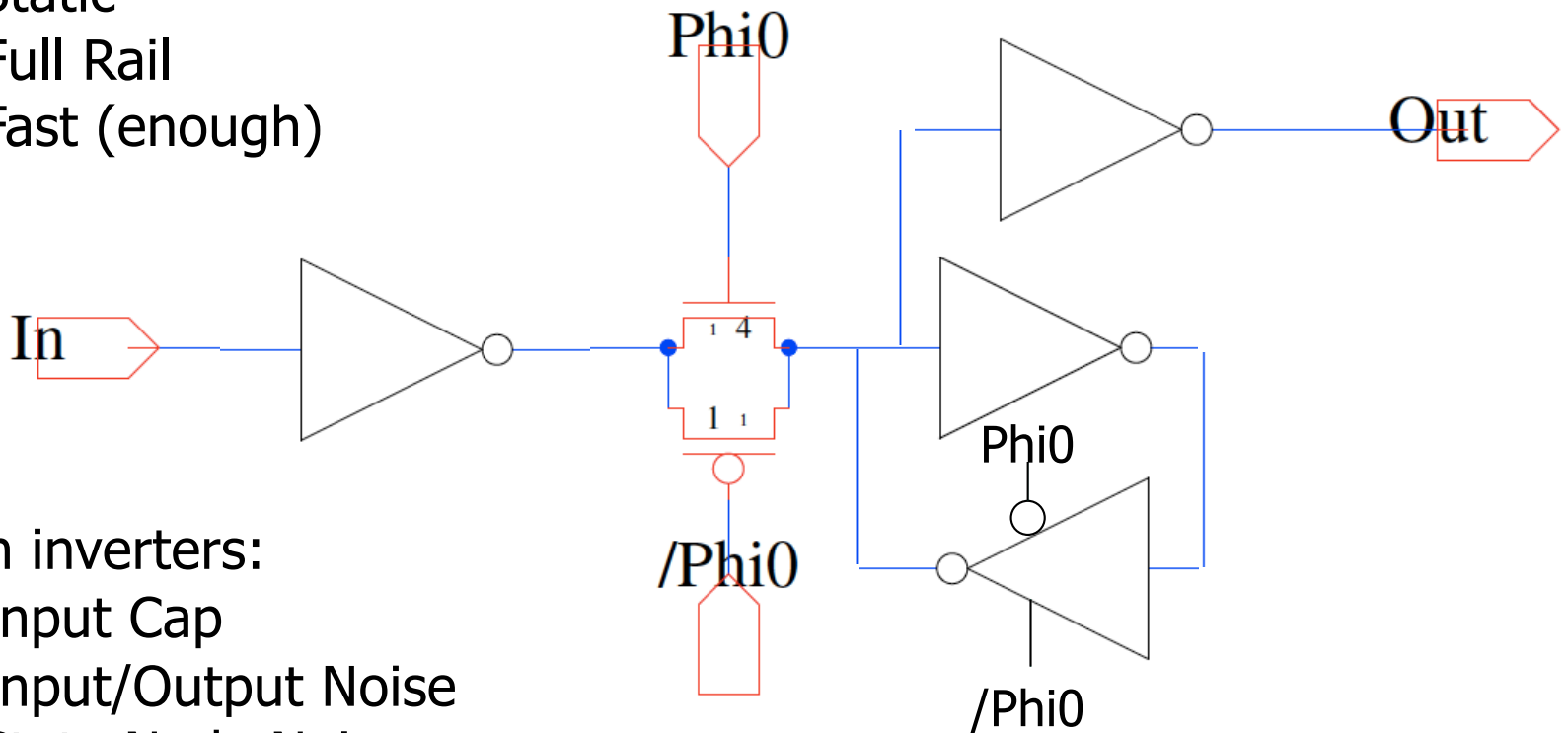

Isolation inverters:


- Input Cap
- Input/Output Noise
- State Node Noise

Disadvantages:

- Large
- High clock loading


Register

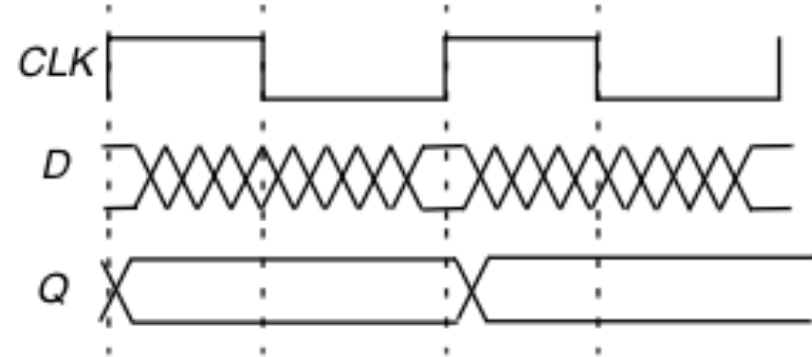- ❑ *Edge-triggered storage element*
- ❑ Positive edge-triggered
 - Input sampled on rising CLK edge
- ❑ Negative edge-triggered
 - Input sampled on falling CLK edge




Latch

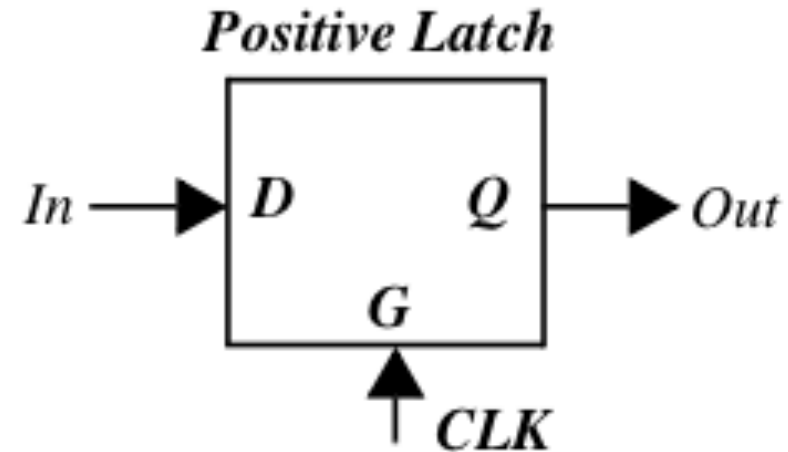- ❑ *Level-sensitive device*
- ❑ Positive Latch
 - Output follows input if CLK high
- ❑ Negative Latch
 - Output follows input if CLK low


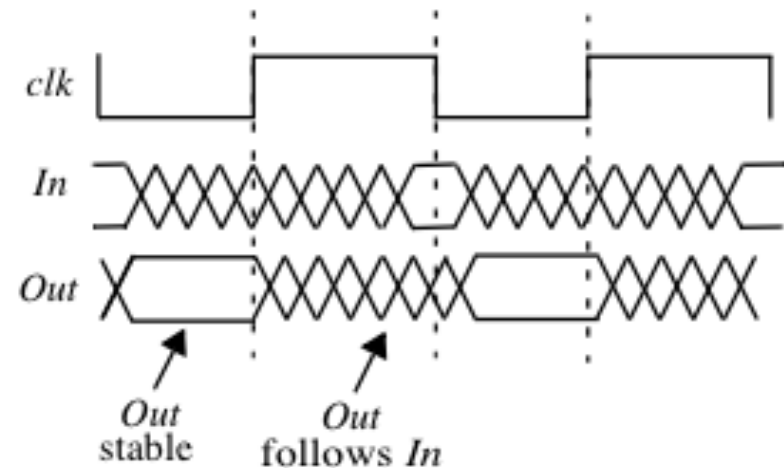
$$Q = \overline{CLK} \cdot Q + CLK \cdot In$$







Shift Register

- How do you make a shift register out of latches?



Positive-Edge Triggered Register

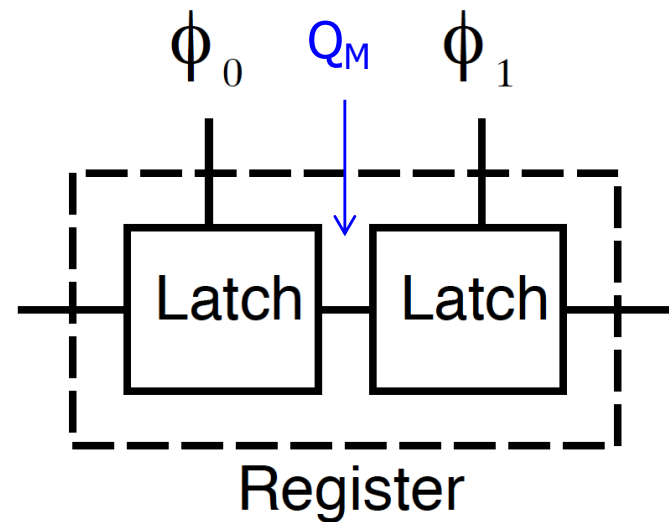 - ❑ Build register from pair of latches
- ❑ What happens when ϕ_0 is high?
- ❑ What happens when ϕ_1 is high?





Positive-Edge Triggered Register

- Build register from pair of latches

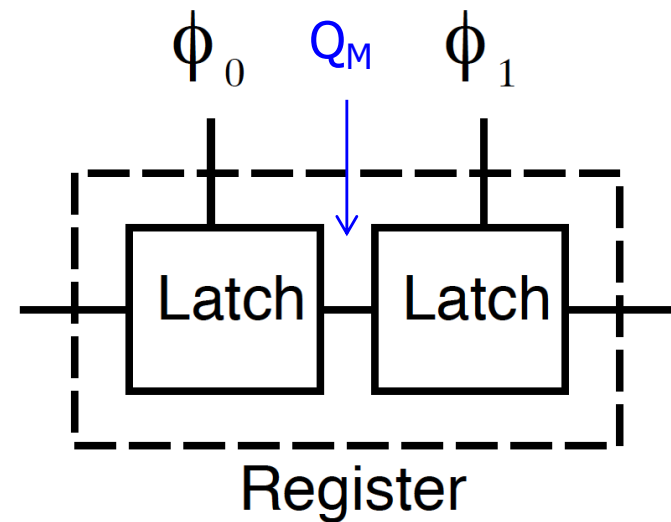 



Positive-Edge Triggered Register

  - ❑ Build register from pair of latches
- ❑ What could go wrong if clocks overlap?




Positive-Edge Triggered Register

  - ❑ Build register from pair of latches
- ❑ Control with non-overlapping clocks




Two Phase Non-Overlapping Clocks

- What timing constraints do we have?

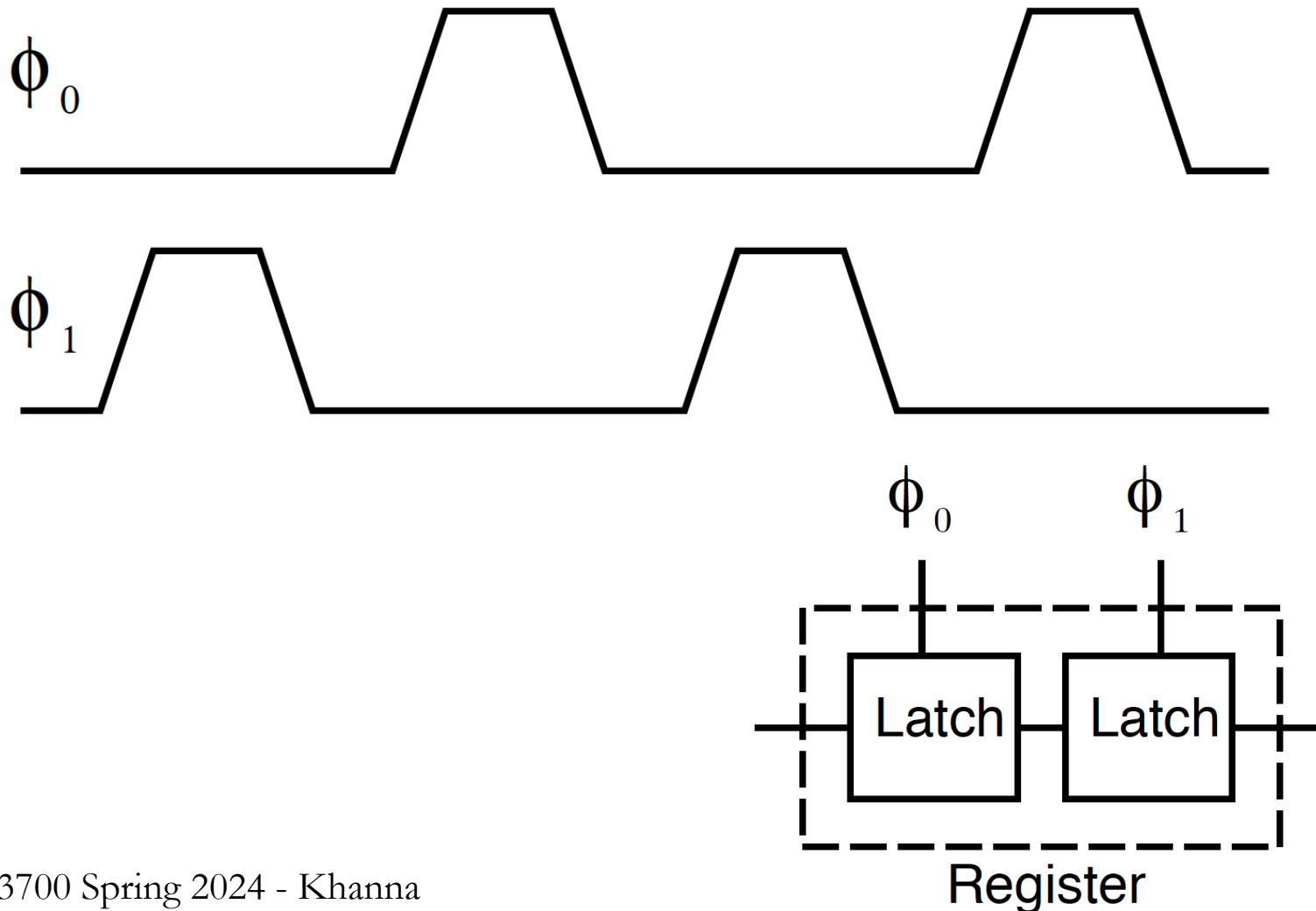


Latch Timing Issues

 - What timing constraints do latches impose?
 - When can ϕ change? (ie. clk switching in relation to data)
 - Setup and hold time
 - How long must ϕ be high?
 - minimum clk period
 - Delay when ϕ is high?




Clocking Discipline

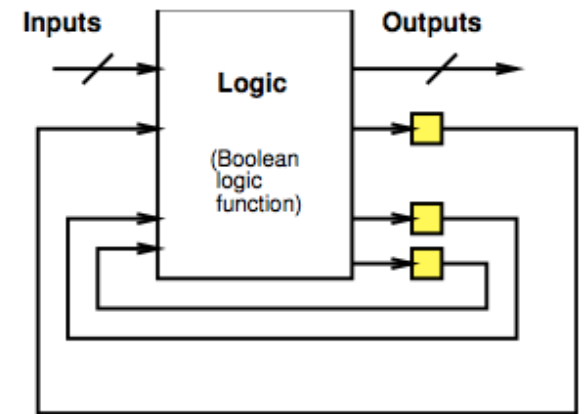- ❑ Follow discipline of combinational logic broken by registers
- ❑ Compute
 - From state elements
 - Through combinational logic
 - To new values for state elements
- ❑ As long as clock cycle long enough,
 - Will get correct behavior



Latch Timing Issues

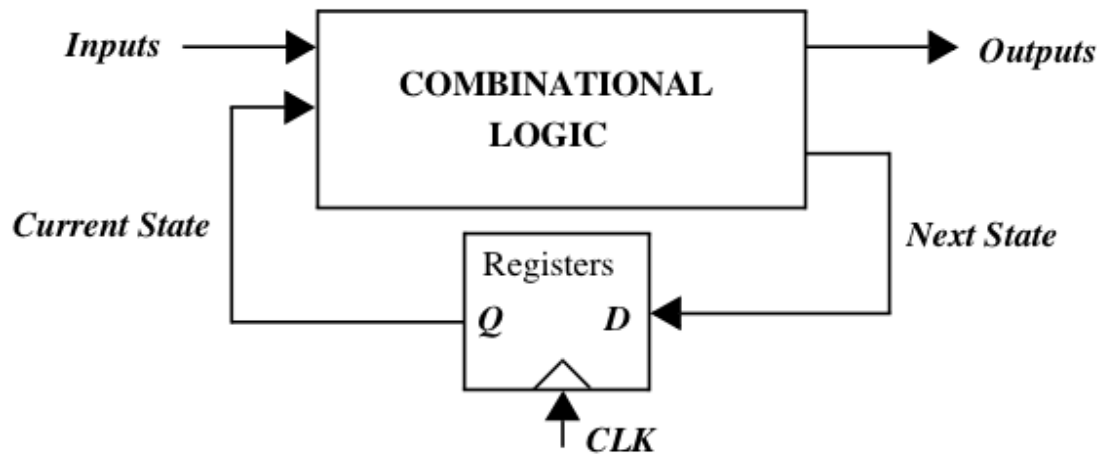


Worst case delays

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$



Minimum delays

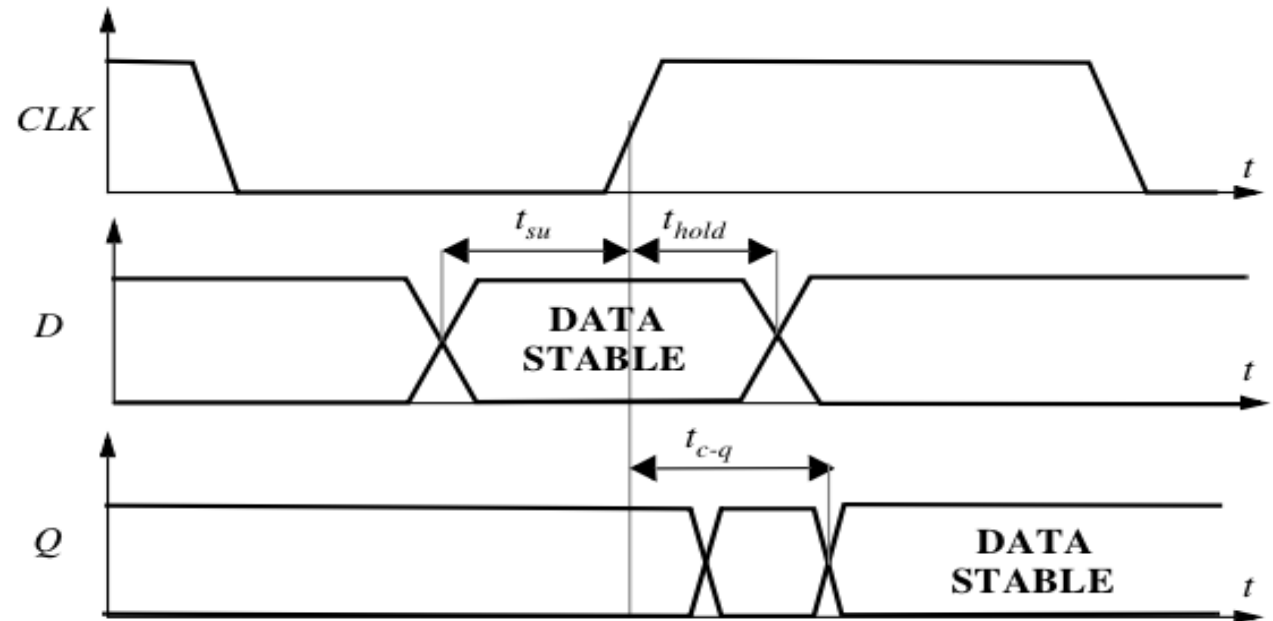

Latch Timing Issues

- ❑ t_{su} = time data (D) must be valid before CLK edge
- ❑ t_{plogic} = worst case propagation delay of logic
- ❑ t_{c-p} = worst case propagation delay of latch


$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

 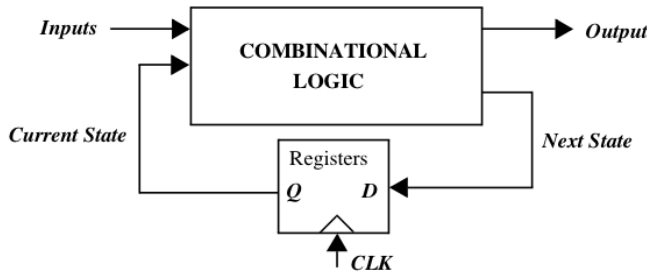

Latch Timing Issues

- ❑ $t_{cdregister}$ = minimum propagation delay of latch
- ❑ $t_{cdlogic}$ = minimum propagation delay of logic
- ❑ t_{hold} = time data (D) must stay valid after CLK edge

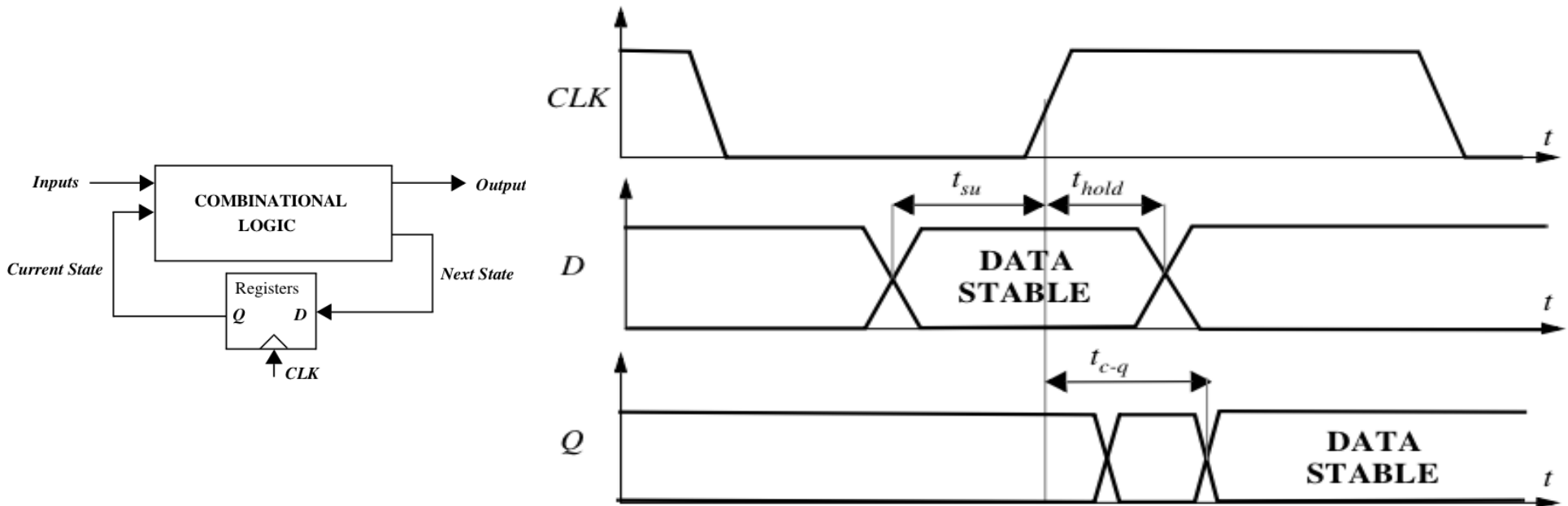
$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$



Timing Example (Preclass5)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

 


$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

Timing Example (Preclass5)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

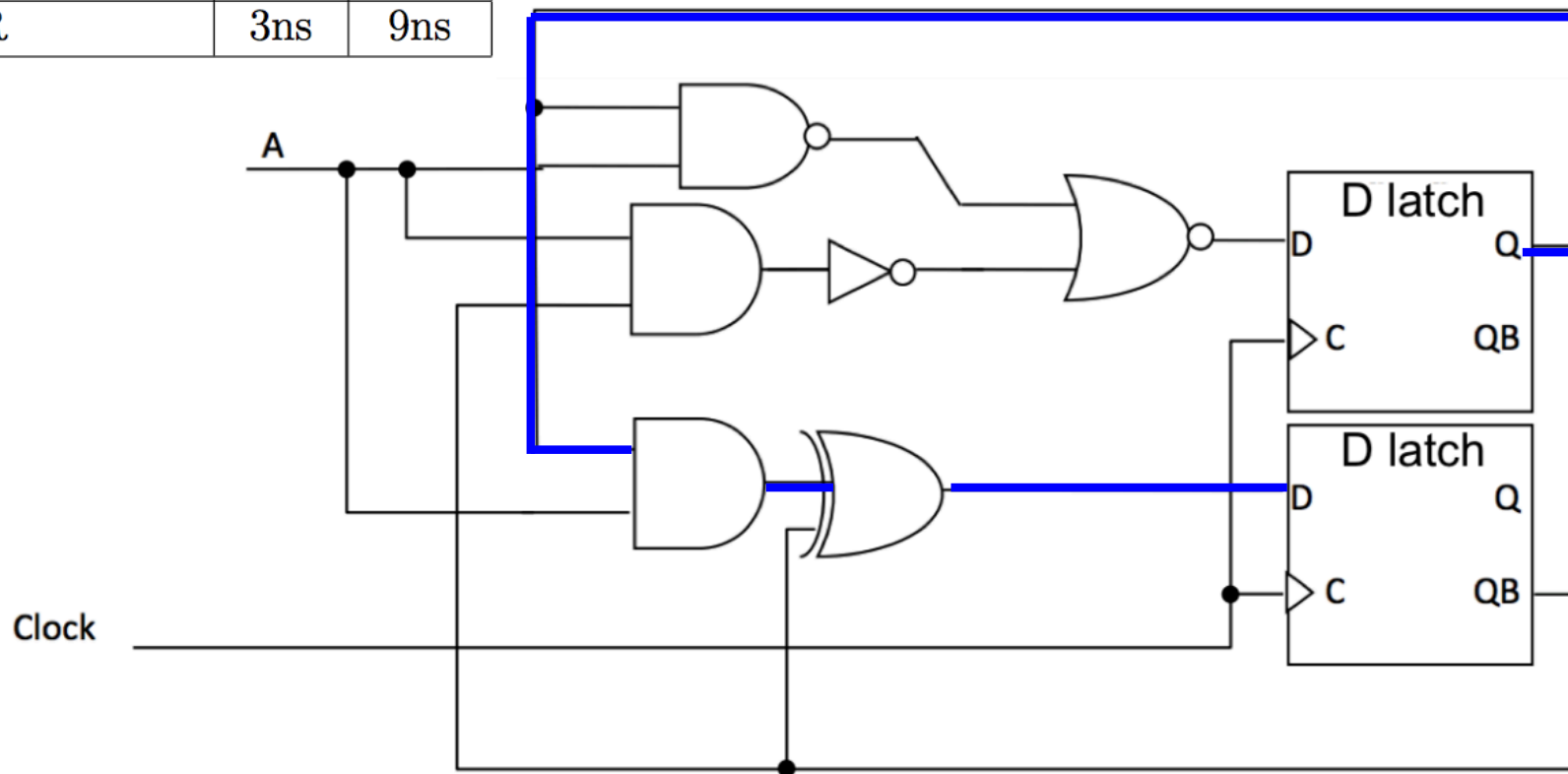


$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

Timing Example (Preclass5)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

 


$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

Timing Example (Preclass5)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

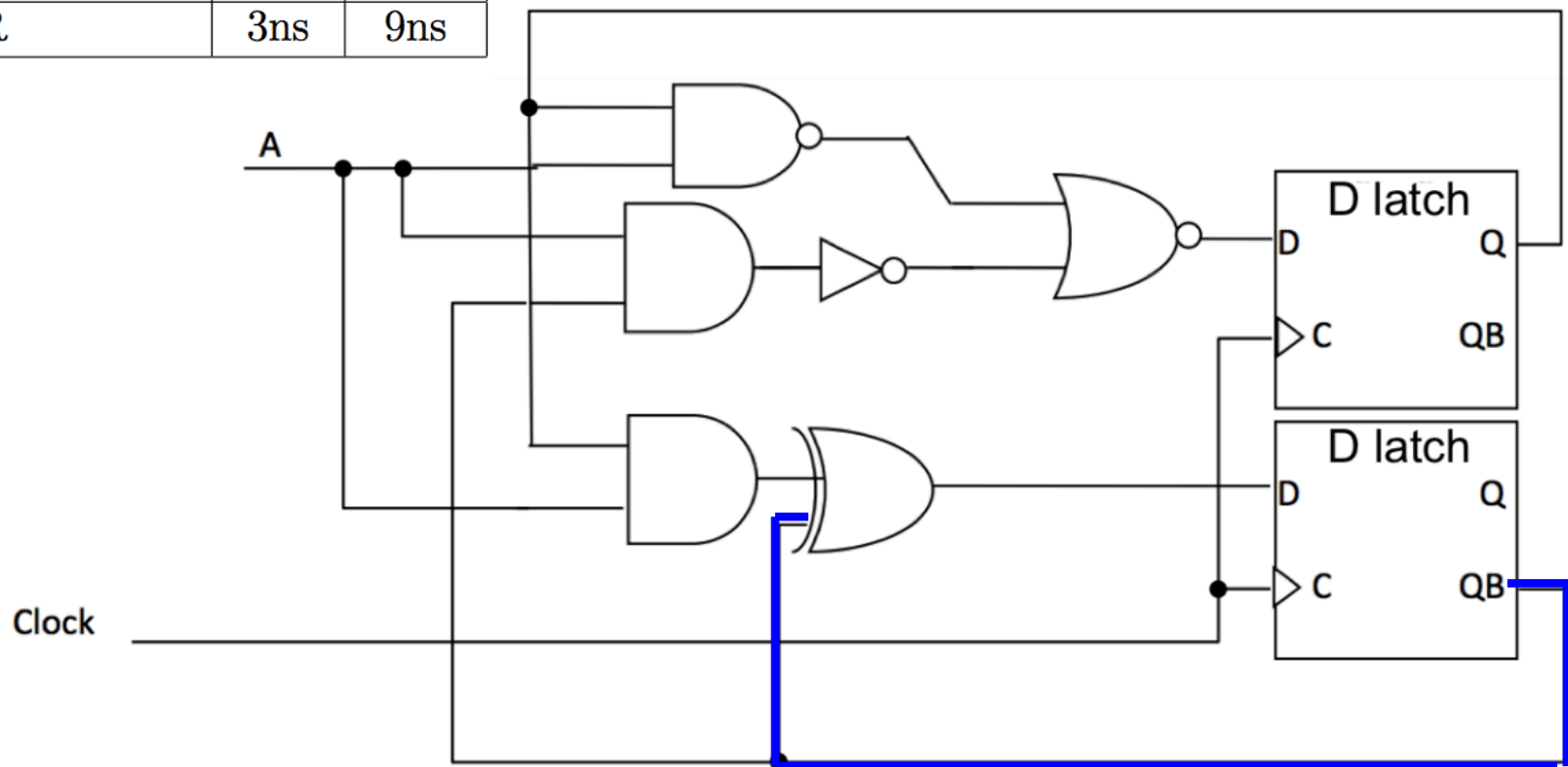


$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

Timing Example (Preclass5)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

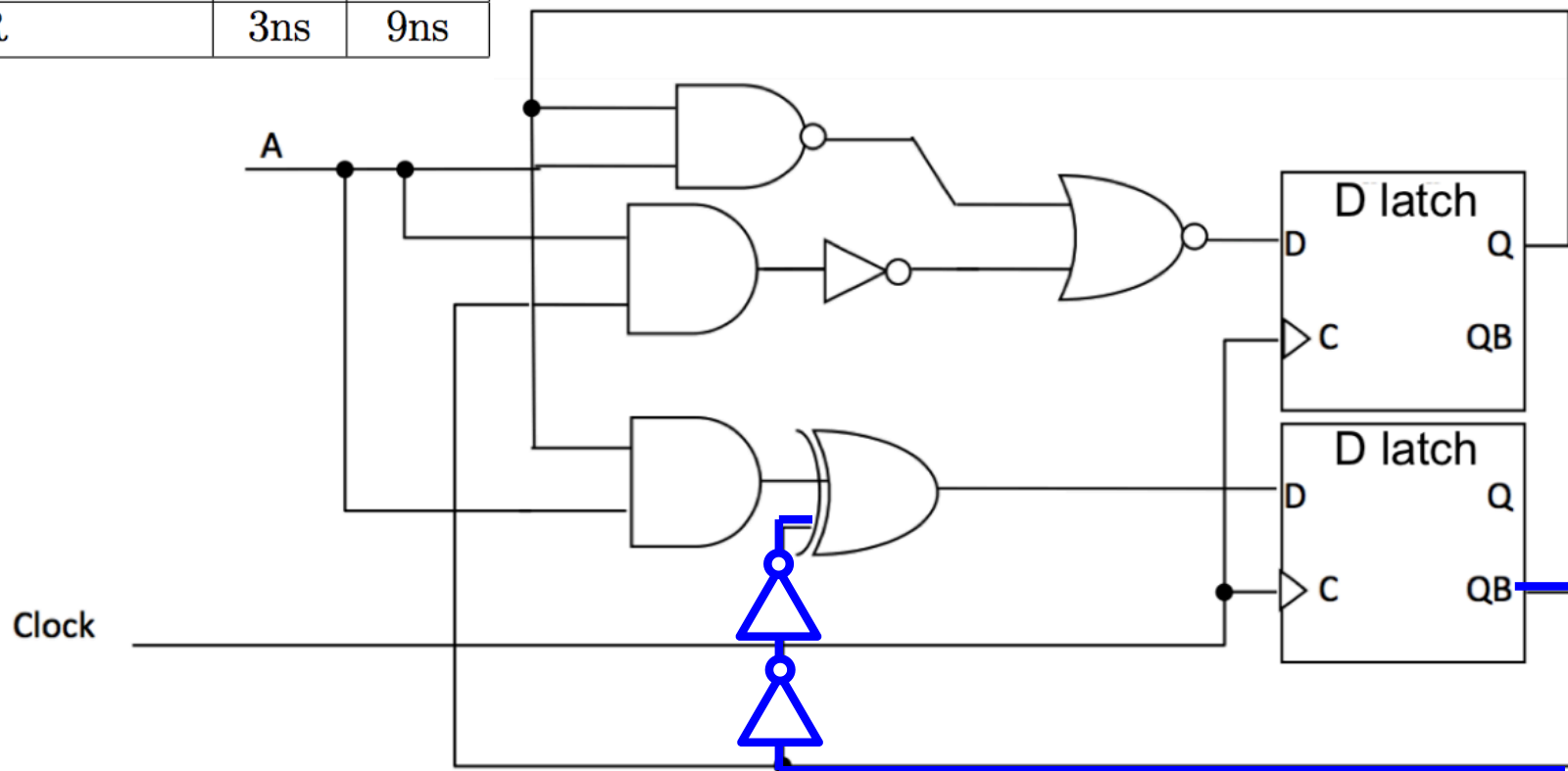

$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$



Ideas

- ❑ Synchronize circuits
 - to external events
 - disciplined reuse of circuitry
- ❑ Leads to clocked circuit discipline
 - Uses state holding element
 - Prevents
 - Timing assumptions
 - (More) complex reasoning about all possible timings



Admin

- ❑ Wednesday 4/3 Midterm 2 (this week)
 - During class in Moore 216
 - Lectures 1-14
 - Closed note, calculator allowed
 - All old exams online
 - 2010-2021
 - TA review session
 - 4/1 7-9pm in Towne 307 (tonight)
- ❑ HW6 release 4/3 (after Midterm 2)
 - Can do all of it now
 - Due **Wednesday 4/10**



Acknowledgement

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Jing Li (University of Pennsylvania)