
 


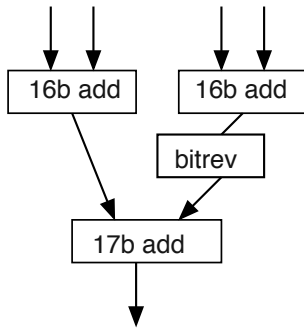Consider a 16b (and 17b) ripple-carry adder built out of 1-bit adder slices. The delay from the three inputs of the 1-bit adder to the two outputs is T_{bit} .



1. What is the worst-case delay through the 16b adder?
2. After a change in an input, what is the **shortest** amount of time before an output bit changes?
3. Consider the somewhat unusual 4-input adder tree shown. Assume negligible ($\ll T_{bit}$) delay in bitrev. (bitrev: $Out[i]=In[17-i]$)



What happens if we provide new set of inputs to this circuit every $20T_{bit}$?

4. How might we implement a latch that behaves as follows:

```


if ( $\phi==1$ )
    Out= $\neg$ In
else
    Out=Out
    
```

- (a) Using combinational logic (at gate level. Hint: Think about a mux...)?

- (b) Using Pass transistors?

| | Min | Max |
|----------|-----|-----|
| OR/AND | 3ns | 5ns |
| NOR/NAND | 2ns | 4ns |
| NOT | 1ns | 2ns |
| XOR | 3ns | 9ns |

| Latch: | | Min | Max |
|--------|-------------------|-----|-----|
| | <i>Clock to Q</i> | 2ns | 3ns |
| | <i>Setup time</i> | 7ns | |
| | <i>Hold time</i> | 6ns | |

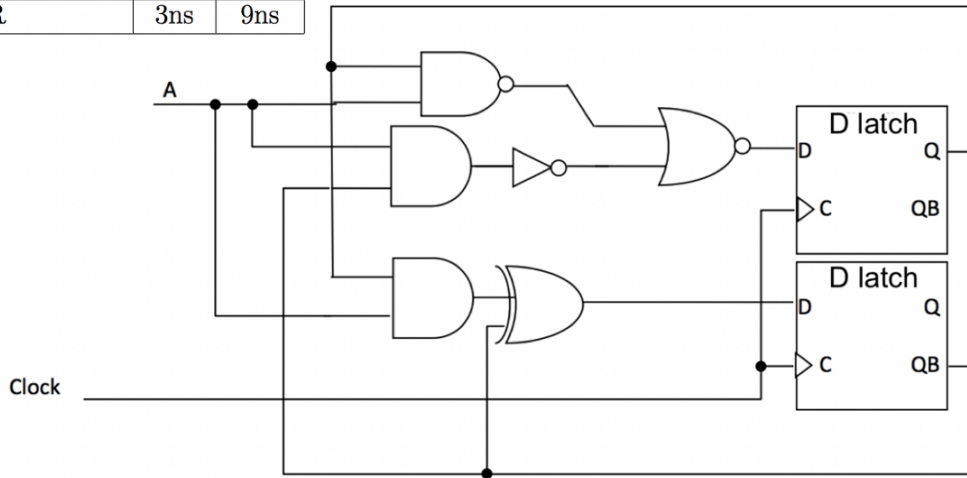

5. Timing Constraints:

$$T \geq t_{c-q} + t_{plogic} + t_{su} \quad (1)$$

$$t_{cdregister} + t_{cdlogic} \geq t_{hold} \quad (2)$$

(a) What is the minimum clock period, T , that ensures correct operation?

(b) Add inverter pairs to the design above such that there are no hold time variations.