

ESE3700: Circuit-Level Modeling, Design and Optimization for Digital Systems

Lec 18: April 10, 2024

Memory Overview and RAM Core





Today

- Memory
 - Classification
 - Architecture
 - RAM Core
 - Periphery (next week)
 - Serial Access Memories (next week)

- Project 2 is on this

Memory Overview






Semiconductor Memory Classification

RWM		NVRWM	ROM
Random Access	Non-Random Access	EPROM E ² PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		




Memory Architecture: Core

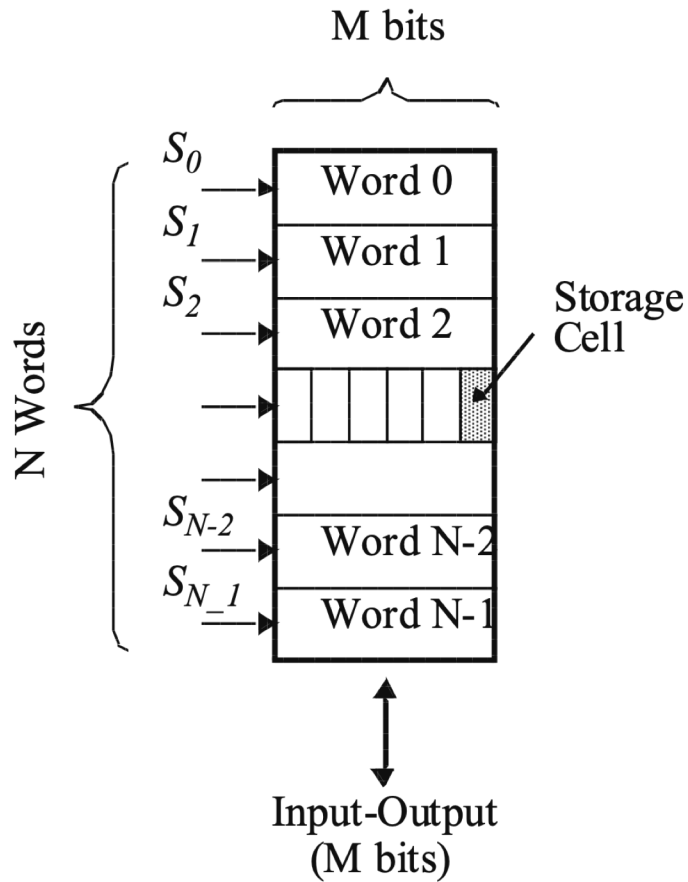

N words \Rightarrow N select signals
Too many select signals

Memory Architecture: Decoders

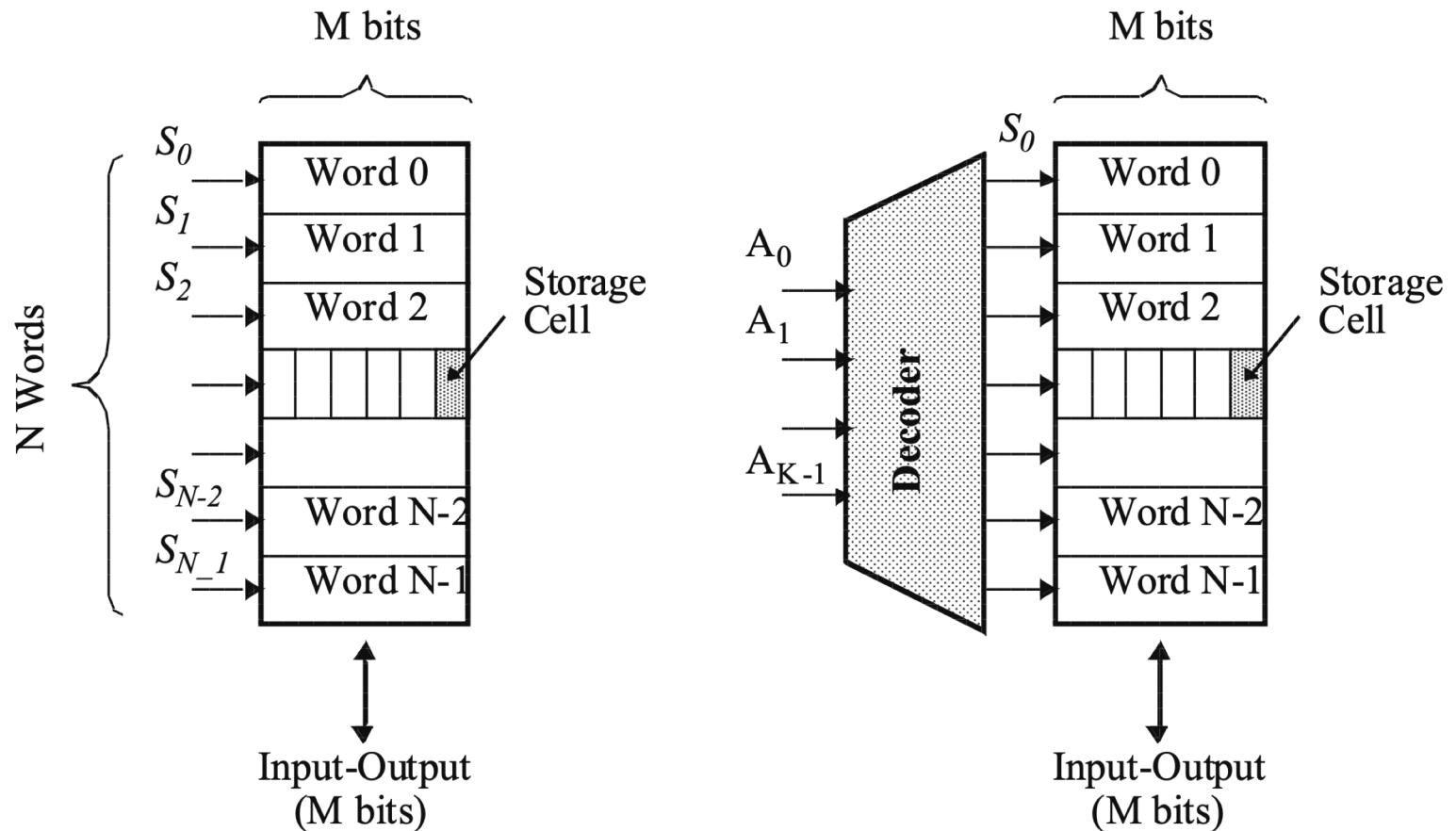


N words \Rightarrow N select signals
Too many select signals

Decoder reduces # of select signals
 $K = \log_2 N$



Array-Structured Memory Architecture

 Problem: ASPECT RATIO or HEIGHT \gg WIDTH



Latches/Register – Can Store a State

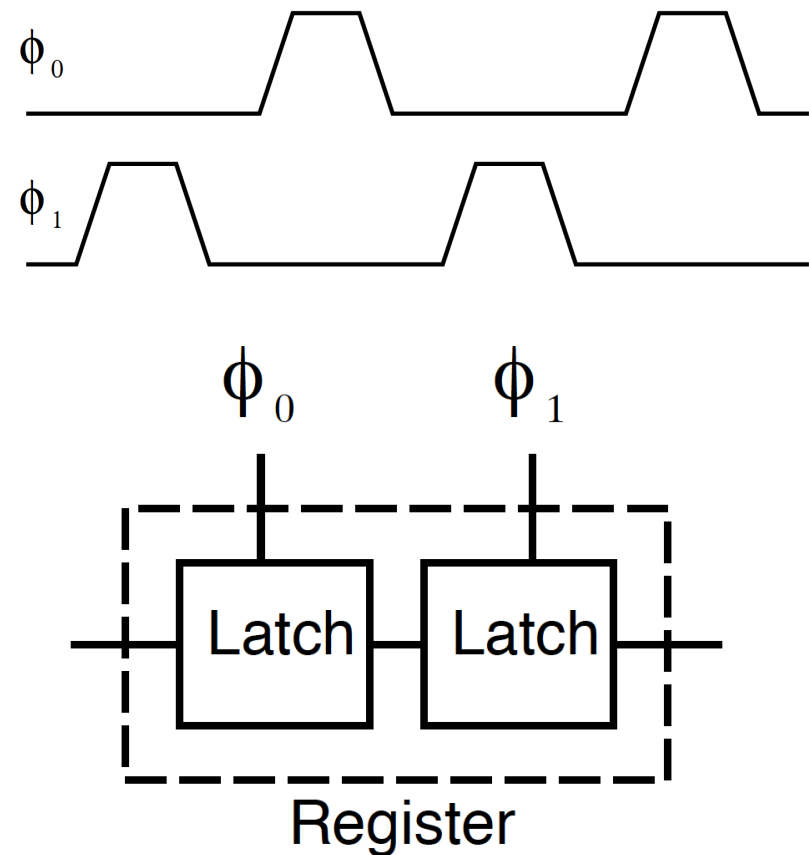 - ❑ Build register from pair of latches
- ❑ Control with non-overlapping clocks




ROM Memories






MOS NOR ROM

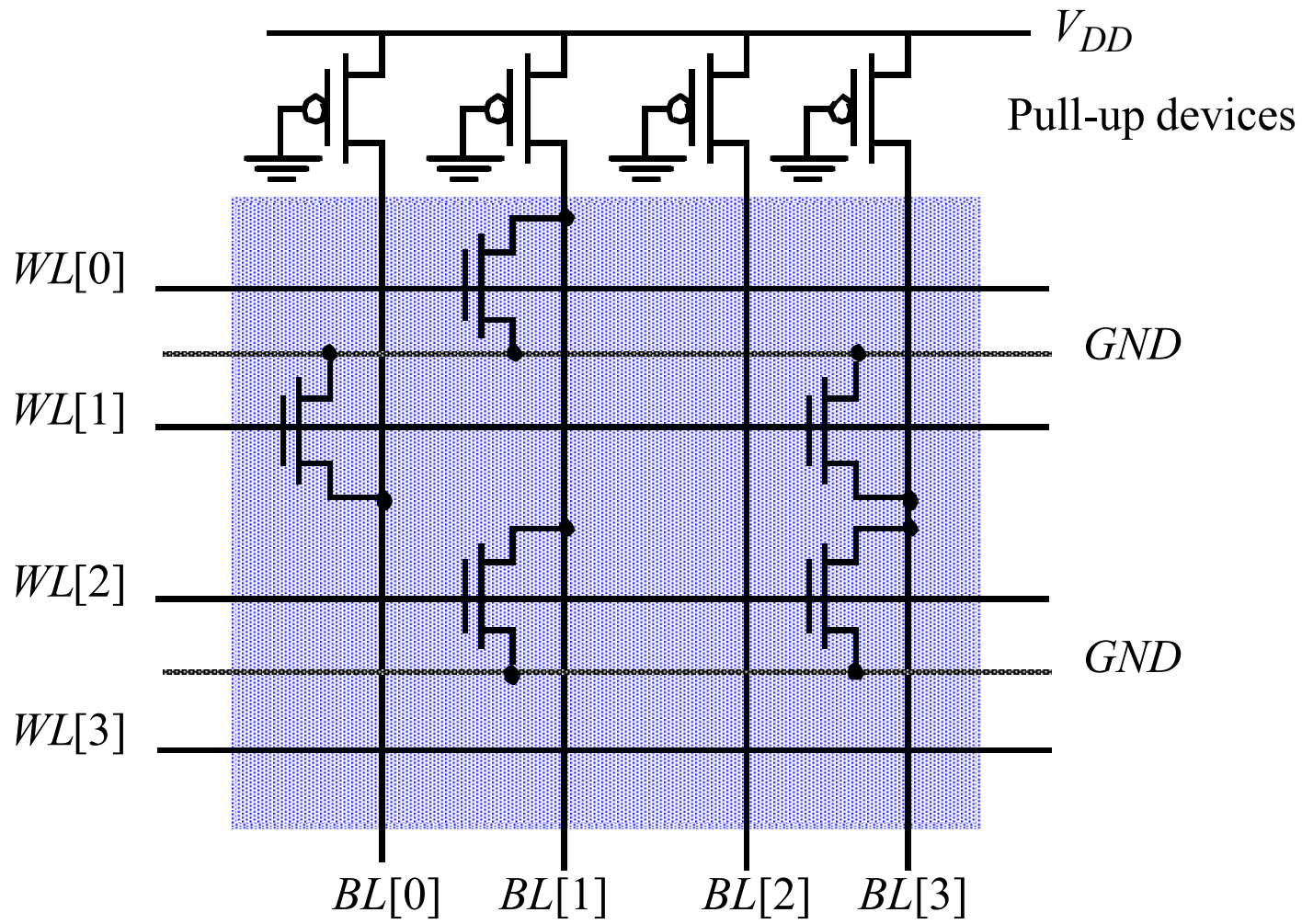




MOS NOR ROM

 




MOS NOR ROM

 




MOS NOR ROM

 




MOS NOR ROM

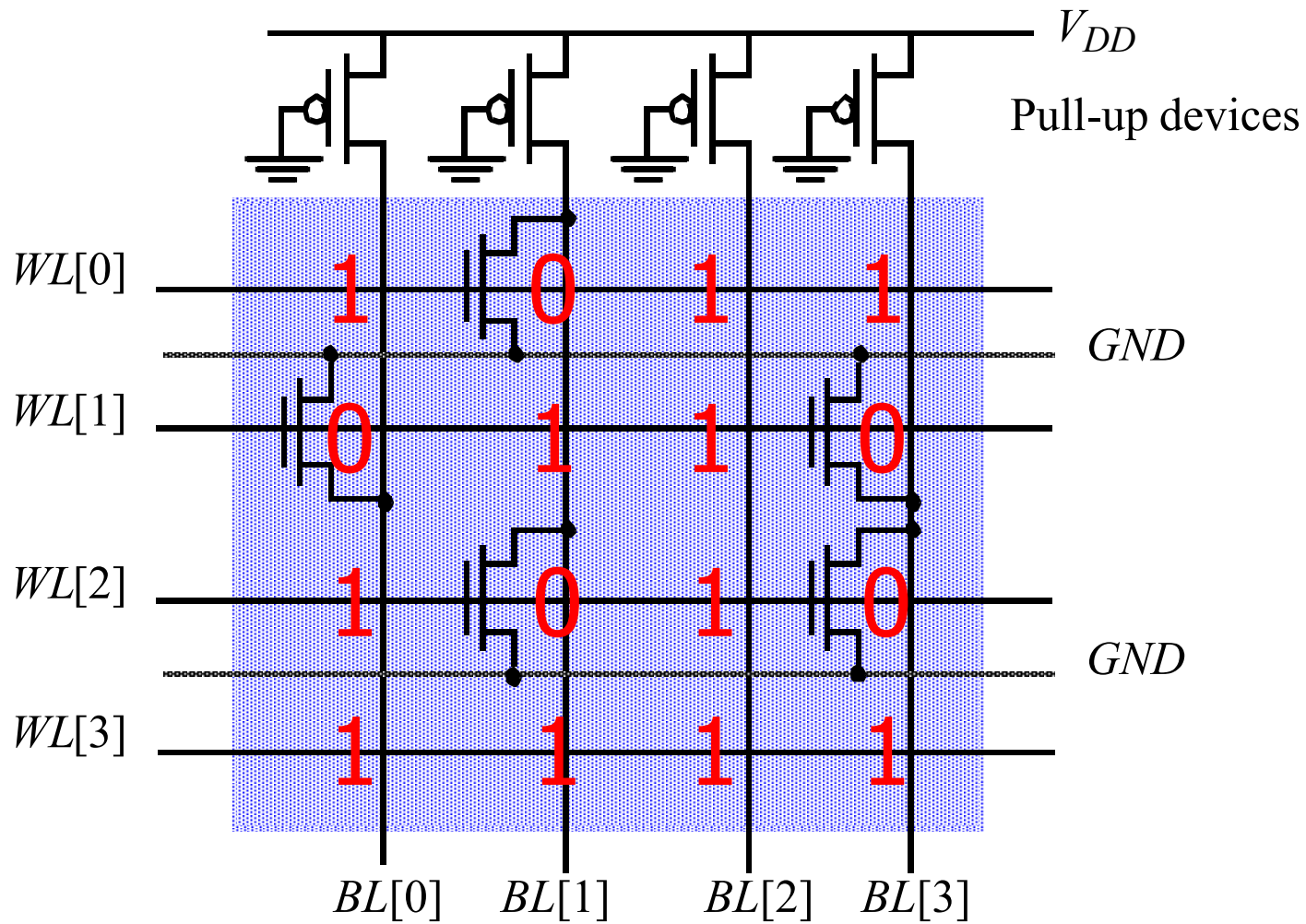




MOS NAND ROM

 

All word lines high by default with exception of selected row




MOS NAND ROM

 

All word lines high by default with exception of selected row




MOS NAND ROM

 

All word lines high by default with exception of selected row

Array-Structured Memory Architecture

 Problem: ASPECT RATIO or HEIGHT \gg WIDTH



Memory Periphery






Periphery

- ❑ Decoders
- ❑ Column Circuitry
 - Bit-line Conditioning
 - Sense Amplifiers
 - Input/Output Buffers
- ❑ Control/Timing Circuitry


Array Architecture

 - ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used




Array Architecture

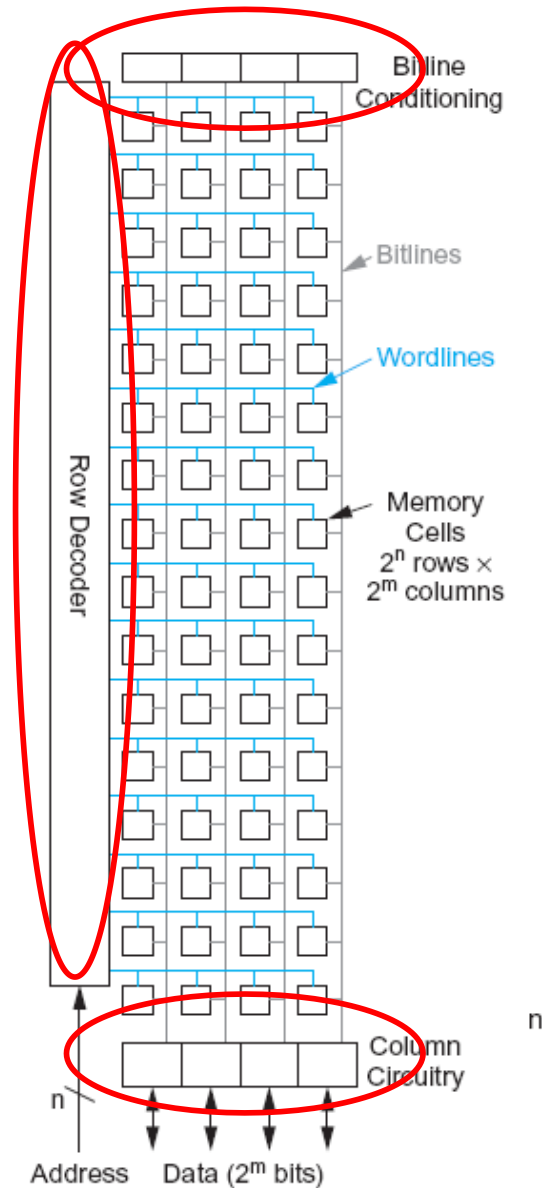- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used



6-transistor CMOS SRAM Cell

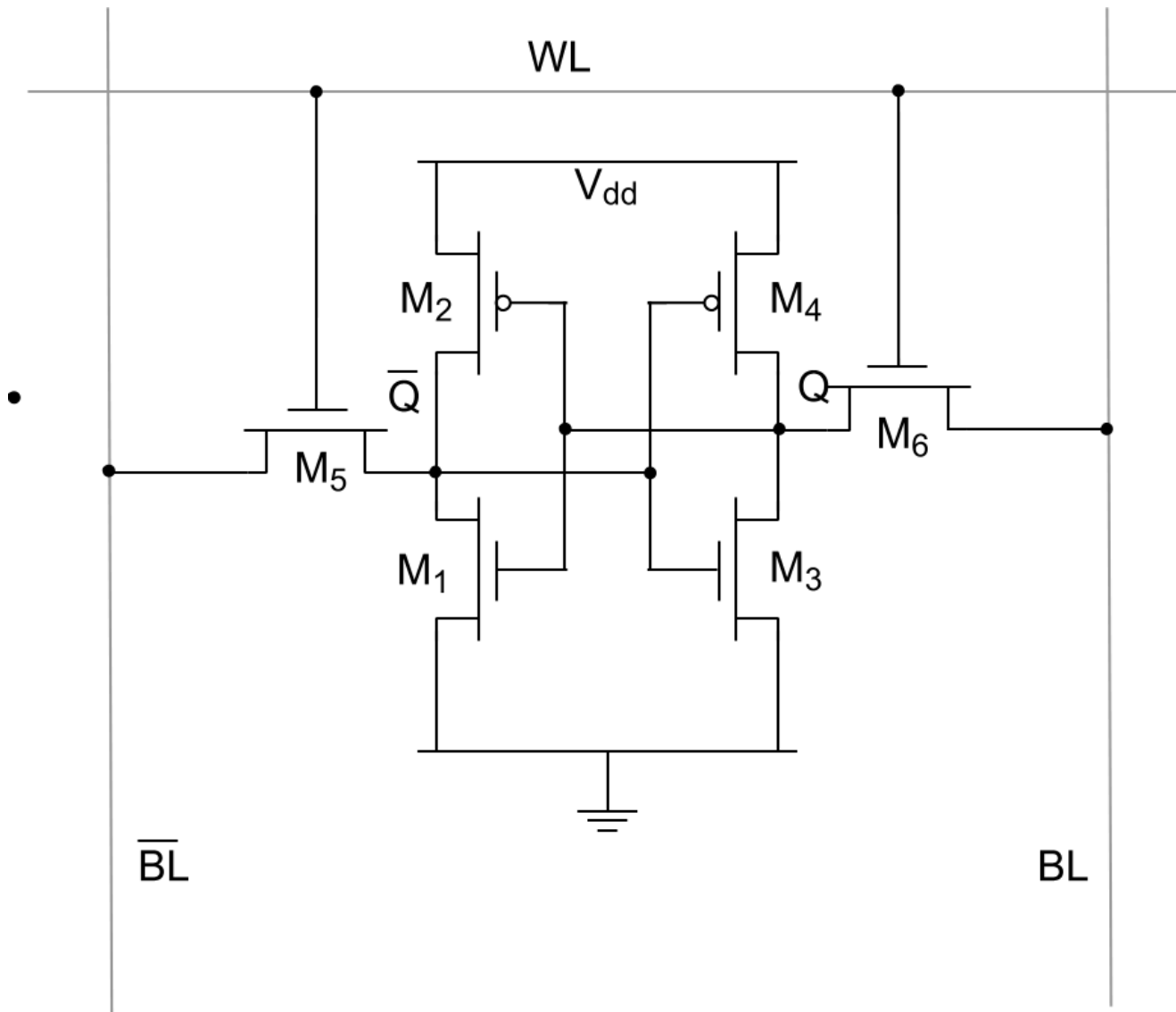


6-transistor CMOS SRAM Cell (preclass 1)


Assume 1 is stored
($Q=1$)

Read Operation:

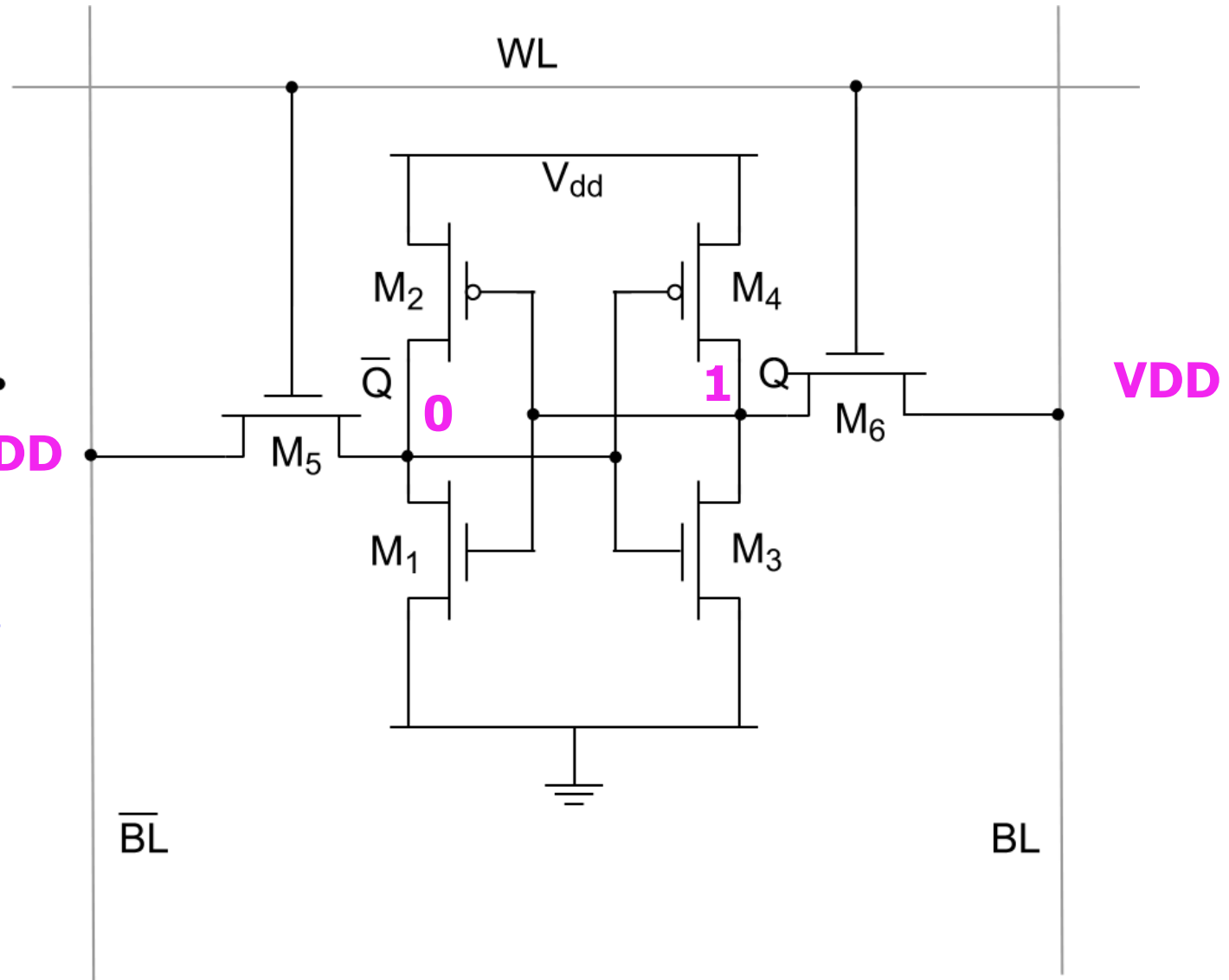- First bitlines get precharged high (VDD)
- Then wordline goes high (VDD)
 - Precharge disconnected first!




CMOS SRAM Analysis (Read)

 

$$k_{n,M5} (V_{DD} - \Delta V - V_{Tn})^2 = k_{n,M1} \left((V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$


CMOS SRAM Analysis (Read)

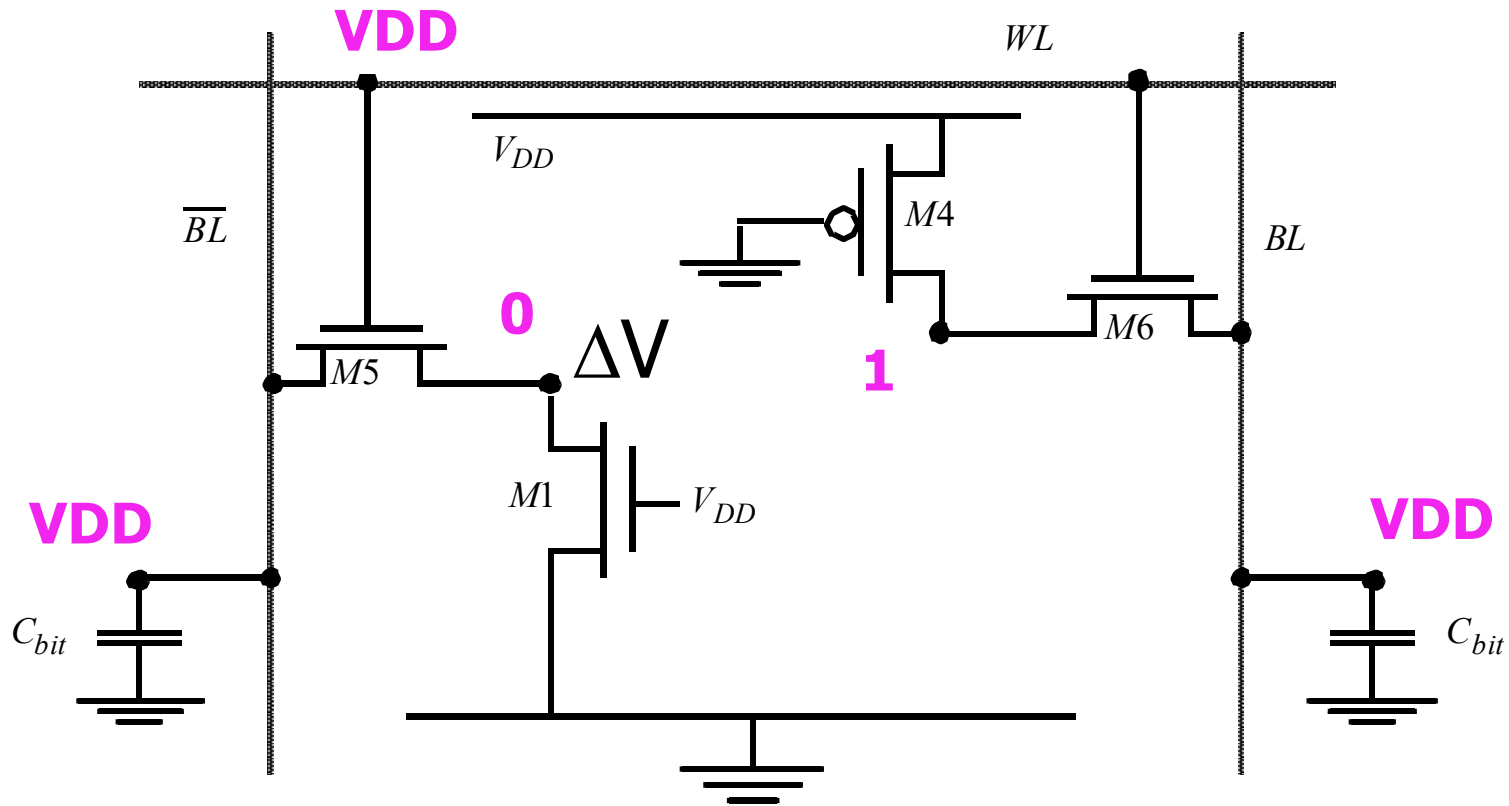

$$\frac{k_{n,M1}}{k_{n,M5}} = \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_5} = \frac{(V_{DD} - \Delta V - V_{Tn})^2}{(V_{DD} - V_{Tn})\Delta V - \frac{\Delta V^2}{2}}$$

Constraint on ΔV ?


CMOS SRAM Analysis (Read)

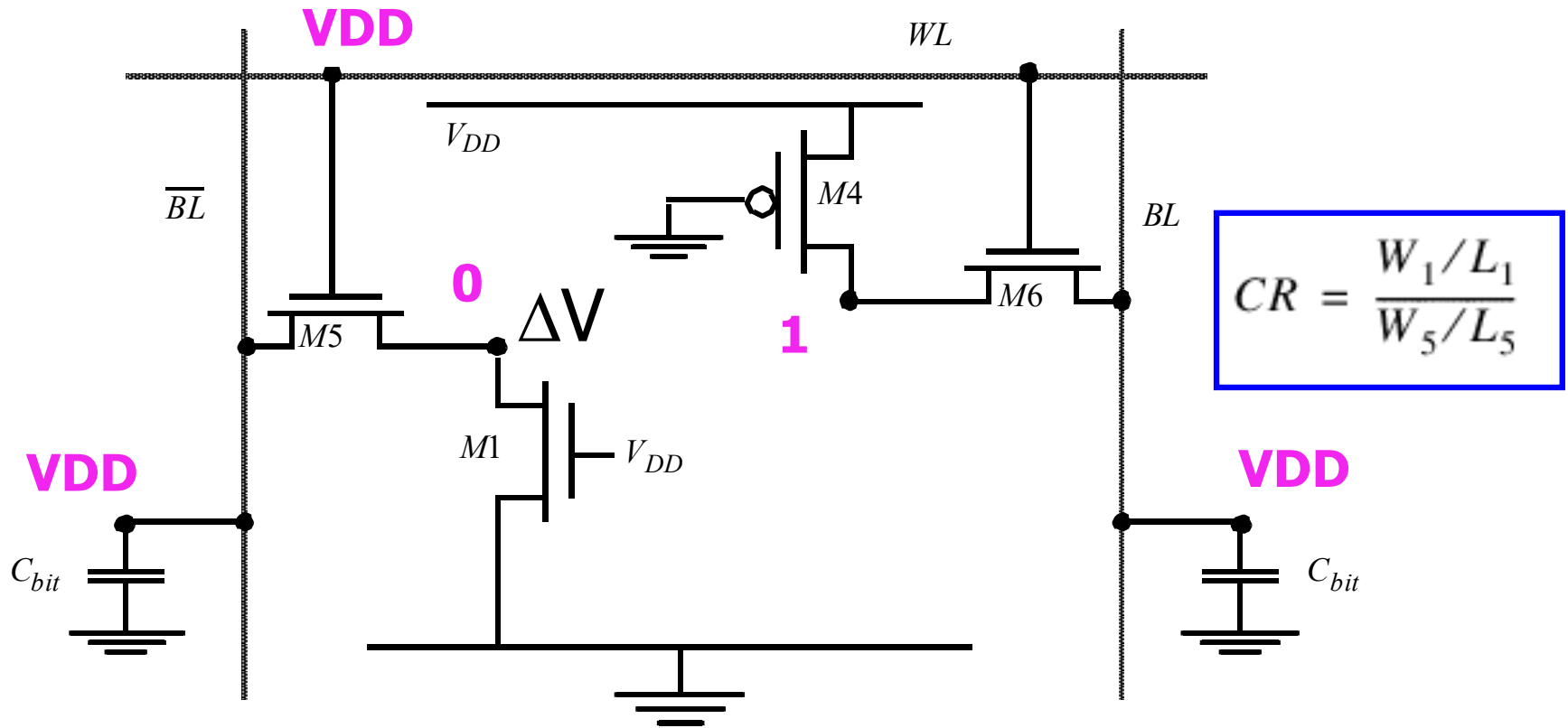

$$\frac{k_{n,M1}}{k_{n,M5}} = \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_5} = \frac{(V_{DD} - \Delta V - V_{Tn})^2}{(V_{DD} - V_{Tn})\Delta V - \frac{\Delta V^2}{2}} \quad \xrightarrow{\Delta V = V_{Tn}} \quad \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_5} = \frac{(V_{DD} - 2V_{Tn})^2}{(V_{DD} - 1.5V_{Tn})V_{Tn}}$$





CMOS SRAM Analysis (Read)

 

$$CR = \frac{W_1/L_1}{W_5/L_5}$$

SRAM Read

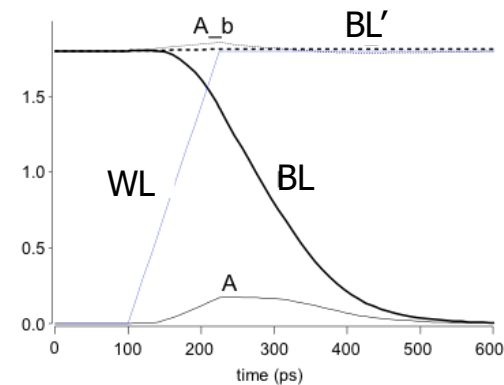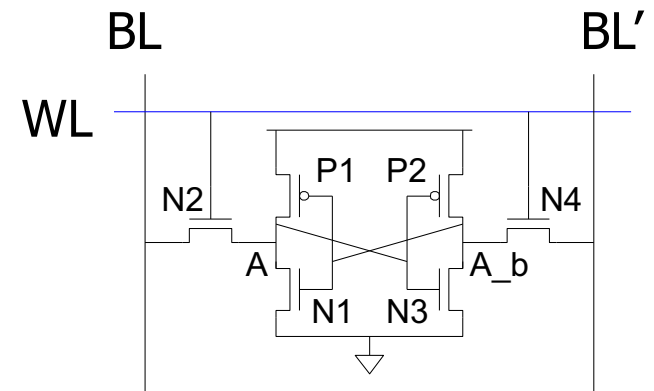- ❑ Precharge both bitlines high
- ❑ Then turn on wordline, WL
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex: $A = 0, A_b = 1$
 - BL discharges, BL' stays high
 - But A bumps up slightly
- ❑ *Read stability*
 - A must not flip
 - $N1 > N2$




6-transistor CMOS SRAM Cell (preclass 2)


Assume 1 is stored
($Q=1$)

Write Operation:

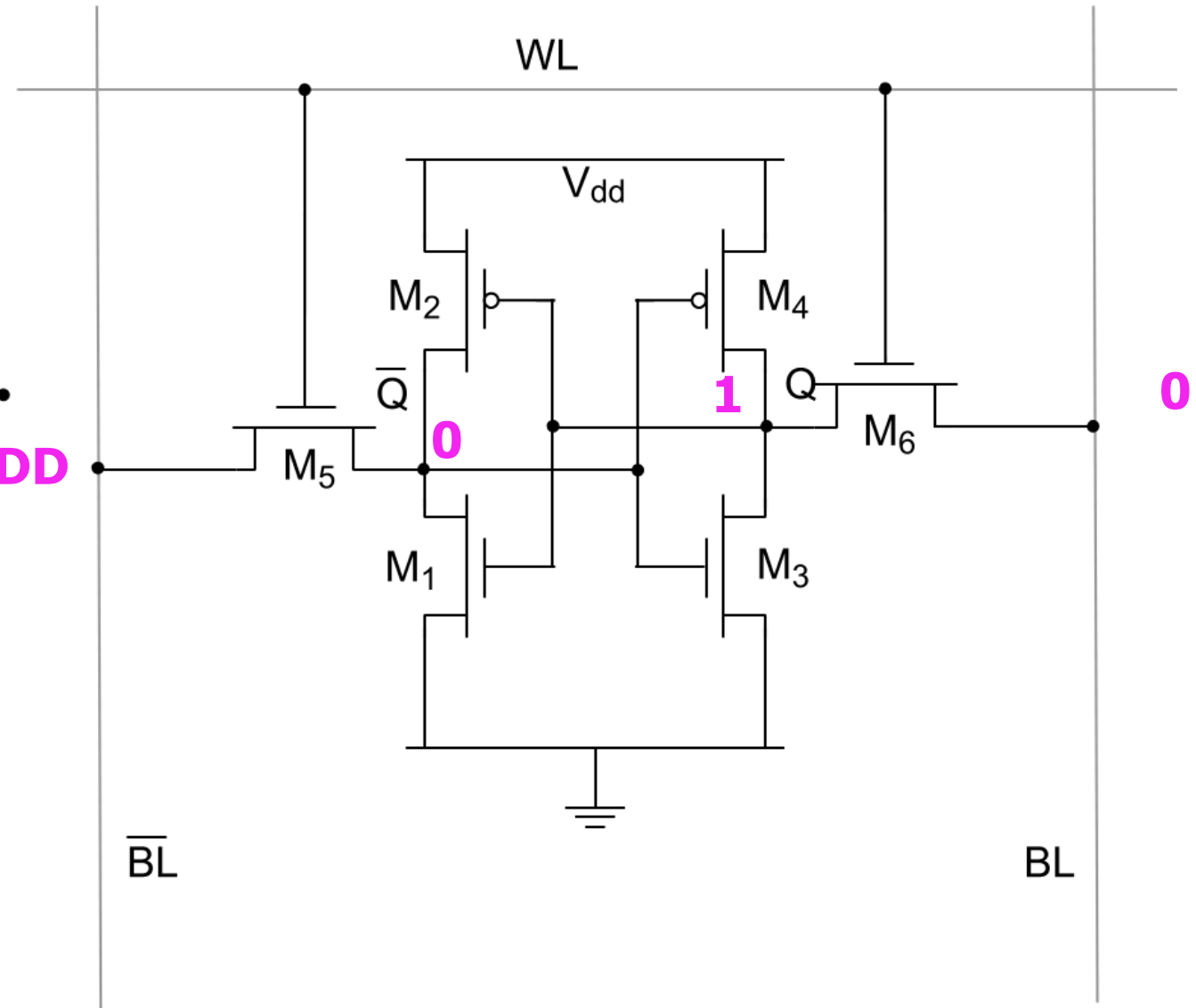- Want to write a 0
- First drive bitlines with input data
- Then wordline goes high (V_{dd})
 - Still driving bitlines




CMOS SRAM Analysis (Write)

 

$$k_{p,M4} (V_{DD} - |V_{Tp}|)^2 = k_{n,M6} \left((V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2} \right)$$

CMOS SRAM Analysis (Write)

 

$$PR = \frac{W_4/L_4}{W_6/L_6}$$


$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$

$$V_Q = V_{Tn}$$

$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_{Tn} - \frac{V_{Tn}^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$





CMOS SRAM Analysis (Write)

 

$$PR = \frac{W_4/L_4}{W_6/L_6}$$

SRAM Write

 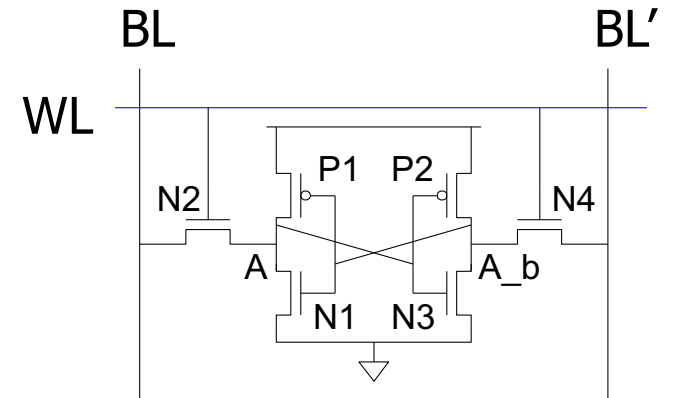- ❑ Drive one bitline high, the other low
 - Depending on write data
- ❑ Then turn on wordline, WL
- ❑ Bitlines overpower cell with new value
- ❑ Ex: $A = 0$, $A_b = 1$, $BL = 1$, $BL' = 0$
 - Force A_b low, then A charges high
- ❑ *Writability*
 - Must overpower feedback inverter
 - $N4 \gg P2$





Column Circuitry


- Some circuitry is required for each column
 - **Required:** Bitline conditioning
 - Precharging
 - Driving input data to bitline

 - **Increased speed:** Sense amplifiers
 - **Aspect ratio (square memory):** Column multiplexing (AKA Column Decoders)



SRAM Column Example


read

 




SRAM Column Example

read

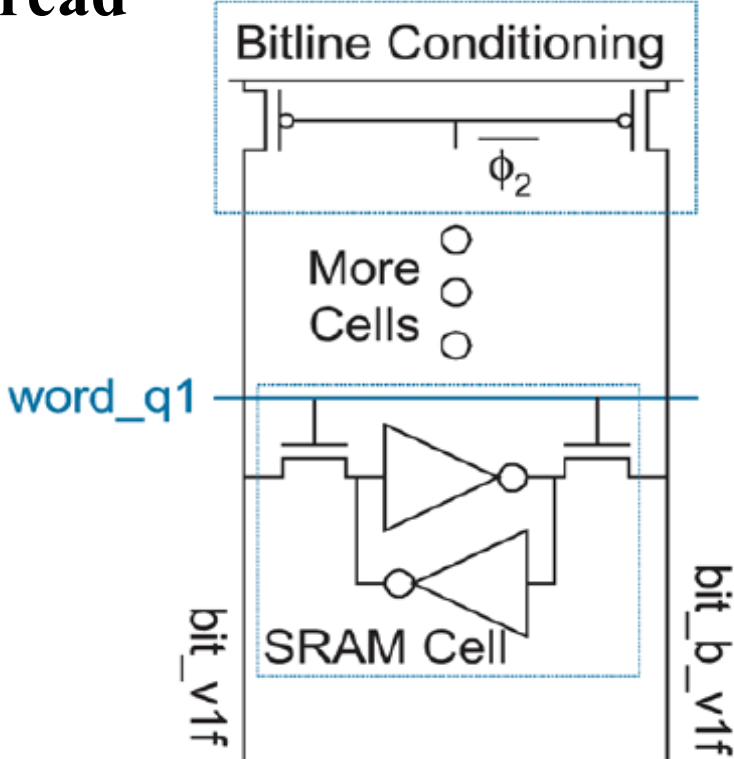


write

 




5T SRAM

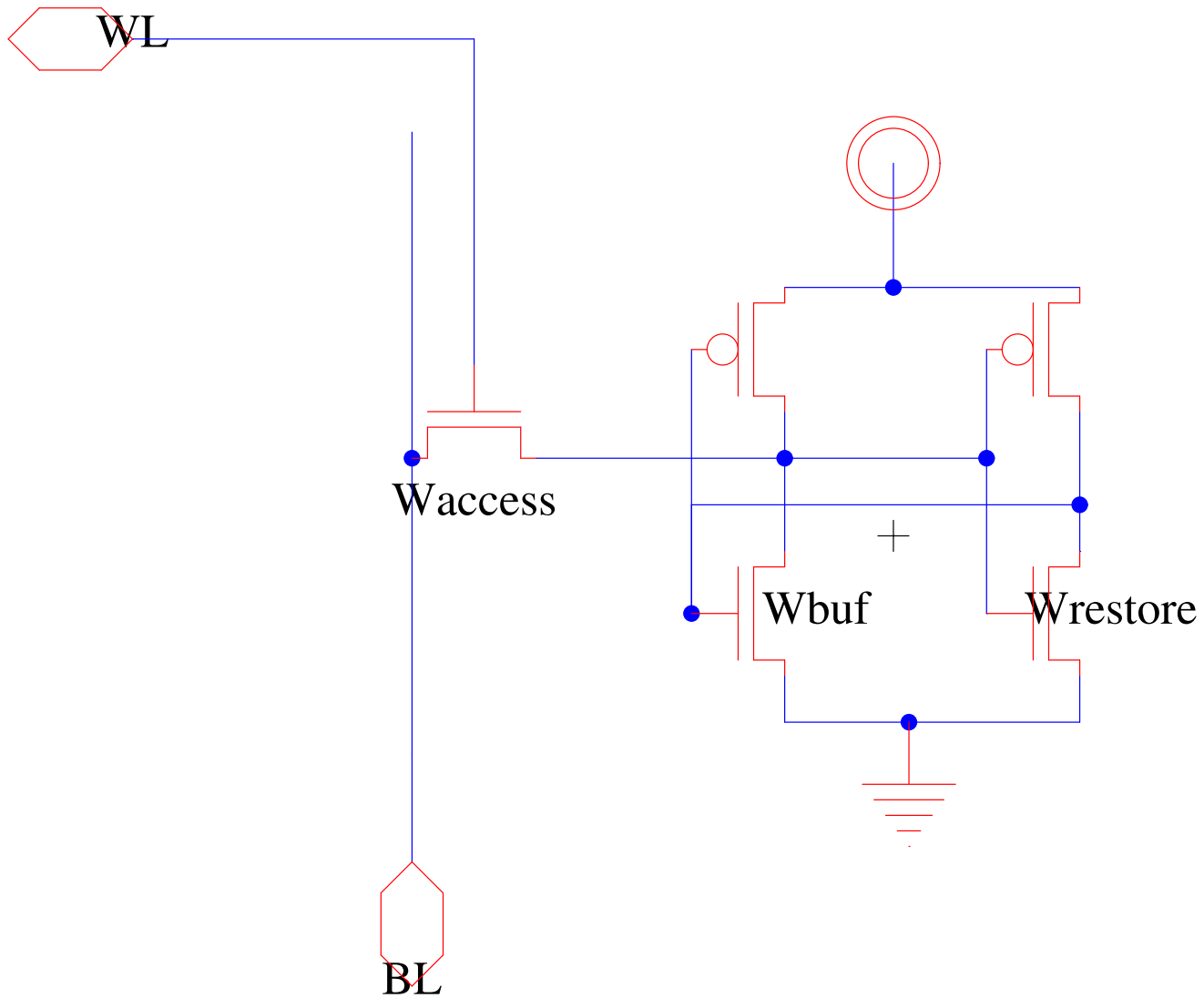

Charge Sharing (Preclass 3)

Initially

- A @ 1V
- B @ 0V
- $Q_A = 1V * C1 = C1$

 


Charge Sharing (Preclass 3)

Initially

- A @ 1V
- B @ 0V
- $Q_A = 1V * C1 = C1$

Close switch

 - $Q_{tot} = V_{final} * (C1 + C0)$
- Charge conservation
 - $Q_A = Q_{tot}$
- $C1 = V_{final} * (C1 + C0)$




$$V_{final} = \frac{C1}{C1 + C0}$$

Consider (preclass 4)


□ Read: What happens to voltage at A when WL turns from 0 → 1?

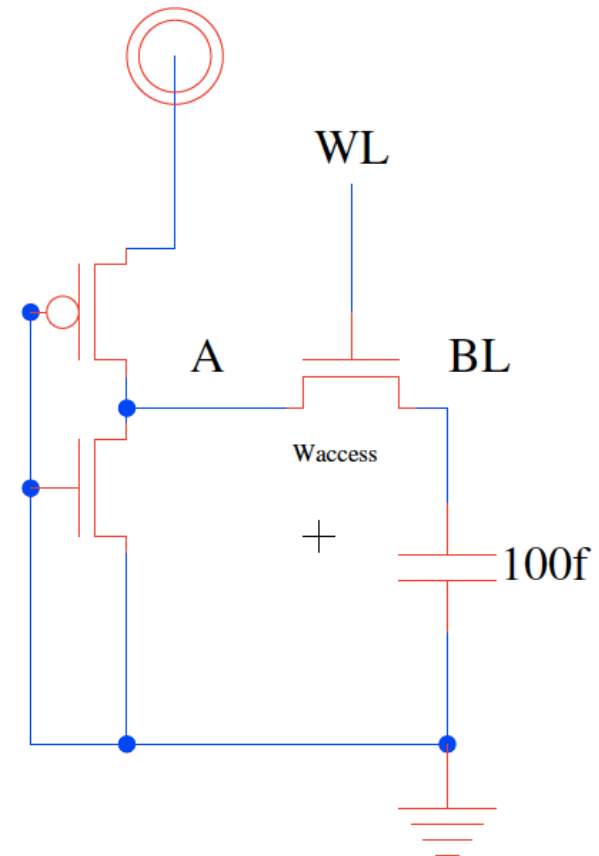- Assume W_{access} large
- $W_{\text{access}} \gg W_{\text{pu}} = 1$
- BL initially 0




Voltage After enable Word Line

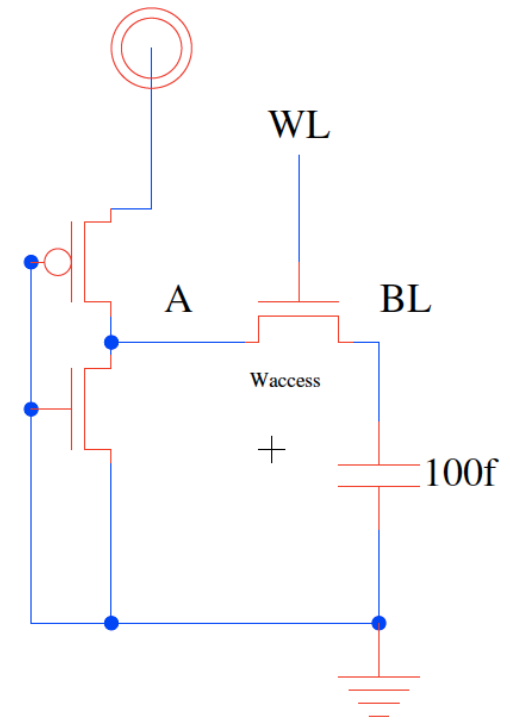- ❑ $Q_{BL} = 0$
- ❑ $Q_A = (1V)(\gamma 2C_0 + \gamma W_{\text{access}} C_0)$
- ❑ $100\text{fF} = C_{BL} \gg C_A = (\gamma(2 + W_{\text{access}})C_0)$




Voltage After enable Word Line

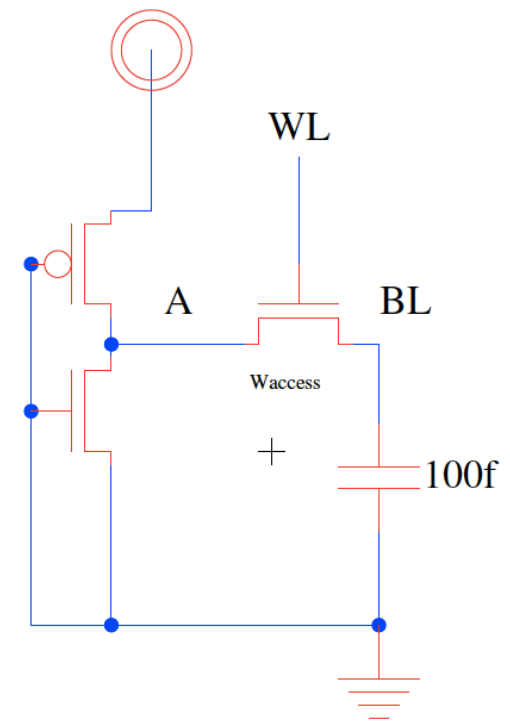- $Q_{BL} = 0$
- $Q_A = (1V)(\gamma 2C_0 + \gamma W_{\text{access}} C_0)$
- $100\text{fF} = C_{BL} \gg C_A = (\gamma(2 + W_{\text{access}})C_0)$
- After enable W_{access} (W_{access} large)
 - Total charge $Q_{BL} + Q_A$ unchanged
 - Charge conservation
 - Distributed over larger capacitance $\sim C_{BL}$
 - $V_A = V_{BL} \sim C_A / C_{BL}$






Simulation: $W_{\text{access}} = 100$

 


Transient Response

 

Consider (5T SRAM) (preclass 5)


□ What happens to voltage at A when WL turns from 0 → 1?

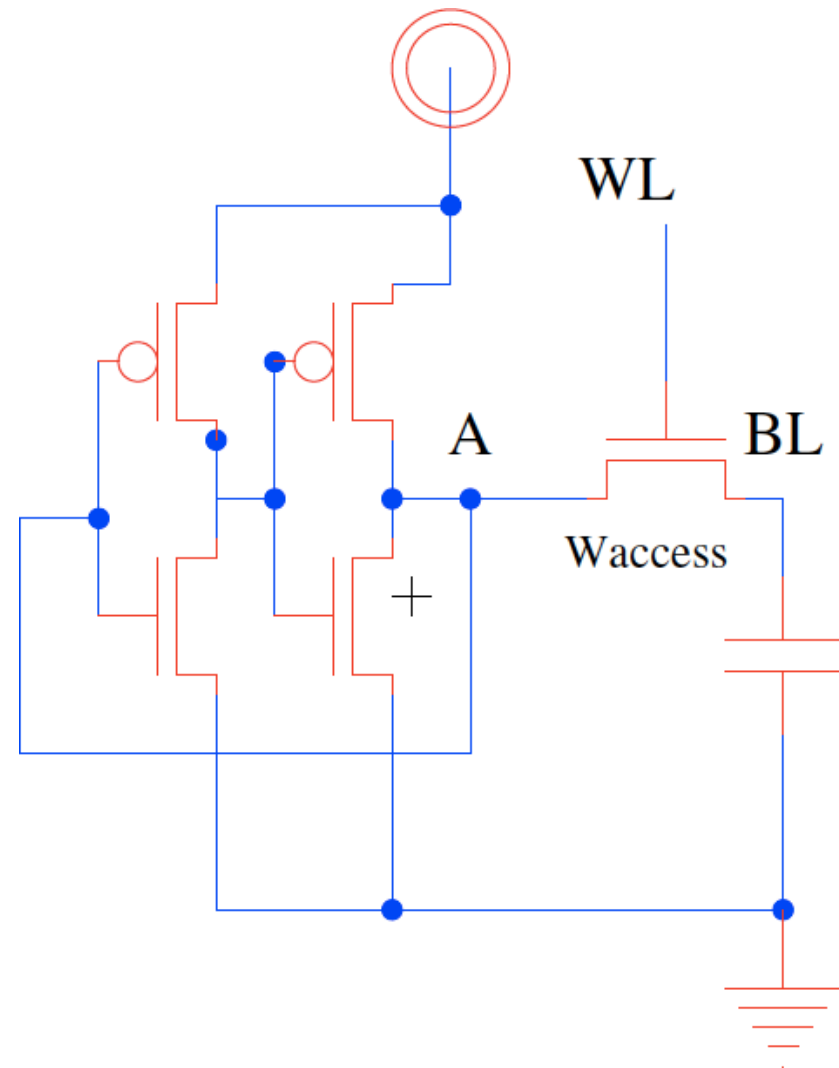- Assume W_{access} large
- A initially 1
- BL initially 0






Simulation $W_{\text{access}} = 20$

 


Transient Response

 




Simulation $W_{\text{access}}=4$

 


Transient Response

 




Charge Sharing

 - ❑ **Conclude:** charge sharing can lead to read upset
 - Charge redistribution/sharing adequate to flip state of bit





$$W_{\text{access}}=20$$

 

$$W_{\text{access}}=4$$

Charge to middle Voltage

 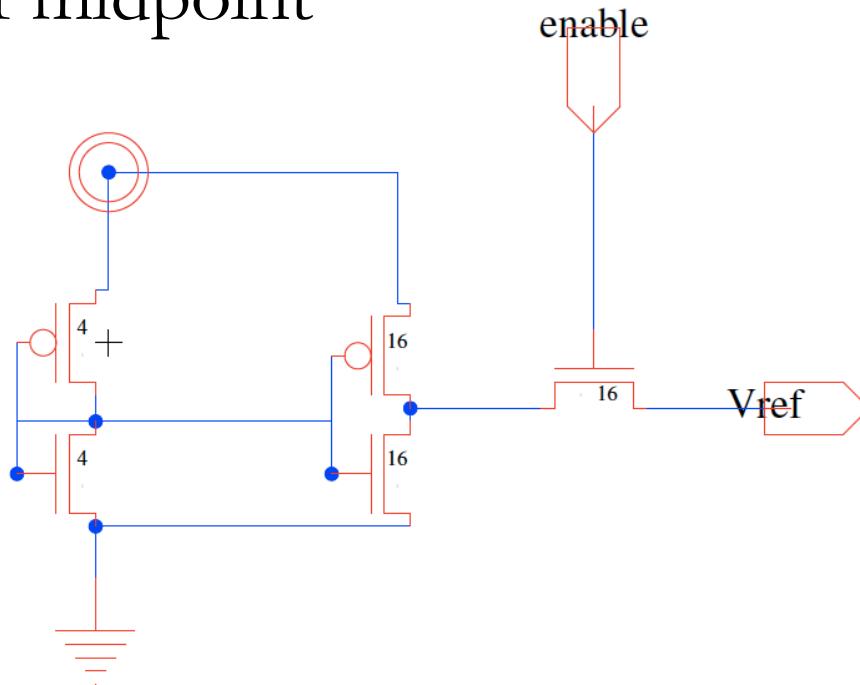
- ❑ Pre-charge bitlines to $V_{dd}/2$ before begin read operation
- ❑ Now charge sharing doesn't swing to opposite side of midpoint






Compare

 - Both $W_{\text{access}}=20$; vary BL precharge voltage




0 precharge

 


$V_{\text{dd}}/2$ precharge



 Simulation $W_{\text{access}}=20$ (precharge $V_{\text{dd}}/2$, reading 0)




Transient Response (reading 0)

 




Simulation $W_{\text{access}}=20$ (with precharge $V_{\text{dd}}/2$)

Transient Response

 

Read 1


Transient Response (reading 0)

 

Read 0

Multiple Ports

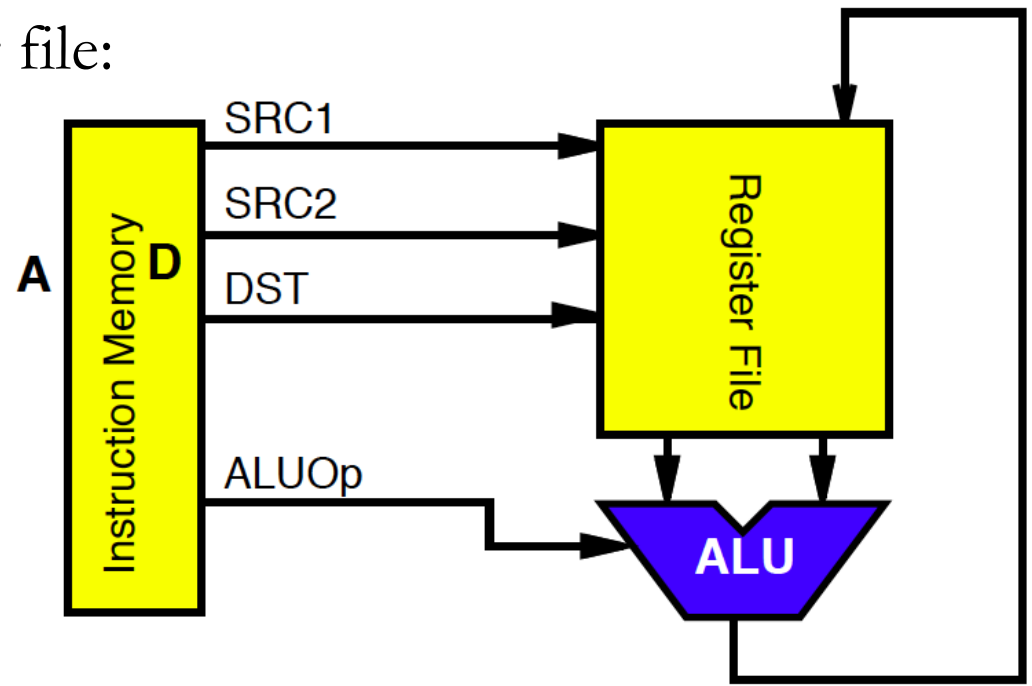
- ❑ We have considered single-ported SRAM
 - One read or one write on each cycle
- ❑ *Multiported* SRAM are needed for register files
- ❑ Examples:
 - Pipelined ALU register file:
 - add r1,r2,r3
 - $R3 \leftarrow R1 + R2$
 - Requires two reads and one write





Dual-Ported SRAM

 
- ❑ Simple dual-ported SRAM
 - Two independent single-ended reads
 - Or one differential write





Multi-Ported SRAM

 
- ❑ Adding more access transistors hurts read stability
- ❑ Multiported SRAM isolates reads from state node
- ❑ Single-ended bitlines save area





Register File Cell

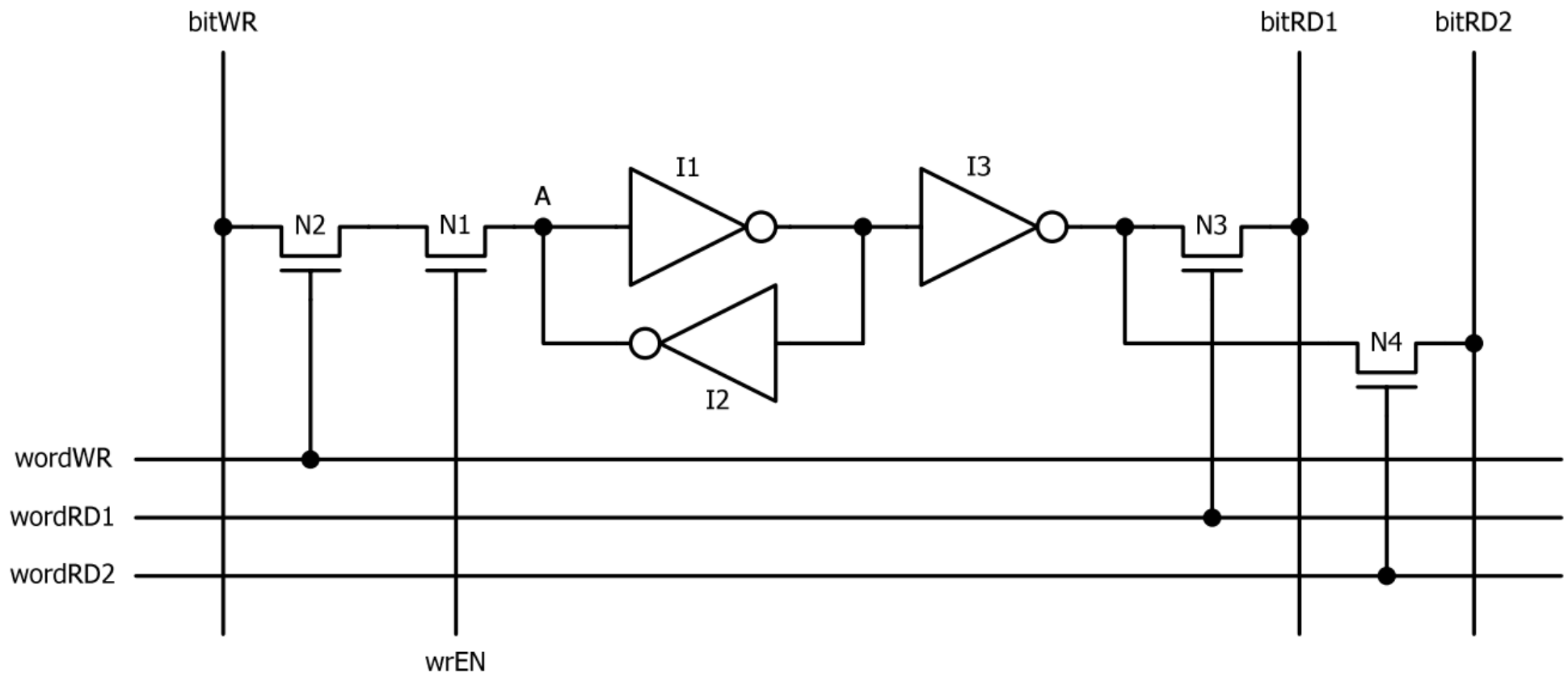- Single-ended 2-read/1-write ports (Slow-write)






DRAM

- ❑ Smaller than SRAM
- ❑ Require data refresh to compensate for leakage


3-Transistor DRAM Cell

- Cell is inverting on read operation

 


3-Transistor DRAM Cell

- Cell is inverting on read operation

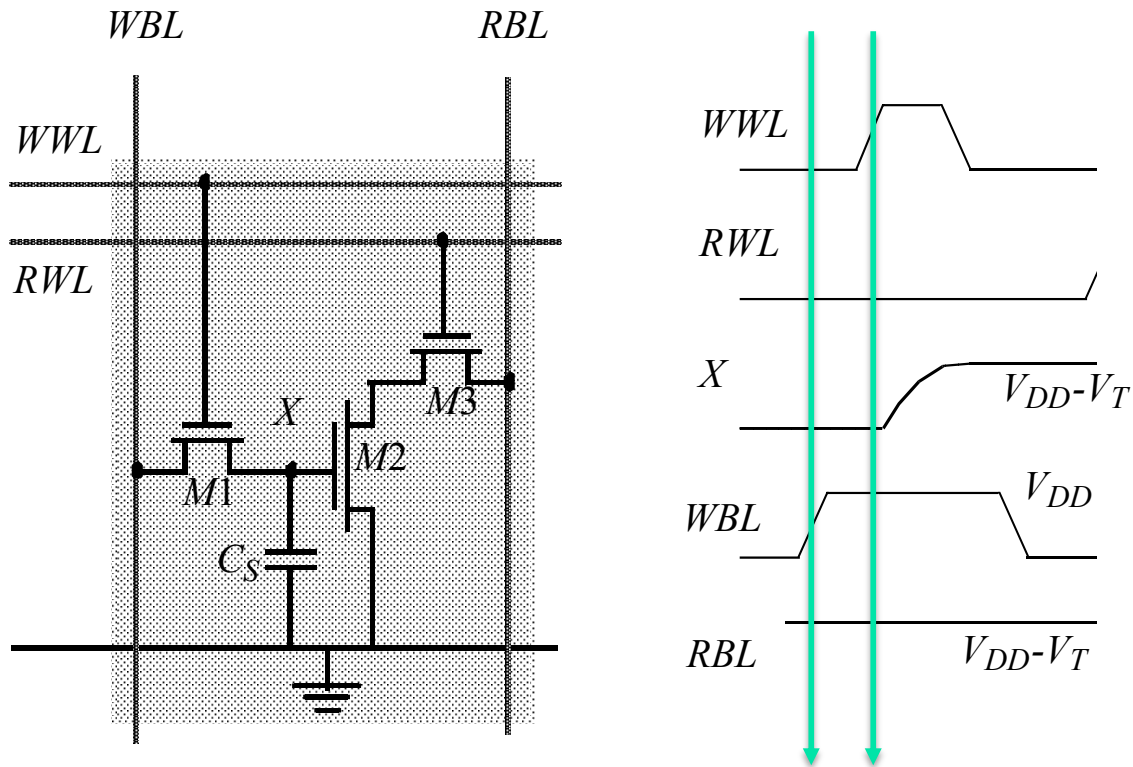


3-Transistor DRAM Cell

- Cell is inverting on read operation

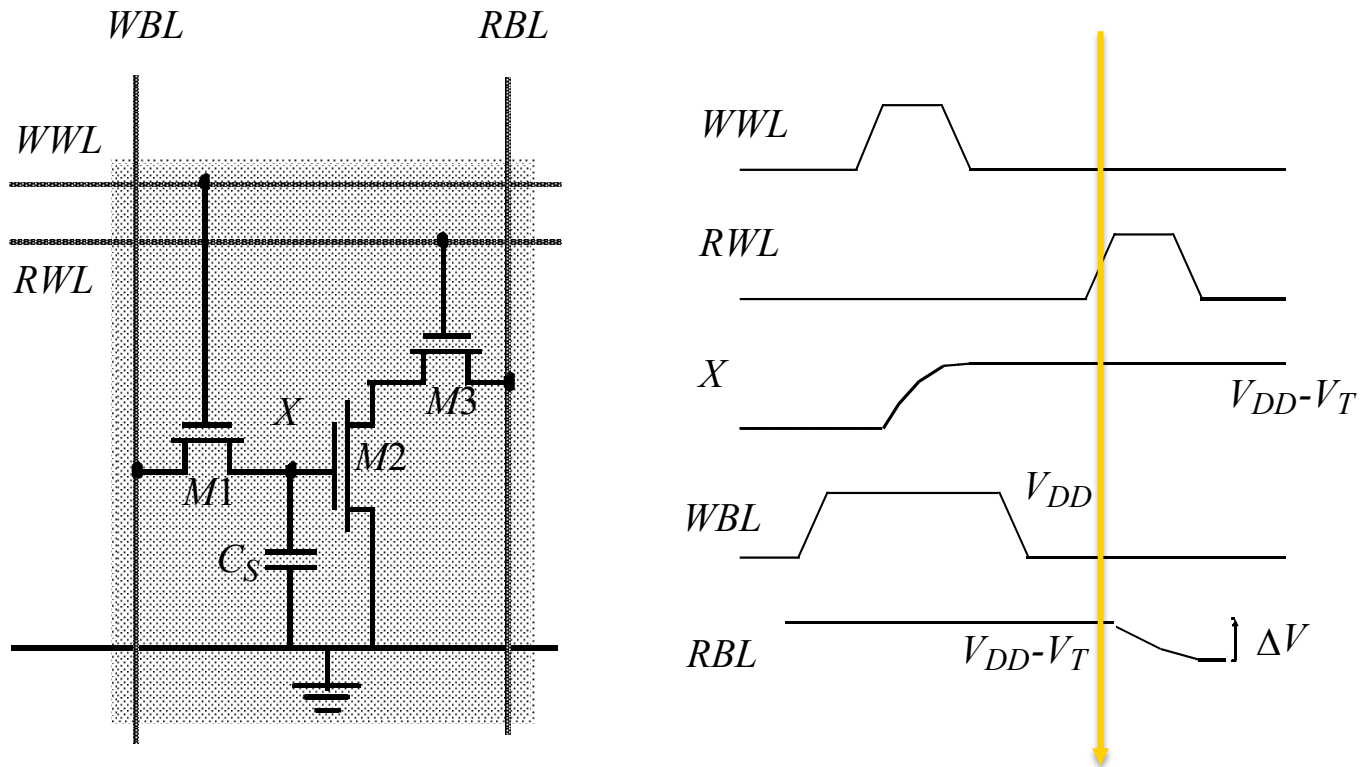

3-Transistor DRAM Cell


- ❑ Cell is inverting on read operation

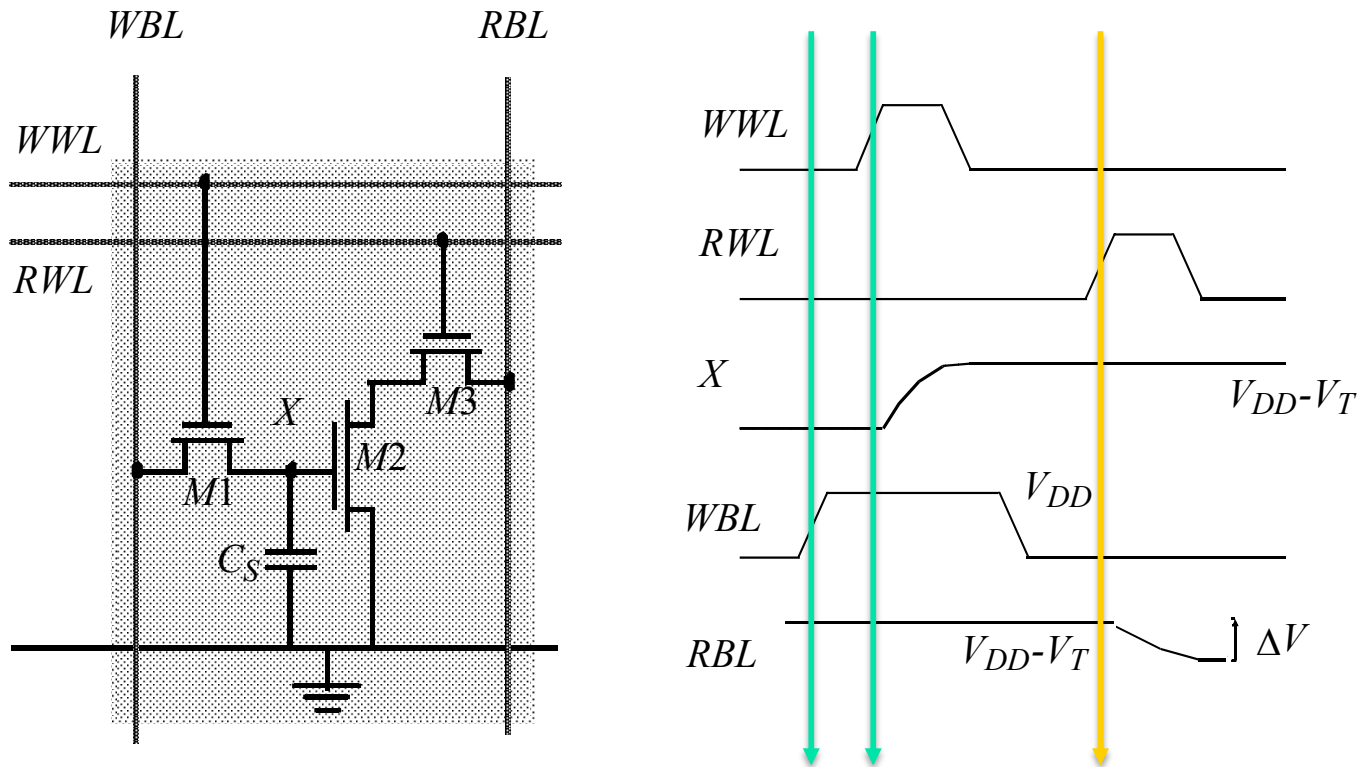


- No constraints on device ratios
- Reads are non-destructive
- Data stored has a V_T drop
 - When storing a 1, value at $X = V_{WWL} - V_{Tn}$



1-Transistor DRAM Cell

 


1-Transistor DRAM Cell

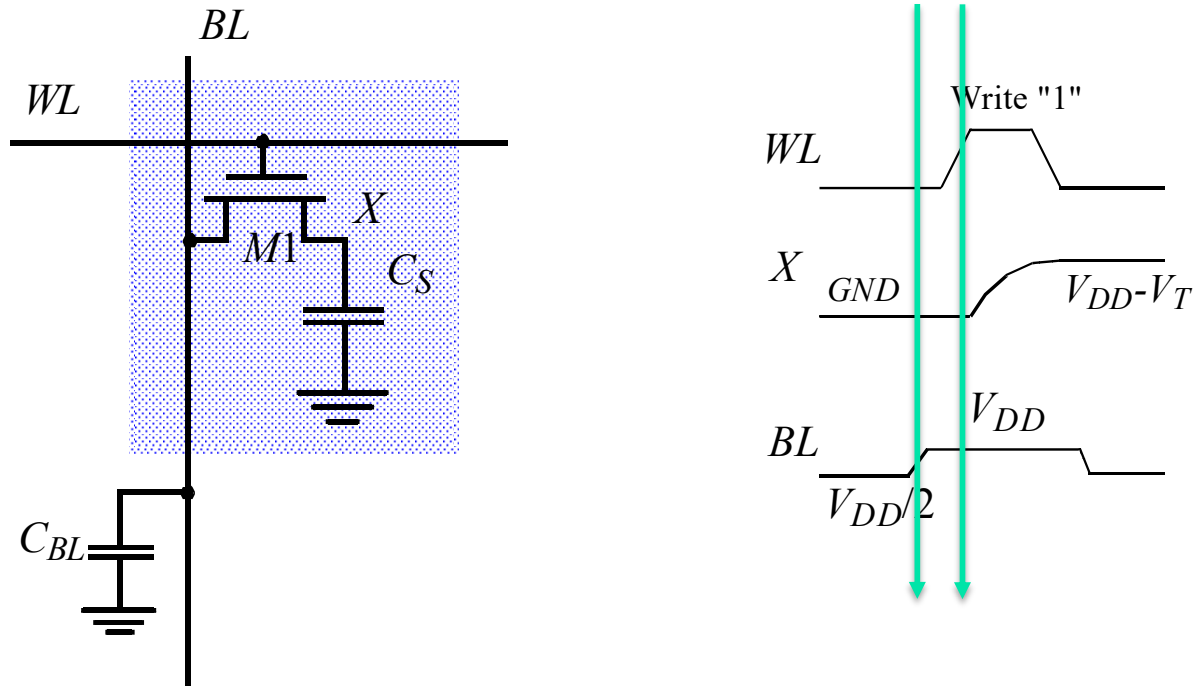

Write: C_s is charged or discharged by asserting WL and BL.

1-Transistor DRAM Cell

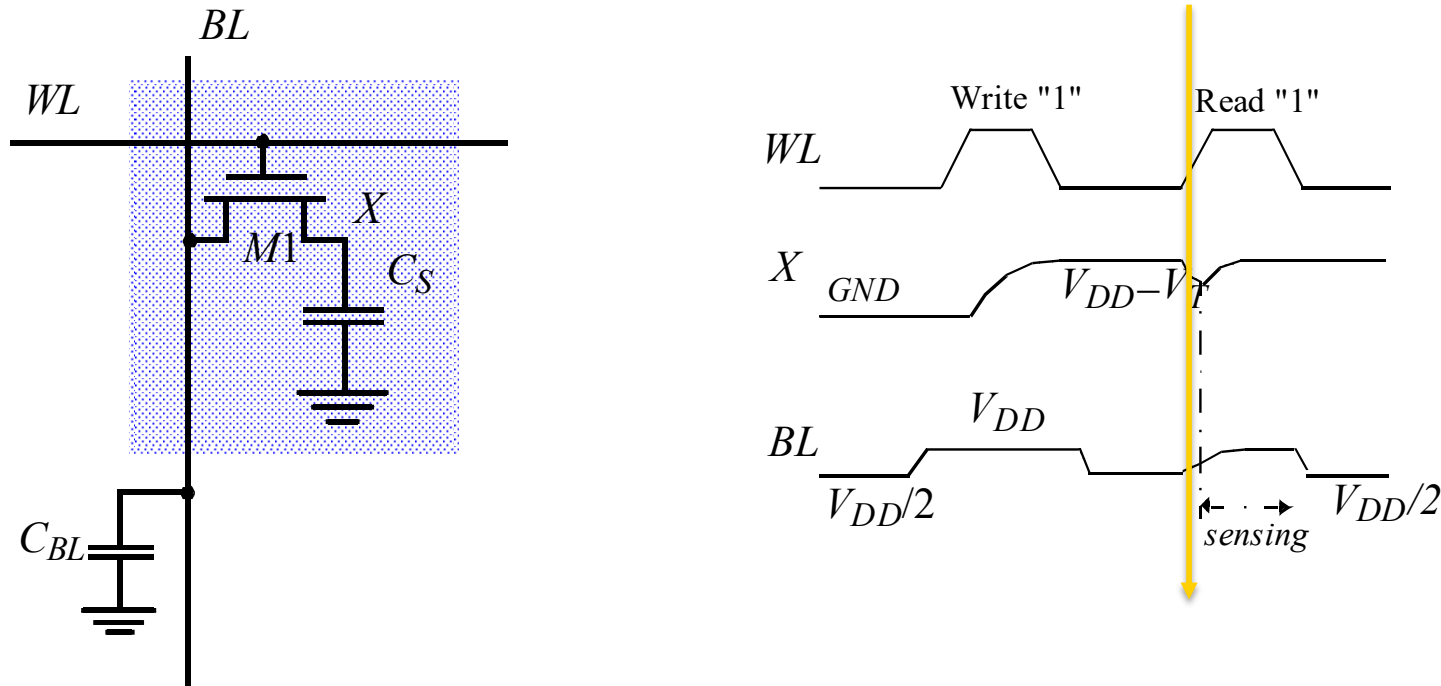



Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes places between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

Voltage swing is small; typically around 250 mV.

1-Transistor DRAM Cell

  

Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes place between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

Voltage swing is small; typically around 250 mV.



DRAM Cell Observations

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out
- ❑ DRAM memory cells are single ended in contrast to SRAM cells
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operation are necessary for correct operation
- ❑ Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This loss can be circumvented by bootstrapping the word lines to a higher value than V_{DD} .



Big Idea

- ❑ 6T SRAM
 - Robust cell when sized carefully
- ❑ 5T SRAM
 - More sensitive to sizing than 6T SRAM
- ❑ Minimize area of repeated cell
 - 6T/5T SRAM
 - Multiport trade off area for function
 - 1T/3T DRAM helps but slower
- ❑ Compensate with periphery (next time...)
 - Decoders
 - Bitline (column) drivers
 - Sensing/Amplification (regeneration/restoration)



Admin

- ❑ Homework 6 due tonight
- ❑ NEW Homework 7
 - Come to lab 4/22 and turn in worksheet for credit
- ❑ Project 2 out now
 - Design SRAM array
 - Work in teams of up to two
 - Milestone due F 4/19
 - Will get feedback from me by M 4/22
 - Final report due Wednesday 5/1



Acknowledgement

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Jing Li (University of Pennsylvania)