

ESE3700: Circuit-Level Modeling, Design and Optimization for Digital Systems

Lec 19: April 15, 2024
RAM Core and Periphery







Today

- Memory
 - Classification
 - Architecture
 - RAM Core
 - Periphery
 - Serial Access Memories

- Project 2 is on this


SRAM Read

 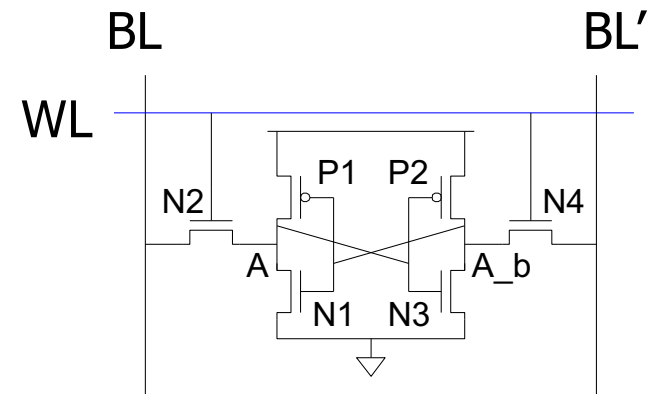- ❑ Precharge both bitlines high
- ❑ Then turn on wordline, WL
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex: $A = 0, A_b = 1$
 - BL discharges, BL' stays high
 - But A bumps up slightly
- ❑ *Read stability*
 - A must not flip
 - $N1 > N2$



SRAM Write

 - Drive one bitline high, the other low
 - Depending on write data
- Then turn on wordline, WL
- Bitlines overpower cell with new value
- Ex: $A = 0$, $A_b = 1$, $BL = 1$, $BL' = 0$
 - Force A_b low, then A charges high
- *Writability*
 - Must overpower feedback inverter
 - $N4 \gg P2$






Column Circuitry


- Some circuitry is required for each column
 - **Required:** Bitline conditioning
 - Precharging
 - Driving input data to bitline
 - **Increased speed:** Sense amplifiers
 - **Aspect ratio (square memory):** Column multiplexing (AKA Column Decoders)

SRAM Column Example


read

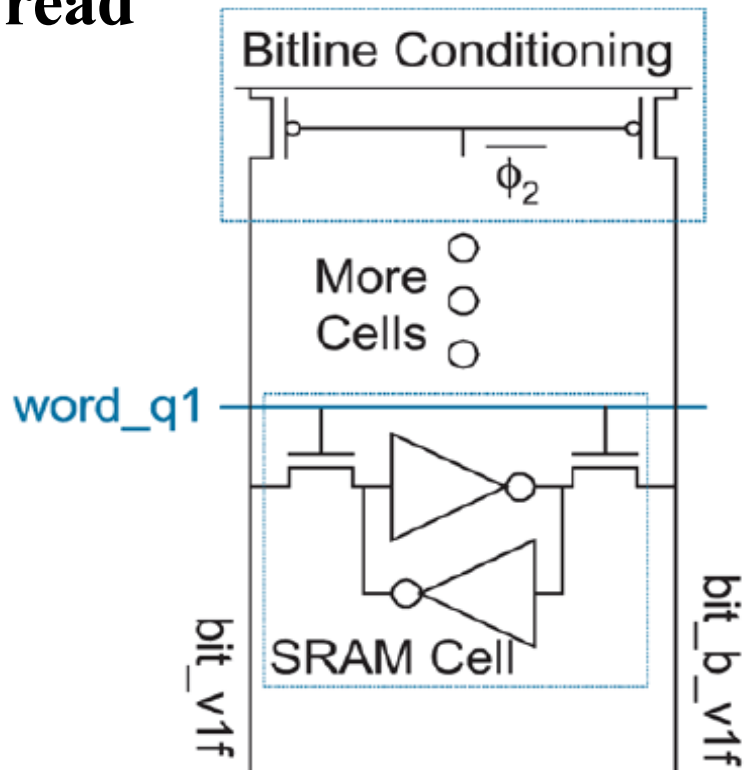

write

 


5T SRAM

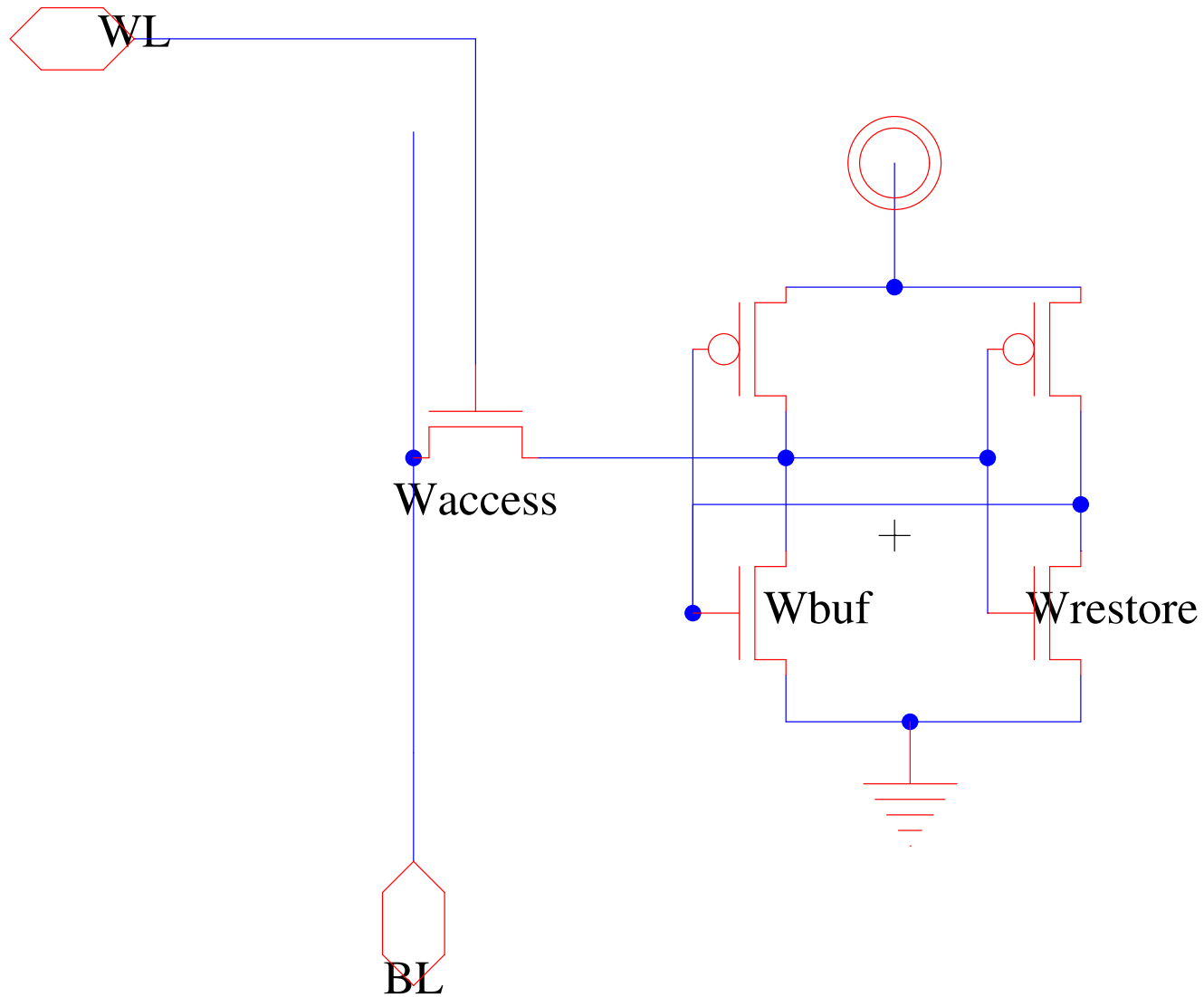

Charge Sharing (Preclass 1)

Initially

- A @ 1V
- B @ 0V
- $Q_A = 1V * C1 = C1$

 


Charge Sharing (Preclass 1)

Initially

- A @ 1V
- B @ 0V
- $Q_A = 1V * C1 = C1$

Close switch

 - $Q_{tot} = V_{final} * (C1 + C0)$
- Charge conservation
 - $Q_A = Q_{tot}$
- $C1 = V_{final} * (C1 + C0)$




$$V_{final} = \frac{C1}{C1 + C0}$$

Consider (preclass 2)


□ Read: What happens to voltage at A when WL turns from 0 → 1?

 - Assume W_{access} large
- $W_{\text{access}} \gg W_{\text{pu}} = 1$
- BL initially 0




Voltage After enable Word Line

 - ❑ $Q_{BL} = 0$
- ❑ $Q_A = (1V)(\gamma 2C_0 + \gamma W_{\text{access}} C_0)$
- ❑ $100\text{fF} = C_{BL} \gg C_A = (\gamma(2 + W_{\text{access}})C_0)$




Voltage After enable Word Line

 
- $Q_{BL} = 0$
- $Q_A = (1V)(\gamma 2C_0 + \gamma W_{\text{access}} C_0)$
- $100\text{fF} = C_{BL} \gg C_A = (\gamma(2 + W_{\text{access}})C_0)$
- After enable W_{access} (W_{access} large)
 - Total charge $Q_{BL} + Q_A$ unchanged
 - Charge conservation
 - Distributed over larger capacitance $\sim C_{BL}$
 - $V_A = V_{BL} \sim C_A / C_{BL}$



Simulation: $W_{\text{access}} = 100$

 


Transient Response

 


Consider (5T SRAM) (preclass 3)

□ What happens to voltage at A when WL turns from 0 → 1?

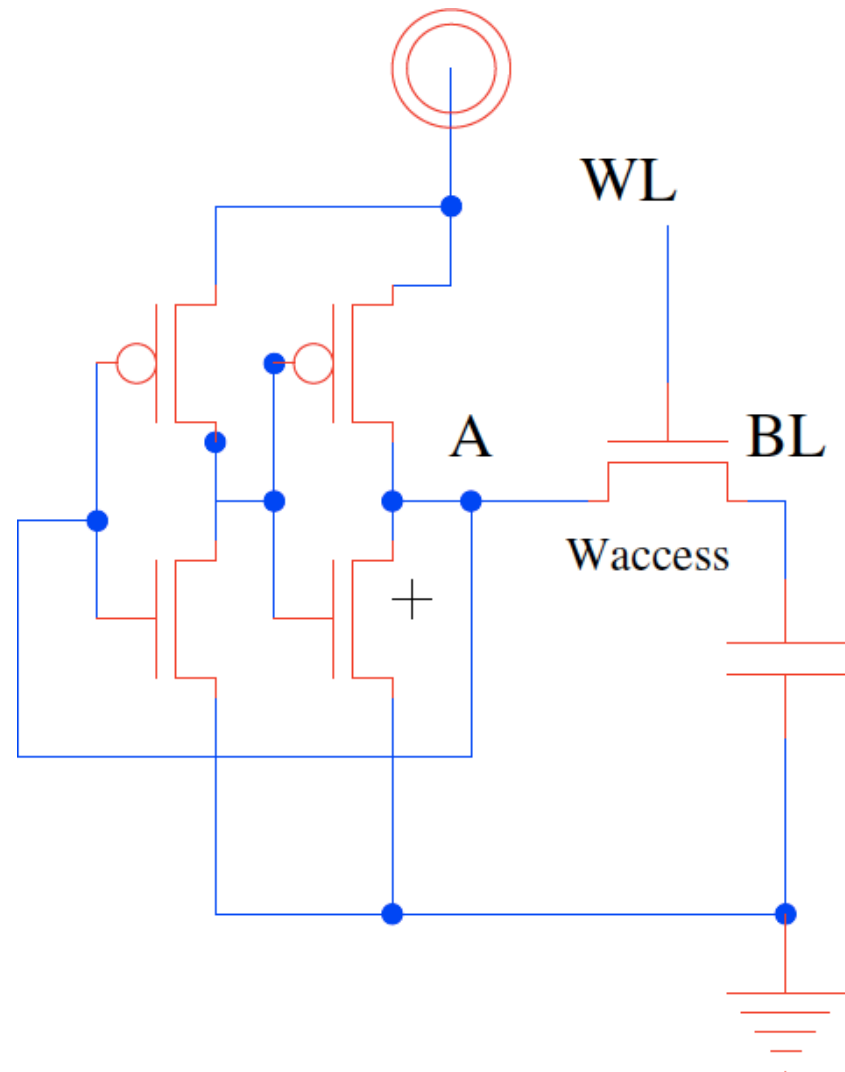
- Assume W_{access} large
- A initially 1
- BL initially 0



Simulation $W_{\text{access}} = 20$

 


Transient Response

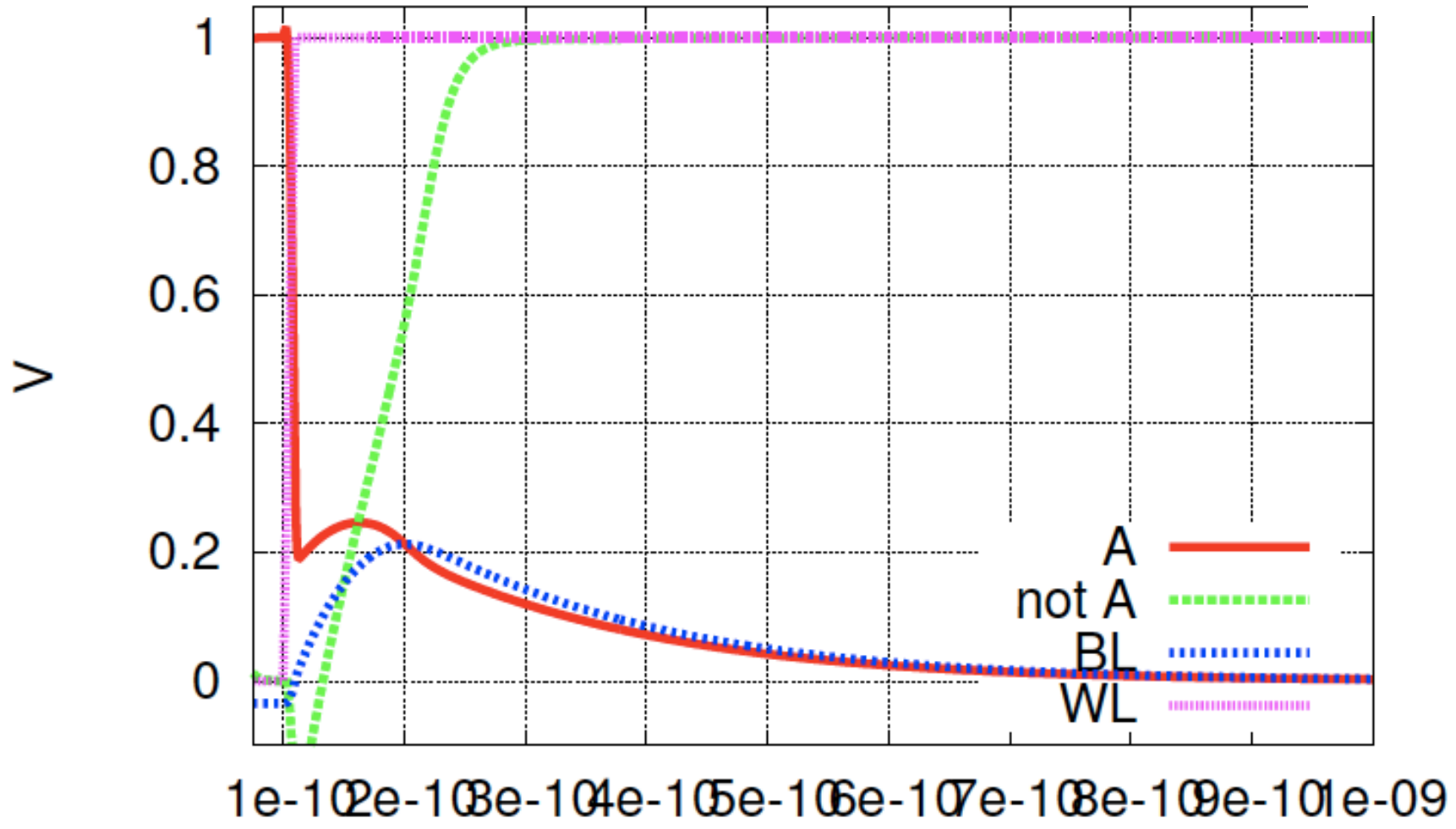




Simulation $W_{\text{access}} = 4$

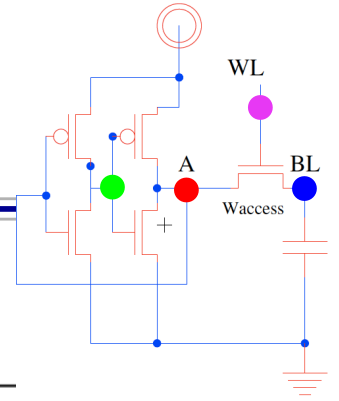


Transient Response

 


Charge Sharing

 - ❑ **Conclude:** charge sharing can lead to read upset
 - Charge redistribution/sharing adequate to flip state of bit





$$W_{\text{access}}=20$$

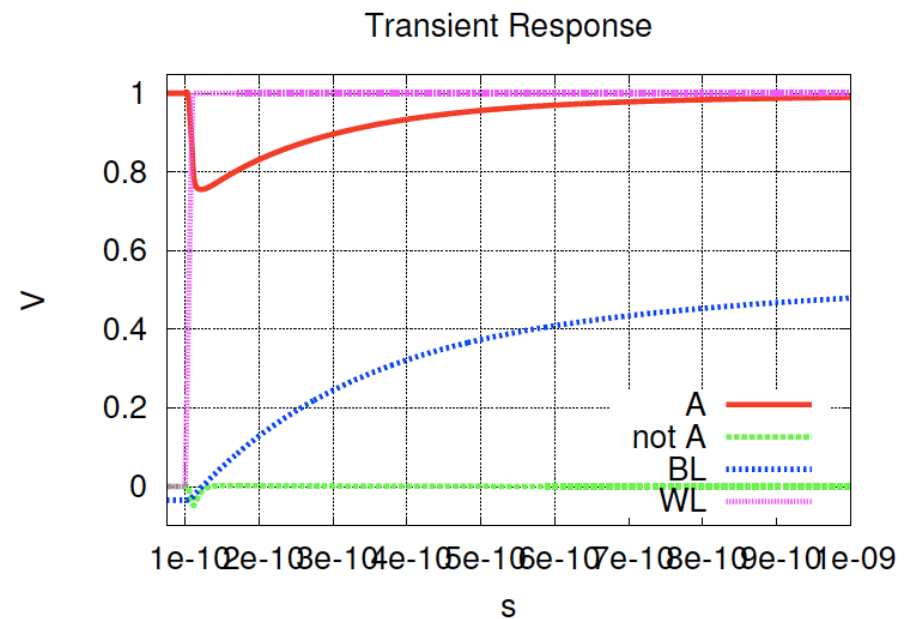

$$W_{\text{access}}=4$$

Charge to middle Voltage

 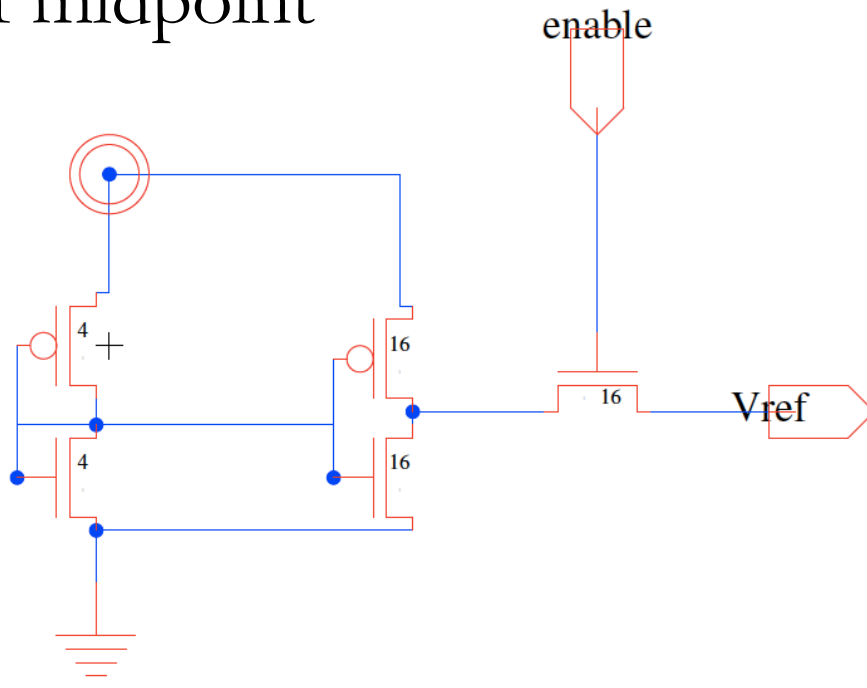
- ❑ Pre-charge bitlines to $V_{dd}/2$ before begin read operation
- ❑ Now charge sharing doesn't swing to opposite side of midpoint





Compare

 - Both $W_{\text{access}}=20$; vary BL precharge voltage




0 precharge




Compare

 Both $W_{\text{access}}=20$; vary BL precharge voltage




0 precharge

 


$V_{\text{dd}}/2$ precharge

 Simulation $W_{\text{access}}=20$ (precharge $V_{\text{dd}}/2$, reading 0)




Transient Response (reading 0)

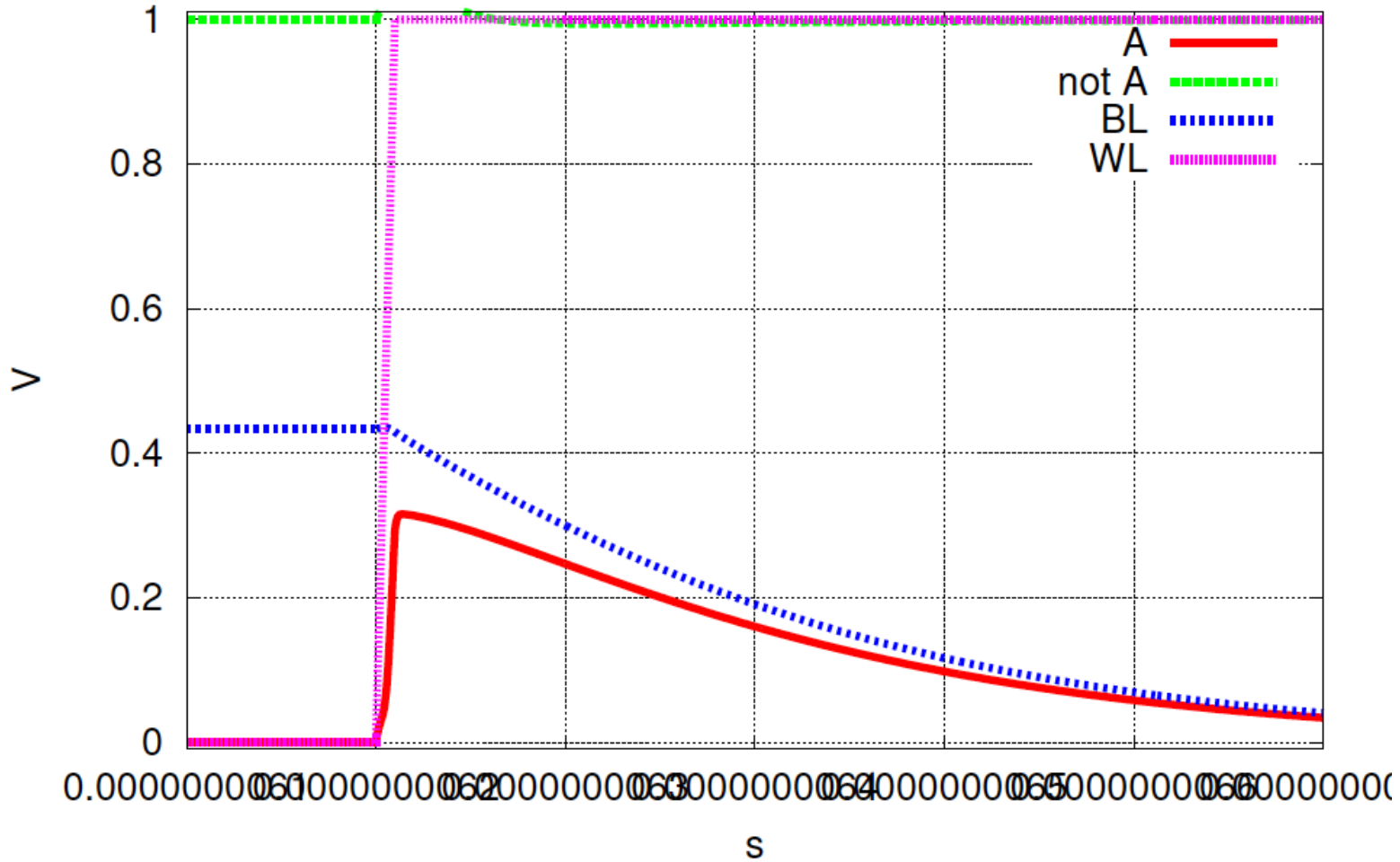




Simulation $W_{\text{access}}=20$ (with precharge $V_{\text{dd}}/2$)

Transient Response

 

Read 1


Transient Response (reading 0)

 

Read 0


Multiple Ports

 - ❑ We have considered single-ported SRAM
 - One read or one write on each cycle
- ❑ *Multiported* SRAM are needed for register files
- ❑ Examples:
 - Pipelined ALU register file:
 - add r1,r2,r3
 - $R3 \leftarrow R1 + R2$
 - Requires two reads and one write




Dual-Ported SRAM

 - Simple dual-ported SRAM
 - Two independent single-ended reads
 - Or one differential write



Dual-Ported SRAM

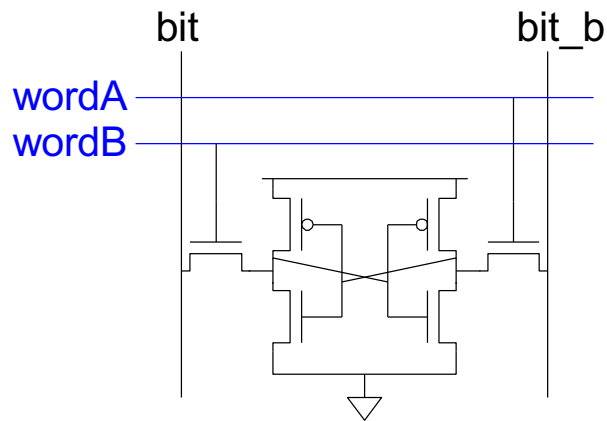
- Simple dual-ported SRAM
 - Two independent single-ended reads
 - Or one differential write



- Do two reads and one write by time multiplexing
 - Read during ph1, write during ph2

Multi-Ported SRAM

 - ❑ Adding more access transistors hurts read stability
- ❑ Multiported SRAM isolates reads from state node
- ❑ Single-ended bitlines save area






DRAM

- ❑ Smaller than SRAM
- ❑ Require data refresh to compensate for leakage


3-Transistor DRAM Cell (preclass 4)

- ❑ Cell is inverting on read operation

 


3-Transistor DRAM Cell

- Cell is inverting on read operation

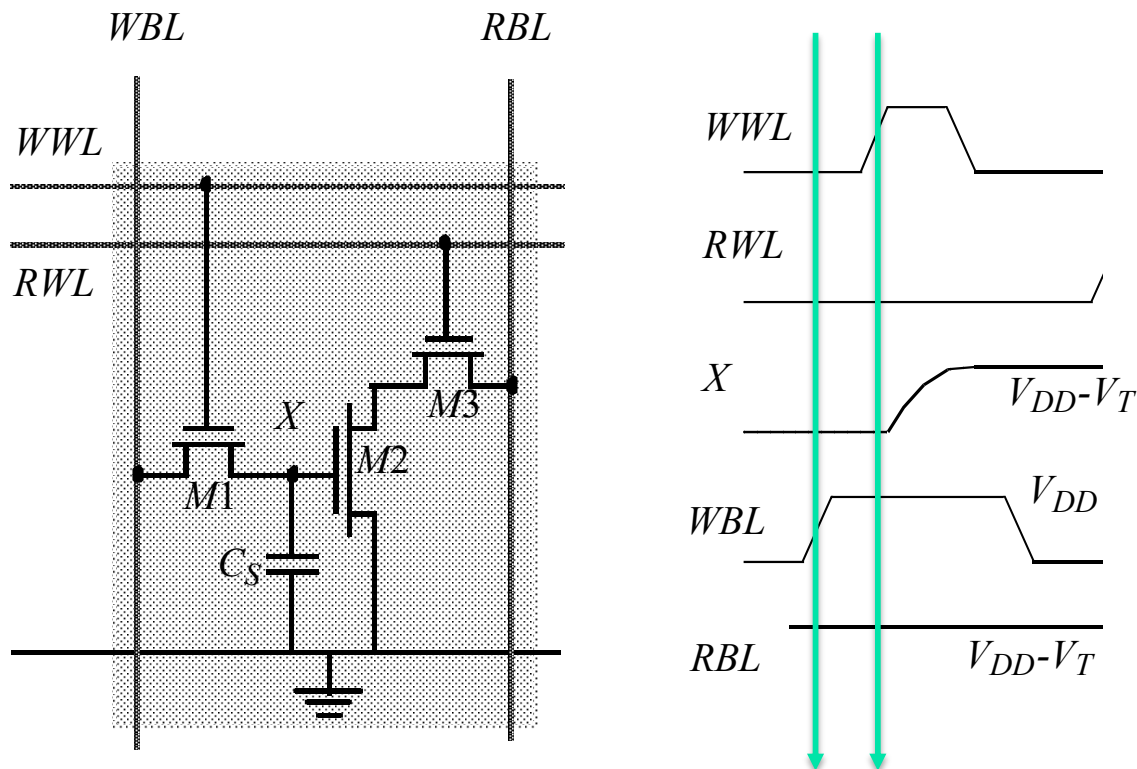


3-Transistor DRAM Cell

- Cell is inverting on read operation

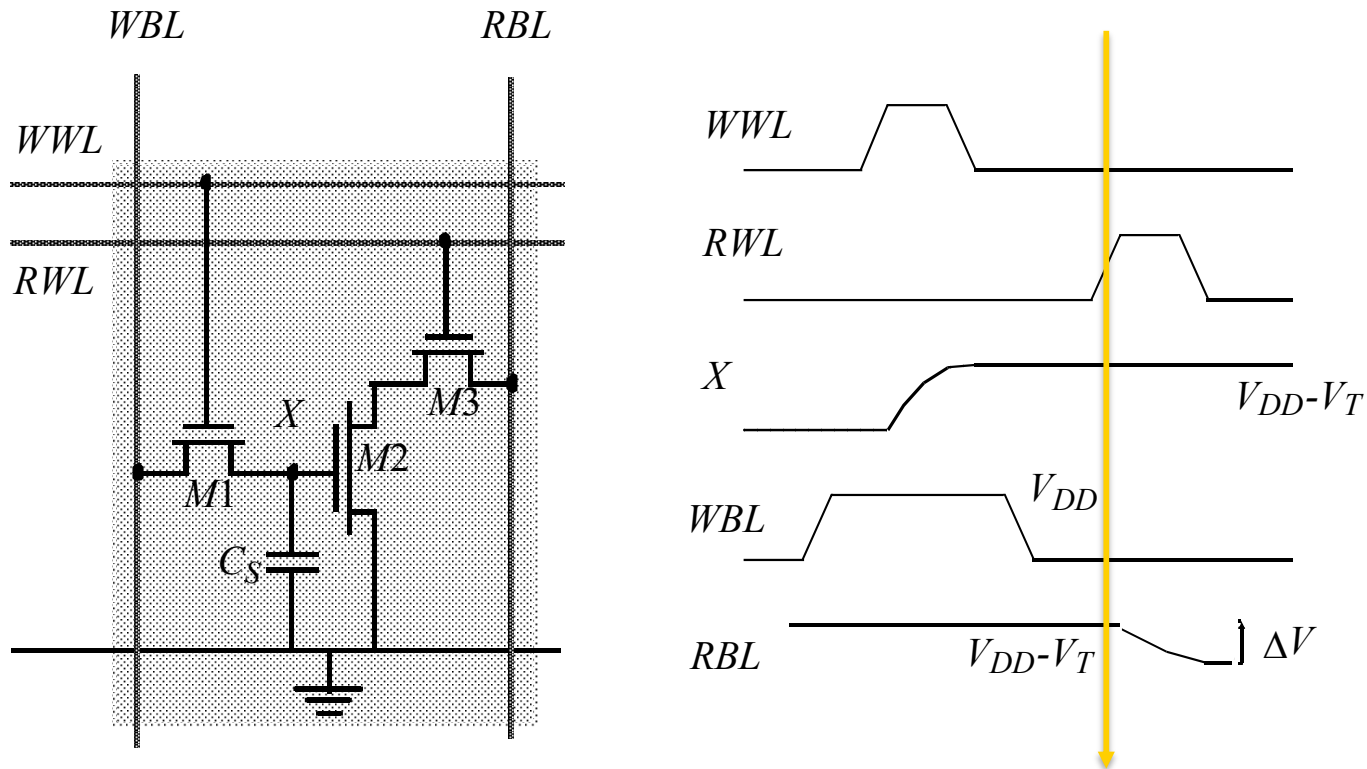


3-Transistor DRAM Cell

- Cell is inverting on read operation


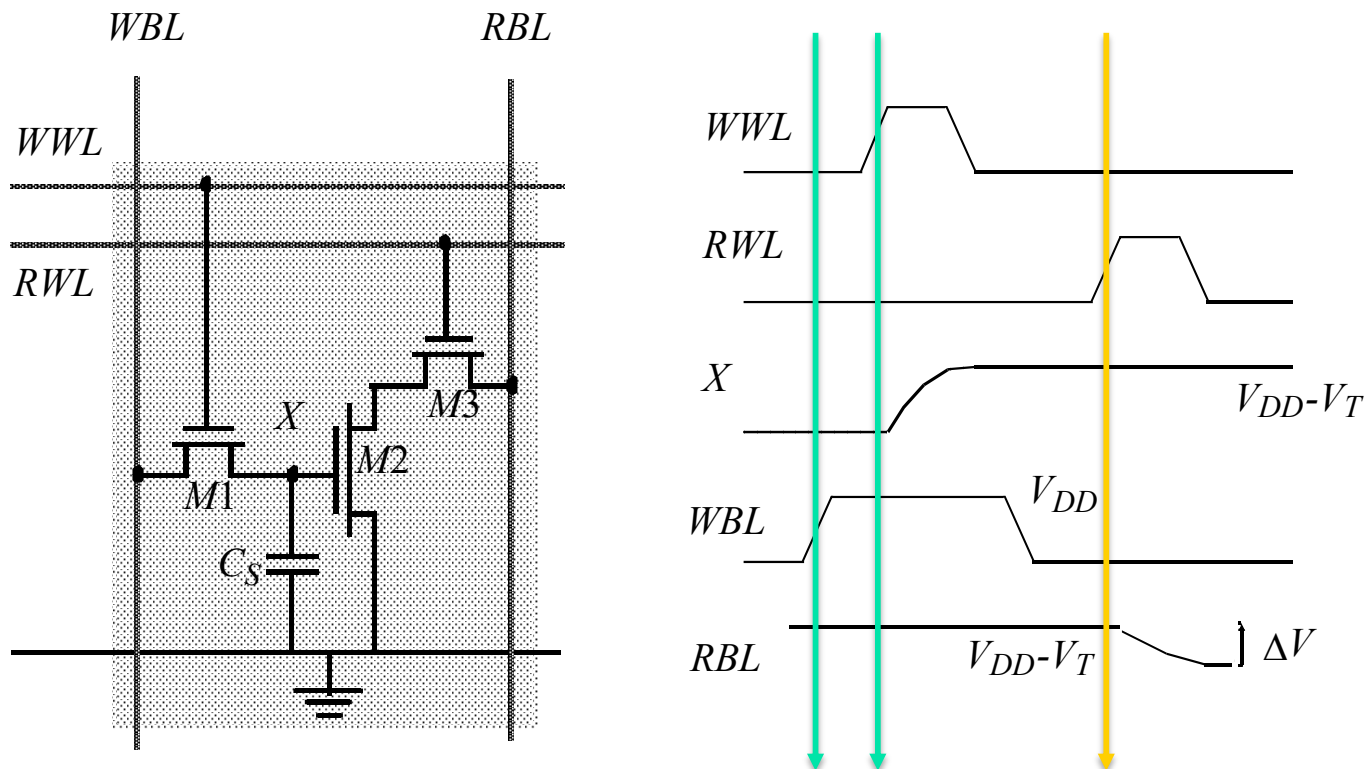


- No constraints on device ratios
- Reads are non-destructive
- Data stored has a V_T drop
 - When storing a 1, value at $X = V_{WWL}-V_{Tn}$

1-Transistor DRAM Cell (preclass 4)

 


1-Transistor DRAM Cell

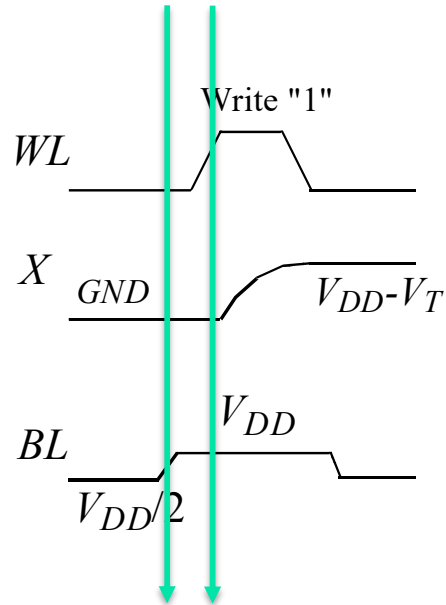 

Write: C_S is charged or discharged by asserting WL and BL.

1-Transistor DRAM Cell

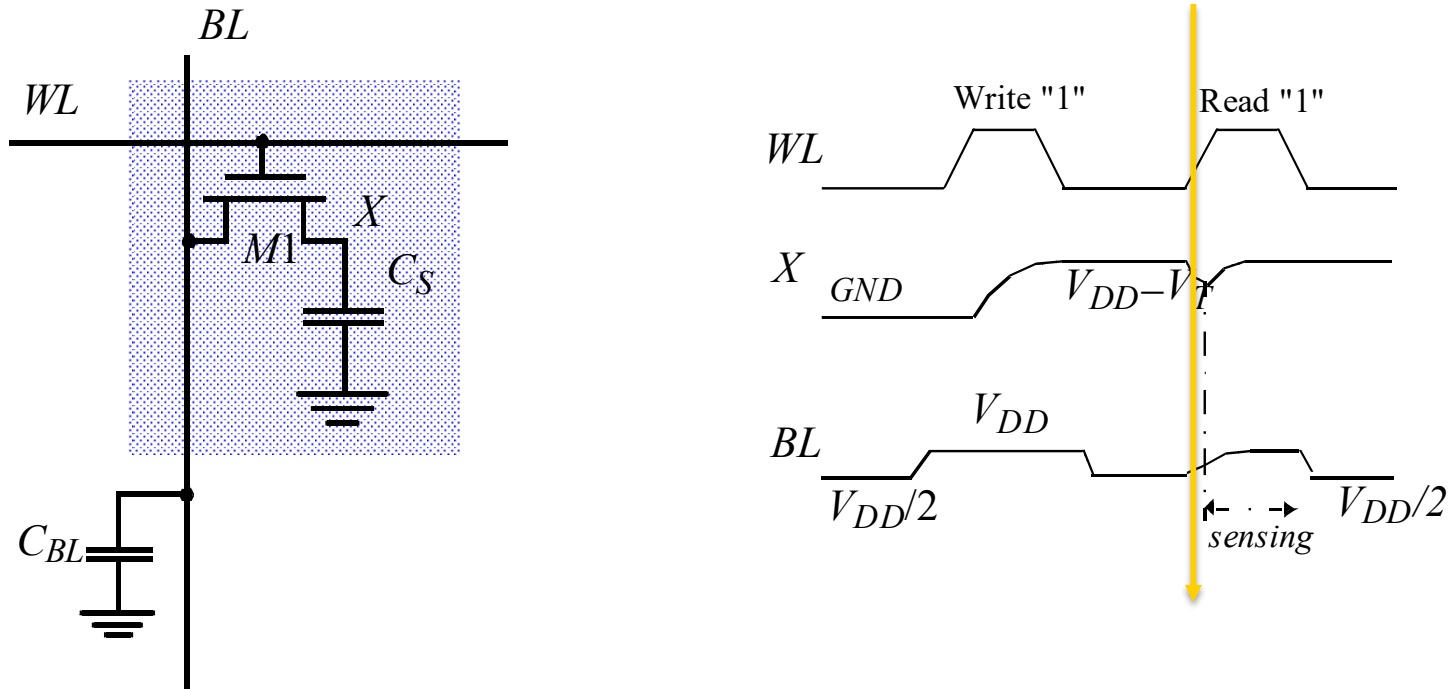

Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes places between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

Voltage swing is small; typically around 250 mV.



DRAM Cell Observations

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out
- ❑ DRAM memory cells are single ended in contrast to SRAM cells
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operation are necessary for correct operation
- ❑ Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This loss can be circumvented by bootstrapping the word lines to a higher value than V_{DD} .

Memory Periphery






Periphery

- ❑ Decoders
- ❑ Column Circuitry
 - Bit-line Conditioning
 - Sense Amplifiers
 - Input/Output Buffers
- ❑ Control/Timing Circuitry


Array Architecture

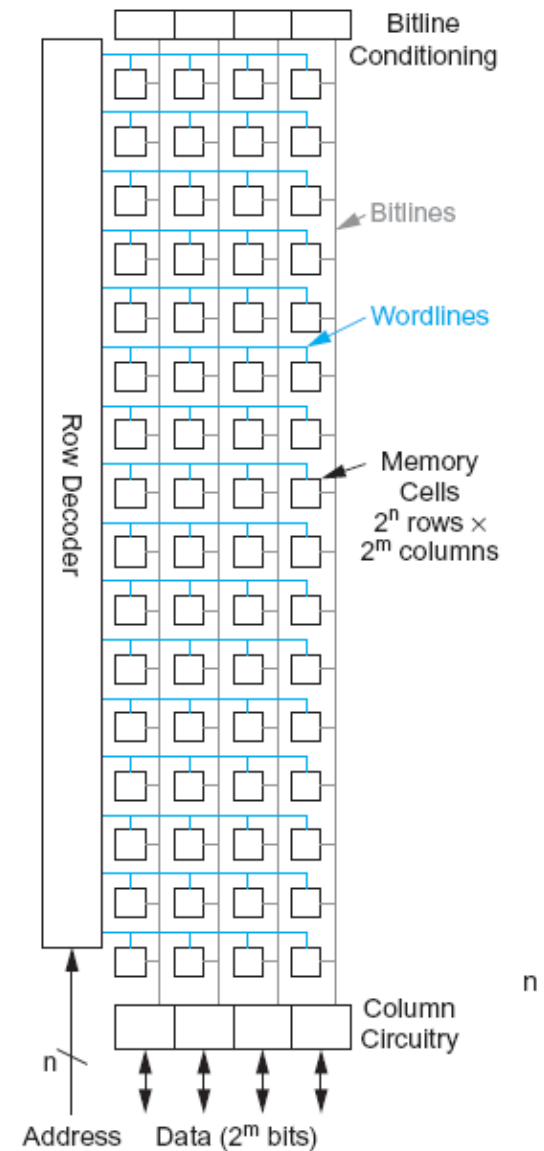- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used



Array Architecture

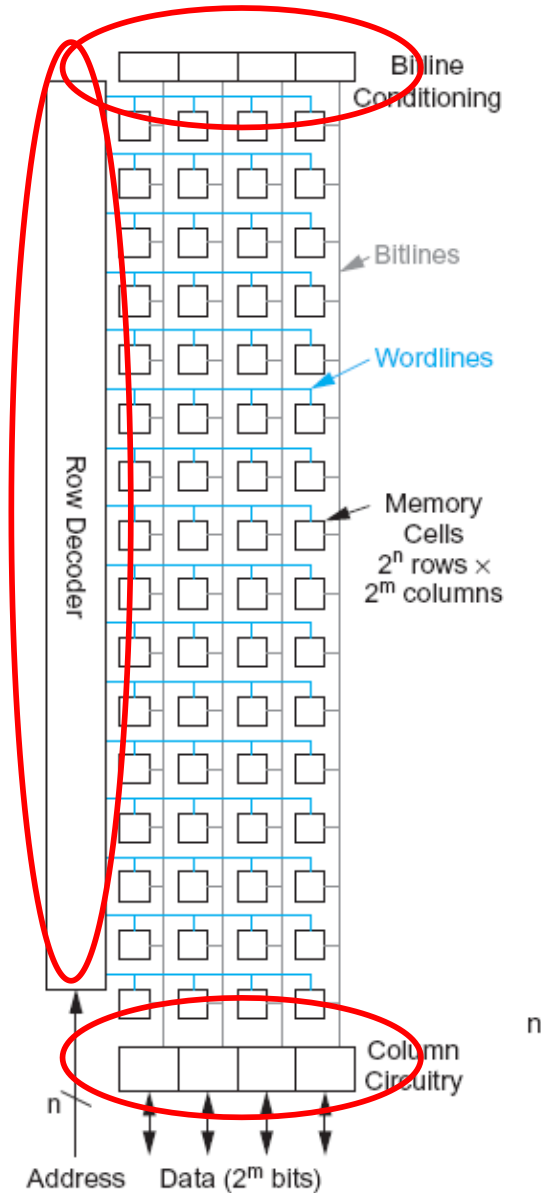- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used




Decoders



Array Architecture

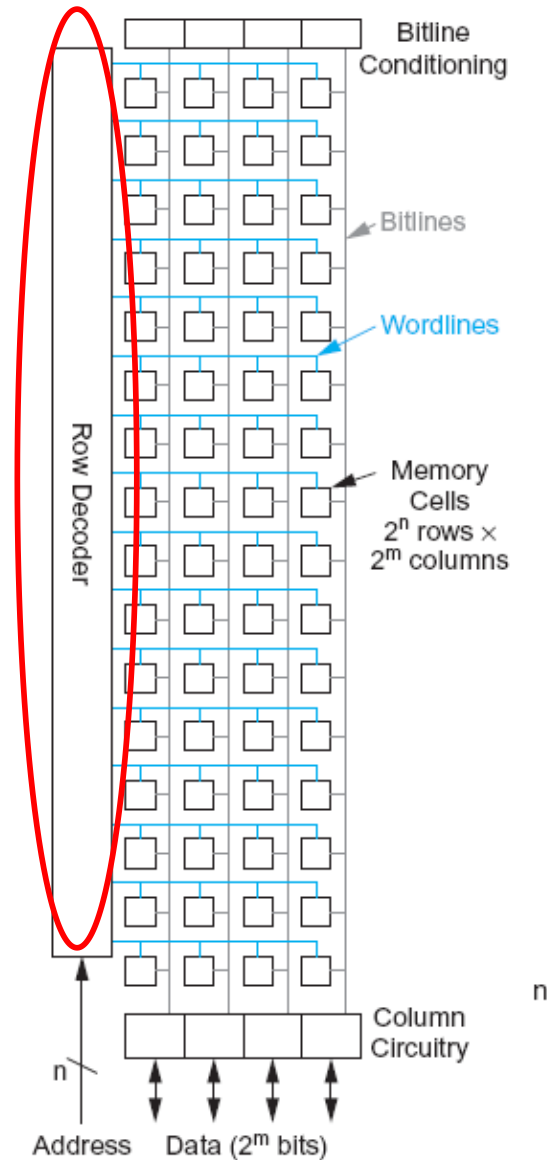
- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used



Decoders


- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates

Static CMOS

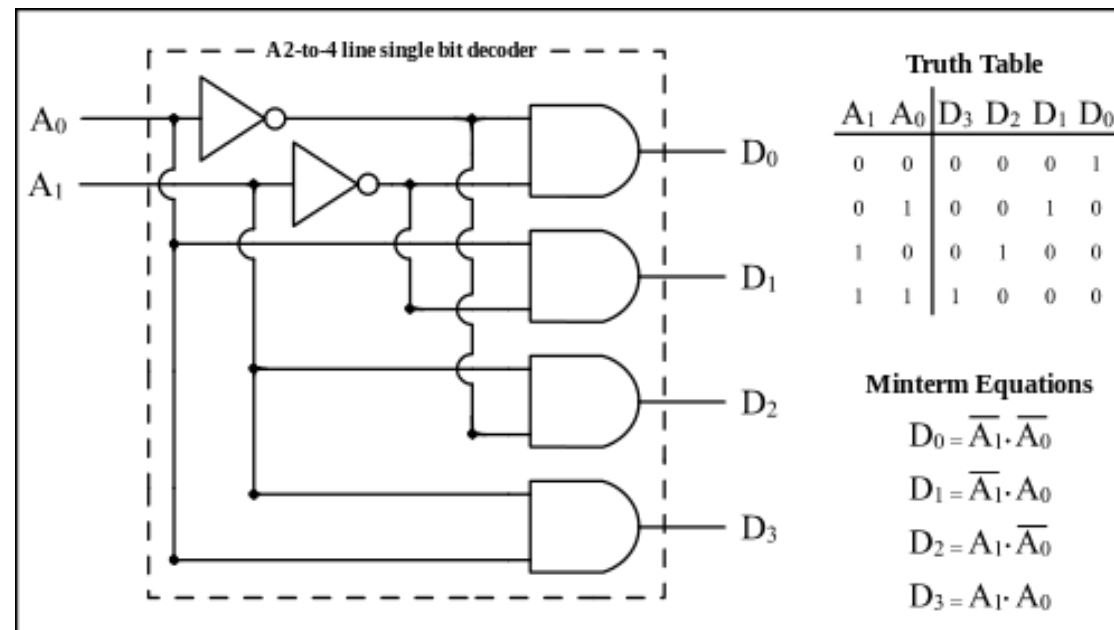


Large Decoders

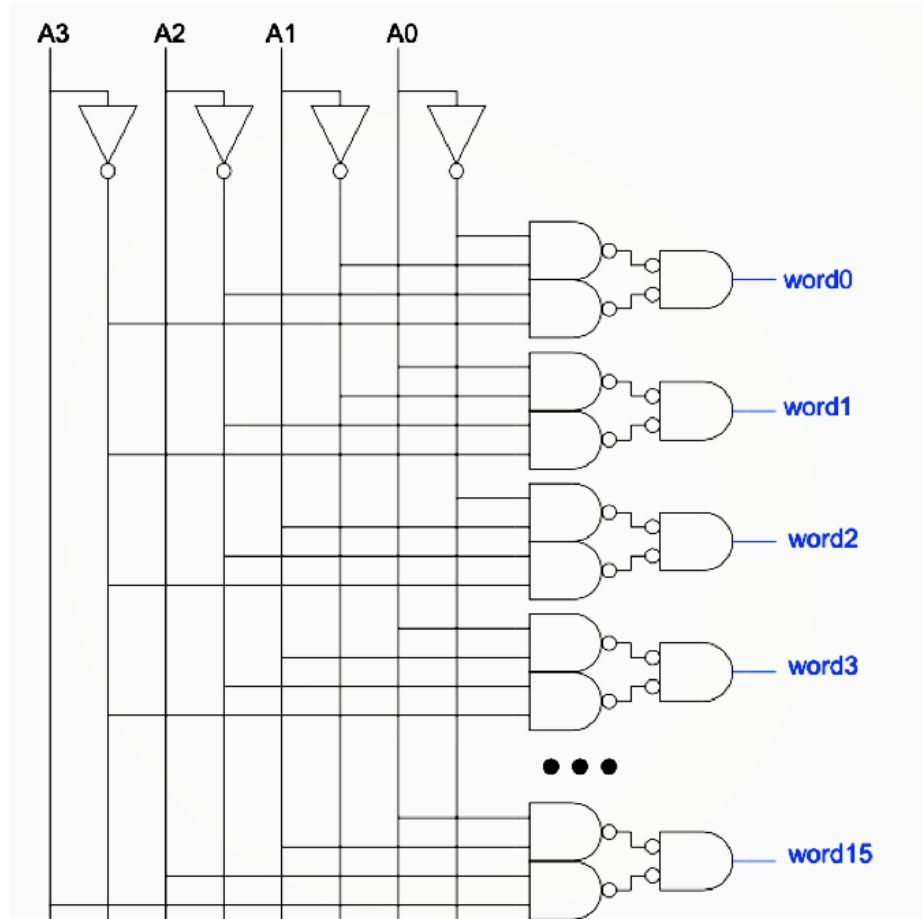- ❑ For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates




Large Decoders

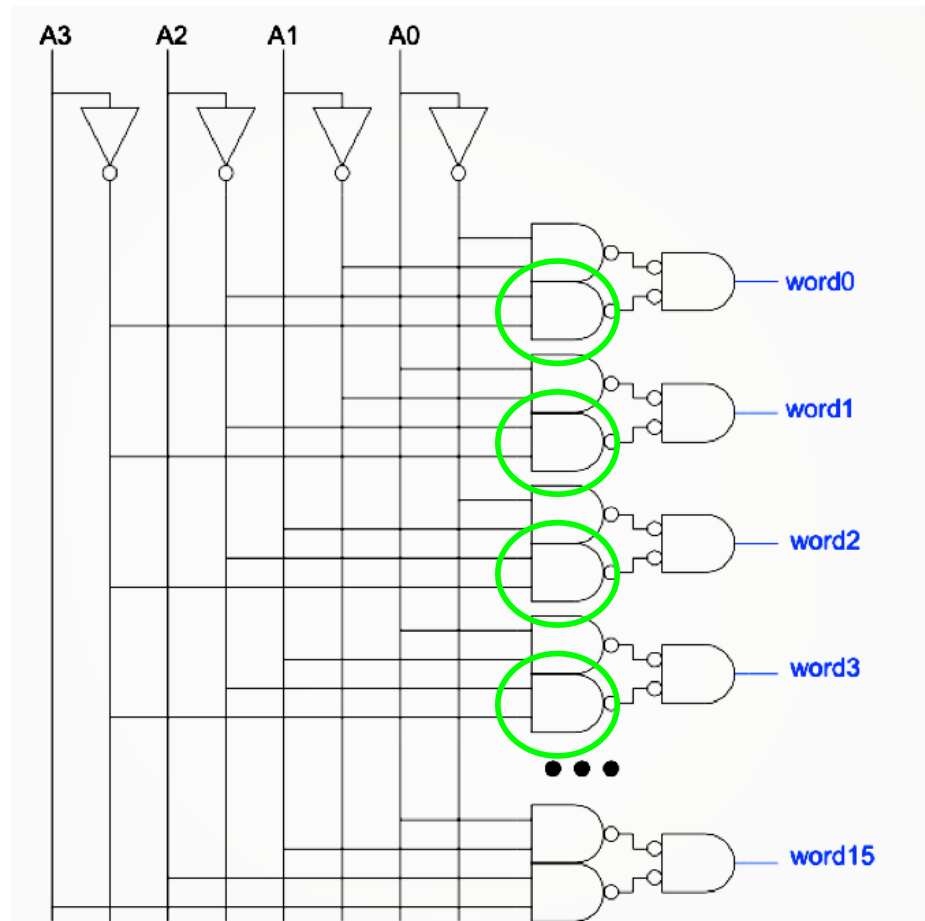- ❑ For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates




Predecoding

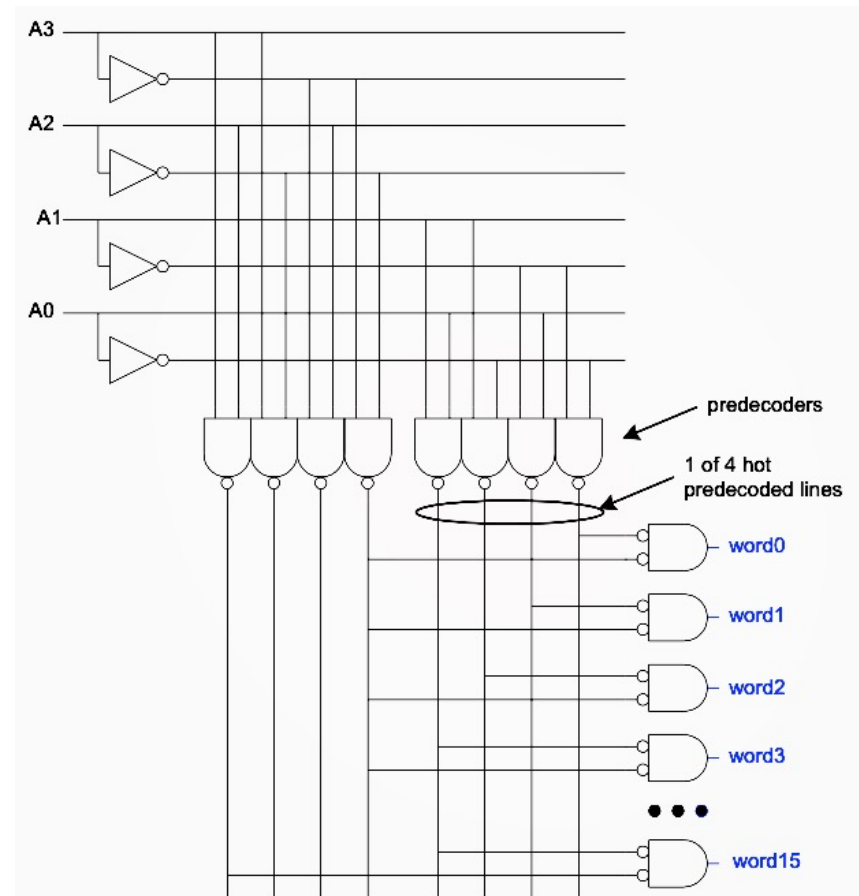
- ❑ Many of these gates are redundant
 - Factor out common gates into predecoder
 - Saves area
 - Same path effort




Row Select: Precharge NAND

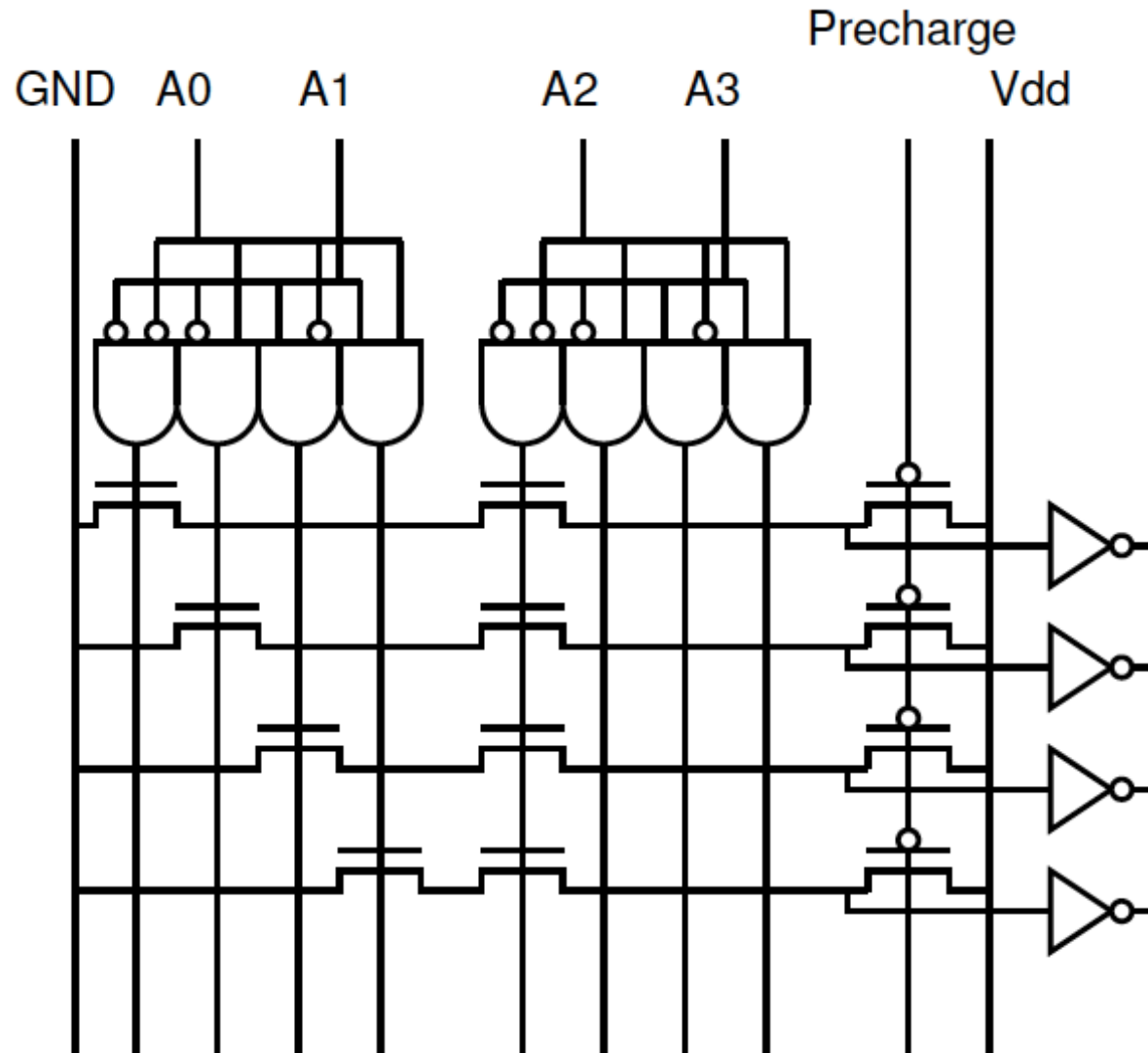

Row Select: Precharge NAND

 

Row Select: Precharge NOR

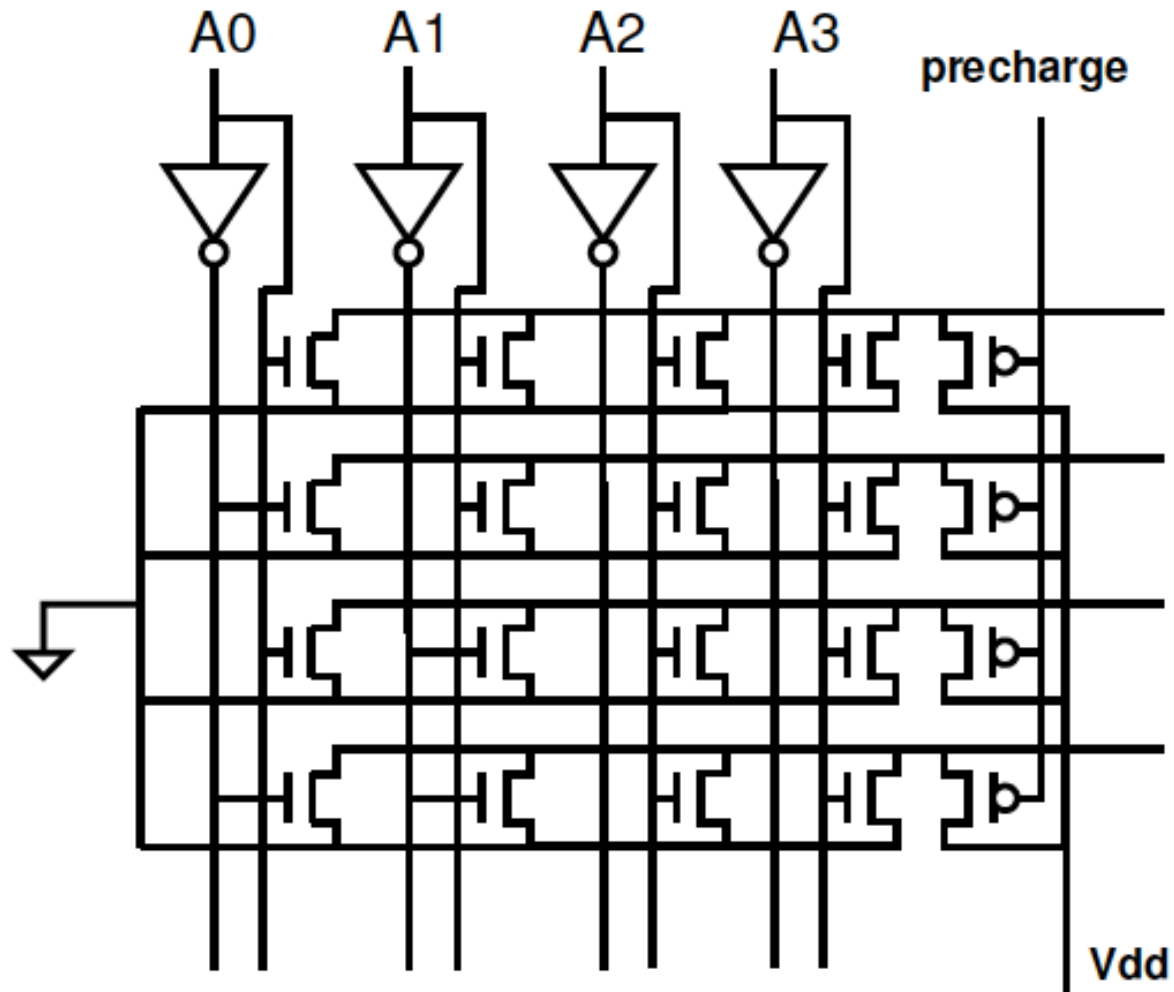


Column Circuitry

& Bit-line Conditioning




Array Architecture

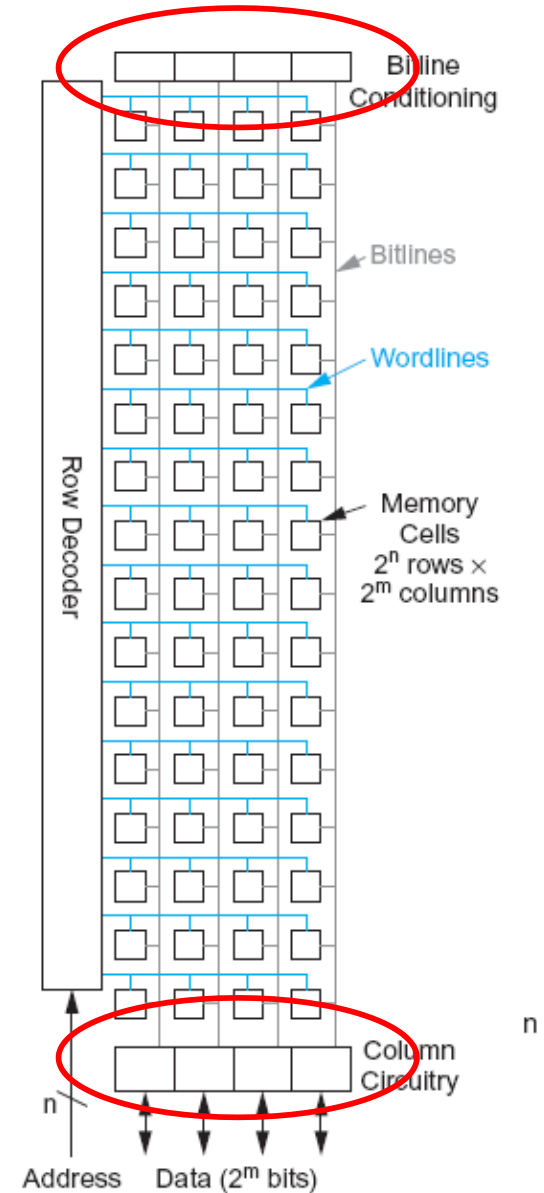- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used



6T SRAM Cell

 
- ❑ Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- ❑ 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- ❑ Read:
 - Precharge BL, BL'
 - Raise WL
- ❑ Write:
 - Drive data onto BL, BL'
 - Raise WL







Bitline Conditioning

 - ❑ Precharge bitlines high before read operations





Bitline Conditioning

- Precharge bitlines high before reads

  

Bitline Conditioning

- Precharge bitlines high before reads

 
 


- What if pre-charged to $V_{DD}/2$?
 - Pros: reduces read-upset
 - Challenge: generate $V_{DD}/2$ voltage on chip

Column Capacitance Consequence



□ Preclass 5: What is capacitance of a bitline?

  - W_{access} (pass transistor size), d rows, $\gamma = C_{\text{diff0}}/C_0$





Column Capacitance Consequence

 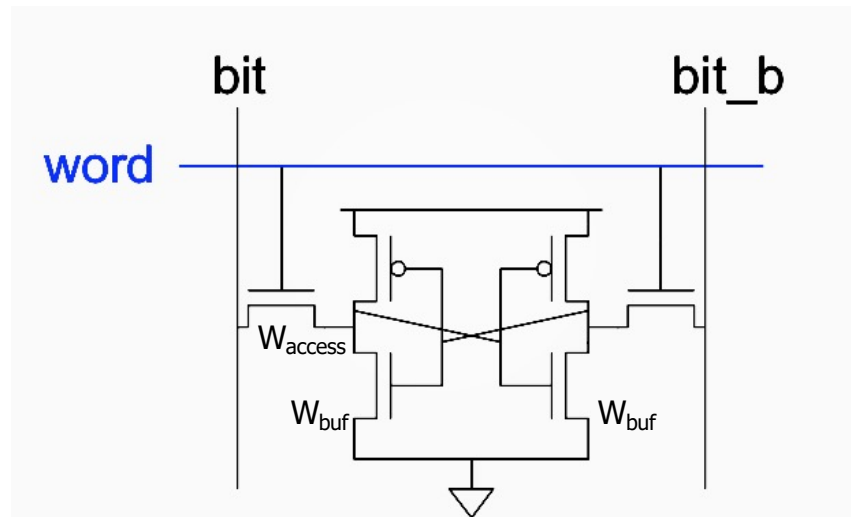- ❑ Preclass 5: What is capacitance of a bitline?
 - ❑ W_{access} (pass transistor size), d rows, $\gamma = C_{\text{diff0}}/C_0$
- ❑ Preclass 6: What is the delay for the cell to drive the bitline during a read?
 - ❑ W_{buf} (inverter size in cell), R_0





Column Capacitance Consequence

 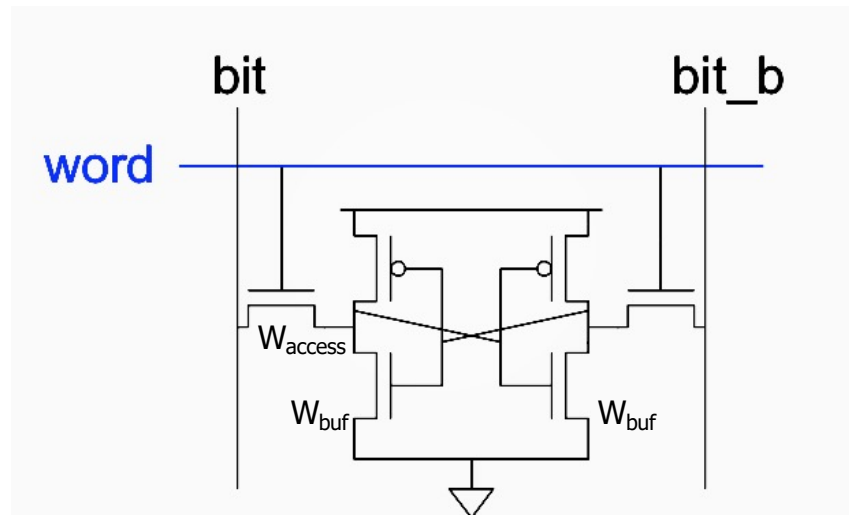- ❑ Preclass 5: What is capacitance of a bitline?
 - ❑ W_{access} (pass transistor size), d rows, $\gamma = C_{\text{diff0}}/C_0$
- ❑ Preclass 6: What is the delay for the cell to drive the bitline during a read?
 - ❑ W_{buf} (inverter size in cell), R_0
- ❑ Preclass 7: $W_{\text{access}} = W_{\text{buf}} = 1$, $\gamma = 1/2$
 - ❑ Delay for $d = 32, 512$?




Column Capacitance Consequence

 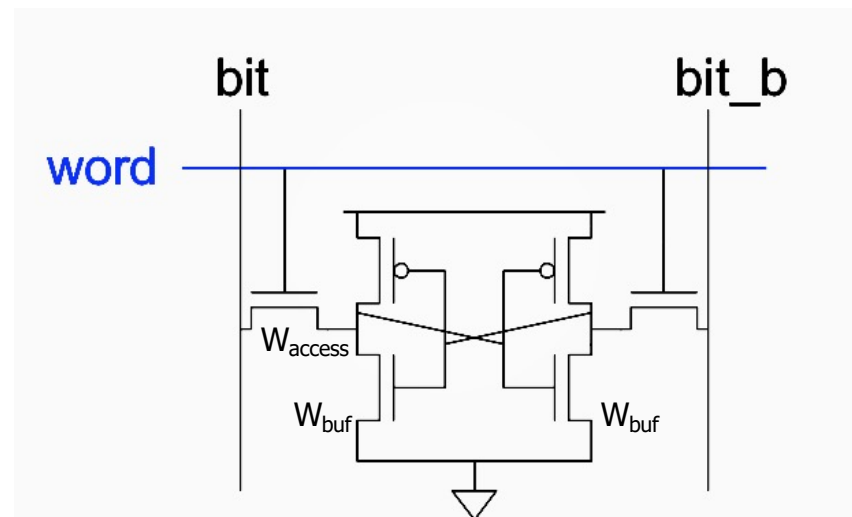- ❑ Preclass 5: What is capacitance of a bitline?
 - ❑ W_{access} (pass transistor size), d rows, $\gamma = C_{\text{diff0}}/C_0$
- ❑ Preclass 6: What is the delay for the cell to drive the bitline during a read?
 - ❑ W_{buf} (inverter size in cell), R_0
- ❑ **Conclude:** Can't size up cell \rightarrow driving bitline will be slow




Sense Amplifiers

 - Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 128 rows x 256 cols
 - 128 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors in each memory cell (small I)
- *Sense amplifiers* are triggered on small voltage swing (ΔV)




Differential Pair Amp

 - ❑ Differential pair requires no clock
- ❑ But always dissipates static power



Clocked Sense Amp

 - ❑ Clocked sense amp saves power
- ❑ Requires sense_clk after enough bitline swing
- ❑ Isolation transistors cut off large bitline capacitance





Word Line Capacitance

□ Preclass 8: What is capacitance of word line (row)?


- W_{access} – transistor width of column device
- w columns
- $\gamma = C_{\text{diff0}} / C_0$

□ Preclass 9: Delay driving word line?

- W_{wldrive} Drive inverter

 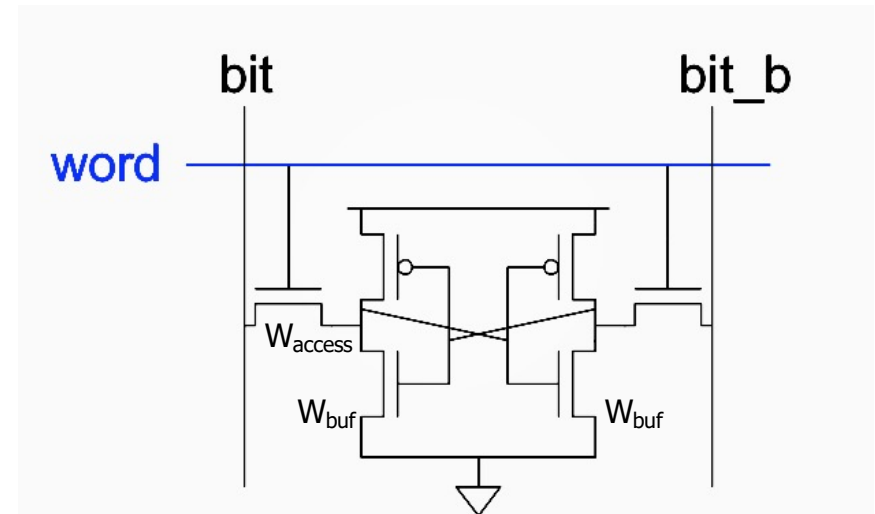


Column Drivers: Memory Bank

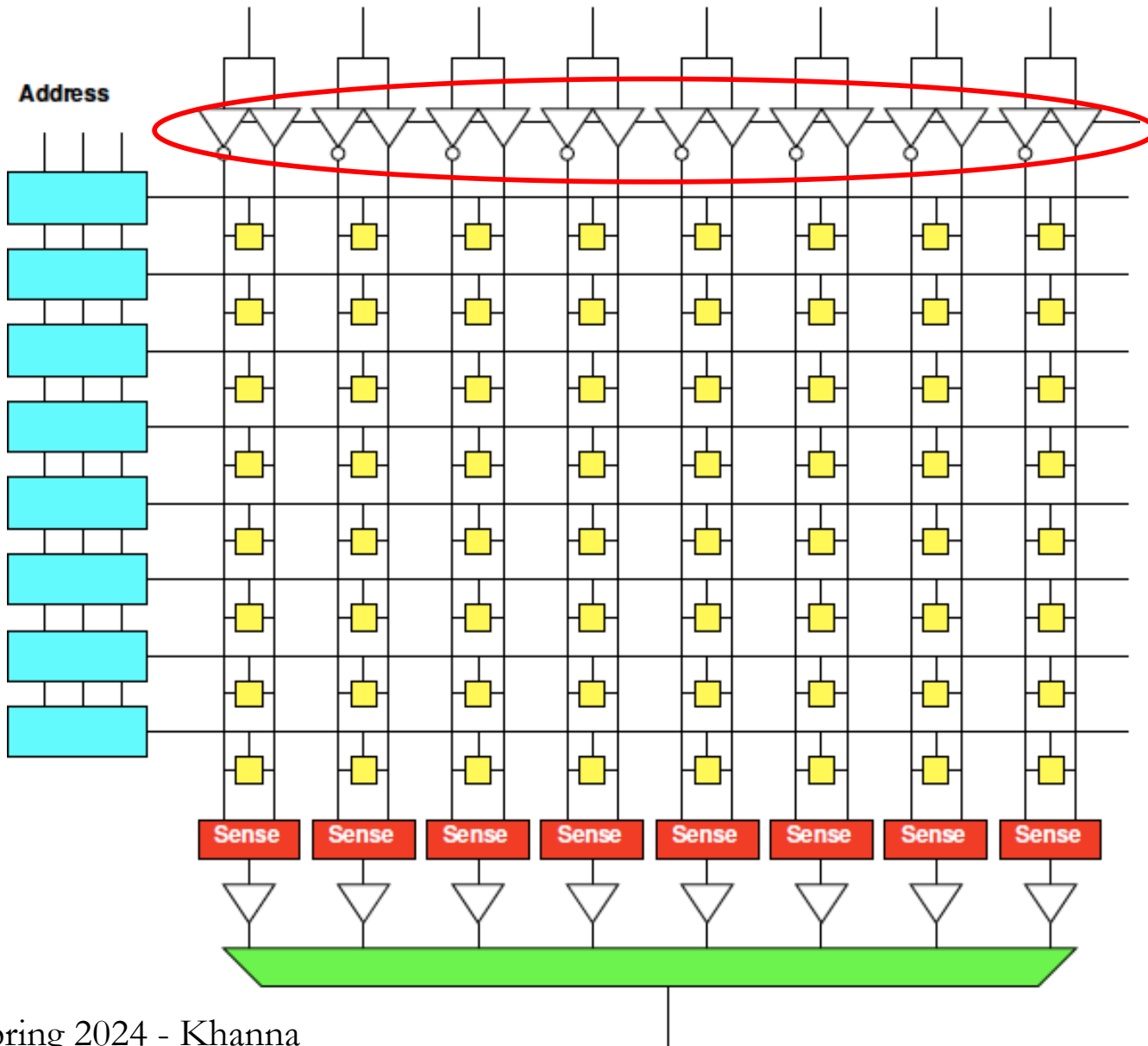

Tristate Buffer

 - ❑ Typically used for signal traveling, e.g. bus
- ❑ Ideally all devices connected to a bus should be disconnected except for active device reading or writing to bus
- ❑ Use high-impedance state to simulate disconnecting






Active-high buffer

Input	En	Ouptut
0	0	Z
1	0	Z
0	1	0
1	1	1






Tristate Buffer

   




Tristate Inverters

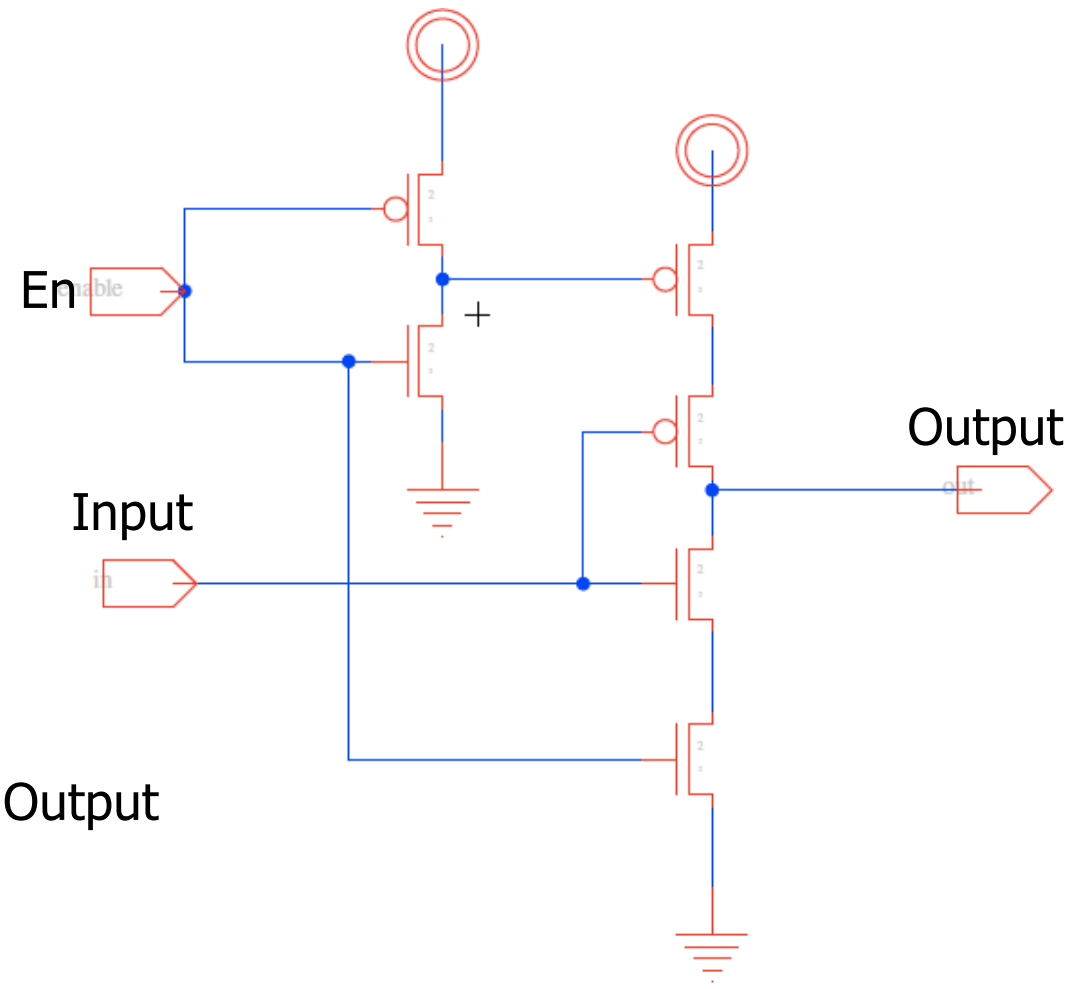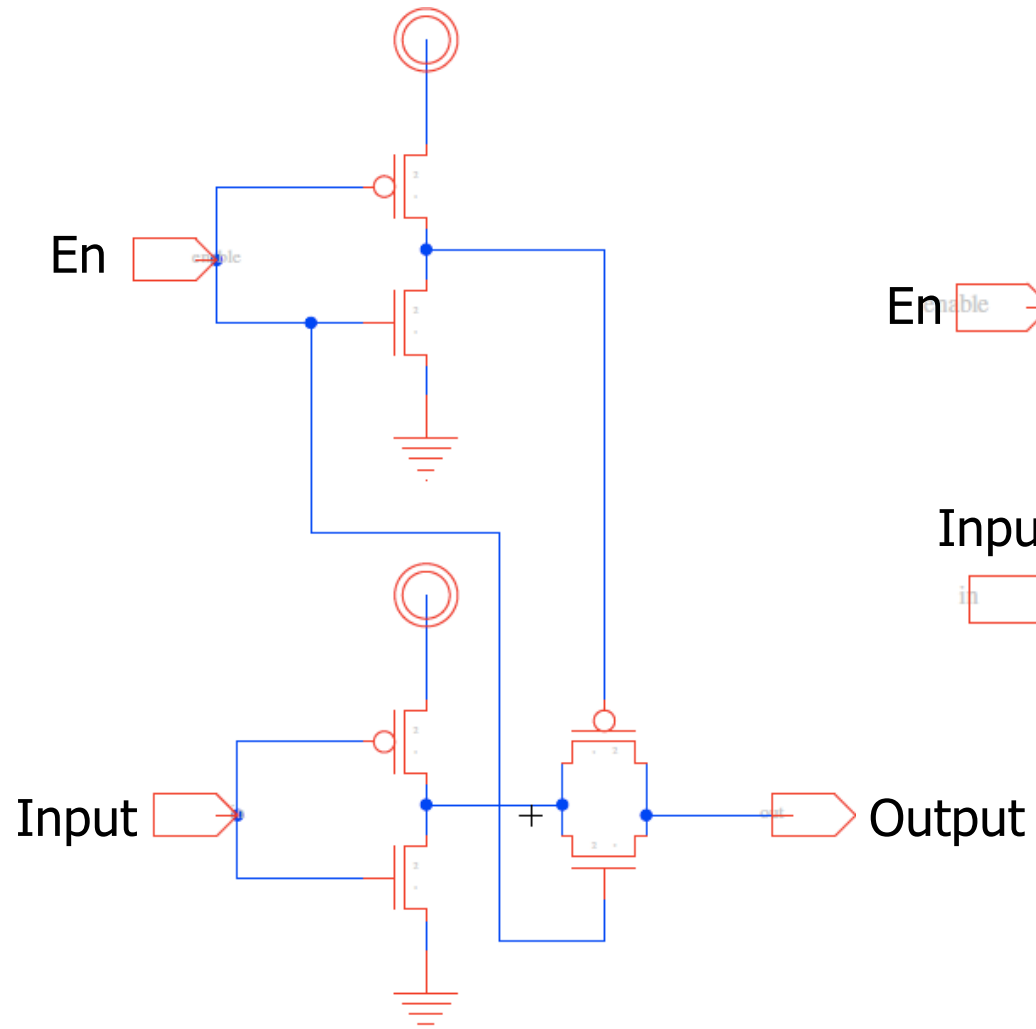 


Memory with column decoder


Size?

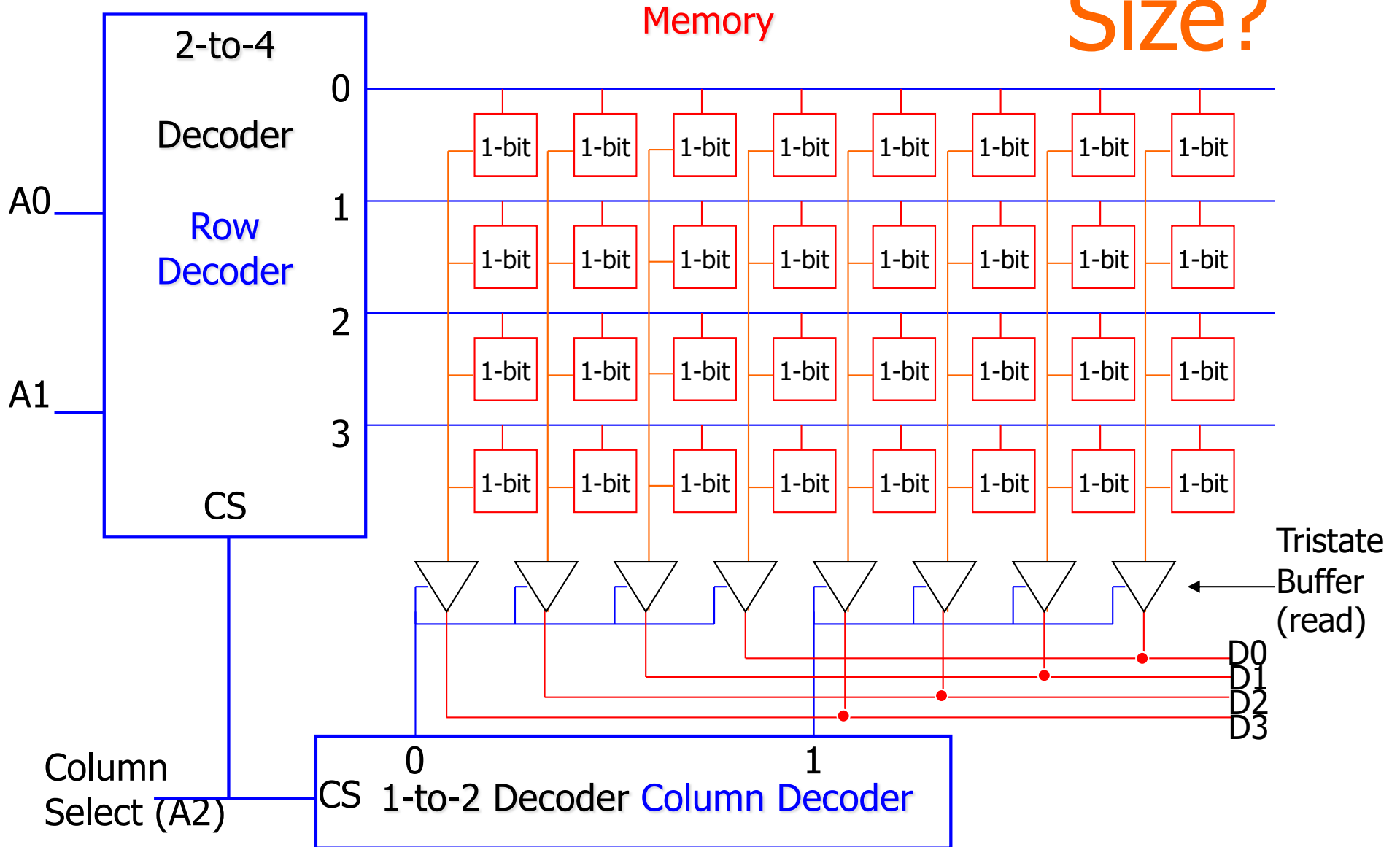


Read/Write Memory

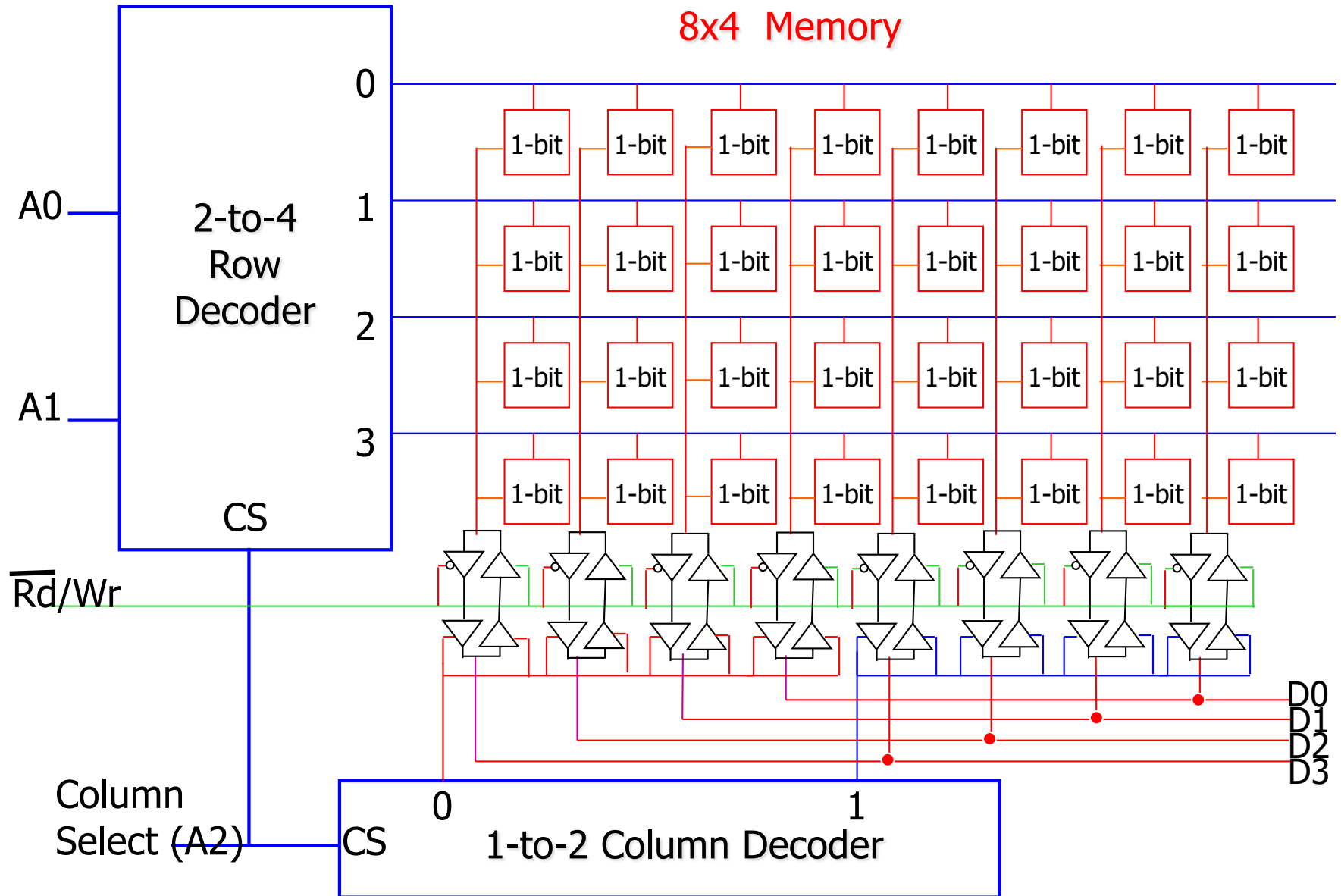

Read/Write Memory

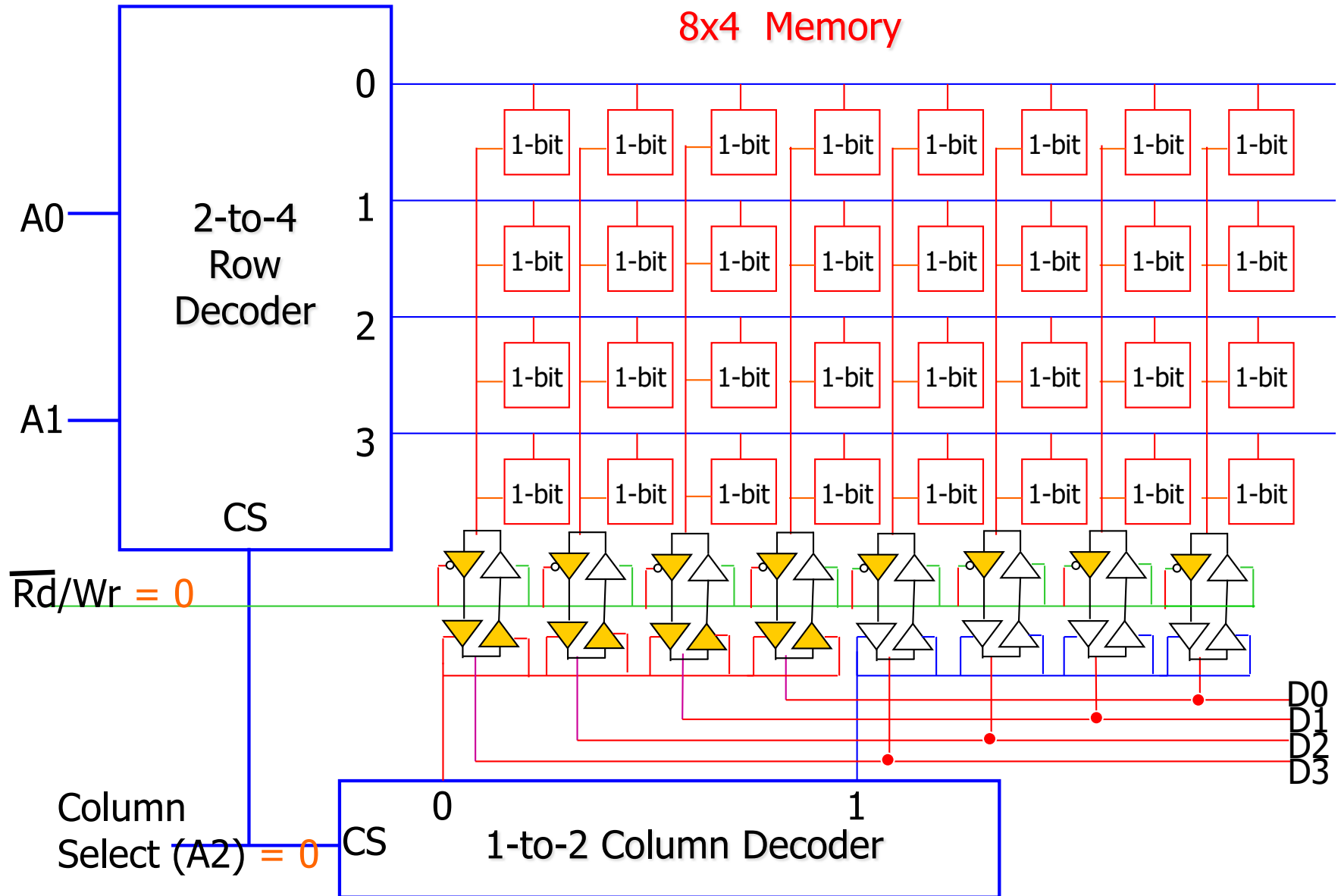

Read/Write Memory

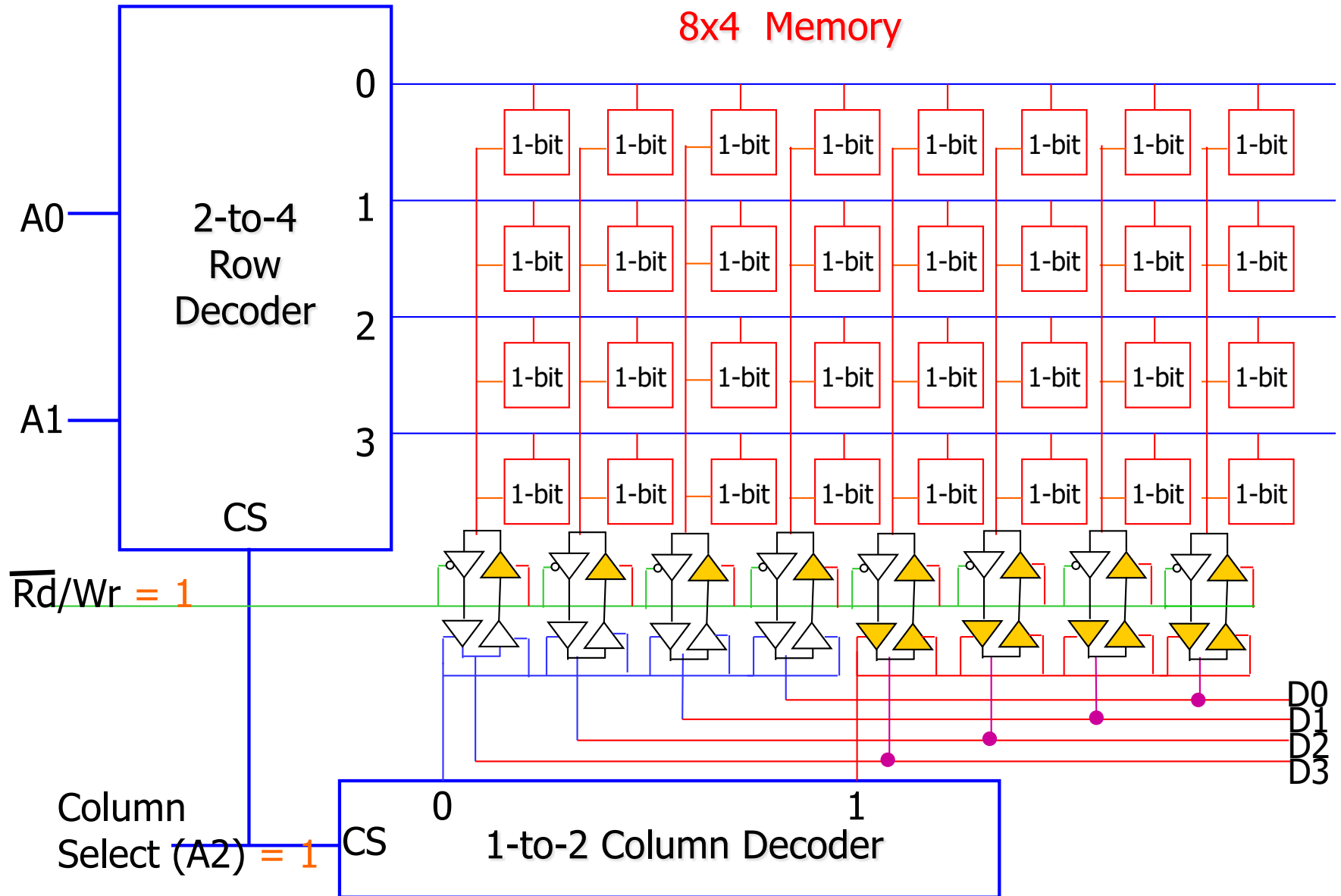




Serial Access Memories

- Serial access memories do not use an address
 - Serial In Parallel Out (SIPO)
 - Parallel In Serial Out (PISO)
 - Shift Registers
 - Queues (FIFO, LIFO)


Serial In Parallel Out

 - 1-bit shift register reads in serial data
 - After N steps, presents N -bit parallel output




Parallel In Serial Out

 - Load all N bits in parallel when $\text{shift} = 0$
 - Then shift one bit out per cycle




Shift Register

 - ❑ *Shift registers* store and delay data
- ❑ Simple design: cascade of registers




Denser Shift Registers

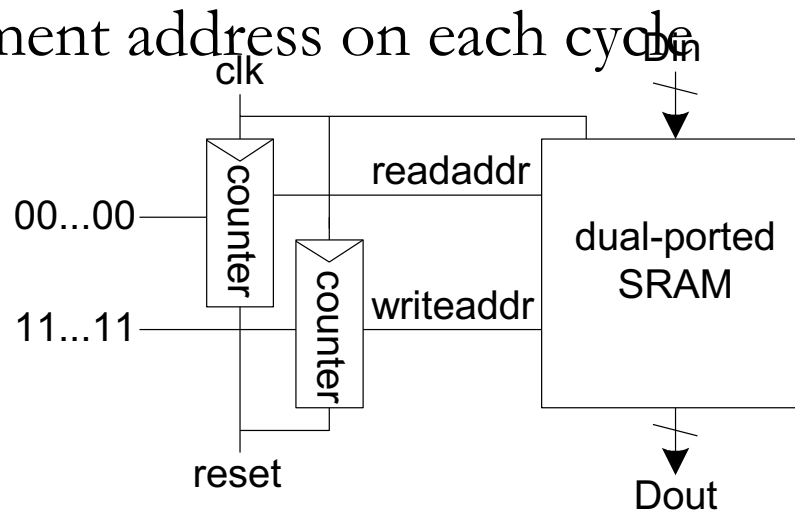- ❑ Flip-flops aren't very area-efficient
- ❑ For large shift registers, keep data in SRAM instead
- ❑ Move read/write pointers to RAM rather than move data
 - Initialize read address to first entry, write to last
 - Increment address on each cycle



Queues

 - ❑ *Queues* allow data to be read and written at different rates.
- ❑ Read and write each use their own clock, data
- ❑ Queue indicates whether it is full or empty
- ❑ Build with SRAM and read/write counters (pointers) storing read/write address





FIFO, LIFO Queues

- ❑ *First In First Out* (FIFO)
 - Initialize read and write pointers to first element
 - Queue is EMPTY
 - On write, increment write pointer
 - If write almost catches read, Queue is FULL
 - On read, increment read pointer
 - If read catches write, Queue is EMPTY
- ❑ *Last In First Out* (LIFO)
 - Also called a *stack*
 - Use a single *stack pointer* for read and write



Idea

- ❑ Memory for compact state storage
- ❑ Minimize area of repeated cell
 - 6T/5T SRAM
 - Muiltport trade off area for function
 - 1T/3T DRAM helps but slower
- ❑ Share circuitry across many bits
 - Minimize area per bit → maximize density
- ❑ Aggressively use:
 - Pass transistors, Ratioing
 - Precharge, Amplifiers to keep area down



Admin

- ❑ Homework 7
 - Come to lab 4/22 and turn in worksheet for credit
- ❑ Project 2 out now
 - Design SRAM array
 - Work in teams of up to two
 - Milestone due F 4/19
 - Will get feedback from me by M 4/22
 - Final report due Wednesday 5/1



Acknowledgement

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Jing Li (University of Pennsylvania)