

 


- Initially: The switch is open and node A is charged to 1V and node B is charged to 0V.

 What is the voltage at node A in steady state after the switch is closed?





 - What is the waveform on A after WL transitions from 0 to 1?



Assume BL initially at 0. How does it depend on W_{access} ?

  - What is the waveform on A after WL transitions from 0 to 1?




Assume:

- BL initially at 0
- A initially at 1

How does it depend on W_{access} ?

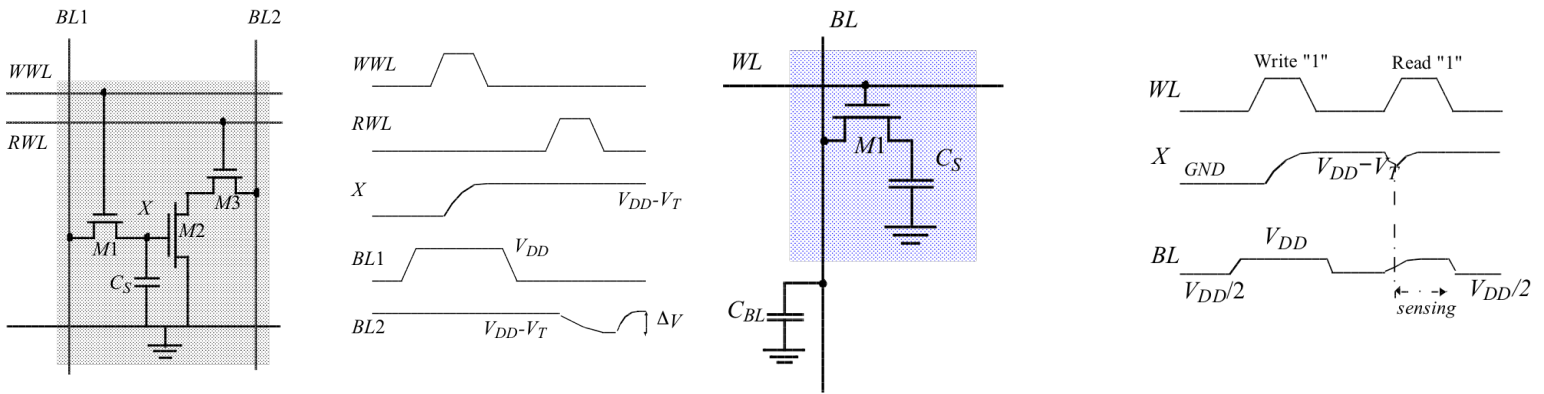4. Below is the 3T DRAM and 1T DRAM cell with waveform for writing a '1' into the cell and then reading the cell.



5. What is capacitance of the bit line? In terms of access transistor width W_{access} , number of words on bit line, d , γ , and C_0 .

6. Delay of memory cell driving bit line? (Read operation) In terms of variables above plus buffer size, W_{buf} , and R_0 .

7. Concrete delay for $W_{access} = W_{buf} = 1$, $\gamma = 0.5$? In terms of $\tau = R_0 C_0$.

Unit	Delay in τ
d=32 (register file)	
d=512 (BRAM or small L1 Cache)	

8. What is the capacitance of the word line? In terms of access transistor width W_{access} , number of bits on the word line, w , γ , and C_0 .

9. Delay driving word line, assuming driven by a driver with equivalent drive strength to W_{wdrive} inverter? (other parameters as above)