

ESE3700: Circuit-Level Modeling, Design and Optimization for Digital Systems

Lec 20: April 24, 2024

Inductive Noise and Crosstalk





Today


- ❑ Inductive Responses
- ❑ Calculating L
- ❑ Where inductances show up
- ❑ Impact of inductance on digital circuits
- ❑ How to address inductive noise

LC Response (preclass 1)

□ What happens here?

$$L \frac{dI_L}{dt} = V_L$$

$$I_C = C \frac{dV_C}{dt}$$

 

LC Response


□ What happens here?

$$L \frac{dI_L}{dt} = V_L \quad I_C = C \frac{dV_C}{dt}$$

$$L \frac{dI}{dt} + V_2 = V_S$$

$$I = C \frac{dV_2}{dt} \Rightarrow \frac{dI}{dt} = C \frac{d^2V_2}{dt^2}$$

$$LC \frac{d^2V_2}{dt^2} + V_2 = V_S$$

 


LC Response

□ What happens here?

$$\omega = \sqrt{\frac{1}{LC}}$$

$$V_2 = A + Be^{j\omega t}$$

 
$$V_2 = V + Be^{j\left(\sqrt{\frac{1}{LC}}\right)t}$$



$$e^{j\theta} = \cos(\theta) + j\sin(\theta)$$




LC Response

 




Response? (preclass 1)

 

RLC Response

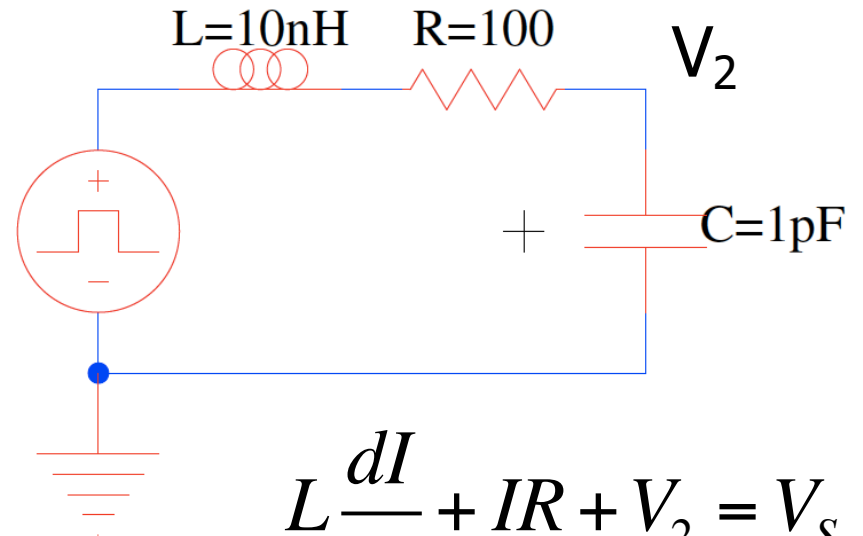

$$L \frac{dI}{dt} + IR + V_2 = V_S$$


$$I = \frac{CdV_2}{dt}$$

RLC Response

$$V_2 = A + Be^{j\omega t}$$

$$\frac{dV_2}{dt} = j\omega Be^{j\omega t}$$
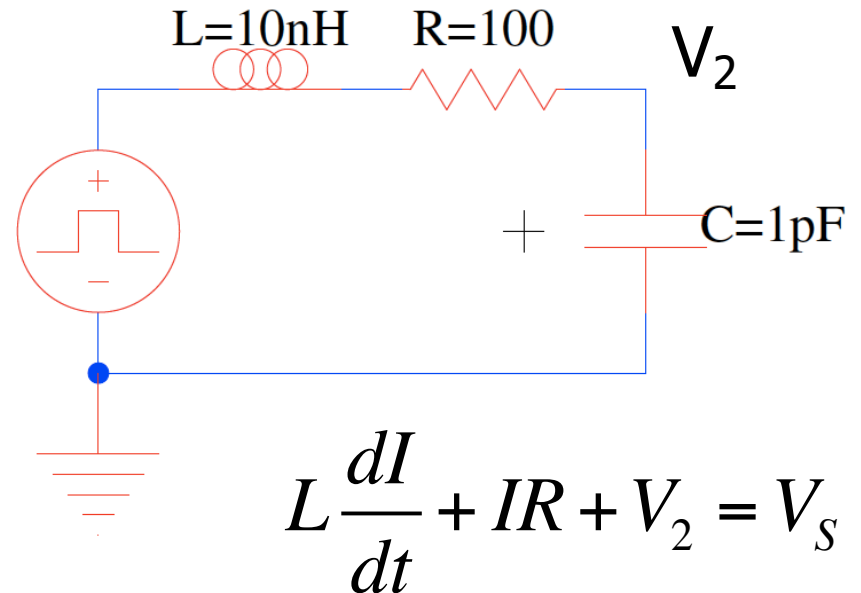
$$\frac{d^2V_2}{dt^2} = -\omega^2 Be^{j\omega t}$$



$$LC \left(\frac{d^2V_2}{dt^2} \right) + RC \left(\frac{dV_2}{dt} \right) + V_2 = V_S$$


$$LC \left(-\omega^2 Be^{j\omega t} \right) + RC \left(j\omega Be^{j\omega t} \right) + A + Be^{j\omega t} = V_S$$

RLC Response

$$V_2 = A + Be^{j\omega t}$$

$$\frac{dV_2}{dt} = j\omega Be^{j\omega t}$$
 
$$\frac{d^2V_2}{dt^2} = -\omega^2 Be^{j\omega t}$$



$$LC(-\omega^2 Be^{j\omega t}) + RC(j\omega Be^{j\omega t}) + A + Be^{j\omega t} = V_S$$

$$A = V_S$$

$$LC(-\omega^2) + RC(j\omega) + 1 = 0$$


RLC Response

$$LC(-\omega^2) + RC(j\omega) + 1 = 0$$

$$\omega^2 - j\omega \frac{R}{L} - \frac{1}{LC} = 0$$

$$\omega = \frac{j \frac{R}{L} \pm \sqrt{\left(-j \frac{R}{L}\right)^2 + \frac{4}{LC}}}{2}$$
 
$$\omega = j \frac{R}{2L} \pm \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$




RLC Response

$$LC(-\omega^2) + RC(j\omega) + 1 = 0$$

$$\omega^2 - j\omega \frac{R}{L} - \frac{1}{LC} = 0$$

$$\omega = \frac{j \frac{R}{L} \pm \sqrt{\left(-j \frac{R}{L}\right)^2 + \frac{4}{LC}}}{2}$$
 
$$\omega = j \frac{R}{2L} \pm \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$



$$V_2 = V_S + B e^{j \left(j \frac{R}{2L} \pm \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \right) t}$$


$$V_2 = V_S + B e^{\left(-\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \right) t}$$

$$V_2 = V_S + B e^{\left(-\frac{R}{2L} \right) t} e^{j \left(\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \right) t}$$

RLC Response (preclass 2)


$$V_2 = V_S + Be^{\left(-\frac{R}{2L}\right)t} e^{\left(j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}\right)t}$$

 - For what R does this circuit oscillate?



RLC Response
 
$$V_2 = V_S + B e^{\left(-\frac{R}{2L}\right)t} e^{\left(j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}\right)t}$$



- For what R does this circuit oscillate?


$$\frac{1}{LC} - \left(\frac{R}{2L}\right)^2 > 0$$

$$\frac{1}{LC} > \left(\frac{R}{2L}\right)^2 \Rightarrow \sqrt{\frac{4L}{C}} > R$$

RLC Response

$$V_2 = V_S + B e^{\left(-\frac{R}{2L}\right)t} e^{j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}t}$$

Decay	Oscillation
-------	-------------

 


□ For what R does this circuit oscillate?

$$\frac{1}{LC} - \left(\frac{R}{2L}\right)^2 > 0$$

$$\frac{1}{LC} > \left(\frac{R}{2L}\right)^2 \Rightarrow \sqrt{\frac{4L}{C}} > R$$

When Oscillate

 
- For what R does this particular circuit oscillate?



When Oscillate

- For what R does this particular circuit oscillate?

$$R < \sqrt{\frac{4L}{C}}$$

 


$$\sqrt{\frac{4L}{C}} = 200$$




RLC Response ($R=100$)

RLC Step Response

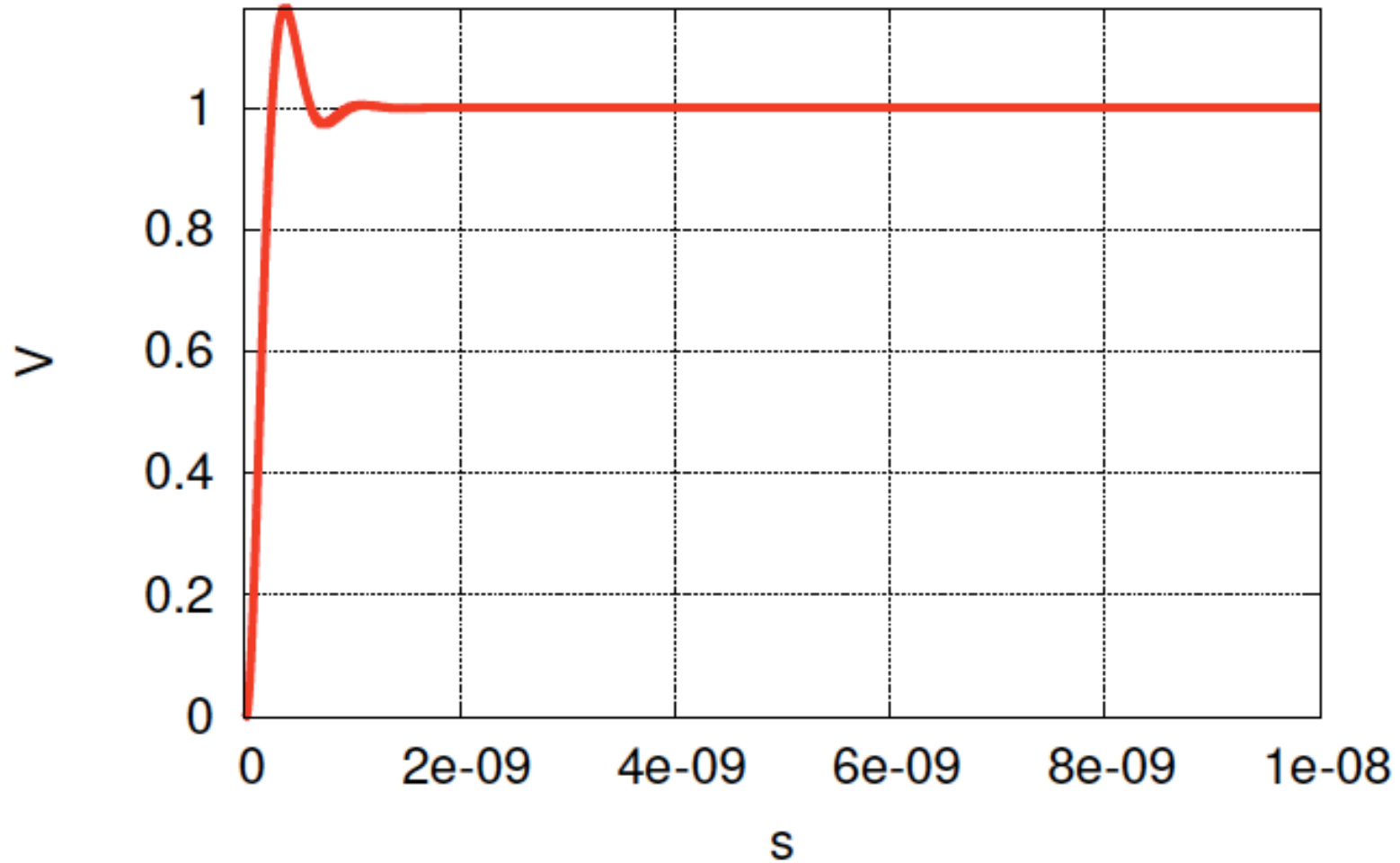



RLC Response

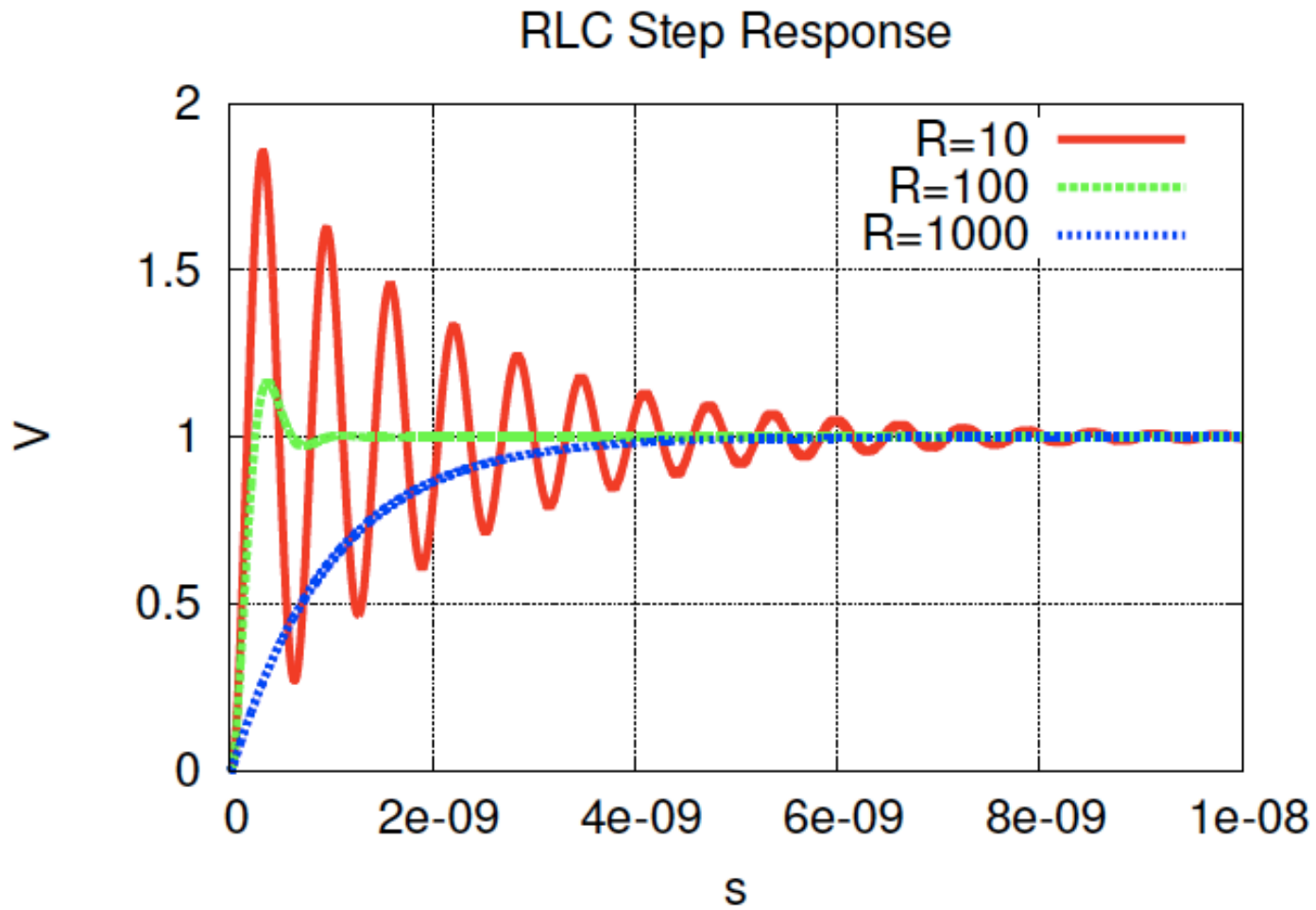


Inductance of Wire




Isolated Wire RC


$$R = \frac{\rho L}{A}$$

 

$$C = \epsilon_d \frac{A}{d}$$

 


Inductance: Wire over Ground Plane

 

$$L \approx l \left(\frac{\mu_0 \mu_r h}{w} \right)$$

Inductance: Wire over Ground Plane

 

$$L \approx l \left(\frac{\mu_0 \mu_r h}{w} \right)$$

$$C = \epsilon_r \epsilon_0 \frac{A}{d} = \epsilon_r \epsilon_0 \frac{wl}{h} = l \left(\epsilon_r \epsilon_0 \frac{w}{h} \right)$$

Inductance: Wire over Ground Plane

$$C' = \epsilon_r \epsilon_0 \frac{w}{h} \quad L' \approx \left(\frac{\mu_0 \mu_r h}{w} \right)$$

$$C' L' = \epsilon \mu$$

C' and L' per unit length

$$L' = \frac{\epsilon \mu}{C'}$$



On Chip Inductance

- ❑ $C_{\text{wire}} = 0.16 \text{ pF}$ (for the 1mm)
- ❑ $C_{\text{wire}} = 0.16 \text{ nF/m}$

- ❑ Permeability $\mu_0 \approx \mu_{\text{SiO}_2} = 12.6 \cdot 10^{-7} \text{ H/m}$
- ❑ Permittivity $\epsilon_{\text{ox}} = 3.5 \cdot 10^{-11} \text{ F/m}$

$$L' = \frac{\epsilon \mu}{C'}$$

On Chip Inductance

- ❑ $C_{\text{wire}} = 0.16 \text{ pF}$ (for the 1mm)
- ❑ $C_{\text{wire}} = 0.16 \text{ nF/m}$
- ❑ Permeability $\mu_0 \approx \mu_{\text{SiO}_2} = 12.6 \cdot 10^{-7} \text{ H/m}$
- ❑ Permittivity $\epsilon_{\text{ox}} = 3.5 \cdot 10^{-11} \text{ F/m}$
- ❑ 276 pH (for 1 mm)

$$L' = \frac{\epsilon \mu}{C'}$$

PCB Trace Inductance (preclass 3)

- Inductance per cm of PCB trace with $h=3\text{mil}$,
 $w=5\text{mil}$ (1mil = .001 inch)

- $\mu_0 = 1.26 \times 10^{-6}$

- $\mu_r = 1$

$$L \approx l \left(\frac{\mu_0 \mu_r h}{w} \right)$$




Comparisons

- ❑ 5mil trace on PCB
 - 7.56nH/cm
- ❑ Breadboard wires (0.6mm diameter)
 - About 7nH/cm
- ❑ On chip wire
 - $0.28\text{nH/mm} = 2.8\text{nH/cm}$

Inductors

 - ❑ Bond pads
- ❑ Package leads
- ❑ Long wire runs
- ❑ Cables



Src: <http://en.wikipedia.org/wiki/File:Wirebonding2.svg>


Where Inductance Arises

In our digital systems







Signal Path

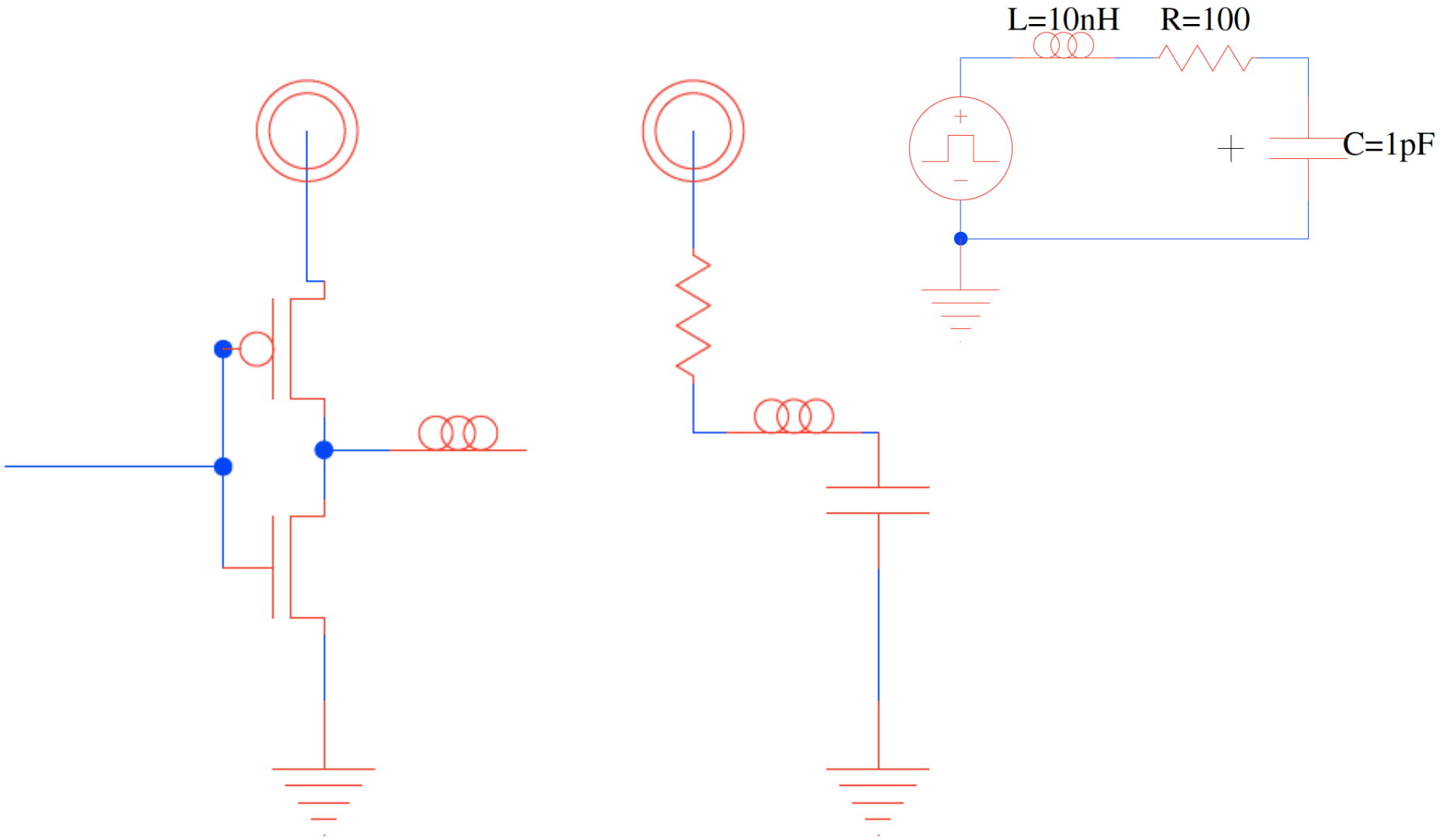




Power Ground

  

Shared Power/Ground Example: 74x04

 

Estimate

- R_{eq}, C_{eq} for gates in parallel
 - $R_0 = 25K \Omega$
 - $C_0 = 0.01 \text{ fF}$
 - say $10C_0=0.1\text{fF}$ for typical load
- 250 gates switching at clock

Decay	Oscillation
$e^{\left(-\frac{R}{2L}\right)t}$	$e^{\left(j\sqrt{\frac{1}{LC}-\left(\frac{R}{2L}\right)^2}\right)t}$

$$V_2 = V_S + B$$

Estimate


- ❑ R_{eq}, C_{eq} for gates in parallel
 - $R_0 = 25K \Omega$
 - $C_0 = 0.01 \text{ fF}$
 - say $10C_0=0.1\text{fF}$ for typical load
- ❑ 250 gates switching at clock
- ❑ $R_{eq} = 100\Omega$ $C_{eq}=25\text{fF}$
- ❑ Assume $L=1\text{nH}$
- ❑ How long to settle? Oscillation freq?

$$V_2 = V_S + B e^{\left(-\frac{R}{2L}\right)t} e^{\left(j\sqrt{\frac{1}{LC}-\left(\frac{R}{2L}\right)^2}\right)t}$$



Decay	Oscillation
-------	-------------



Power Ground

 


RLC Response

  

Today's chips: Multiple Power/Ground Pins

- Use many power/ground pins

 

- Divide switching gates by pins
 - To get effective load on each pin

Improve Performance







Minimize the L

- ❑ Make wires short
- ❑ Use power and ground planes
 - Think of power plane as a very wide wire

$$L \approx l \left(\frac{\mu_0 \mu_r h}{w} \right)$$


Flip Chip, Area IO

  


http://www.izm.fraunhofer.de/en/abteilungen/high_density_interconnectwaferlevelpackaging/arbeitsgebiete/arbeitsgebiet1

Add Good C's

 
- Bypass Capacitors – inside the inductances
 - On board
 - On package
 - On chip




Bypass Capacitor Example

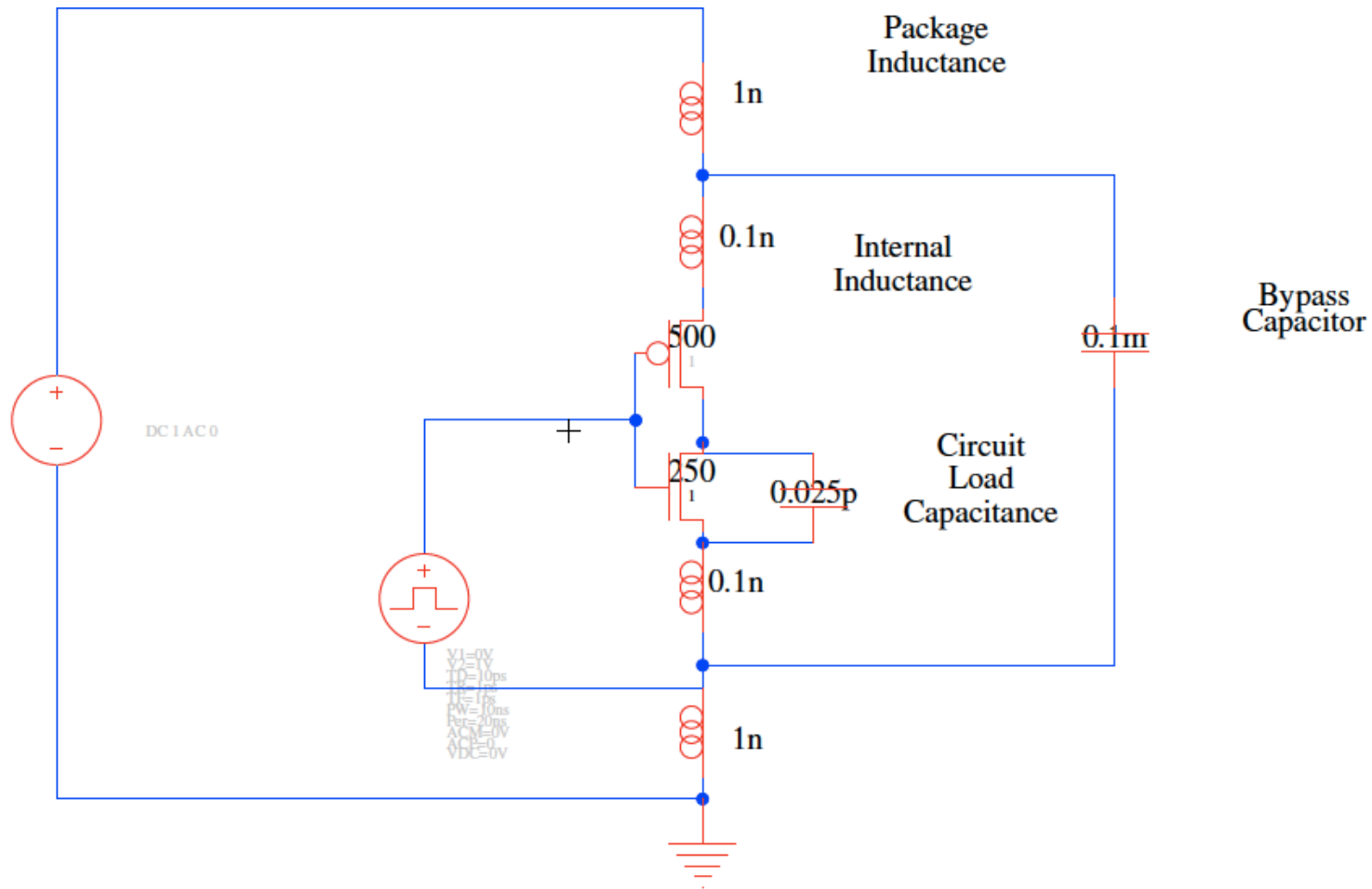


Bypass Capacitor Example

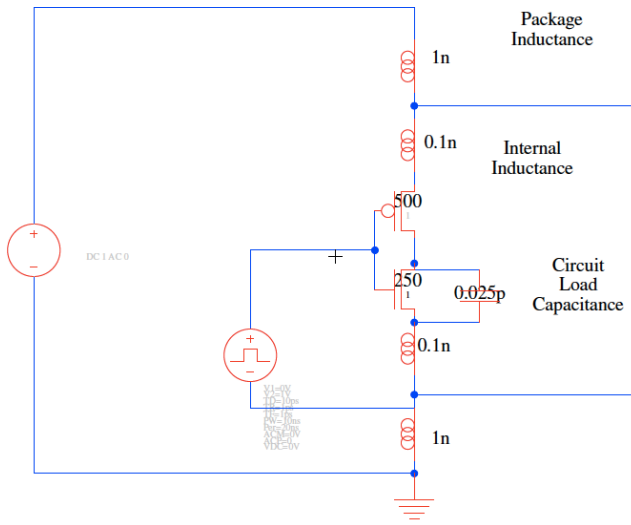

No bypass cap

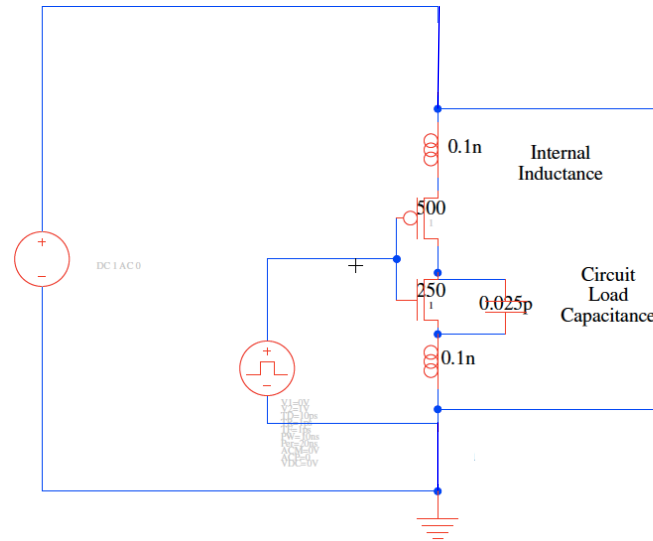


No package inductance

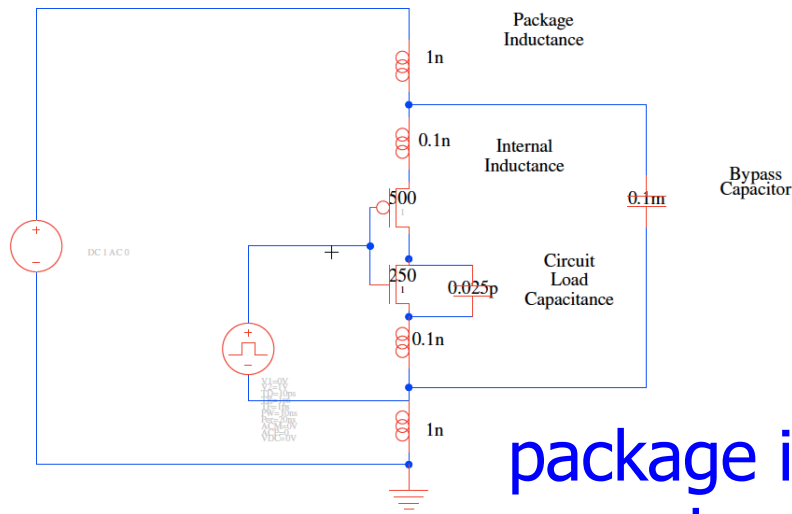

package inductance w/
bypass cap


Bypassed Supplies (@ transistor)

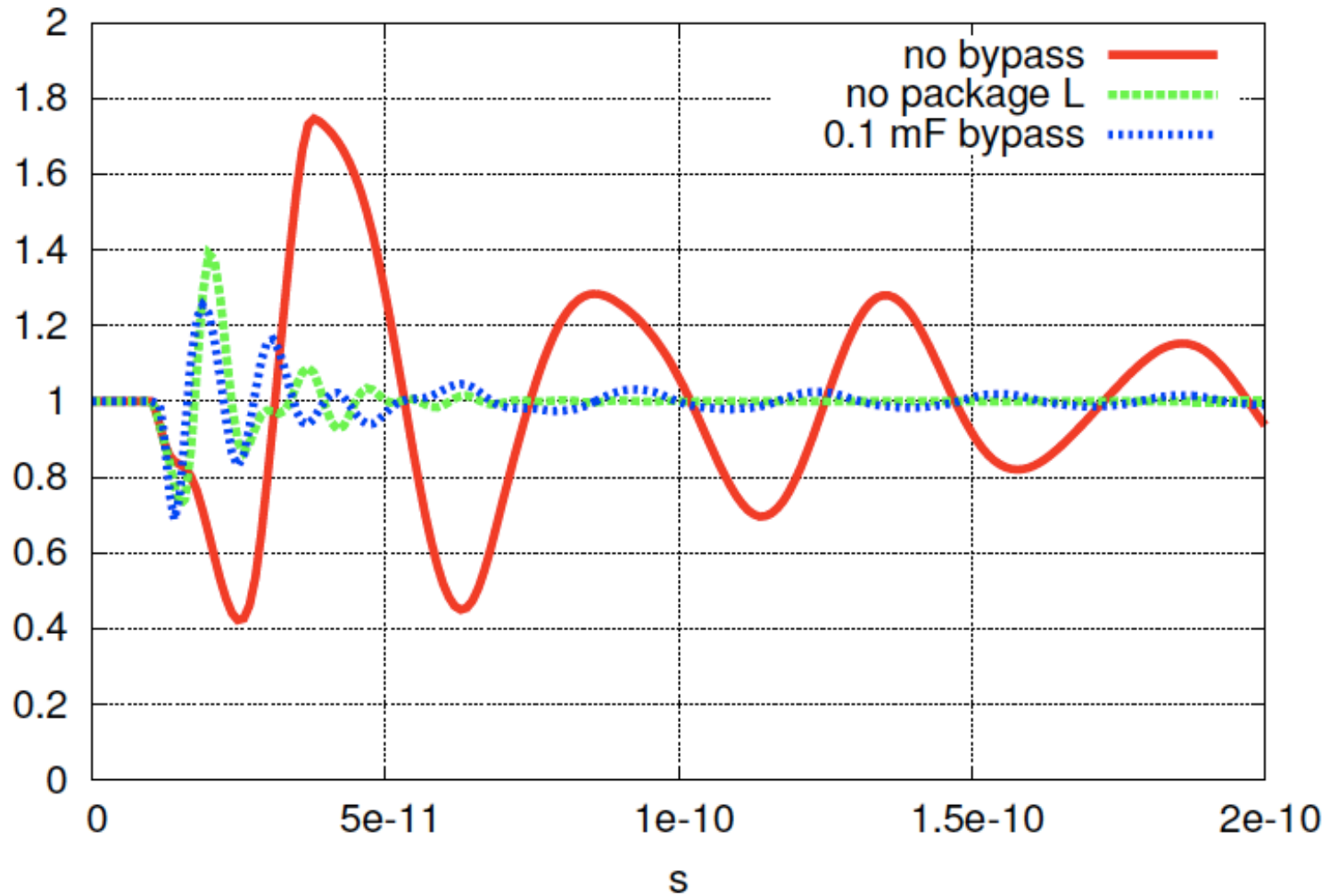*** spice deck for cell model_nobypass{sch} from library test





Bypassed Output

 


Crosstalk




Capacitance

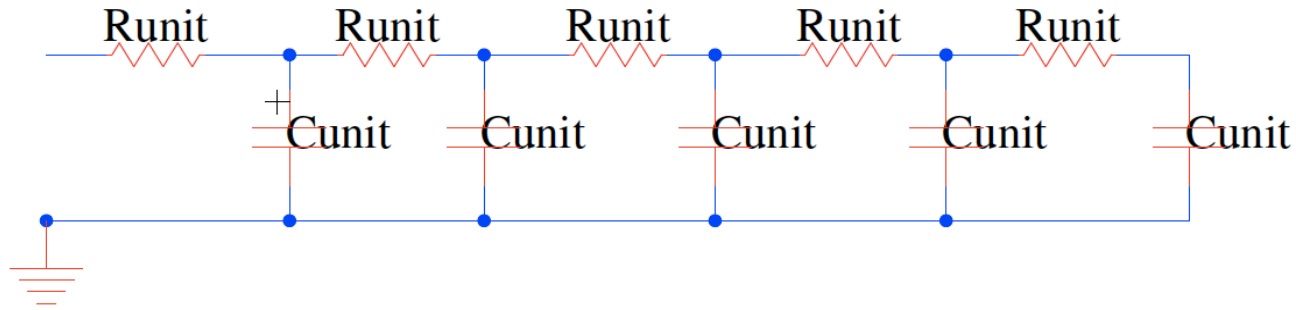- There are capacitors everywhere
- We already talked about
 - Wires modeled as a distributed RC network



 - Parasitic capacitances between terminals on transistor





Capacitance Everywhere

- Potentially a capacitor between any two conductors
 - On the chip
 - On the package
 - On the board
- All wires
 - Package pins
 - PCB traces (what you did in lab)
 - Cable wires
 - Bit/word lines




Capacitance...

- ❑ ...decreases with conductor separation
- ❑ ...increases with size
- ❑ ...depends on dielectric

$$C = \epsilon_r \epsilon_0 \frac{A}{d}$$

Wire Capacitance

 - ❑ Changes in voltage on one wire may couple through parasitic capacitance to an adjacent wire





Crosstalk


- ❑ A wire has high capacitance to its neighbor.
 - When the neighbor switches from 1- \rightarrow 0 or 0- \rightarrow 1, the wire tends to switch too.
 - Called capacitive *coupling* or *crosstalk*.
- ❑ Crosstalk effects
 - Noise on non-switching wires
 - Increased delay on switching wires

Qualitative




Undriven Wire

 - ❑ What happens to undriven wire?
- ❑ Where do we have undriven wires?




Undriven Wire

 - ❑ What happens to undriven wire?
- ❑ Where do we have undriven wires?



Driven Wire

 
- What happens to a driven “neighbor” wire?
 - One wire switches
 - Neighbors driven but not switch
 - What happens to neighbors?



Driven Wire

□ What happens to a driven “neighbor” wire?

■ One wire switches

 



Clocked Logic


- ❑ CMOS driven lines
- ❑ Clocked logic
 - Willing to wait to settle/evaluate
- ❑ Impact is on delay
 - May increase delay of transitions

Quantitative





Isolated Wire RC

$$R = \frac{\rho L}{A}$$

 


$$C = \epsilon_d \frac{A}{d}$$

  


Wire step response (preclass 4)

- Step response for isolated wire?

 


Undriven Adjacent Wire (preclass 5)

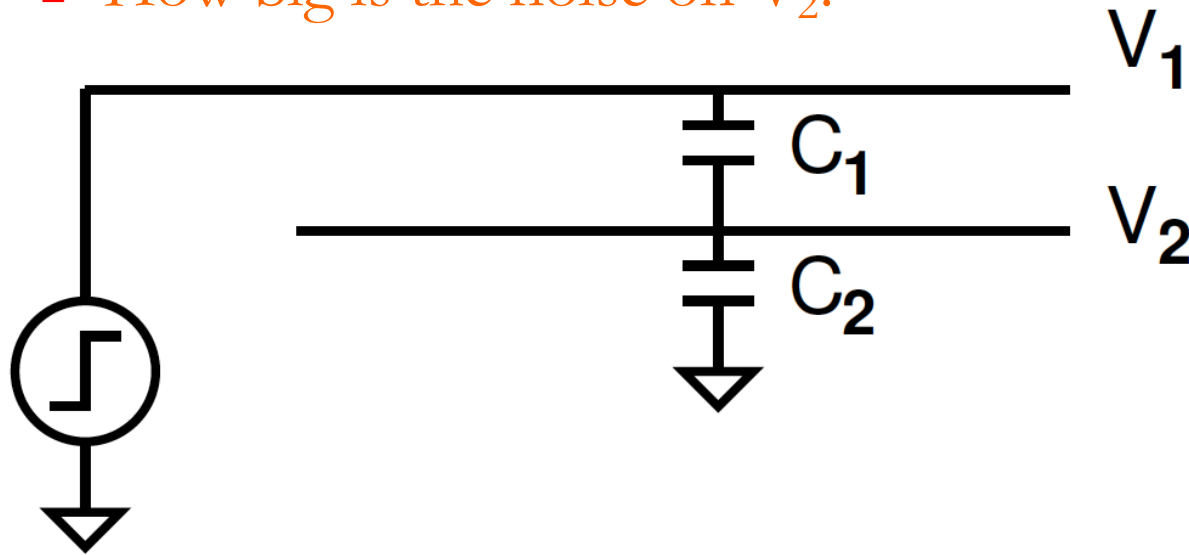- V_1 transitions from 0 to V
 - How big is the noise on V_2 ?



Undriven Adjacent Wire

 
- V_1 transitions from 0 to V
 - How big is the noise on V_2 ?



$$I(t) = C \frac{dV(t)}{dt}$$

Undriven Adjacent Wire

 - V_1 transitions from 0 to V
 - How big is the noise on V_2 ?




$$I(t) = C \frac{dV(t)}{dt}$$

Undriven Adjacent Wire

□ V_1 transitions from 0 to V

■ How big is the noise on V_2 ?

 

$$I(t) = C \frac{dV(t)}{dt}$$

$$C_1 \frac{d(V_1(t) - V_2(t))}{dt} = C_2 \frac{dV_2(t)}{dt}$$

$$C_1 \frac{dV_1(t)}{dt} = (C_1 + C_2) \frac{dV_2(t)}{dt}$$



$$C_1 V_1(t) = (C_1 + C_2) V_2(t)$$

$$V_2(t) = \frac{C_1}{C_1 + C_2} V_1(t)$$

$$C_1 = 10pF$$


$$C_2 = 20pF$$

  SPICE $C_1=10\text{pF}$, $C_2=20\text{pF}$



Good (?) Capacitance

 
- High capacitance to ground plane (C_2)
 - Limits node swing from adjacent conductors



$$V_2 = \left(\frac{C_1}{C_1 + C_2} \right) V_1$$


Driven Adjacent Wire (preclass 5)

 - What happens when neighbor line is driven?




Driven Adjacent Wire

 
- What happens when neighbor line is driven?
 - Recovers with time constant: $R_2(C_1+C_2)$



 Spice: $R_2=1\text{K}$, $C_1=10\text{pF}$, $C_2=20\text{pF}$



 *** spice deck for cell test_cap_undriven{sch} from library




Magnitude of Noise on Driven Line (preclass 6)

□ Magnitude of diversion depends on relative time constants

■ $\tau_1 \ll \tau_2$


■ $\tau_1 \gg \tau_2$

■ $\tau_1 \sim \tau_2$

 


Magnitude of Noise on Driven Line

 - Magnitude of diversion depends on relative time constants
 - $\tau_1 \ll \tau_2$
 - full diversion, then recover
 - $\tau_1 \gg \tau_2$
 - Drive capacitor (C_2) faster than line 1 can change
 - little noise
 - $\tau_1 \sim \tau_2$
 - Somewhere in between




 Spice: $C_1=1\text{pF}$, $C_2=2\text{pF}$




Switching Line with Finite Drive

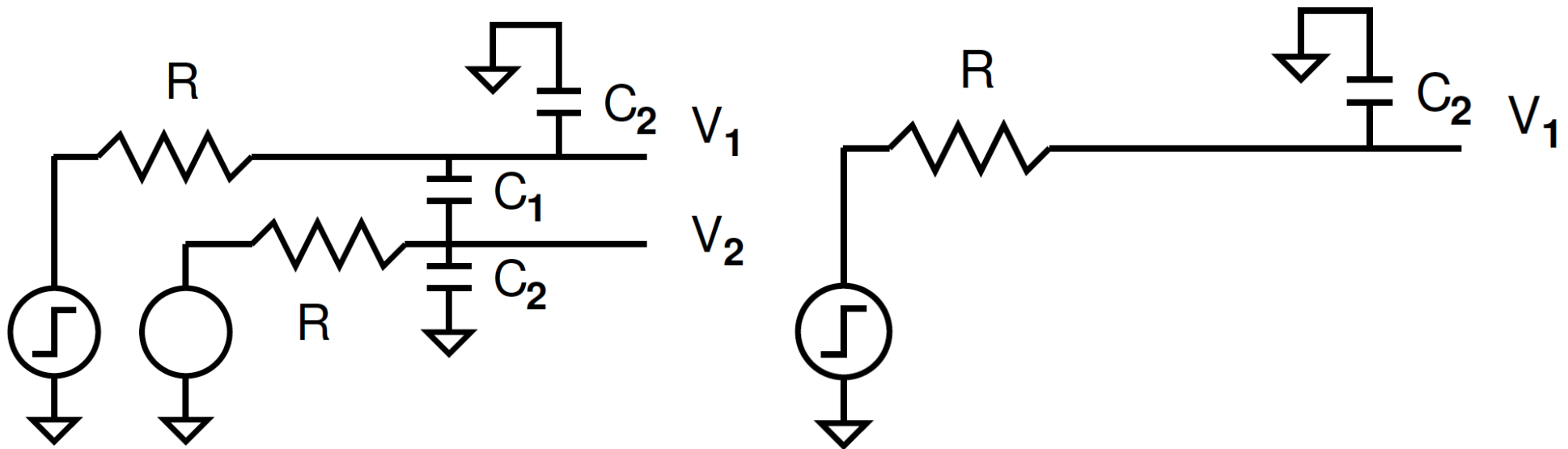- What impact does the presence of the neighbour line have on the **switching** line?
 - All previous questions were about noise on non-switching wire
 - Finite drive (R)




Simultaneous Transition

 - What happens if lines transition in opposite directions?




Simultaneous Transition

 - What happens if lines transition in opposite directions?
 - Must charge C_1 by $2V$
 - Or looks like $2C_1$ between wires




Simultaneous Transition

 - What happens if lines transition in same direction?




Simultaneous Transition

 - What happens if lines transition in same direction?
 - Looks like no coupling capacitor!





Simulation


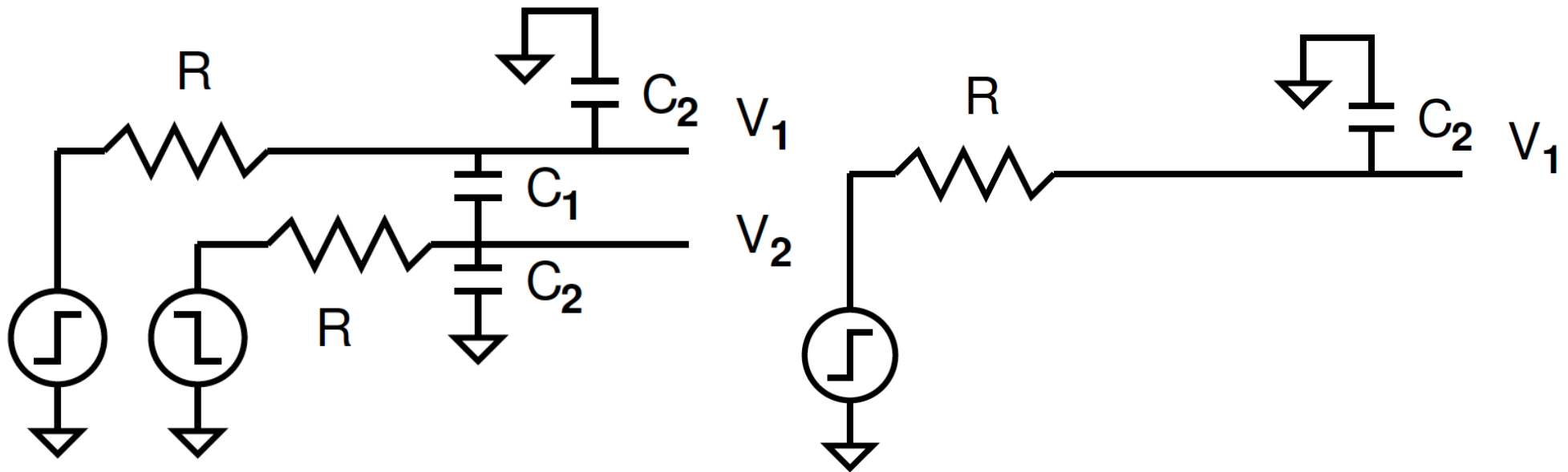
- ❑ V_2 switching at $1/4$ frequency of V_1
- ❑ No crosstalk reference case where no V_2





Crosstalk Neighbor Simulations

  



Crosstalk Neighbor Simulations

  


Crosstalk Neighbor Simulations

  



Crosstalk Neighbor Simulations

  

Simulation Setup

 

Crosstalk Simulation

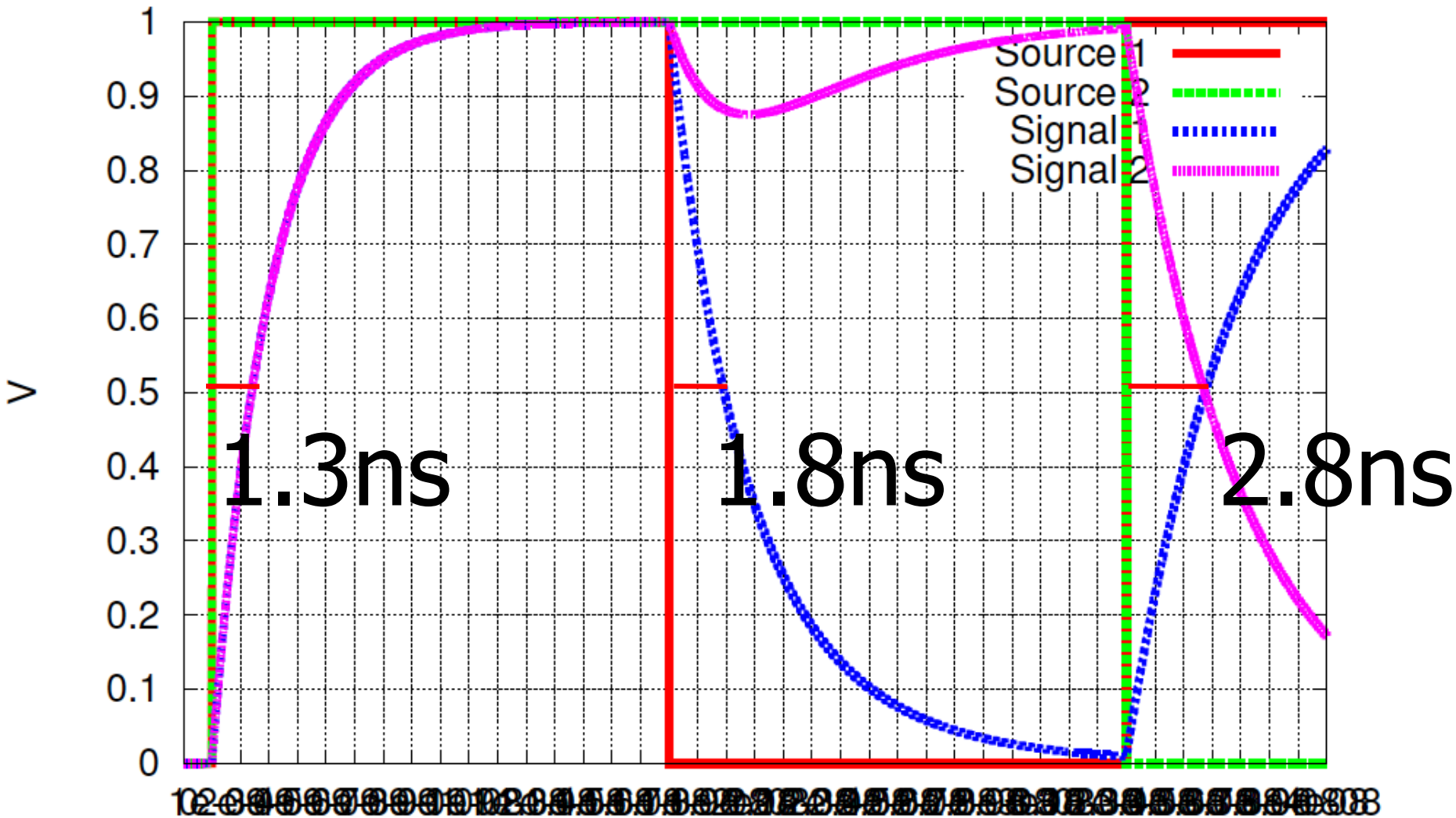
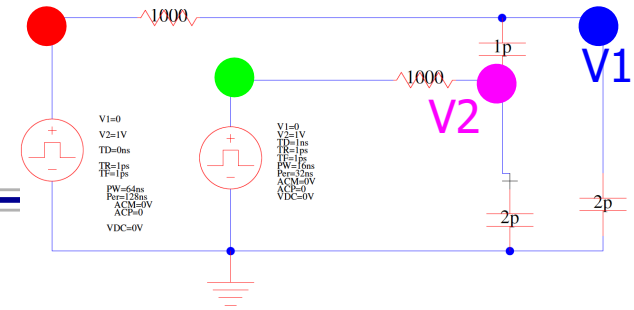


Where Does it Arise?






Cables and PCB Wires

 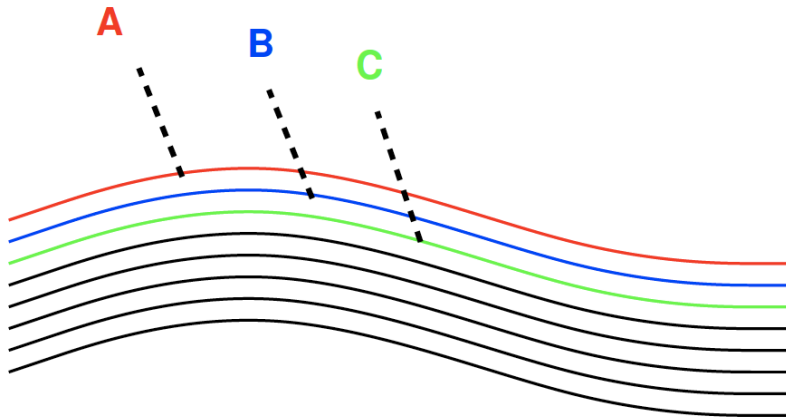


Source; <http://en.wikipedia.org/wiki/File:Flachbandkabel.jpg>

Printed Circuit Board

 


Source: <http://en.wikipedia.org/wiki/File:Testpad.JPG>

Interconnect Cross Section

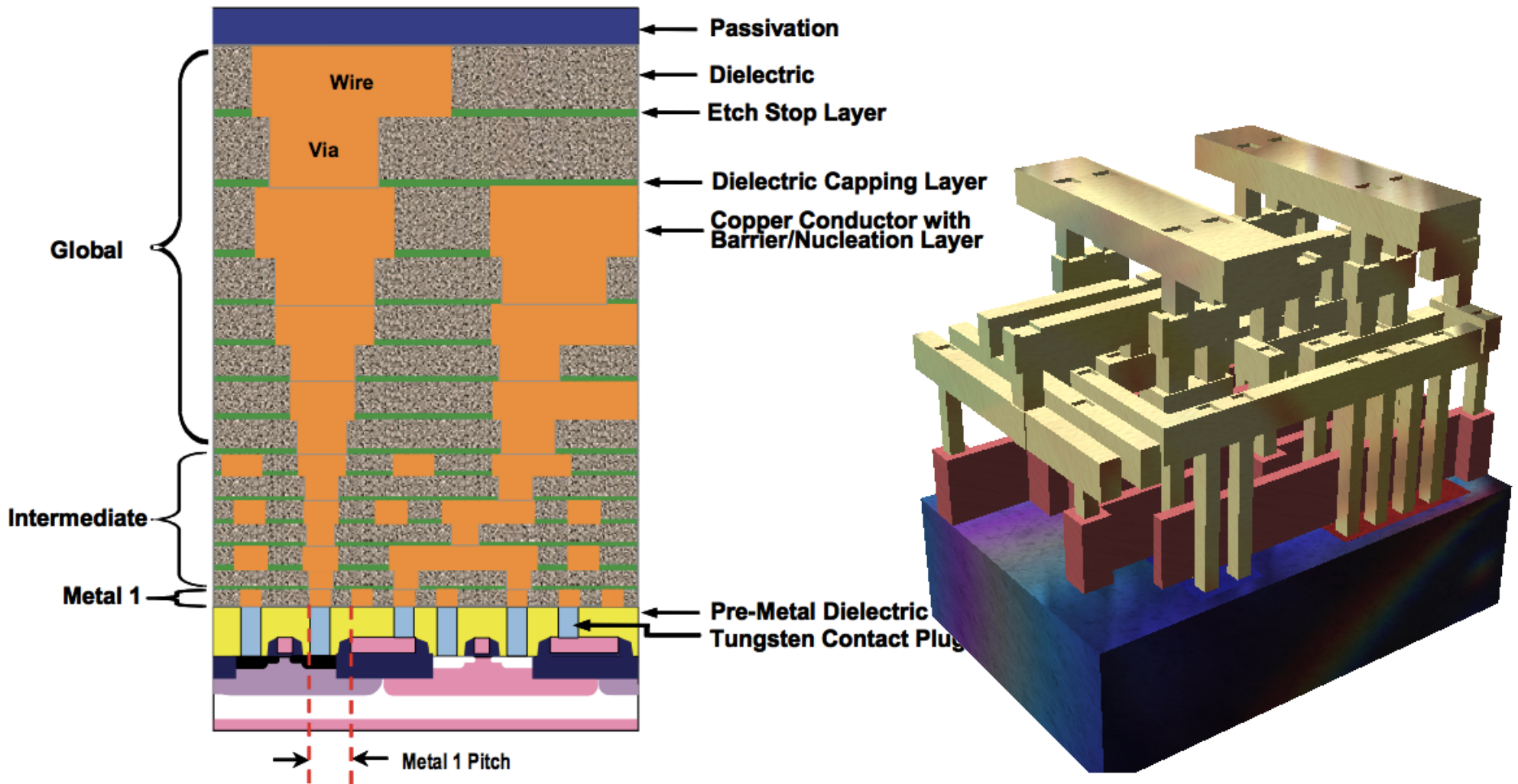


Standard Cell Area

 



Wires

 - Will be capacitively coupled to many adjacent wires of varying degrees





Noise Implications

- ❑ *So what* if we have noise?
- ❑ If the noise is less than the noise margin, nothing happens
- ❑ Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
 - But glitches cause extra delay
 - Also cause extra power from false transitions
- ❑ Dynamic logic never recovers from glitches
 - Can't correct mid-cycle, need precharge nodes
- ❑ Memories and other sensitive circuits also can produce the wrong result






Wire Engineering

- ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:

Wire Engineering

   - Goal: achieve delay, area, power goals with acceptable noise
- Degrees of freedom:
 - Width
 - Spacing
 - Layer










Wire Engineering

□ Goal: achieve delay, area, power goals with acceptable noise

□ Degrees of freedom:


- Width
- Spacing
- Layer
- Shielding

     

Idea

- Long wires are inductive
 - **Avoid** them
 - Especially on power supplies
- Bypass capacitors help
 
$$V_2 = V_S + B e^{\left(-\frac{R}{2L}\right)t} e^{\left(j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}\right)t}$$





Idea

- ❑ Capacitance is everywhere
- ❑ Especially between adjacent wires
- ❑ Will get “noise” from crosstalk
- ❑ Clocked and driven wires
 - Slow down transitions
- ❑ Undriven wires voltage changed
- ❑ Can cause spurious transitions



Admin

- Project 2
 - Due Wednesday 5/1
 - Feedback by Wednesday