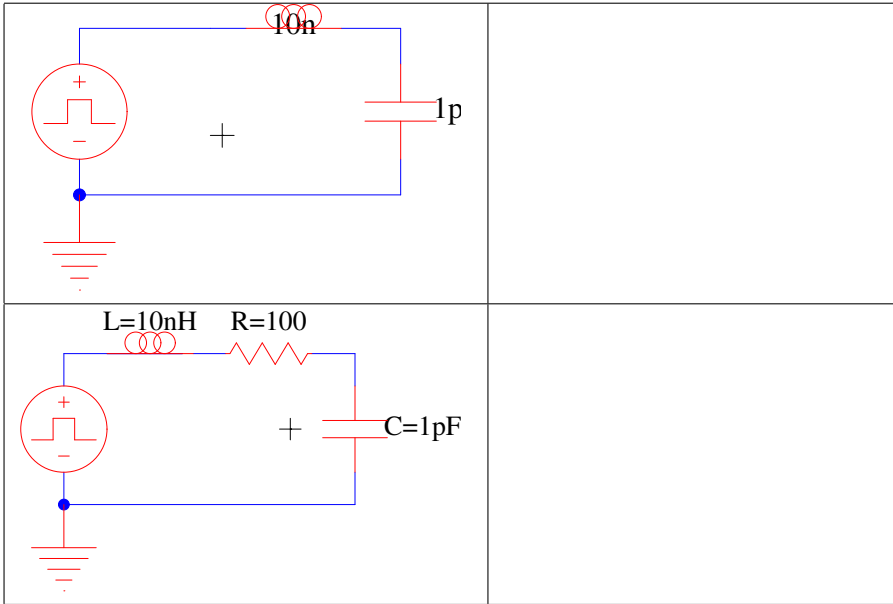


1. What is the step response (voltage on top plate of capacitor)? Draw the general shape.




2. The RLC response is given as $V_C = V_S + B e^{(-\frac{R}{2L})t} e^{j\left(\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}t\right)}$. For what values of R does this oscillate?

3. Inductance of a PCB Trace over a ground plane: $L \approx l \left(\frac{\mu_0 \mu_r h}{w} \right)$


- Height above ground plane: $h = 3\text{mil}$ (1 mil = 0.001 inches)
- Width of trace: $w = 5\text{mil}$
- $\mu_0 \approx 1.26 \times 10^{-6} \text{ H/m}$
- $\mu_r \approx 1.0$

Per centimeter of PCB trace, how much inductance?

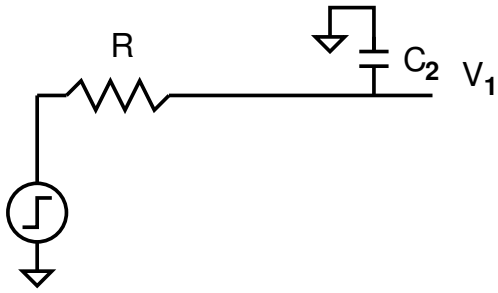
4. What happens at V_1 when the input switches?



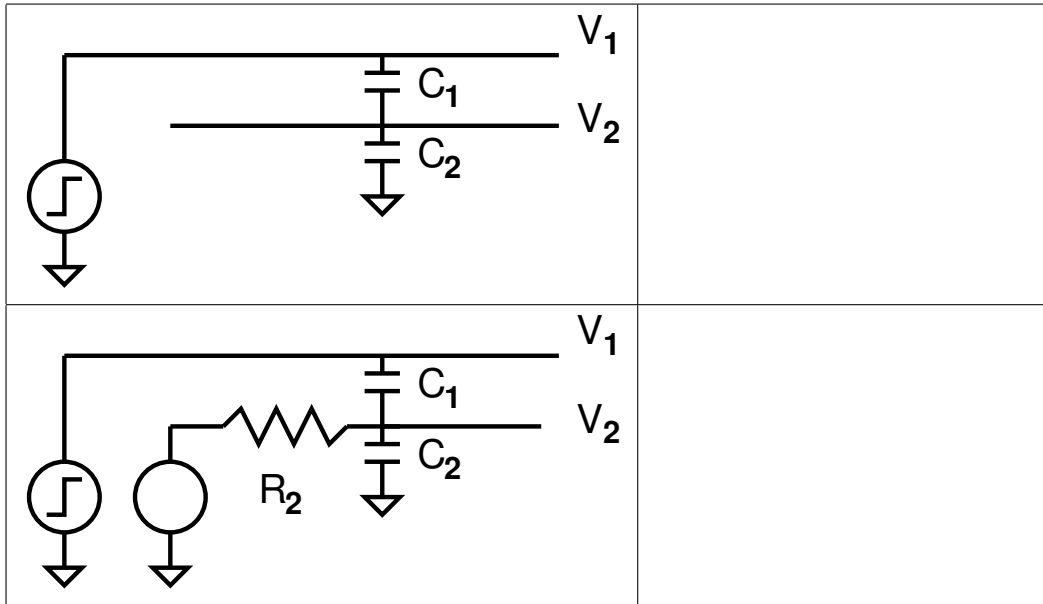5. What happens to V_2 when V_1 switches?



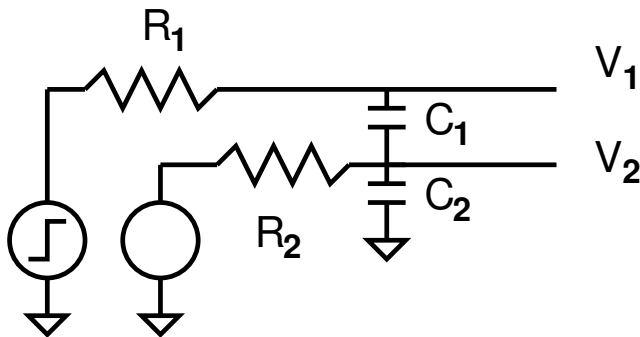6. What happens to V_2 when V_1 switches?



$\tau_1 \ll \tau_2$	
$\tau_1 \approx \tau_2$	
$\tau_1 \gg \tau_2$	