

# ESE3700: Circuit-Level Modeling, Design and Optimization for Digital Systems

---

Lec 21: April 29, 2024  
Transmission Line





# Today

---

- ❑ Saw in action in lab
- ❑ Where transmission lines arise?
- ❑ General wire formulation
- ❑ Lossless Transmission Line
- ❑ End of Transmission Line?
- ❑ Termination
- ❑ Discuss Lossy
- ❑ Implications


# Where Transmission Lines Arise

---


 
# Transmission Lines

- ❑ Cable: coaxial
- ❑ PCB
  - Strip line
  - Microstrip line
- ❑ Twisted Pair (Cat5)





# Transmission Lines

---

- How did the traces behave in lab?
- How does this differ from
  - Ideal equipotential?
  - RC-wire on chip?



# Transmission Lines

---

- This is what long wires/cables look like
  - Aren't an ideal equipotential
  - Signals take time to propagate
  - Maintain shape of input signal
    - Within limits
  - Shape and topology of wiring effects how signals propagate



# Transmission Lines

---

- Need theory/model to support design
  - Reason about behavior
  - Understand what can cause noise
  - Engineer high performance/speed communication

# Wire Formulation

---







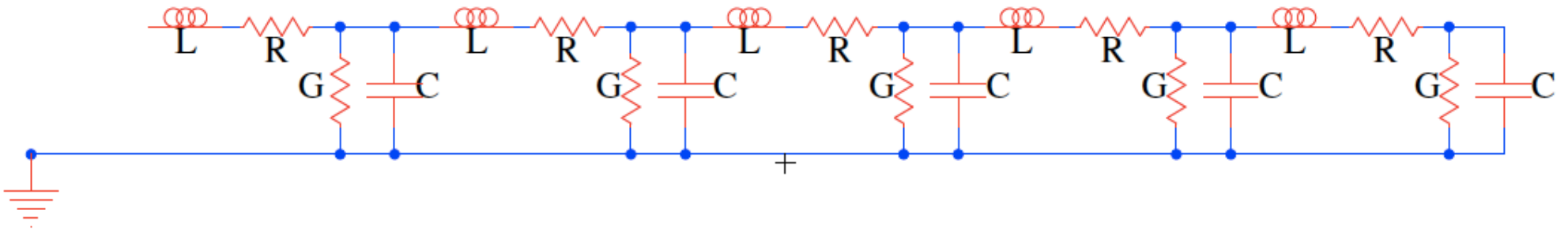
# Wires


- In general, our “wires” have distributed R, L, C components






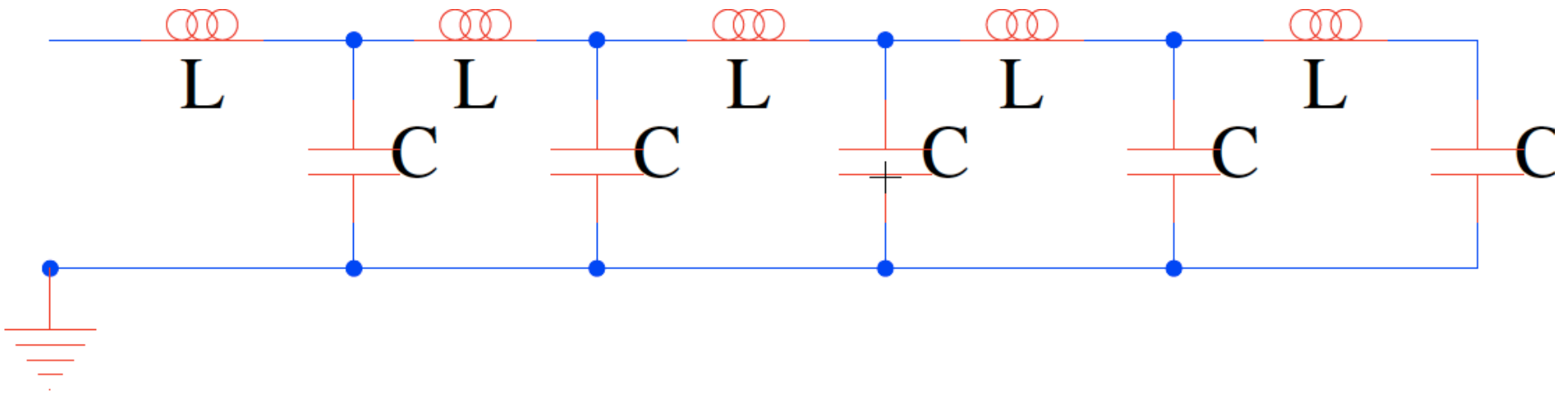
# Transmission Line

- When resistance is negligible
  - Have LC wire = Lossless Transmission Line
    - No energy dissipation (loss) through R's
  - More typical of printed circuit board (PCB) wires and bond wires



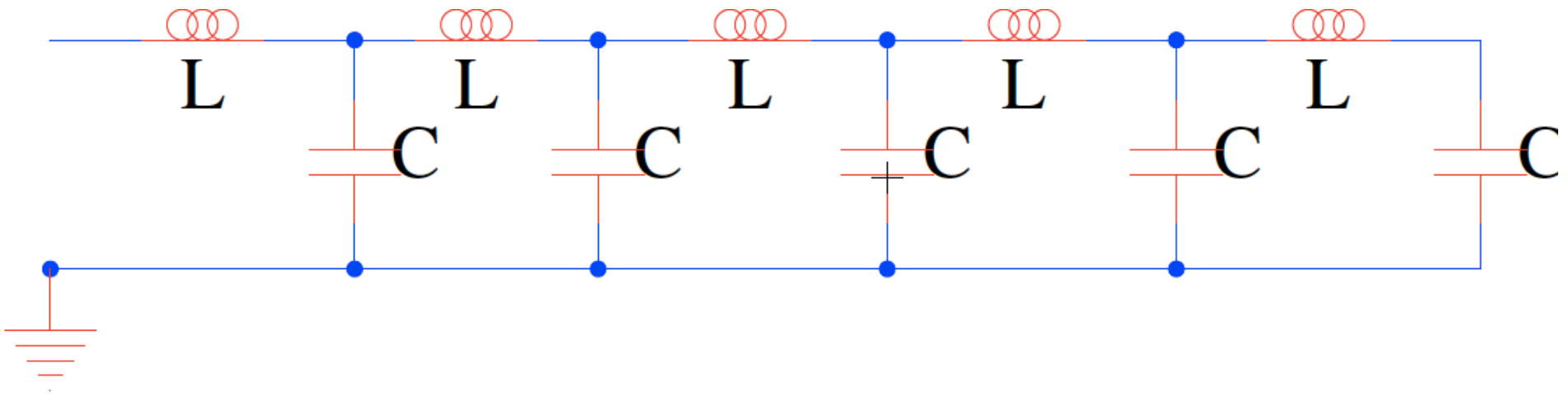
 
# Build Intuition from LC (Preclass 2)

- ❑ What did one LC do?
- ❑ What will chain do?


  
# Build Intuition from LC (Preclass 2)

- ❑ What did one LC do?
- ❑ What will chain do?





# Intuitive: Lossless


---

- Pulses travel as waves without distortion
  - (up to a characteristic frequency)




# SPICE Simulation


---

 

# Step Response SPICE

 


LC Ladder

 





# Pulse Response SPICE

 


Step Reponse 20 element LC Ladder

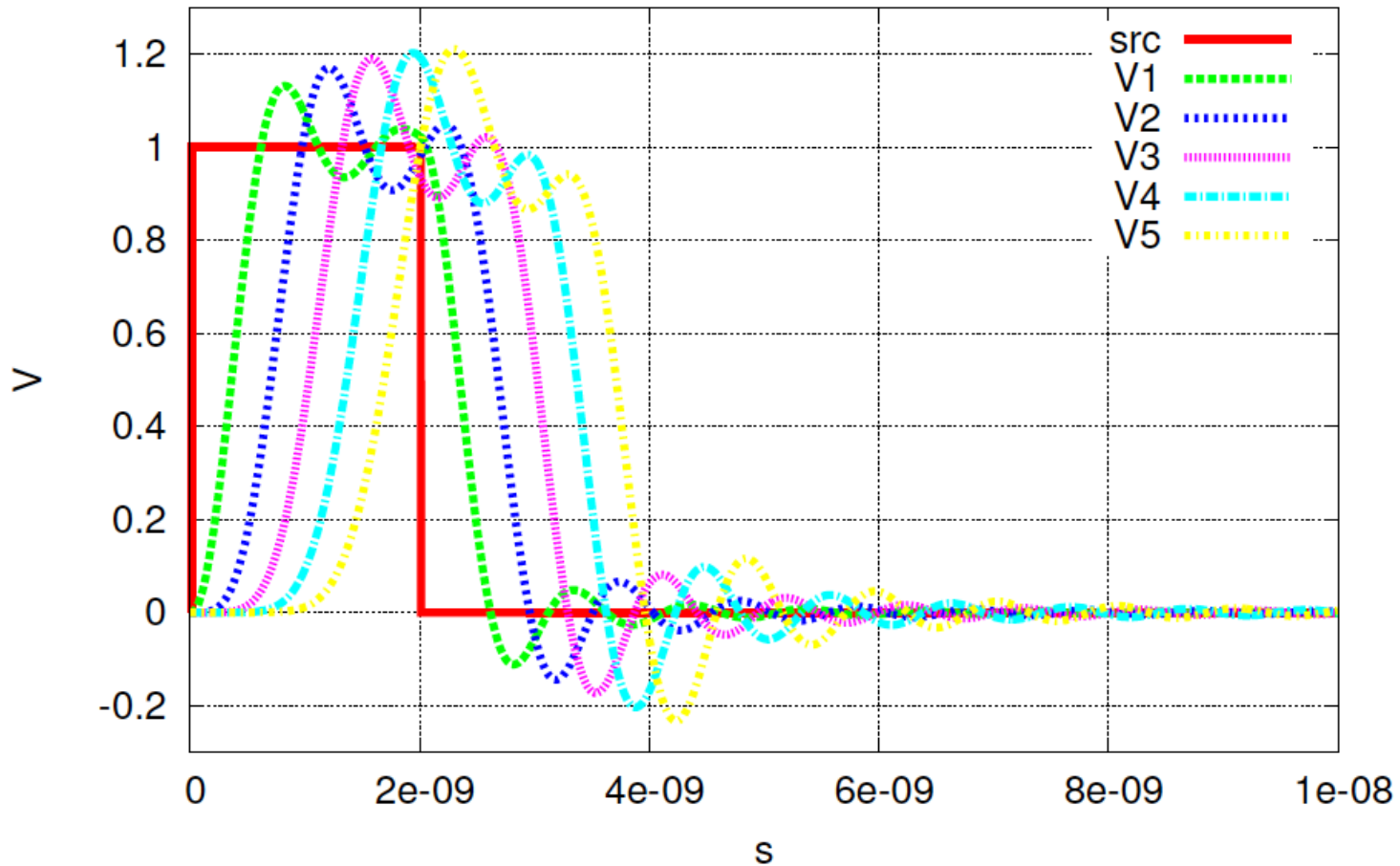

# Contrast RC Wire

 


RC Ladder

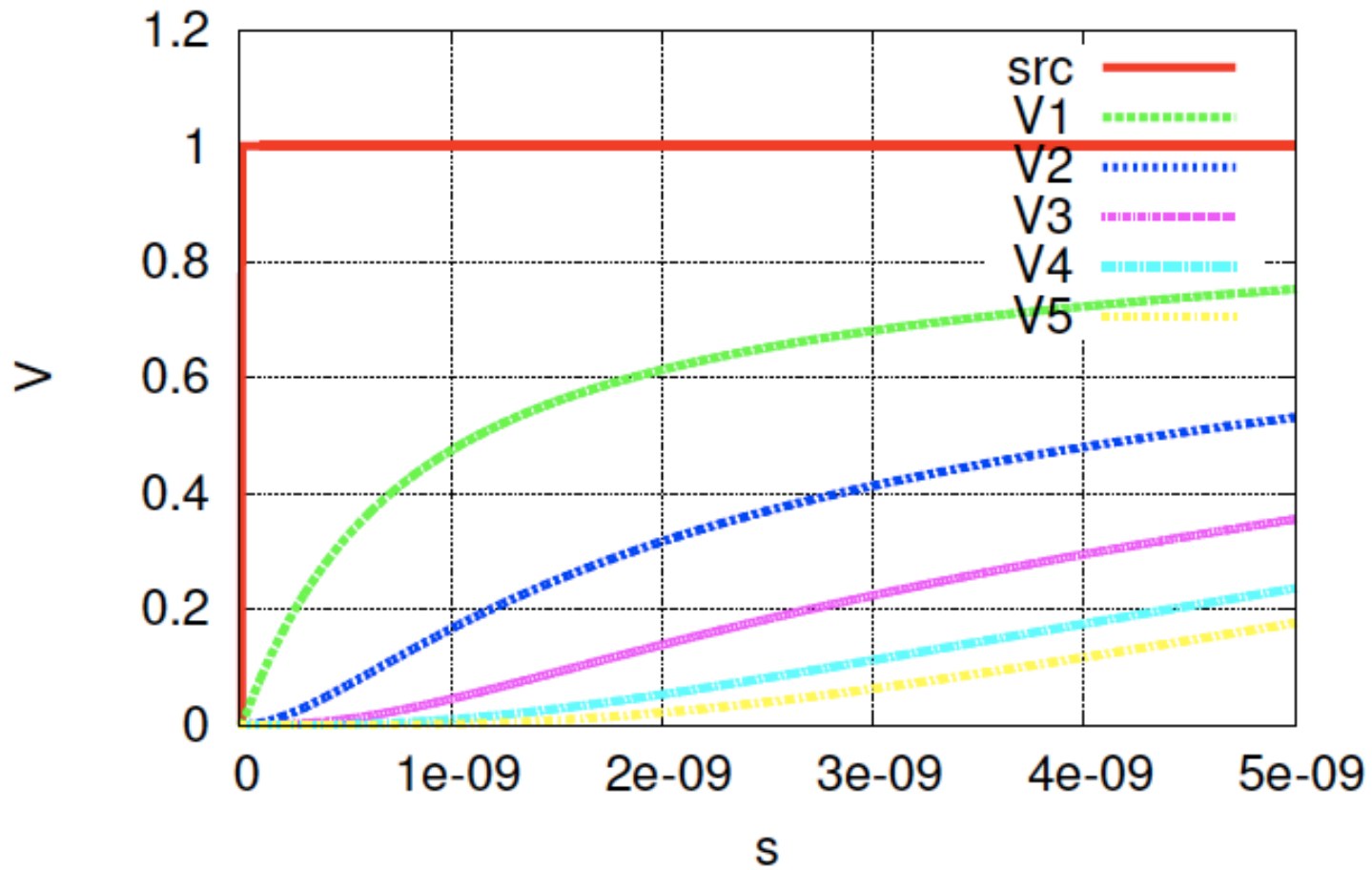




# Contrast

 


>

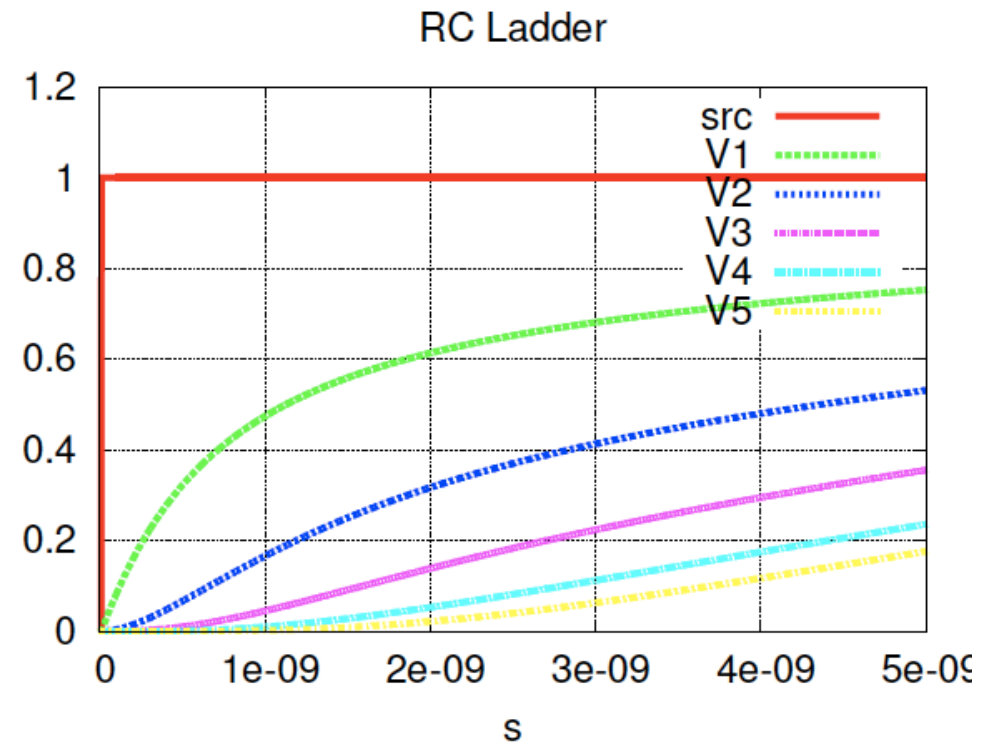

 
# Model

- Now voltage is a function of time **and** position
  - Position along wire – distance from source
- Want to get  $V(x,t)$ 
  - And  $I(x,t)$


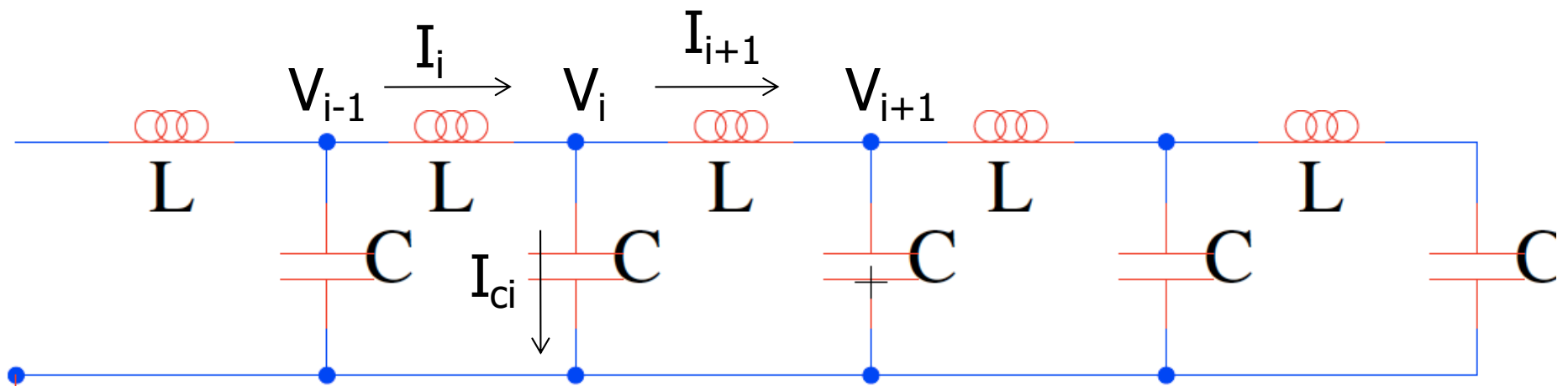
# Setup Relations

- $i$  is a node,  $x$  is the distance from source,  $\Delta x$  is distance between nodes
- Position along wire:  $x = i \Delta x$
- So  $V_i(t) = V(x = i\Delta x, t)$





# Implication

---

- Wave equation:

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

- Solution:

$$V(x, t) = A + Be^{x-wt}$$

- What is  $w$ ?



# Implication

---

- Wave equation:

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

- Solution:

$$V(x, t) = A + Be^{x-wt}$$

- What is  $w$ ?

$$Be^{x-wt} = LCw^2 Be^{x-wt}$$


$$w = \sqrt{\frac{1}{LC}}$$

$w$  is the rate of propagation

# Propagation Rate in Example



- $L=1\mu\text{H}$
- $C=1\text{pF}$
- What is  $w$ ?

$$w = \frac{1}{\sqrt{LC}}$$

 





# Signal Propagation

  


# Signal Propagation

 

## Delay linear in length

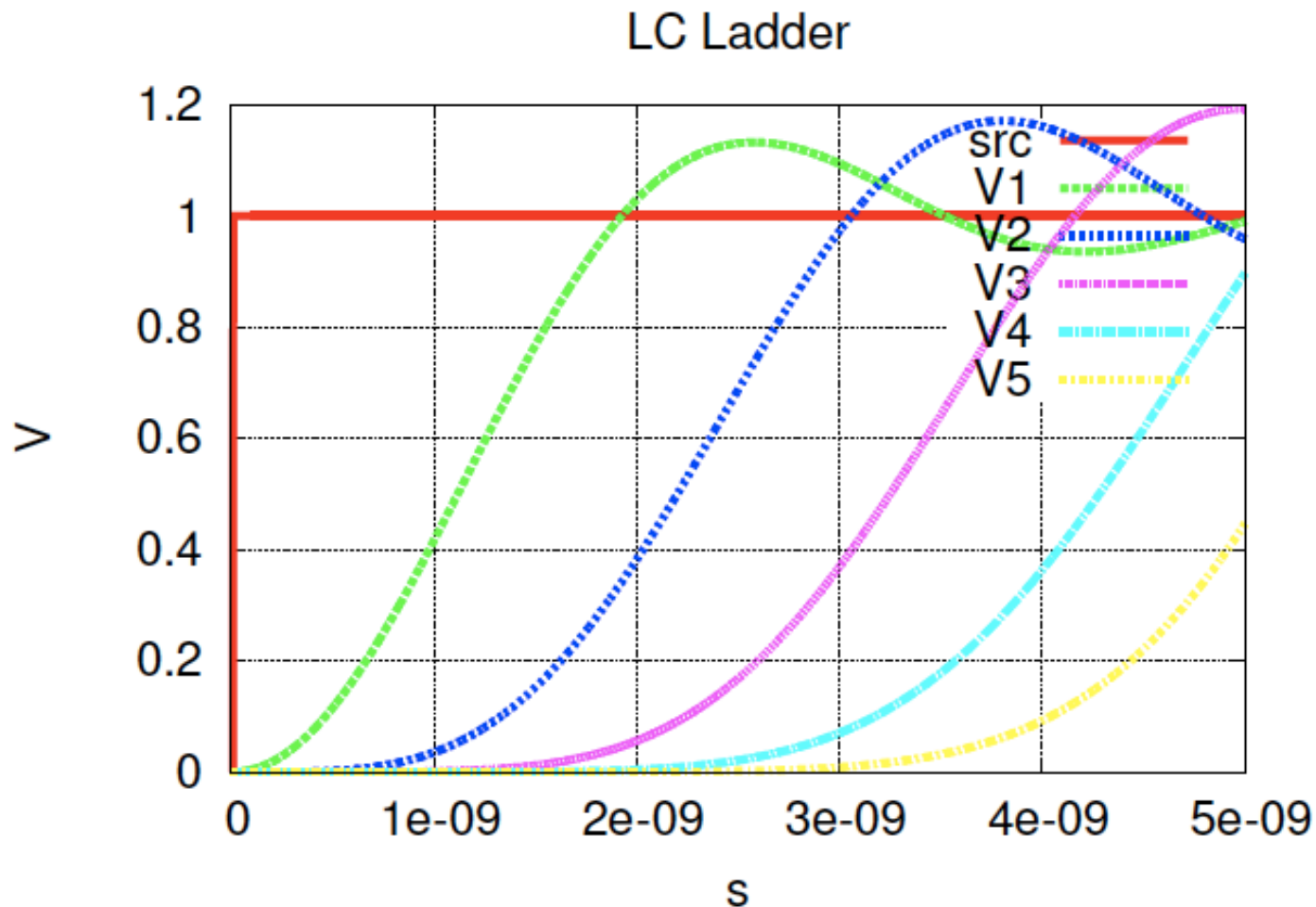


# Contrast RC Wire

 

RC wire delay quadratic  
in length

RC Ladder

 


# Longer LC (open)

- 40 Stages
- $L=100\text{nH}$
- $C=1\text{pF}$

$$w = \frac{1}{\sqrt{LC}}$$


Stage delay? How long to propagate?

 

# Reflection Teaser: Pulse Travel RC


□ V1,V3,V4,V5,V6 about 10 stages apart

40 stage LC Ladder (open)

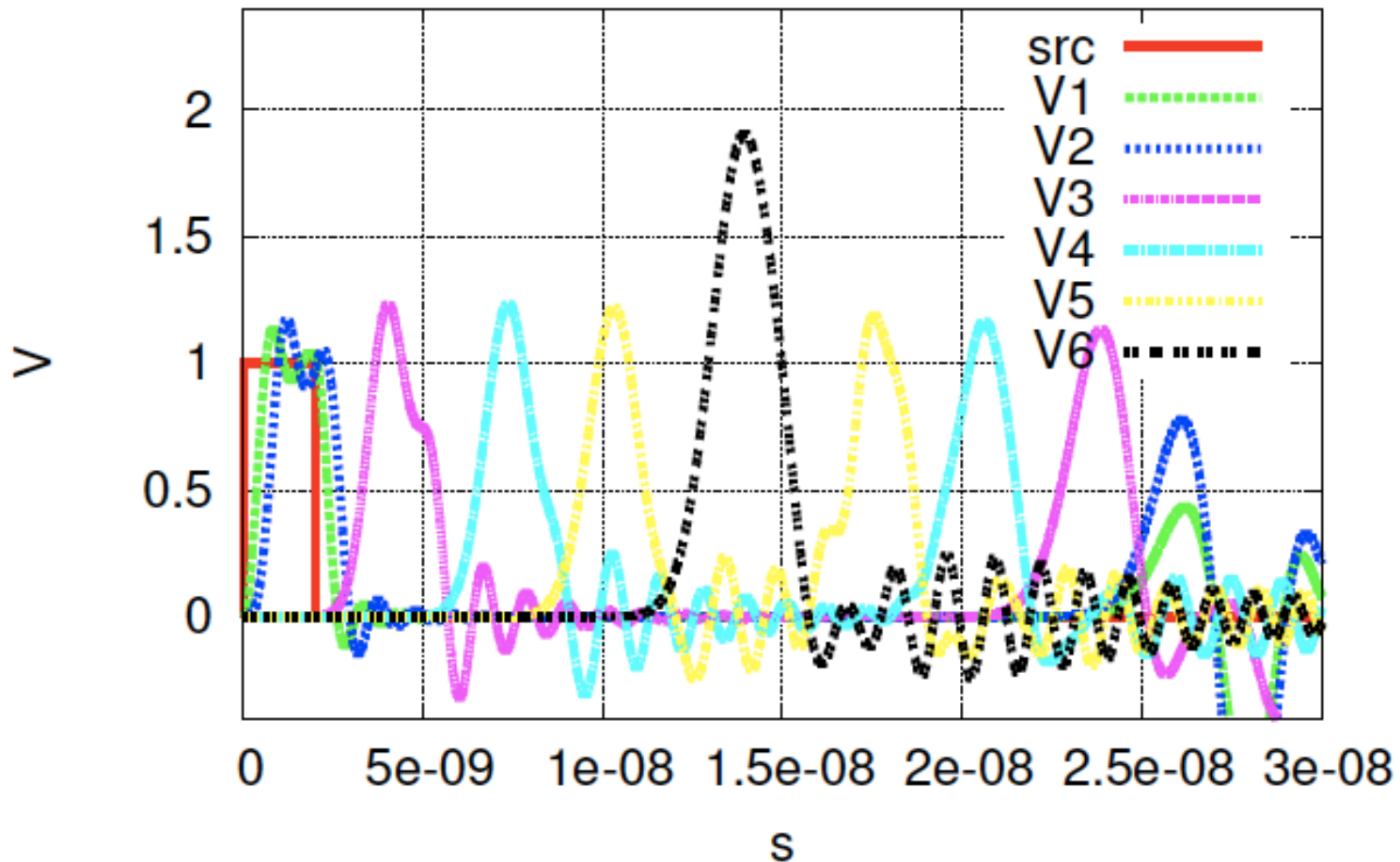
 
# Wire “Resistance” (preclass 4)

- What is the resistance at  $V_i$  ?
  - $Q$  needed to charge  $C$  to  $V_i$ ?
  - $I_i$  given velocity  $w$ ?
  - $R = V_i/I_i$ ?




# Wire “Resistance”

- $Q = CV_i$
- $I_i = dQ/dt$
- Moving at rate  $w$
- $I_i = wCV_i$
- $R = V_i/I_i = 1/(wC)$

$$w = \frac{1}{\sqrt{LC}}$$


$$R = \frac{\sqrt{LC}}{C}$$

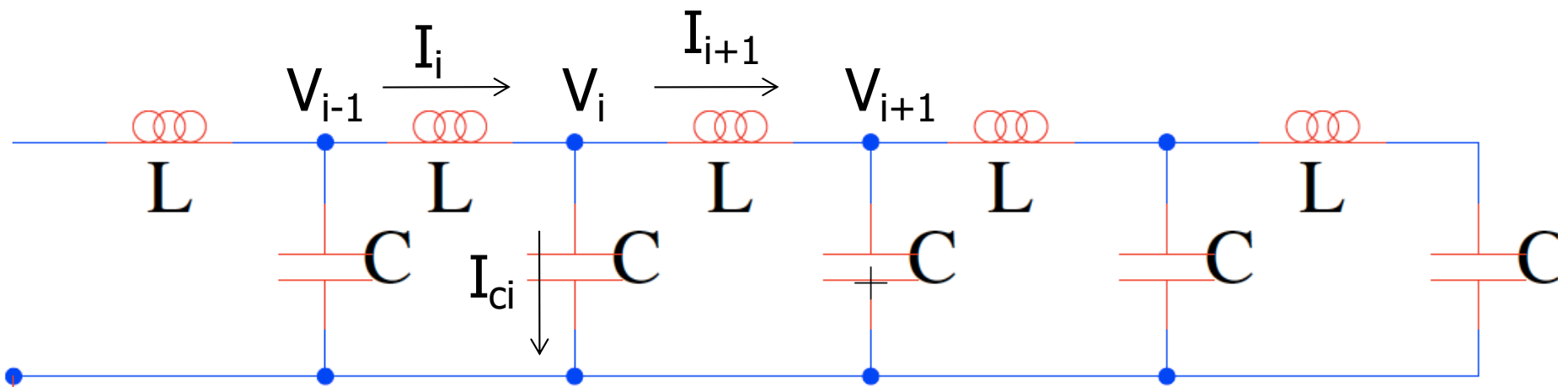
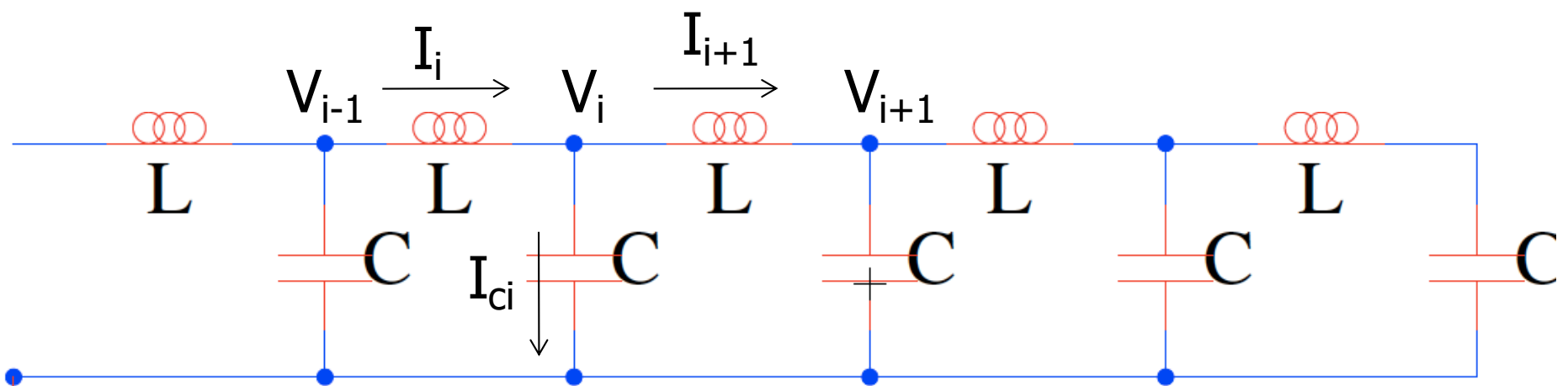
# Characteristic Impedance

□  $Z_0 = R$

$$R = \frac{\sqrt{LC}}{C} = \sqrt{\frac{L}{C}} = Z_0$$






# Infinite Lossless Transmission Line

- Transmission line looks like resistive load

$$Z_0 = \sqrt{\frac{L}{C}}$$

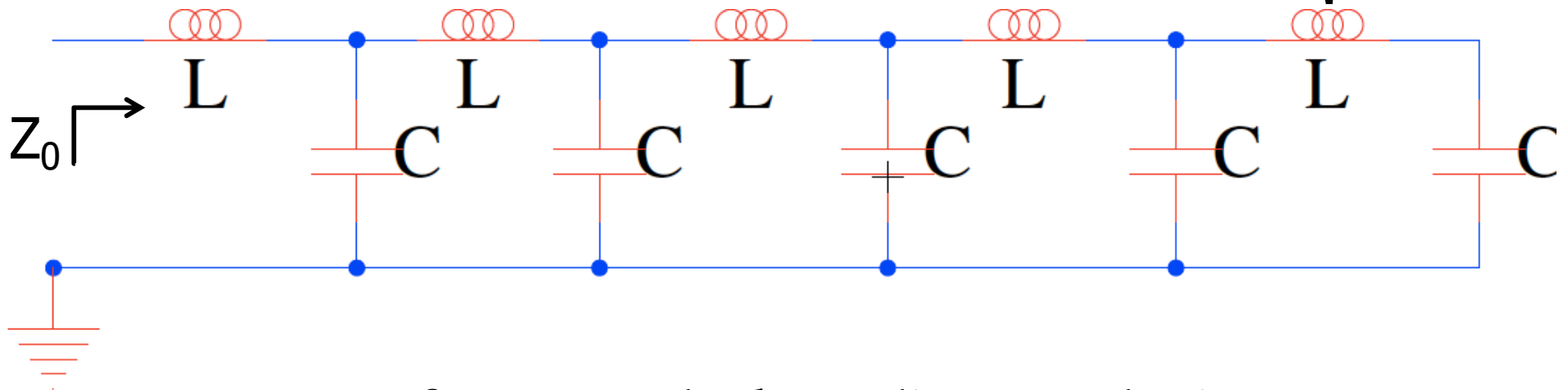

- Input waveform travels down line at velocity
  - Without distortion

$$w = \frac{1}{\sqrt{LC}}$$



# Transmission Line Agenda

---

- ~~See in action in lab~~
- ~~Where transmission lines arise?~~
- ~~General wire formulation~~
- ~~Lossless Transmission Line~~
- ~~Impedance~~
- End of Transmission Line?
  - Open, short, matched
- Termination
- Discuss Lossy
- Implications




# End of Line


---

- What happens at the end of the transmission line?
  - Short Circuit
  - Terminate with  $R=Z_0$
  - Open Circuit
  
- What did the reflections look like in each case in lab?


# Open

 


## LC Ladder

 


Terminate  $R=Z_0$

 


LC Ladder

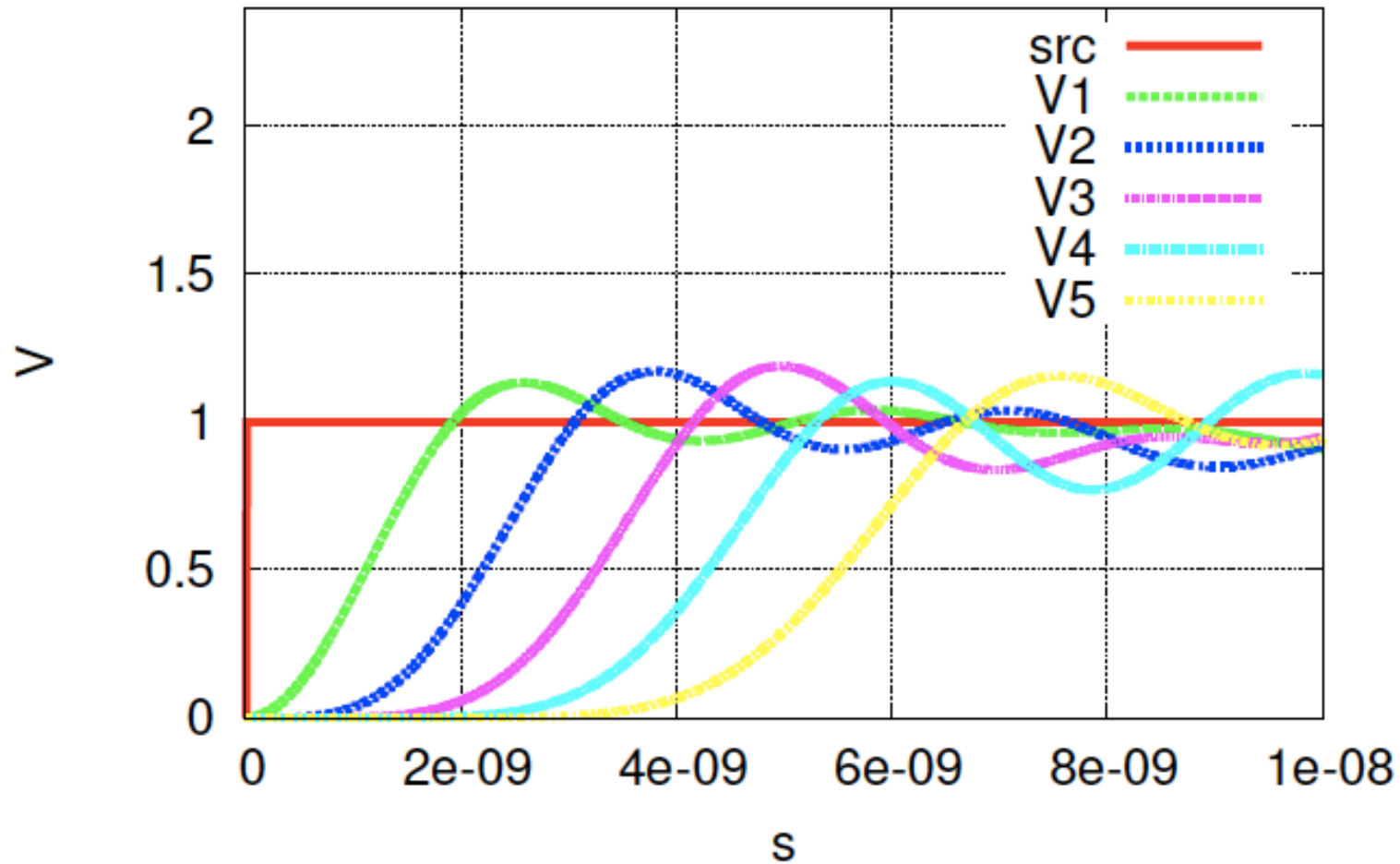

# Short

 

LC Ladder (short)

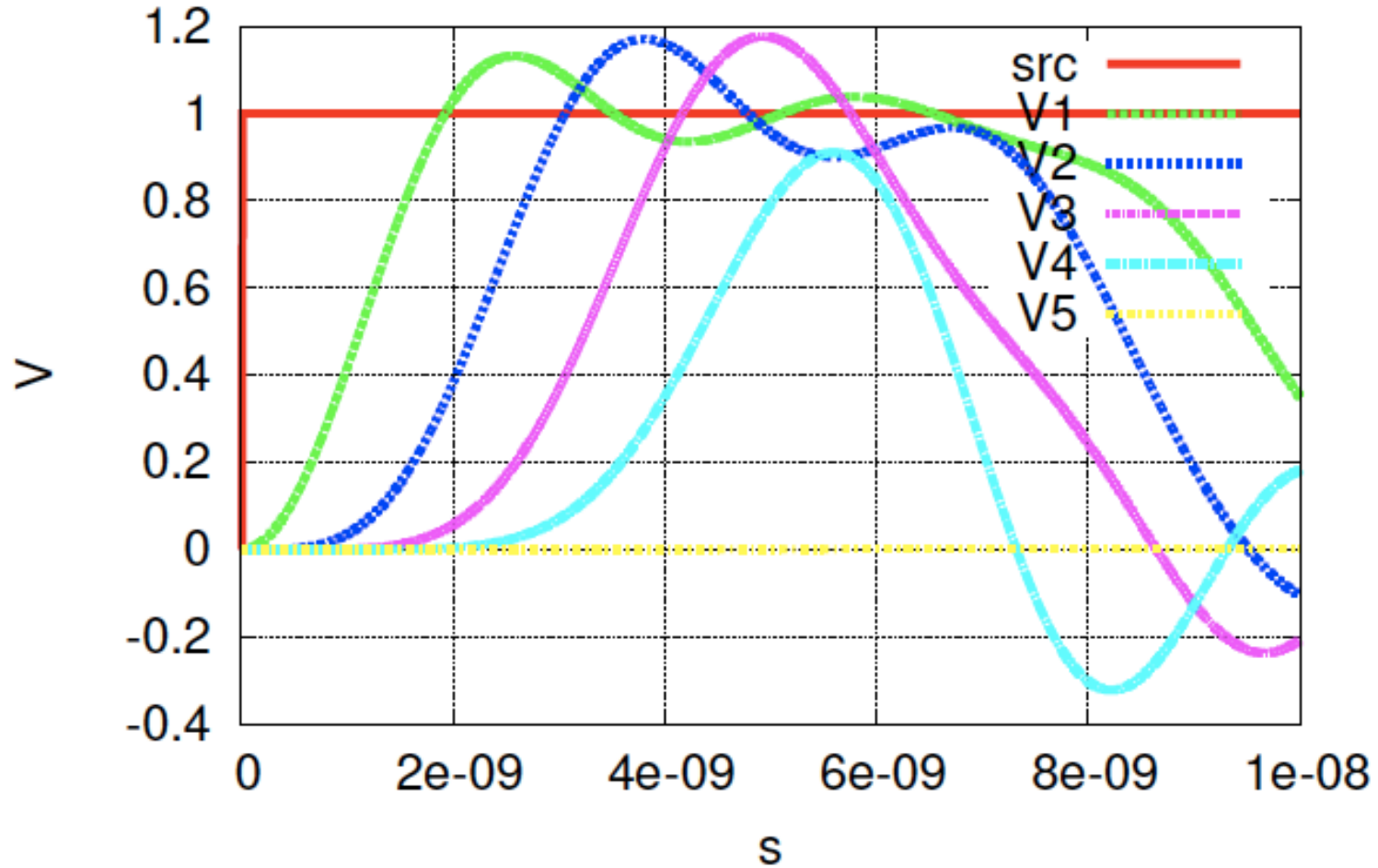


# Longer LC (open)

- ❑ 40 Stages
- ❑  $L=100\text{nH}$
- ❑  $C=1\text{pF}$

$$w = \frac{1}{\sqrt{LC}}$$


Stage delay? How long to propagate?

 

- ❑ Drive with 2ns Pulse
- ❑ No termination (open circuit)
  - What reflection do we expect?

# Pulse Travel RC



□ V1,V3,V4,V5,V6 about 10 stages apart

 


  
# Analyze End of Line


- Incident Wave, Reflected Wave, Transverse Wave



Source: [https://en.wikipedia.org/wiki/Reflection\\_coefficient](https://en.wikipedia.org/wiki/Reflection_coefficient)
 
# Analyze End of Line


- Incident wave  $V_i = I_i \times Z_0$
- @  $T - \delta$   $V_i$  is voltage on line
- $V_t$  is what goes forward
  - Voltage seen by end of line at  $T$
- $V_r$  is the reflected voltage that starts moving back towards source at  $T + \delta$


 
# Reflection

Reflection coefficient

$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_r$$



# Analyze End of Line

□  $V_i + V_r = V_t$

$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_r$$

$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_t - V_i$$


$$V_i \left( \frac{R - Z_0}{R + Z_0} + 1 \right) = V_t$$

$$V_i \left( \frac{2R}{R + Z_0} \right) = V_t$$

Transmission coefficient
 
# Reflection

- Sanity check with previous
  - Short
  - Matched
  - Open




$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_r$$





# Visualization


□ <https://tinyurl.com/y2jortrq>

 

# Pulse Travel RC

□ V1,V3,V4,V5,V6 about 10 stages apart

  

 



# Back to Source

---





# Back at Source? (Preclass 5)

---

- What happens at source?
  - Depends on how it's terminated
  - Looks like a sink end now




$$R \neq Z_0$$

---

- What happens?
  - 75  $\Omega$  termination on 50  $\Omega$  line

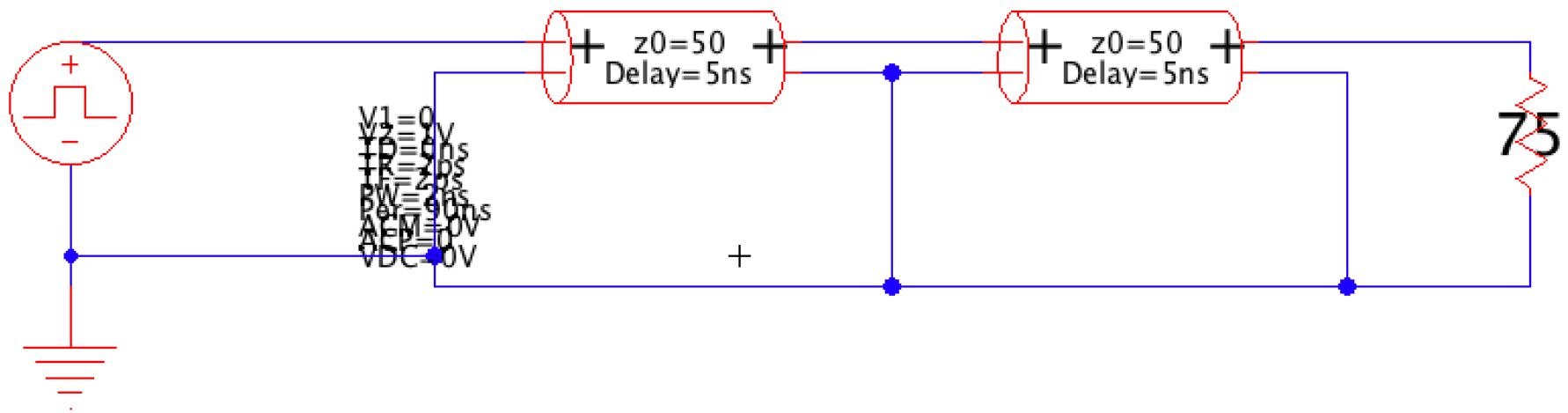
# Transmission Line Symbol

- ❑ Specify delay of full Tline and characteristic impedance
- ❑ Need reference



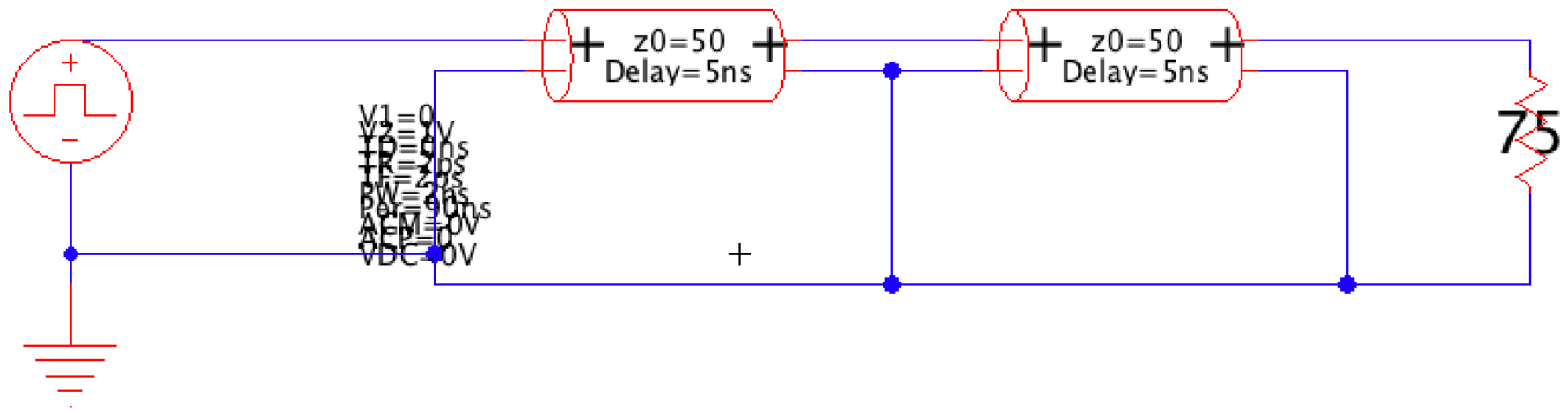
# Simulation (Preclass 6)


- ❑ For these, with direct drive from voltage source
  - Source looks like short circuit (not typical of CMOS)
    - Source cannot be changed



# 50Ω line, 75Ω termination

 


## Mismatch Termination

 


$$V_r = V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_i \left( \frac{75 - 50}{75 + 50} \right) = 0.2V_i$$

# 50Ω line, 75Ω termination

 


## Mismatch Termination

 


$$V_r = V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_i \left( \frac{75 - 50}{75 + 50} \right) = 0.2V_i$$

# 50Ω line, 75Ω termination

 


## Mismatch Termination

 


$$V_r = V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_i \left( \frac{75 - 50}{75 + 50} \right) = 0.2V_i$$



# 50Ω line, 75Ω termination

 


## Mismatch Termination

 


$$V_r = V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_i \left( \frac{75 - 50}{75 + 50} \right) = 0.2V_i$$

# Source Series Termination


□ What happens here?

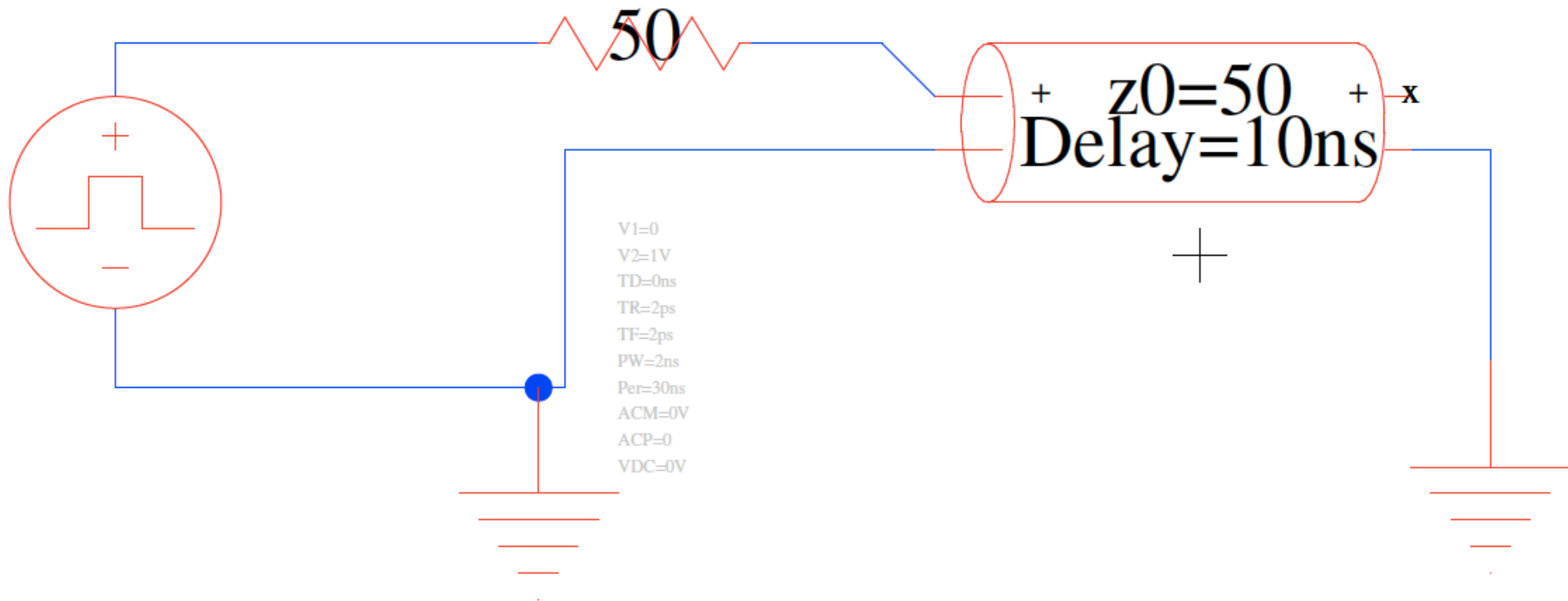

# Simulation


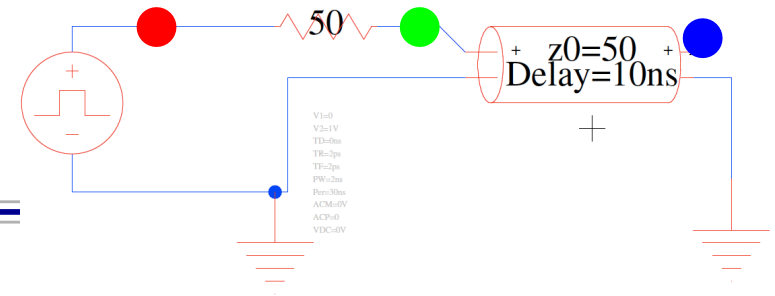


Series Terminated Transmission Line

 

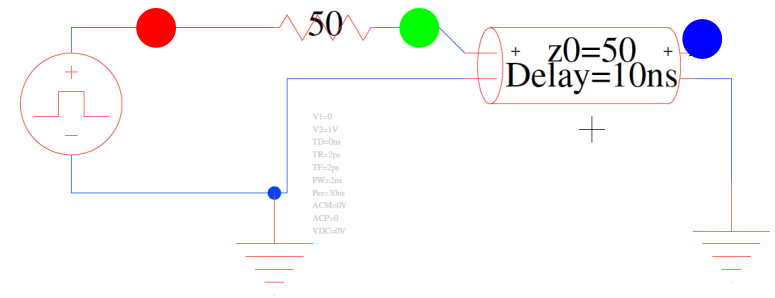 
# Series Termination

- ❑  $R_{\text{series}} = Z_0$
- ❑ Initial voltage divider
  - Half voltage pulse propagates down Tline
- ❑ End of line open circuit
  - Sees single transition to full voltage (full reflection)
- ❑ Reflection returns to source and sees termination  $R_{\text{series}} = Z_0$
- ❑ No further reflections




# Termination Cases

- Termination in parallel at Sink

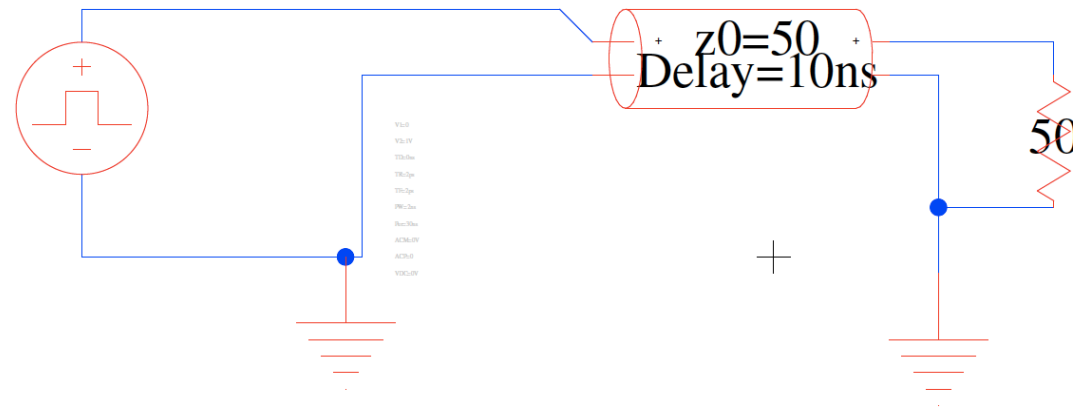


- Termination in series at Source

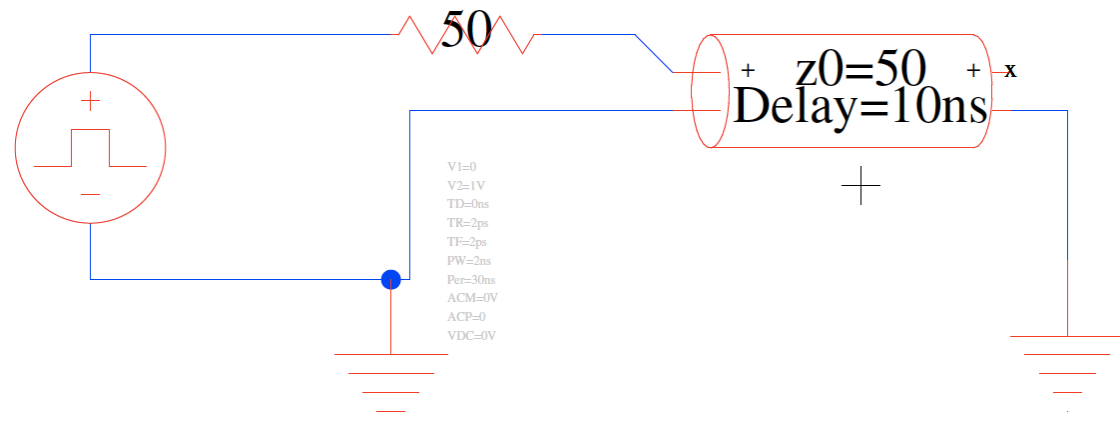

 
# CMOS Driver / Receiver

- Driver: What does a CMOS driver look like at the source?
  - $I_{d,sat} = 1200\mu\text{A}/\mu\text{m}$  @ 45nm,  $V_{dd} = 1\text{V}$
- Receiver: What does a CMOS inverter look like at the sink?


 
# CMOS Driver


- Driver: What does a CMOS driver look like at the source?
- $I_{d,sat} = 1200\mu\text{A}/\mu\text{m}$  @ 45nm,  $V_{dd} = 1\text{V}$
- Min size:
  - $I_{drive} = 1200\mu\text{A}/\mu\text{m} * 45\text{nm} = 54\mu\text{A}$
  - $R_{out} = V_{dd}/I_{drive} = 18\text{k}\Omega$


 
# CMOS Driver

□ Driver: What does a CMOS driver look like at the source?

- $I_{d,sat} = 1200\mu\text{A}/\mu\text{m}$  @ 45nm,  $V_{dd} = 1\text{V}$
- Min size:
  - $I_{drive} = 1200\mu\text{A}/\mu\text{m} * 45\text{nm} = 54\mu\text{A}$
  - $R_{out} = V_{dd}/I_{drive} = 18\text{k}\Omega$
- $W = 370$ 
  - $I_{drive} = 1200\mu\text{A}/\mu\text{m} * 45\text{nm} * 370 = 20\text{mA}$
  - $R_{out} = V_{dd}/I_{drive} = 50\Omega$





# Idea

- Signal propagates as wave down transmission line
  - Delay linear in wire length
  - Speed
  - Impedance
- Behavior at end of line depends on termination
- Both src and sink are “ends” with reflections

$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$V_r = V_i \left( \frac{R - Z_0}{R + Z_0} \right)$$



# Transmission Line Agenda

---

- See in action in lab
- Where transmission lines arise?
- General wire formulation
- Lossless Transmission Line
- Impedance
- End of Transmission Line?
  - Open, short, matched
- Physical Geometry
- Discuss Lossy
- Implications/Effects

# Transmission Lines Specifics


---

Characteristics arise from their geometry


 
# Coaxial Cable

- ❑ Inner core conductor: radius  $r$
- ❑ Insulator: out to radius  $R$
- ❑ Outer core shield (ground)





$$L = \left( \frac{\mu}{2\pi} \right) \ln \left( \frac{R}{r} \right) \quad Z_0 = \left( \frac{1}{2\pi} \right) \left( \sqrt{\frac{\mu}{\epsilon}} \right) \ln \left( \frac{R}{r} \right)$$

- ❑ RG-58  $Z_0 = 50\Omega$  – networking
- ❑ RG-59  $Z_0 = 75\Omega$  – video
- ❑ HDMI  $Z_0 = 100\Omega$  – video


  
# Printed Circuit Board



- Stripline
  - Trace between ground planes



$$Z_0 = \left(\frac{1}{4}\right) \left(\sqrt{\frac{\mu}{\epsilon}}\right) \ln\left(\frac{1 + W/b}{t/b + W/b}\right)$$
  
# Printed Circuit Board

- Microstrip line
  - Trace over single supply plane



$$Z_0 = \left( \frac{1}{2\pi} \right) \left( \sqrt{\frac{\mu}{(0.475\epsilon_r + 0.67)\epsilon_0}} \right) \ln \left( \frac{4h}{0.536W + 0.67t} \right)$$

# Twisted Pair

- Category 5 ethernet cable
  - $Z_0=100\Omega$
  - $w=0.64c_0$



# Implications

---







## Example (Preclass 7)

---

- ❑ 25 meter category-5e cable ( $Z_0=100\Omega$ ,  $w=0.64c$ )
  - $c = 3 \times 10^8$  m/s
- ❑ Supporting 1Gb/s ethernet
  - 4 pairs at 250Mb/s
- ❑ a) Time to send data from one end to the other?
- ❑ b) Time between bits at 250Mb/s?
- ❑ c) Bits on each pair in the cable?



# Pipeline Bits

---

- For properly terminated transmission line
  - Do not need to wait for bits to arrive at sink
  - Can stick new bits onto wire



# Limits to Bit Pipelining (Preclass 8)


---

- What limits? (why only 250Mb/s)

# Limits to Bit Pipelining (Preclass 3)
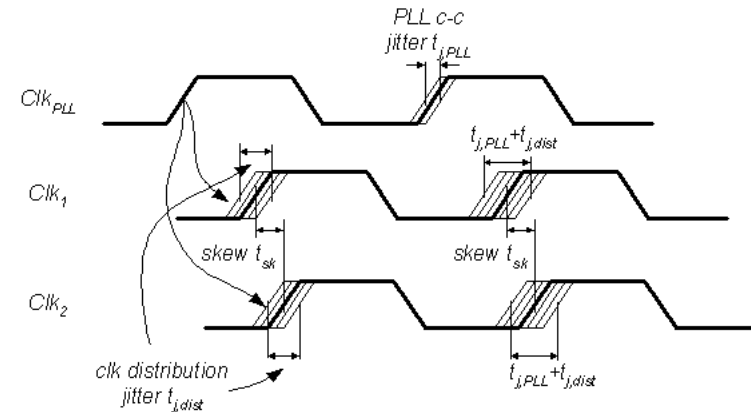
## □ What limits? (why only 250Mb/s)

- Rise time/signal distortion
- Clocking
  - Skew
  - Jitter
- For bus
  - Wire length differences between lines







# Termination / Mismatch

---

- ❑ Wires do look like these transmission lines
- ❑ We are terminating them in some way when we connect to chip (gate)
  - Need to be deliberate about how terminate, if we care about high performance

  
# Where is Mismatch?

- ❑ Vias
- ❑ Wire corners
- ❑ Branches
- ❑ Connectors
- ❑ Board-to-cable
- ❑ Cable-to-cable



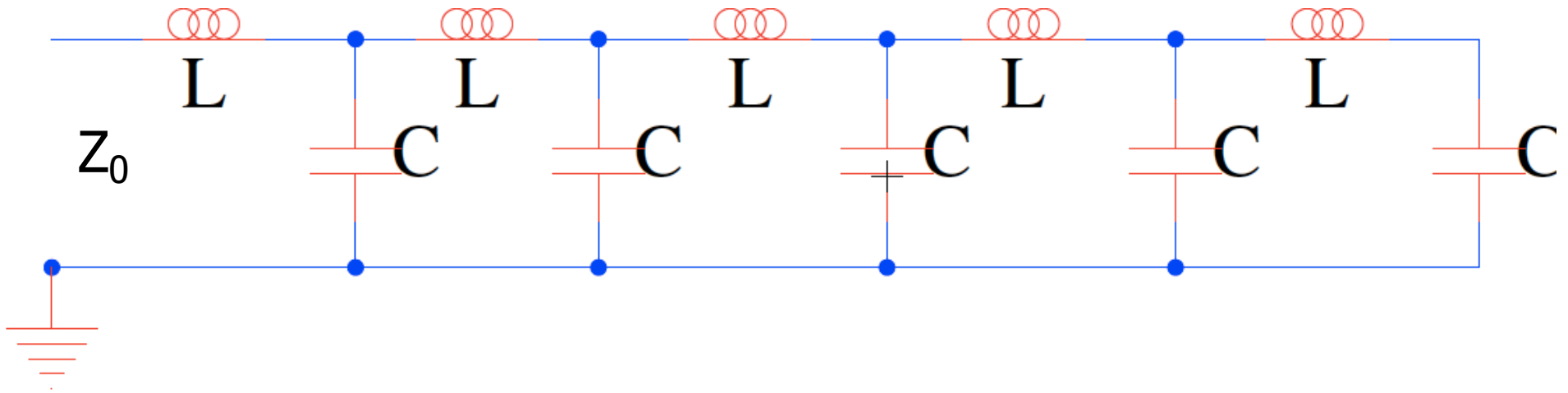
# Lossless Transmission Line

- What prevents us from having a 500km cat-5 cable?


 
# Lossy Transmission Line (Preclass 9)

- How do addition of R's change?
  - Concretely, discretely think about  $R=0.2\Omega$  every meter on  $Z_0=100\Omega$ 
    - what does each R do? Voltage impact?






# Lossy Transmission Line

- Each  $R$  is a mismatched termination

$$V_t = V_i \left( \frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right)$$

- Each  $R$  is a voltage divider

 
$$V_{i+1} = V_t \left( \frac{Z_0}{R + Z_0} \right)$$


 
# Lossy Transmission Line

$$V_{i+1} = V_i \left( \frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left( \frac{Z_0}{R + Z_0} \right)$$


$$V_{snk} = V_{src} \left( \left( \frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left( \frac{Z_0}{R + Z_0} \right) \right)^N$$


 
# Lossy Transmission Line (Preclass 9)


- How long before drop voltage by half?  
 $R=0.2\Omega$  every meter on  $Z_0=100\Omega$

$$V_{snk} = V_{src} \left( \left( \frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left( \frac{Z_0}{R + Z_0} \right) \right)^N$$


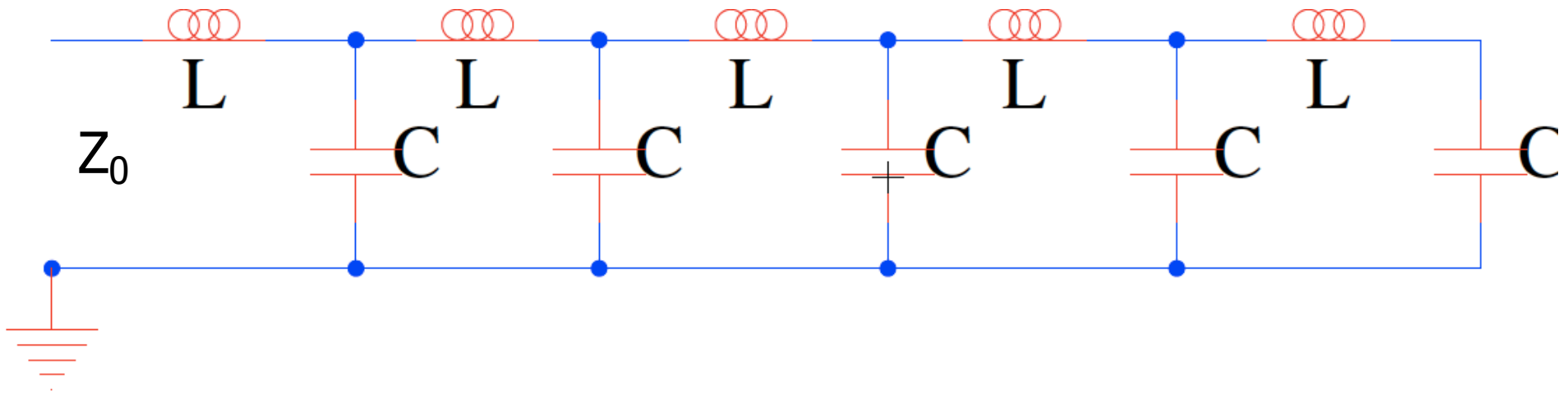
# Lossless Transmission Line

- What prevents us from having a 500km cat-5 cable?
  - Not actually lossless!



# More Examples...


---

Time Permitting


 
# Impedance Change (Preclass 10)

- What happens if there is an impedance change in the wire?  $Z_0=75\Omega$ ,  $Z_1=50\Omega$ 
  - What reflections and transmission do we get?



# $Z_0=75, Z_1=50$ (Preclass 10)


□ At junction:

■ Reflects

■  $V_r = (50-75)/(50+75)V_i = -0.2V_i$

■ Transmits

■  $V_t = (100/(50+75))V_i = 0.8V_i$

 

$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_r$$

$$V_i \left( \frac{2R}{R + Z_0} \right) = V_t$$

# Impedance Change $Z_0=75$ , $Z_1=50$ (Preclass 10)


At junction:

Reflects


$$V_r = -0.2V_i$$

Transmits

$$V_t = 0.8V_i$$

 


Mismatch Transmission Line

 


S



# What happens at branch?

 


Assume all  $50\Omega$

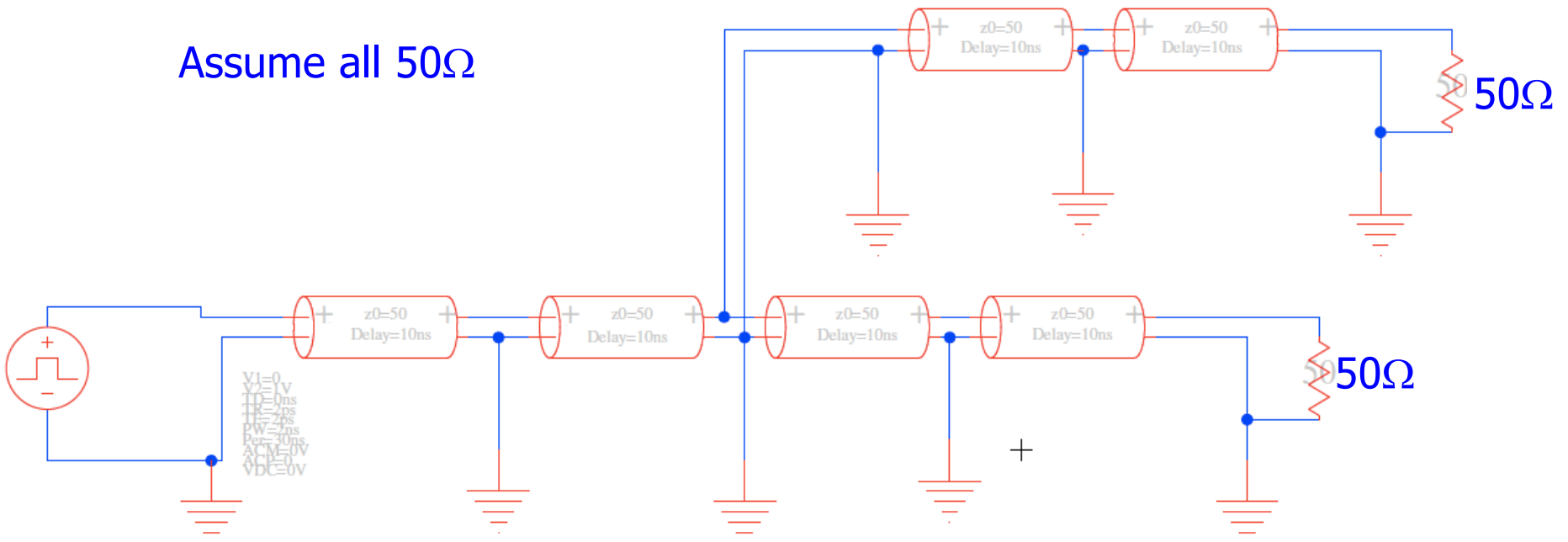
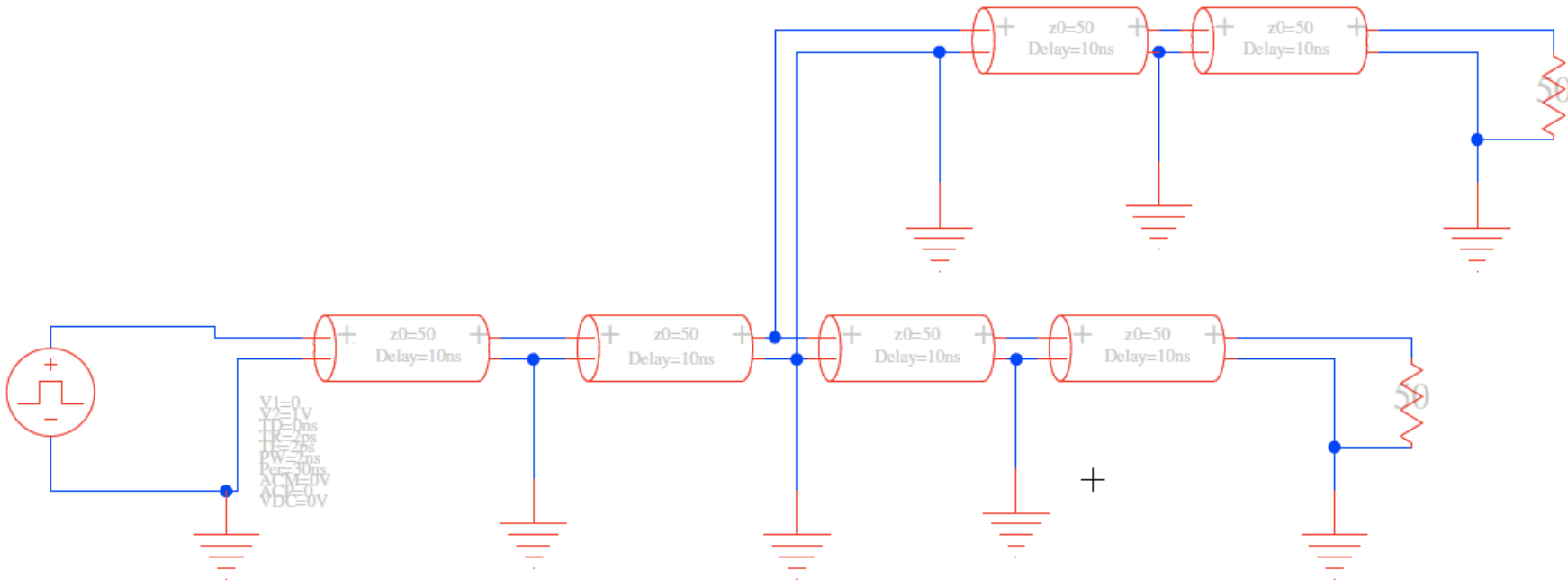
# Branch (preclass 11)

- Transmission line sees two  $Z_0$  in parallel
  - Looks like  $Z_0/2$



$$Z_0 = 50, Z_1 = 25$$


□ At junction:

■ Reflects

■  $V_r = (25 - 50) / (25 + 50) V_i = -0.33 V_i$

■ Transmits

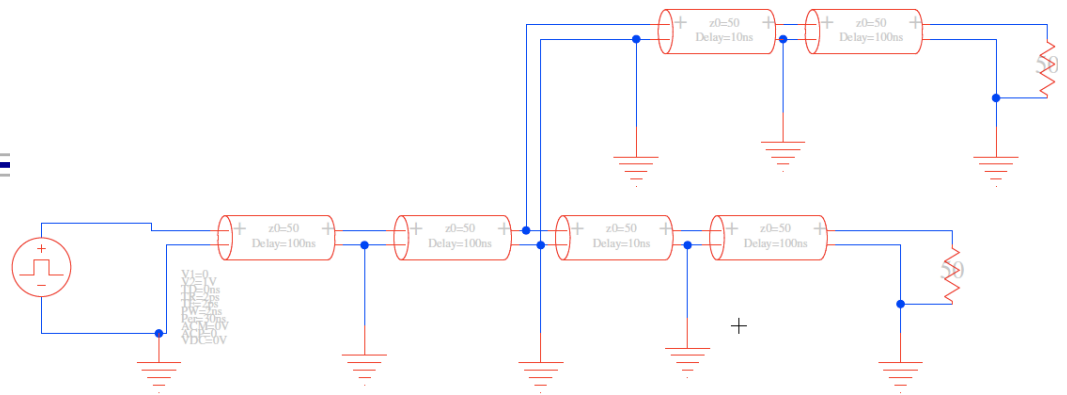■  $V_t = (50 / (25 + 50)) V_i = 0.67 V_i$




$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_r$$


$$V_i \left( \frac{2R}{R + Z_0} \right) = V_t$$
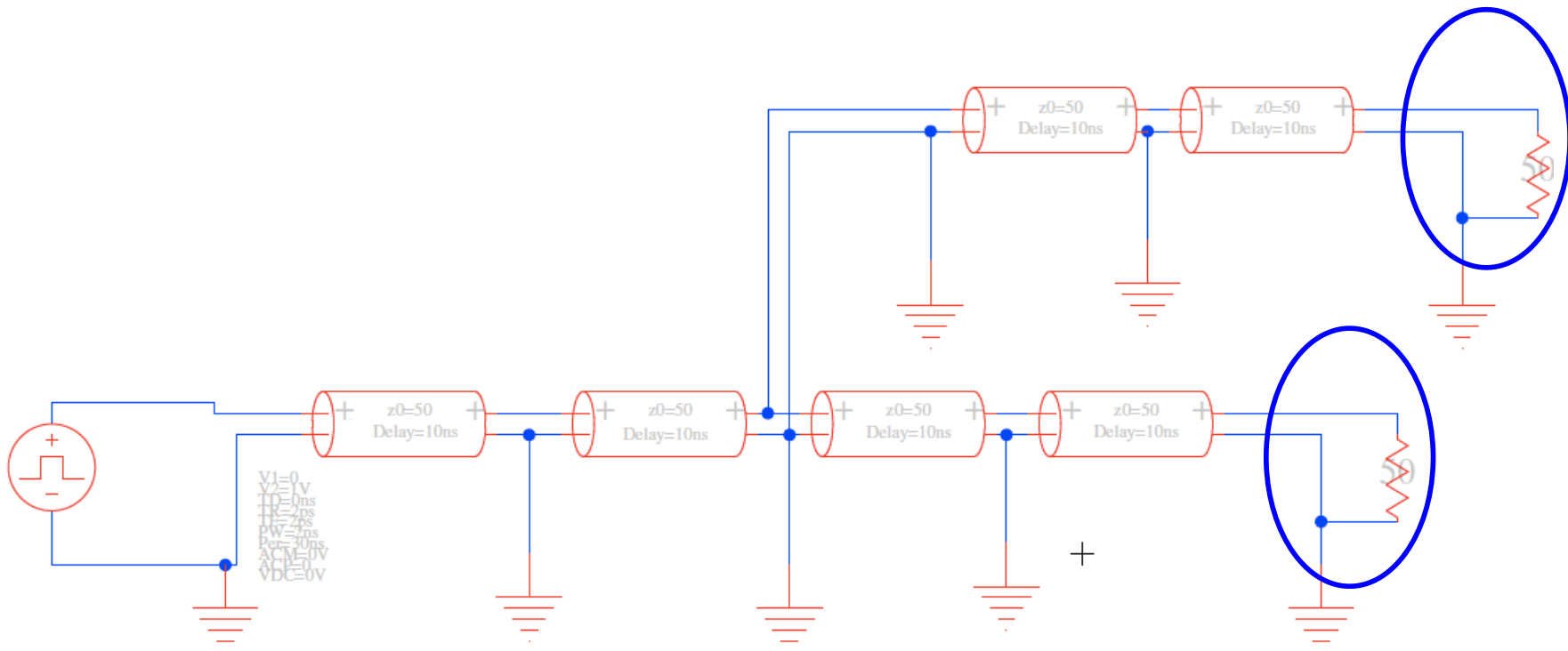
# End of Branch

- ❑ What happens at end?
- ❑ If ends in matched, parallel termination
  - No further reflections



# Branch Simulation

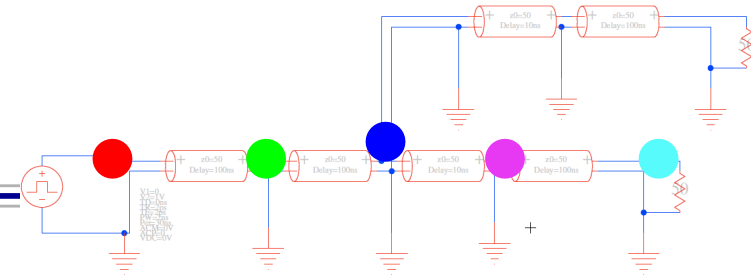

At junction:


Reflects

$$V_r = -0.33V_i$$

Transmits


$$V_t = 0.67V_i$$

Branch Line Termination

 

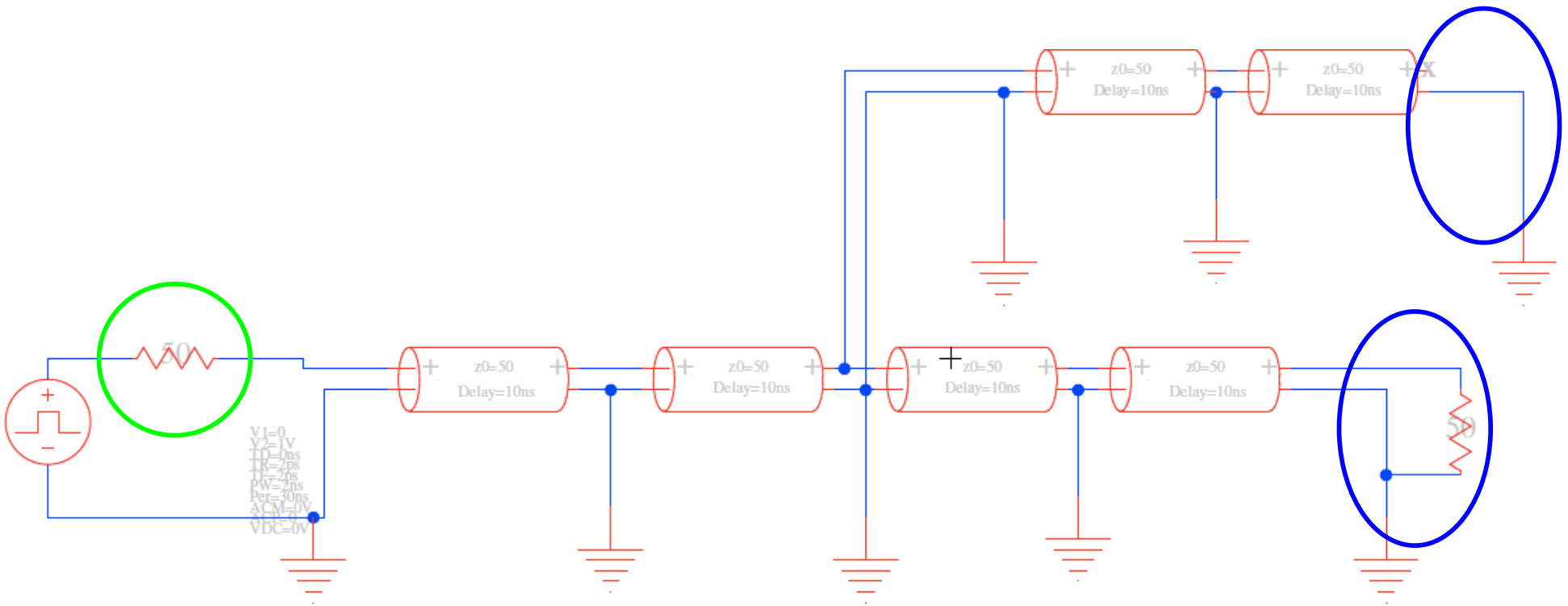
# Branch with Open Circuit?

- ❑ What happens if branch open circuit?
- ❑ And source termination?



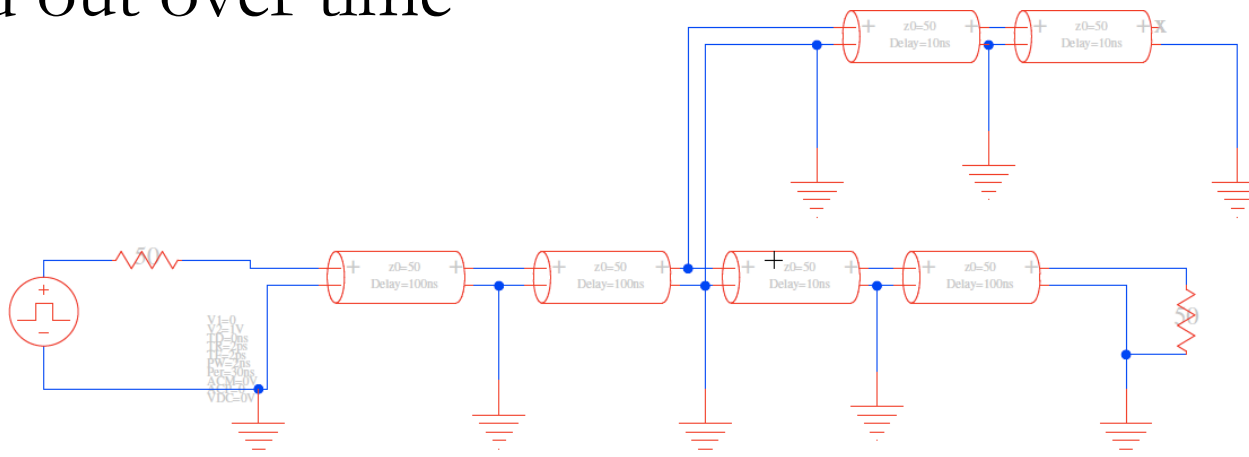
# Branch with Open Circuit


- ❑ Reflects at end of open-circuit stub
- ❑ Reflection returns to branch
  - ...and encounters branch again
  - Send transmission pulse to both
    - Source and other branch
- ❑ Sink sees original pulse as multiple smaller pulses spread out over time



# Open Branch Simulation

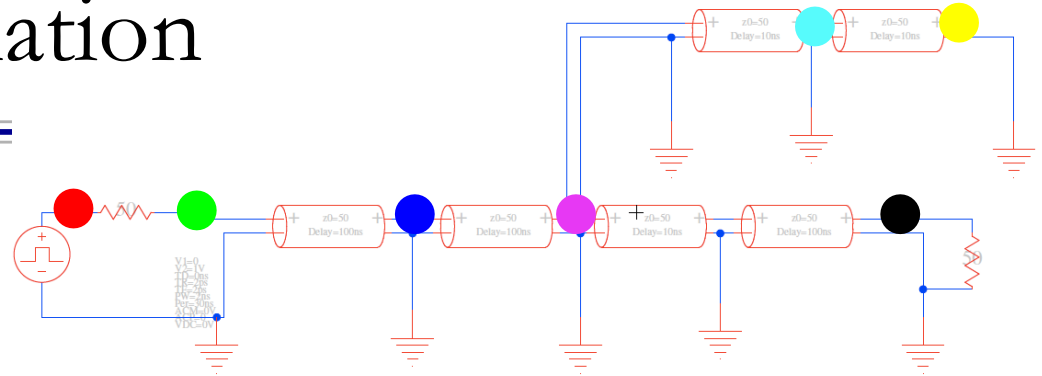


Branch Open Line

 




# Open Branch Simulation

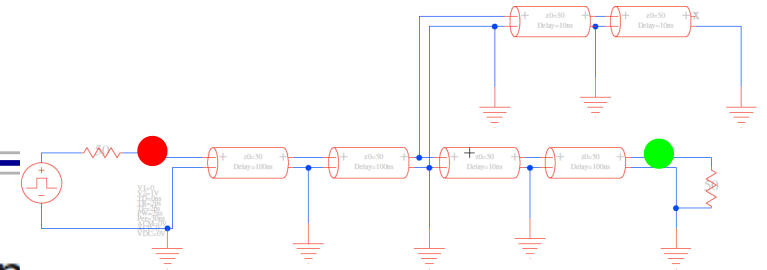

Branch Open Line

 



# Transmission Line Noise

---

- ❑ Frequency limits
- ❑ Imperfect termination
- ❑ Mismatched segments/junctions/vias/connectors
- ❑ Loss due to resistance in line
  - Limits length



# Idea

---

- ❑ Transmission lines
  - high-speed
  - high throughput
  - long-distance signaling
- ❑ Termination
- ❑ Signal quality losses

$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$V_r = V_i \left( \frac{R - Z_0}{R + Z_0} \right)$$



# Admin

---

- ❑ Wednesday 5/1 Project 2 Due
  - Can turn it in up to Friday 5/3 midnight with no penalty
    - No submissions accepted after 5/3
- ❑ Final (T 5/7)
  - 3-5pm in Towne 311
  - Cumulative: Lec 1 – 19
    - Big Idea slides from each lecture
  - Finals 2010—2021 online
    - Coverage was different
  - Wednesday lecture review/course summary
  - TA review session F 5/3 3-5pm, Towne 307