

ESE3700: Circuit Level Modeling, Design, and Optimization for Digital Systems


Lec 22: May 1, 2024
Review

Objective

- At circuit level, how do we implement robust digital systems that are...

- High-speed
- Low-power
- Area-efficient

with given technology

 

3rd generation Intel Core


Learning

- How to **model** digital logic and reason about behaviors and performances
- How to **design** circuits and perform simulations for functional verification and performance analysis
- How to **optimize** circuits using various techniques

CMOS Logic


- Complementary metal-oxide semiconductor
- PMOS pullup network implements f
- NMOS pulldown network implements f'

-Why not the other way around?

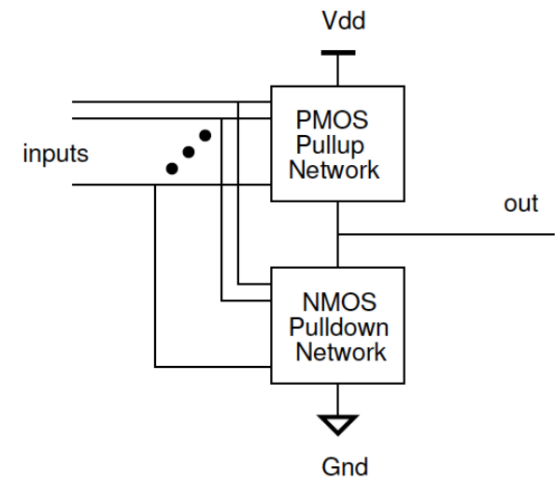



MOSFET Model

 - Zeroth-order model:
 - Transistor as switch
- First order model:
 - Transistor as resistive driver (R_{on})
 - Transistor's gate as capacitive load (C_g)
- What do models tell?
 - Reason about logic
 - Reason about RC delay



MOSFET Model

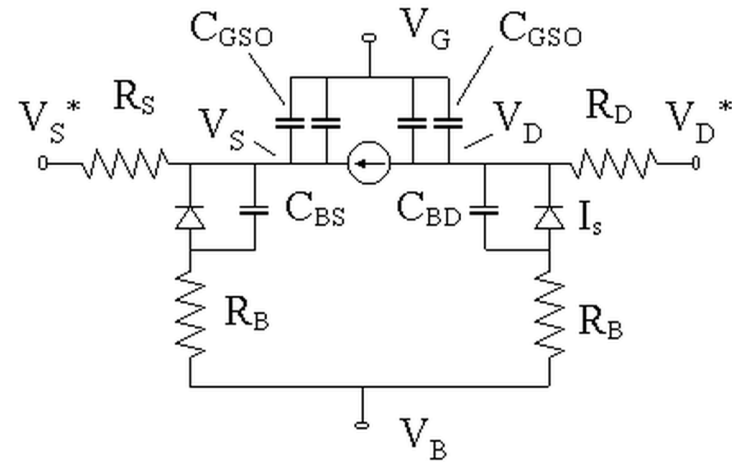 - Spice model of NMOS
- Parameters should look familiar



http://ecee.colorado.edu/~bart/book/book/chapter7/ch7_5.htm

Restoration

- Output not going to rail
- Noise problems

-Consequence?

→ Voltage seen at the input can be degraded

-What can we do?

→ Restoration with proper noise margins


Definition:

$$NM_h = V_{oh} - V_{ih}$$

: How much “high” output voltage can drop and still be recognized as “high”

$$NM_l = V_{il} - V_{ol}$$

 : How much “low” output voltage can rise and still be recognized as “low”




Restoration

- Necessity observed throughout the course
 - Pass-transistor signal degradation (i.e. $V_{dd} - V_{thn}$)
 - Ratioed-logic noise margin
 - Inductive noise
 - Crosstalk noise
 - Reflections
- Becomes more important as the circuit complexity increases
 - Want to maintain robust signal everywhere


MOS Transistor Operation

 - Operating regions:
 - Sub-threshold (cutoff), $V_{gs} < V_{th}$
 - Resistive (linear), $V_{gs} > V_{th}$
 - Saturation (active), $V_{ds} > V_{gs} - V_{th}$
- Strength scales by (W/L)
- Channel as varying resistance
- Short channel effects
 - Velocity saturation
 - Drain-Induced Barrier Lowering (DIBL)
 - Hot electron effect





MOS Transistor Capacitance

 - Capacitances at each terminal of the transistor
- Capacitances vary with V_{gs} (operating region)
- Implications...?
→ Overshooting



Layout

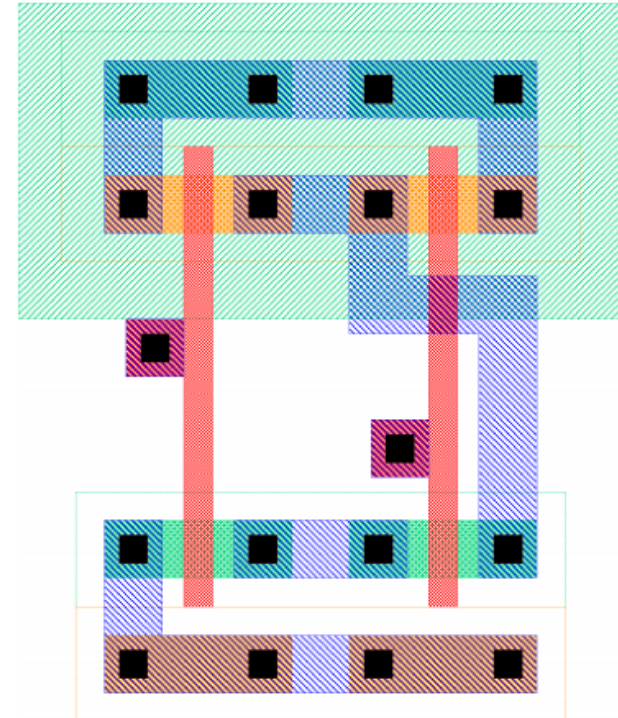 - Can identify what each part of layout is/does
- Design rules for fabrication
- Multiple metal layers for routing
- Bigger picture?
 - Interconnect and parasitics
 - Effects on performance




Scaling

- 32nm → 22nm → 14nm → 7nm
 - Final ITSR report 2015
- Observed scaling of:

Area, capacitance, resistance, threshold, current, gate delay, wire delay, and power

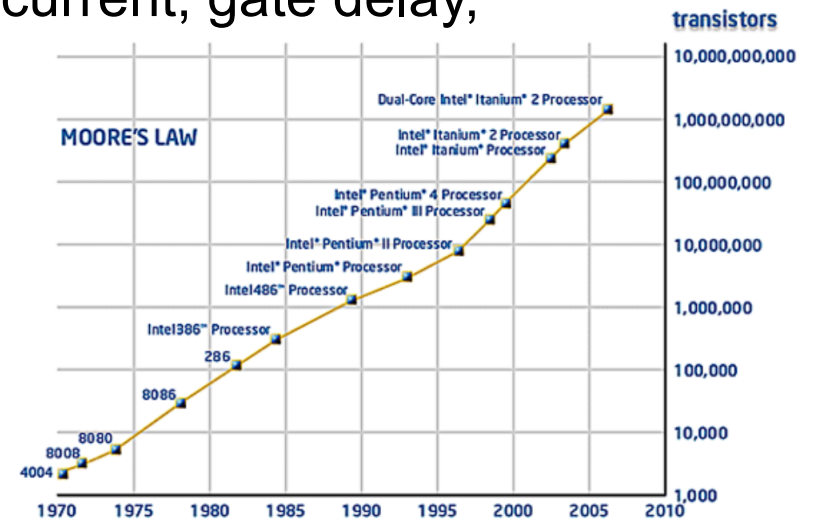- Will Moore's law continue?
- Implications:
 - Material-science view
 - Power density limits
 - Other options for improvement...



τ Model




- $\tau = R_0C_0$ modeling for delay
- Impact of transistor sizing (W and L) on R and C
- Fan-out, driving stages, and sizing
 - i.e. Multiple inverter stages
- Identify worst case delay scenarios for different gates
- Tradeoff between large gates vs small gates (# stages, fanin/fanout)

$$C = \epsilon_r \epsilon_0 \frac{A}{d}$$

$$R = \frac{\rho L}{A}$$



Driving Large Load

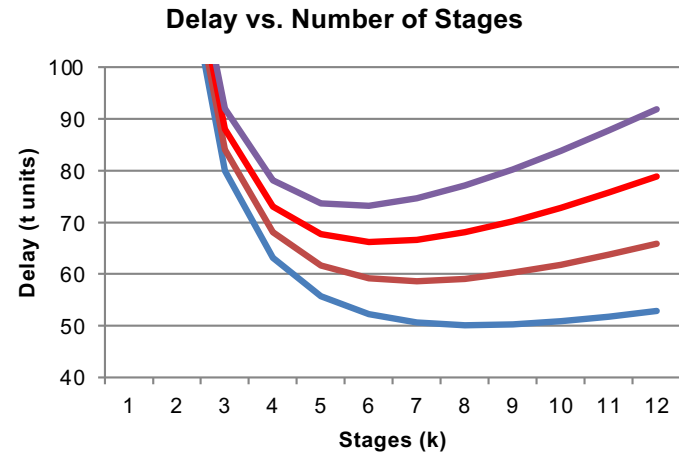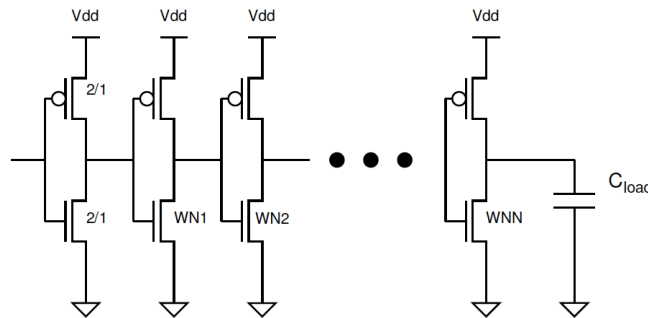 - To drive large loads
 - Scale buffers geometrically
 - Exponential scale up in buffer size ($r = e$)
- Scale factor: 3—4 typically
 - One origin of fanout 4 target



Repeaters in Wiring

  - Observed delay problems in RC chain
 - Delay will scale by L^2 (N^2)
 - Elmore delay
- How do we minimize delay?
 - Buffer the wires
- Parameters to consider for buffering
 - # of buffers
 - Length of segment
 - Size of buffers



Repeaters in Wiring


- Insights
 - Length of optimal segment is a function of technology (not a function of length of wire)
 - Same applies to the buffer sizing
 - Delay scales linearly in length with proper buffering
- Food for thought
 - Is buffering energy-efficient?

$$L_{seg}^* = \frac{L}{N} = \sqrt{2 \left(\frac{R_{buf} \times (C_{self} + C_{load})}{R_u \times C_u} \right)}$$

$$W = \sqrt{\frac{R_0 \times C_{wire}}{R_{wire} \times 2C_0}}$$

Energy and Power

 - Static
 - Subthreshold leakage, gate-drain leakage
- Capacitive switching
 - Charge & discharge output load
- Short Circuit
 - When both N and P devices are on



Energy and Power

- Why Important...?

Capacitive Switching

$$E = V_{dd} \int I(t) dt$$

$$Q = CV = \int I(t) dt$$

$$E = CV_{dd}^2$$

Short Circuit

$$Q=I \times t$$

$$Q=CV$$

$$E = V_{dd} \times \left(I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right) \right)$$

$$E = V_{dd} \times Q_{sc}$$

$$E = C_{sc} V_{dd}^2$$

Static

$$I_{DS} = I_S \left(\frac{W}{L} \right) e^{\left(\frac{V_{GS}}{nkT/q} \right)} \left(1 - e^{-\left(\frac{V_{DS}}{kT/q} \right)} \right) (1 + \lambda V_{DS})$$

Energy and Power Optimization

- Ignoring leakage,
 - Energy proportional to V^2
 - Delay proportional to $1/V$
 - $E\tau$ - Energy & delay tradeoff
 - V_{th} effect on
 - Speed
 - Switching energy
 - Leakage energy
 - From project, logic family, logic optimization, sizing, ...
Rich energy optimization space to explore
- $P_{tot} = P_{static} + P_{sc} + P_{dyn}$
 - $P_{dyn} + P_{sc} = a(\frac{1}{2}C_{load} + C_{sc})V^2f$
 - $P_{tot} \approx a(\frac{1}{2}C_{load} + C_{sc})V^2f + VI'_s(W/L)e^{-Vt/(nkT/q)}$

Ratioed Logic

- Build single pull-up (pull-down) control network
- Compared to CMOS,


Pros:

- Less transistor
- Less area...?
- Less capacitive load...?

Cons:

- Constant power dissipation
- Need careful sizing (noise margin)

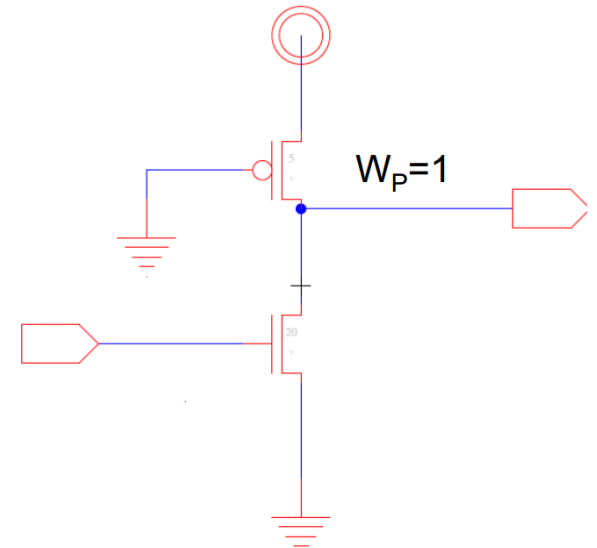Tradeoff between noise margin and area & capacitance



Pass Transistor Logic

- Simple switch-based logic
- Compared to CMOS,

Pros:


- Less transistor...?
- Less area...?
- Less capacitive load...?

Cons:


- Needs restoration (buffering)
- Can be slow
- Limited voltage lowering for energy reduction

Pass transistor with restoration stages vs CMOS

 Needs to take into account diffusion capacitance, $\forall C_g \rightarrow$ Elmore delay




Idea: Design Space Explore

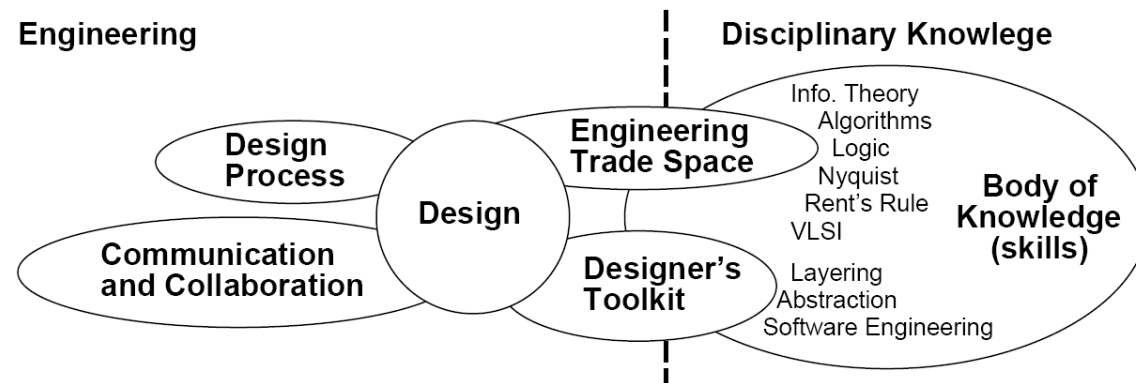

- Identify options
 - All the knobs you can turn
 - Topology
 - (A) Gate choice, logical optimization (B) Fanin, fanout, (C) Serial vs. parallel
 - Gate style / logic family
 - (D) CMOS, Ratioed (N load, P load)
 - (E) Transistor Sizing (F) Vdd (G) Vth
- Explore space systematically and formulate continuum where possible

Elmore Delay

 - Chain of pass-transistors modeled into RC chain
- Cannot use simple τ model for delay (What if $v = 0$?)
- Use refined model for more accurate delay calculation
- Where else do we observe RC chain?
- Wire




- Using elmore model,

$$\begin{aligned}
 & R_{unit} \cdot (N \cdot C_{unit}) + R_{unit} \cdot ((N-1) \cdot C_{unit}) \\
 & \quad + R_{unit} \cdot (N-2) \cdot C_{unit} + \dots + R_{unit} \cdot C_{unit} \\
 & = (R_{unit} \cdot C_{unit}) \cdot (N + N-1 + N-2 + \dots + 1) \\
 & = R_{unit} \cdot C_{unit} \cdot N^2 / 2
 \end{aligned}$$

$$\text{Delay} = \sum_{\text{path}} \left(R_i \times \sum_{i \xrightarrow{\text{path}} j} C_j \right)$$


Synchronous Circuits & Clocking

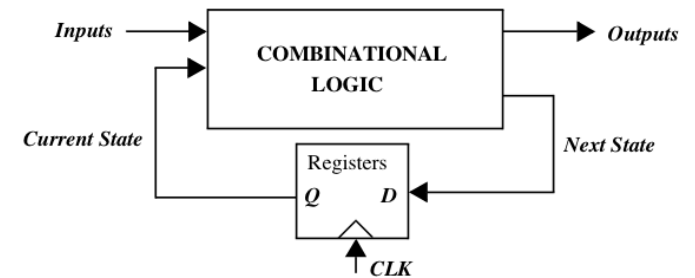- Reuse logic resources
→ Add state elements (latches, registers)
- Clocking discipline
 - Setup and hold times
 - $\text{clk} \rightarrow \text{q}$ delay for data output from state element




$$T \geq t_{c-q} + t_{plogic} + t_{su}$$
 
$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$




Dynamic Logic

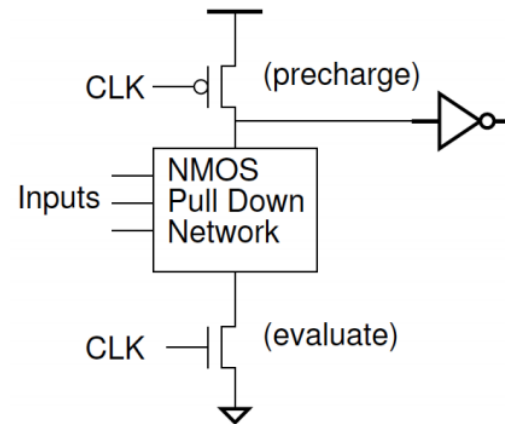- Clocking can be used for dynamic logic family
 - Domino logic
- Disable pull-up (pull-down) during evaluation; no static power
 - Needs precharge for disabling next-stage NMOS evaluation
 - Can involve extra clocking energy, precharge energy, complexity



Memory

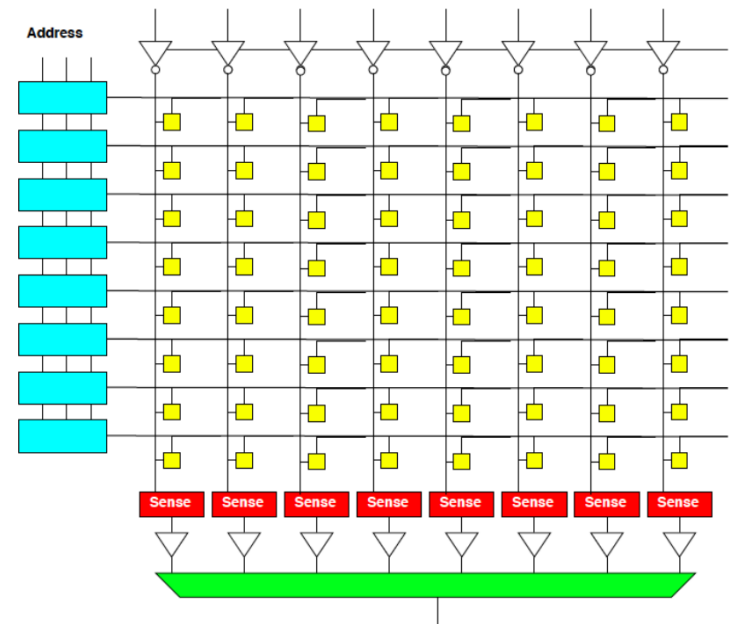- Memory bank organized for
 - Economic wire and area usage
 - Maximize storage density
 - Share peripherals
- Main components:
 - SRAM Memory cell: cross-coupled inv.
 - Write drivers (tristate buffers)
 - Decoder (column/row)
 - Precharge
 - Sense amplifier



Memory

- What did we use to build?
 - CMOS
 - Memory cell cross-coupled inverter
 - Buffers
 - Pass transistor
 - Access transistor
 - Decoder
 - Ratioed Logic
 - NAND/NOR ROM
 - 6T SRAM sizing


And more for energy optimization...

Memory

- Robustness
 - Charge-sharing effect and read-write upsets
 - Need to carefully size cell
 - One solution was to use pre-charge of $V_{dd}/2$
 - Prevent voltage swing and read-write upset
- Scaling
 - Deeper (more rows) memory will need strong driver and precharge
 - Wider (more columns) memory will need strong addressing
- Implications
 - Want to use high V_{th} from energy stand-point (sacrifice speed for energy)
 - Routing wires also scale with memory size
 - Need to be concerned about parasitic capacitances, crosstalk, noise...

Inductive Noise

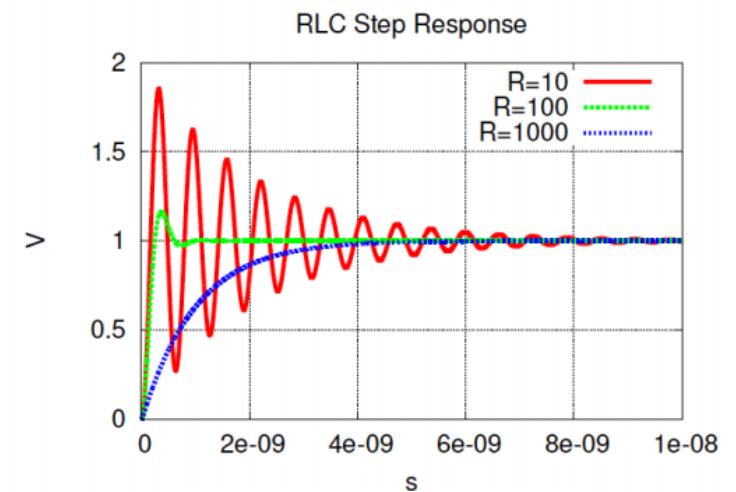
- Sources?
 - Wire (scales with length)
 - Bond & package pins
- Where?
 - Signal paths and power supplies
- Problems?
 - RLC response
 - Oscillation can dominate (HW8)
- Solutions?
 - Make wire short
 - Bypass capacitor (Lab 2)



$$R < \sqrt{\frac{4L}{C}}$$

Crosstalk

 - Sources?
 - Wire (scales with size/spacing)
- Where?
 - Cables
 - PCB wires
- Problems?
 - Noise
 - Spurious transition
- Solutions?
 - Orthogonal routing
 - Increase pitch
 - Separate with ground/power shield wires (lab2)



Transmission Lines

- From LC lossless transmission line model
 - Signal propagates as wave down transmission line
- Behaviour at the end of the line is determined by termination type (short, open, or specific impedance)
- Where would the termination matching be important?
 - Vias
 - Branches
 - Cable-to-cable
 - Board-to-cable

$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

$$V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_r$$

$$V_i \left(\frac{R - Z_0}{R + Z_0} + 1 \right) = V_t$$

Admin

- Wednesday 5/1 Project 2 Due
- Can turn it in up to Friday 5/3 midnight with no penalty

- Final (T 5/7) 3-5pm in Towne 311
- TA review session F 5/3 3-5pm, Towne 307