 


Assume V_{in} is 0 for $t < 0$ and steps to 1V at $t = 0$.

1. What value does $V_{measure}$ take on as $t \rightarrow \infty$?

2. Assume V_{in} is 0 for $t < 0$ and steps to 1V at $t = 0$. The circuit is then allowed to achieve steady-state.




- (a) What is the final value of $V_{measure}$? What is the time constant, τ ?
- (b) How many seconds does it take before $V_{measure}$ reaches 90% of the final value? Use the table below and $e = 2.72$.

t (in ps)	$e^{-t/\tau}$	$1 - e^{-t/\tau}$
0		
0.1		
1		
2		
2.3		


(c) At what time does $V_{measure}$ reach 50% of its value? Use $\ln(0.5) = -0.69$.

 3. Assume each gate puts a load of 1 on each of its two inputs. (All intersecting wires are **not** connected)



What is the load on the most heavily loaded gate output?	
What is the load on the least heavily loaded gate output?	

 4. Assuming $R_{on,p}=R_{on,n}=R_{on}$, what are all the possible equivalent resistance values of the gate output stage?




Hint: How many cases are there? What is the resistance for each of the cases?


Case	Resistance

REFERENCE:






N-type MOSFET

 



Zero-Order Model

 

First-Order Model

     

I_{ds} unbounded when $V_{gs} > V_{th}$

  

(even this is a simplified approximation)

Step at $V_{gs} = V_{th}$

Reminder:

	NMOS	PMOS
Threshold	$V_{thn} > 0$	$V_{thp} < 0$ $V_{thp} \approx -V_{thn}$
Conduct	positive input $V_{gs} > V_{thn}$	negative input $V_{gs} < V_{thp}$
Drain	most positive terminal	most negative terminal
Source	most negative terminal (source of electrons)	most positive terminal (source of holes)

$$V_{gs} = V_g - V_s \tag{1}$$