

# ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 7: February 14, 2024

Layout and Area, MOS Scaling




# One Parasitic Capacitance Implication

---

Feedback Capacitance  $C_{gd}$
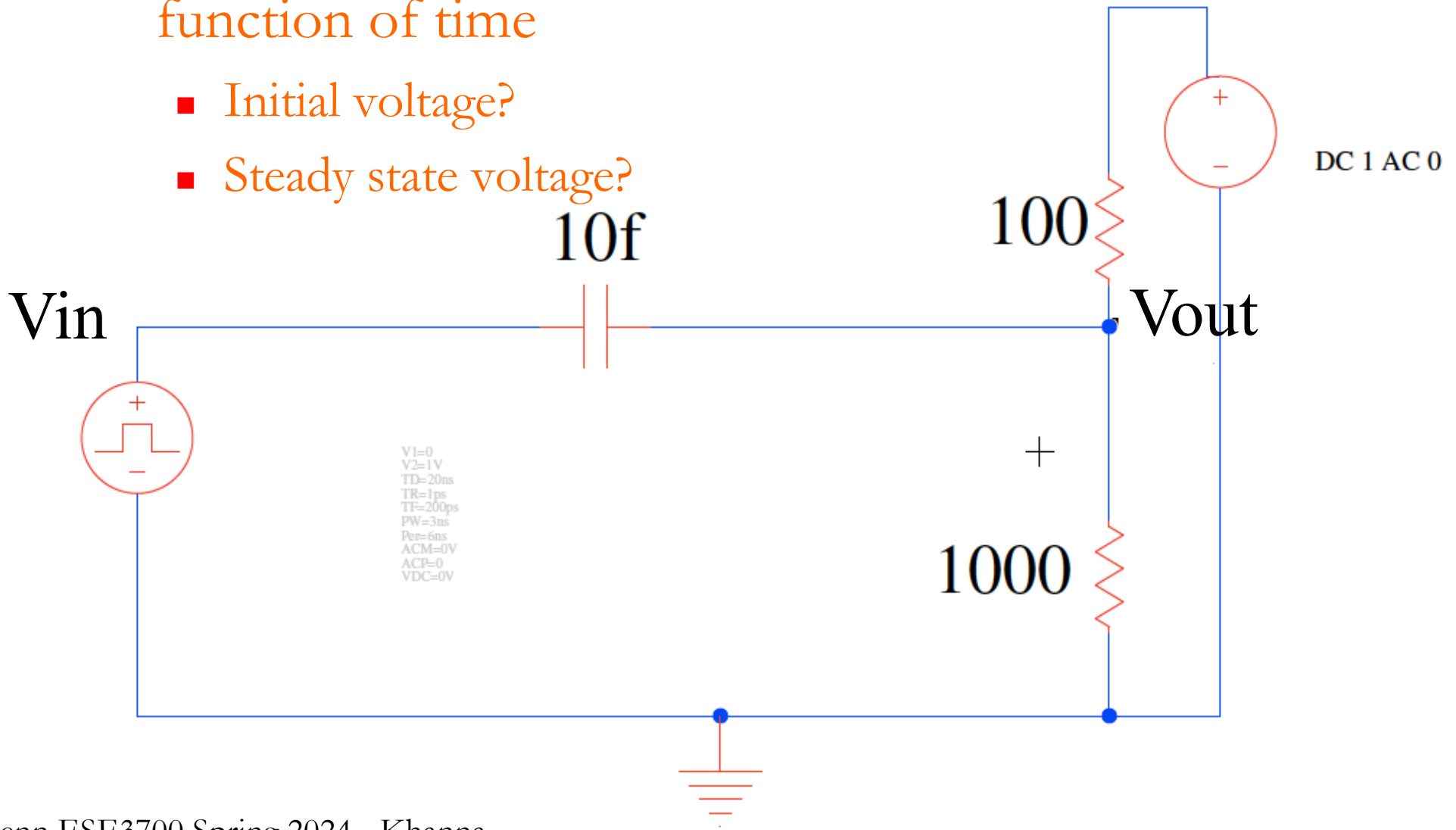
# Step Response? (Preclass 1)


- $V_{in}$  steps from 0 to 1, what does  $V_{out}$  look like as a function of time
  - Initial voltage?
  - Steady state voltage?





# Step Response


Voltage peaking!

 


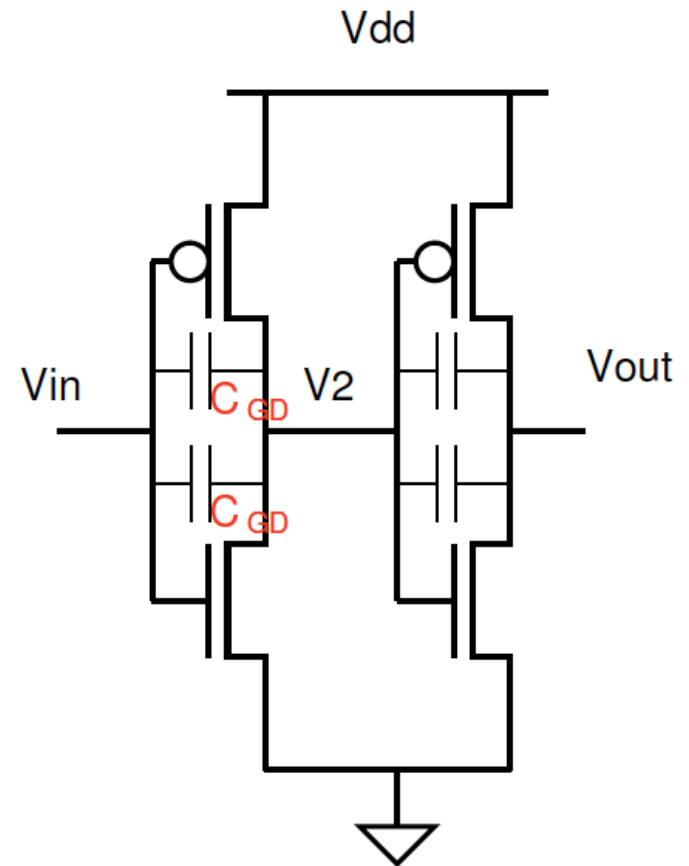
# Impact of $C_{GD}$


- What does  $C_{GD}$  do to the switching response here?
  - $V_2$
  - $V_{out}$




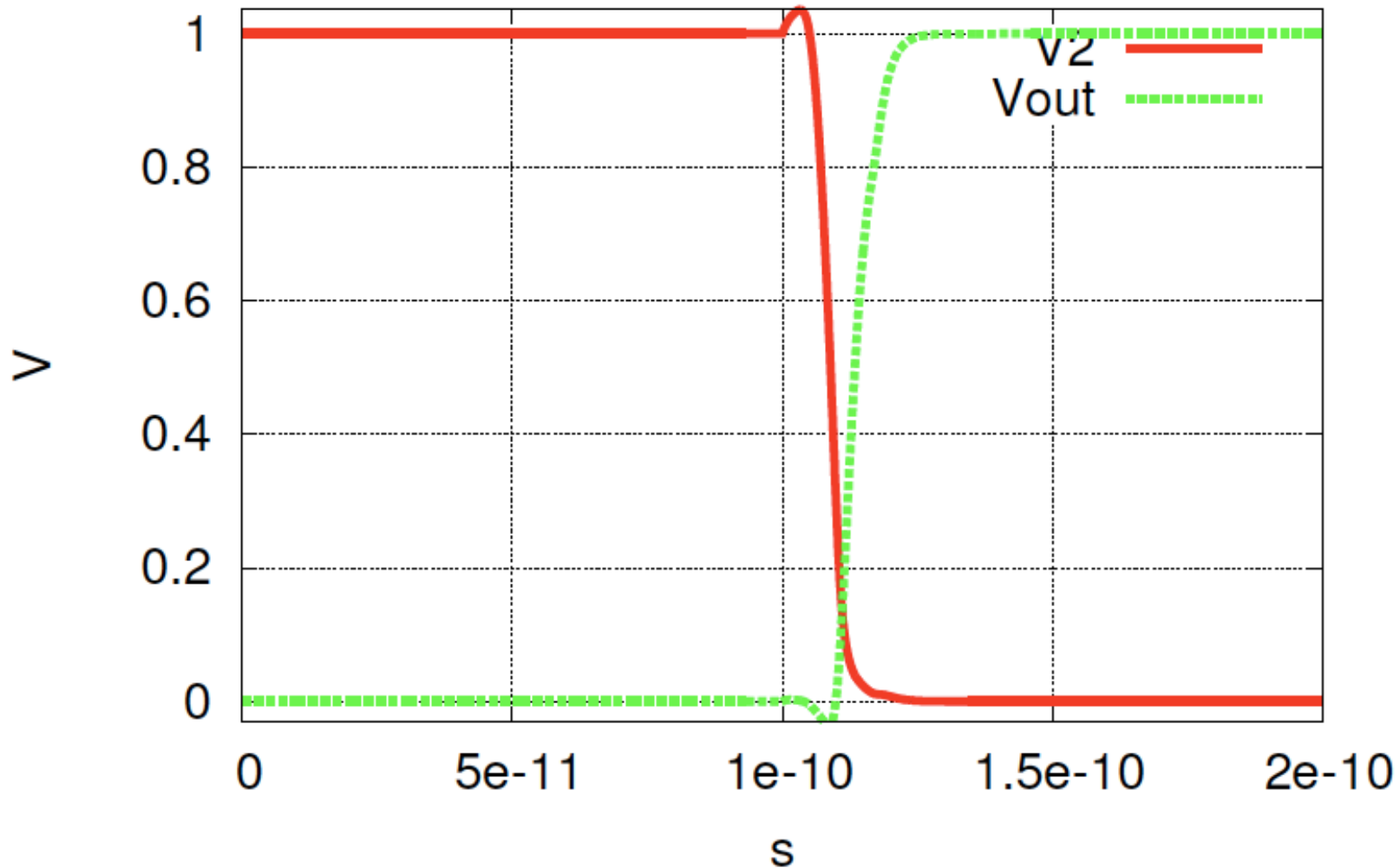
# Impact of $C_{GD}$

\*\*\* spice deck for cell flat\_inv{sch} from library test





# Today

---


- Layout
  - Transistors
  - Gates
- Design rules
- Standard cells
- VLSI Scaling Trends/Disciplines



# Transistor




Side view

 

Perspective view
 
# Layout


- ❑ Sizing & positioning of transistors
- ❑ Designer controls  $W$ ,  $L$
- ❑  $t_{\text{ox}}$  fixed for process
  - Sometimes thick/thin oxide “flavors”






# NMOS Geometry

---

 


Top view

 

Perspective view
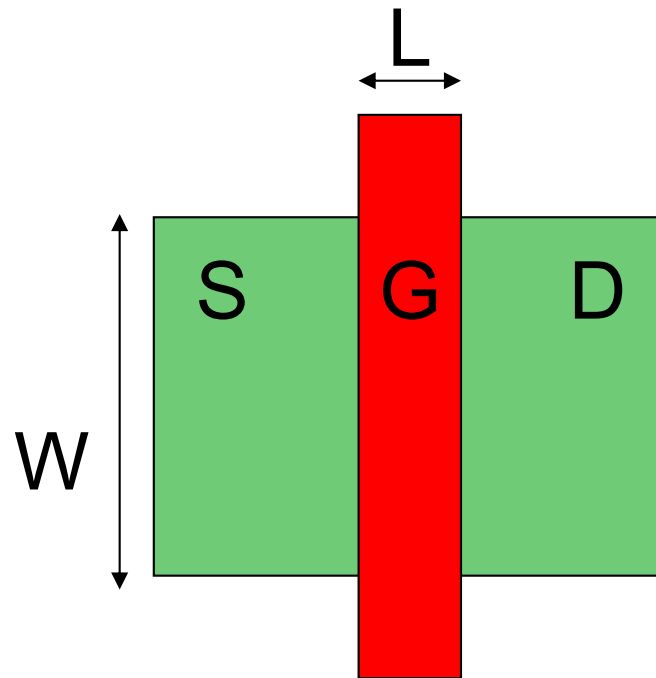
# NMOS Geometry


- Color scheme
  - Red: gate (polysilicon material)
  - Green: source and drain areas (n type diffusion)



Top view
 
# NMOS vs PMOS

- ❑ NMOS built on p substrate
- ❑ PMOS built on n substrate
  - Needs an N-well




Rabaey text, Fig 2.1





 
# PMOS Geometry

- Color scheme
  - Red: gate
  - Orange: source and drain areas (p type)
  - Green: n well
- NMOS built on p wafer
  - Must add n well material to build PMOS



 
 
 
# Body Contact

- ❑ “Fourth terminal”
- ❑ Needed to set voltage around device
  - PMOS:  $V_b = V_{dd}$
  - NMOS:  $V_b = GND$
- ❑ At right: PMOS (orange) with bulk contact (dark green)



  
 
# Body Contact

- ❑ Needed to set voltage around device
  - PMOS:  $V_b = V_{dd}$
  - NMOS:  $V_b = \text{GND}$
- ❑ What happens if NMOS body contact is  $V_{dd}$ ?
  - Polarity of field wrong
  - Increase  $V_{th}$  (need higher voltage to invert the channel)





# Transistor Geometry

  


NMOS

PMOS

B S G D

D G S B

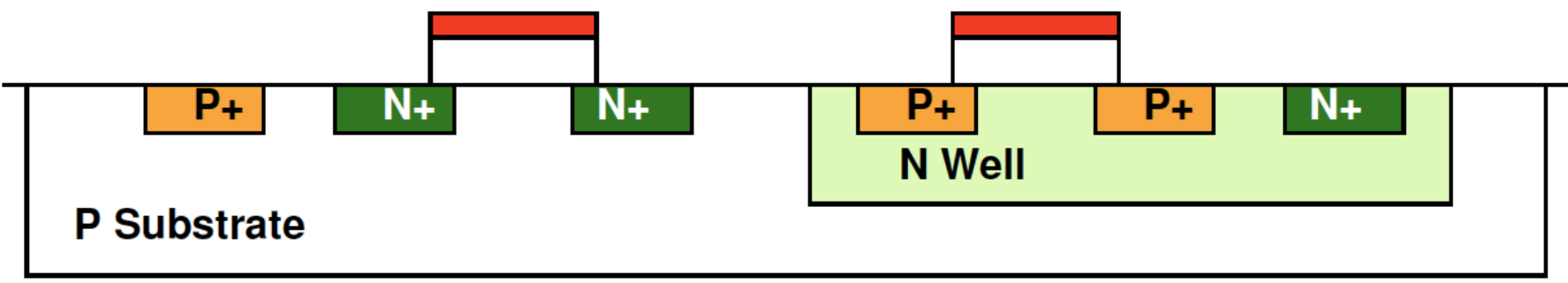


P Substrate

N Well

 
# Interconnect

- Connect transistors
  - Different layers of metal
    - “Contact” - metal to transistor
    - “Via” - metal to metal



 
# Interconnect

- Connect transistors
  - Different layers of metal
    - “Contact” - metal to transistor
    - “Via” - metal to metal




# Interconnect Cross Section

 

ITRS 2007


 
# Masks

- ❑ Define areas want to see in layer
  - Think of “stencil” for material deposition
- ❑ Use photoresist (PR) to form the “stencil”
  - Grow PR over entire wafer
  - Expose PR through mask
  - PR dissolves in exposed areas
  - Material is deposited/etched
    - Only “sticks” in area w/ dissolved PR




  
# Reverse Engineer Inverter Layout (Preclass 2)







# Layout Revisited

---


- How to “decode” circuit from layout?

 

# Reverse Engineer Inverter Layout

 

# Reverse Engineer Inverter Layout





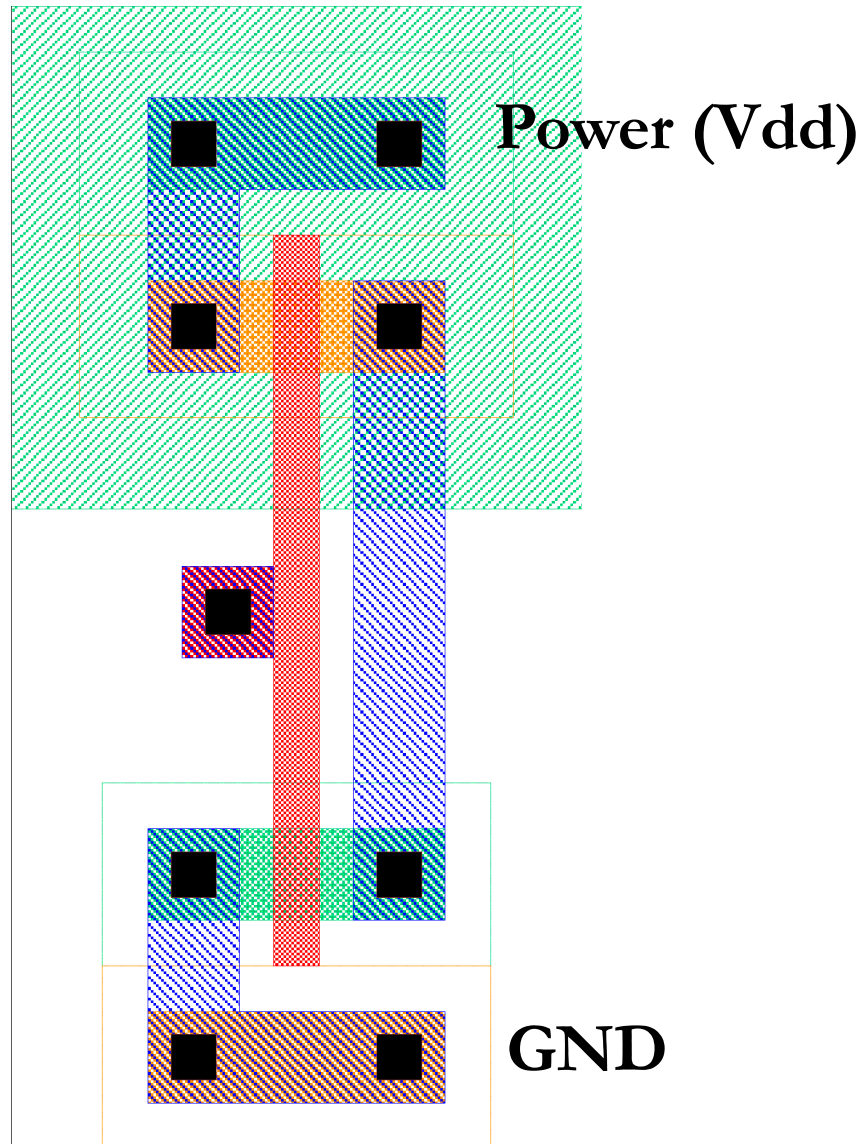


- Where is PMOS transistor?
- NMOS?



# Layout to Circuit


- 1. Identify transistors

     



# Inverter Layout

□ Where is Input?

 






# Inverter Layout


□ Where is Input?

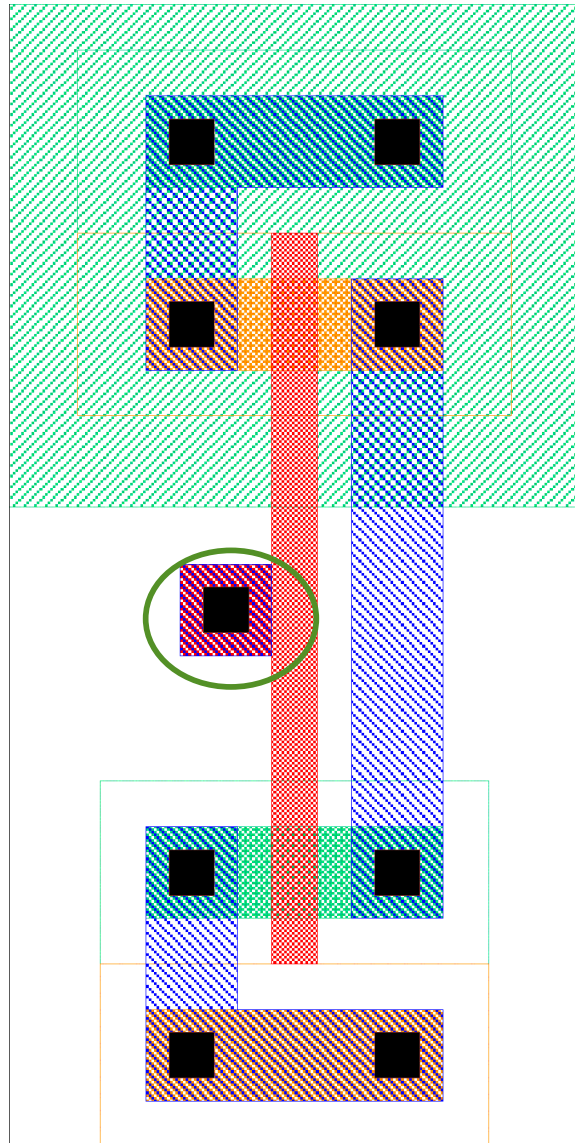



# Inverter Layout

□ Where is Output?

 







# Inverter Layout

□ Where is Output?

 




# Layout to Circuit

 


 - 2. Add connections
  - Drain connection







# Layout to Circuit

 


## □ 2. Add connections

### ■ Gate connection

  




# Layout to Circuit

 


 - 2. Add connections
  - pMOS-source to VDD







# Layout to Circuit

 

 - 2. Add connections
  - nMOS source to GND



# Typical N-Well CMOS Process





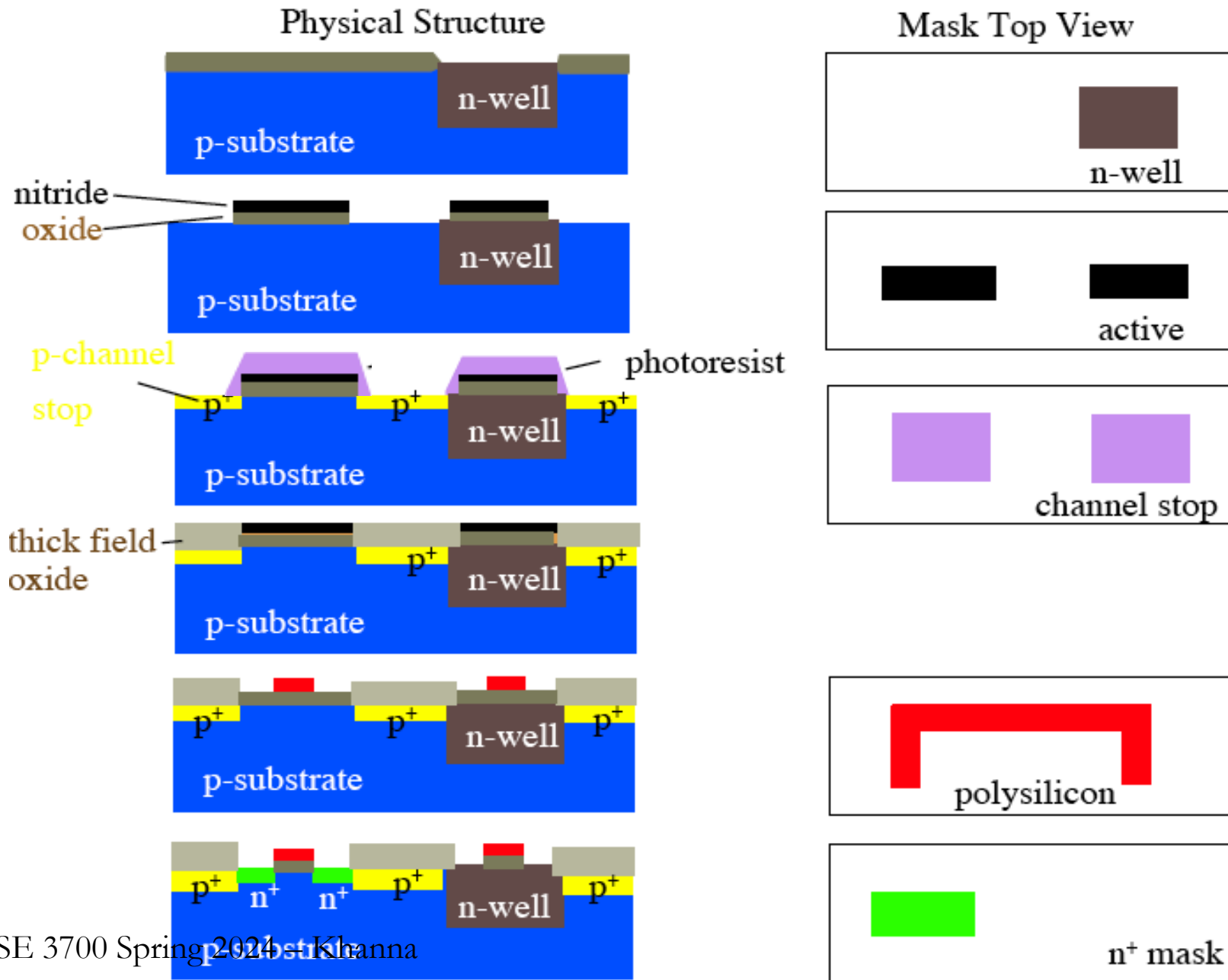





# Typical N-Well CMOS Process

Physical Structure

Mask Top View

     

# Design Rules

 

- Why not adjacent transistors?
  - Plenty of empty space
  - If area is money, pack in as much as possible
    - Shortens connections
- Recall: processing is imprecise
  - Margin of error for process variation






# Design Rules

---

- ❑ Contract between process engineer & designer
  - Minimum width/spacing
  - Can be (often are) process specific
  
- ❑ Lambda rules: scalable design rules
  - In terms of  $\lambda = 0.5 L_{\min}$  ( $L_{\text{drawn}}$ )
  - Can migrate designs from similar process with lambda factor


# Design Rules: Some Examples

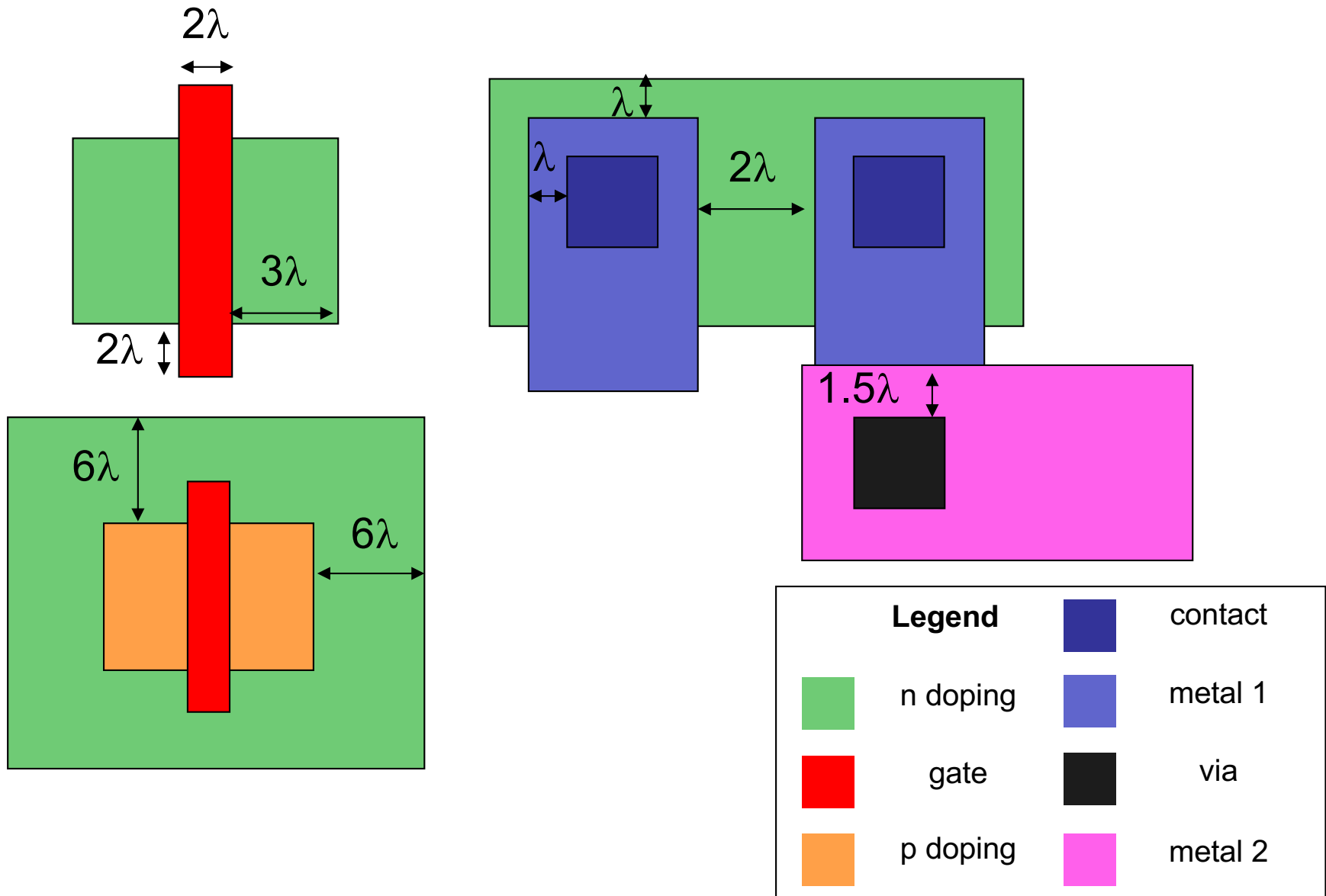

# Potential Consequences of Design Rule Violations


## ❑ Inter-Layer Design Rule Origins

Intended Transistor

 

Catastrophic Error – Unintended misalignment cause Source-Drain short circuit

Intended Unrelated Poly & Diffusion

 

Catastrophic Error – Unintended overlap cause fabrication of a parasitic Transistor

# Potential Consequences of Design Rule Violations

## □ Inter-Layer Design Rule Origins


### Contact and Via Masks

M1 contact to n-diffusion  
M1 contact to p-diffusion  
M1 contact to poly

-> Contact Mask


Mn contact to Mn-1 for n = 2, 3,..

-> Via Mask

 




# Layout #2 (preclass 3)

 

 
# Layout #2 (preclass 3)

- How many transistors?
  - PMOS?
  - NMOS?
- How connected?
  - PMOS, NMOS?
- Inputs connected how?
- Outputs?
- What is it?


 
# Symbolic Layout (Preclass 4)


- Stick diagrams capture spatial relationships, but abstract away design rules



- What is the gate function?
  - How many NMOS? PMOS? D/S connections?
  - Draw schematic

 
# Standard Cells

- Lay out gates so that heights match
  - Rows of adjacent cells
  - Standardized sizing of gate heights
- Motivation: automated place and route
  - EDA tools convert HDL to layout






# Standard Cells

 


Fanout 4x	0.5 $\mu\text{m}$	1.0 $\mu\text{m}$	2.0 $\mu\text{m}$
<i>A1_tphl</i>	0.595	0.711	0.919
<i>A1_tplh</i>	0.692	0.933	1.360
<i>B1_tphl</i>	0.591	0.739	1.006
<i>B1_tplh</i>	0.620	0.825	1.1.81
<i>C1_tphl</i>	0.574	0.740	1.029
<i>C1_tplh</i>	0.554	0.728	1.026

**3-input NAND cell**  
 (from Mississippi State Library)  
 characterized for fanout of 4 and  
 for three different technologies

# Standard Cell Layout Example

 


# Standard Cell Area

 




# Standard Cell Layout Example

 

<http://www.laytools.com/images/StandardCells.jpg>




# Standard Cell Layout Example

 

<http://www.laytools.com/images/StandardCells.jpg>




# 4x4 6T SRAM Memory

 

 
# Circuit Extraction

- ❑ Circuit extraction extracts a schematic representation of a layout, including transistors, wires, and possibly wire and device resistance and capacitance.




- ❑ Circuit extraction is used for LVS, and for spice simulation of layouts

# Circuit Extraction

 



# Circuit Extraction

 


# Scaling

---



 
# Scaling Technology

- ❑ **Premise:** features scale “uniformly”
  - everything gets better in a predictable manner
  
- ❑ **Parameters:**
  - $\lambda$  (lambda) -- Mead and Conway ( $L=2\lambda$ )
  - F -- Half pitch – ITRS ( $F=2\lambda=L$ )
  - S – scale factor – Rabaey
    - $F'=F/S$
    - $S>1$






# Microprocessor Trans Count 1971-2015

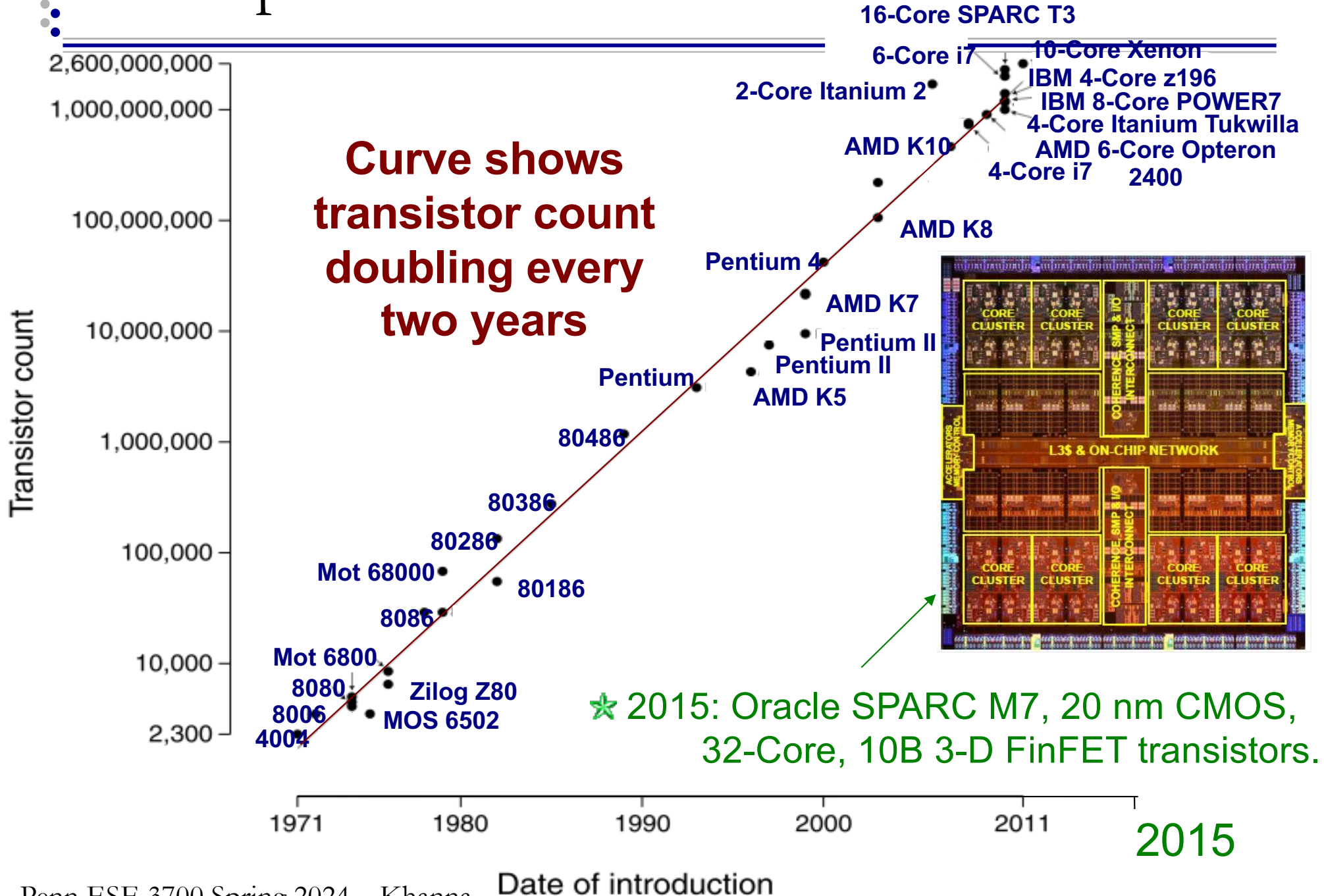**Curve shows transistor count doubling every two years**





# Intel Cost Scaling

   

<http://www.anandtech.com/show/8367/intels-14nm-technology-in-detail>





# More Moore → Scaling


---

- ❑ Geometrical Scaling
  - continued shrinking of horizontal and vertical physical feature sizes
- ❑ Design Equivalent Scaling
  - design technologies that enable high performance, low power, high reliability, low cost, and high design productivity even if neither geometrical nor equivalent scaling can be used

# 22nm 3D FinFET Transistor

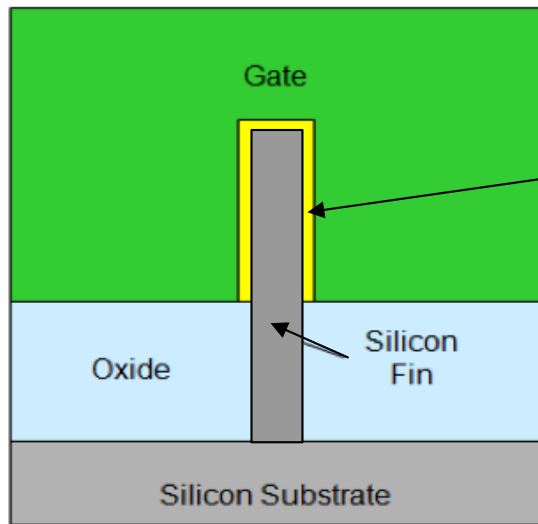 

High-k  
gate  
dielectric

 

Tri-Gate transistors with multiple fins connected together increases total drive strength for higher performance

[http://download.intel.com/newsroom/kits/22nm/pdfs/22nm-Details\\_Presentation.pdf](http://download.intel.com/newsroom/kits/22nm/pdfs/22nm-Details_Presentation.pdf)




# ITRS Roadmap

---

- ❑ International Technology Roadmap for Semiconductors
  - Try to predict where industry going
- ❑ ITRS 2.0 started in 2015 with new focus
  - System Integration, Heterogeneous Integration, Heterogeneous Components, Outside System Connectivity, More Moore, Beyond CMOS and Factory Integration.
  
- ❑ <http://www.itrs2.net/>



# More-than-Moore

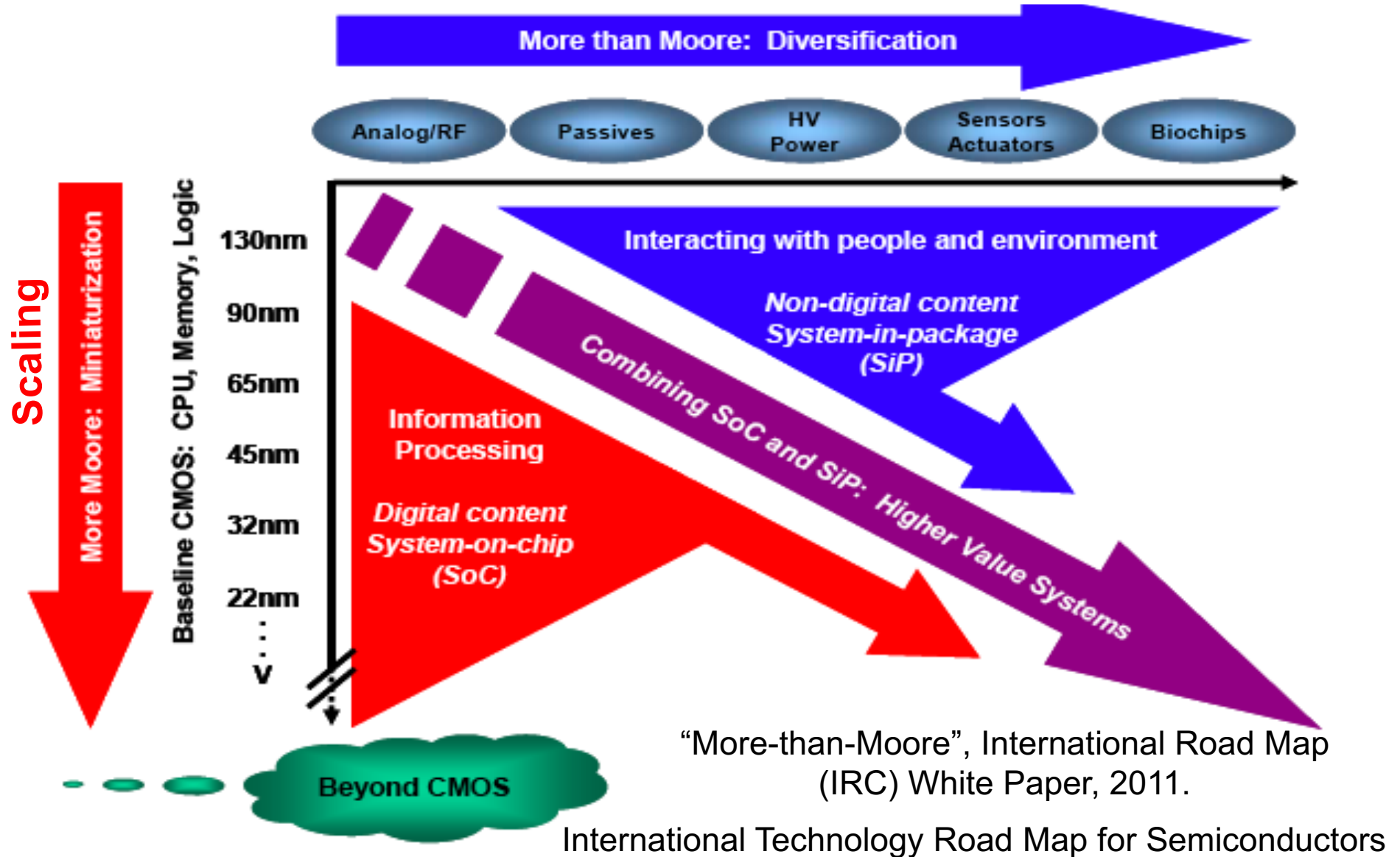



## Question (Preclass 5)

---

- Scaling from 32nm  $\rightarrow$  22nm, what is  $1/S$ ?
  - Scaling minimum gate length
  - And pitch distance

# MOS Transistor *Scaling* - (1974 to present)

---


$1/S=0.7$   
per technology node  
[0.5x per 2 nodes]



**Source: 2001 ITRS - Exec. Summary, ORTC  
Figure, Andrew Kahng**

 
# Scaling

- ❑ Channel Length ( $L$ )
- ❑ Channel Width ( $W$ )
- ❑ Oxide Thickness ( $t_{ox}$ )
- ❑ Doping ( $N_a$ )
- ❑ Voltage ( $V_{DD}, V_t$ )


 
# Full Scaling (Ideal Scaling)

- ❑ Channel Length ( $L$ )  $1/S$
- ❑ Channel Width ( $W$ )  $1/S$
- ❑ Oxide Thickness ( $t_{ox}$ )  $1/S$
- ❑ Doping ( $N_a$ )  $S$
- ❑ Voltage ( $V_{DD}, V_{t}$ )  $1/S$





# Effects on Physical Properties and Specs?


---

- Area
- Capacitance
  - $C_{\text{ox}}$  and  $C_{\text{gate}}$
- Resistance
- Current ( $I_d$ )
- Gate Delay ( $\tau_{\text{gd}}$ )
- Wire Delay ( $\tau_{\text{wire}}$ )
- Power
  - Same frequency
  - Scaled frequency
- Power Density
  - Same frequency
  - Scaled frequency

## Preclass 6
 
# Area

- $\lambda' \rightarrow \lambda/S$
- Area impact?
- $A = L \times W$
- 



# Area

- $\lambda' \rightarrow \lambda/S$

- *Area impact?*

- $A = L \times W$


- $A' \rightarrow A/S^2$

- $32\text{nm} \rightarrow 22\text{nm}$

- 50% area

- $2 \times$  transistor capacity  
for same area

$$1/S=0.7$$

 




# Capacitance
 
## □ Capacitance per unit area scaling?


- $C_{\text{ox}} = \epsilon_{\text{SiO}_2} / t_{\text{ox}}$
- $t'_{\text{ox}} \rightarrow t_{\text{ox}} / S$



# Capacitance
 
## □ Capacitance per unit area scaling?


- $C_{\text{ox}} = \epsilon_{\text{SiO}_2} / t_{\text{ox}}$
- $t'_{\text{ox}} \rightarrow t_{\text{ox}} / S$
- $C'_{\text{ox}} \rightarrow C_{\text{ox}} \times S$



# Capacitance
 
## □ Gate Capacitance scaling?


- $C_{\text{gate}} = A \times C_{\text{ox}}$
- $A' \rightarrow A/S^2$
- $C'_{\text{ox}} \rightarrow C_{\text{ox}} \times S$



# Capacitance

 
## □ Gate Capacitance scaling?

- $C_{\text{gate}} = A \times C_{\text{ox}}$
- $A' \rightarrow A/S^2$
- $C'_{\text{ox}} \rightarrow C_{\text{ox}} \times S$
- $C'_{\text{gate}} \rightarrow C_{\text{gate}}/S$



 
# Wire Resistance

- Resistance scaling?
- $R = \rho L / (W * t)$ 
  - L, t remain similar (not scaled)
- $W \rightarrow W / S$


 
# Wire Resistance

- Resistance scaling?
- $R = \rho L / (W * t)$ 
  - L, t remain similar (not scaled)
- $W \rightarrow W / S$
- $R' \rightarrow R \times S$



# Current

- ❑ Which Voltages matter here? ( $V_{gs}, V_{ds}, V_{th} \dots$ )
- ❑ Transistor charging looks like voltage-controlled current source
- ❑ Saturation Current scaling?


$$I_d = (\mu C_{OX}/2)(W/L)(V_{gs} - V_{TH})^2$$

$$V_{gs}, V_{TH}: V' \rightarrow V/S$$

$$W' \rightarrow W/S$$

$$L' \rightarrow L/S$$

$$C'_{ox} \rightarrow C_{ox} \times S$$

 



# Current

- ❑ Which Voltages matters here? ( $V_{gs}, V_{ds}, V_{th} \dots$ )
- ❑ Transistor charging looks like voltage-controlled current source
- ❑ Saturation Current scaling?


$$I_d = (\mu C_{OX} / 2) (W / L) (V_{gs} - V_{TH})^2$$

$$V_{gs}, V_{TH}: V' \rightarrow V / S$$

$$W' \rightarrow W / S$$

$$L' \rightarrow L / S$$

$$C'_{ox} \rightarrow C_{ox} \times S$$

 

$$I'_d = (\mu C_{OX} S / 2) ((W / S) / (L / S)) (V_{gs} / S - V_{TH} / S)^2$$

# Current

- ❑ Which Voltages matters here? ( $V_{gs}, V_{ds}, V_{th} \dots$ )
- ❑ Transistor charging looks like voltage-controlled current source
- ❑ Saturation Current scaling?

$$I_d = (\mu C_{OX} / 2) (W / L) (V_{gs} - V_{TH})^2$$


$$V_{gs}, V_{TH}: V' \rightarrow V / S$$

$$W' \rightarrow W / S$$

$$L' \rightarrow L / S$$

$$C'_{ox} \rightarrow C_{ox} \times S$$

$$I'_d \rightarrow I_d / S$$

 

# Current

## □ Velocity Saturation Current scaling?


$$V_{gs}, V_{TH}: V' \rightarrow V/S$$

$$L' \rightarrow L/S$$

$$W' \rightarrow W/S$$

$$C'_{ox} \rightarrow C_{ox} S$$
 
$$I_{DS} \approx v_{sat} C_{OX} W \left( V_{GS} - V_{TH} - \frac{V_{DSAT}}{2} \right)$$



# Current

## □ Velocity Saturation Current scaling?

$$V_{gs}, V_{TH}: V' \rightarrow V/S$$


$$L' \rightarrow L/S$$

$$W' \rightarrow W/S$$

$$C'_{ox} \rightarrow C_{ox} S$$


$$I'_d \rightarrow I_d/S$$
 
$$I_{DS} \approx v_{sat} C_{OX} W \left( V_{GS} - V_{TH} - \frac{V_{DSAT}}{2} \right)$$


 
# Gate Delay

- Gate Delay scaling?
- $\tau_{gd} = Q/I = (CV)/I$
- $V' \rightarrow V/S$
- $I'_d \rightarrow I_d/S$
- $C'_g \rightarrow C_g/S$



# Gate Delay

- Gate Delay scaling?


- $\tau_{gd} = Q/I = (CV)/I$

- $V' \rightarrow V/S$

- $I'_d \rightarrow I_d/S$

- $C'_g \rightarrow C_g/S$

- $\tau'_{gd} \rightarrow \tau_{gd}/S$

 



# Wire Delay

---

- Wire delay scaling?
- $\tau_{\text{wire}} = R \times C$
- $R' \rightarrow R \times S$
- $C' \rightarrow C / S$
- Again assuming (logical) wire lengths remain constant





# Wire Delay

---

- Wire delay scaling?
- $\tau_{\text{wire}} = R \times C$
- $R' \rightarrow R \times S$
- $C' \rightarrow C / S$
- $\tau'_{\text{wire}} \rightarrow \tau_{\text{wire}}$
- Again assuming (logical) wire lengths remain constant



# Power Dissipation (Dynamic)

---

- Capacitive (Dis)charging scaling?
  - $P = (1/2)CV^2f$
  
  - $V' \rightarrow V/S$
  - $C' \rightarrow C/S$



# Power Dissipation (Dynamic)

---

□ Capacitive (Dis)charging scaling?

□  $P = (1/2)CV^2f$

□  $V' \rightarrow V/S$

□  $C' \rightarrow C/S$

□  $P' \rightarrow P/S^3$

# Power Dissipation (Dynamic)

## □ Capacitive (Dis)charging scaling?

$$\square P = (1/2)CV^2f$$

$$\square V' \rightarrow V/S$$

$$\square C' \rightarrow C/S$$

$$\square P' \rightarrow P/S^3$$

## □ Increase Frequency?

$$\square \tau_{gd} \rightarrow \tau_{gd}/S$$

$$\square \text{So: } f \rightarrow f \times S$$

# Power Dissipation (Dynamic)

## □ Capacitive (Dis)charging scaling?

$$\square P = (1/2)CV^2f$$

$$\square V' \rightarrow V/S$$

$$\square C' \rightarrow C/S$$

$$\square P' \rightarrow P/S^3$$

## □ Increase Frequency?

$$\square \tau_{gd} \rightarrow \tau_{gd}/S$$

$$\square \text{So: } f \rightarrow f \times S$$

$$\square P \rightarrow P/S^2$$



# Effects?

---

- Area  $1/S^2$
- Capacitance ( $C_{ox}, C_g$ )  $S, 1/S$
- Resistance  $S$
- Threshold ( $V_{th}$ )  $1/S$
- Current ( $I_d$ )  $1/S$
- Gate Delay ( $\tau_{gd}$ )  $1/S$
- Wire Delay ( $\tau_{wire}$ )  $1$
- Power  $1/S^3, 1/S^2$

**$1/S=0.7$**



# Power Density

---

- ❑  $P' \rightarrow P/S^2$  (increased frequency)
- ❑  $P' \rightarrow P/S^3$  (same frequency)
- ❑  $A' \rightarrow A/S^2$
  
- ❑ Power Density:  $P/A$  two cases?






# Power Density

---

- $P' \rightarrow P/S^2$  (increased frequency)
- $P' \rightarrow P/S^3$  (same frequency)
- $A' \rightarrow A/S^2$
  
- Power Density:  $P/A$  two cases?
  - $P/A \rightarrow P/A$  increase freq.
  - $P/A \rightarrow (P/A)/S$  same freq.
 
# Big Idea

- ❑ Layouts are physical realization of circuit
  - Geometry tradeoff
    - Can decrease spacing at the cost of yield
    - Design rules
- ❑ Can go from circuit to stick diagram/layout or stick diagram/layout to circuit by inspection
- ❑ Moderately predictable VLSI Scaling
  - unprecedented capacities/capability growth for engineered systems
  - ...but hits physical limit






# Admin

---

- ❑ HW3 out now – due 2/16 (Friday)
  - Don't forget the demo/video of SPICE workflow
    - Get TA checkoff or submit video in Canvas
- ❑ Midterm 1 Wednesday 2/21 (next week)
  - 1.5 hrs during class in Moore 216
  - Midterm 1 TA review session, Saturday 2-4pm
    - location TBD. Keep an eye on Ed
  - Covers lecture 1-6
  - Old exams posted on previous years websites
    - Note old exams were for 2hrs
- ❑ HW 4 posted on 2/21



# Midterm 1 - Coverage

---

## □ Lec 1 - 6

- Identify CMOS/non-CMOS
- Identify CMOS function
- Any logic function → CMOS gate
- Noise Margins / Restoration
- Circuit first order switching rise/fall times
  - Output equivalent resistance
  - Load capacitance
- MOS Model
  - Identify transistor region of operation
  - Analysis with transistor IV models
  - MOS capacitance models



# Acknowledgement

---

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Jing Li (University of Pennsylvania)