

# ESE3700: Circuit-Level Modeling, Design and Optimization for Digital Systems

---

Lec 9: February 26, 2024

Performance Inverters and Gates





# Previously

---

- Delay as RC-charging
- Transistor
  - Capacitance
  - Drive Current
  - Function of geometry ( $W/L$ )



# Today

---

- $\tau$ -model
- Sizing
- Large Fanout
- Capacitance Revisited
  - Miller Effect
- Delay in Gates
- Data Dependent Delay
- Large Fanin



# Transistor Sizing

---

- What happens to  $I_{ds}$  as a function of  $W$ ?

$$I_{DS} \approx v_{sat} C_{OX} W \left( V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$

- What happens to  $C_g$  as a function of  $W$ ?

$$C_G \propto C_{ox} WL$$

# Transistor Sizing

---

- What happens to  $I_{ds}$  as a function of  $W$ ?

$$I_{DS} \approx v_{sat} C_{OX} W \left( V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$

- What happens to  $C_g$  as a function of  $W$ ?

$$C_G \propto C_{ox} WL$$

- **Conclude:** faster transistors present more load on their inputs



# First Order Delay (preclass 1)

---

- ❑  $I_0 = I_{ds}$  of minimum size NMOS device
- ❑  $C_0 =$  gate capacitance of minimum size NMOS device
  
- ❑  $I_{drive} = WI_0$
- ❑  $C_g = WC_0$



# First Order Delay (preclass 1)

---

- ❑  $R_0$  = Resistance of minimum size NMOS device
- ❑  $C_0$  = gate capacitance of minimum size NMOS device
  
- ❑  $R_{\text{drive}} = R_0/W$
- ❑  $C_g = WC_0$



# $\tau$ model

---

- ❑ All delays are RC delays
- ❑ Always have an  $R_0C_0$  term
- ❑  $\tau = R_0C_0$
- ❑ Express all delays in  $\tau$  units
- ❑ Like  $\lambda$  units for measurement
  - Separate delay into
    - Technology dependent term  $\tau = R_0C_0$
    - Technology independent coefficient



# How to Size Transistors (preclass 2)


## □ How should we size to equalize Rise and Fall?

### ■ Given:

### ■ $\mu_n = 500 \text{cm}^2/\text{Vs}$ , $\mu_p = 200 \text{cm}^2/\text{Vs}$
 
### ■ $R_{\text{drive}} = R_0/2$ ( $I_{\text{drive}} = 2I_0$ )

$$I_{DS} = \mu C_{OX} \frac{W}{L} (V_{GS} - V_T)^2$$



# How to Size Transistors (preclass 2)


## □ How should we size to equalize Rise and Fall?

### ■ Given:

### ■ $\mu_n = 500 \text{cm}^2/\text{Vs}$ , $\mu_p = 200 \text{cm}^2/\text{Vs}$

 
### ■ $R_{\text{drive}} = R_0/2$ ( $I_{\text{drive}} = 2I_0$ )

$$I_{DS} = \mu C_{OX} \frac{W}{L} (V_{GS} - V_T)^2$$



### ■ What is input capacitance for sized devices?


# Size Transistors – Minimum Avg Delay

 

- $\beta$  of 2.4 (= 31 k $\Omega$ /13 k $\Omega$ ) gives symmetrical response
- $\beta$  of 1.6 to 1.9 gives optimal performance



# SPICE Simulation 22nm

 



# Equalizing Delay


---

- For simplicity, for now
  - Assume  $W_p = W_n$  equalizes  $I_{ds}$ 
    - I.e.  $I_{0,n} = I_{0,p}$  and  $R_{0n} = R_{0p}$


 
# Multistage Delay

- ❑ Total delay = sum of stage delays
- ❑ What is delay here?
  - From (P1,N1) to final capacitive load





 
# Inverter Sizing

---

- Delay from V1 to V4 of all min size transistors?





 
# Inverter Sizing

---

- What is the impact of the delay if we double size of all the transistors?








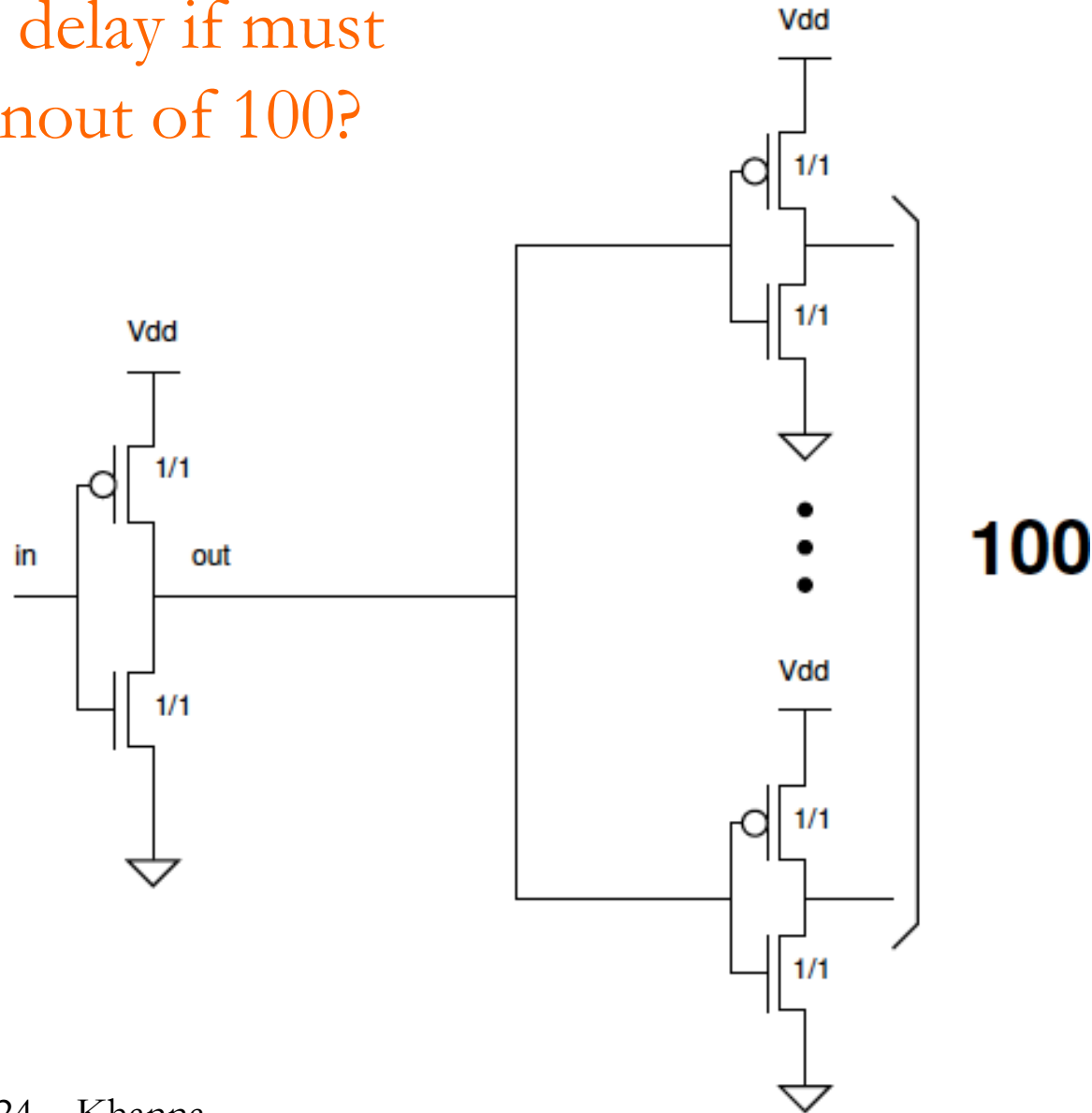
# Large Fanout Delay (preclass 3)

- What is delay if must drive fanout of 100?




# Graduated Fanout Delay (preclass 3)

□ What is delay here?

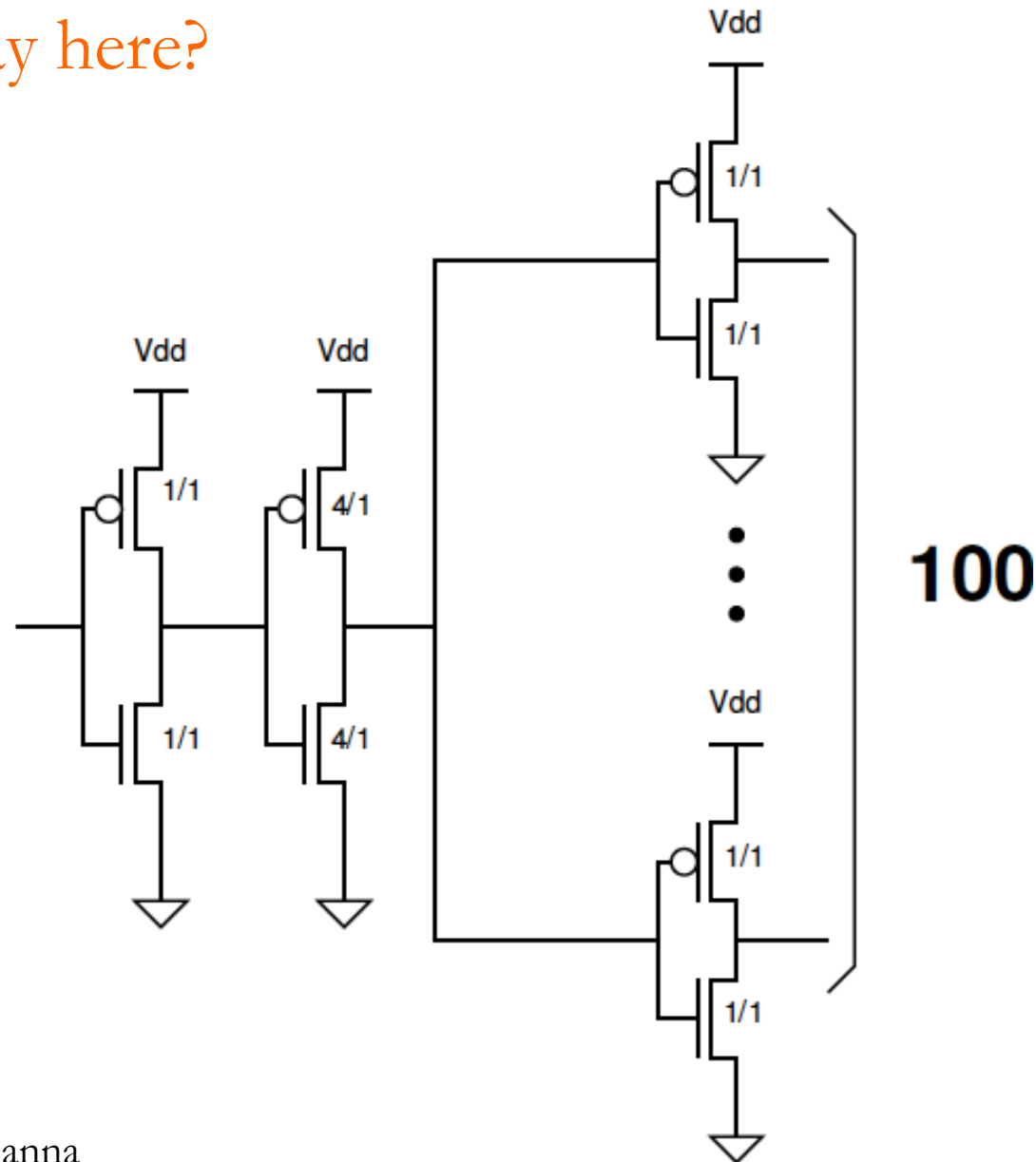
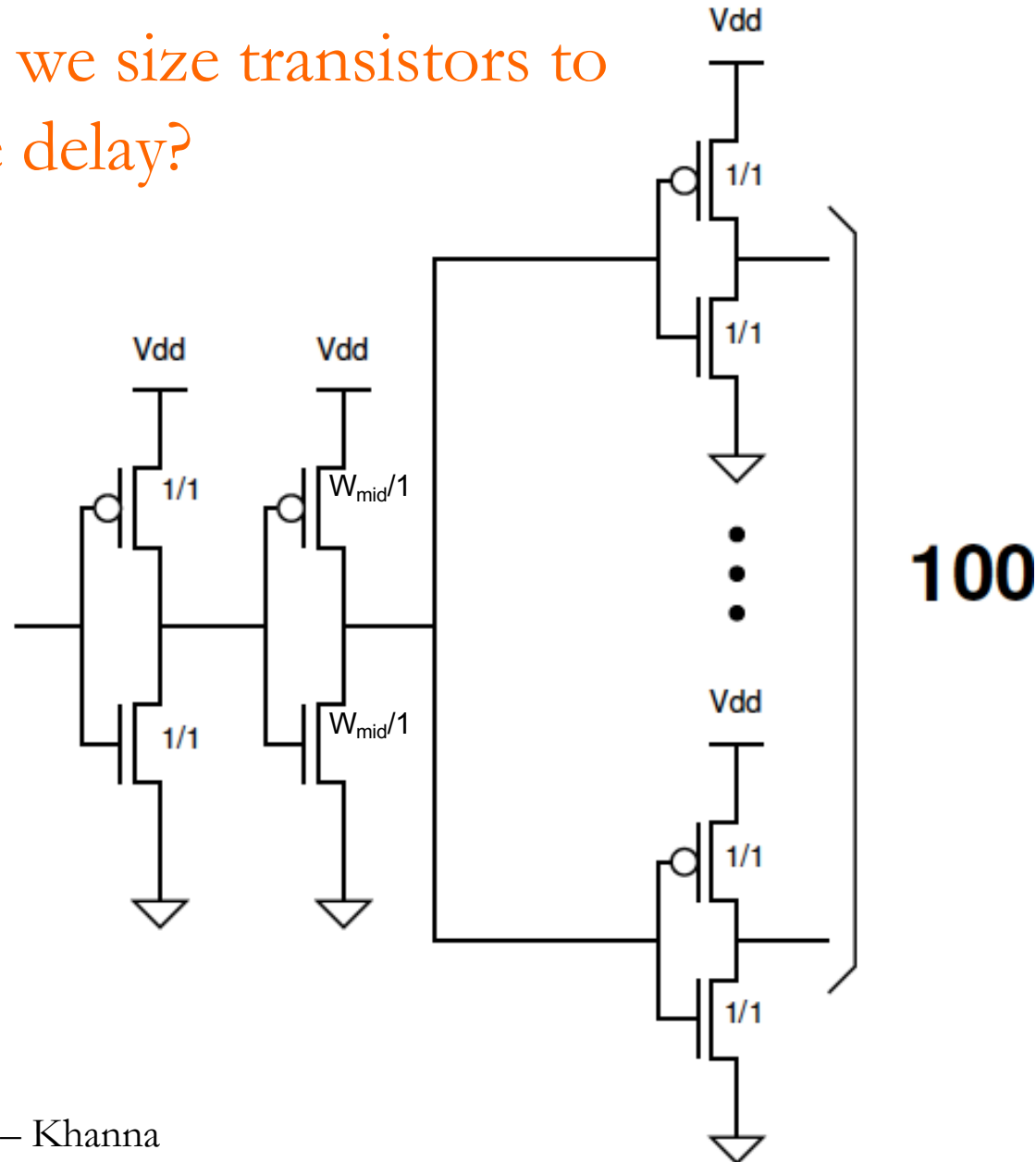
# Optimize Fanout Delay (preclass 4)

- How can we size transistors to minimize delay?





# Optimizing (preclass 4)

---

□ Derivate to minimize

$$\tau_{est} = R_0 \times 2W_{mid}C_0 + \frac{R_0}{W_{mid}} \times 200C_0$$

$$\frac{\partial \tau_{est}}{\partial W_{mid}} = 0$$


$$2R_0C_0 - \frac{200}{W_{mid}^2} R_0C_0 = 0$$

$$W_{mid} = \sqrt{100} = 10$$




# Delay? (preclass 4)

- Delay at optimal  $W_{mid}$ ?

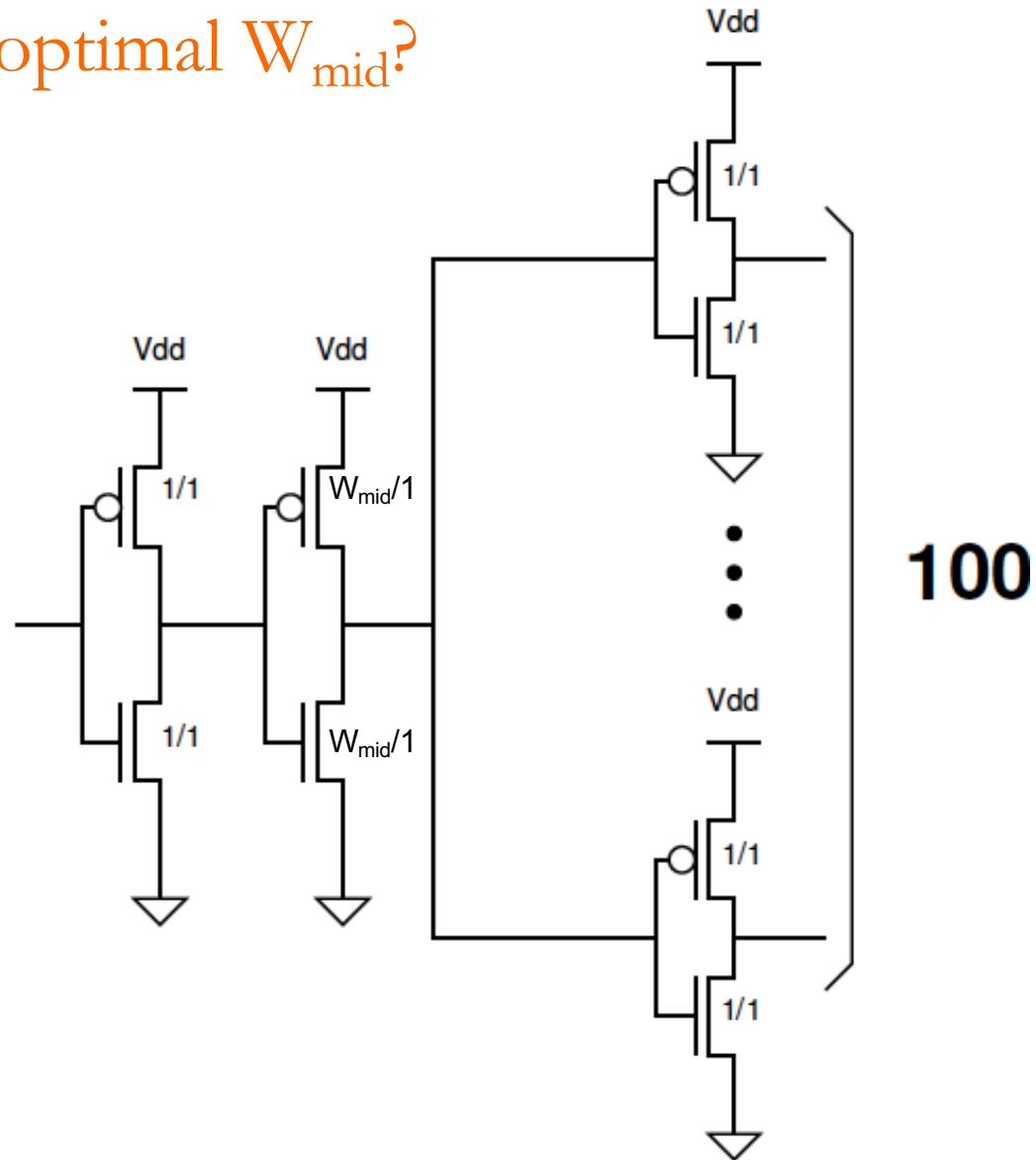

# Try Again with More Stages (preclass 6)


- What is the delay here?

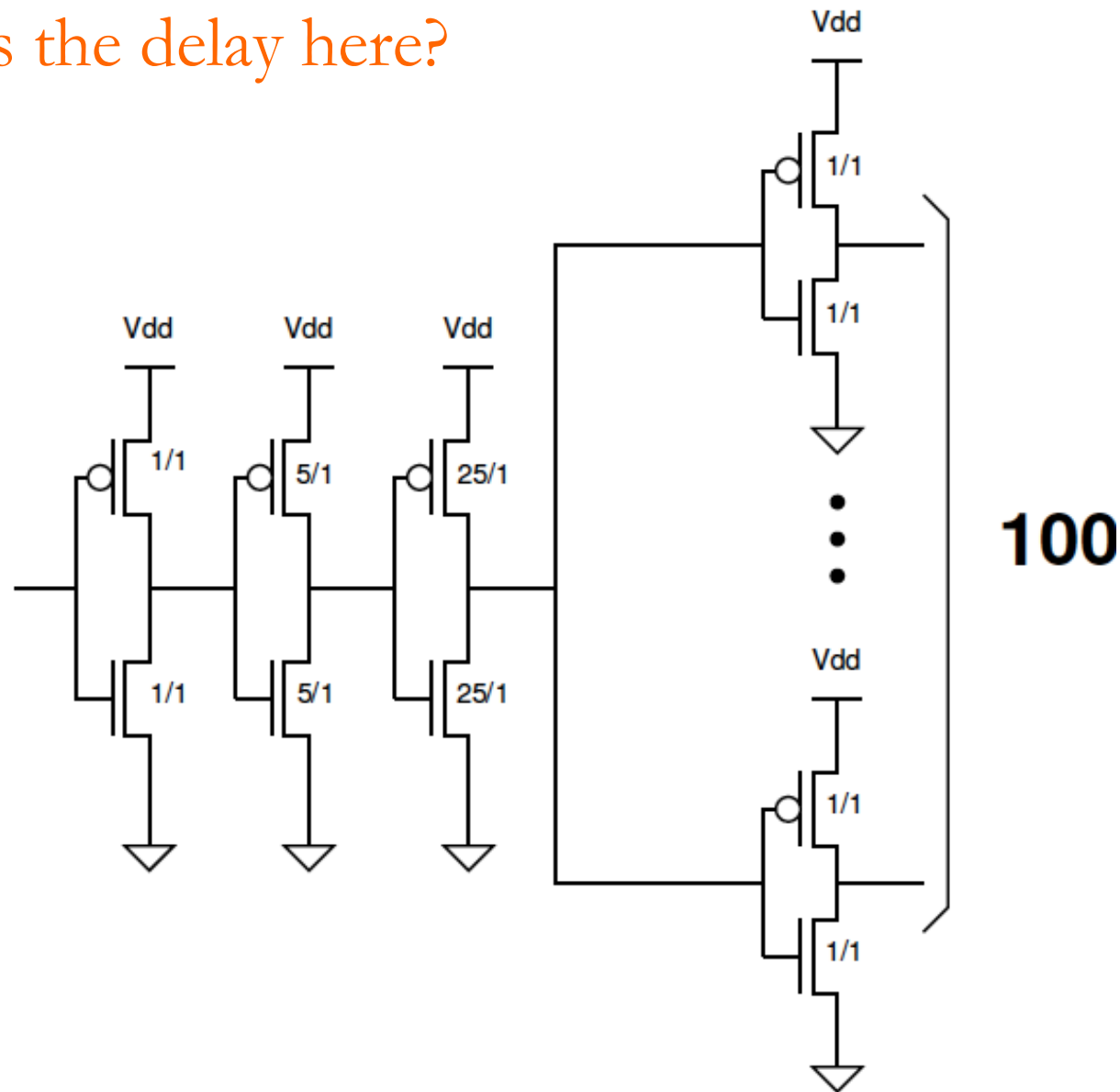







# ...and Again (preclass 5)

□ Delay here?

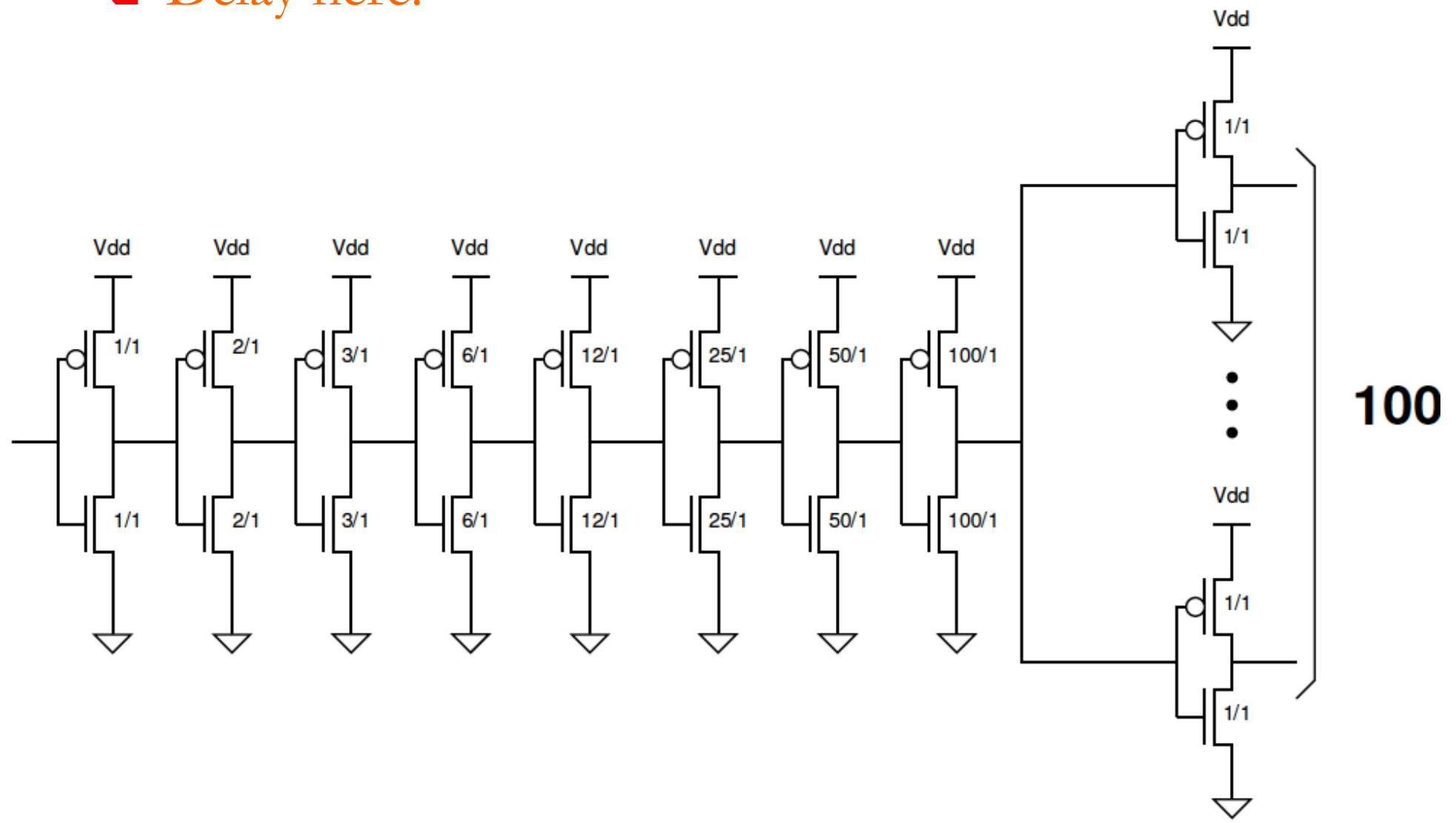



# Delay Summary

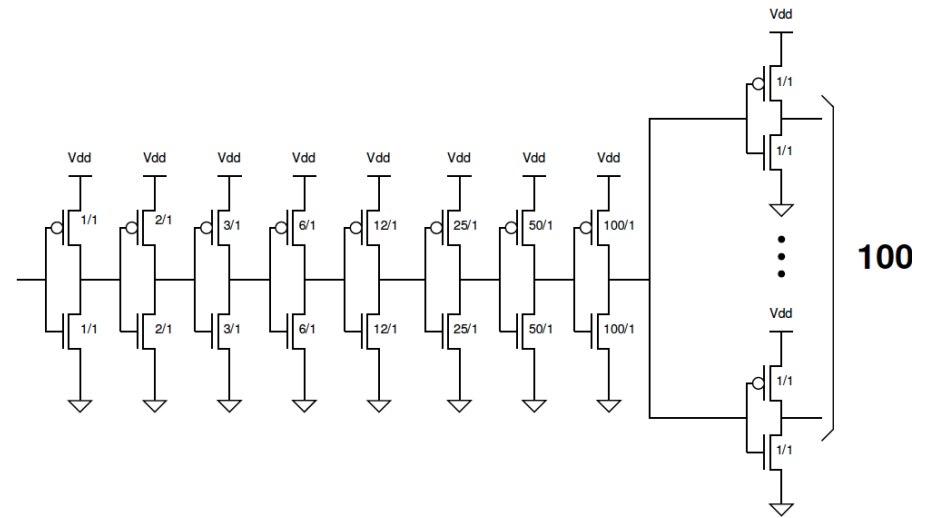   





# Lesson

---

- ❑ Don't drive large fanout with a single stage
- ❑ Must scale up over a number of stages
- ❑ ...but not too many
- ❑ Exact number will be technology dependent


---

Gates



# Inverter Performance (preclass 5, row 1)


- Sized for  $R_0/2$  drive resistance, ( $R_0=R_{n0}$ )

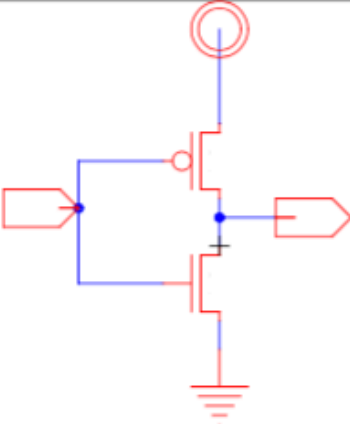	$R_{p0} = R_{n0}$			$R_{p0} = 2R_{n0}$		
	$W_p$	$W_n$	$C_a$	$W_p$	$W_n$	$C_a$
	2	2	$4C_0$	4	2	$6C_0$



 
# Data Dependent Delay

- Drive resistance depends on input values
  - Delay depends on input data
  - Analyze using worst case delay



 
# Transistor Sizing (preclass 6, row 2)

- How should we size to equalize worst-case rise/fall times for  $R_{\text{drive}} = R_0/2$ ?


 
# Transistor Sizing (preclass 6, row 3)


- How size for equal rise/fall for  $R_{\text{drive}} = R_0/2$ ?




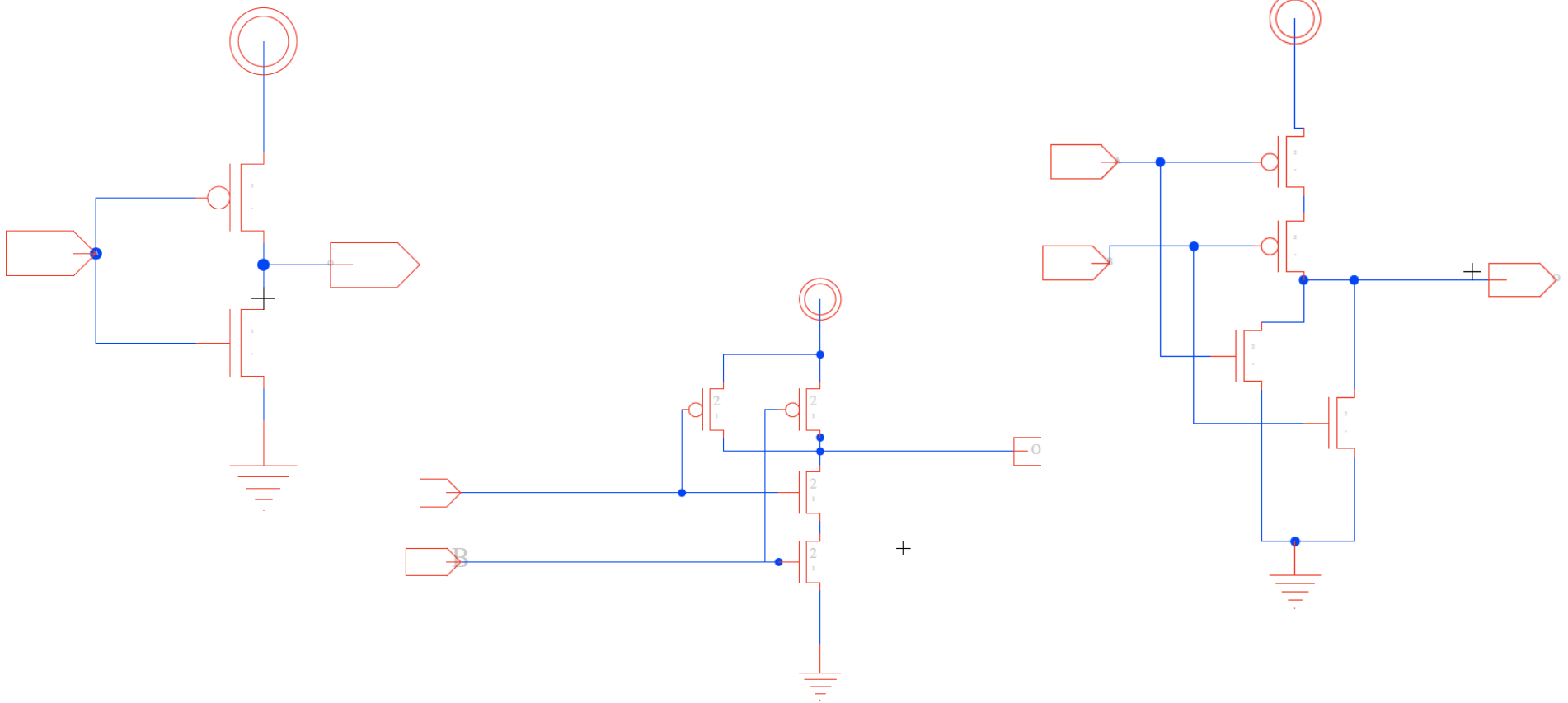
# Input Load

- Input capacitance per input in each case?





# Observe


---

- Ratio of Input Load Capacitance to Output Drive Strength:  $C_{\text{InLoad}}/I_{\text{ds}}$ 
  - Differs with gate function
  - Gate efficiency



 
# Transistor Sizing (preclass 6, row 4)

- Size equalize rise/fall times  $R_{drive} = R_0/2?$





# Series Transistors

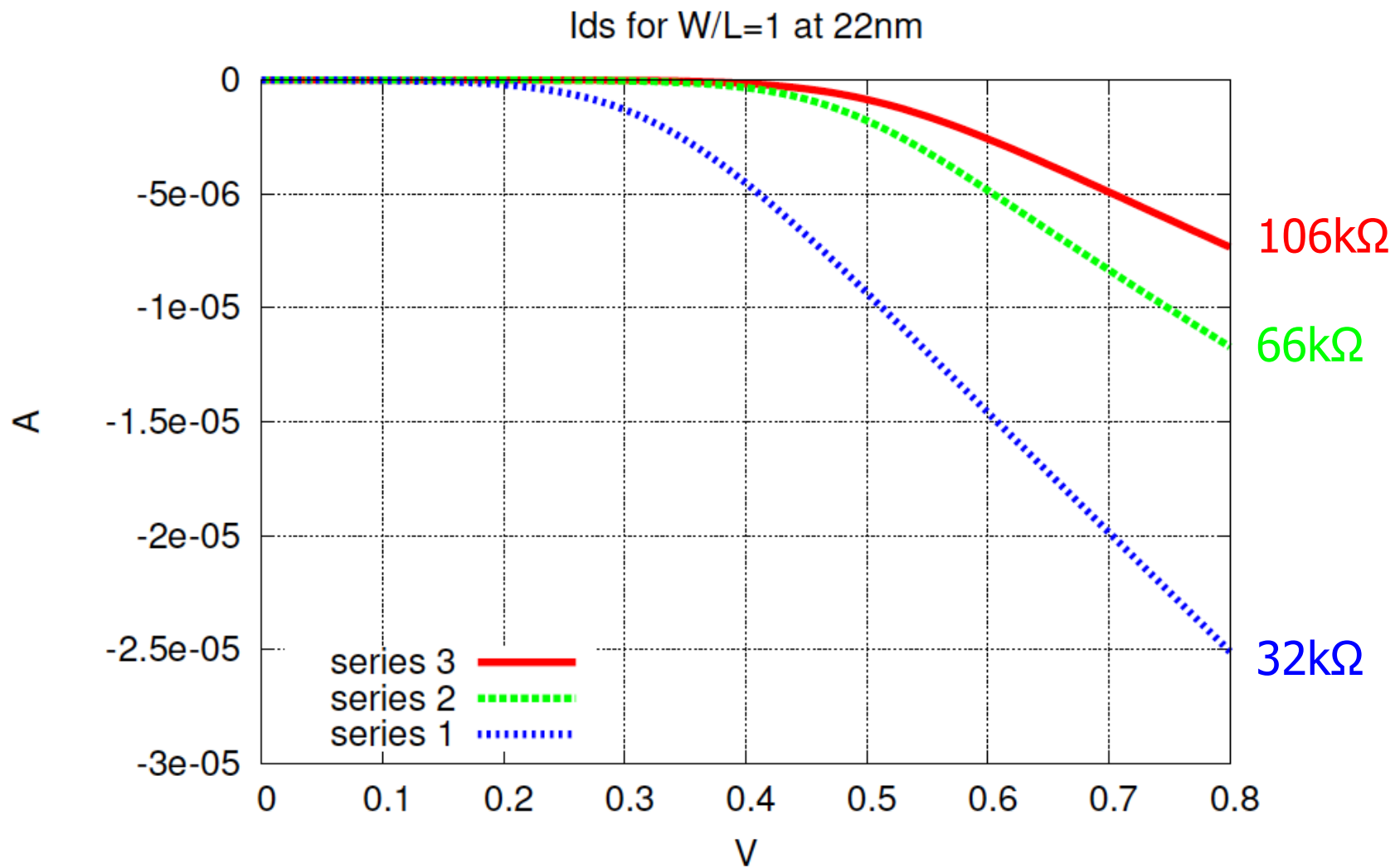



# Increasing Fanin (preclass 7)

---

- What happens to input capacitance as fanin ( $k$ ) increases
  - Keeping output drive the same
    - E.g.  $R_{\text{drive}} = R_0/2$
- $k$ -input nand gate has what input capacitance?



# Fanin

---


- ❑ **Conclude:** gates slow down with fanin
  - Less drive per input capacitance
  - $C_{\text{InLoad}}/I_{\text{ds}}$  increases

# nand32 (preclass 8, row 1)
 
## □ single-stage nand32

$R_{n0} = R_{p0}$  case only

- Delay with  $R_0/2$  input drive and  $4C_0$  load?




# nand32 (preclass 8, row 1)
 
## □ single-stage nand32

$R_{n0} = R_{p0}$  case only


- Delay with  $R_0/2$  input drive and  $4C_0$  load?




# Which is Faster? (preclass 8, rows 2&3)

□ nand32

$R_{n0} = R_{p0}$  case only

 

nand4-inv-nand4-inv-nand2

 

$(\text{nand2-inv})^4\text{-nand2}$



# Lesson

---


- ❑ Large gates are slow / inefficient
  - High capacitive load / drive current
- ❑ Small gates can be inefficient
  - Need many stages
- ❑ Staging over moderate size gates minimizes delay
- ❑ Exact size will be technology dependent






# And-Or Chain


---

 
 
# Delay of each implementation? (preclass 9)



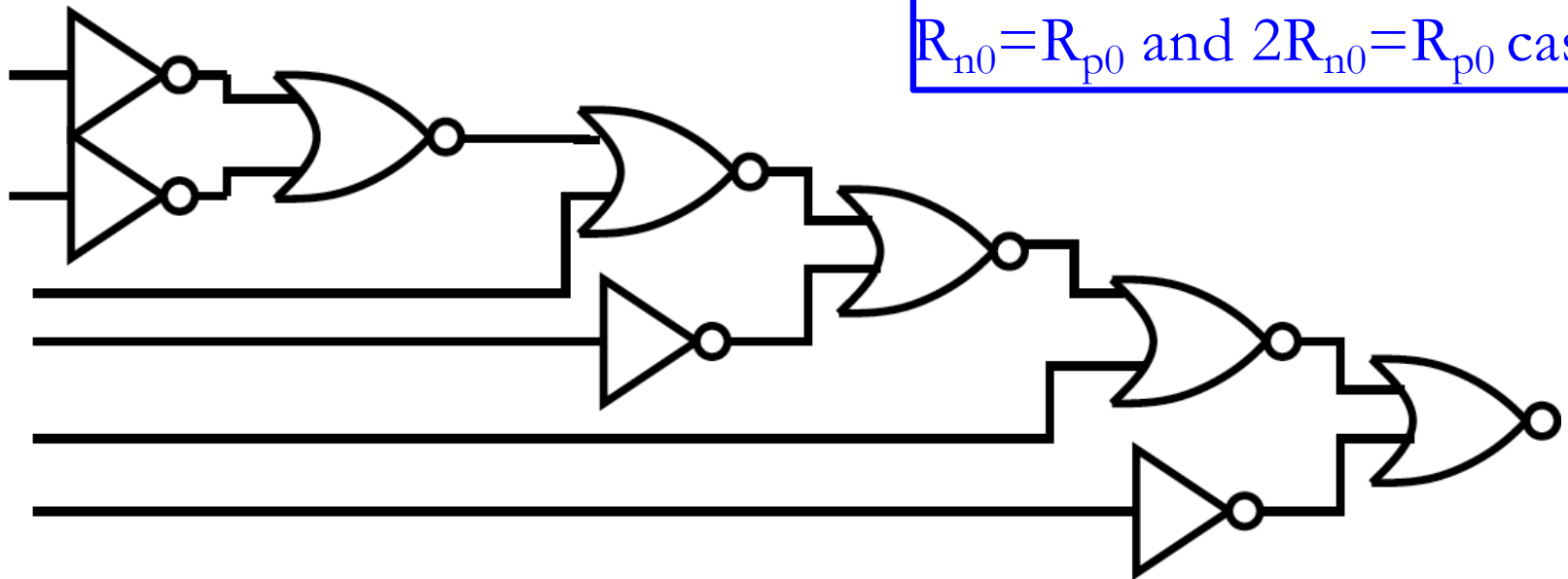
$R_{n0} = R_{p0}$  and  $2R_{n0} = R_{p0}$  cases





# Take Away?

- ❑ nor vs. nand

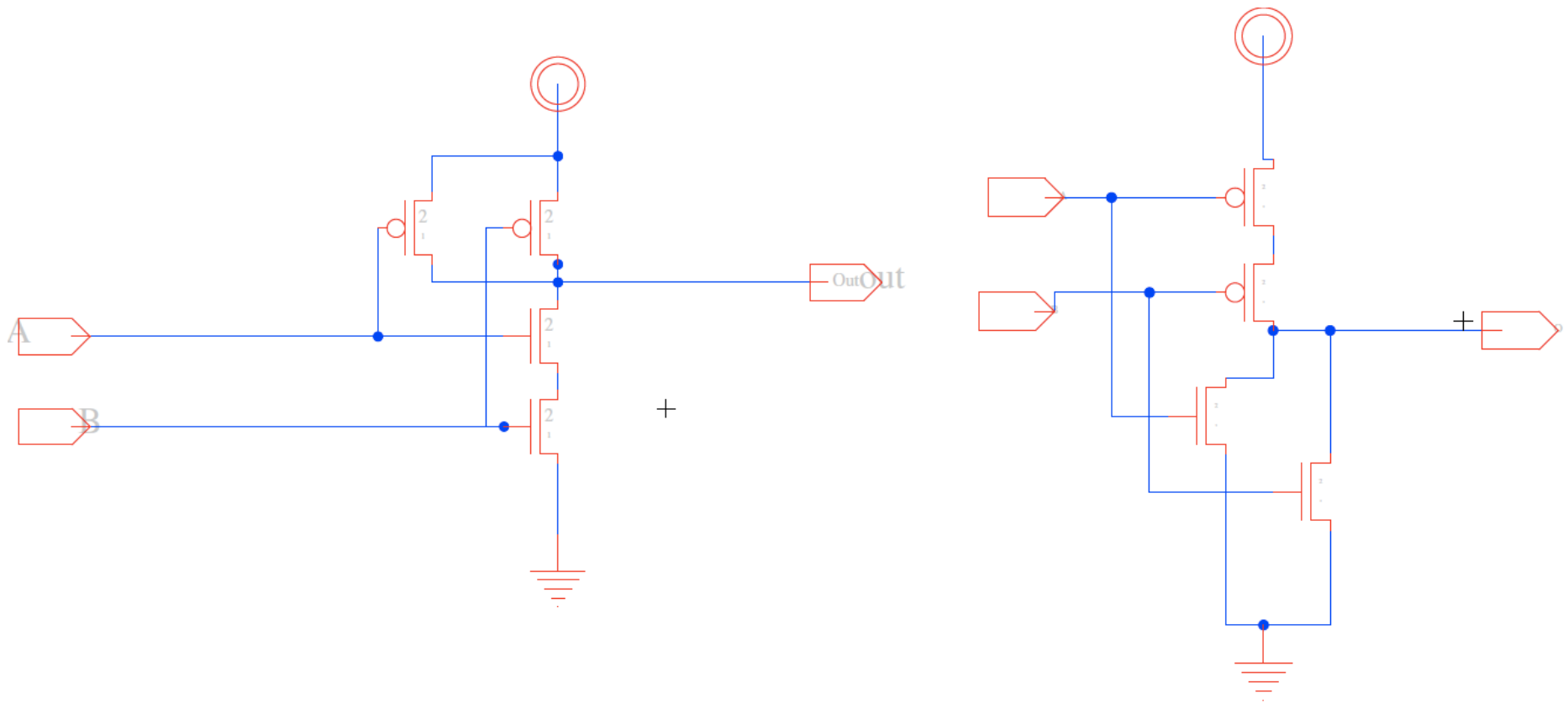



# Ideas

---

- ❑ First order reason in  $\tau = R_0C_0$  units
- ❑ Scaling everything up doesn't help
- ❑ Gates have different efficiencies
  - Drive strength per unit input capacitance
- ❑ Without velocity saturation
  - Reason to prefer nand over nor
- ❑ With velocity saturation
  - nands and nors are similar efficiency
- ❑ Large fanin and fanout slow gates
  - Decompose into stages
  - ...but not too many



# Admin

---

- ❑ HW4 due Wednesday 2/28
- ❑ Drop date is tomorrow 2/27



# Acknowledgement

---

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Jing Li (University of Pennsylvania)


---

## Miller Effect (Optional)






# Capacitance Reminder

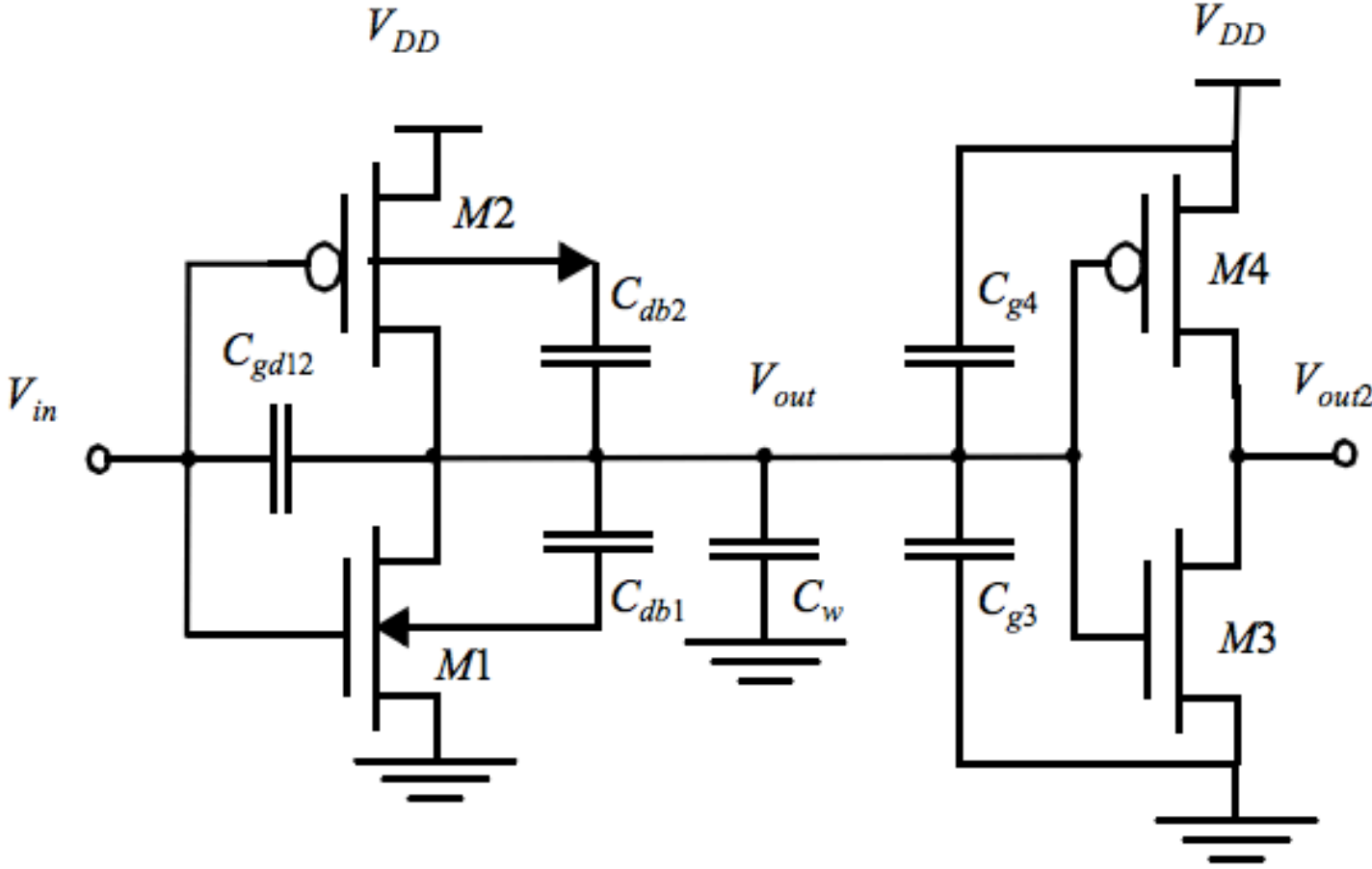




# Charge on Capacitors (preclass 6)

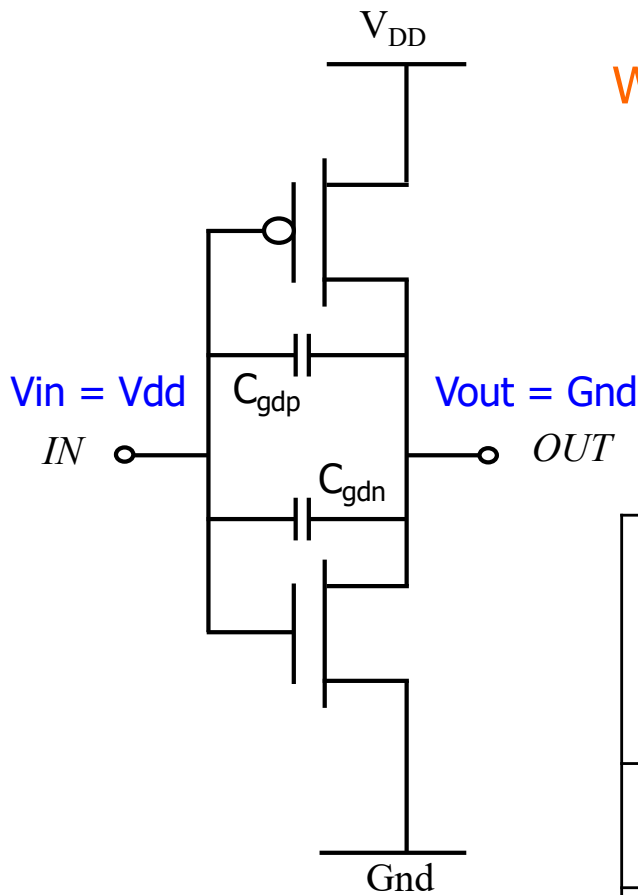

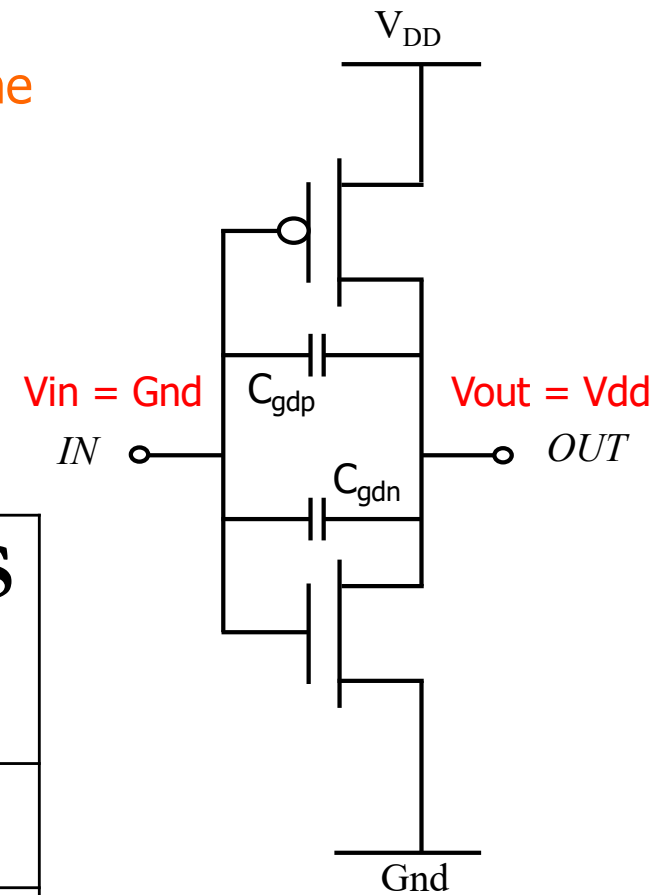What is charge,  $Q$ , on each of the capacitors when  $V_{in} = V_{DD}$  and  $V_{in} = G_{nd}$ ?



	PMOS	NMOS
$V_{in}$	$C_{gdp}$	$C_{gdn}$
$V_{DD}$		
$G_{nd}$		



# Questions


---

- ❑ What is  $\Delta Q$  on each  $C_{gd}$  when input switched?
- ❑ Assuming  $\Delta V = V_{dd}$ , what is equivalent capacitance?


	<b>PMOS</b>	<b>NMOS</b>
Vin	$C_{gdp}$	$C_{gdn}$
Vdd		
Gnd		
 
# Miller Effect For an Inverter

- ❑ Feedback capacitance ( $C_{gd}$ ) between input and output must swing  $2 V_{dd}$
- ❑ Or...behaves same as a double-sized capacitor on the output



# Miller Effect For an Inverter

 

**“A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.”**