

Let:

- $R_0$  – equivalent resistance of minimum size ( $W = L = 1$ ) NMOS transistor
- $I_0$  – equivalent current of minimum size ( $W = L = 1$ ) NMOS transistor
- $C_0$  – gate capacitance of minimum size transistor
- $\tau = R_0 C_0$  – technology-specific delay unit (maybe more accurate today  $\tau = C_0/I_0$ )

1. What are  $I_{ds}$ , R, and C in terms of  $I_0$ ,  $R_0$ , and  $C_0$  for a transistor with width  $W$ :

$R_{drive}$	
$I_{drive}$	
$C_{gate}$	

2. How size for equal rise/fall times assuming  $\mu_n=500 \text{ cm}^2/(V \cdot s)$  and  $\mu_p=200 \text{ cm}^2/(V \cdot s)$ , velocity saturated, and  $|V_{Tp}| = |V_{Tn}|$  and targeting  $R_{drive} = \frac{R_0}{2}$ .

	$W_p$	$W_n$	$C_{in}$ in multiples of $C_0$

3. What is the delay in  $\tau$  units?

	Delay		Delay

4. How should we size the transistors in middle stage?

	$W_p$	$W_n$	Delay in $\tau$

5. What is the delay in  $\tau$  units?

	Delay

We will evaluate two cases now.



- (a) Extreme velocity saturation where  $R_{p0} = R_{n0}$  (i.e.  $I_{ds}$  at rails is same for equally sized N and P devices—simplifying assumption we made for examples from last class)
  - (b)  $R_{p0} = 2R_{n0}$  (i.e.  $I_{ds}$  PMOS at rails is half  $I_{ds}$  of NMOS)
6. How can you size for equal, worst-case rise/fall times assuming targeting  $R_{drive} = \frac{R_0}{2}$  for the two cases above?  $C_a$  is the capacitance of the A input.

	$R_{p0} = R_{n0}$			$R_{p0} = 2R_{n0}$		
	$W_p$	$W_n$	$C_a$	$W_p$	$W_n$	$C_a$
	2	2	$4C_0$	4	2	$6C_0$


7. For a k-input NAND gate, sized for equal, worst-case rise/fall times and targeting  $R_{drive} = \frac{R_0}{2}$ :

	$R_{p0} = R_{n0}$	$R_{p0} = 2R_{n0}$
What is $C_{in}$ as a function of $k$ ?		

8. Assuming sized for  $\frac{R_0}{2}$  drive as above, and input also driven by  $R_{drive} = \frac{R_0}{2}$ , compare the delay of the following three nand32 implementations for the  $R_{p0} = R_{n0}$  case. Include the delay of driving the input and assume each implementation has an output load of  $4C_0$ .

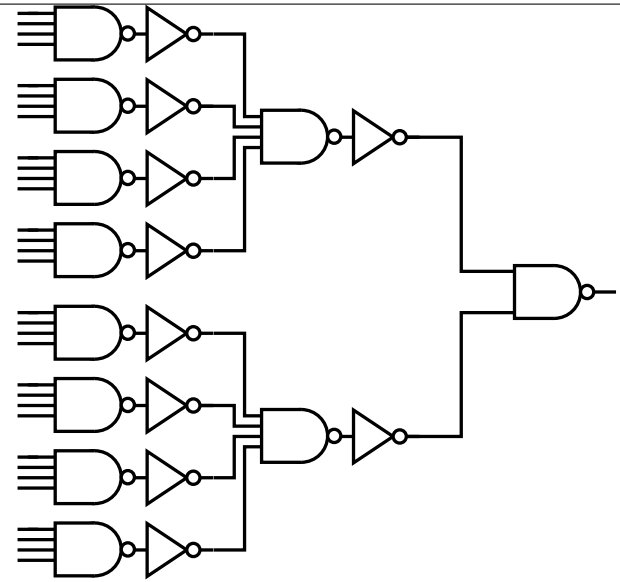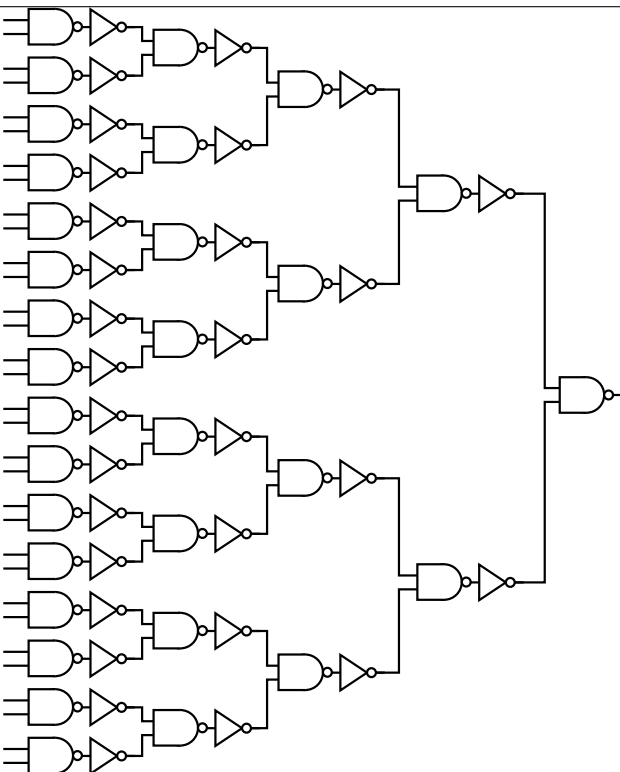Organization	Delay
<p>single-stage nand32</p> 	
	

 9. What is the delay for each of the two implementations below for this logical computation:



Assume  $R_{drive} = \frac{R_0}{2}$  sizing of gates from previous page, and input also driven by  $R_{drive} = \frac{R_0}{2}$ . Assume each implementation has an output load of  $2C_0$ .

	Delay	
	$R_{p0} = R_{n0}$	$R_{p0} = 2R_{n0}$