

**University of Pennsylvania**  
**Department of Electrical and System Engineering**  
**Circuit-Level Modeling, Design, and Optimization for Digital Systems**

ESE3700, Spring 2024

Midterm 1

Wednesday, February 21

---


- 5 problems with weights indicated.
- Parts within a problem will not be weighted equally.
- Calculators allowed. (non-cellphone)
- Closed book = No text or notes allowed.

<b>Name:</b> <a href="#">Answers</a>
--------------------------------------

Grade:


Q1	
Q2	
Q3	
Q4	
Q5	
Total	<a href="#">Mean: 86.25, Std: 12.8</a>

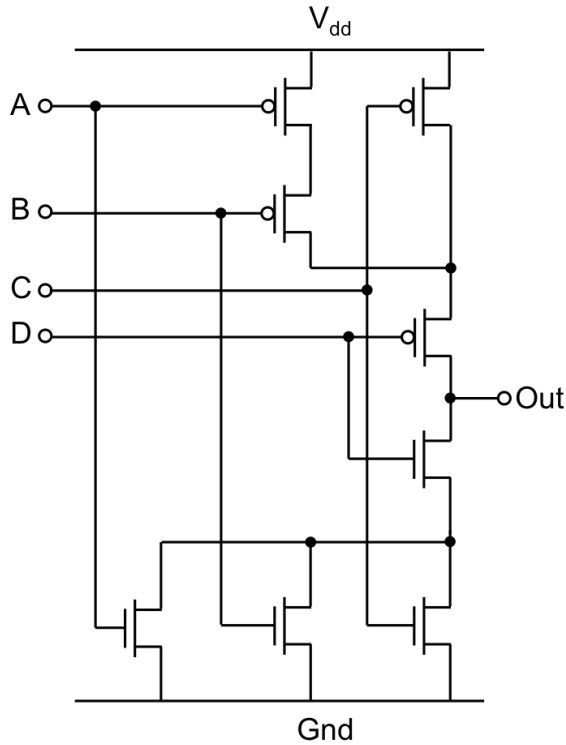1. (27 points) Identify if the following circuits are CMOS, why or why not, and their functions. [Show your work for partial credit consideration.]




(a)

CMOS? (circle one)	Yes	No
(if CMOS) Function (Out)		
(if not CMOS) Why not?	Output undriven for $A=B=C=1, D=0$	

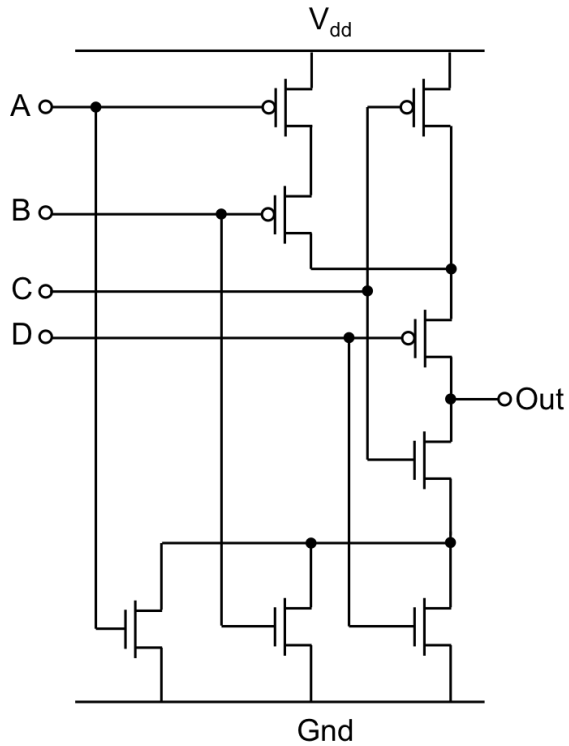

(b)


CMOS? (circle one)	Yes	No
(if CMOS) Function (Out)		
(if not CMOS) Why not?	Output undriven for C=0, D=1	

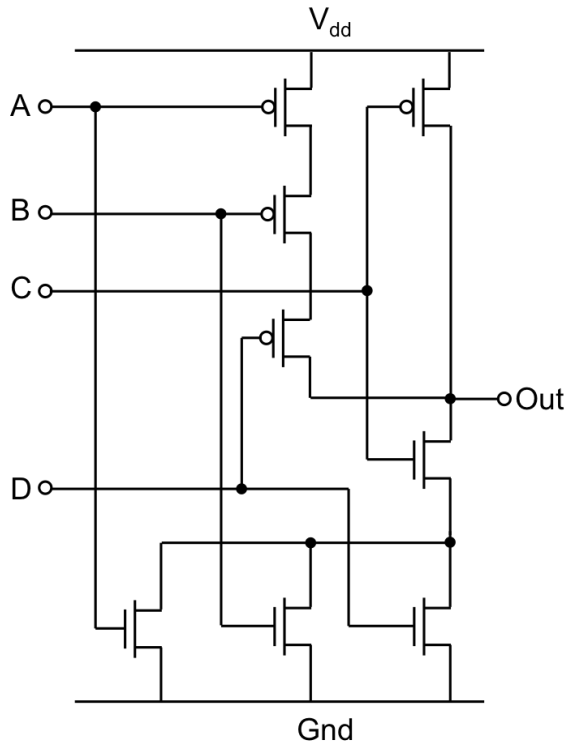

(c)

CMOS? (circle one)	Yes      No
(if CMOS) Function (Out)	$Out = \frac{C}{(A + B + D) \cdot C}$
(if not CMOS) Why not?	

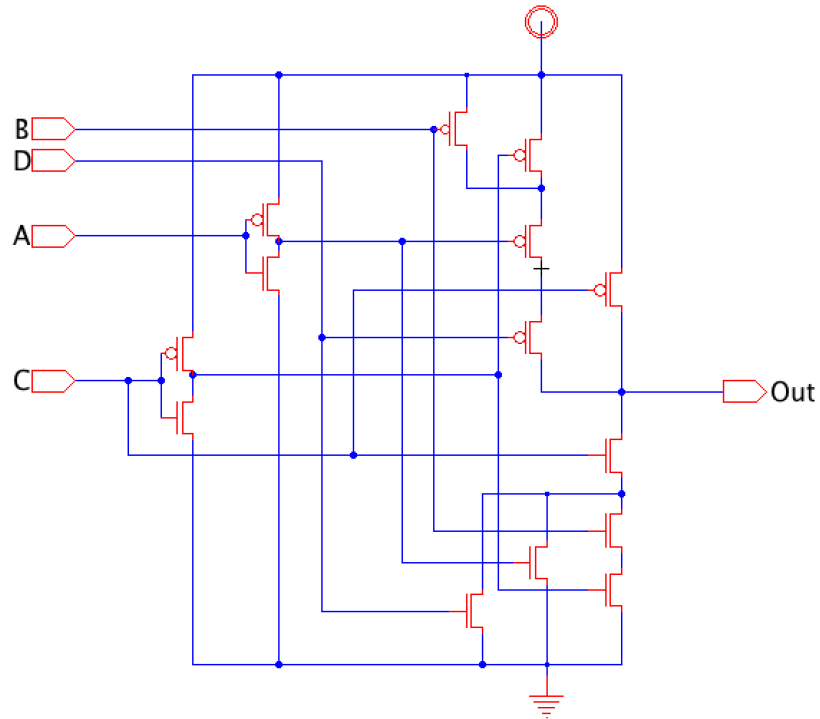2. (26 points) Consider the following circuit:



Assume:

- all transistors are same size.
- all on transistors have resistance  $R_{on}$ .
- all transistors have total gate capacitance  $C_g$ .

(a) Identify the output function.

$$Out = (\overline{B} + C) \cdot A \cdot \overline{D} + \overline{C}$$

(b) Extra credit: Simplify the output function to the minimum sum of products. A K-map grid is provided here for your use.

CD \ AB	00	01	11	10
00	1	1		
01	1	1		
11	1	1		1
10	1	1		1

$$Out = \overline{C} + \overline{D} \cdot A$$

(c) Lowest resistance driving output?

Case:  $A=1, B=C=D=0$

Resistance:  $\frac{3}{4}R_{on}$

(d) Highest resistance driving output?

Case:  $A=B=C=1, D=0$

Resistance:  $3R_{on}$

(e) Lowest capacitance of an input?

Which:  $A,B,D$

Capacitance:  $2C_g$

(f) Highest capacitance of an input?

Which:  $C$

Capacitance:  $4C_g$

**For parts (g)-(h), assume input inverters have 0 delay and all inputs are ideal. I.e. the input  $A$  and  $\bar{A}$  have identical switching characteristics.**

(g) Worst-case 10-90 rise time for one of these gates driving a C-input input of another of these gates?

Case:  $B=C=1, D=0, A:0 \rightarrow 1$

Rise Time Expression:  $2.2 \cdot 3R_{on} \cdot 4C_g = 26.4R_{on}C_g$


(h) Worst-case 10-90 fall time for one of these gates driving a D-input input of another of these gates?

Case:  $A=B=C=1, D:0 \rightarrow 1$


Rise Time Expression:  $2.2 \cdot 2R_{on} \cdot 2C_g = 8.8R_{on}C_g$

[Show calculation for partial credit consideration.]

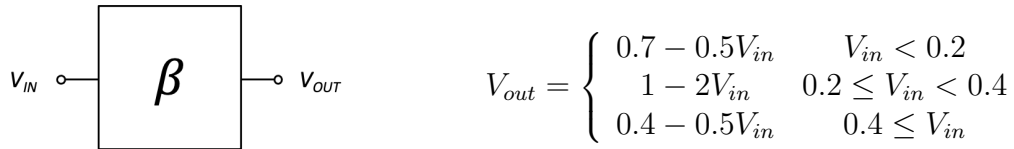
3. (25 pts) For this problem we consider a new non-CMOS technology integrated with a CMOS technology. In addition, to the CMOS gates, we have a non-CMOS  $\beta$ -gate where:



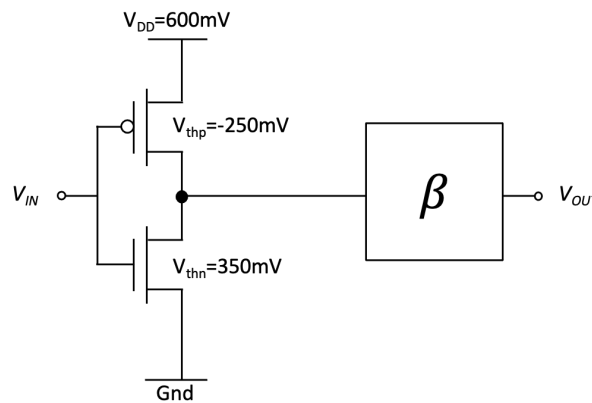Consider the following non-CMOS circuit of a CMOS inverter cascaded with the non-CMOS  $\beta$ -gate. The transistor thresholds are specified on the schematic.



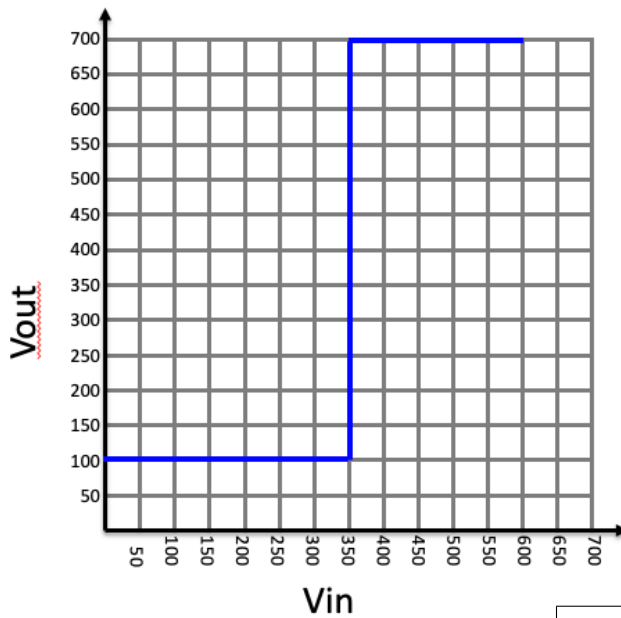- (a) Draw the transfer function of the cascaded gate and identify noise margins that will provide restoration.



$V_{OH}$	700mV
$V_{IH}$	350mV
$V_{IL}$	350mV
$V_{OL}$	100mV
$NM_L$	250mV
$NM_H$	350mV

- (b) What function does the circuit perform?

Buffer

For reference:

NMOS:

$V_{GS}$	$V_{DS}$	Mode
$> V_{th}$	$< V_{GS} - V_{th}$ $> V_{GS} - V_{th}$	Resistive Saturation
$< V_{th}$		Subthreshold


PMOS:

$V_{GS}$	$V_{DS}$	Mode
$< V_{th}$	$> V_{GS} - V_{th}$ $< V_{GS} - V_{th}$	Resistive Saturation
$> V_{th}$		Subthreshold


(You may work on this almost blank page for Problem 3.)



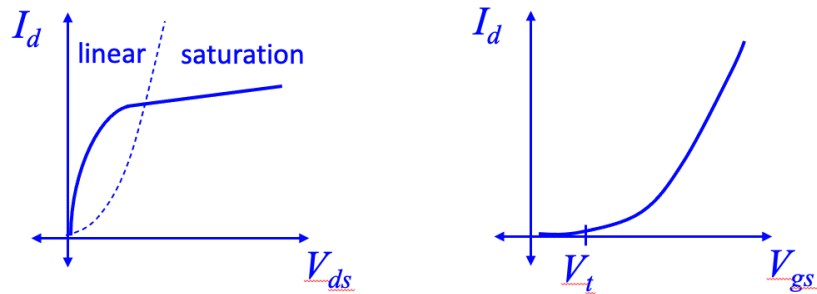4. (10pts) For an NMOS device, draw the IV relationships between drain current and the drain-to-source voltage and gate-to-source voltage ( $I_d$  vs.  $V_{GS}$  and  $I_d$  vs.  $V_{DS}$ ). Label all relevant features. Assume long channel behaviour.



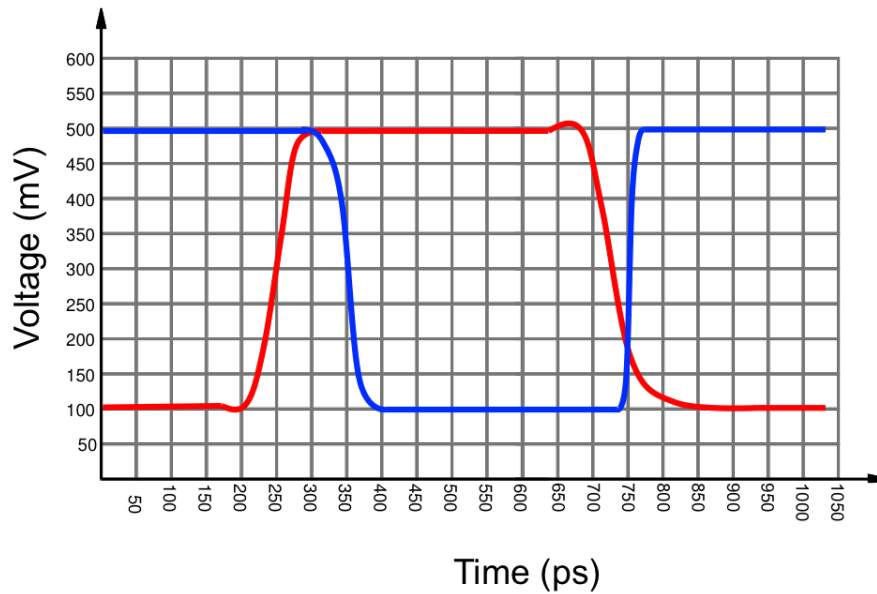5. (12pts) Below are transient waveforms for the input (red) and output (blue) to a logic block. Find the  $\tau_{PLH}$ ,  $\tau_{PHL}$ , and  $\tau_P$  of the logic block. Make sure to include the units.



$\tau_{PLH}$ : 25ps  $\tau_{PHL}$ : 100ps  $\tau_P$ : 62.5ps