

Structure

- LUT sequences ubiquitous

Penn ESE680-002 Spring2007 -- DeHon

Hardwired Logic Blocks

Single Output

Penn ESE680-002 Spring2007 -- DeHon

Hardwired Logic Blocks

Two outputs

9

Penn ESE680-002 Spring2007 -- DeHon

Delay Model

- $T_{\text{cascade}} = T(3\text{LUT}) + T(\text{mux})$
- Don't pay
 - General interconnect
 - Full 4-LUT delay

10

Penn ESE680-002 Spring2007 -- DeHon

Options

11

Penn ESE680-002 Spring2007 -- DeHon

Chung & Rose Study

Figure 8: Delay Study HLB Topologies

12

Penn ESE680-002 Spring2007 -- DeHon [Chung & Rose, DAC '92]

Cascade LUT Mappings

Logic Block	N_R	% decr in N_R	D_{int} (ns)	% decr in D_{int}
K4	5.4	0	30	0
L2-2	4.2	22	26	13
L2-3	3.4	37	22	27
L2-4	3.1	43	21	30
L2-5	3.0	44	21	30
L3-3.2	4.0	26	25	17
L3-4.2	3.0	44	21	30
L3-4.3	3.1	43	21	30
L3-5.2.2	3.1	43	21	30
L3-5.3	3.0	44	21	30
L3-5.4	2.9	46	20	33
L3-6.4	2.8	48	20	33

Table 3: Delay Performance of Different HLBs

[Chung & Rose, DAC '92]


Block Cet	2-inp L2-3	X4000 CLB	4-inp L2-3	4-inp L3-4.2
byrom	40	36	26	19
ab2	77	71	48	37
ab4	126	122	82	61
apex7	44	38	27	20
l3	92	90	56	43
c1354	131	91	80	59
cl	21	17	15	11
cc	17	8	5	7
cmf2a	8	5	5	4
comp	27	17	14	13
count	21	21	14	10
decod	19	10	8	8
emx	10	5	5	5
vda	96	97	70	53
vml	3	3	3	2
Net HLBs	603	561	421	300
LUT Bits	16072	22440	20208	20480
Ratio	0.70	1	0.90	0.91
HLB pins	6530	6171	3473	3440
Ratio	1.06	1	0.80	0.88

Table 2: Area Measures of Different HLBs

13

Penn ESE680-002 Spring2007 -- DeHon

ALU vs. Cascaded LUT?

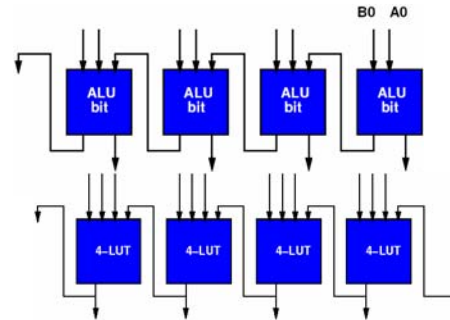

Penn ESE680-002 Spring2007 -- DeHon

14


Datapath Cascade

- ALU/LUT (datapath) Cascade
 - Long “serial” path w/out general interconnect
 - Pay only Tmux and nearest-neighbor interconnect

Penn ESE680-002 Spring2007 -- DeHon

15

4-LUT Cascade ALU

 


Penn ESE680-002 Spring2007 -- DeHon

16

ALU vs. LUT ?

 - Compare/contrast
- ALU
 - Only subset of ops available
 - Denser coding for those ops
 - Smaller
 - ...but interconnect dominates
 - [Datapath width orthogonal to function]




Penn ESE680-002 Spring2007 -- DeHon

17

Parallel Prefix LUT Cascade?

 - Can we do better than $N \times T_{mux}$?
- Can we compute LUT cascade in $O(\log(N))$ time?
- Can we compute mux cascade using parallel prefix?




- Can we make mux cascade associative?

Penn ESE680-002 Spring2007 -- DeHon

18

Parallel Prefix Mux cascade

 - How can mux transform $S \rightarrow \text{mux-out}$?
 - $A=0, B=0 \rightarrow \text{mux-out}=0$
 - $A=1, B=1 \rightarrow \text{mux-out}=1$
 - $A=0, B=1 \rightarrow \text{mux-out}=S$
 - $A=1, B=0 \rightarrow \text{mux-out}=\neg S$




Penn ESE680-002 Spring2007 -- DeHon

19

Parallel Prefix Mux cascade

 - How can mux transform $S \rightarrow \text{mux-out}$?
 - $A=0, B=0 \rightarrow \text{mux-out}=0$ Stop = S
 - $A=1, B=1 \rightarrow \text{mux-out}=1$ Generate = G
 - $A=0, B=1 \rightarrow \text{mux-out}=S$ Buffer = B
 - $A=1, B=0 \rightarrow \text{mux-out}=\neg S$ Invert = I




Penn ESE680-002 Spring2007 -- DeHon

20

Parallel Prefix Mux cascade

 - How can 2 muxes transform input?
- Can I compute 2-mux transforms from 1 mux transforms?



Penn ESE680-002 Spring2007 -- DeHon

21

Two-mux transforms

- $SS \rightarrow S$ • $GS \rightarrow S$ • $BS \rightarrow S$ • $IS \rightarrow S$
- $SG \rightarrow G$ • $GG \rightarrow G$ • $BG \rightarrow G$ • $IG \rightarrow G$
- $SB \rightarrow S$ • $GB \rightarrow G$ • $BB \rightarrow B$ • $IB \rightarrow I$
- $SI \rightarrow G$ • $GI \rightarrow S$ • $BI \rightarrow I$ • $II \rightarrow B$

Penn ESE680-002 Spring2007 -- DeHon

22


Generalizing mux-cascade

- How can N muxes transform the input?
- Is mux transform composition associative?

Penn ESE680-002 Spring2007 -- DeHon


23

Parallel Prefix Mux-cascade

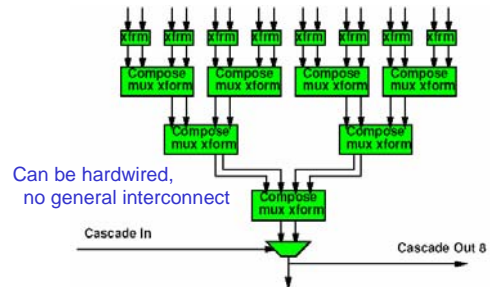


Penn ESE680-002 Spring2007 -- DeHon

24

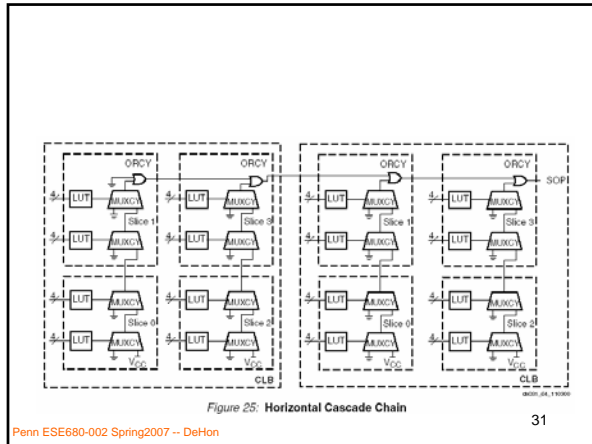


Penn ESE680-002 Spring2007 -- DeHon

31

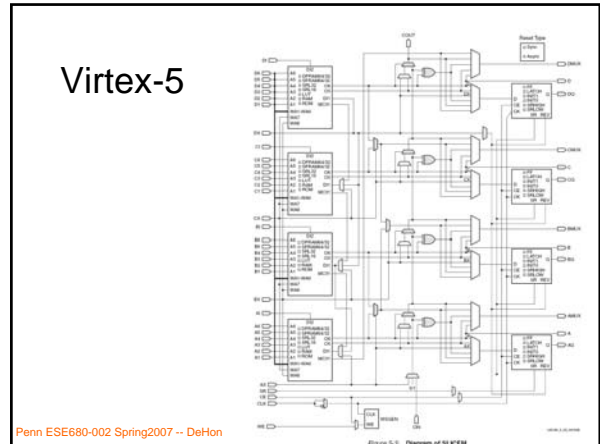


Penn ESE680-002 Spring2007 -- DeHon

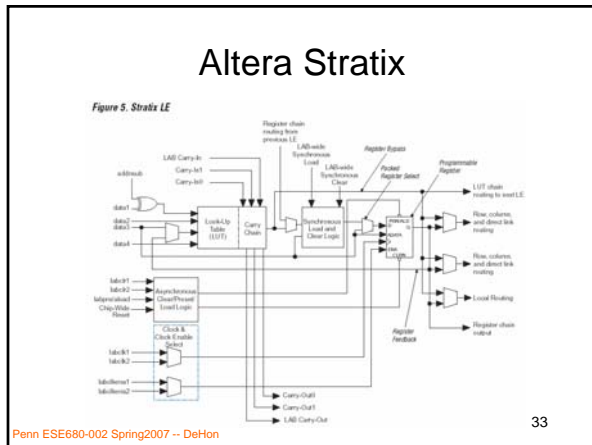


Penn ESE680-002 Spring2007 -- DeHon

33

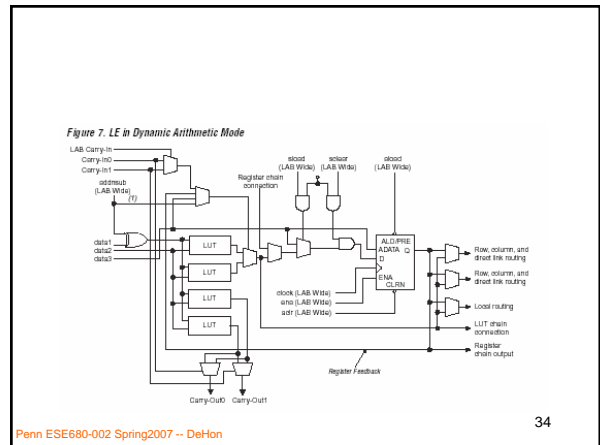


Penn ESE680-002 Spring2007 -- DeHon

34

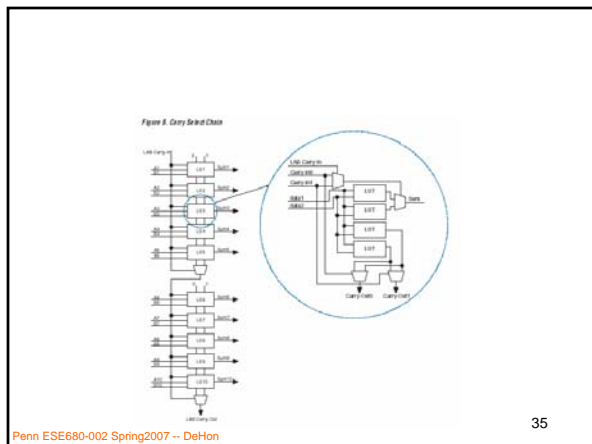

Penn ESE680-002 Spring2007 -- DeHon

35

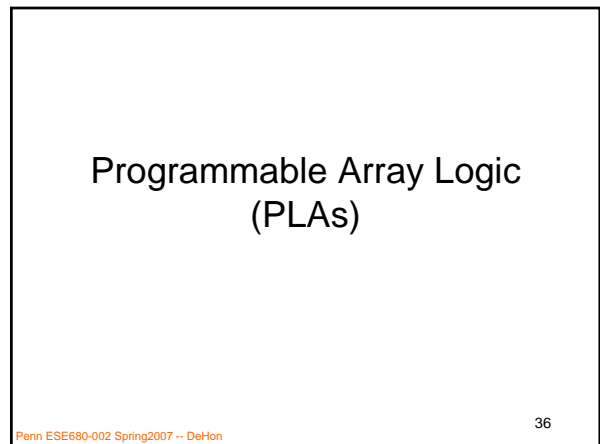

Penn ESE680-002 Spring2007 -- DeHon

36

PLA


- Directly implement flat (two-level) logic
 - $O = a*b*c*d + !a*b!*d + b!*c*d$
- Exploit substrate properties allow wired-OR

Penn ESE680-002 Spring2007 -- DeHon

37

Wired-or

 - Connect series of inputs to wire
- Any of the inputs can drive the wire high




Penn ESE680-002 Spring2007 -- DeHon

38

Wired-or

- Implementation with Transistors

 


Penn ESE680-002 Spring2007 -- DeHon

39

Programmable Wired-or

 
- Use some memory function to programmable connect (disconnect) wires to OR
- Fuse:



Penn ESE680-002 Spring2007 -- DeHon


Programmable Wired-or

- Gate-memory model

 

Penn ESE680-002 Spring2007 -- DeHon

Diagram Wired-or

 


Penn ESE680-002 Spring2007 -- DeHon

42

Wired-or array

 - Build into array
 - Compute many different **or** functions from set of inputs




Penn ESE680-002 Spring2007 -- DeHon

43

Combined or-arrays to PLA

 - Combine two or (**nor**) arrays to produce PLA (**and-or** array)




Programmable Logic Array

Penn ESE680-002 Spring2007 -- DeHon

44

PLA

 
- Can implement each **and** on single line in first array
- Can implement each **or** on single line in second array



Penn ESE680-002 Spring2007 -- DeHon

PLA

 - Efficiency questions:
 - Each **and/or** is linear in total number of potential inputs (not actual)
 - How many product terms between arrays?



Penn ESE680-002 Spring2007 -- DeHon

PLA Product Terms

- Can be exponential in number of inputs
- E.g. n-input **xor** (parity function)
 - When flatten to two-level logic, requires exponential product terms
 - $a^*!b+!a*b$
 - $a^*!b^*!c+!a*b^*!c+!a^*!b^*c+a^*b^*c$
- ...and shows up in important functions
 - Like addition...

Penn ESE680-002 Spring2007 -- DeHon

47

PLAs

- Fast Implementations for large ANDs or ORs
- Number of P-terms **can be** exponential in number of input bits
 - most complicated functions
 - not exponential for many functions
- Can use arrays of small PLAs
 - to exploit structure
 - like we saw arrays of small memories last time

Penn ESE680-002 Spring2007 -- DeHon

48


PLAs vs. LUTs?

- Look at Inputs, Outputs, P-Terms
 - minimum area (one study, see paper)
 - $K=10, N=12, M=3$
- A(PLA 10,12,3) comparable to 4-LUT?
 - 80-130%?
 - 300% on ECC (structure LUT can exploit)
- Delay?
 - Claim 40% fewer logic levels (4-LUT)
 - (general interconnect crossings)

[Kouloheris & El Gamal/CICC'92] 49

Penn ESE680-002 Spring2007 -- DeHon


PLA

 

Penn ESE680-002 Spring2007 -- DeHon


50

PLA and Memory

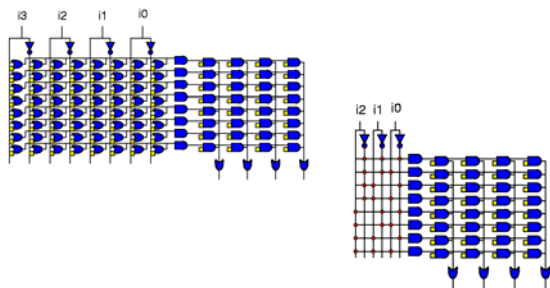

Penn ESE680-002 Spring2007 -- DeHon


PLA and PAL

 

PAL = Programmable Array Logic

Penn ESE680-002 Spring2007 -- DeHon


Conventional/Commercial FPGA

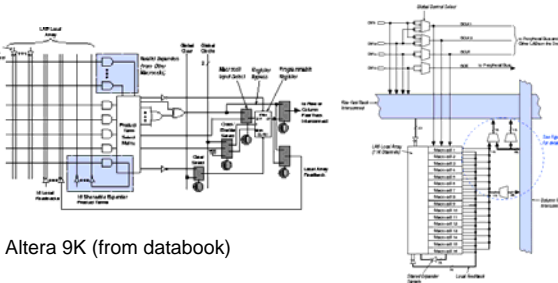

Altera 9K (from databook)

Penn ESE680-002 Spring2007 -- DeHon

Conventional/Commercial FPGA

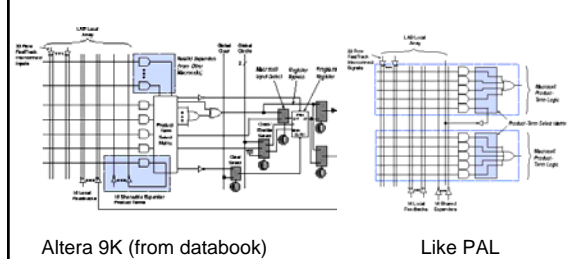

Altera 9K (from databook)

Like PAL

Penn ESE680-002 Spring2007 -- DeHon

54

Big Ideas [MSB Ideas]

- Programmable Interconnect allows us to exploit that structure
 - want to match to application structure
 - Prog. interconnect delay expensive
- Hardwired Cascades
 - key technique to reducing delay in programmables
- PLAs
 - canonical two level structure
 - hardwire portions to get Memories, PALS

Penn ESE680-002 Spring2007 -- DeHon

Big Ideas [MSB-1 Ideas]

- Better structure match with hardwired LUT cascades

Penn ESE680-002 Spring2007 -- DeHon

56