

## ESE680-002 (ESE534): Computer Organization

Day 2: January 10, 2007  
Logic and FSM Review



Penn ESE680-002 Spring2007 -- DeHon

## Last Time

- Computational Design as an Engineering Discipline
- Importance of Costs

Penn ESE680-002 Spring2007 -- DeHon

2

## Today

- Simple abstract computing building blocks
  - gates, boolean logic
  - registers, RTL
- Logic in Gates
  - optimization
  - properties
  - costs
- Sequential Logic

Penn ESE680-002 Spring2007 -- DeHon

3

## Computer Architecture vs. Logic Design

- Logic Design is a mature discipline
  - There are a set of systematic techniques to implement and optimize
  - We can automate those techniques
- Nonetheless, solutions change with costs
  - We can automate wrt a single cost
  - Still work to do for multiple, incomparable costs

Penn ESE680-002 Spring2007 -- DeHon

4

## Stateless Functions (Combinational Logic)

- Compute some “**function**”
  - $f(i_0, i_1, \dots, i_n) \rightarrow o_0, o_1, \dots, o_m$
- Each unique input vector
  - implies a particular, deterministic, output vector

Penn ESE680-002 Spring2007 -- DeHon

5

## Specification in Boolean logic

- $o = a + b$
- $o = / (a * b)$
- $o = a * / b$
- $o = a * / b + b$
- $o = a * b + b * c + d * e + / b * f + f * a + abcdef$
- $o = (a + b) / (b + c) + / b * / c$

Penn ESE680-002 Spring2007 -- DeHon

6

## Implementation in Gates


- **Gate:** small Boolean function
- **Goal:** assemble gates to *cover* our desired Boolean function
- Collection of gates should implement *same* function
- *I.e.* collection of gates and Boolean function should have same Truth Table

Penn ESE680-002 Spring2007 -- DeHon

7

## Covering with Gates

$$o = (a+b)(b+c) + b^*/c$$

 

Penn ESE680-002 Spring2007 -- DeHon

8

## Equivalence


- There is a **canonical** specification for a Boolean function
  - its Truth Table
- Two expressions, gate netlists, a gate netlist and an expression -- are the same iff.
  - They have the same truth table

Penn ESE680-002 Spring2007 -- DeHon

9
 
## Netlist

- **Netlist:** collection of interconnected gates
  - A list of all the gates and what they are connected to



Penn ESE680-002 Spring2007 -- DeHon

10

## Truth Table

$$o = a^*/b^*c + a^*b^*/c + a^*b^*/c + a^*/b^*c$$

a	b	c	o
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


Penn ESE680-002 Spring2007 -- DeHon

11

## How many gates?

$$o = a^*/b^*c + a^*b^*/c + a^*b^*/c + a^*/b^*c$$

a	b	c	o
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 


Penn ESE680-002 Spring2007 -- DeHon

## How many gates?

$$o = (a+b)(b+c) + b^*c$$

a	b	c	o
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

Penn ESE680-002 Spring2007 -- DeHon

13

## Engineering Goal

- Minimize resources
  - area, gates
- Exploit *structure* of logic
- “An Engineer can do for a dime what everyone else can do for a dollar.”

Penn ESE680-002 Spring2007 -- DeHon

14

## Sum of Products

$$o = a^*b^*c + a^*b^*c + a^*b^*c + a^*b^*c$$

$$o = (a+b)(b+c)$$

$$- a^*b + a^*c + b^*c$$

$$o = (a+b)(b+c) + b^*c$$

$$- a^*b + a^*c + b^*c + b^*c$$

Penn ESE680-002 Spring2007 -- DeHon

15

## Minimum Sum of Products

$$o = a^*b^*c + a^*b^*c + a^*b^*c + a^*b^*c$$

$$/b^*c + b^*c$$

Penn ESE680-002 Spring2007 -- DeHon

16

## Minimum Sum of Products

$$o = (a+b)(b+c)$$

$$a^*b + a^*c + b^*c$$

$$a^*b + a^*c + b^*c$$

$$a^*b + b^*c$$

		ab			
		00	01	11	10
c	0	0	0	1	1
	1	0	0	0	1

Penn ESE680-002 Spring2007 -- DeHon

17

## Redundant Terms

$$o = (a+b)(b+c)$$

$$- a^*b + a^*c + b^*c$$

$$- a^*b + b^*c$$

		ab			
		00	01	11	10
c	0	0	0	1	1
	1	0	0	0	1

Penn ESE680-002 Spring2007 -- DeHon

18

## There is a Minimum Area Implementation

- $o = (a+b)(b+c)$ 
  - $a^*b + a^*c + b^*c$
  - $a^*b + b^*c$

$$\begin{array}{r} \phantom{c} \phantom{00} \phantom{01} \phantom{11} \phantom{10} \\ \phantom{c} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \phantom{1} \\ c \phantom{0} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \\ \hline \phantom{c} \phantom{00} \phantom{01} \phantom{11} \phantom{10} \end{array}$$

Penn ESE680-002 Spring2007 -- DeHon

19

## There is a Minimum Area Implementation

- Consider all combinations of fewer gates:
  - any smaller with same truth table?
  - there must be a smallest one.

Penn ESE680-002 Spring2007 -- DeHon

20

## Not Always MSP

- $o = (a+b)(c+d)$ 
  - $a^*b + a^*c + b^*c + b^*d$
- Product of Sums smaller...

3 2-input gates

7 2-input gates

Penn ESE680-002 Spring2007 -- DeHon

21

## Minimize Area

- Area minimizing solutions **depends** on the technology cost structure
- Consider:
  - I1:  $((a*b) + (c*d))*e*f$
  - I2:  $((a*b*e*f) + (c*d*e*f))$
- Area:
  - I1:  $2*A(\text{and2}) + 1*A(\text{or2}) + 1*A(\text{and3})$
  - I2:  $2*A(\text{and4}) + 1*A(\text{or2})$

Penn ESE680-002 Spring2007 -- DeHon

22

## Minimize Area

- I1:  $((a*b) + (c*d))*e*f$
- I2:  $((a*b*e*f) + (c*d*e*f))$
- Area:
  - I1:  $2*A(\text{and2}) + 1*A(\text{or2}) + 1*A(\text{and3})$
  - I2:  $2*A(\text{and4}) + 1*A(\text{or2})$
- all gates take unit area:
  - $A(I2) = 3 < A(I1) = 4$
- gate size proportional to number of inputs:
  - $A(I1) = 2*2 + 2 + 3 = 9 < A(I2) = 2*4 + 2 = 10$

Penn ESE680-002 Spring2007 -- DeHon

23

## Best Solution Depends on Costs

- This is a simple instance of the general point:
  - ... When technology costs change
    - the optimal solution changes.
- In this case, we can develop an automated decision procedure which takes the costs as a parameter.

Penn ESE680-002 Spring2007 -- DeHon

24

## Don't Cares

- Sometimes will have incompletely specified functions:

a	b	c	o
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	x
1	0	0	x
1	0	1	0
1	1	0	0
1	1	1	0

Penn ESE680-002 Spring2007 -- DeHon

25

## Don't Cares

- Will want to pick don't care values to minimize implementation costs:

a	b	c	o	a	b	c	o
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	1
0	1	0	1	0	1	0	1
0	1	1	x	0	1	1	1
1	0	0	x	1	0	0	0
1	0	1	0	1	0	1	0
1	1	0	0	1	1	0	0
1	1	1	0	1	1	1	0

Penn ESE680-002 Spring2007 -- DeHon

26

## NP-hard in General

- Logic Optimization
  - Two Level Minimization
  - Covering w/ reconvergent fanout
- Are NP-hard in general
  - ...but that's not to say it's not viable to find an optimal solution.
- Cover how to attack in an EDA class
  - can point you at rich literature
  - can find software to do it for you

Penn ESE680-002 Spring2007 -- DeHon

27

## Delay in Gates


- Simple model:
  - each gate contributes a fixed delay for passing through it
  - can be different delay for each gate type
  - e.g.
    - inv = 50ps
    - nand2=100ps
    - nand3=120ps
    - and2=130ps

Penn ESE680-002 Spring2007 -- DeHon

28
 
## Path Delay

- Simple Model: Delay along path is the sum of the delays of the gates in the path



Path Delay = Delay(And3i2)+Delay(Or2)

Penn ESE680-002 Spring2007 -- DeHon

29

## Critical Path


- Path lengths in circuit may differ
- Worst-case performance of circuit determined by the longest path
- Longest path designated **Critical Path**

Penn ESE680-002 Spring2007 -- DeHon

30
 
## Multiple Paths

Path Delay = Delay(Or2i1)+Delay(And2)+Delay(Or2)




Path Delay = Delay(And3i2)+Delay(Or2)

Penn ESE680-002 Spring2007 -- DeHon

31

## Critical Path = Longest

Path Delay = 3

 


Path Delay = 2

Penn ESE680-002 Spring2007 -- DeHon

32
 
## Critical Path

- There is always a set of critical paths
  - set such that the path length of the members is at least as long as any other path length
- May be many such paths



Penn ESE680-002 Spring2007 -- DeHon

## Minimum Delay

- There is a minimum delay for a given function and technology cost.
- Like area:
  - consider all circuits of delay 1, 2, ....
  - Work from 0 time (minimum gate delay) up
  - stop when find a function which implements the desired logic function
  - by construction no smaller delay implements function

Penn ESE680-002 Spring2007 -- DeHon

34

## Delay also depend on Costs

- Consider again:
  - I1:  $((a*b) + (c*d))*e*f$
  - I2:  $((a*b*e*f)+(c*d*e*f))$
- Delay:
  - I1:  $D(\text{and2})+D(\text{or2})+D(\text{and3})$
  - I2:  $D(\text{and4})+D(\text{or2})$

Penn ESE680-002 Spring2007 -- DeHon

35

## Delay also depend on Costs

- Delay:
  - I1:  $D(\text{and2})+D(\text{or2})+D(\text{and3})$
  - I2:  $D(\text{and4})+D(\text{or2})$
- $D(\text{and2})=130\text{ps}$ ,  $D(\text{and3})=150\text{ps}$ ,  $D(\text{and4})=170\text{ps}$ 
  - $D(I2)=(170+D(\text{or2})) < D(I1)=(130+150+D(\text{or2}))$
- $D(\text{and2})=90\text{ps}$ ,  $D(\text{and3})=100\text{ps}$ ,  $D(\text{and4})=200\text{ps}$ 
  - $D(I2)=(200+D(\text{or2})) > D(I1)=(90+100+D(\text{or2}))$

Penn ESE680-002 Spring2007 -- DeHon

36

## Delay and Area Optimum Differ

- I1:  $((a*b) + (c*d))*e*f$
- I2:  $((a*b*e*f)+(c*d*e*f))$
- $D(\text{and}2)=130\text{ps}$ ,  $D(\text{and}3)=150\text{ps}$ ,  $D(\text{and}4)=170\text{ps}$ 
  - $D(I2)<D(I1)$
- gate size proportional to number of inputs:
  - $A(I1)<A(I2)$
- **Induced Tradeoff** -- cannot always *simultaneously* minimize area and delay cost

Penn ESE680-002 Spring2007 -- DeHon

37

## Does delay in Gates make Sense?

- Consider a balanced tree of logic gates of depth (tree height)  $n$ .
- Does this have delay  $n$ ?
  - (unit delay gates)
- How big is it? (unit gate area)
- How long a side?
- Minimum wire length from input to output?

Penn ESE680-002 Spring2007 -- DeHon

38

## Delay in Gates make Sense?

- (continuing example)
- How big is it? (unit gate area)  $2^n$
- How long a side?  $\text{Sqrt}(2^n) = 2^{(n/2)}$
- Minimum wire length from input to output?
  - $2*2^{(n/2)}$
- Delay per unit length? (speed of light limit)
  - $\text{Delay} \propto 2^{(n/2)}$

Penn ESE680-002 Spring2007 -- DeHon

39

## It's not all about costs...

- ...or maybe it is, just not always about a single, linear cost.
- Must manage complexity
  - Cost of developing/verifying design
  - Size of design can accomplish in fixed time
    - (limited brainpower)
- **Today:** human brainpower is most often the bottleneck resource limiting what we can build.

Penn ESE680-002 Spring2007 -- DeHon

40

## Review Logic Design

- Input specification as Boolean logic equations
- Represent canonically
  - remove specification bias
- Minimize logic
- Cover minimizing target cost

Penn ESE680-002 Spring2007 -- DeHon

41

## If's


- If  $(a*b + /a*/b)$ 
  - $c=d$
- else
  - $c=e$
  
- $t=a*b+/a*/b$
- $c=t*d + /t*e$

Penn ESE680-002 Spring2007 -- DeHon

42
 
## If → Mux Conversion

- Often convenient to think of IF's as Multiplexers
- If  $(a*b + !a*/b)$   
 $c=d$
- else  
 $c=e$




Penn ESE680-002 Spring2007 -- DeHon

43
 
## Muxes

- Mux:  
 – Selects one of two (several) inputs based on control bit




Penn ESE680-002 Spring2007 -- DeHon

44
 
## Mux Logic

- Of course, Mux is just logic:  
 – mux out =  $!s*a + s*b$




- Two views logically equivalent  
 – mux view more natural/abstract when inputs are multibit values (datapaths)

Penn ESE680-002 Spring2007 -- DeHon

45
 
## What about Tristates/busses?

- Tristate logic:  
 – output can be 1, 0, or undriven  
 – can wire together so outputs can share a wire



- Is this anything different?

Penn ESE680-002 Spring2007 -- DeHon

46

## Tristates

- **Logically:**  
 – No, can model correct/logical operation of tristate bus with Boolean logic  
 – Bus undriven (or multiply driven) is Don't-Care case  
 • no one should be depending on value
- **Implementation:**  
 – sometimes an advantage in distributed control  
 • don't have to build monolithic, central controller

Penn ESE680-002 Spring2007 -- DeHon

## Finite Automata

- Recall from CSE262 (maybe ESE200?)
- A DFA is a quintuple  $M = \{K, \Sigma, \delta, s, F\}$   
 –  $K$  is finite set of states  
 –  $\Sigma$  is a finite alphabet  
 –  $s \in K$  is the start state  
 –  $F \subseteq K$  is the set of final states  
 –  $\delta$  is a transition function from  $K \times \Sigma$  to  $K$

Penn ESE680-002 Spring2007 -- DeHon

48



## Finite Automata

- Less formally:
  - Behavior depends not just on input
    - (as was the case for combinational logic)
  - Also depends on state
  - Can be completely different behavior in each state
  - Logic/output now depends on state and input

Penn ESE680-002 Spring2007 -- DeHon

49

## Minor Amendment

- A DFA is a sextuple  $M = \{K, \Sigma, \delta, s, F, \Sigma_o\}$ 
  - $\Sigma_o$  is a finite set of output symbols
  - $\delta$  is a transition function from  $K \times \Sigma$  to  $K \times \Sigma_o$

Penn ESE680-002 Spring2007 -- DeHon

50

## What power does the DFA add?

Penn ESE680-002 Spring2007 -- DeHon

51

## Power of DFA

- Process unbounded input with finite logic
- State is a finite representation of what's happened before
  - finite amount of stuff can remember to synopsize the past
- State allows behavior to depend on past (on context)

Penn ESE680-002 Spring2007 -- DeHon

52

## Registers

- New element is a state element
- Canonical instance is a register:
  - remembers the last value it was given until told to change
  - typically signaled by clock



Penn ESE680-002 Spring2007 -- DeHon

53

## Issues of Timing...

- ...many issues in detailed implementation
  - glitches and hazards in logic
  - timing discipline in clocking
  - ...
- We're going to work above that level for the most part this term.
- Watch for these details in ESE570

Penn ESE680-002 Spring2007 -- DeHon

54

## Same thing with registers


- Logic becomes:
  - if (state=s1)
    - boolean logic for state 1
      - (including logic for calculate next state)
  - else if (state=s2)
    - boolean logic for state2
  - ...
  - if (state=sn)
    - boolean logic for state n

Penn ESE680-002 Spring2007 -- DeHon

55
 
## Finite-State Machine (FSM)

- Logic core
- Plus registers to hold state



Penn ESE680-002 Spring2007 -- DeHon

## State Encoding

- States not (necessarily) externally visible
- We have *freedom* in how to encode them
  - assign bits to states
- Usually want to exploit freedom to minimize implementation costs
  - area, delay, energy
- (again, algorithms to attack -- EDA)

Penn ESE680-002 Spring2007 -- DeHon

57

## Multiple, Interacting FSMs

- What do I get when I wire together more than one FSM?

Penn ESE680-002 Spring2007 -- DeHon

58

## Multiple, Interacting FSMs

- What do I get when I wire together more than one FSM?
- Resulting composite is also an FSM
  - Input set is union of input alphabets
  - State set is product of states:
    - e.g. for every  $s_{a_i}$  in A.K and  $s_{b_j}$  in B.K there will be a composite state  $(s_{a_i}, s_{b_j})$  in AB.K
  - Think about concatenating state bits

Penn ESE680-002 Spring2007 -- DeHon

59

## Multiple, Interacting FSMs

- In general, could get product number of states
  - $|AB.K| = |A|^*|B|$  ... can get large fast
- All composite states won't necessarily be reachable
  - so real state set may be  $< |A|^*|B|$

Penn ESE680-002 Spring2007 -- DeHon

60

## Multiple, Interacting FSMs

- Multiple, “independent” FSMs
  - often have implementation benefits
    - localize inputs need to see
    - simplify logic
  - decompose/ease design
    - separate into small, understandable pieces
  - can sometimes obscure behavior
    - not clear what composite states are reachable

Penn ESE680-002 Spring2007 -- DeHon

61

## FSM Equivalence

- Harder than Boolean logic
- Doesn't have unique canonical form
- Consider:
  - state encoding not change behavior
  - two “equivalent” FSMs may not even have the same number of states
  - can deal with **infinite** (unbounded) input
  - ...so cannot enumerate output in all cases

Penn ESE680-002 Spring2007 -- DeHon

62

## FSM Equivalence

- What matters is external observability
  - FA accepts and rejects same things
  - FSM outputs same signals in response to every possible input sequence
- Possible?
  - Finite state suggests there is a finite amount of checking required to verify behavior

Penn ESE680-002 Spring2007 -- DeHon

63

## FSM Equivalence Flavor


- Given two FSMs A and B
  - consider the composite FSM AB
  - Inputs wired together
  - Outputs separate
- Ask:
  - is it possible to get into a composite state in which A and B output different symbols?
- There is a literature on this

Penn ESE680-002 Spring2007 -- DeHon

64
 
## FSM Specification

- St1: goto St2
- St2:
  - if (I==0) goto St3
  - else goto St4
- St3:
  - output o0=1
  - goto St1
- St4:
  - output o1=1
  - goto St2
- Could be:
  - behavioral language
  - computer language
  - state-transition graph



Penn ESE680-002 Spring2007 -- DeHon

5

## Systematic FSM Design

- Start with specification
- Can compute boolean logic for each state
  - If conversion...
  - including next state translation
  - Keep state symbolic (s1, s2...)
- Assign states
- Then have combinational logic
  - has current state as part of inputs
  - produces next state as part of outputs
- Design comb. Logic and add state registers

Penn ESE680-002 Spring2007 -- DeHon

66

## Admin: Reminder

- No class **Monday**
  - MLK Holiday
- Next class is Wednesday
  - Logic assignment **due** Wednesday
- Office Hours
  - Nachiket F 12:30-2:00pm (GRW 57)
  - André T 4:00-5:30pm
    - This week Moore 305 (eventually GRW262)

Penn ESE680-002 Spring2007 -- DeHon

67

## Big Ideas [MSB Ideas]

- Can implement any Boolean function in gates
- Can implement any FA with gates and registers

Penn ESE680-002 Spring2007 -- DeHon

68

## Big Ideas [MSB-1 Ideas]

- Canonical representation for combinational logic
- Transformation
  - don't have to implement the input literally
  - only have to achieve same semantics
  - trivial example: logic minimization
- There is a minimum delay, area
- Minimum depends on cost model

Penn ESE680-002 Spring2007 -- DeHon

69