

**University of Pennsylvania**  
**Department of Electrical and System Engineering**  
**Computer Organization**

ESE534, Spring 2010

HW1: Logic

Wednesday, January 13

---

**Due:** Monday, January 25, 12:00PM (except A.3, C.2 as noted)

**For all assignments in this class:** Writeups *must* be done in electronic form and submitted through blackboard. Use CAD or drawing tools where appropriate. **Handwritten assignments and hand-drawn figures are not acceptable.**

You may do sections (A and B) or (B and C). C is primarily intended as a more challenging (interesting) alternative for students who have already had considerable experience with digital logic.

You may use hierarchial schematics. Use of a schematic drawing program for circuits is encouraged.

## A: Basic Logic

1. Implement  $A > B$  out of 2-input NAND gates; assume  $A$  and  $B$  are 4b unsigned numbers. (**Hint:** design the bit slice and show how the bit slices compose for 4b numbers.)
2. Using your comparison function from A.1, show logic for a spatial sorting function to sort 4, 4b inputs into ascending order.
3. Show the logic (RTL logic – *i.e.* logic equations and registers) for a simple vending machine. [Defer this to Monday, February 1 – return with HW2.]

Inputs:  $n$ ,  $d$ , and  $q$ , (nickle, dime, quarter)

Output:  $v$  (vend),  $nc$  (nickle change)

Function: Collect  $\geq 30$  cents, then vend and give change in nickles.

- Don't worry about running out of nickles to provide as change.
- Include a diagram of your state-transition graph in your writeup.
- **Hint:** It is probably easier **not** to use adders and datapath logic for this problem.

Course Web Page: <<http://www.seas.upenn.edu/~ese534/>>

## B: Properties of Boolean Functions

1. Consider all two-input functions. (How many functions are there?)  
For each function, identify if the function is universal; you may tie the inputs of a function to a constant 0 or 1. Your writeup should be a table, with the following entries for each two-input function:
  - list on-set minterms (*i.e.* the truth table)
  - logic expression for function
  - universal?
  - explanation of why or why not
2. Counting each gate as unit size, give a bound on the size ratio between an optimal implementation of an arbitrary  $n$ -input function when the implementation may use an optimal mixture of the full set of 2-input functions from B.2 as gates compared to an implementation which uses only 2-input NOR gates.

## C: Advanced Logic Problems

1. Using only two-input NOR gates, give a bound on the number of different functions that can be implemented with depth  $l$ . (Your bound should be non-trivial, but does not need to be tight.)
2. Firing Squad – Design the logic for an FSmodule. [Defer this to Monday, February 1 – return with HW2.]
  - FSmodules can be assembled into a 1d array of arbitrary length.
  - Each FSmodule is connected exclusively to his left and right neighbors.
  - The leftmost FSmodule will get a start input.
  - FSmodules may have configuration input bits which distinguish the leftmost and rightmost modules from the rest (*i.e.* a module will be leftmost, rightmost, or a chained element).
  - All FSmodules are clocked together.
  - Data can travel from one FSmodule to his adjacent neighbor in one cycle.
  - You can have a constant number of wires between adjacent FSmodules (independent of the length of the 1d array).
  - The state in an FSmodule is finite and independent of the length of the 1d array.
  - In response to an input pulse on the leftmost module, the array of FSmodules should all, simultaneously flash an output light.
  - The number of cycles between the input pulse and the synchronized firing of the FSmodules' lights is not restricted.

Show your state-transition graph and gate logic (you may write equations for the logic as long as the equations identify the primitive gates). Describe the operation of your solution.