

ESE534: Computer Organization

Day 14: March 17, 2010
Compute 1: LUTs



Previously


- Instruction Space Modeling
 - huge range of densities
 - huge range of efficiencies
 - large architecture space
 - modeling to understand design space
- Empirical Comparisons
 - Ground cost of programmability

Today

- Look at Programmable Compute Blocks
- Specifically LUTs
- Recurring theme:
 - define parameterized space
 - identify costs and benefits
 - look at typical application requirements
 - compose results, try to find best point


Compute Function

 - What do we use for “compute” function
- Any Universal
 - NANDx
 - ALU
 - LUT




Lookup Table

 - Load bits into table
 - 2^N bits to describe
 - $\rightarrow 2^{2^N}$ different functions
- Table translation
 - performs logic transform



Lookup Table

 

We could...


- Just build a large memory = large LUT
- Put our function in there
- What's wrong with that?

How big is a k-LUT?


- k-input, 1-output?
- k-input, m-output?

FPGA = Many small LUTs

Alternative to one big LUT

 

Toronto FPGA Model

 


What's best to use?

- Small LUTs
- Large Memories
- ...small LUTs or large LUTs
- **Continuum question:** how big should our memory blocks used to perform computation be?

Start to Sort Out: Big vs. Small Luts

- Establish equivalence
 - how many small LUTs equal one big LUT?

“gates” in 2-LUT ?

 


Penn ESE534 Spring2010 -- DeHon

13

How Much Logic in a LUT?

 - Lower Bound?
 - Concrete: 4-LUTs to implement M-LUT?
- Not use all inputs?
 - 0 ... maybe 1
- Use all inputs?
 - $(M-1)/3$



$(M-1)/(k-1)$ for K-lut


example M-input AND
 • cover 4 ins w/ first 4-LUT,
 • 3 more and cascade input
 with each additional

14

Penn ESE534 Spring2010 -- DeHon

How much logic in a LUT?

 - Upper Upper Bound:
 - M-LUT implemented w/ 4-LUTs
 - $M\text{-LUT} \leq 2^{M-4} + (2^{M-4} - 1) \leq 2^{M-3}$ 4-LUTs



Penn ESE534 Spring2010 -- DeHon

15

How Much?

- Lower Upper Bound:
 - 2^M functions realizable by M-LUT
 - Say Need n 4-LUTs to cover; compute n :
 - strategy count functions realizable by each
 - $(2^{2^4})^n \geq 2^{2^M}$
 - $n \log(2^{2^4}) \geq \log(2^{2^M})$
 - $n 2^4 \log(2) \geq 2^M \log(2)$
 - $n 2^4 \geq 2^M$
 - $n \geq 2^{M-4}$

Penn ESE534 Spring2010 -- DeHon

16

How Much?

- Combine
 - Lower Upper Bound
 - Upper Lower Bound
 - (number of 4-LUTs in M-LUT)

$$2^{M-4} \leq n \leq 2^{M-3}$$

Penn ESE534 Spring2010 -- DeHon

17

Memories and 4-LUTs

- For the **most complex** functions
 - an M-LUT has $\sim 2^{M-4}$ 4-LUTs
- ◇ SRAM 32Kx8 $\lambda=0.6\mu\text{m}$
 - $170M\lambda^2$ (21ns latency)
 - $8 \cdot 2^{11} = 16K$ 4-LUTs
- ◇ XC3042 $\lambda=0.6\mu\text{m}$
 - $180M\lambda^2$ (13ns delay per CLB)
 - 288 4-LUTs
- Memory is 50+x denser than FPGA
 - ... and faster

Penn ESE534 Spring2010 -- DeHon

18

Memory and 4-LUTs

- For “regular” functions?
 - ◇ 15-bit parity
 - entire 32Kx8 SRAM
 - 5 4-LUTs
 - (2% of XC3042 ~ $3.2M\lambda^2 \sim 1/50\text{th Memory}$)

16-bit Adder from Memory and 3-LUTs


- How many inputs? outputs?
- Area for single large LUT?
- How many 3-LUTs?
- Area per 3-LUT?
- Area to implement adder with 3-LUTs?
- Ratio?

Memory and 4-LUTs

- Same 32Kx8 SRAM
 - ◇ 7b Add
 - entire 32Kx8 SRAM (largest will support)
 - 14 4-LUTs
 - (5% of XC3042, $8.8M\lambda^2 \sim 1/20\text{th Memory}$)


LUT + Interconnect

 - Interconnect allows us to exploit **structure** in computation
- Consider addition:
 - N-input add takes
 - 2N 3-LUTs
 - one N-output (2N)-LUT
 - $N \times 2^{(2N)} \gg 2N \times 2^3$
 - $N=16: 16 \times 2^{32} \gg 2 \times 16 \times 2^3$
 - $2^{36} \gg 2^8 \rightarrow \text{factor of } 2^{28} = 256 \text{ Million}$






LUT + Interconnect

- Interconnect allows us to exploit **structure** in computation
- Even if Interconnect was 99% of the area ($100 \times$ logic area)
 - Would still be worth paying!
 - Add: $N \times 2^{(2N)} \gg 2N \times (2^3 \times 128)$
 - $N=16: 16 \times 2^{36} \gg 2 \times 16 \times 2^{10} = 2^{15}$
 - $\rightarrow \text{factor of } 2^{21} = 2 \text{ Million}$
- Structure exploitation to avoid exponential costs is worth it!

 

Different Instance of a Familiar Concept




 
 
 
- The most general functions are huge
- Applications exhibit **structure**
 - Typical functions not so complex
- Exploit structure to optimize “common” case



- ### Toronto Experiments
- Want to determine best K for LUTs
 - Bigger LUTs
 - handle complicated functions efficiently
 - less interconnect overhead
 - Smaller LUTs
 - handle regular functions efficiently
 - interconnect allows exploitation of compute structure
 - What's the typical complexity/structure?
 - [Rose et al., JSSC 25(5):1217–1225, 1990] 28
- Penn ESE534 Spring2010 -- DeHon


- ### Standard Systematization
- Define a design/optimization space
 - pick key parameters
 - e.g. K = number of LUT inputs
 - Build a cost model
 - Map designs
 - Look at resource costs at each point
 - Compose:
 - Logical Resources ⊕ Resource Cost
 - Look for best design points
- Penn ESE534 Spring2010 -- DeHon 29

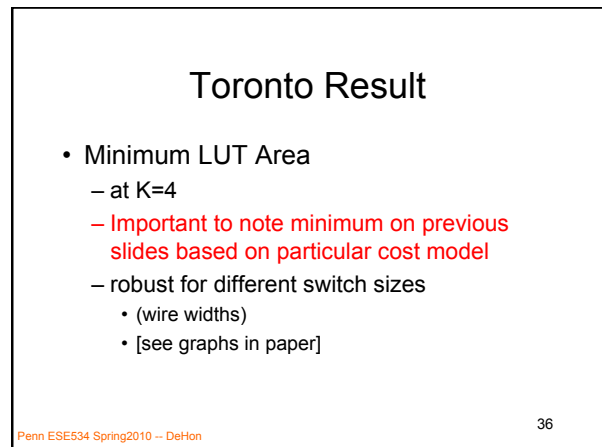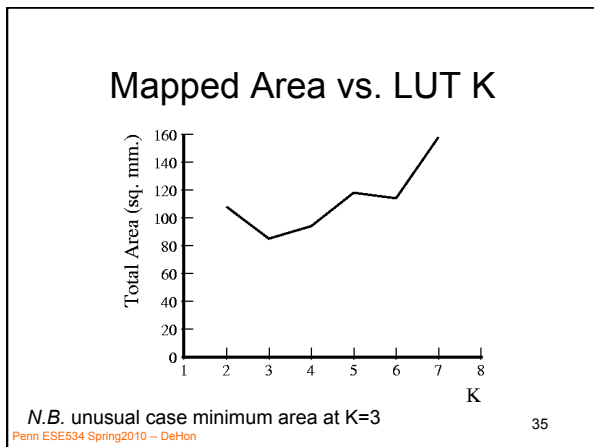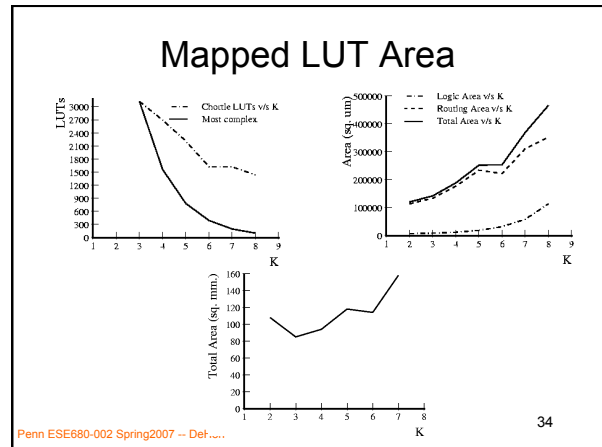 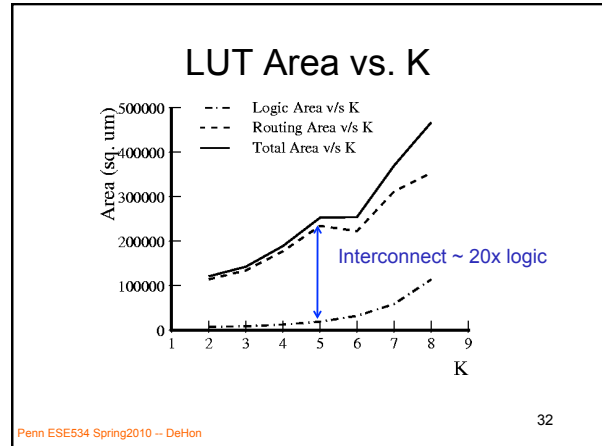 - ### Toronto LUT Size
-
- Map to K-LUT
 - use Chortle
 - Route to determine wiring tracks
 - global route
 - different channel width W for each benchmark
 - Area Model for K and W
 - A_{lut} exponential in K
 - Interconnect area based on switch count
- Penn ESE534 Spring2010 -- DeHon 30



Implications

 - Custom? / Gate Arrays?
- More restricted logic functions?



Penn ESE534 Spring2010 -- DeHon

37


Delay

Penn ESE534 Spring2010 -- DeHon

38

Delay?

 - Circuit Depth in LUTs?
- Lower bound?
- “Simple Function” → M-input AND




Penn ESE534 Spring2010 -- DeHon

39

Delay?

 - M-input “Complex” function
 - 1 table lookup for M-LUT
 - Lower Upper bound: $\lceil \log_k(2^{(M-k)}) \rceil + 1$
 - $\log_k(2^{(M-k)}) = (M-k)\log_k(2)$



Penn ESE534 !

40

Some Math


- $Y = \log_k(2)$
- $k^Y = 2$
- $Y \log_2(k) = 1$
- $Y = 1/\log_2(k)$
- $\log_k(2) = 1/\log_2(k)$
- $(M-k)\log_k(2)$
- $(M-k)/\log_2(k)$

Penn ESE534 Spring2010 -- DeHon

41

Delay?

 - M-input “Complex” function
 - Lower Upper bound: $\lceil \log_k(2^{(M-k)}) \rceil + 1$
 - $\log_k(2^{(M-k)}) = (M-k)\log_k(2)$
 - Lower Upper Bound: $\lceil (M-k)/\log_2(k) \rceil + 1$




Penn ESE534 !

42

Delay?

 - M-input "Complex" function
 - Upper Bound:
 - use each k-lut as a $k - \log_2(k)$ input mux
 - Upper Bound: $\lceil (M-k)/\log_2(k - \log_2(k)) \rceil + 1$




Penn ESE534 :

43

Delay?

 - M-input "Complex" function
 - 1 table lookup for M-LUT
 - between: $\lceil (M-k)/\log_2(k) \rceil + 1$
 - and $\lceil (M-k)/\log_2(k - \log_2(k)) \rceil + 1$



Penn ESE534 :

44


Delay

- Simple:** $\log M$
- Complex:** linear in M
- Both scale as $1/\log(k)$

Penn ESE534 Spring2010 -- DeHon

45

Circuit Depth vs. K

 


[Rose et al., JSSC 27(3):281-287, 1992] 46

Penn ESE534 Spring2010 -- DeHon

LUT Delay vs. K

 
- For small LUTs:
 - $t_{LUT} \approx C_0 + C_1 \times K$
- Large LUTs:
 - add length term
 - $C_2 \times \sqrt{2^K}$
- Plus Wire Delay
 - $\sim \sqrt{\text{area}}$



Penn ESE534 Spring2010 -- DeHon

47

Delay vs. K

 


Delay = Depth \times ($t_{LUT} + t_{interconnect}$)

Why not satisfied with this model?

Penn ESE534 Spring2010 -- DeHon

48

 Delay vs. K (proper critical path interconnect)



Penn ESE534 Spring2010 -- DeHon

[Luu et al., FPGA 2009]

49

Observation

- General interconnect is expensive
- “Larger” logic blocks
 - ↳ fewer interconnect crossings
 - ↳ reduces interconnect delay
 - ↳ get larger
 - ↳ less area efficient
 - don't match structure in computation
 - ↳ get slower
 - Happens faster than modeled here due to area

Penn ESE534 Spring2010 -- DeHon

50

Admin

- Reading
 - Today's: classic paper...definitely read
 - Wed. → no required reading
- Next Wednesday will have guest lecture
 - Relevant to final project

Penn ESE534 Spring2010 -- DeHon

51

Big Ideas [MSB Ideas]

- Memory most dense programmable structure for the **most complex** functions
- Memory inefficient (scales poorly) for structured compute tasks
- **Most tasks have structure**
- Programmable interconnect allows us to exploit that structure

Penn ESE534 Spring2010 -- DeHon

52

Big Ideas [MSB-1 Ideas]

- Area
 - LUT count decrease w/ K, but slower than exponential
 - LUT size increase w/ K
 - exponential LUT function
 - empirically linear routing area
 - Minimum area around K=4

Penn ESE534 Spring2010 -- DeHon

53

Big Ideas [MSB-1 Ideas]

- Delay
 - LUT depth decreases with K
 - in practice closer to $\log(K)$
 - Delay increases with K
 - small K linear + large fixed term

Penn ESE534 Spring2010 -- DeHon

54