

ESE534: Computer Organization

Day 2: January 20, 2010
Universality, Gates, Logic

Work Preclass Exercise



Penn ESE534 Spring2010 -- DeHon

Last Time

- Computational Design as an Engineering Discipline
- Importance of Costs

Penn ESE534 Spring2010 -- DeHon

2

Today

- Universality
- Simple abstract computing building blocks
 - gates, Boolean Equations
 - RTL Logic (at least the logic part)
- Logic in Gates
 - optimization
 - properties
 - Costs

Penn ESE534 Spring2010 -- DeHon

3

Preclass 1

- Do the Case 1 circuits calculate the same thing?
- Case 2?

Penn ESE534 Spring2010 -- DeHon

4

General

- How do we define equivalence?
 - How do we determine if two circuits are equivalent?

Penn ESE534 Spring2010 -- DeHon

5

Model: Stateless Functions (Combinational Logic)

- Compute some **“function”**
 - $f(i_0, i_1, \dots, i_n) \rightarrow o_0, o_1, \dots, o_m$
- Each unique input vector
 - implies a particular, deterministic, output vector

Penn ESE534 Spring2010 -- DeHon

6

Boolean Equivalence

- Two functions are equivalent when
 - They have the same outputs for every input vector
 - *i.e.*, they have the same truth table
- There is a **canonical** specification for a Boolean function
 - its Truth Table

Penn ESE534 Spring2010 -- DeHon

7

Implementation in Gates


- **Gate**: small Boolean function
- **Goal**: assemble gates to *cover* our desired Boolean function
- Collection of gates should implement *same* function
- *i.e.* collection of gates and Boolean function should have same Truth Table

Penn ESE534 Spring2010 -- DeHon

8

Netlist

 - **Netlist**: collection of interconnected gates
 - A list of all the gates and what they are connected to



Penn ESE534 Spring2010 -- DeHon

9

Implementation

- How can I implement any Boolean function with gates?

Penn ESE534 Spring2010 -- DeHon

10

Implementation

- Single output {0, 1}
 - Use inverters to produce complements of inputs
 - For each input case (minterm)
 - If output is a 1
 - Develop an AND to detect that case
 - » Decompose AND into gates
 - OR together all such minterms
 - Decompose OR into gates
- Multiple outputs
 - Repeat for each output

Penn ESE534 Spring2010 -- DeHon

11

Universal set of primitives

- What primitives did I need to support previous implementation set?
- **Conclude**: can implement any Boolean function by a netlist of gates selected from a small set.
- **Homework (B.1)**: How small can set be?

Penn ESE534 Spring2010 -- DeHon

12

Boolean Equations

- $o = /a*/b*c + /a*b*/c + a*b*/c + a*/b*c$

- Another way to express Boolean functions

a	b	c	o
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Penn ESE534 Spring2010 -- DeHon

13

Boolean Equations

- $o = /a*/b*c + /a*b*/c + a*b*/c + a*/b*c$

- Another way to express Boolean functions

a	b	c	o
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Penn ESE534 Spring2010 -- DeHon

14

Boolean Equations

- Can be more compact:

$$O = a*b*c*d*e + /a*/b*/c*/d*/e$$

- Often use in Register Transfer Language (RTL) expressions
 - Write logic (boolean equations) occur between registers
 - Homework 1 A.3 (deferred to HW2)

Penn ESE534 Spring2010 -- DeHon

15

If's

- If ($a*b + /a*/b$)

$$c = d$$

- else

$$c = e$$

- $t = a*b + /a*/b$

- $c = t*d + /t*e$

How does this turn into Boolean logic?

Penn ESE534 Spring2010 -- DeHon

16

If → Mux Conversion


- Often convenient to think of IF's as Multiplexers

- If ($a*b + /a*/b$)

$$c = d$$

- else

$$c = e$$

 


Penn ESE534 Spring2010 -- DeHon

17

Muxes

- Mux:

 - Selects one of two (several) inputs based on control bit




Penn ESE534 Spring2010 -- DeHon

18

Mux Logic

 - Of course, Mux is just logic:
 - mux out = $\bar{s}a + s\bar{b}$



- Two views logically equivalent
 - mux view more natural/abstract when inputs are multibit values (datapaths)

Penn ESE534 Spring2010 -- DeHon

19

Engineering Goal

- Minimize resources
 - area, gates
- Exploit *structure* of logic
- “An Engineer can do for a dime what everyone else can do for a dollar.”

Penn ESE534 Spring2010 -- DeHon

20

Sum of Products

- $o = \bar{a}\bar{b}c + a\bar{b}c + a\bar{b}\bar{c} + a\bar{b}c$
- $o = (a+b)(\bar{b}+c)$
 - $a\bar{b} + a\bar{c} + b\bar{c}$
- $o = (a+\bar{b})(\bar{b}+c) + \bar{b}c$
 - $a\bar{b} + a\bar{c} + \bar{b}c + \bar{b}c$

Penn ESE534 Spring2010 -- DeHon

21

Minimum Sum of Products

- $o = \bar{a}\bar{b}c + a\bar{b}c + a\bar{b}\bar{c} + a\bar{b}c$
- $\bar{b}c + \bar{b}c$

Penn ESE534 Spring2010 -- DeHon

22

Minimum Sum of Products

- $o = (a+b)(\bar{b}+c)$
- $a\bar{b} + a\bar{c} + b\bar{c}$
- $a\bar{b} + a\bar{c} + b\bar{c}$
- $a\bar{b} + b\bar{c}$

		ab			
		00	01	11	10
c	0	0	1	1	1
	1	0	0	0	1

Term $a\bar{c}$ is redundant

Penn ESE534 Spring2010 -- DeHon

23

Least Cost is not always MSP

- $o = (a+b)(c+d)$ 3 2-input gates
 - $a\bar{b} + a\bar{c} + b\bar{c} + b\bar{d}$
 - $(a\bar{b} + a\bar{c}) + (b\bar{c} + b\bar{d})$ 7 2-input gates
- Product of Sums smaller...

Penn ESE534 Spring2010 -- DeHon

24

Logic Optimization

- There are many logical equivalent specifications for a function.
- Freedom to choose
- Exploit to select one that costs the least

- Potentially different from the one specified by the designer

Penn ESE534 Spring2010 -- DeHon

25

Cheapest?

- Which of the equivalent solutions is cheapest depends on the cost model.

Penn ESE534 Spring2010 -- DeHon

26

Minimize Area

- Area minimizing solutions **depends** on the technology cost structure
- Consider:
 - I1: $((a*b) + (c*d))*e*f$
 - I2: $((a*b*e*f)+(c*d*e*f))$
- Area:
 - I1: $2*A(\text{and2})+1*A(\text{or2})+1*A(\text{and3})$
 - I2: $2*A(\text{and4})+1*A(\text{or2})$

Penn ESE534 Spring2010 -- DeHon

27

Minimize Area

- I1: $((a*b) + (c*d))*e*f$
- I2: $((a*b*e*f)+(c*d*e*f))$
- Area:
 - I1: $2*A(\text{and2})+1*A(\text{or2})+1*A(\text{and3})$
 - I2: $2*A(\text{and4})+1*A(\text{or2})$
- all gates take unit area:
 - $A(I2)=3 < A(I1)=4$
- gate size proportional to number of inputs:
 - $A(I1)=2*2+2+3=9 < A(I2)=2*4+2=10$

Penn ESE534 Spring2010 -- DeHon

28

Best Solution Depends on Costs

- This is a simple instance of the general point:
 - ...When technology costs change
 - the optimal solution changes.
- In this case, we can develop an algorithm that takes the costs as a parameter.

Penn ESE534 Spring2010 -- DeHon

29

Don't Cares

- Sometimes will have incompletely specified functions:

a	b	c	o
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	x
1	0	0	x
1	0	1	0
1	1	0	0
1	1	1	0

Penn ESE534 Spring2010 -- DeHon

30

Don't Cares

- Will want to pick don't care values to minimize implementation costs:

a	b	c	o	a	b	c	o
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	1
0	1	0	1	0	1	0	1
0	1	1	x	0	1	1	1
1	0	0	x	1	0	0	0
1	0	1	0	1	0	1	0
1	1	0	0	1	1	0	0
1	1	1	0	1	1	1	0

Penn ESE534 Spring2010 -- DeHon

31

NP-hard in General

See end of Slide set

- Logic Optimization
 - Two Level Minimization
 - Covering w/ reconvergent fanout
- Are NP-hard in general
 - ...but that's **not** to say it's not viable to find an optimal solution.
- Cover how to attack in an ESE535
 - can point you at rich literature
 - can find software to do it for you

Penn ESE534 Spring2010 -- DeHon

32

Delay in Gates


- Simple model:
 - each gate contributes a fixed delay for passing through it
 - can be different delay for each gate type
 - e.g.
 - inv = 10ps
 - nand2=15ps
 - nand3=20ps
 - and2=22ps

Penn ESE534 Spring2010 -- DeHon

33

Path Delay

 - Simple Model: Delay along path is the sum of the delays of the gates in the path



$$\text{Path Delay} = \text{Delay}(\text{And3i2}) + \text{Delay}(\text{Or2})$$

Penn ESE534 Spring2010 -- DeHon

34

Critical Path


- Path lengths in circuit may differ
- Worst-case performance of circuit determined by the longest path
- Longest path designated **Critical Path**

Penn ESE534 Spring2010 -- DeHon

35

Multiple Paths
 
$$\text{Path Delay} = \text{Delay}(\text{Or2i1}) + \text{Delay}(\text{And2}) + \text{Delay}(\text{Or2})$$




$$\text{Path Delay} = \text{Delay}(\text{And3i2}) + \text{Delay}(\text{Or2})$$

Penn ESE534 Spring2010 -- DeHon

36

Critical Path = Longest

Path Delay = 3

 


Path Delay = 2

Penn ESE534 Spring2010 -- DeHon

37

Critical Path

 - There is always a set of critical paths
 - set such that the path length of the members is at least as long as any other path length
- May be many such paths



Penn ESE534 Spring2010 -- DeHon

Delay also depend on Costs

- Consider again:
 - I1: $((a*b) + (c*d))*e*f$
 - I2: $((a*b*e*f)+(c*d*e*f))$
- Delay:
 - I1: $D(\text{and2})+D(\text{or2})+D(\text{and3})$
 - I2: $D(\text{and4})+D(\text{or2})$

Penn ESE534 Spring2010 -- DeHon

39

Delay also depend on Costs


- Delay:
 - I1: $D(\text{and2})+D(\text{or2})+D(\text{and3})$
 - I2: $D(\text{and4})+D(\text{or2})$
- $D(\text{and2})=22\text{ps}$, $D(\text{and3})=27\text{ps}$, $D(\text{and4})=33\text{ps}$
 - $D(I2)=(33+D(\text{or2})) < D(I1)=(22+27+D(\text{or2}))$

Penn ESE534 Spring2010 -- DeHon

40

Gate Delay

Why delay increase with number inputs?

 

Penn ESE534 Spring2010 -- DeHon

41

Delay also depend on Costs

- Delay:
 - I1: $D(\text{and2})+D(\text{or2})+D(\text{and3})$
 - I2: $D(\text{and4})+D(\text{or2})$
- $D(\text{and2})=22\text{ps}$, $D(\text{and3})=27\text{ps}$, $D(\text{and4})=33\text{ps}$
 - $D(I2)=(33+D(\text{or2})) < D(I1)=(22+27+D(\text{or2}))$
- $D(\text{and2})=22\text{ps}$, $D(\text{and3})=27\text{ps}$, $D(\text{and4})=55\text{ps}$
 - $D(I2)=(55+D(\text{or2})) > D(I1)=(22+27+D(\text{or2}))$

Penn ESE534 Spring2010 -- DeHon

42

Delay and Area Optimum Differ

- I1: $((a*b) + (c*d))*e*f$
- I2: $((a*b*e*f)+(c*d*e*f))$
- $D(\text{and}2)=22\text{ps}$, $D(\text{and}3)=27\text{ps}$, $D(\text{and}4)=33\text{ps}$
 - $D(I2)<D(I1)$
- gate size proportional to number of inputs:
 - $A(I1)<A(I2)$
- **Induced Tradeoff** -- cannot always *simultaneously* minimize area and delay cost

Penn ESE534 Spring2010 -- DeHon

43

Does delay in Gates make Sense?

- Consider a balanced tree of logic gates of depth (tree height) n .
- Does this have delay n ?
 - (unit delay gates)
- How big is it? (unit gate area)
- How long a side?
- Minimum wire length from input to output?

Penn ESE534 Spring2010 -- DeHon

44

Delay in Gates make Sense?

- (continuing example)
- How big is it? (unit gate area) 2^n
- How long a side? $\text{Sqrt}(2^n) = 2^{(n/2)}$
- Minimum wire length from input to output?
 - $2*2^{(n/2)}$
- Delay per unit length? (speed of light limit)
 - $\text{Delay} \propto 2^{(n/2)}$

Penn ESE534 Spring2010 -- DeHon

45

It's not all about costs...

- ...or maybe it is, just not always about a single, linear cost.
- Must manage complexity
 - Cost of developing/verifying design
 - Size of design can accomplish in fixed time
 - (limited brainpower)
- **Today:** human brainpower is most often the bottleneck resource limiting what we can build.

Penn ESE534 Spring2010 -- DeHon

46

Admin: Reminder

- Slides on web (morning before class)
 - Post-class may updated if feedback/class indicates something unclear
- Reading: Monday's on Blackboard
- Assignment 1 Due Monday
 - Beginning of class
 - **Note deferring** A.3/C.2 to HW2
- Feedback sheets
 - Office hour preferences / constraints

Penn ESE534 Spring2010 -- DeHon

47

Big Ideas [MSB Ideas]

- Can implement any Boolean function in gates
 - Small set of gates are **universal**, allowing us to implement any Boolean function

Penn ESE534 Spring2010 -- DeHon

48

Big Ideas [MSB-1 Ideas]

- Canonical representation for combinational logic
- Transformation
 - don't have to implement the input literally
 - only have to achieve same semantics
 - trivial example: logic minimization
- Minimum depends on cost model
- Often tradeoff between costs (area-delay)

Penn ESE534 Spring2010 -- DeHon

49


Post Lecture

- **Fanout:** output of gate drives inputs of more than one gate
- **Reconvergent Fanout:** multiple of the gates consuming one gates output contribute toward an output

Penn ESE534 Spring2010 -- DeHon

50


Reconvergent Fanout

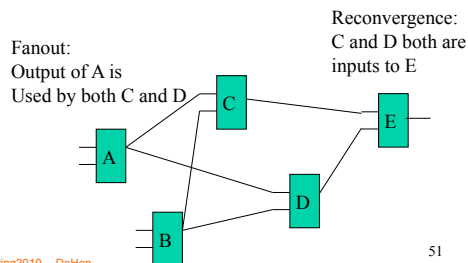

Penn ESE534 Spring2010 -- DeHon

51

Non-Reconvergent Fanout

 

Penn ESE534 Spring2010 -- DeHon

52

Post Lecture: NP-Hard

- NP-Hard
 - http://www.claymath.org/millennium/P_vs_NP/
 - Essay targeted at non-expert: <http://vlsicad.eecs.umich.edu/BK/Slots/cache/www.cs.chalmers.se/~een/PeqNP.ps>

Penn ESE534 Spring2010 -- DeHon

53