

ESE534: Computer Organization

Day 3: January 25, 2010
Arithmetic

Work preclass exercise



Penn ESE534 Spring2010 -- DeHon

Last Time

- Boolean logic \Rightarrow computing **any** finite function
- Saw gates...and a few properties of logic

Penn ESE534 Spring2010 -- DeHon

2

Today

- Addition
 - organization
 - design space
 - parallel prefix

Penn ESE534 Spring2010 -- DeHon

3

Why?

- Start getting a handle on
 - Complexity
 - Area and time
 - Area-time tradeoffs
 - Parallelism
 - Regularity
- Arithmetic underlies much computation
 - grounds out complexity

Penn ESE534 Spring2010 -- DeHon


4

Preclass

Penn ESE534 Spring2010 -- DeHon

5

Circuit 1

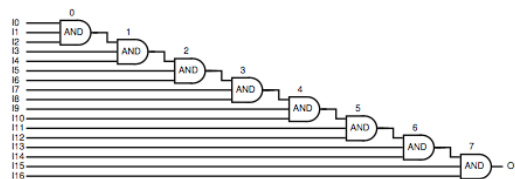


- Can the delay be reduced?
- How?
- To what?

Penn ESE534 Spring2010 -- DeHon

6


Tree Reduce AND

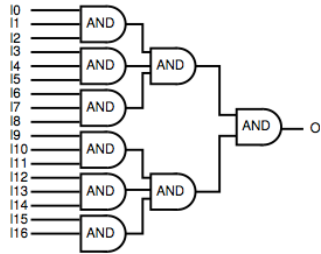

Penn ESE534 Spring2010 -- DeHon

7

Circuit 2

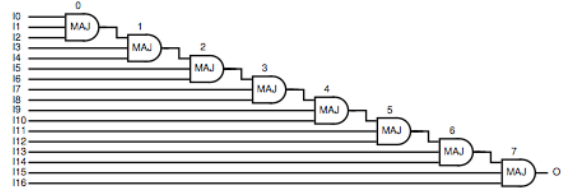


- Can the delay be reduced?

Penn ESE534 Spring2010 -- DeHon

8

Circuit 3

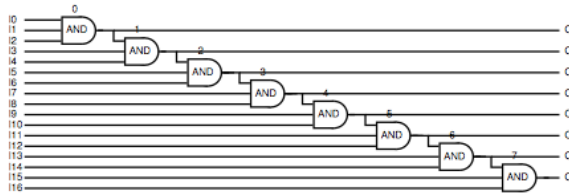


- Can the delay be reduced?

Penn ESE534 Spring2010 -- DeHon

9

Brute Force Multi-Output AND

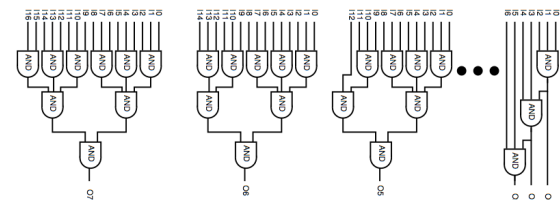


- How big?
- ~38 here

Penn ESE534 Spring2010 -- DeHon ... in general about $N^2/2$

10

Brute Force Multi-Output AND

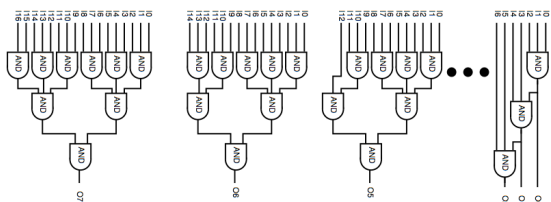


- Can we do better?

Penn ESE534 Spring2010 -- DeHon

11

Circuit 4

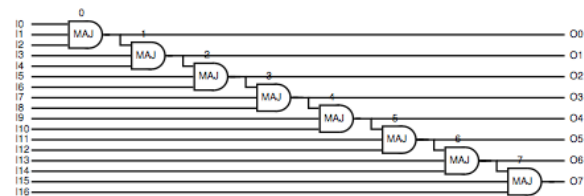

- Can the delay be reduced?

Penn ESE534 Spring2010 -- DeHon

12

Addition

Example: Bit Level Addition

- Addition
 - Base 2 example

C: 11011010000
A: 01101101010
B: 01100101100
S: 11010010110


Addition Base 2

- $A = a_{n-1} * 2^{(n-1)} + a_{n-2} * 2^{(n-2)} + \dots + a_1 * 2^1 + a_0 * 2^0$
 $= \sum (a_i * 2^i)$
- $S = A + B$
- What is the function for s_i ... carry $_i$?
- $s_i = \text{carry}_i \text{ xor } a_i \text{ xor } b_i$
- $\text{carry}_i = (a_{i-1} + b_{i-1} + \text{carry}_{i-1}) \geq 2$
 $= a_{i-1} * b_{i-1} + a_{i-1} * \text{carry}_{i-1} + b_{i-1} * \text{carry}_{i-1}$
 $= \text{MAJ}(a_{i-1}, b_{i-1}, \text{carry}_{i-1})$


Ripple Carry Addition

- Shown operation of each bit
- Often convenient to define logic for each bit, then assemble:

– bit slice

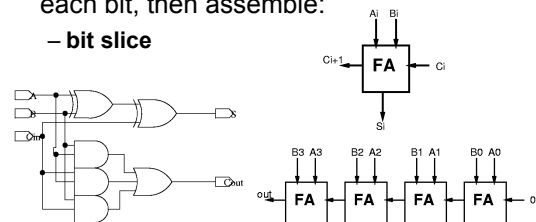

Ripple Carry Analysis

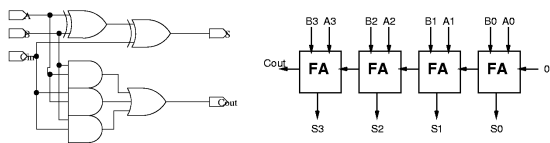


What is area and delay for N-bit RA adder?
 [unit delay gates]

- Area: $O(N)$ [6n]
- Delay: $O(N)$ [2n]


Can we do better?

- Lower delay?

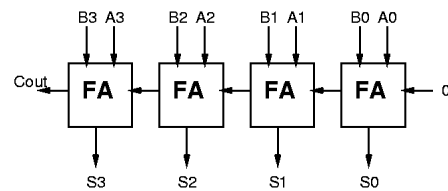

Important Observation

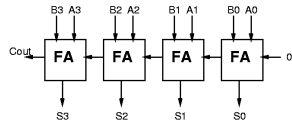- Do we have to wait for the carry to show up to begin doing useful work?
 - We do have to know the carry to get the right answer.
 - How many values can the carry take on?




Penn ESE534 Spring2010 -- DeH

19

Idea

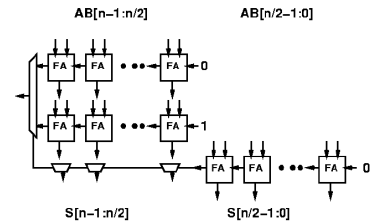
- Compute both possible values and select correct result when we know the answer



Penn ESE534 Spring2010 -- Di

Preliminary Analysis

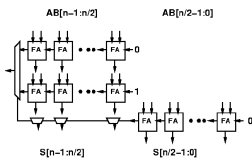- Delay(RA) -- Delay Ripple Adder
- Delay(RA(n)) = $k \cdot n$ [k=2 this example]
- Delay(RA(n)) = $2 \cdot (k \cdot n/2) = 2 \cdot \text{DRA}(n/2)$
- Delay(P2A) -- Delay Predictive Adder
- Delay(P2A) = $\text{DRA}(n/2) + D(\text{mux}2)$
- ...almost half the delay!



Penn ESE534 Spring2010 -- DeHon


Recurse

- If something works once, do it again.
- Use the predictive adder to implement the first half of the addition

Penn ESE534 Spring2010 -- DeHon

22

Recurse

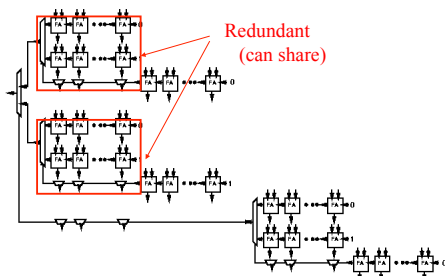

N/4

Penn ESE534 Spring2010 -- DeHon

23

Recurse

- If something works once, do it again.
- Use the predictive adder to implement the first half of the addition
- Delay(P4A(n)) = $\text{Delay}(\text{RA}(n/4)) + D(\text{mux}2) + D(\text{mux}2)$
- Delay(P4A(n)) = $\text{Delay}(\text{RA}(n/4)) + 2 \cdot D(\text{mux}2)$

Penn ESE534 Spring2010 -- DeHon

24

Recurse

- By now we realize we've been using the wrong recursion
 - should be using the Predictive Adder in the recursion
- $\text{Delay}(\text{PA}(n)) = \text{Delay}(\text{PA}(n/2)) + D(\text{mux}2)$
- Every time cut in half...?
- How many times cut in half?
- $\text{Delay}(\text{PA}(n)) = \log_2(n) * D(\text{mux}2) + C$
 - $C = \text{Delay}(\text{PA}(1))$
 - if use FA for PA(1), then $C=2$

Penn ESE534 Spring2010 -- DeHon

25

Another Way


(Parallel Prefix)

Penn ESE534 Spring2010 -- DeHon

26

CLA

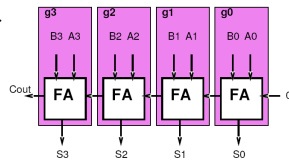- Think about each adder bit as a computing a function on the carry in
 - $C[i] = g(c[i-1])$
 - Particular function f will depend on $a[i], b[i]$
 - $g = f(a, b)$



Penn ESE534 Spring2010 -- DeHon

27


Maybe better to show this as a specialization:

$g(c) = \text{carry}(a=0, b=0, c)$
 $= \text{carry}(a=1, b=0, c)$
 $= \text{carry}(a=0, b=1, c)$
 $= \text{carry}(a=1, b=1, c)$

Functions

- What functions can $g(c[i-1])$ be?

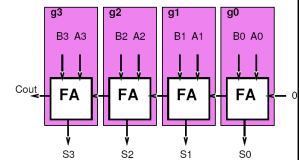- $g(x) = 1$
 - $a[i] = b[i] = 1$
- $g(x) = x$
 - $a[i] \text{ xor } b[i] = 1$
- $g(x) = 0$
 - $a[i] = b[i] = 0$



Penn ESE534 Spring2010 -- DeHon

28

Functions

- What functions can $g(c[i-1])$ be?

- $g(x) = 1$ **Generate**
 - $a[i] = b[i] = 1$
- $g(x) = x$ **Propagate**
 - $a[i] \text{ xor } b[i] = 1$
- $g(x) = 0$ **Squash**
 - $a[i] = b[i] = 0$

Penn ESE534 Spring2010 -- DeHon


29

Combining

- Want to combine functions
 - Compute $c[i] = g_i(g_{i-1}(c[i-2]))$
 - Compute compose of two functions

- What functions will the compose of two of these functions be?

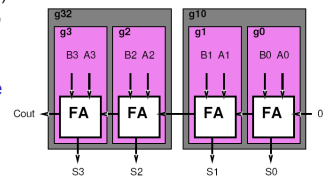- Same as before
 - Propagate, generate, squash



Penn ESE534 Spring2010 -- DeHon

30

Compose Rules (LSB MSB)

- GG
- GP
- GS
- PG
- PP
- PS
- SG
- SP
- SS


[work on board]

Compose Rules (LSB MSB)


- GG = G
- GP = G
- GS = S
- PG = G
- PP = P
- PS = S
- SG = G
- SP = S
- SS = S

Combining

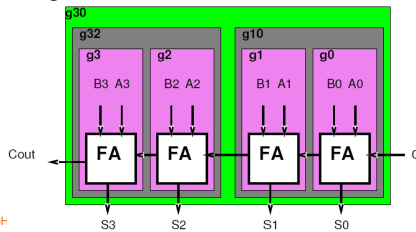- Do it again...
- Combine $g[i-3, i-2]$ and $g[i-1, i]$
- What do we get?




Reduce Tree

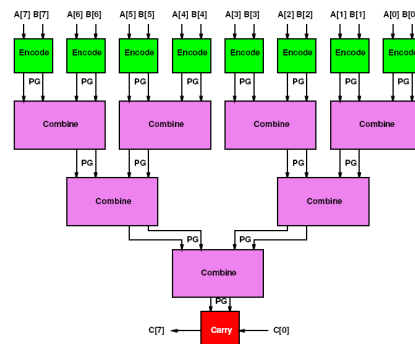


Reduce Tree

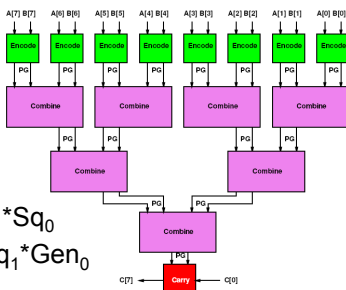- $Sq = A^*/B$
- $Gen = A*B$
- $Sq_{out} = Sq_1 + Gen_1 * Sq_0$
- $Gen_{out} = Gen_1 + Sq_1 * Gen_0$



Reduce Tree

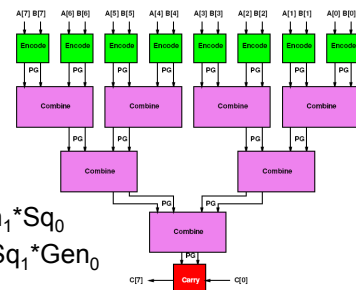- $Sq = A^*/B$
- $Gen = A*B$
- $Sq_{out} = Sq_1 + Gen_1 * Sq_0$
- $Gen_{out} = Gen_1 + Sq_1 * Gen_0$
- Delay and Area?



Reduce Tree


- $Sq = A * B$
- $Gen = A * B$
- $Sq_{out} = Sq_1 + /Gen_1 * Sq_0$
- $Gen_{out} = Gen_1 + /Sq_1 * Gen_0$
- $A(Encode) = 2$
- $D(Encode) = 1$
- $A(Combine) = 4$
- $D(Combine) = 2$
- $A(Carry) = 2$
- $D(Carry) = 1$

Penn ESE534 Spring2010 -- DeHon

37

Reduce Tree: Delay?

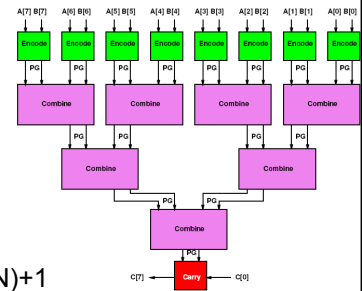- $D(Encode) = 1$
- $D(Combine) = 2$
- $D(Carry) = 1$




$$\text{Delay} = 1 + 2\log_2(N) + 1$$

Penn ESE534 Spring2010 -- DeHon

38

Reduce Tree: Area?

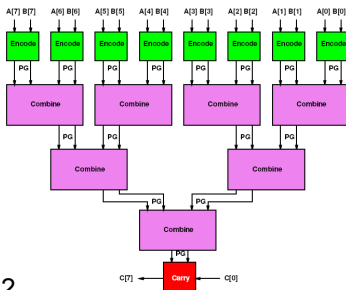- $A(Encode) = 2$
- $A(Combine) = 4$
- $A(Carry) = 2$




$$\text{Area} = 2N + 4(N-1) + 2$$

Penn ESE534 Spring2010 -- DeHon

39

Reduce Tree: Area & Delay

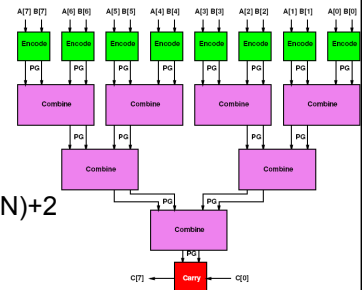- $\text{Area}(N) = 6N - 2$
- $\text{Delay}(N) = 2\log_2(N) + 2$




Penn ESE534 Spring2010 -- DeHon

40

Intermediates

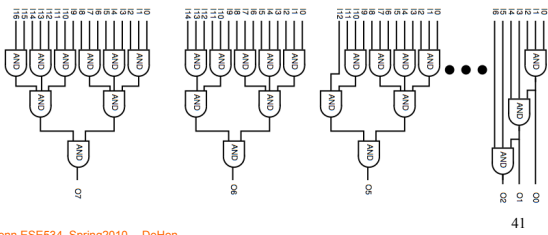
- Can we compute intermediates efficiently?



Penn ESE534 Spring2010 -- DeHon

41


Prefix Tree

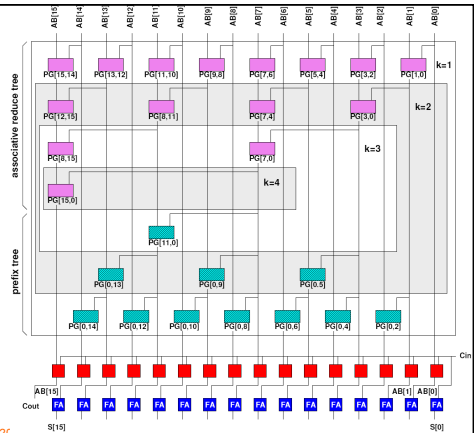

Penn ESE534 Spring2010 -- DeHon

Prefix Tree


- Share terms

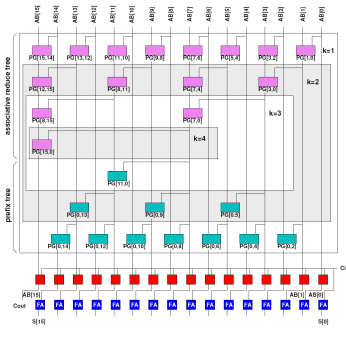

Penn ESE534 Spring2010 -- DeHon

Intermediates

- Share common terms

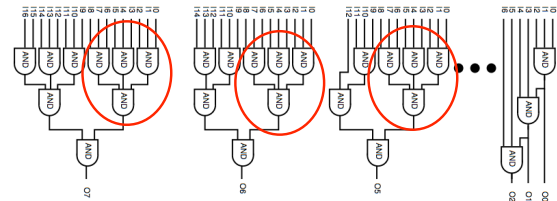


Penn ESE534 Spring2010 -- DeHon

44


Prefix Tree

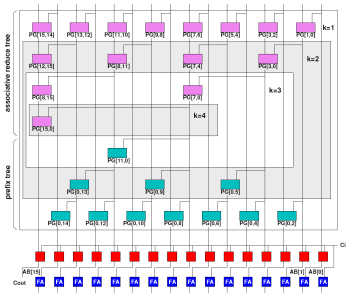- Share terms
- Reduce computes spans
 - 0:3, 4:5
- Reverse tree
 - Combine spans for missing 0:i (i<N)
 - E.g. 0:3+4:5 → 0:5
- Same size as reduce tree



Penn ESE534 Spring2010 -- DeHon


Prefix Tree

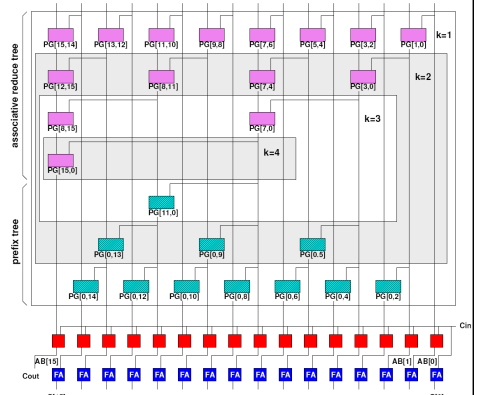

Penn ESE534 Spring2010 -- DeHon

Parallel Prefix Area and Delay?

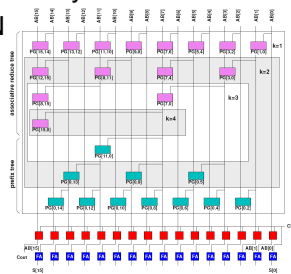- Roughly twice the area/delay
- Area = $2N + 4N + 4N + 2N = 10N$
- Delay = $4 \log_2(N) + 2$



Penn ESE534 Spring2010 -- DeHon

Parallel Prefix

- Important **Pattern**
- Applicable any time operation is *associative*
 - Or can be made assoc. as in MAJ case
- Examples of associative functions?
 - Non-associative?
- Function Composition is always associative

Penn ESE534 Spring2010 -- DeHon

48

Note: Constants Matter

- Watch the constants
- Asymptotically this Carry-Lookahead Adder (CLA) is great
- For small adders can be smaller with
 - fast ripple carry
 - larger combining than 2-ary tree
 - mix of techniques
- ...will depend on the technology primitives and cost functions

Penn ESE534 Spring2010 -- DeHon

49

Two's Complement

- positive numbers in binary
- negative numbers
 - subtract 1 and invert
 - (or invert and add 1)

Penn ESE534 Spring2010 -- DeHon

50

Two's Complement

- 2 = 010
- 1 = 001
- 0 = 000
- -1 = 111
- -2 = 110

Penn ESE534 Spring2010 -- DeHon

51

Addition of Negative Numbers?

- ...just works

A: 111	A: 110	A: 111	A: 111
B: 001	B: 001	B: 010	B: 110
S: 000	S: 111	S: 001	S: 101

Penn ESE534 Spring2010 -- DeHon

52

Subtraction


- Negate the subtracted input and use adder
 - which is:
 - invert input and add 1
 - works for both positive and negative input
- $-001 \rightarrow 110 + 1 = 111$
 $-111 \rightarrow 000 + 1 = 001$
 $-000 \rightarrow 111 + 1 = 000$
 $-010 \rightarrow 101 + 1 = 110$
 $-110 \rightarrow 001 + 1 = 010$

Penn ESE534 Spring2010 -- DeHon

53

Subtraction (add/sub)

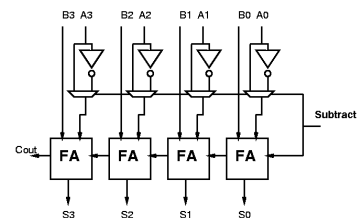- **Note:** you can use the “unused” carry input at the LSB to perform the “add 1”



Penn ESE534 Spring2

54

Overflow?

A: 111 A: 110 A: 111 A: 111
B: 001 B: 001 B: 010 B: 110
S: 000 S: 111 S: 001 S: 101

A: 001 A: 011 A: 111
B: 001 B: 001 B: 100
S: 010 S: 100 S: 011

- $\text{Overflow} = (A.s == B.s) * (A.s != S.s)$

Admin

- Office Hours: W2pm

Big Ideas [MSB Ideas]

- Can build arithmetic out of logic

Big Ideas [MSB-1 Ideas]

- Associativity
- Parallel Prefix
- Can perform addition
 - in log time
 - with linear area