

ESE534: Computer Organization

Day 4: January 27, 2010
Sequential Logic
(FSMs, Pipelining, FSMD)



Previously

- Boolean Logic
- Gates
- Arithmetic
- Complexity of computations
 - E.g. area and delay for addition

Today



- Sequential Logic
 - Add registers, state
 - Finite-State Machines (FSM)
 - Register Transfer Level (RTL) logic
 - Datapath Reuse
 - Pipelining
 - Latency and Throughput
 - Finite-State Machines with Datapaths (FSMD)

Preclass

- Can we solve the problem entirely using Boolean logic functions?

Latches, Registers

  - New element is a state element.
- Canonical instance is a register:
 - remembers the last value it was given until told to change
 - typically signaled by clock




Why Registers?

Reuse

- In general, we want to reuse our components in time

- not disposable logic

 - How do we do allow guarantee disciplined reuse?



Penn ESE534 Spring2010 -- DeHon

7

To Reuse Logic...


- Make sure all logic completed evaluation
 - Outputs of gates are valid
 - Meaningful to look at them
 - Gates are “finished” with work and ready to be used again
- Make sure consumers get value
 - Before being overwritten by new calculation (new inputs)

Penn ESE534 Spring2010 -- DeHon

8

Synchronous Logic Model

 - Data starts
 - Inputs to circuit
 - Registers
- Perform combinational (boolean) logic
- Outputs of logic
 - Exit circuit
 - Clocked into registers
- Given long enough clock
 - Think about registers getting values updated by logic on each clock cycle



Penn ESE534 Spring2010 -- DeHon

9

Issues of Timing...

- ...many issues in detailed implementation
 - glitches and hazards in logic
 - timing discipline in clocking
 - ...
- We're going to (mostly) work above that level for the most part this term.
 - Will talk about the delay of logic between registers
- Watch for these details in ESE370/570

Penn ESE534 Spring2010 -- DeHon

10

Preclass

- How do we build an adder for arbitrary input width?

Penn ESE534 Spring2010 -- DeHon

11

Preclass

- What did the addition of state register(s) do for us?

Penn ESE534 Spring2010 -- DeHon

12

Added Power


- Process *unbounded* input with finite logic
- State is a **finite** (bounded) representation of what's happened before
 - finite amount of stuff can remember to synopsize the past
- State allows behavior to depend on past (on context)

Penn ESE534 Spring2010 -- DeHon

13

Finite-State Machine (FSM) (Finite Automata)

 
- Logic core
- Plus registers to hold state



Penn ESE534 Spring2010 -- DeHon

FSM Model

 
- FSM – a model of computations
- More powerful than Boolean logic functions
- Both
 - Theoretically
 - practically



Penn ESE534 Spring2010 -- DeHon

Formal FSM Specification (Abstract from implementation)

 - An FSM is a sextuple $M = \{K, \Sigma, \delta, s, F, \Sigma_o\}$
 - K is finite set of states
 - Σ is a finite alphabet for inputs
 - $s \in K$ is the start state
 - $F \subseteq K$ is the set of final states
 - Σ_o is a finite set of output symbols
 - δ is a transition function from $K \times \Sigma$ to $K \times \Sigma_o$



Penn ESE534 Spring2010 -- DeHon

16

Finite State Machine

- Less formally:
 - Behavior depends not just on input
 - (as was the case for combinational logic)
 - Also depends on state
 - Can be completely different behavior in each state
 - Logic/output now depends on both
 - state and input

Penn ESE534 Spring2010 -- DeHon

17

Specifying an FSM


- Logic becomes:
 - if (state=s1)
 - boolean logic for state 1
 - (including logic for calculate next state)
 - else if (state=s2)
 - boolean logic for state2
 - ...
 - if (state=sn)
 - boolean logic for state n

Penn ESE534 Spring2010 -- DeHon

18

FSM Specification

 - St1: goto St2
 - St2:
 - if ($! = 0$) goto St3
 - else goto St4
 - St3:
 - output $o0=1$
 - goto St1
 - St4:
 - output $o1=1$
 - goto St2
- Could be:
 - behavioral language
 - computer language
 - state-transition graph
 - extract from gates + registers



Penn ESE534 Spring2010 -- DeHon

State Encoding

- States not (necessarily) externally visible
- We have *freedom* in how to encode them
 - assign bits to states
- Usually want to exploit freedom to minimize implementation costs
 - area, delay, energy
- (there are algorithms to attack – ESE535)

Penn ESE534 Spring2010 -- DeHon

20

FSM Equivalence

- Harder than Boolean logic
- Doesn't have unique canonical form
- Consider:
 - state encoding not change behavior
 - two "equivalent" FSMs may not even have the same number of states
 - can deal with **infinite** (unbounded) input
 - ...so cannot enumerate output in all cases
 - No direct correspondence of a truth table

Penn ESE534 Spring2010 -- DeHon

21

FSM Equivalence

- What matters is external observability
 - FSM outputs same signals in response to every possible input sequence
- Possible?
 - Finite state suggests there is a finite amount of checking required to verify behavior

Penn ESE534 Spring2010 -- DeHon

22

FSM Equivalence Flavor


- Given two FSMs A and B
 - consider the composite FSM AB
 - Inputs wired together
 - Outputs separate
- Ask:
 - is it possible to get into a composite state in which A and B output different symbols?
- There is a literature on this

Penn ESE534 Spring2010 -- DeHon

23

Systematic FSM Design

 - Start with specification
- Can compute boolean logic for each state
 - If conversion...
 - including next state translation
 - Keep state symbolic (s_1, s_2, \dots)
- Assign state encodings
- Then have combinational logic
 - has current state as part of inputs
 - produces next state as part of outputs
- Design comb. logic and add state registers



Penn ESE534 Spring2010 -- DeHon

24

Arbitrary Adder

- Work through design as FSM if necessary


RTL

- Register Transfer Level description
- Registers + Boolean logic
- Most likely: what you've written in Verilog, VHDL


Datapath Reuse

Reuse: "Waiting" Discipline

 - Use registers and timing for orderly progression of data




Example: 4b Ripple Adder

 

- Recall 2 gates/FA
- How fast can we clock this?
- Min Clock Cycle: 8 gates A, B to S3


Can we do better?

- Clock faster, reuse elements sooner?

 

Stagger Inputs

 
- Correct if expecting A,B[3:2] to be staggered one cycle behind A,B[1:0]
- ...and succeeding stage expects S[3:2] staggered from S[1:0]



Penn ESE534 Spring2010 -- DeHon

Align Data / Balance Paths

 Good discipline to line up pipe stages in diagrams.




Penn ESE534 Spring2010 -- DeHon.

Speed

How fast can we clock this?


What is the delay from A,B to S3?

 

Penn ESE534 Spring2010 -- DeHon.

Pipelining and Timing

 - Once introduce pipelining
 - Clock cycle = rate of reuse
 - Is not the same as the delay to complete a computation




Penn ESE534 Spring2010 -- DeHon

34

Pipelining and Timing

 - Throughput
 - How many results can the circuit produce per unit time
 - If can produce one result per cycle,
 - Reciprocal of clock period
- Throughput this design?




Penn ESE534 Spring2010 -- DeHon

35

Pipelining and Timing

 
- Latency
 - How long does it take to produce one result
 - Product of clock cycle and number of clocks between input and output
- Latency this design?



Penn ESE534 Spring2010 -- DeHon

36

Example: 4b RA pipe 2

 

- Recall 2 gates/FA
- Latency and Throughput:
- Latency: 8 gates to S3
- Throughput: 1 result / 4 gate delays max

Penn ESE534 Spring2010 -- DeHon

37

Deeper?


- Can we do it again?
- What's our limit?
- Why would we stop?

Penn ESE534 Spring2010 -- DeHon

38

More Reuse

 
- Saw could pipeline and reuse FA more frequently
- Suggests we're **wasting** the FA part of the time in non-pipelined
 - What is FA3 doing while FA0 is computing?



Penn ESE534 Spring2010 -- DeHon

More Reuse (cont.)

 - If we're willing to take 4 gate-delay units, do we need 4 FAs?




Penn ESE534 Spring2010 -- DeHon

40

Ripple Add (pipe view)

Can pipeline to FA.

What if don't need the throughput?

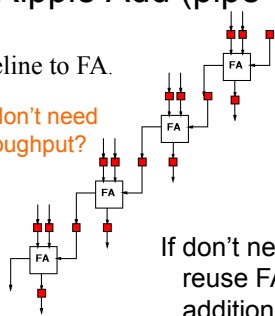


If don't need throughput, reuse FA on **SAME** addition.

Penn ESE534 Spring2010 -- DeHon

41

Bit Serial Addition

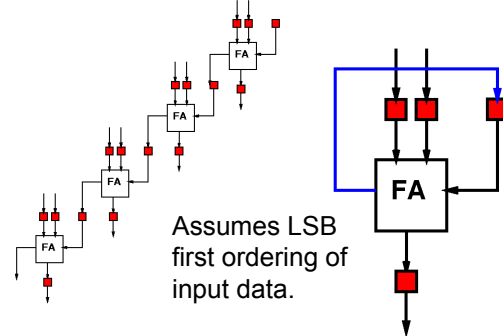


Assumes LSB first ordering of input data.

Penn ESE534 Spring2010 -- DeHon

42

Bit Serial Addition: Pipelining

 - Latency and throughput?
 - Latency: 8 gate delays
 - 10 for 5th output bit
- Throughput: 1 result / 10 gate delays
- Registers do have time overhead
 - setup, hold time, clock jitter



Penn ESE534 Spring2010 -- DeHon

43

Multiplication

- Can be defined in terms of addition
- Ask you to play with implementations and tradeoffs in homework 2
 - Out today
 - Pickup from syllabus page on web

Penn ESE534 Spring2010 -- DeHon

44

Design Space for Computation

Penn ESE534 Spring2010 -- DeHon

45

Compute Function

- Compute:


$$y = Ax^2 + Bx + C$$
- Assume
 - $D(\text{Mpy}) > D(\text{Add})$
 - E.g. $D(\text{Mpy})=24, D(\text{Add})=8$
 - $A(\text{Mpy}) > A(\text{Add})$
 - E.g. $A(\text{Mpy})=64, A(\text{Add})=8$

Penn ESE534 Spring2010 -- DeHon

46

Spatial Quadratic

Latency?
Throughput?
Area?

 


- $D(\text{Quad}) = 2 \cdot D(\text{Mpy}) + D(\text{Add}) = 56$
- Throughput $1 / (2 \cdot D(\text{Mpy}) + D(\text{Add})) = 1/56$
- $A(\text{Quad}) = 3 \cdot A(\text{Mpy}) + 2 \cdot A(\text{Add}) = 208$ ⁴⁷

Penn ESE534 Spring2010 -- DeHon

47

Pipelined Spatial Quadratic

Latency?
Throughput?
Area?

 

- $D(\text{Quad}) = 3 \cdot D(\text{Mpy}) = 72$
- Throughput $1 / D(\text{Mpy}) = 1/24$
- $A(\text{Quad}) = 3 \cdot A(\text{Mpy}) + 2 \cdot A(\text{Add}) + 6A(\text{Reg}) = 232$ ⁴⁸

Penn ESE534 Spring2010 -- DeHon

48

Quadratic with Single Multiplier and Adder?


- We've seen reuse to perform the **same** operation
 - pipelining
 - bit-serial, homogeneous datapath
- We can also reuse a resource in time to perform a **different** role.

Penn ESE534 Spring2010 -- DeHon

49

Repeated Operations

 
- What operations occur multiple times in this datapath?
 - x^2x , $A^*(x^2x)$, B^*x
 - $(Bx)+c$, $(A^*x^2x)+(Bx+c)$



Penn ESE534 Spring2010 -- DeHon

Quadratic Datapath

 - Start with one of each operation
- (alternatives where build multiply from adds...e.g. homework)




Penn ESE534 Spring2010 -- DeHon

51

Quadratic Datapath

 - Multiplier serves multiple roles
 - x^2x
 - $A^*(x^2x)$
 - B^*x
- Will need to be able to steer data (switch interconnections)




Penn ESE534 Spring2010 -- DeHon

52

Quadratic Datapath

 
- Multiplier serves multiple roles
 - x^2x
 - $A^*(x^2x)$
 - B^*x
- x, x^2x, x
- x, A, B



Penn ESE534 Spring2010 -- DeHon

Quadratic Datapath

 
- Multiplier serves multiple roles
 - x^2x
 - $A^*(x^2x)$
 - B^*x
- x, x^2x
- x, A, B



Penn ESE534 Spring2010 -- DeHon


Quadratic Datapath

 - Adder serves multiple roles
 - $(Bx)+c$
 - $(A*x*x)+(Bx+c)$
- one always mpy output
- $C, Bx+C$



Penn ESE534 Spring2010 -- DeHon


Quadratic Datapath

 

Penn ESE534 Spring2010 -- DeHon

Quadratic Datapath

- Add input register for x

 


Penn ESE534 Spring2010 -- DeHon

Quadratic Control

- Now, we just need to control the datapath
- What control?

 - Control:
 - LD x
 - LD $x*x$
 - MA Select
 - MB Select
 - AB Select
 - LD $Bx+C$
 - LD Y



Penn ESE534 Spring2010 -- DeHon


FSMD

- FSMD = FSM + Datapath
- Stylization for building controlled datapaths such as this (a **pattern**)
- Of course, an FSMD is just an FSM
 - it's often easier to think about as a datapath
 - synthesis, place and route tools have been notoriously bad about discovering/ exploiting datapath structure

Penn ESE534 Spring2010 -- DeHon

59

Quadratic FSMD

 

Penn ESE534 Spring2010 --

60

Quadratic FSMD Control


- S0: if (go) LD_X; goto S1
 - else goto S0
- S1: MA_SEL=x, MB_SEL[1:0]=x, LD_x*x
 - goto S2
- S2: MA_SEL=x, MB_SEL[1:0]=B
 - goto S3
- S3: AB_SEL=C, MA_SEL=x*x, MB_SEL=A
 - goto S4
- S4: AB_SEL=Bx+C, LD_Y
 - goto S0

Penn ESE534 Spring2010 -- DeHon

61

Quadratic FSMD Control

 
- S0: if (go) LD_X; goto S1
 - else goto S0
- S1: MA_SEL=x, MB_SEL[1:0]=x, LD_x*x
 - goto S2
- S2: MA_SEL=x, MB_SEL[1:0]=B
 - goto S3
- S3: AB_SEL=C, MA_SEL=x*x, MB_SEL=A
 - goto S4
- S4: AB_SEL=Bx+C, LD_Y
 - goto S0



Penn ESE534 Spring2010 -- DeHon

Quadratic FSM

 - $D(\text{mux3}) = D(\text{mux2}) = 1$
- $A(\text{mux2}) = 2$
- $A(\text{mux3}) = 3$
- $A(\text{QFSM}) \approx 10$
- Latency/Throughput/Area?
- Latency: $5 \cdot (D(\text{MPY}) + D(\text{mux3})) = 125$
- Throughput: $1/\text{Latency} = 1/125$
- Area: $A(\text{Mpy}) + A(\text{Add}) + 5 \cdot A(\text{Reg}) + 2 \cdot A(\text{Mux2}) + A(\text{Mux3}) + A(\text{QFSM}) = 109$



Penn ESE534 Spring2010 -- DeHon

63

Admin: Reminder

- Chrome and Blackboard don't mix
- Next homework due Monday
- Office hours W2pm
 - 30 minutes after class

Penn ESE534 Spring2010 -- DeHon

64

Big Ideas [MSB Ideas]

- Registers allow us to reuse logic
- Can implement any FSM with gates and registers
- Pipelining
 - increases parallelism
 - allows reuse in time (same function)
- Control and Sequencing
 - reuse in time for different functions
- Can tradeoff Area and Time

Penn ESE534 Spring2010 -- DeHon

65

Big Ideas [MSB-1 Ideas]

- RTL specification
- FSMD idiom

Penn ESE534 Spring2010 -- DeHon

66