

# ESE534: Computer Organization

Day 3: January 23, 2012  
Arithmetic

Work preclass exercise



Penn ESE534 Spring2012 -- DeHon

## Last Time

- Boolean logic  $\Rightarrow$  computing **any** finite function
- Saw gates...and a few properties of logic

Penn ESE534 Spring2012 -- DeHon

2

## Today

- Addition
  - organization
  - design space
  - parallel prefix

Penn ESE534 Spring2012 -- DeHon

3

## Why?

- Start getting a handle on
  - Complexity
    - Area and time
    - Area-time tradeoffs
  - Parallelism
  - Regularity
- Arithmetic underlies much computation
  - grounds out complexity

Penn ESE534 Spring2012 -- DeHon


4

## Preclass

Penn ESE534 Spring2012 -- DeHon

5

## Circuit 1

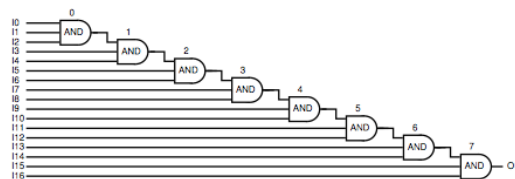


- Can the delay be reduced?
- How?
- To what?

Penn ESE534 Spring2012 -- DeHon

6


### Tree Reduce AND

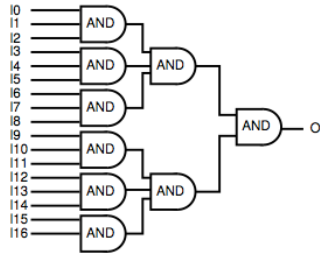

Penn ESE534 Spring2012 -- DeHon

7

### Circuit 2

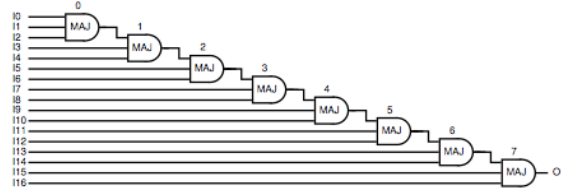


- Can the delay be reduced?

Penn ESE534 Spring2012 -- DeHon

8

### Circuit 3

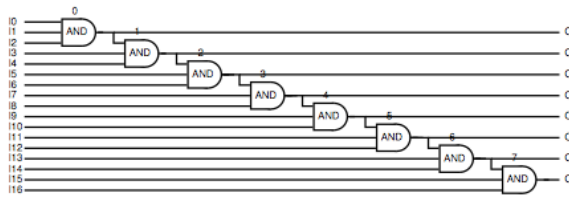


- Can the delay be reduced?

Penn ESE534 Spring2012 -- DeHon

9

### Brute Force Multi-Output AND

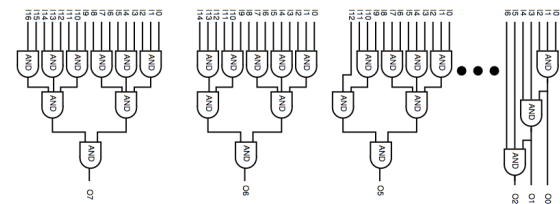


- How big?
- ~38 here

Penn ESE534 Spring2012 -- DeHon ... in general about  $N^2/2$

10

### Brute Force Multi-Output AND

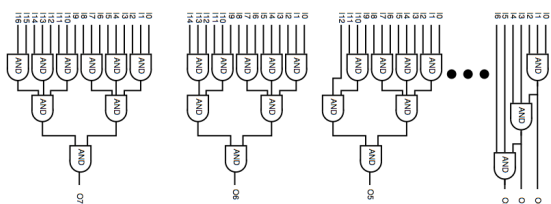


- Can we do better?

Penn ESE534 Spring2012 -- DeHon

11

### Circuit 4

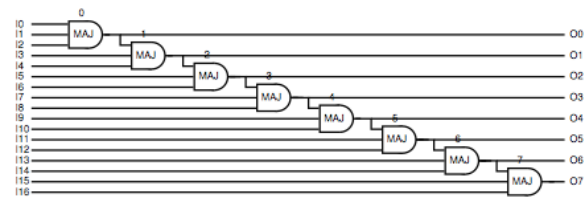

- Can the delay be reduced?

Penn ESE534 Spring2012 -- DeHon

12

## Addition

## Example: Bit Level Addition

- Addition
  - Base 2 example
  - **Work together**


**C: 1101101000**  
**A: 0110110101**  
**B: 0110010110**  
**S: 11010010110**

## Addition Base 2


- $A = a_{n-1} * 2^{(n-1)} + a_{n-2} * 2^{(n-2)} + \dots + a_1 * 2^1 + a_0 * 2^0$   
 $= \sum (a_i * 2^i)$
- $S = A + B$
- **What is the function for  $s_i$  ... carry $_i$ ?**
- $s_i = \text{carry}_i \text{ xor } a_i \text{ xor } b_i$
- $\text{carry}_i = (a_{i-1} + b_{i-1} + \text{carry}_{i-1}) \geq 2$   
 $= a_{i-1} * b_{i-1} + a_{i-1} * \text{carry}_{i-1} + b_{i-1} * \text{carry}_{i-1}$   
 $= \text{MAJ}(a_{i-1}, b_{i-1}, \text{carry}_{i-1})$
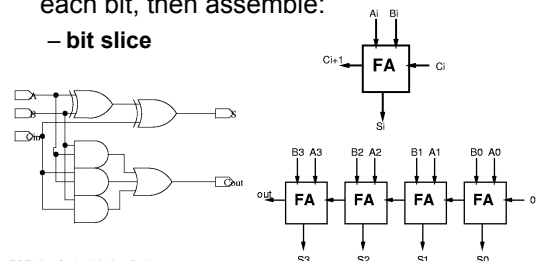
## Ripple Carry Addition

- Shown operation of each bit
- Often convenient to define logic for each bit, then assemble:



## Ripple Carry Analysis

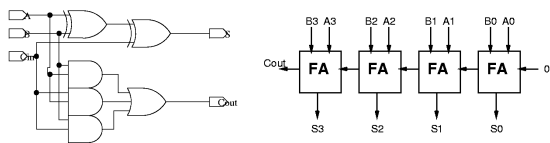


**What is area and delay for N-bit RA adder?**  
 [unit delay gates]

- Area:  $O(N)$  [6n]
- Delay:  $O(N)$  [2n]


## Can we do better?

- **Lower delay?**

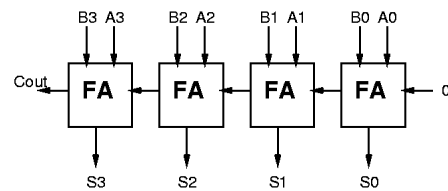
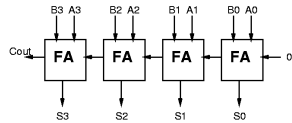
## Important Observation

- Do we have to wait for the carry to show up to begin doing useful work?
  - We do have to know the carry to get the right answer.
  - How many values can the carry take on?




Penn ESE534 Spring2012 -- DeH

19
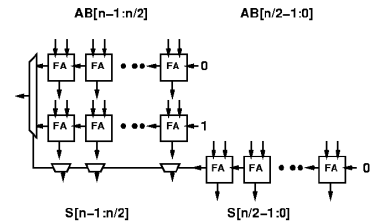
## Idea


- Compute both possible values and select correct result when we know the answer



Penn ESE534 Spring2012 -- Di
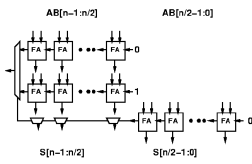
## Preliminary Analysis

- Delay(RA) -- Delay Ripple Adder
- Delay(RA(n)) =  $k*n$  [k=2 this example]
- Delay(RA(n)) =  $2*(k*n/2) = 2*DRA(n/2)$
- Delay(P2A) -- Delay Predictive Adder
- Delay(P2A) =  $DRA(n/2) + D(\text{mux2})$
- ...almost half the delay!



Penn ESE534 Spring2012 -- DeHon


## Recurse

- If something works once, do it again.
- Use the predictive adder to implement the first half of the addition

Penn ESE534 Spring2012 -- DeHon

22


## Recurse

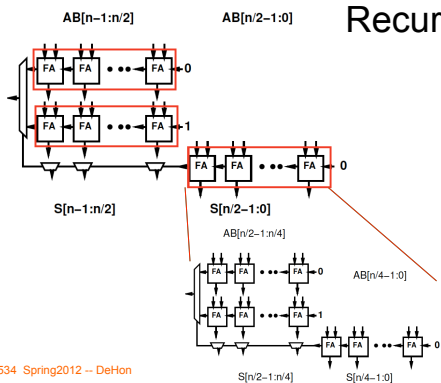

Penn ESE534 Spring2012 -- DeHon

23

## Recurse

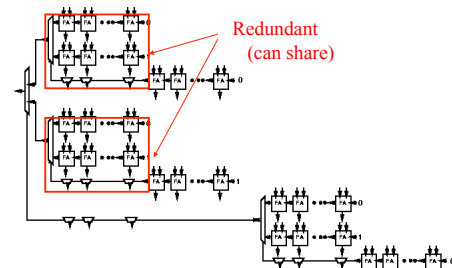

Penn ESE534 Spring2012 -- DeHon

N/4

24

## Recurse

- If something works once, do it again.
- Use the predictive adder to implement the first half of the addition
- $\text{Delay}(P4A(n)) = \text{Delay}(RA(n/4)) + D(\text{mux}2) + D(\text{mux}2)$
- $\text{Delay}(P4A(n)) = \text{Delay}(RA(n/4)) + 2 * D(\text{mux}2)$

Penn ESE534 Spring2012 -- DeHon

25

## Recurse

- By now we realize we've been using the wrong recursion
  - should be using the Predictive Adder in the recursion
- $\text{Delay}(PA(n)) = \text{Delay}(PA(n/2)) + D(\text{mux}2)$
- Every time cut in half...?
- How many times cut in half?
- $\text{Delay}(PA(n)) = \log_2(n) * D(\text{mux}2) + C$ 
  - $C = \text{Delay}(PA(1))$ 
    - if use FA for PA(1), then  $C=2$

Penn ESE534 Spring2012 -- DeHon

26

## Another Way


(Parallel Prefix)

Penn ESE534 Spring2012 -- DeHon

27
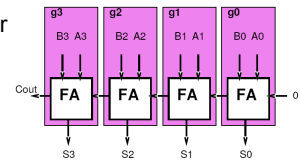
## CLA

- Think about each adder bit as a computing a function on the carry in
  - $C[i] = g(c[i-1])$
  - Particular function  $f$  will depend on  $a[i]$ ,  $b[i]$
  - $g = f(a, b)$




Penn ESE534 Spring2012 -- DeHon

28
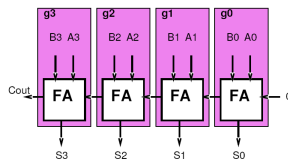
## Functions

- What are the functions  $g(c[i-1])$ ?
  - $g(c) = \text{carry}(a=0, b=0, c)$
  - $g(c) = \text{carry}(a=1, b=0, c)$
  - $g(c) = \text{carry}(a=0, b=1, c)$
  - $g(c) = \text{carry}(a=1, b=1, c)$



Penn ESE534 Spring2012 -- DeHon

29

## Functions


- What are the functions  $g(c[i-1])$ ?
  - $g(x) = 1$  Generate
    - $a[i] = b[i] = 1$
  - $g(x) = x$  Propagate
    - $a[i] \text{ xor } b[i] = 1$
  - $g(x) = 0$  Squash
    - $a[i] = b[i] = 0$

Penn ESE534 Spring2012 -- DeHon

30
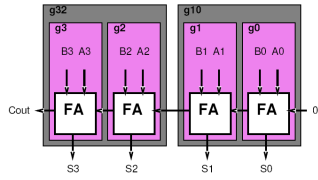
## Combining

- Want to combine functions
  - Compute  $c[i]=g_i(g_{i-1}(c[i-2]))$
  - Compute compose of two functions
- What functions will the compose of two of these functions be?
  - Same as before
    - Propagate, generate, squash



## Compose Rules (LSB MSB)

- GG
- GP
- GS
- PG
- PP
- PS
- SG
- SP
- SS


[work on board]

## Compose Rules (LSB MSB)


- GG = G
- GP = G
- GS = S
- PG = G
- PP = P
- PS = S
- SG = G
- SP = S
- SS = S
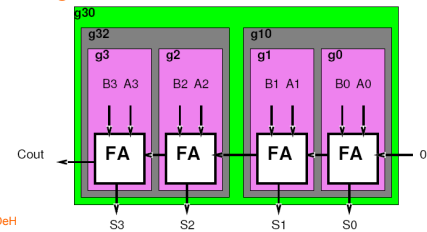
## Combining

- Do it again...
- Combine  $g[i-3, i-2]$  and  $g[i-1, i]$
- What do we get?




## Reduce Tree

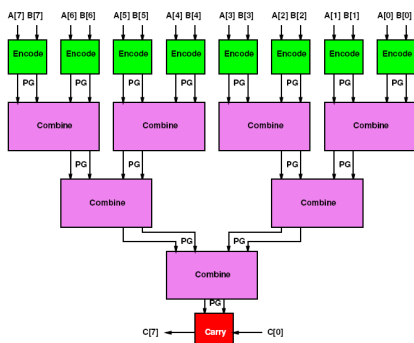

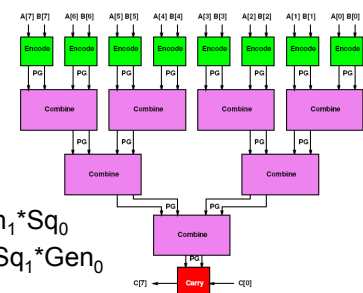
## Reduce Tree

- $Sq = /A*/B$
- $Gen = A*B$
- $Sq_{out} = Sq_1 + /Gen_1 * Sq_0$
- $Gen_{out} = Gen_1 + /Sq_1 * Gen_0$


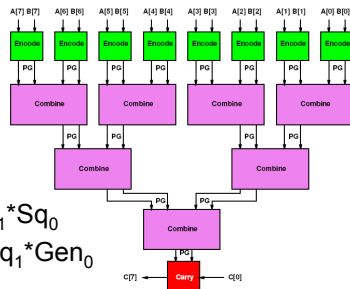
## Reduce Tree

- $Sq = A^*/B$
- $Gen = A^*B$
- $Sq_{out} = Sq_1 + Gen_1 * Sq_0$
- $Gen_{out} = Gen_1 + Sq_1 * Gen_0$
- Delay and Area?



Penn ESE534 Spring2012 -- DeHon

37

## Reduce Tree

- $Sq = A^*/B$
- $Gen = A^*B$
- $Sq_{out} = Sq_1 + Gen_1 * Sq_0$
- $Gen_{out} = Gen_1 + Sq_1 * Gen_0$
- $A(Encode) = 2$
- $D(Encode) = 1$
- $A(Combine) = 4$
- $D(Combine) = 2$
- $A(Carry) = 2$
- $D(Carry) = 1$


Penn ESE534 Spring2012 -- DeHon

38

## Reduce Tree: Delay?

- $D(Encode) = 1$
- $D(Combine) = 2$
- $D(Carry) = 1$

$$Delay = 1 + 2\log_2(N) + 1$$

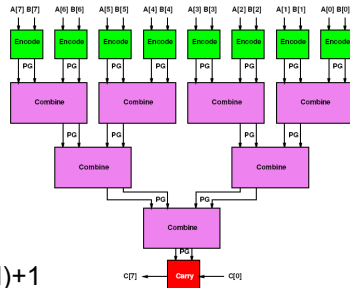


Penn ESE534 Spring2012 -- DeHon

39

## Reduce Tree: Area?

- $A(Encode) = 2$
- $A(Combine) = 4$
- $A(Carry) = 2$

$$Area = 2N + 4(N-1) + 2$$

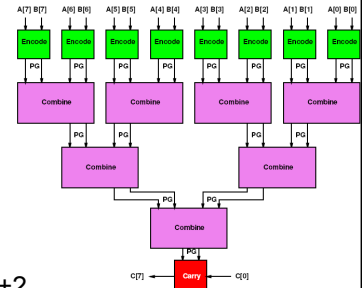


Penn ESE534 Spring2012 -- DeHon

40
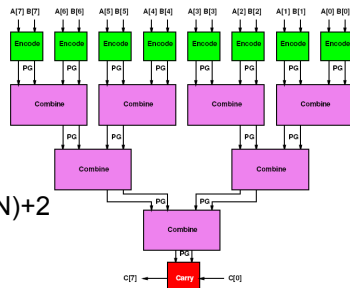
## Reduce Tree: Area & Delay


- $Area(N) = 6N - 2$
- $Delay(N) = 2\log_2(N) + 2$









Penn ESE534 Spring2012 -- DeHon

41







## How Relate?

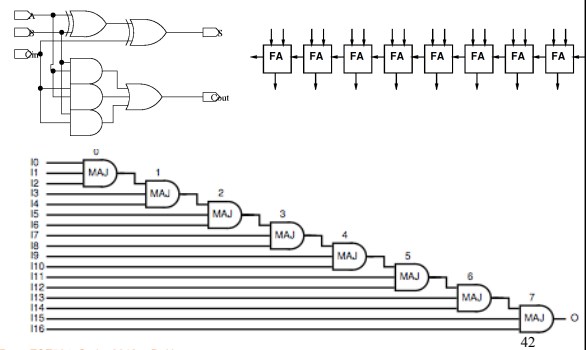

Penn ESE534 Spring2012 -- DeHon

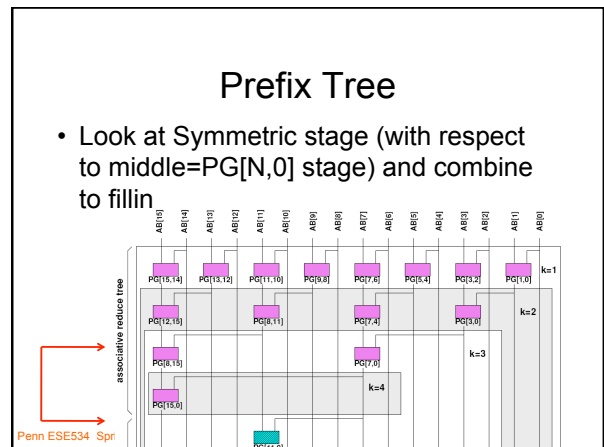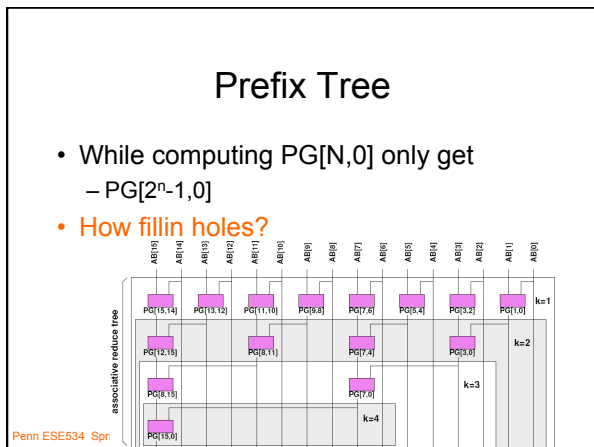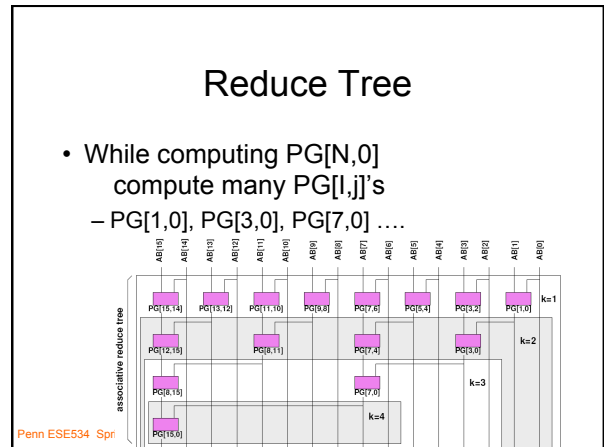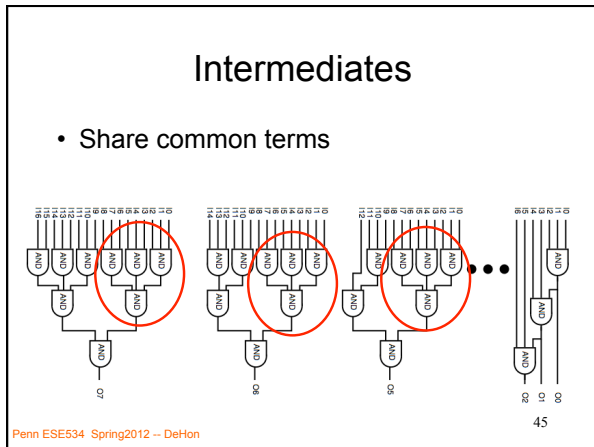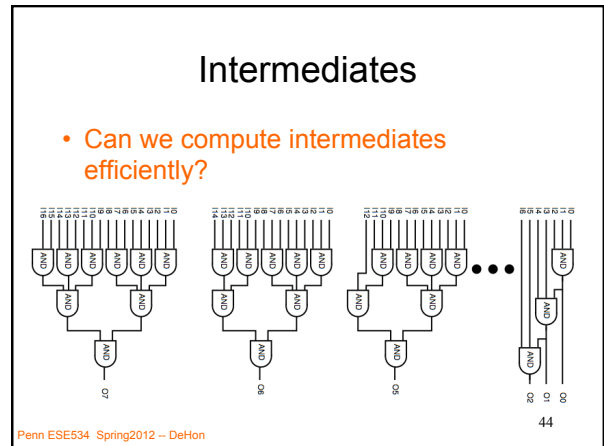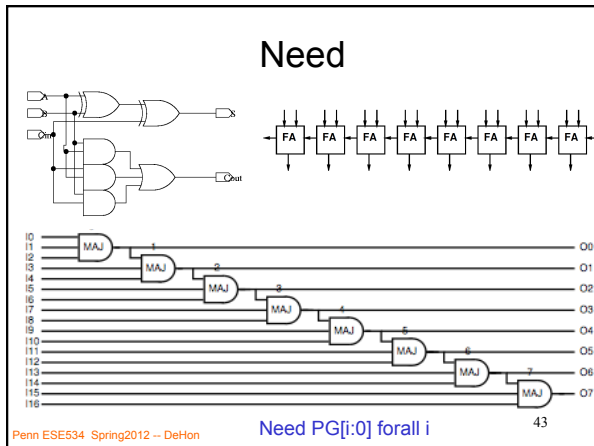



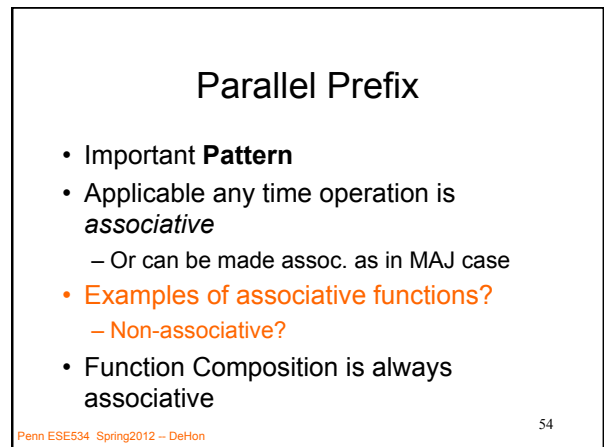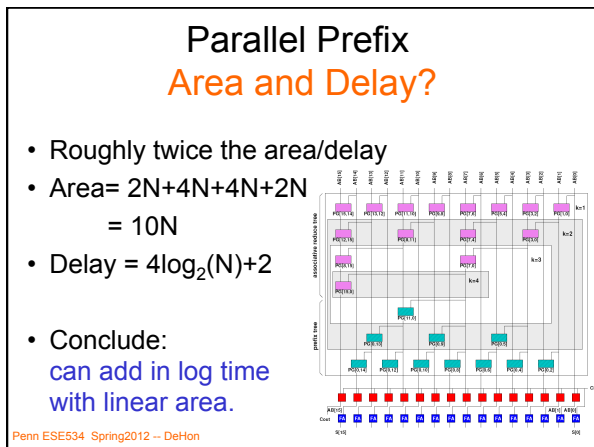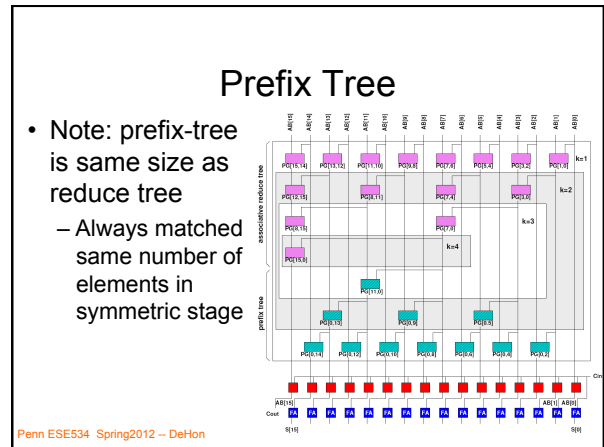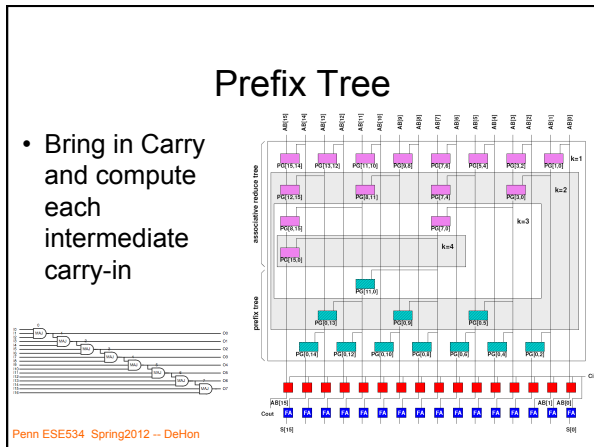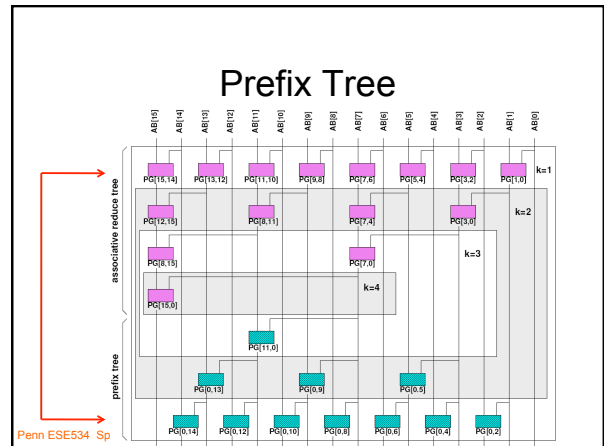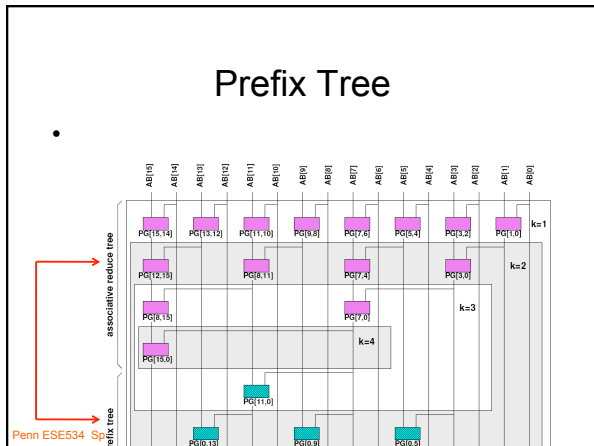

## Note: Constants Matter

- Watch the constants
- Asymptotically this Carry-Lookahead Adder (CLA) is great
- For small adders can be smaller with
  - fast ripple carry
  - larger combining than 2-ary tree
  - mix of techniques
- ...will depend on the technology primitives and cost functions

Penn ESE534 Spring2012 -- DeHon

55

## Two's Complement

- positive numbers in binary
- negative numbers
  - subtract 1 and invert
  - (or invert and add 1)

Penn ESE534 Spring2012 -- DeHon

56

## Two's Complement

- 2 = 010
- 1 = 001
- 0 = 000
- -1 = 111
- -2 = 110

Penn ESE534 Spring2012 -- DeHon

57

## Addition of Negative Numbers?

- ...just works

A: 111	A: 110	A: 111	A: 111
B: 001	B: 001	B: 010	B: 110
S: 000	S: 111	S: 001	S: 101

Penn ESE534 Spring2012 -- DeHon

58

## Subtraction


- Negate the subtracted input and use adder
    - which is:
      - invert input and add 1
      - works for both positive and negative input
- $-001 \rightarrow 110 + 1 = 111$   
 $-111 \rightarrow 000 + 1 = 001$   
 $-000 \rightarrow 111 + 1 = 000$   
 $-010 \rightarrow 101 + 1 = 110$   
 $-110 \rightarrow 001 + 1 = 010$

Penn ESE534 Spring2012 -- DeHon

59
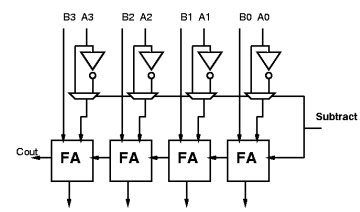
## Subtraction (add/sub)

- **Note:** you can use the “unused” carry input at the LSB to perform the “add 1”



Penn ESE534 Spring2

## Overflow?

A: 111    A: 110    A: 111    A: 111  
B: 001    B: 001    B: 010    B: 110  
S: 000    S: 111    S: 001    S: 101

A: 001    A: 011    A: 111  
B: 001    B: 001    B: 100  
S: 010    S: 100    S: 011

- $\text{Overflow} = (\text{A.s} == \text{B.s}) * (\text{A.s} != \text{S.s})$

## Admin

- HW2 out today
- Reading for Wednesday online

## Big Ideas [MSB Ideas]

- Can build arithmetic out of logic

## Big Ideas [MSB-1 Ideas]

- Associativity
- Parallel Prefix
- Can perform addition
  - in log time
  - with linear area