

ESE534 Computer Organization

Day 9: February 13, 2012
Interconnect Introduction



Previously

- Universal building blocks
- Programmable Universal Temporal Architecture


Today

- Universal Spatially Programmable
- Crossbar
- Programmable compute blocks
- Hybrid Spatial/Temporal
- Bus
- Ring
- Mesh

Spatial Programmable

Day 8

Temporal Programmable

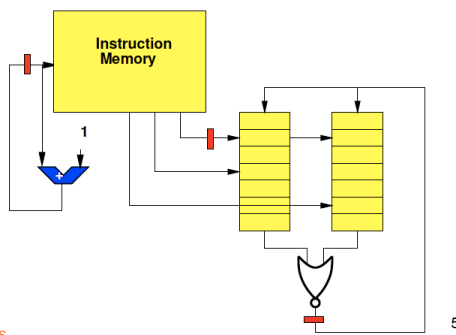


Spatially Programmable

- Program up “any” function
- Not sequentialize in time
- *E.g.* Want to build any FSM

Needs?

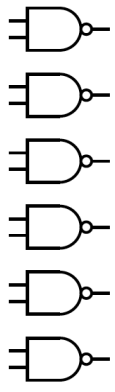- Need a collection of gates.
- **What else will we need?**




7

Penn ESE534 Spring2012 -- DeHon

Needs

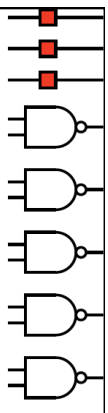- Need some registers
- Need way to programmably wire gates together




8

Penn ESE534 Spring2012 -- DeHon

Multiplexer Interconnect

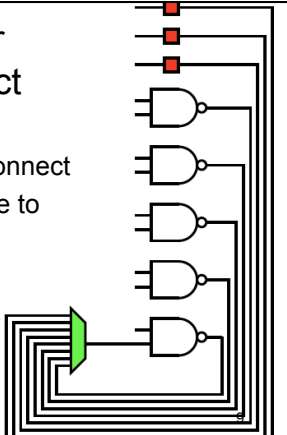- Use a multiplexer for programmable interconnect
- Can select any source to be an input for a gate
- **How big is an N-input multiplexer?**




7

Penn ESE534 Spring2012 -- DeHon

Sources?

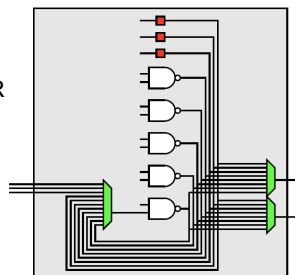- **What are potential sources?**
 - Inputs to circuit -- I
 - Outputs of gates -- G
 - Outputs of registers -- R
- $N=I+G+R$




10

Penn ESE534 Spring2012 -- DeHon

Sinks

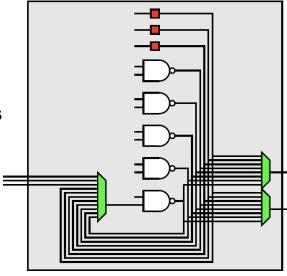- **Which things need programmable inputs? (and how many?)**
 - Circuit outputs -- O
 - Gate -- needs one per input -- kG
 - Assuming k-input gates
 - Registers -- R
 - $M = O+R+kG$



11

Penn ESE534 Spring2012 -- DeHon

N-input, M-output Multiplexing

- **Area?**
- **Instruction Bits?**
- **Data input switching**
 - **Capacitance Switched?**
 - **Delay?**
- **Control input switching**
 - **Capacitance switched?**
 - **Delay?**

12

Penn ESE534 Spring2012 -- DeHon

Mux Programmable Interconnect


- Area $M \times N = (I+G+R) \times (O+kG+R)$
 $= kG^2 + \dots$
- Scales faster than gates!

Interconnect Costs


- We can do better than this
 - Touch on a little later in lecture
 - Dig into details later in term
- Even when we do better
- Interconnect can be dominate
 - Area, delay, energy
 - Particularly for Spatial Architectures
 - (saw in HW4, memory can dominate for Temporal Architectures)

Dominant Time


Design	Path	Total Delay	LUT Delay	Inter. %
Altera 10K130V-2	LUT-local-LUT	2.5 ns	2.1 ns	16%
	LUT-row-local-LUT	6.6 ns	2.1 ns	68%
	LUT-column-local-LUT	11.1 ns	2.1 ns	81%
	LUT-row-column-local-LUT	15.6 ns	2.1 ns	87%
	LUT-row-fanout-local-LUT (fanout)	28 ns	2.1 ns	90%

 

Dominant Power [Energy]

 

 XC4003A data from Eric Kusse (UCB MS 1997)




Crossbar

- Allows us to connect any of a set of inputs to any of the outputs.
- This is functionality provided with our muxes

Crossbar Structure

- Can be more efficient

 


Penn ESE534 Spring2012 -- DeHon

19

Crossbar Costs

 
- Area still goes as $M \times N$
- Delay proportional to $M + N$
 - More realistic even for mux implementation
- Energy still goes as $M \times N$



Penn ESE534 Spring2012 -- DeHon

20


Crossbar Notation

 

Penn ESE534 Spring2012 -- DeHon

21

Gates with Crossbar Interconnect

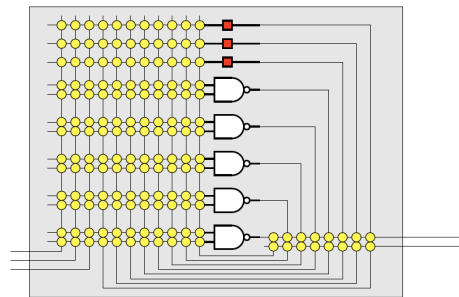

Penn ESE534 Spring2012 -- DeHon

--


Programmable Functions

Penn ESE534 Spring2012 -- DeHon

23

Universal Computation with Fixed Compute Operator

 - Being minimalists, show do not need compute to be programmable
 - Just use fixed nor2 or nand2




Penn ESE534 Spring2012 -- DeHon

--

Mux can be a programmable gate

 - bool mux4(bool a, b, c, d, s0, s1) {
 return(mux2(mux2(a,b,s0),
 mux2(c,d,s0),
 s1));
 }




Penn ESE534 Spring2012

25

Mux as Logic

 - bool and2(bool x, y) {
 return (mux4(false,false,false,true,x,y));
 }
- bool or2(bool x, y) {
 return (mux4(false,true,true,true,x,y));
 }
- Just by routing "data" into this mux4,
 – Can select **any** two input function




Penn ESE534 Spring2012 -- DeHon

26

Programmable Compute

 - Can use programmable gate in place of **nor** gate




Specifying the function of the gate becomes part of the instruction.

Penn ESE534 Spring2012 -- DeHon

27

Is an Adder Universal?

 - Assuming interconnect:
 – (big assumption as we have just seen)
 – Consider:
 A: 001a
 B: 000b
 S: 00cd
- What's c?



Penn ESE534 Spring2012 -- DeHon

Practically


- To reduce (some) interconnect,
 and to reduce number of operations,
 do tend to build a bit more general
 "universal" computing function

Penn ESE534 Spring2012 -- DeHon

29

Arithmetic Logic Unit (ALU)

 - Observe:
 – with small tweaks can get many functions
 with basic adder components




Penn ESE534 Spring2012 -- DeHon

30


ALU Size

- Adder took 6 2-input gates.
- How many 2-input gates did your ALU bitslice require? (HW4.1d?)

Arithmetic and Logic Unit

 


ALU Functions

 


- $A+B$ w/ Carry
- $B-A$
- $A \text{ xor } B$ (squash carry)
- $A*B$ (squash carry)
- $/A$

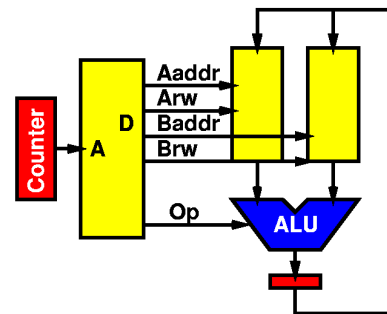Slightly more conventional Programmable Architecture




Instructions

 - Identify the bits which control the function of our programmable device as:
 - *Instructions*



Multibit Word Ops

 - What are we doing when we make the ALU (and register file) width > 1
 - E.g. $w=16$ on HW4
- Benefit?
- Limitation?




Interconnect

Optimization and Design Space


Switching w-bit words

- Consider grouping outputs (inputs) into w-bit words
 - E.g. maybe operators are 16-bit ALUs
- How does this change switching requirements?
 - Don't need to switch bit 3 to bit 7
 - Reduces switching needed

Switching words (w=2 shown)

 

Also share memories


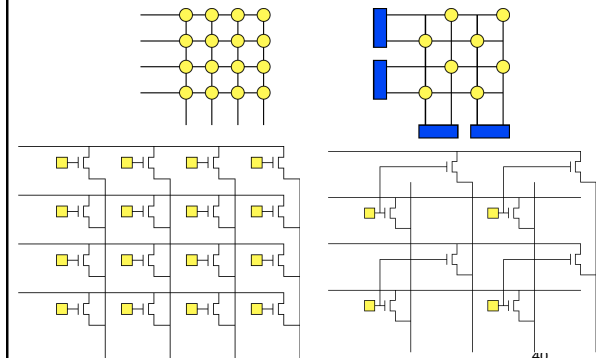


Switching w-bit words

- N/w w-bit inputs, M/w w-bit outputs
- Instruction Bits
 - Factor of w fewer outputs to switch
 - Factor of w fewer inputs $\rightarrow M/w(\log_2(N/w))$
- Area:
 - Factor of w fewer switches, w^2 memories
- Delay:
 - Factor of w fewer sources
- Energy:
 - Factor of w fewer switches

Locality

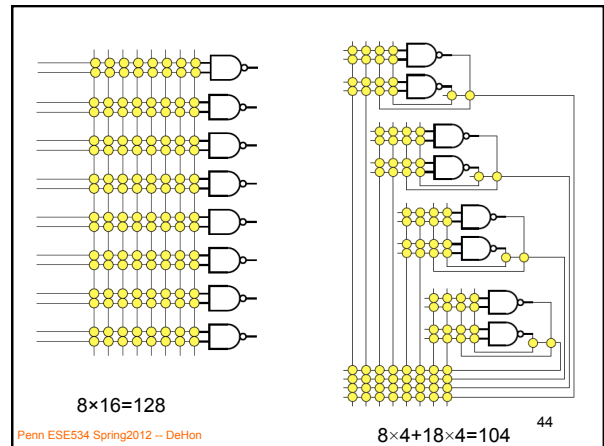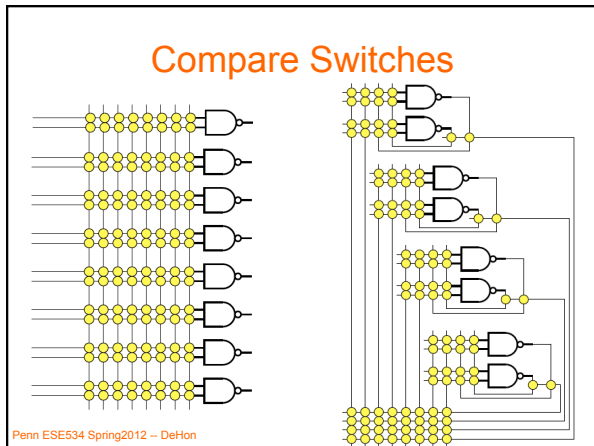- Maybe we don't need to connect everything to everything?
- Cluster groups of C things at leaves
 - CG gates, CR registers
 - Limit cluster I/O – CI, CO
 - Crossbar within cluster
 - Crossbar among clusters



- ### Comparing
- Full Crossbar needs: kG^2 switches
 - How many switches needed for:
 - CG gates per cluster
 - CI inputs to cluster
 - CO outputs from cluster
 - (ignore registers and circuit input/output)
- Penn ESE534 Spring2012 -- DeHon 45

- ### Costs
- Cluster Input Crossbar:
 - Inputs: $CI+CG$
 - Outputs: kCG
 - Cluster Output Crossbar:
 - Input: CG
 - Output: CO
 - Master Crossbar:
 - Inputs: $(G/CG) \times CO$
 - Outputs: $(G/CG) \times CI$
 - $(G/CG) \times CO \times (G/CG) \times CI$
 - $(G/CG) \times (k \times CG^2 + k \times CG \times CI + CG \times CO)$ 46
-
- Penn ESE534 Spring2012 -- DeHon


- ### Costs
- Cluster: $G^2 \times (CI \times CO / CG^2) + k \times G \times (CG + CI + CO)$
 - Full Crossbar: kG^2
 - Compare at: $CG=8, CI=CO=2, G=256, k=2$
 - Cluster case?
 - Full crossbar case?
- Penn ESE534 Spring2012 -- DeHon 47

Hybrid Temporal/Spatial

Penn ESE534 Spring2012 -- DeHon 48

Extremes

- Fully Spatial
- Fully Temporal

 

Penn ESE534 Spring2012 -- DeHon

49

General Case Between


- How many concurrent operators?
- How much serialization?

Penn ESE534 Spring2012 -- DeHon

50

Separate Data Memory and Compute

- Memory banks and compute

 


Penn ESE534 Spring2012 -- DeHon

51

Crossbar Generalized

 - What's different about this crossbar?
 - Compared to one we used in purely sequential case in first part of lecture?




Penn ESE534 Spring2012 -- DeHon

52

Dynamic Crossbar

 - Need to switch crossbar configuration on each cycle




Penn ESE534 Spring2012 -- DeHon

53

Dynamic Crossbar

 - Switching time matters
- Must also supply crossbar controls
 - More wires into array
 - How many?
- Area
 - Bit-level switching case? $N (1+\log(N)) M$
 - W-bit word case? $\sim N (1+\log(N)/W) M$



Penn ESE534 Spring2012 -- DeHon

54


Note on Remainder

- Rest of lecture to introduce issues
 - Be illustrative
- Not intended to be comprehensive
- Will return to interconnect and address systematically starting on Day 15

Class Ended Here


Local Memory Case

- Put memory local to compute

 


Reduce Interconnect?

 - How can we reduce interconnect?
 - Maybe don't need to deliver a non-local value to every bank on every cycle?
 - Maybe don't need to communicate everywhere?




Single Global Bus

 


Single Global Bus

- Pros and Cons?

 

Multiple Global Busses

 


Penn ESE534 Spring2012 -- DeHon

61

Interconnect Resource

 
- Can communication B values per cycle
- Could be dominant area/energy
 - Don't want too large
- Could be bottleneck in computation?
 - Don't want too small
- Example of an architectural parameter



Penn ESE534 Spring2012 -- DeHon

62

Nearest Neighbor Interconnect

 


Penn ESE534 Spring2012 -- DeHon

63

Nearest Neighbor Interconnect

 
- Compare to crossbar?
 - Number can transmit per cycle?
 - Area?



Penn ESE534 Spring2012 -- DeHon

64

Ring Interconnect

 


Penn ESE534 Spring2012 -- DeHon

65

Ring Interconnect

 - Compare to bus?
 - Area?
 - Cycle time?
 - Data transfers/cycle?





Penn ESE534 Spring2012 -- DeHon

66

Ring Interconnect

  - Compare to xbar?
 - Area?
 - Cycle time?
 - Data transfers/cycle?




Penn ESE534 Spring2012 -- DeHon

67

Mesh Interconnect

- Nearest neighbors in 2D


 


Penn ESE534 Spring2012 -- DeHon

68

Mesh Interconnect

  - Compare to ring?
 - Area?
 - Latency?
 - Throughput?



P

69

Interconnect Design Space

- Large interconnect design space
- We will be exploring systematically
 - Day15—18+24

Penn ESE534 Spring2012 -- DeHon

70

Admin

- Drop Date Friday
- HW5 out – 1 problem due Monday
 - Next due following Monday
- No class next Wednesday (2/23)
 - Class this Wednesday and Monday
 - Office hours this Tuesday (not next)
- Reading for Wednesday, Monday on Blackboard

Penn ESE534 Spring2012 -- DeHon

71

Big Ideas

- Interconnect can be programmable
- Interconnect area/delay/energy can dominate compute area
- Exploiting structure can reduce area
 - Word structure
 - Locality

Penn ESE534 Spring2012 -- DeHon

72