

# CMOS Transistors

## Introduction to Computer Systems, Fall 2022

**Instructor:** Travis McGaha

**TAs:**

Ali Krema

Andrew Rigas

Anisha Bhatia

Audrey Yang

Craig Lee

Daniel Duan

David LuoZhang

Eddy Yang

Ernest Ng

Heyi Liu

Janavi Chadha

Jason Hom

Katherine Wang

Kyrie Dowling

Mohamed Abaker

Noam Elul

Patricia Agnes

Patrick Kehinde Jr.

Ria Sharma

Sarah Luthra

Sofia Mouchtaris

🌐 When poll is active, respond at **pollev.com/tqm**

📱 Text **TQM** to **37607** once to join

# How familiar are you with E&M concepts like voltage, current & charge?

I am very familiar with these topics

I am somewhat familiar with these topics

I am neither particularly familiar or unfamiliar with these topics

I am somewhat unfamiliar with these topics

I am very unfamiliar with these topics

I have never taken a class or studied these topics

I prefer not to say

Powered by  **Poll Everywhere**

Start the presentation to see live content. For screen share software, share the entire screen. Get help at [pollev.com/app](https://pollev.com/app)

# Logistics

- ❖ HW00 Binary Quiz: **This Friday** 9/16 @ 11:59 pm
  - Quiz On Canvas
  - Should have everything you need
  
- ❖ Chek-in01: Due this Monday @ 4:59 pm
  - To be released Thursday
  
- ❖ HW01 bits.c: to be released sometime this week
  - Will require VM setup (also to be released soon)
  - Has you “program” in C
  - Should have everything needed from lectures
    - VM Stuff will have information in the HW1 specification & recitation

# Lecture Outline

- ❖ **Physics Background**
- ❖ CMOS Transistor
- ❖ CMOS Logical Circuits
- ❖ CMOS Circuit Design

# Disclaimer:

- ❖ This course is NOT assuming you know E&M Physics
  - It may help to have some background
  - I am going to give a VERY simplified view of E&M Physics
  
- ❖ If you want to know more of the details with transistors & how they work, courses like ESE 2150 (Electrical Circuits and Systems) may appeal to you

# Charge, Current, Voltage


*This is a big simplification*

- ❖ Charge can be either positive or negative
  - Electrons are common units of negative charge and can move through conductive material
  - Like charges repel, opposite charges attract
- ❖ Current: the rate of flow of positive charge
- ❖ Voltage: Positive charge want to move from places with high voltage to lower voltage
  - (vice versa for negative charge)
  - sometimes called “electric pressure”
  - Measured relative to a reference point (usually called “ground”)
 
# Voltage & Current Analogy

*This is a big simplification*


- ❖ Imagine we have a slanted pipe
  - One end on the ground, the other end is in the air
  - Water is placed in the high end of the pipe
  - What happens next?


 
# Voltage & Current Analogy

*This is a big simplification*


- ❖ Water flows to the bottom!
  - The water can be thought of positive charge
  - Positive charge moves from higher voltage to lower voltage




 
# Circuit example


- ❖ Consider the following example circuit



 
# Circuit example w/ Switch

- ❖ Circuits can also have a switch
  - The switch can be open or close

If the switch is closed, charge can flow through like it is a wire




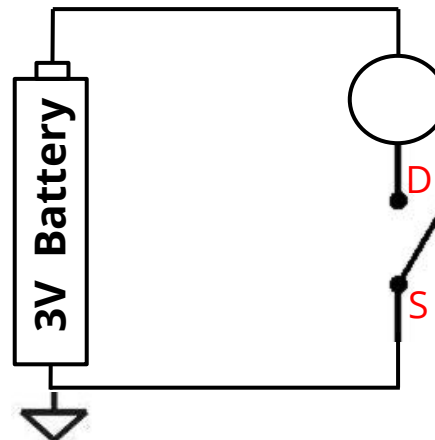If the switch is open, charge cannot flow through


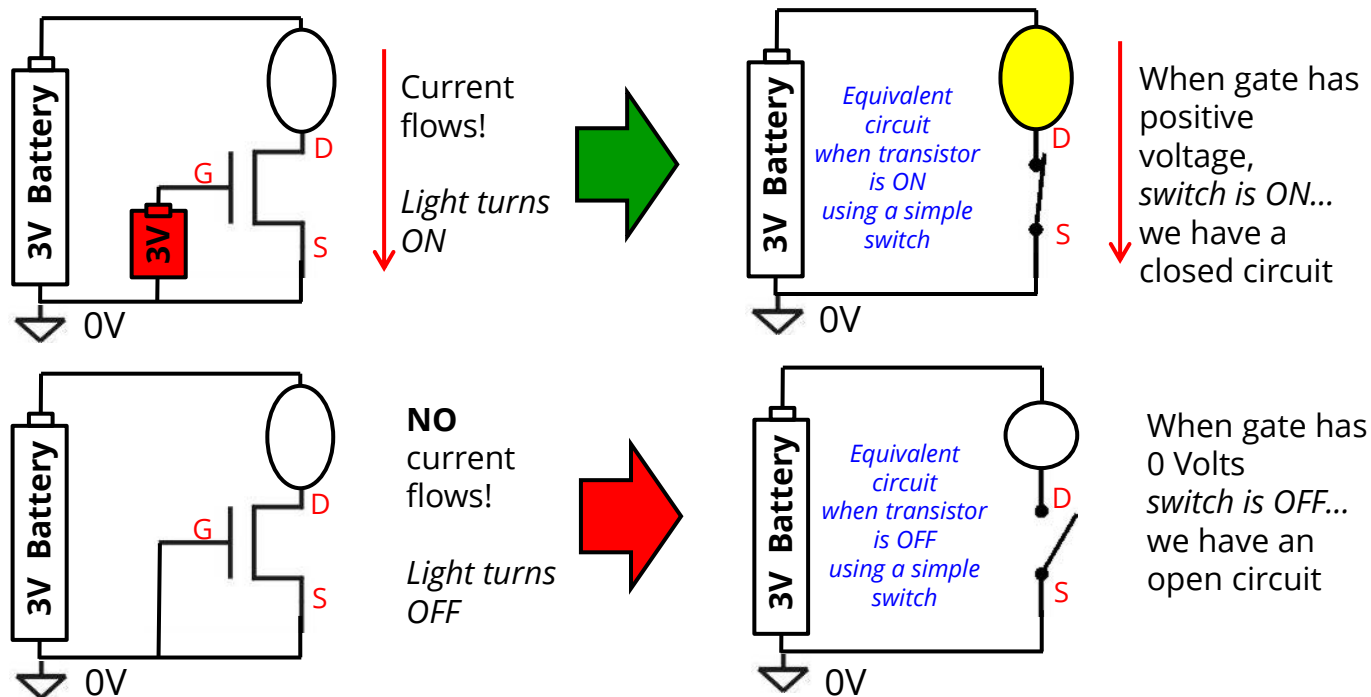
# What Is a Transistor (MOSFET Type)?

- ❖ An electrical device that acts as an **electrical switch**; it's typically made from Silicon
  - 3 electrical contacts/terminals: **G**ate, **D**rain, **S**ource
  - **G**ate controls flow of current between **D**rain and **S**ource terminals; this style transistor is called a MOSFET



# Lecture Outline

- ❖ Physics Background
- ❖ **CMOS Transistor**
- ❖ CMOS Logical Circuits
- ❖ CMOS Circuit Design


# Two Types of MOSFET

## ❖ nMOS



- **GATE Voltage MUST BE  $>$  Body, Source, Drain to be ON**
- **(voltage must be high)**
 
## ❖ pMOS


- **GATE Voltage MUST BE  $<$  Body, Source, Drain to be ON**
- **(Voltage must be low)**



**nMOSFET**

  

**pMOSFET**

 


*Do not forget to draw the circle.*


# CMOS: pMOSFET & nMOSFET in Complement

 **3V on the input (the gates) turns the light OFF!**


- What if the input is set to 0V?
  - 0V turns NMOS **OFF**
  - 0V turns PMOS **ON**
  - **Light has "3V" across it!**
  - Current flows in this circuit, so light turns **ON!**




# CMOS: pMOSFET & nMOSFET in Complement

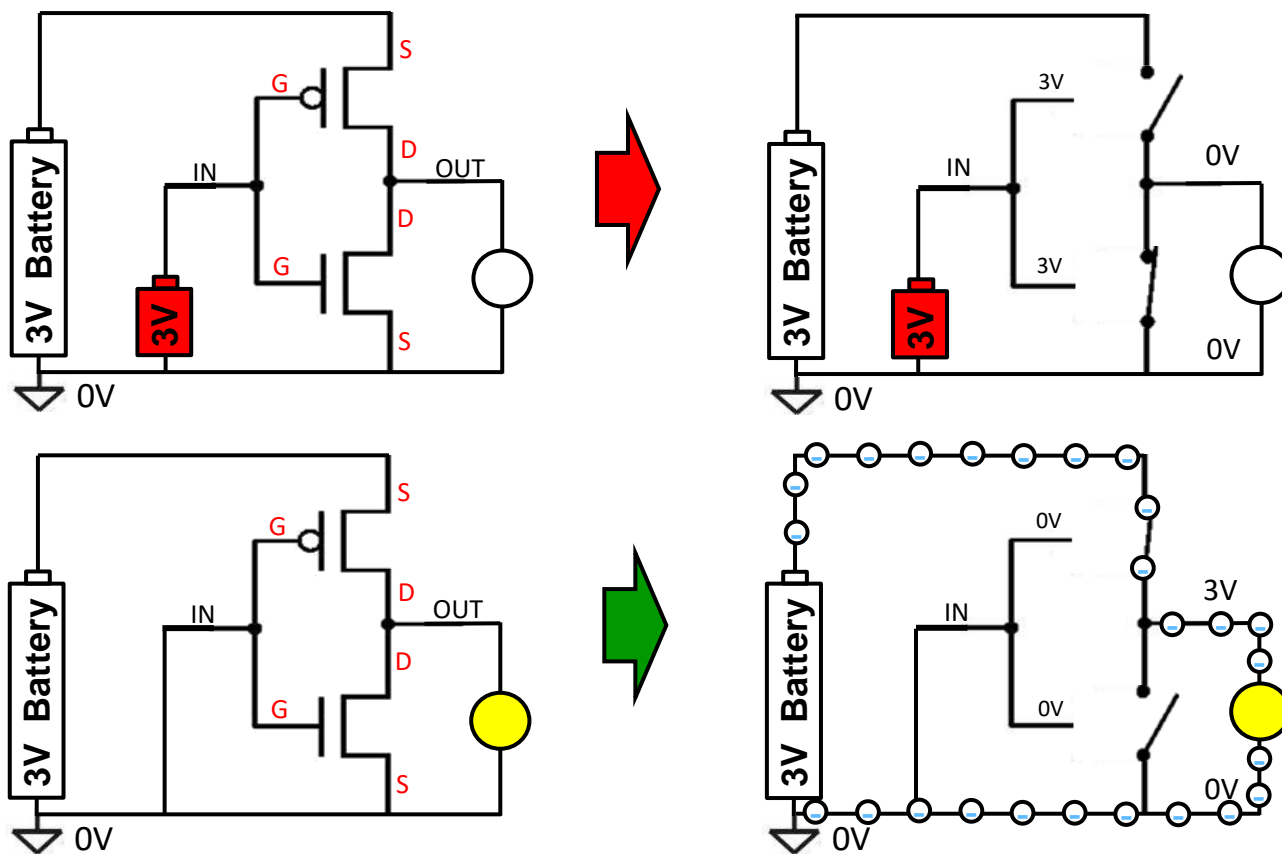


# More Common Electrical Symbols

 


*Circuit Drawings so far*

 

*Standard notation to use going forward*

 

High Voltage  
(3V, V<sub>dd</sub>, etc)

 

Low Voltage (0V),  
typically ground  
(GND)



# Lecture Outline

- ❖ Physics Background
- ❖ CMOS Transistor
- ❖ **CMOS Logical Circuits**
- ❖ CMOS Circuit Design

# Voltages as Bits

- ❖ Transistors are the basis for all digital electronics
  - We've seen that they work by controlling the flow of charge
  
- ❖ We can map bits onto different voltages:
  - High voltage – we'll call this state "1"
  - Low voltage – we'll call this state "0"

*\*\*Only two relevant voltages*



Computers use transistors as switches to manipulate bits

- Before transistors: tubes, electro-mechanical relays (pre 1950s)
- Mechanical adders (punch cards, gears) as far back as mid-1600s

# CMOS Transistors Simplified


nMOS



Input	Output
1	Connected
0	Dis-connected

# CMOS Transistors Simplified

pMOS

 


Circle = "negation"

Input	Output
1	Dis-connected
0	Connected

# CMOS Transistors Simplified

Circle = "negation"

 

PMOS



NMOS

Input	Output
1	Dis-connected
0	Connected

Input	Output
1	Connected
0	Dis-connected

# CMOS Circuits as Logical Circuits


- ❖ Instead of thinking of voltages, we can analyze our circuit think of in terms of bits “1” or “0”

- ❖ Consider our previous circuit:

- Output is the same as whatever “source” it is connected to
- pMOS: on when input is low
- nMOS: on when input is high

- ❖ Truth Table

Input	pMOS State	nMOS state	Output
1	Disconnected	Connected	0
0	Connected	Disconnected	1

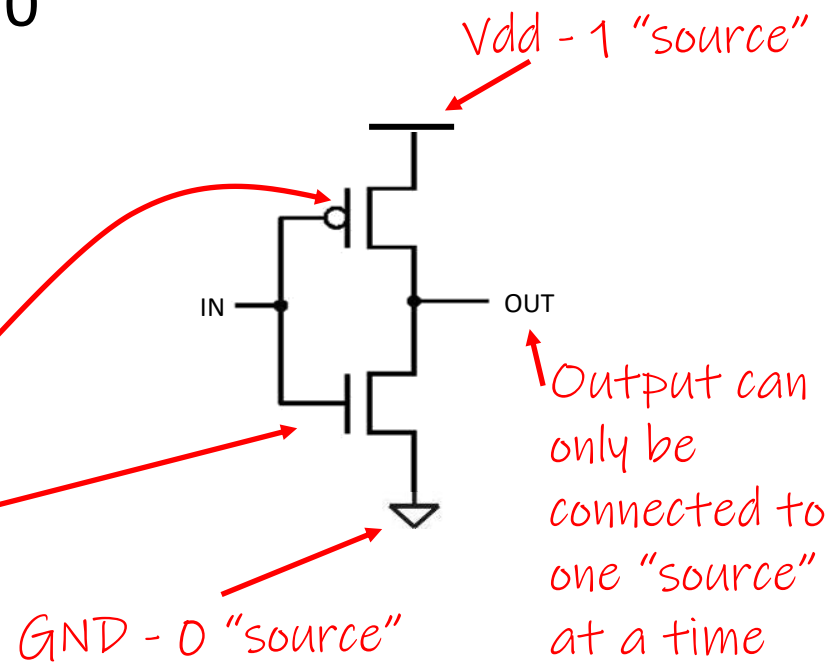

*This is the same as a "NOT" operation*

# PUN & PDN

- ❖ We can split our "NOT" circuit into two halves:

- ❖ **Pull Up Network (PUN)**


- "Pulls" the output "Up" to "1"

- Can only contain pMOS Transistors

- ❖ **Pull Down Network (PDN)**

- "Pulls" the output "down" to "0"

- Can only contain nMOS Transistors

 

- ❖ Output can only be connected to "1" or "0" at any time

- Exactly one of PUN or PDN can be "ON" at a time

- ❖ We will see more complex examples in a moment

# nMOS & pMOS in PUNs & PDNs


- ❖ **In a digital circuit there are only two relevant voltage levels, the low voltage level, GND (0), and the high voltage level, Vdd (1).**
  - An nMOS transistor is only ON when the gate voltage is higher than the source and drain voltages
  - A pMOS transistor is only ON when the gate voltage is lower than the source and drain voltages
- ❖ Therefore, an nMOS transistor can only be used to pass a low voltage and a pMOS transistor can only be used to pass a high voltage
- ❖ nMOS can only be used for the PDN
- ❖ pMOS can only be used for the PUN


 
# The NAND (NOT-AND) Circuit

❖  $\text{NAND} == \text{NOT AND} == \sim(A \& B)$

*Note: parallel structure on top,  
series on bottom*



Parallel Transistors: only one needs to be on for a connection to be made across them  
(Similar to using an OR)

Series Transistors: BOTH need to be on for a connection to be made across them  
(Similar to using an AND)


*NAND Transistor Level*

# The NAND (NOT-AND) Circuit


❖  $\text{NAND} == \text{NOT AND} == \sim(A \& B)$

*Sample Input: A=0, B=1*

 *Note: parallel structure on top,  
series on bottom*



*NAND Transistor Level*

 


*NAND  
Truth Table*

A	B	C
0	0	1
0	1	1
1	0	1
1	1	?
 
# The NAND (NOT-AND) Circuit


❖  $\text{NAND} == \text{NOT AND} == \sim(A \& B)$

*Note: parallel structure on top,  
series on bottom*



*NAND Transistor Level*

*Sample Input: A=1, B=1*

 


*NAND  
Truth Table*

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

 
# The NAND (NOT-AND) Circuit

Note: parallel structure on top,  
series on bottom



NAND Transistor Level

Sample Input:  $A=0, B=1$

 


A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

NAND Gate  
Truth Table
 
# Poll Everywhere

[pollev.com/tqm](https://pollev.com/tqm)


- ❖ Is this legal, if so, what's the truth table? If not, why?


 
# Poll Everywhere

[pollev.com/tqm](http://pollev.com/tqm)

- ❖ Is this legal, if so, what's the truth table? If not, why?



*Legal!*

A	Output
0	1
1	0


$\sim A = \text{output}$

*This is the "not" circuit*
 
# Poll Everywhere

[pollev.com/tqm](https://pollev.com/tqm)


- ❖ Is this legal, if so, what's the truth table? If not, why?


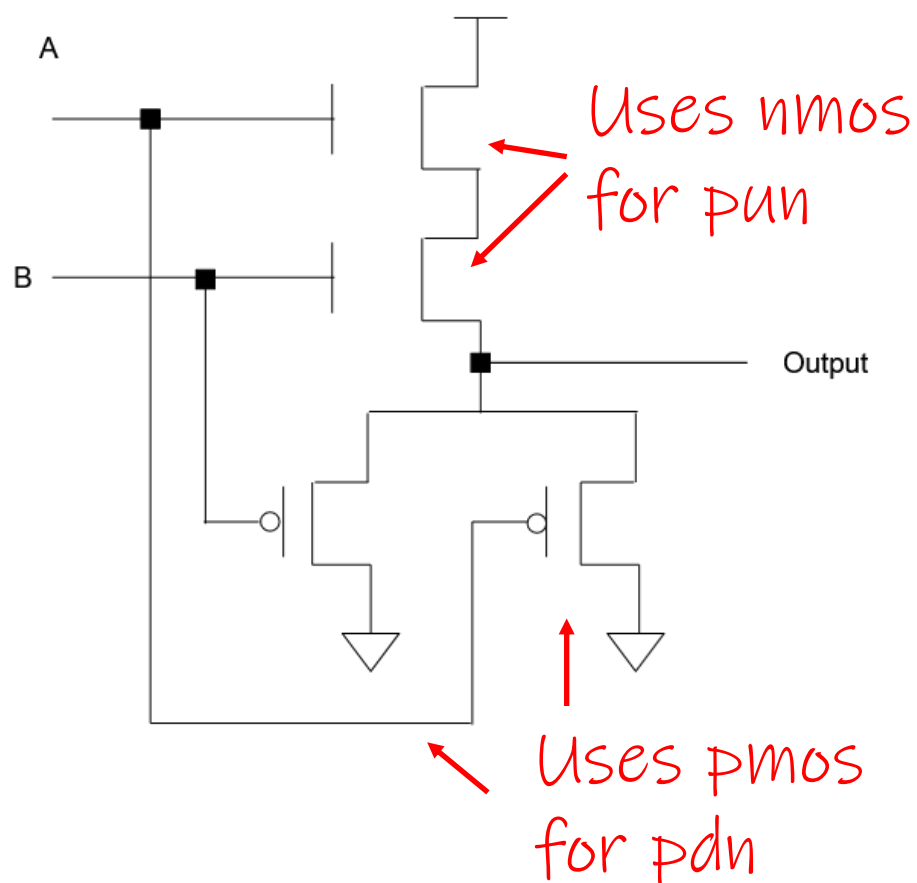
# Poll Everywhere

[pollev.com/tqm](http://pollev.com/tqm)

- ❖ Is this legal, if so, what's the truth table? If not, why?



Illegal


Why?


 
# Poll Everywhere

[pollev.com/tqm](https://pollev.com/tqm)


❖ Is this legal, if so, what's the truth table? If not, why?


 
# Poll Everywhere

[pollev.com/tqm](http://pollev.com/tqm)

❖ Is this legal, if so, what's the truth table? If not, why?



*Legal!*

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0


$$\sim(A|B) = \text{output}$$

*This is "nor"*
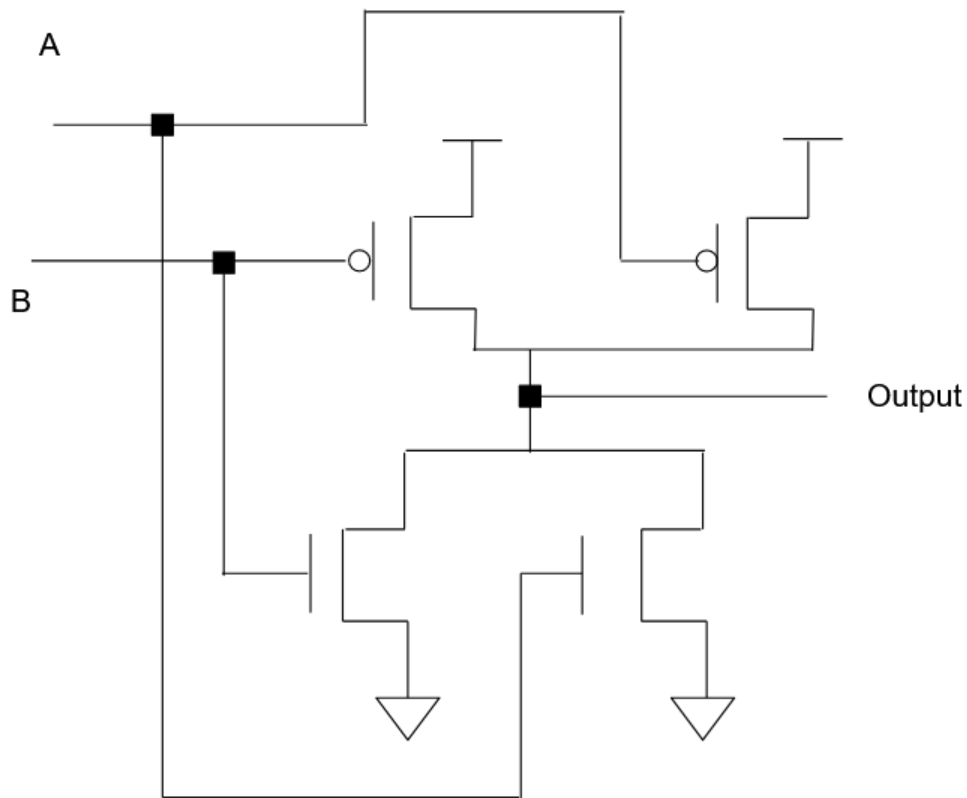
# Poll Everywhere

[pollev.com/tqm](https://pollev.com/tqm)


- ❖ Is this legal, if so, what's the truth table? If not, why?


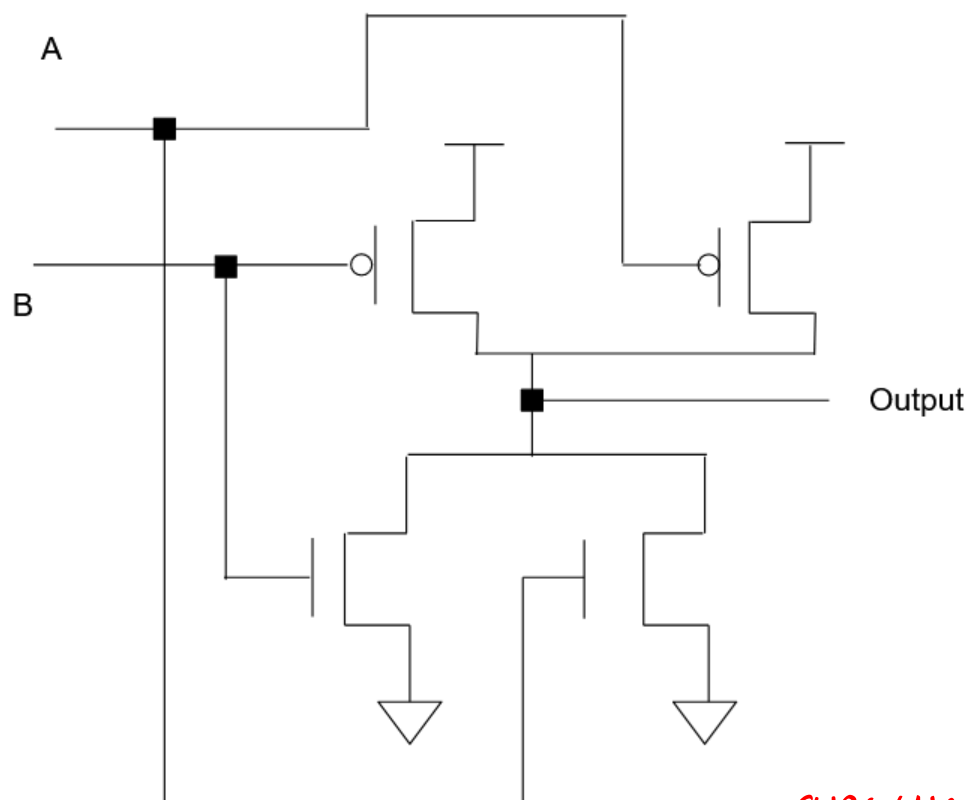
# Poll Everywhere

[pollev.com/tqm](http://pollev.com/tqm)

- ❖ Is this legal, if so, what's the truth table? If not, why?



Illegal

Why?

Consider inputs

$a = 0$

$b = 1$

ground and power both connected to output!!!!!!

# Lecture Outline

- ❖ Physics Background
- ❖ CMOS Transistor
- ❖ CMOS Logical Circuits
- ❖ **CMOS Circuit Design**

# Rules & Suggestions For Design

## ❖ Rules:

- You cannot have pMOS transistors in the PDN
- You cannot have nMOS in the PUN
- Exactly one of PDN/PUN must be “on” at a time
  - Cannot have neither connected to output
  - Cannot have both connected to output
- Every transistor in the PDN must have a complimentary transistor in the PUN
  - When any transistor in PDN is ON, its compliment transistor is OFF

## ❖ Suggestions

- Start with the PDN and then do the PUN (most find it easier)
- Simplify logic before you design any part of the circuit


# NOR Circuit Design Walkthrough

- ❖ First, start with the Boolean Expression
  - NOR is NOT-OR, which is
$$\sim(A \mid B) \leftarrow \text{statement for when output is 1 (True)}$$
- ❖ Since I like to start with PDN, find the cases when output is FALSE, then simplify
  - This can be done by negating the original expression
  - $\sim\sim(A \mid B) \leftarrow \text{statement for when output is 0 (False)}$
  - $(A \mid B) \leftarrow \text{simplified by identity property}$

# NOR Circuit Design Walkthrough

- ❖ With the expression for the PDN (when output is 0), translate it to a circuit diagram for the PDN
  - OR's become transistors in parallel
  - AND's become transistors in series

$(A \mid B)$  becomes

 




# NOR Circuit PUN (Strategy 1)

- ❖ With the simplified expression for PDN, negate it to get the expression for PUN
    - $(A \mid B)$  becomes  $\sim(A \mid B)$
    - Simplify
      - $\sim(A \mid B)$
      - $(\sim A \ \& \ \sim B)$  // by De Morgan's Law
  - ❖ From here, we can convert  $(\sim A \ \& \ \sim B)$  into a PUN
- In this example, initial PUN expression is the same as the original expression. This is not always the case*
 
# NOR Circuit PUN (Strategy 1)

- ❖ From here, we can convert ( $\sim A$  &  $\sim B$ ) into a PUN
  - OR's become transistors in parallel
  - AND's become transistors in series
  - pMOS transistors have an implicit "NOT"
    - pMOS only turns on when input is low (0)





The reason for the circle in pMOS:  
 Circle represents a "Not" or negation
  
# NOR Circuit PUN (Strategy 2)


- ❖ Alternative way to get the PUN from the PDN
  - Series relations in PDN become Parallel relations in PUN
  - Parallel relations in PUN become Series relations in PUN
  - nMOS transistors become pMOS transistors

*This is just a "short-cut" for applying De Morgan's to the PDN*


 
# Completed NOR Circuit

- ❖ Finally, all you have to do is combine the PDN and PUN
  - To be safe, check your work and create a truth table



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0