

Combinational Logic

Introduction to Computer Systems, Fall 2022

Instructor: Travis McGaha

TAs:

Ali Krema

Andrew Rigas

Anisha Bhatia

Audrey Yang

Craig Lee

Daniel Duan

David LuoZhang

Eddy Yang

Ernest Ng

Heyi Liu

Janavi Chadha

Jason Hom

Katherine Wang

Kyrie Dowling

Mohamed Abaker

Noam Elul

Patricia Agnes

Patrick Kehinde Jr.

Ria Sharma

Sarah Luthra

Sofia Mouchtaris

🌐 When poll is active, respond at **pollev.com/tqm**

📱 Text **TQM** to **37607** once to join

How Many CU's are you taking? (including this class)

6 or more

5 or 5.5

4 or 4.5

3 or 3.5

2 or 2.5

less than 2

Powered by  **Poll Everywhere**

Start the presentation to see live content. For screen share software, share the entire screen. Get help at pollev.com/app

Logistics

- ❖ HW01 bits.c: **This Friday** 9/16 @ 11:59 pm
 - Will require VM setup
 - Has you “program” in C
 - Should have everything you need
 - Terminal & starting demo in Recitations this week

- ❖ HW02 Combinational Logic: to be released this week
 - Written Homework, submitted to gradescope
 - **NO EXTENSIONS OVER 72 HOURS**


- ❖ Check-in01: **Due Monday @ 4:59 pm**
 - Coming out soon

Lecture Outline

- ❖ **Incrementor**
- ❖ Adder & Subtractor
- ❖ Mux
- ❖ Multiplier & Others

Combinational Logic

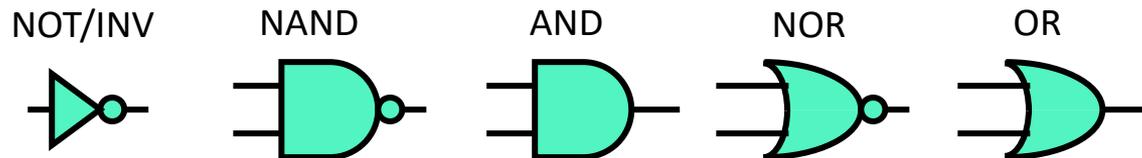- ❖ Boolean functions where the output is a pure function of the inputs
 - There is no “memory” or “stored state”
- ❖ So far, we have basic logic gates from last lecture:




- ❖ We can build more complex "gates" that we can use as building blocks for a processor
- ❖ This Lecture: start implementing binary arithmetic >:]

Aside: XOR Gate

- ❖ Performs the XOR operation


A	B	OUT
0	0	0
0	1	1
1	0	1
1	1	0

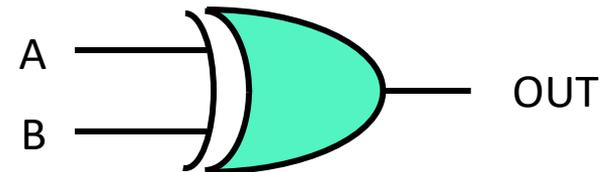

Creating an Incrementor

- ❖ Let's create a 16-bit incrementor!
 - Input: **A** (as a 16 bit 2C integer)
 - Output: **S** = $A + 1$ (as a 16-bit 2C integer)
 - Ignore the overflow case for now
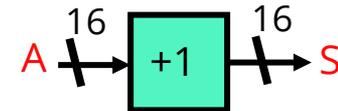
$$\begin{array}{r} 0000000011001011 \\ + 0000000000000001 \\ \hline 0000000011001100 \end{array}$$




- ❖ Theoretical Approach:
 - Use a PLA-like technique to implement the circuit
 - Problem: 2^{16} or 65536 different inputs, 16-bit output
 - This is impractical

One Bit Incrementor "PLA"

- ❖ Implementing a single-column of an incrementor


$$\begin{array}{r}
 0000000011001011 \\
 +0000000000000001 \\
 \hline
 0000000011001100
 \end{array}$$

(Ignore LSB for now)

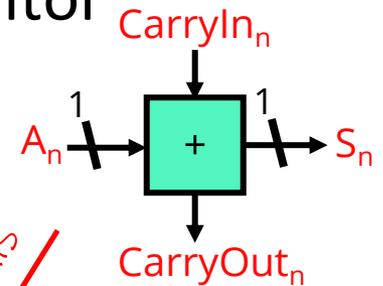

- Inputs: A_n , C_{in}
- Outputs: S_n , C_{out}

A_n	C_{in}	S_n	C_{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

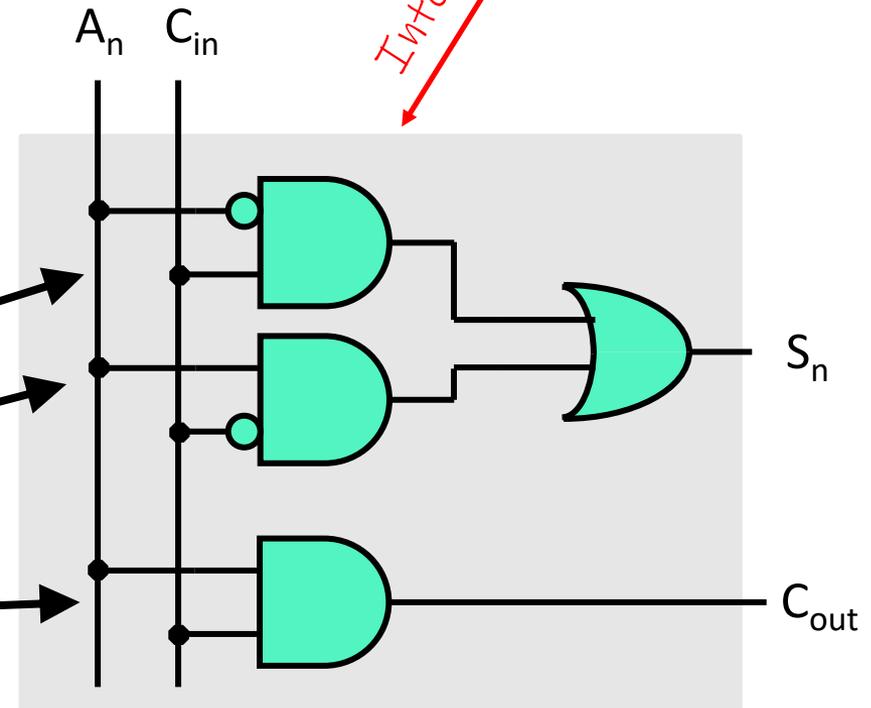

 **Poll Everywhere**pollev.com/tqm

❖ Which of the follow is an equivalent expression for S_n ?

A. $(A_n \& \sim C_{in}) \& (\sim A_n \& C_{in})$

B. $(A_n \mid \sim C_{in}) \& (\sim A_n \mid C_{in})$

C. $\sim(C_{in} \wedge A_n)$

D. $A_n \wedge C_{in}$

E. I'm not sure

A_n	C_{in}	S_n
0	0	0
0	1	1
1	0	1
1	1	0

 **Poll Everywhere**pollev.com/tqm

❖ Which of the follow is an equivalent expression for S_n ?

A. $(A_n \& \sim C_{in}) \& (\sim A_n \& C_{in})$

B. $(A_n \mid \sim C_{in}) \& (\sim A_n \mid C_{in})$

C. $\sim(C_{in} \wedge A_n)$

D. $A_n \wedge C_{in}$


\wedge is XOR

E. I'm not sure

A_n	C_{in}	S_n
0	0	0
0	1	1
1	0	1
1	1	0



One Bit Incrementor Alternative

 - ❖ Can implement with an XOR gate instead



N-bit Incrementor

  - ❖ We can chain the 1-bit Incrementors together
 - Carry-out for bit N , is Carry-in for bit $N+1$
- ❖ 4-bit Incrementor example:





4-bit incrementor
 "implemented" using 4
 1-bit half-adders

Can easily scale to 16-bits

...but how do we
 start off the least-significant bit?

N-bit incrementor LSB

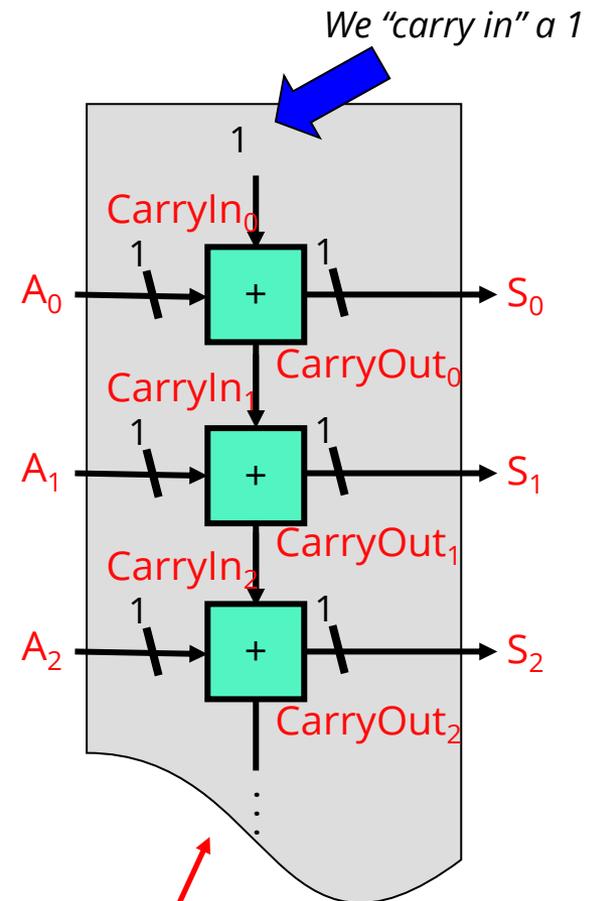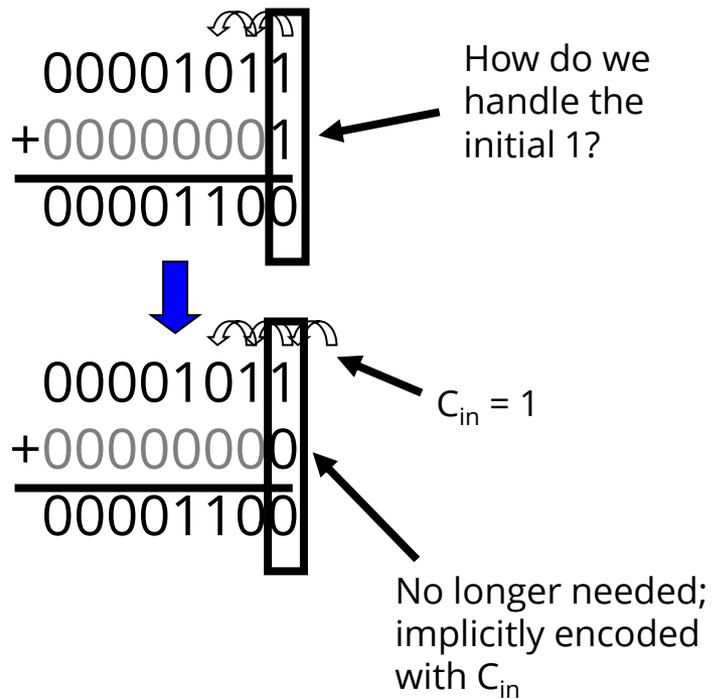- ❖ How do we handle the Least significant bit?





REMEMBER: This is all made of logic gates

Lecture Outline



- ❖ Incrementor
- ❖ **Adder & Subtractor**
- ❖ Mux
- ❖ Multiplier & Others

Adder

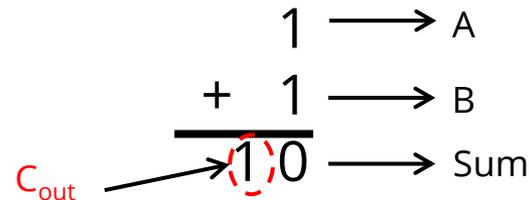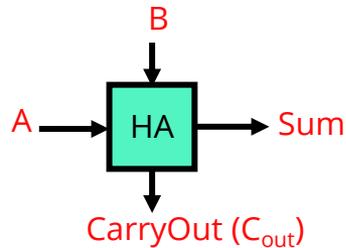- ❖ Similar to incrementor, but doesn't quite work:
 - Incrementor only had to add 2 bits




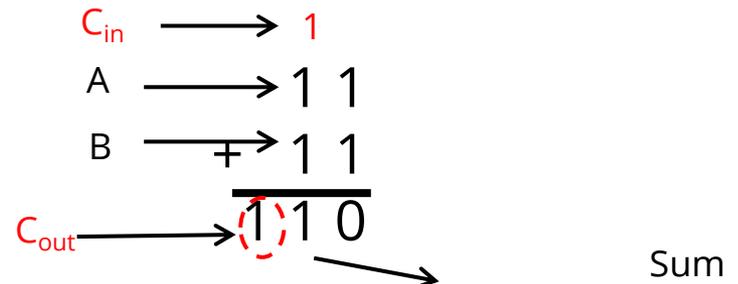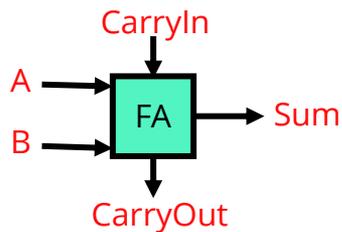- Works for the LSB, since there is no “carry in” for the LSB
- Bits other than the LSB may need to add two bits + carry in




One-Bit Adder

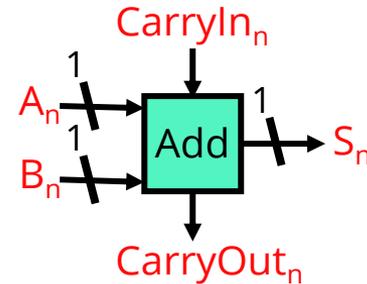- ❖ Like incrementor, we will build a 1-bit component first
- ❖ Start from a truth table
- ❖ Create a PLA from it





A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

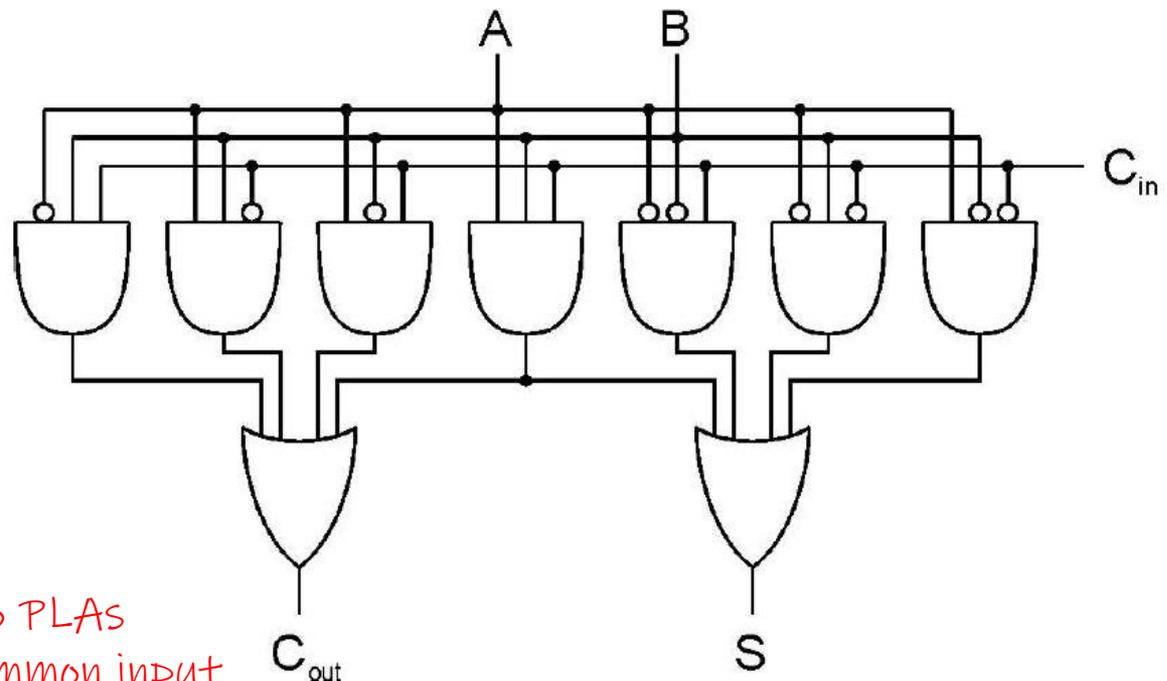

This is just two PLAs fused on the common input

N-Bit Adder

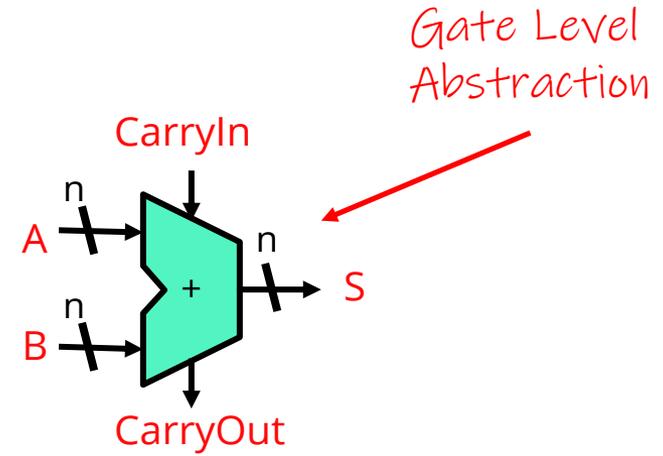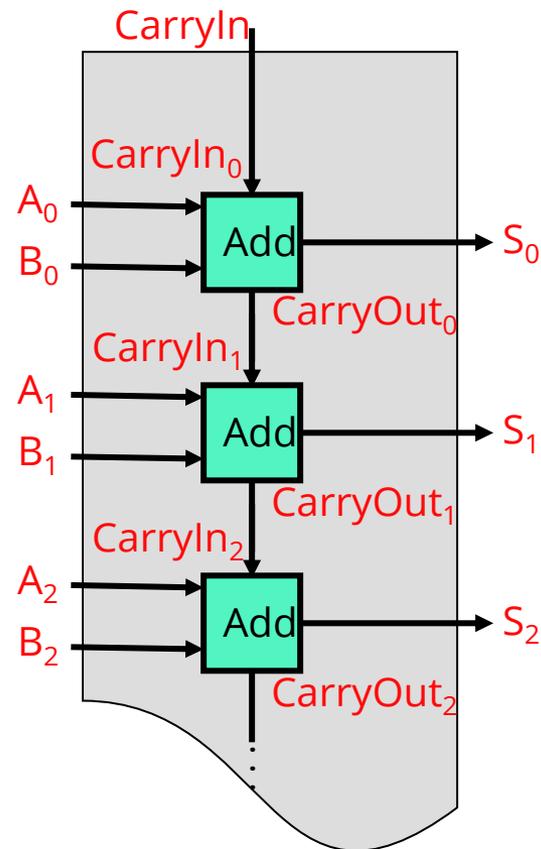

CarryOut: useful for detecting overflow

CarryIn: assumed to be zero if not present

Aside: Efficiency

❖ Full Disclosure:

- Our adder: Ripple-carry adder
- **No one really uses ripple-carry adders**
- Why? *way* too slow
- Latency proportional to n


❖ We can do better:

- Many ways to create adders with latency proportional to $\log_2(n)$
- In theory: constant latency (build a big PLA)
- In practice: too much hardware, too many high-degree gates
- “Constant factor” matters, too
- If you continue to CIS 471, you’ll encounter “carry look ahead adders”, more efficient architecture

Subtractor


- ❖ Build a subtractor from an adder
 - Calculate $A - B = A + -B$
 - Negate B
 - Recall $-B = \text{NOT}(B) + 1$

Approach #1

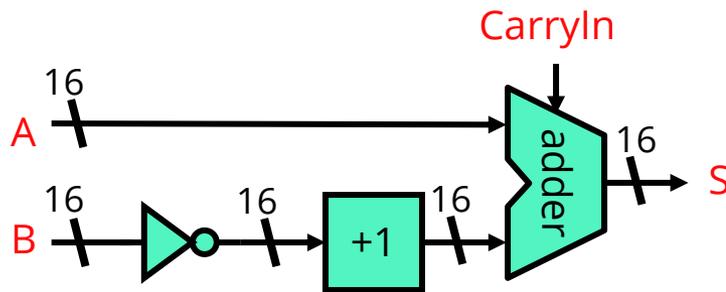

We "carry in" a 1
(no longer need incrementer)

Approach #2

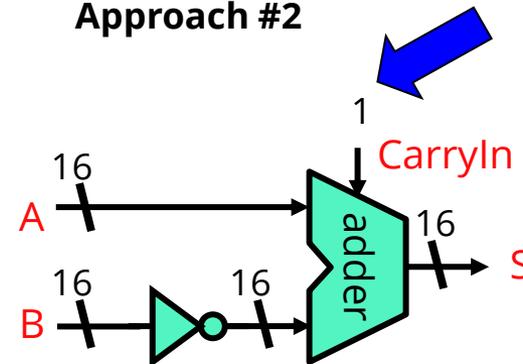

Why is approach #2 better?

Can we combine this with the adder?

Lecture Outline



- ❖ Incrementor
- ❖ Adder & Subtractor
- ❖ **Mux**
- ❖ Multiplier & Others

The Multiplexer


- ❖ Selector/Chooser of signals
- ❖ Shorthand: "Mux"

Note: selector bits map all "0" to be the top input, and increment each input "down"

  If you don't want to follow this ordering, label your MUX in the HW




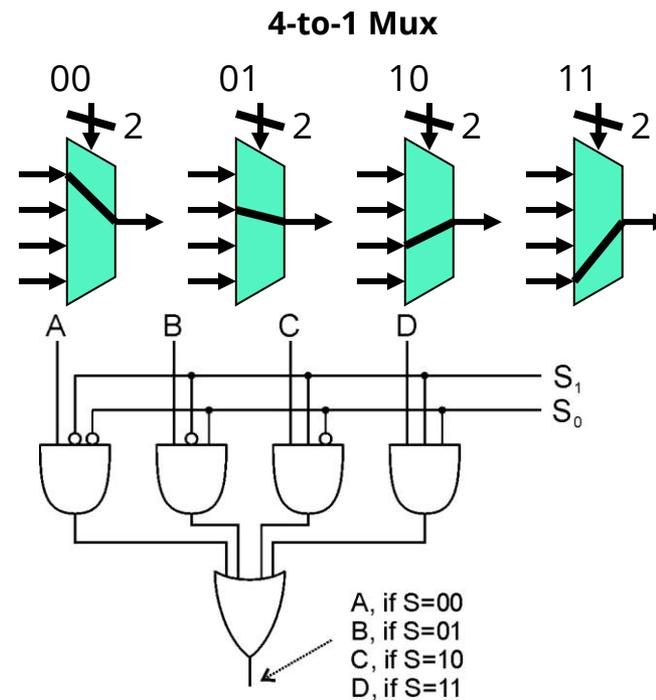Input "S" selects A or B to attach to "O" output
Acts like an "IF/ELSE" statement



The Multiplexor In General

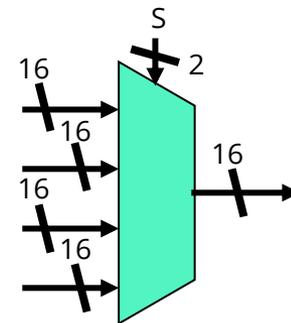- ❖ In General
 - N select bits chooses from 2^N inputs
 - An incredibly useful building block
- ❖ Multi-bit Muxes
 - Can switch an entire “bus” or group of signals
 - Switch n -bits with n muxes with the same select bits



Poll Everywhere

pollev.com/tqm

❖ What is the output of the following mux with selector bits 10


A. 10

B. 01

C. 00

D. 11

E. I'm not sure

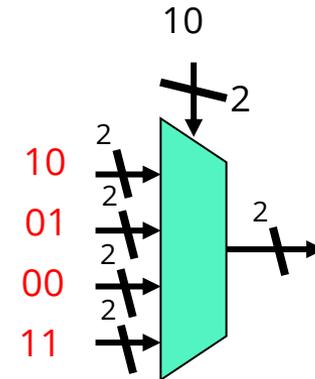

Poll Everywhere

pollev.com/tqm

❖ What is the output of the following mux with selector bits 10


A. 10

B. 01


C. 00

D. 11


E. I'm not sure

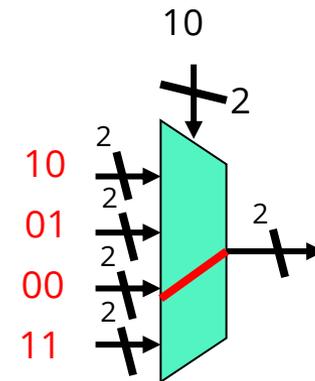

Adder/Subtractor - Approach #1

 

Adder/Subtractor - Approach #2

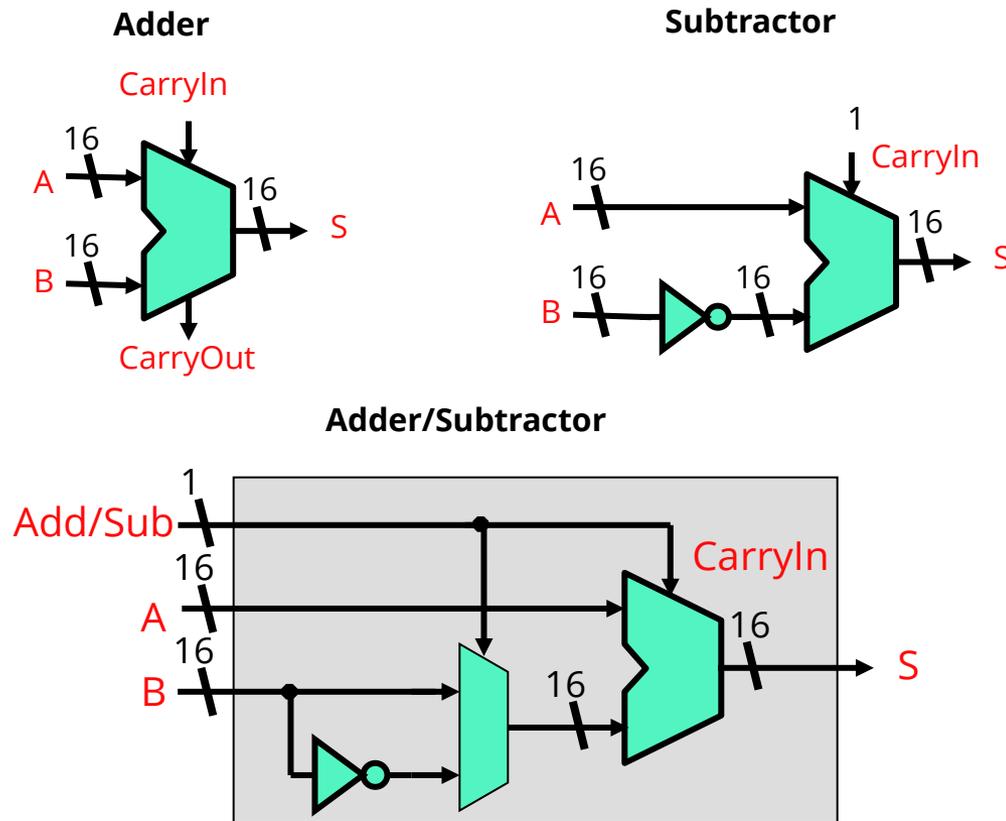


Lecture Outline

- ❖ Incrementor
- ❖ Adder & Subtractor
- ❖ Mux
- ❖ **Multiplier & Others**

Creating a Multiplier

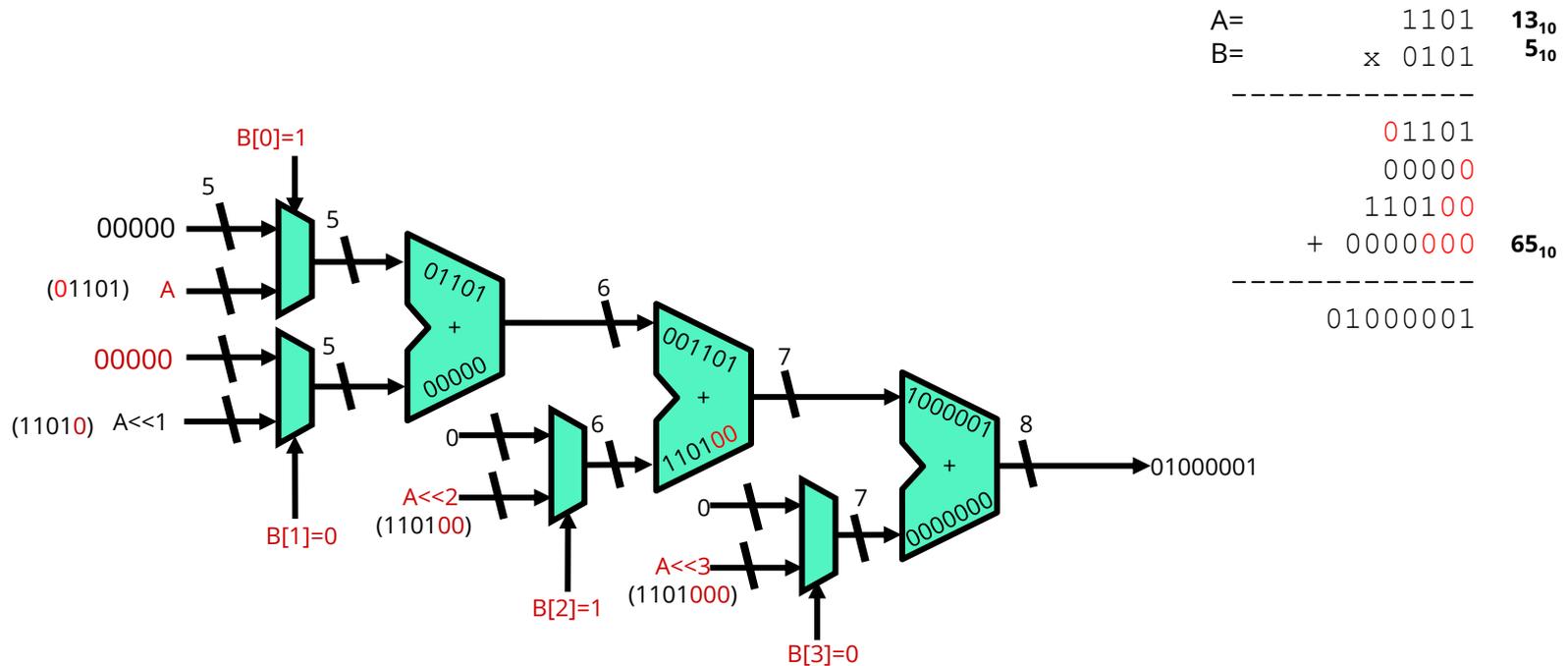- ❖ Combinational Multiplier using adders & muxes
 - Let's build a 4-bit multiplier that makes an 8-bit product
 - Recall: shifting is the same as multiplying by powers of 2
 - **Notation in this example: $B[0]$, means LSB bit of B**



Arithmetic Algos

- ❖ Multiplication:
 - More time efficient algos exist(Karatsuba and others)

- ❖ Divide/mod?
 - Much harder than multiplication
 - Most implementations are not combinational, but are sequential (more on sequential logic starting next lecture)

- ❖ Bitwise ops (AND, OR, XOR, ...)
 - Easy

- ❖ Arbitrary left-right shift
 - Can be done with just muxes (try it if you want!)