

# Datapath and Control Signals


CIS 2400 Recitation 5

# Recitation Outline

- Datapath & Control Signals
  - Register File
  - ALU
  - Memory
  - Branch Unit
- Practice Problems

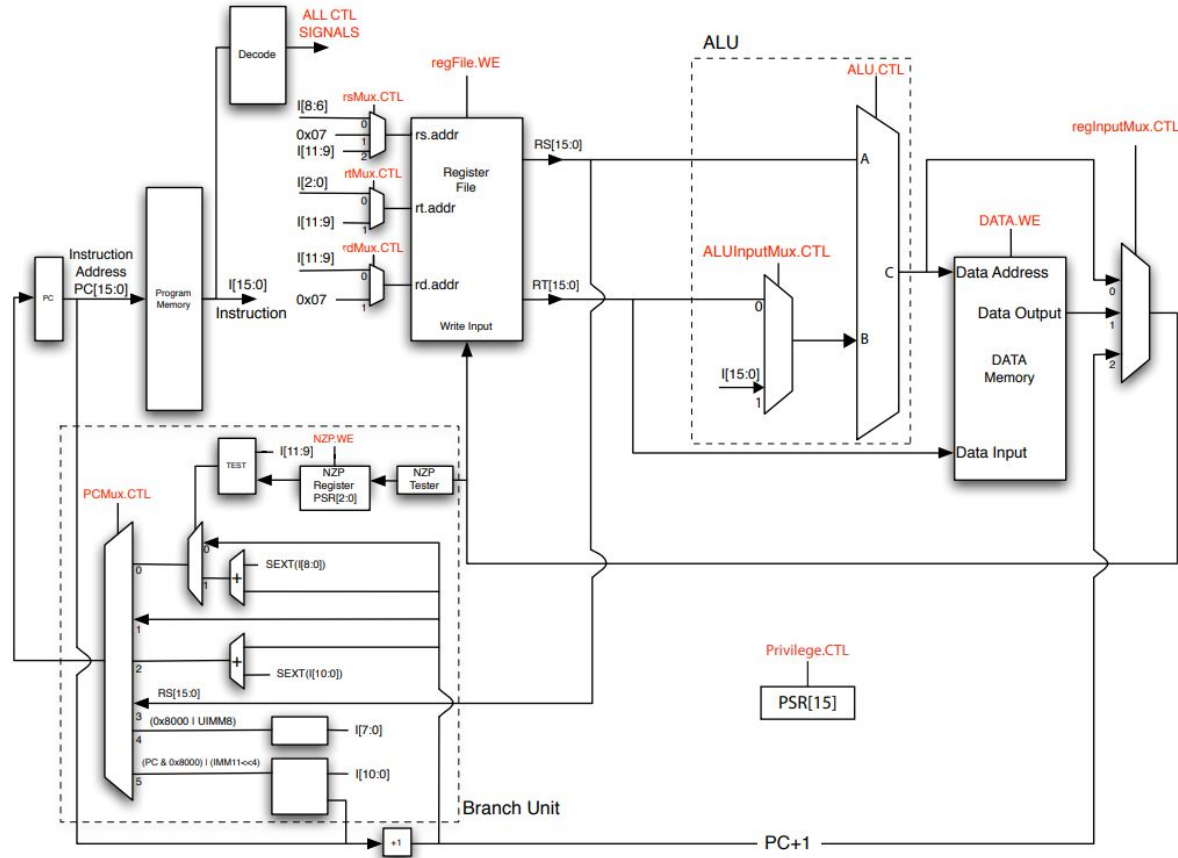
# Datapath & Control Signals

Single Cycle Implementation of the LC4 ISA



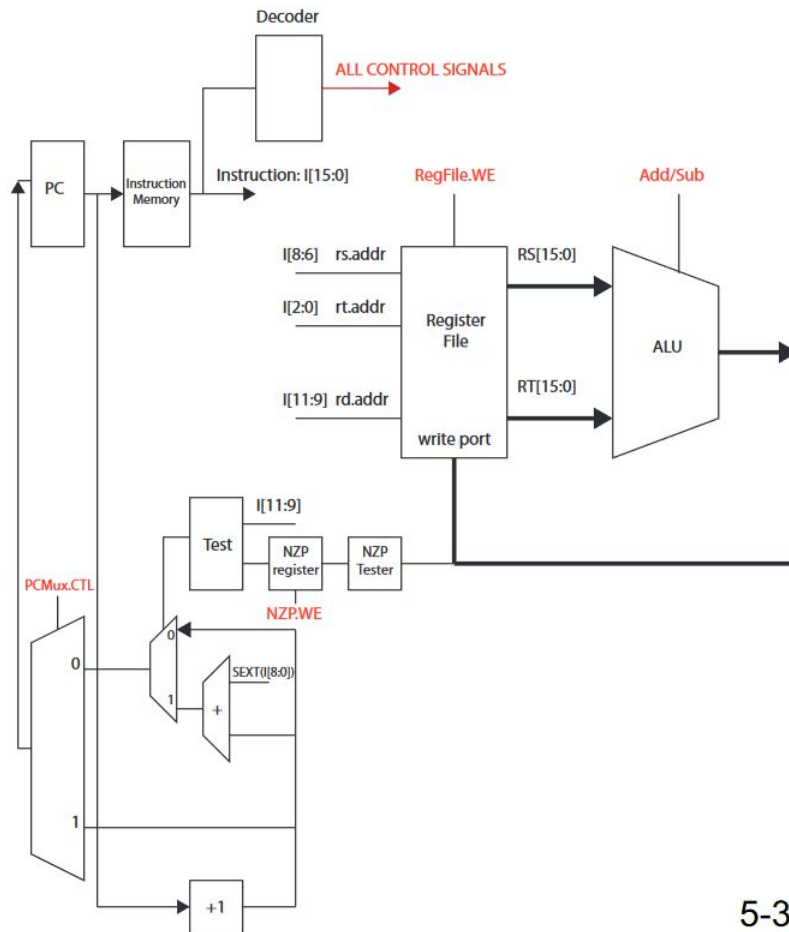
# This is Datapath

- This is a lot
- What does it do?
  - Executes Code
  - Has many control signals to “control” execution
  - Executes code “one step at a time”
  - ...


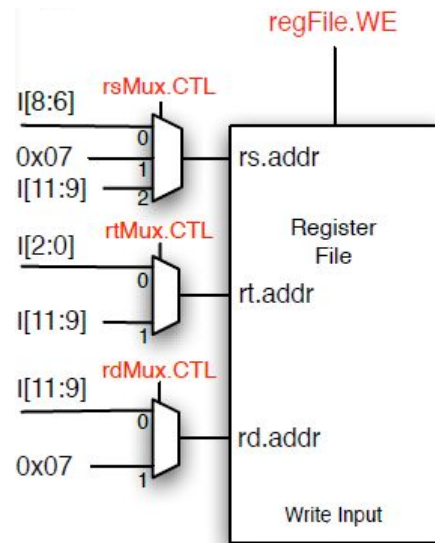
## Datapath Components: Register File


- Stores Registers R0, R1, R2 ... R7
  - Registers are “temporary variables”
  - Sometimes have conventions
    - R7 often used to store the program counter
  - Control signals used to specify where to read register addresses from the 16 bit instruction code
- regFile.WE should be enabled iff one of R0 – R7 is being written to, disabled otherwise



Note: “iff” = “if and only if”
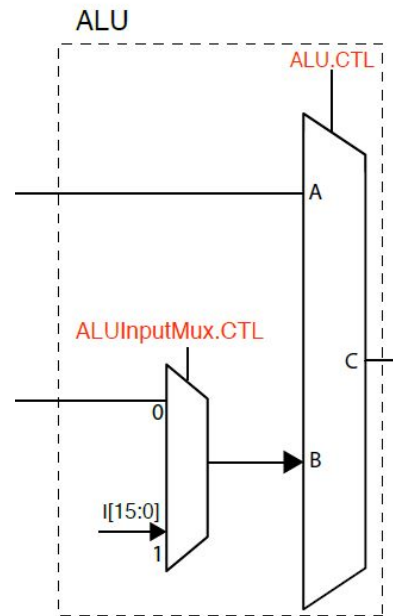
# Datapath Components: ALU


- Arithmetic Logic Unit (ALU)
  - Performs arithmetic operations and logical operations
  - (ALU.CTL) decides which operation is performed
  - ALUInputMux.CTL controls one of the inputs



# Datapath Components: ALU

ALUInputMux.CTL	1	0	$B[15:0] = RT[15:0]$ - B input to ALU = RT
		1	$B[15:0] = I[15:0]$ - B input to ALU = Instruction Word


Signal Name	# of bits	Value	Action
ALU.CTL	6		
Arithmetic Ops	0	$C = A + B$	Addition
	1	$C = A * B$	Multiplication
	2	$C = A - B$	Subtraction
	3	$C = A / B$	Division
	4	$C = A \% B$	Modulus
	5	$C = A + \text{SEXT}(B[4:0])$	
	6	$C = A + \text{SEXT}(B[5:0])$	
Logical Ops	8	$C = A \text{ AND } B$	Bitwise Logical Product
	9	$C = \text{NOT } A$	Bitwise Negation
	10	$C = A \text{ OR } B$	Bitwise Logical Sum
	11	$C = A \text{ XOR } B$	Bitwise Exclusive OR
	12	$C = A \text{ AND } \text{SEXT}(B[4:0])$	
	Comparator Ops	16	$C = \text{signed-CC}(A-B)$
17		$C = \text{unsigned-CC}(A-B)$	[-1, 0, +1]
18		$C = \text{signed-CC}(A - \text{SEXT}(B[6:0]))$	[-1, 0, +1]
19		$C = \text{unsigned-CC}(A - \text{SEXT}(B[6:0]))$	[-1, 0, +1]
Shifter Ops		24	$C = A \ll B[3:0]$
	25	$C = A \ggg B[3:0]$	Shift Right Arithmetic
	26	$C = A \gg B[3:0]$	Shift Right Logical
	Constant Ops	32	$C = \text{SEXT}(B[8:0])$
33		$C = (A \& 0xFF)   (B[7:0] \ll 8)$	

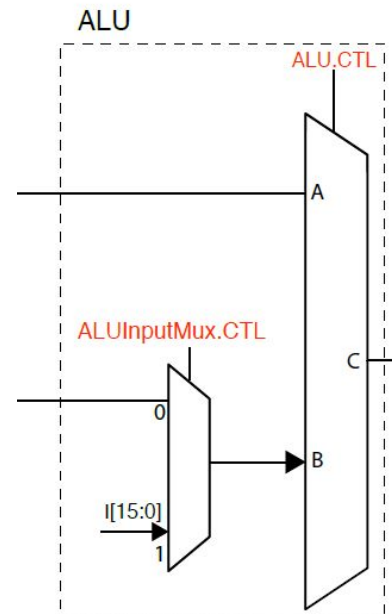



 
## Datapath Components: Data Memory

- Longer term storage than registers
- More difficult to access, need individual instructions to read/write (LDR/STR)
- One Control Signal DATA.WE
  - Should be 1 iff you are **storing** something in memory, 0 otherwise



 
## Datapath Components: regInputMux.ctl

- Inputs:
  - 0 -> ALU result (in case we need to store operation result, e.g. ADD, AND, MOD, etc.)
  - 1 -> Data Output (in case we load from memory)
  - 2 -> PC + 1 (in case we need to store PC + 1 into R7)
- Output:
  - Goes into write input of Register File (since we are storing into register file!)



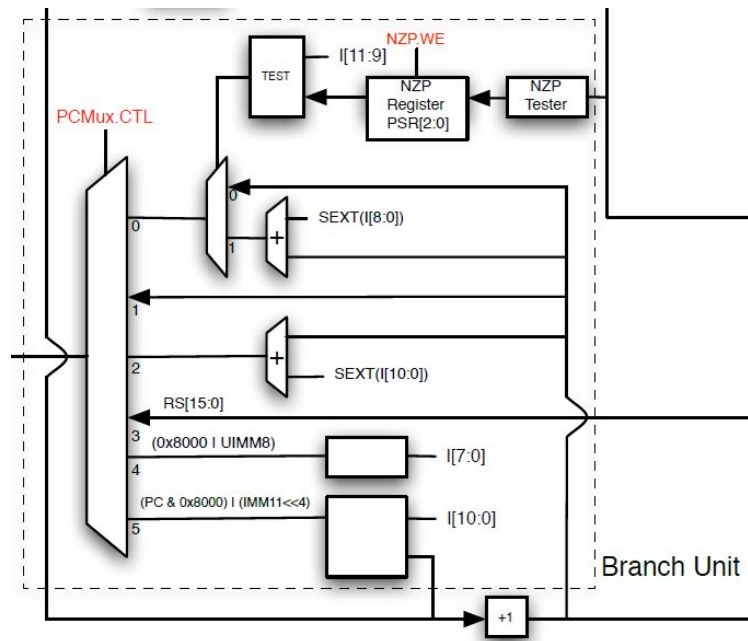
# Datapath Components: Branch Unit

- PCMux.CTL
  - “How are we changing PC?”
  - How PC is updated
  - Usually is 1  
(means  $pc = pc + 1$ )
- NZP.WE
  - “Are we modifying NZP bits?”
  - should be 1 iff regFile.WE is 1 or instruction explicitly sets NZP



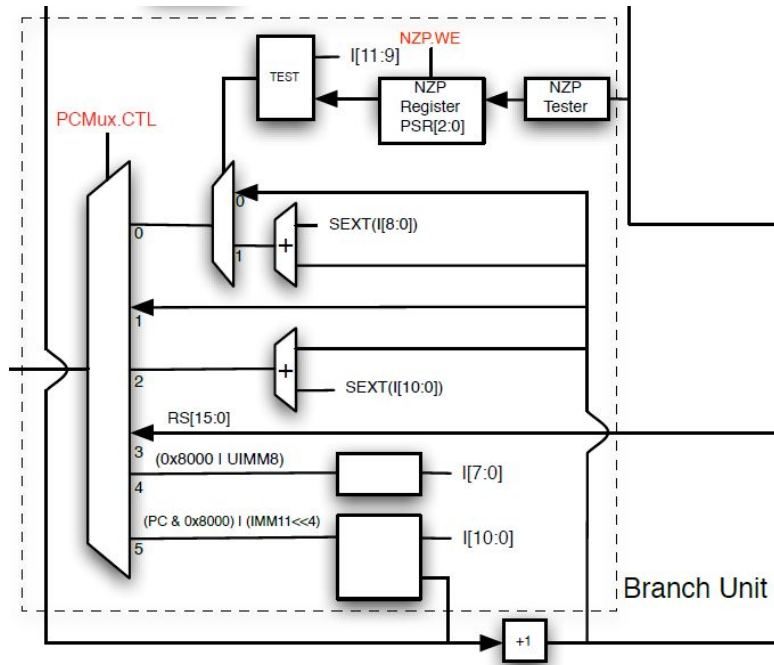
# Datapath Components: Branch Unit Breakdown

- PCMux.CTL
  - 0 ->  $PC = PC + 1$  (if not branching)
  - 0 ->  $PC = PC + 1 + \text{sext}(\text{IMM9})$  (if branching)
  - 1 ->  $PC = PC + 1$
  - 2 ->  $PC = PC + 1 + \text{sext}(\text{IMM11})$
  - 3 ->  $PC = RS$
  - 4 ->  $PC = (0x8000 \mid \text{UIMM8})$
  - 5 ->  $PC = (PC \& 0x8000) \mid (\text{IMM11} \ll 4)$


 
# Datapath Components: Privilege

- Privilege determines whether we are in “User” mode or “Supervisor” mode.
  - Some things (like Operating System stuff) requires Supervisor mode (More in next week’s lectures)
- Privilege.CTL
  - Decides how the Privilege Bit (which is stored in PSR) should change.
  - Should be 2 most of the time
    - We aren’t changing privilege for most instructions
  - TRAP and RTI
    - Instructions that change PSR[15]



Privilege.CTL	2	0	PSR[15] = 0 - Clear privilege bit
		1	PSR[15] = 1 - Set privilege bit
		2	PSR[15] unchanged - no change to privilege bit

## Exercises

- Write out all control signals of the following instructions
  - SUB
  - LDR
  - TRAP
  - RTI
  - CONST
  - BRzp

# Control Signals: SUB



rsMux.CTL →	0
rtMux.CTL →	0
rdMux.CTL →	0
regFile.WE →	1
ALUInputMux.CTL →	0
ALU.CTL →	2
DATA.WE →	0
regInputMux.CTL →	0
NZP.WE →	1
Privilege.CTL →	2
PCMux.CTL →	1

LDR Rd Rs IMM6
 $Rd = \text{dmem}[Rs + \text{sext}(IMM6)]$ 

## Control Signals: LDR

---

 0110 ddds ssii iiii

rsMux.CTL →	0
rtMux.CTL →	X (not used)
rdMux.CTL →	0
regFile.WE →	0
ALUInputMux.CTL →	1
ALU.CTL →	6
DATA.WE →	0
regInputMux.CTL →	1
NZP.WE →	1
Privilege.CTL →	2
PCMux.CTL →	1



TRAP UIMM8

 $R7 = PC + 1; PC = (0x8000 \mid \text{UIMM8}); PSR[15] = 1$ 

## Control Signals: TRAP

---

 1111 xxxx uuuu uuuu

rsMux.CTL →	X
rtMux.CTL →	X
rdMux.CTL →	1 (store in R7)
regFile.WE →	1
ALUInputMux.CTL →	X
ALU.CTL →	X
DATA.WE →	0
regInputMux.CTL →	2 (store PC + 1)
NZP.WE →	1
Privilege.CTL →	1 (PSR[15] = 1)
PCMux.CTL →	4 (0x8000   UIMM8)

# Control Signals: RTI

PC = R7; PSR [15] = 0 1000 xxxx xxxx xxxx

rsMux.CTL → 1 (retrieve R7)

rtMux.CTL → X

rdMux.CTL → X

regFile.WE → 0

ALUInputMux.CTL → X

ALU.CTL → X

DATA.WE → 0

regInputMux.CTL → X


NZP.WE → 0

Privilege.CTL → 0 (PSR[15] = 0)

PCMux.CTL → 3 (PC = R7)

# Control Signals: CONST

rsMux.CTL →	X
rtMux.CTL →	X
rdMux.CTL →	0
regFile.WE →	1
ALUInputMux.CTL →	1
ALU.CTL →	33
DATA.WE →	0
regInputMux.CTL →	0
NZP.WE →	0
Privilege.CTL →	2
PCMux.CTL →	1

 

$$(Z|P) ? PC = PC + 1 + (\text{sext}(\text{IMM9}) \text{ offset to } \langle \text{Label} \rangle)$$

0000 011i iiii iiii

## Control Signals: BRzp

rsMux.CTL →	X
rtMux.CTL →	X
rdMux.CTL →	X
regFile.WE →	0
ALUInputMux.CTL →	X
ALU.CTL →	X
DATA.WE →	0
regInputMux.CTL →	X
NZP.WE →	0 (not changing NZP, only using them)
Privilege.CTL →	2
PCMux.CTL →	0 (branch or not branch based on NZP)

# That's all we have for today!

## Reminders:

- TA-lead recitations will take place on
  - Tuesdays 6:30-8:00pm in Moore 100A
  - Wednesday 12:00-1:30pm in Moore 100C
- Check the course website for OH times