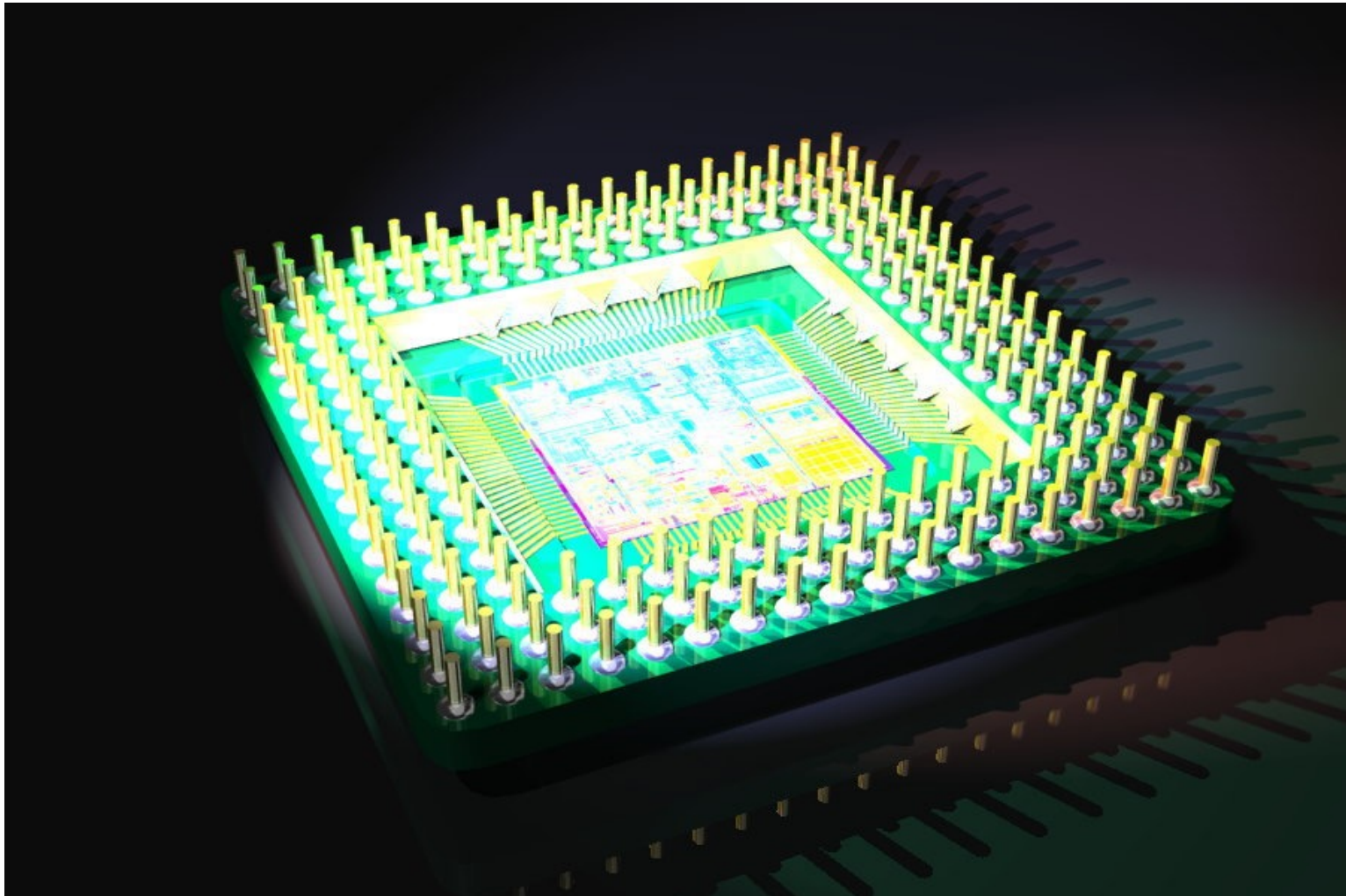


Chapter 3 (Part 0)


Transistors & Gates

Based on slides © McGraw-Hill
Additional material © 2004/2005/2006 Lewis/Martin
Additional material © 2008 Roth
Additional material © 2010 Taylor
Additional material © 2013 Farmer

Inside a microprocessor



Transistor: Building Block of Computers

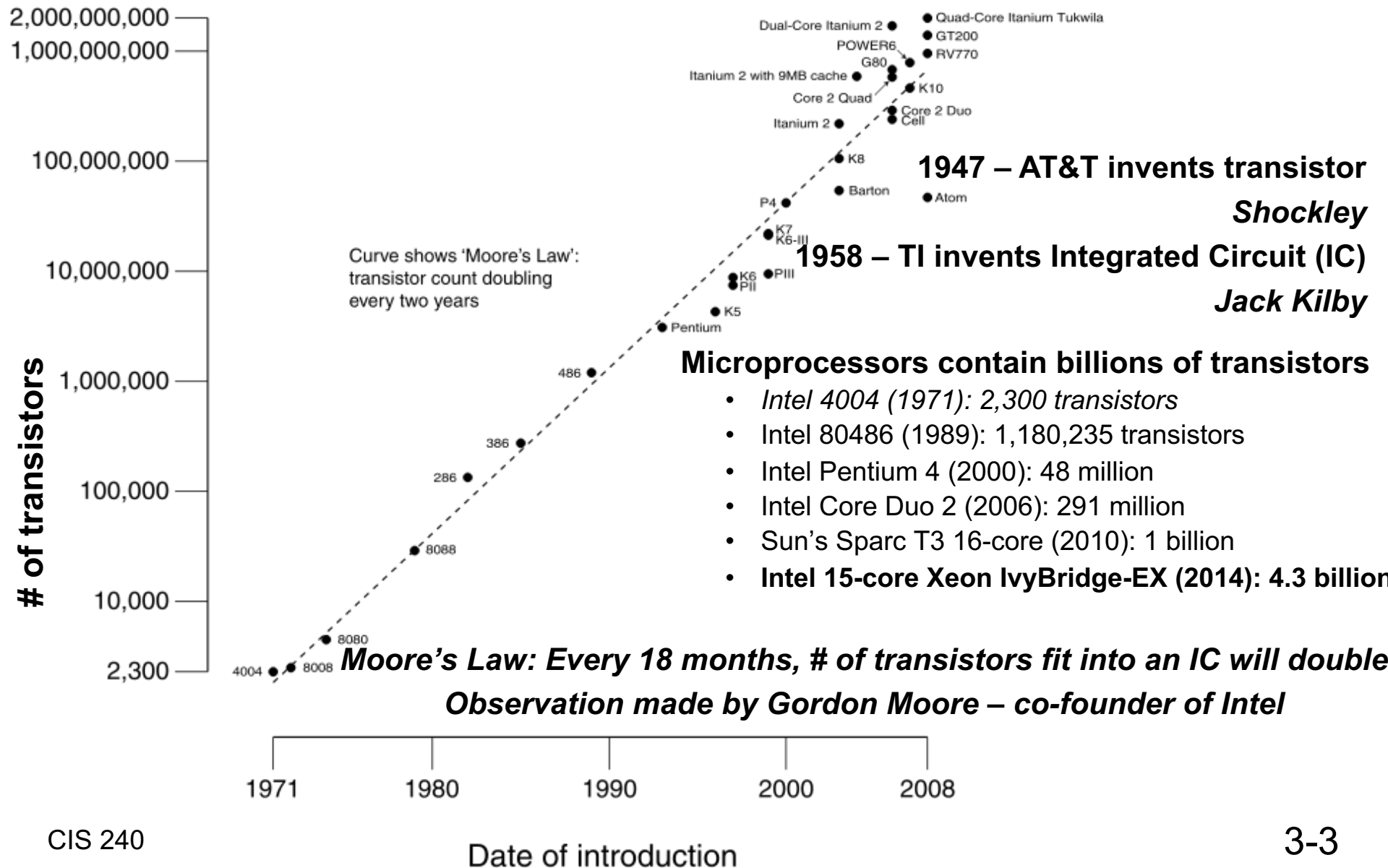


Transistor: Building Block of Computers

So what exactly is a transistor?

- A semiconductor device used to...
AMPLIFY or SWITCH electronic signals in a circuit
CPUs mostly use the “SWITCH” capability

How does a SWITCH form the basis of a computer?

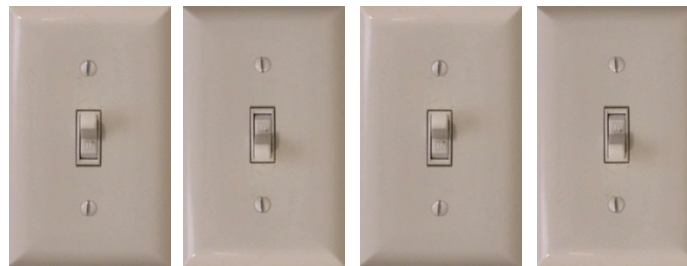- Previously...we introduced “binary digital system”
 - Two symbols: 0 and 1, represents two states
- Switch also represents two states: OFF and ON



ON
1

OFF
0

ON
1

OFF
0

- Combine them to make logic: AND/OR/NOT

CIS 240 • Even higher: adders/mux/decoders, finally CPUs (LC4)

How Does a Computer Represent Data?

At the lowest level, a computer has electronic “plumbing”

- Operates by controlling the flow of electrons

Easy to recognize two conditions

1. Presence of a voltage – we’ll call this state “1”
2. Absence of a voltage – we’ll call this state “0”



Computer use transistors as switches to manipulate bits

- Before transistors: tubes, electro-mechanical relays (pre 1950s)
- Mechanical adders (punch cards, gears) as far back as mid-1600s


How do transistors work?

→ 1st we need a mini-Physics review...

- Electricity corresponds to the flow of charged particles, typically electrons. (see Ben Franklin)
 - Current = flow of charge carried by electrons
 - Voltage = *motivation* for current to flow (potential difference)



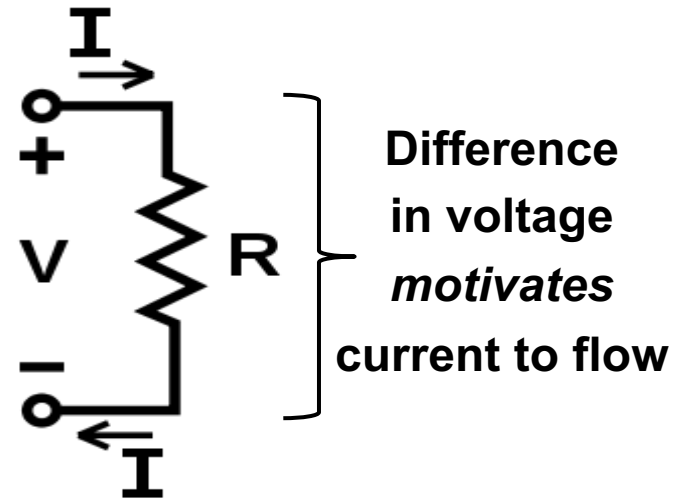Difference
In height
motivates
water to flow



Ohm's Law: $V = IR$

Charge

Atoms contain two types of charged particles, protons in the nucleus and electrons that orbit the nucleus. Their charges are equal magnitude and opposite sign

Charge is measured in Coulombs

The charge of an electron is approximately 1.6×10^{-19} Coulombs

Like charges repel and opposite charges attract

Current

Current refers to the flow of charged particles

Current is measured in Amperes where a 1 Ampere current refers to a flow of one Coulomb of charge per second


Voltage

The potential difference between two points is referred to as voltage it can be defined as the amount of work required to move one Coulomb of charge between the two locations.

Voltage/Current and Electric Field

E-field: produces “voltage difference”

Aka: motivation for charge to flow

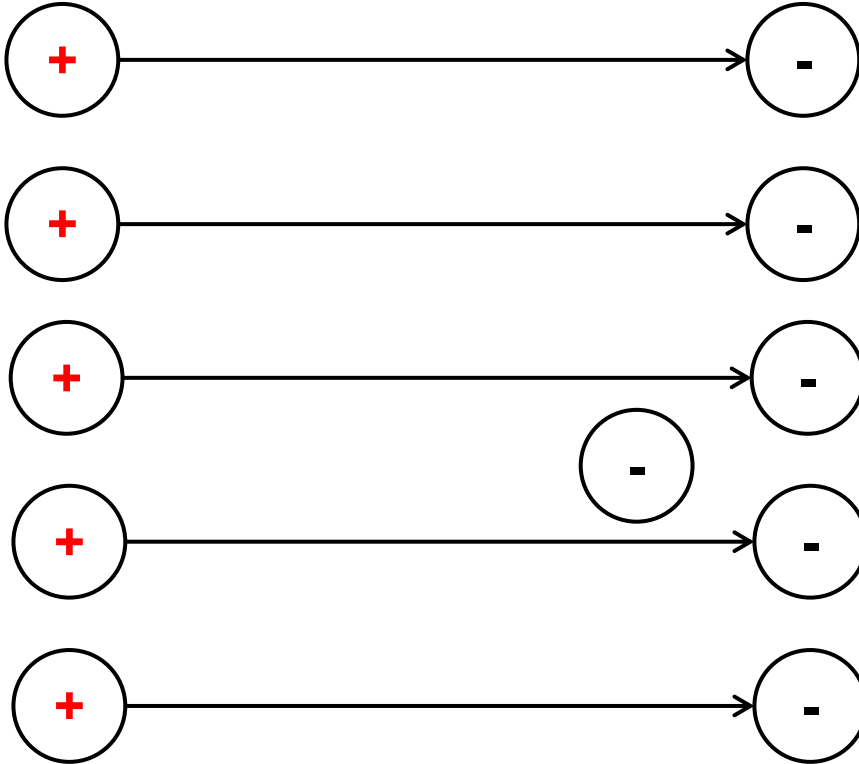


←
Direction of charge carrier (e-)

→
Direction of current

Battery provides voltage

Aka: *voltage difference*

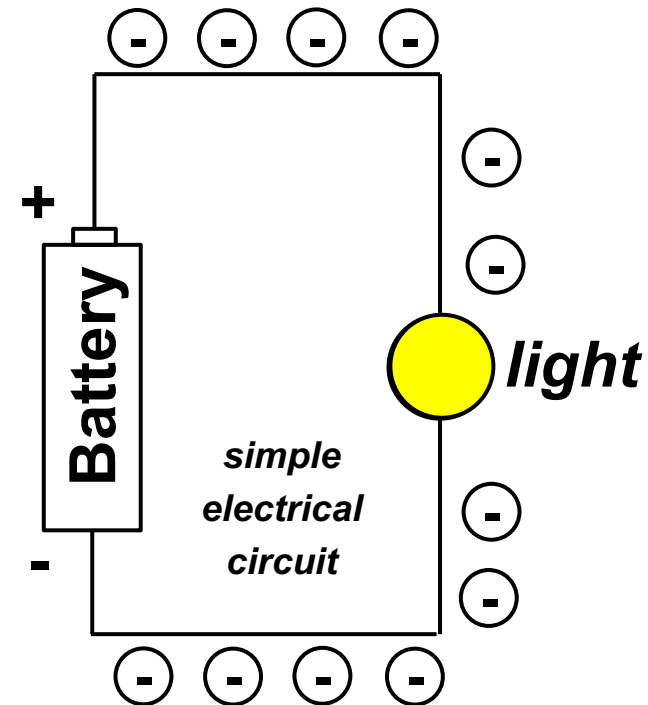


←
Direction of current


Ohm's Law: $V = IR$ 3-12

Switches control flow of current in a circuit

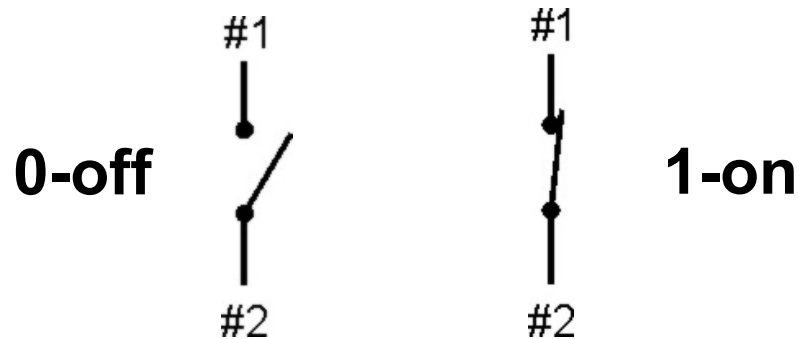- A switch inherently represents two states, on/off




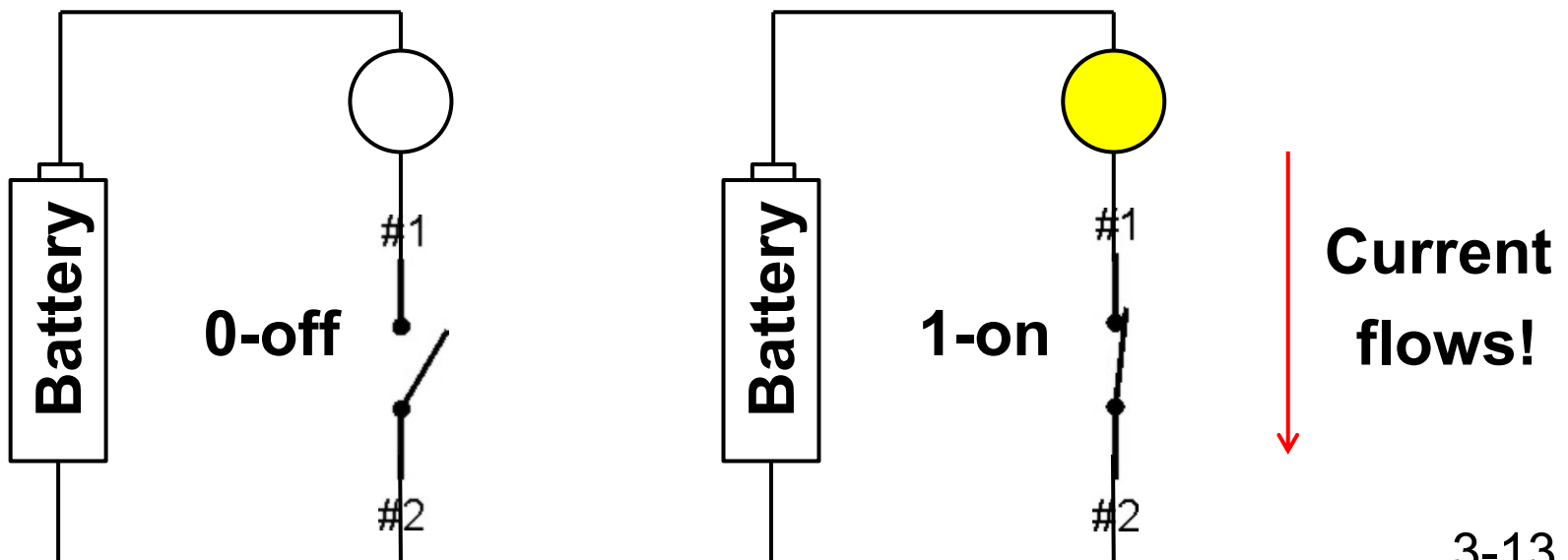- When put in a circuit, can start/stop current flow



Transistor as electronic switch

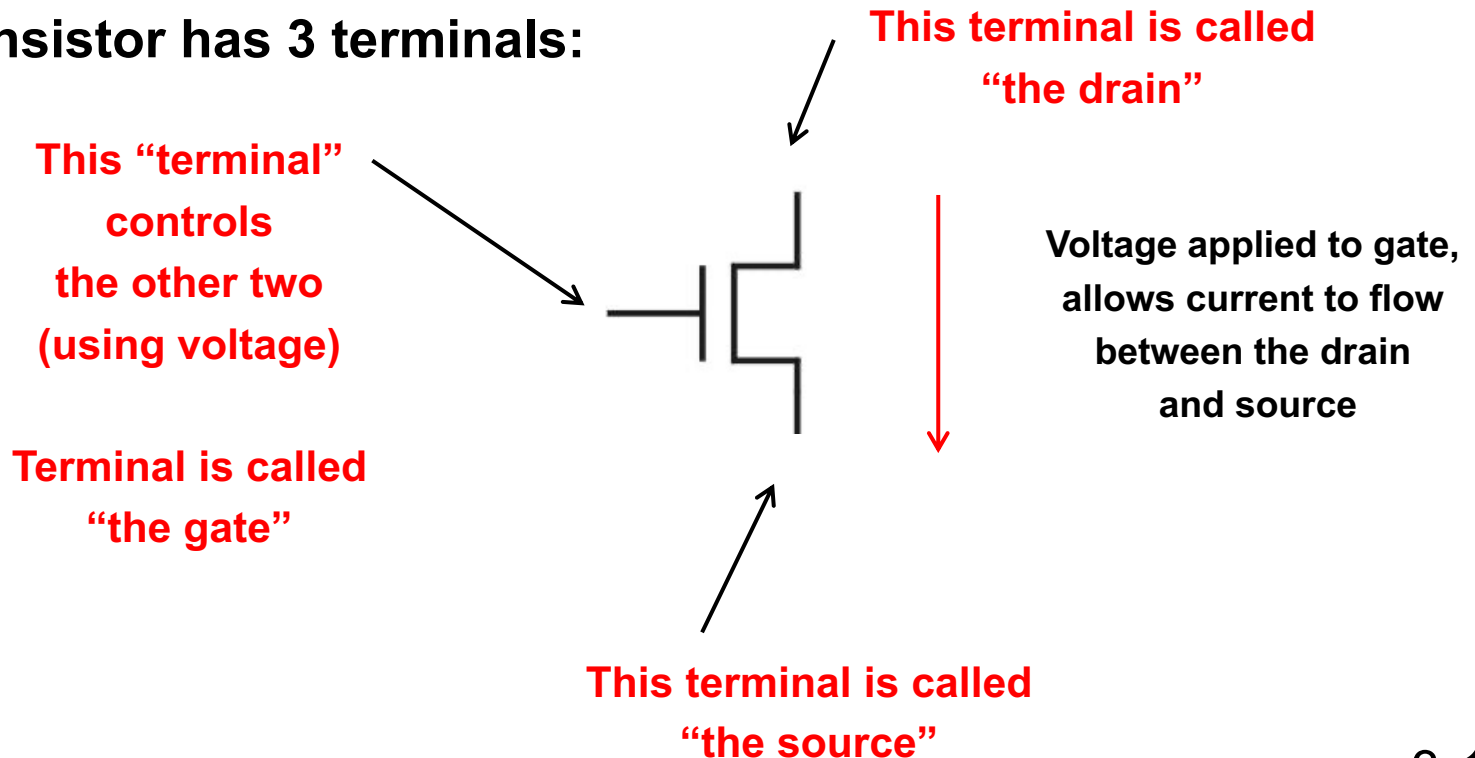- In the last example, someone must manually “flip” the switches to control the “input” to our circuits
- In a computer we need a way to “remotely” flip the switch
 - Transistor offers us this capability
 - We use voltage, to remotely flip the switch
- A transistor has 3 terminals:





How does a transistor work?

Begin at the beginning (*what is it made of ?*)

- Currently transistors are made of Silicon
 - Atomic symbol: Si – atomic number 14
- In its crystalline state, silicon atoms form covalent bonds with four neighbors using their 4 outer electrons
- At room temperature, Silicon is a semiconductor


14	IVA	4A
6	C	Carbon 12.011
14	Si	Silicon 28.0855
32	Ge	Germanium 72.64
50	Sn	Tin 118.71
82	Pb	Lead 207.2
114		

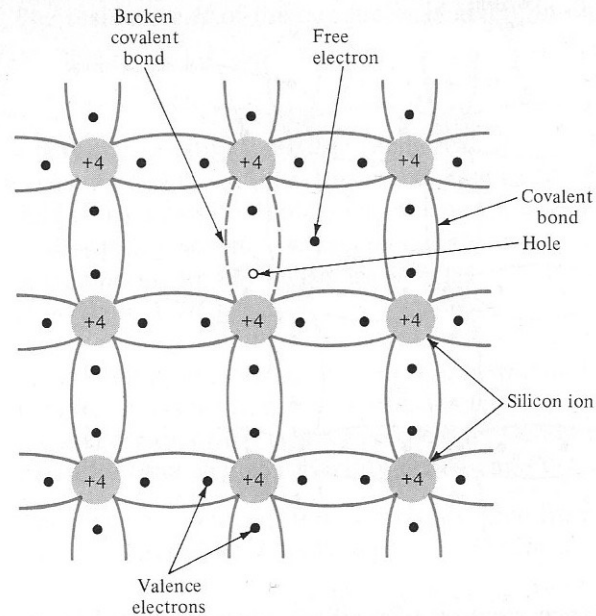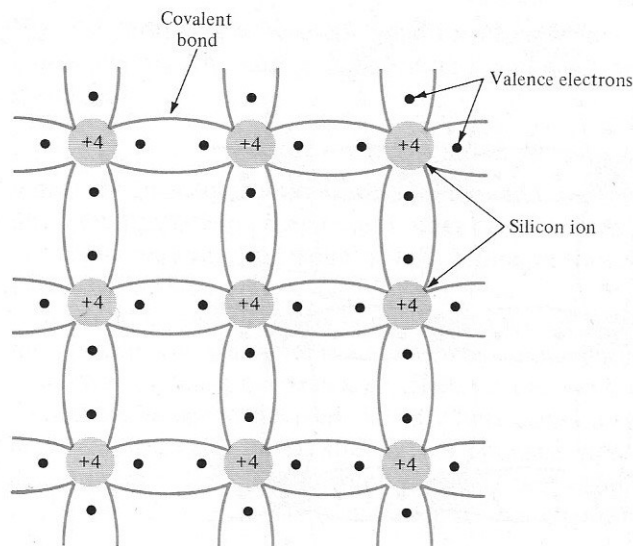

Doping – not what you think

We can improve the conduction of Silicon by doping it with other elements.

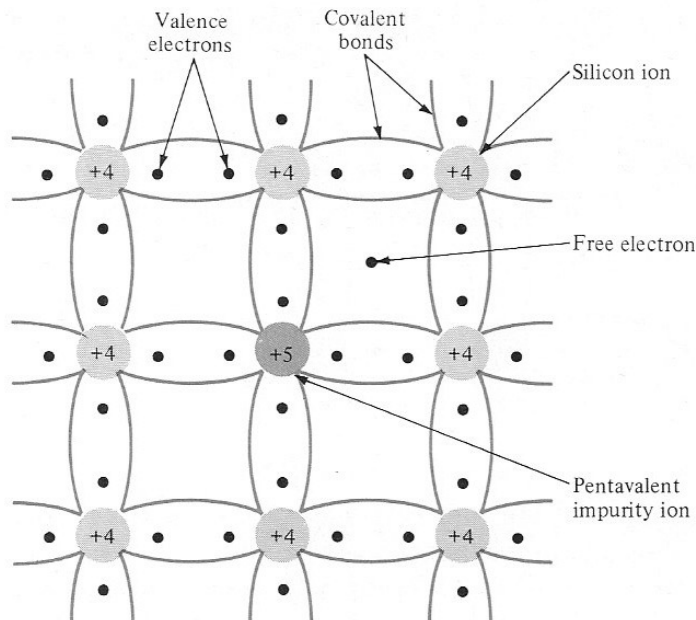
- N-type regions are formed by adding small amounts of elements that have more than 4 electrons in their outer shell and, these extra electrons can serve as charge carriers.
- N-type dopants – antimony (Sb), phosphorus(P), arsenic (As)



13 IIIA 3A	14 IVA 4A	15 VA 5A
5 B Boron 10.811	6 C Carbon 12.011	7 N Nitrogen 14.00674
13 Al Aluminum 26.981539	14 Si Silicon 28.0855	15 P Phosphorus 30.973762
31 Ga Gallium 69.732	32 Ge Germanium 72.64	33 As Arsenic 74.92159
49 In Indium 114.818	50 Sn Tin 118.71	51 Sb Antimony 121.760

P-type doping

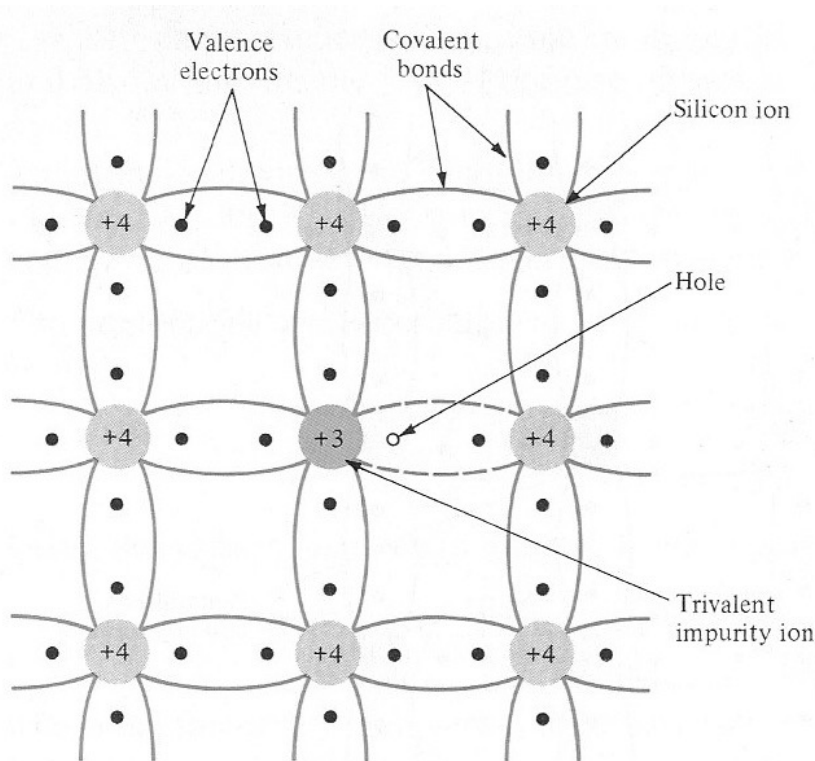- P-type materials are formed by adding elements that have 3 electrons in their outer valence shell.
- These atoms create spaces in the lattice of covalent bonds into which electrons can flow.
- P-type dopants : boron (B), gallium (Ga), indium (In)



13 IIIA 3A	14 IVA 4A	15 VA 5A
5 B Boron 10.811	6 C Carbon 12.011	7 N Nitrogen 14.00674
13 Al Aluminum 26.981539	14 Si Silicon 28.0855	15 P Phosphorus 30.973762
31 Ga Gallium 69.732	32 Ge Germanium 72.64	33 As Arsenic 74.92159
49 In Indium 114.818	50 Sn Tin 118.71	51 Sb Antimony 121.760

Bottom Line

- **N-type materials are good semiconductors because they have extra electrons which are negatively charged and can be used to carry a current.**
- **P-type materials are good semiconductors because they have extra spaces into which electrons can move. These 'holes' can be thought of as positive charge carriers.**

LET'S MAKE A DIODE

Review so far...

Our goal is to make an electronic “switch” (a transistor)

- **A device that will allow us to control the flow of current in a circuit**

Doping:


- **Add an “impurity” to silicon (our semiconductor)...**
...to make it a better conductor of current
 - **nType – Impurity added, adds extra “electrons” to silicon**
 - **pType – Impurity added, takes away electrons, making “holes”**

How we’ll do this:


- **Use nType and pType Silicon to create a device that controls the direction of current flow in a circuit (like a one-way valve)**
- **Next, we’ll configure our valve and add a lever (gate) to it**
 - **So we can turn current flow on/off in a circuit**
 - **Then we’ll have a transistor!**

A Diode (a pn-junction)

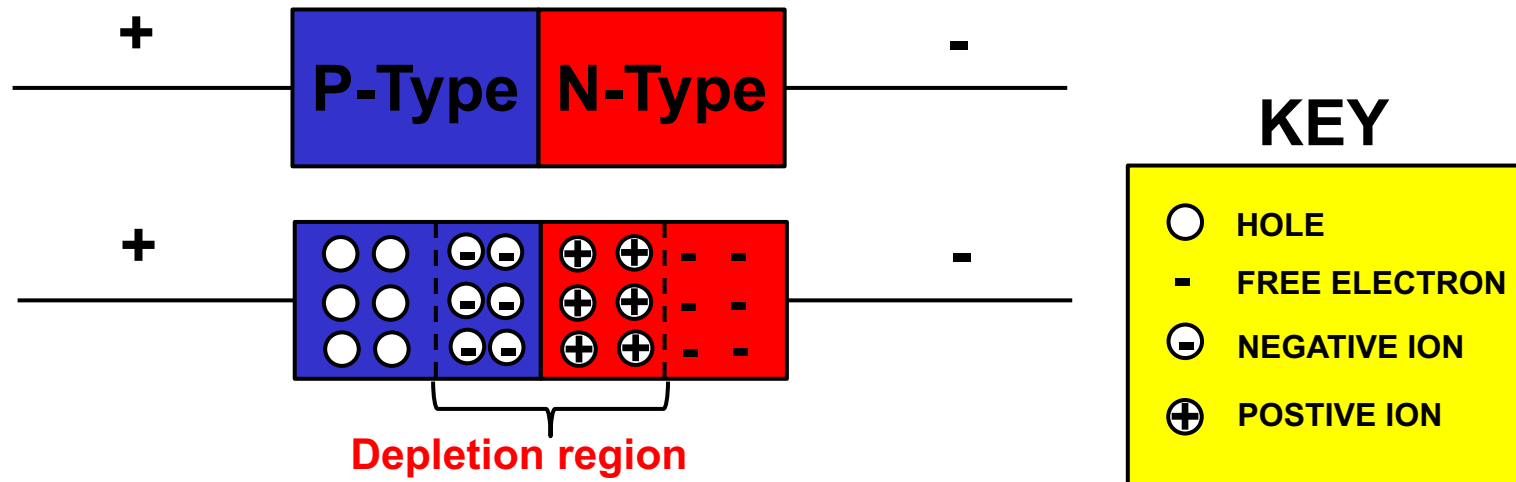- A union of P-type and N-type materials
- Functions as a one-way “valve” in an electric circuit
- Only allows current to flow in one direction




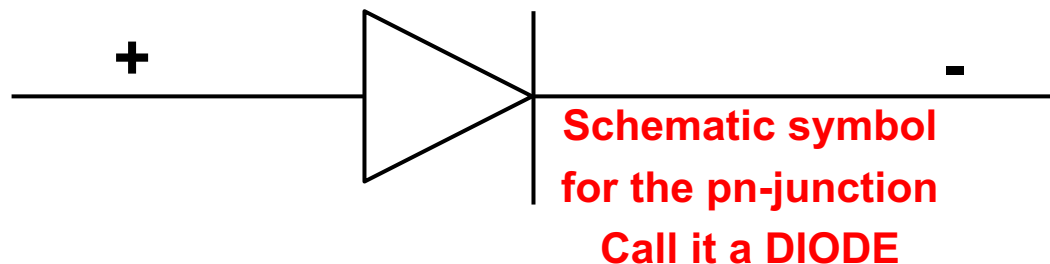PN Junction reaches “equilibrium” setting up an E-field that stops flow of additional electrons across the junction



A Diode (a pn-junction)

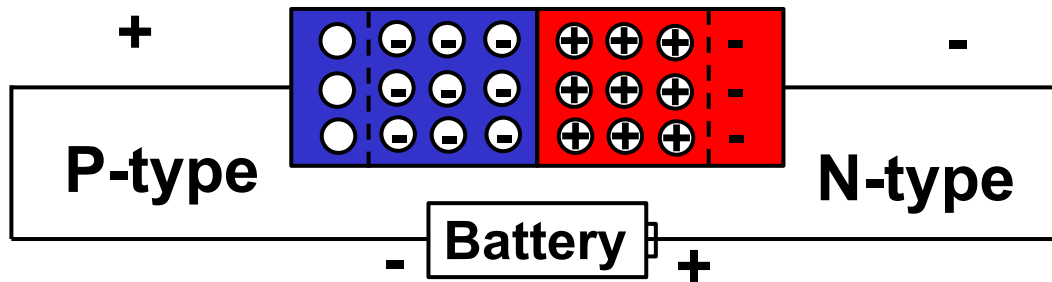
- Reverse bias (battery against the +/- terminal of diode):
 - Depletion region gets bigger (E-field gets stronger)
 - reduces/stops flow of current from + to -
 - Impedes flow of electrons through junction



KEY

○	HOLE
-	FREE ELECTRON
⊖	NEGATIVE ION
⊕	POSTIVE ION

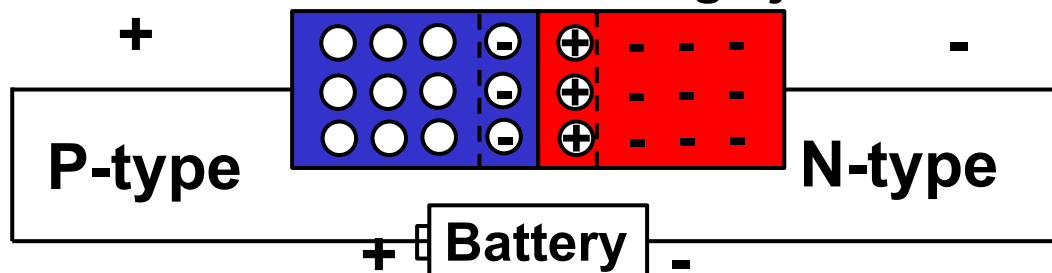- Forward bias:
 - Depletion region gets smaller (E-field shrinks)
 - Allows current to flow from + to -
 - Allows flow of electrons through junction




*A diode is
Like a 1-way valve
Only lets current
In 1 direction in a
circuit*

LET'S MAKE A TRANSISTOR


Next up...the MOSFET (your 1st Transistor!)

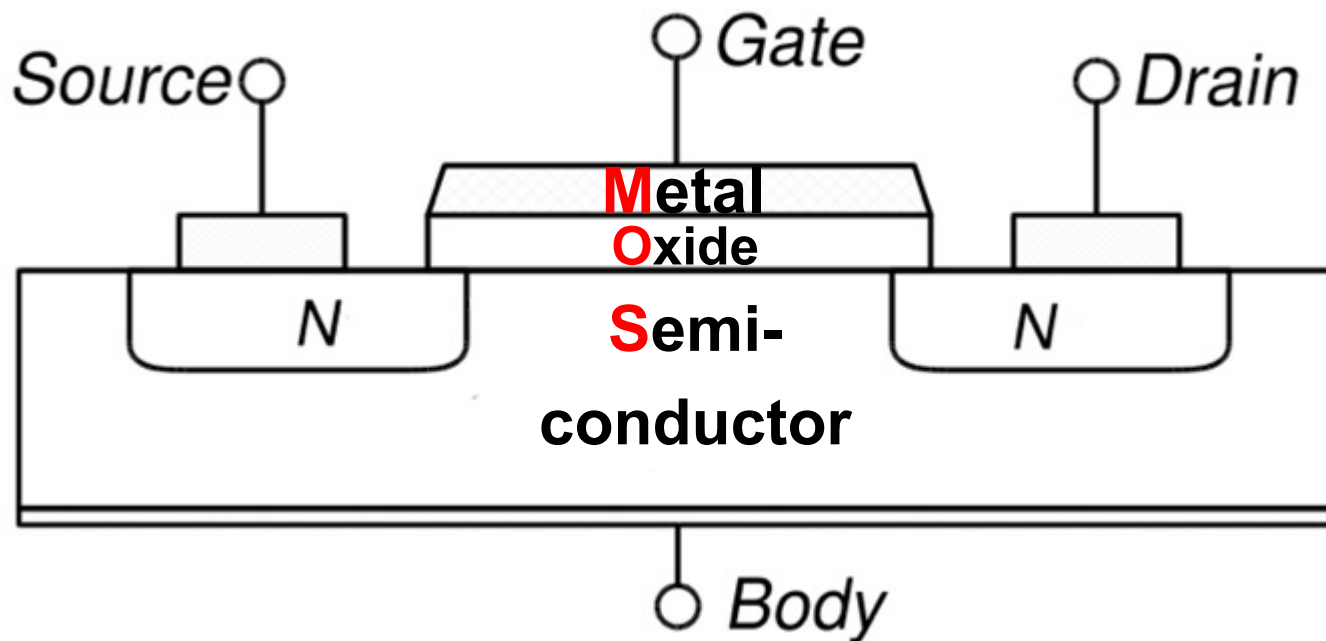- **MOSFET** : **Metal Oxide Semiconductor Field Effect Transistor**
- Picture shows a cross section of such a device.
- Notice it has 4 electrical terminals: **Source/Drain/Gate/Body**




Next up...the MOSFET (your 1st Transistor!)

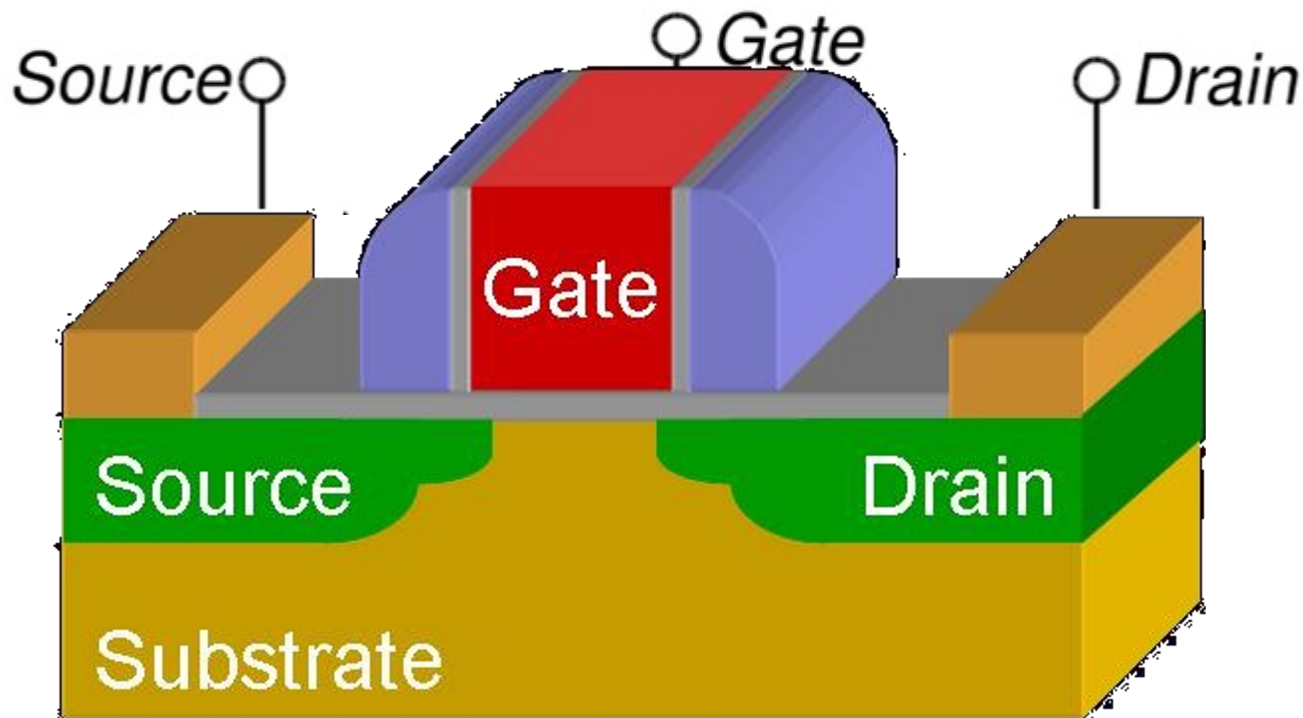- MOSFET : **Metal Oxide Semiconductor Field Effect Transistor**
- Picture shows a cross section of such a device.
- Notice it has 4 electrical terminals: **Source/Drain/Gate/Body**




How we want it to work...

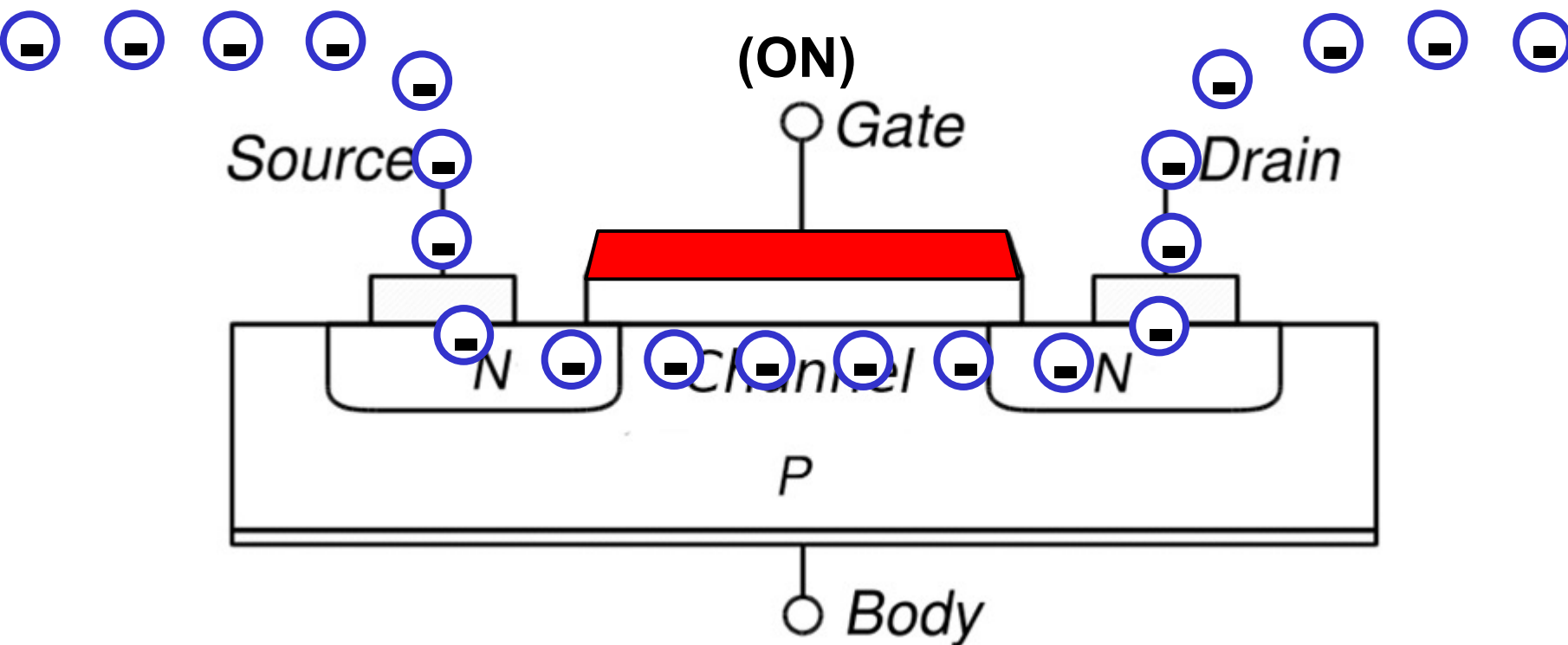- Goal: Pass current through this device (from drain to source)
 - BUT we want to control that current (using the gate terminal)
 - If GATE is ON
 - electrons pass from source to drain through channel




How we want it to work...

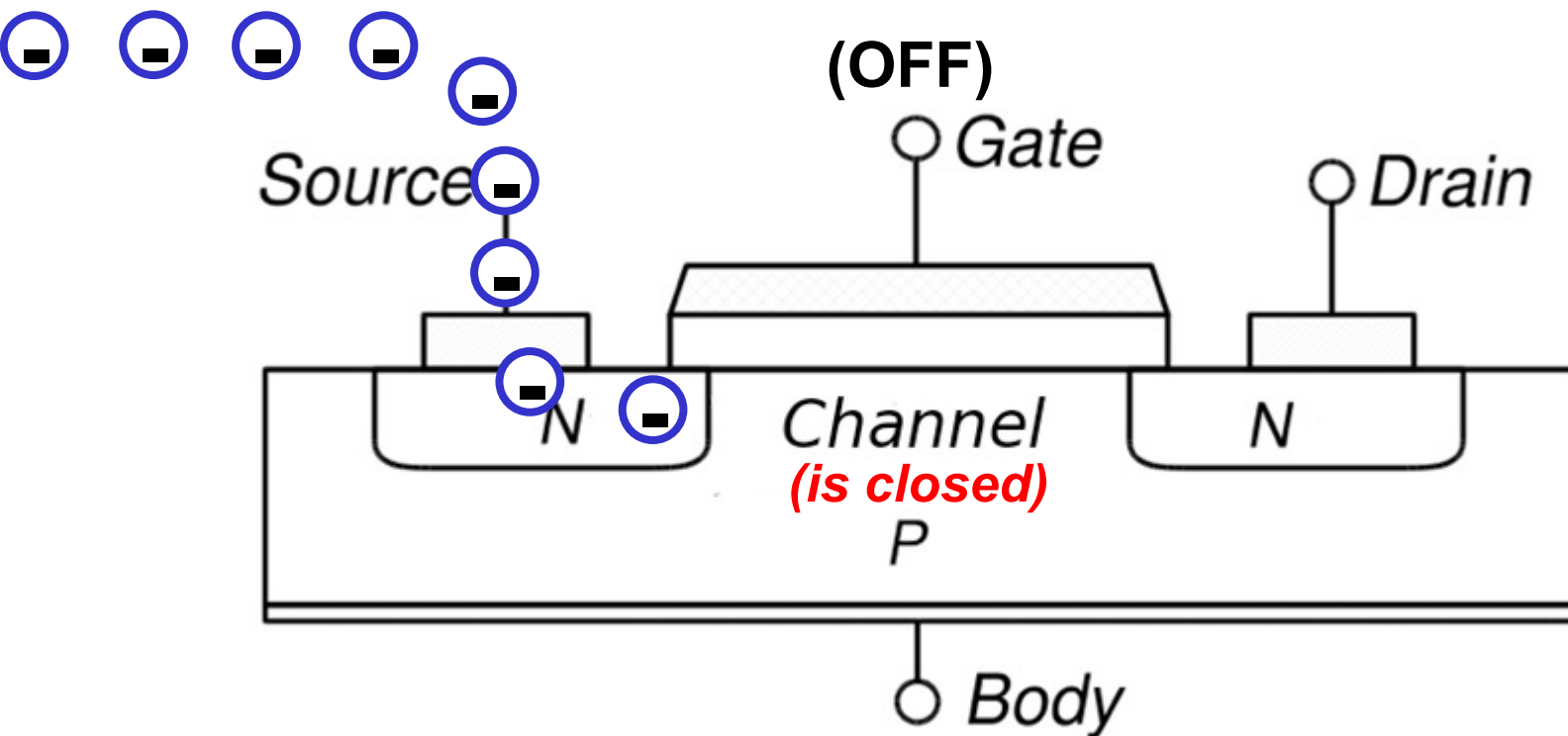- Goal: Pass current through this device (from drain to source)
 - BUT we want to control that current (using the gate terminal)
 - If GATE is OFF
 - electrons cannot pass through channel




How we achieve this behavior...

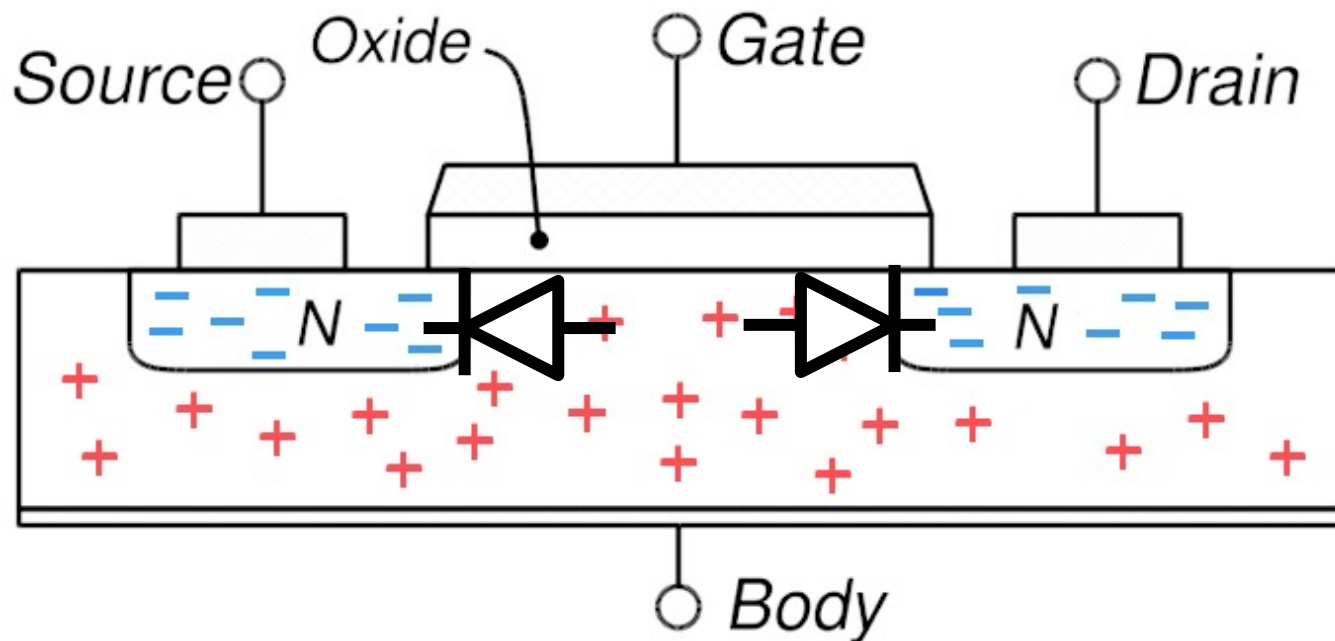- At “rest” we have (closed state)
 - 2 n-type spots (source/drain)
 - 1 p-type spot (channel region)
 - 2 back-to-back p-n junction diodes!
 - Halts flow of electrons through channel (channel doesn't exist!)




How we achieve this behavior...

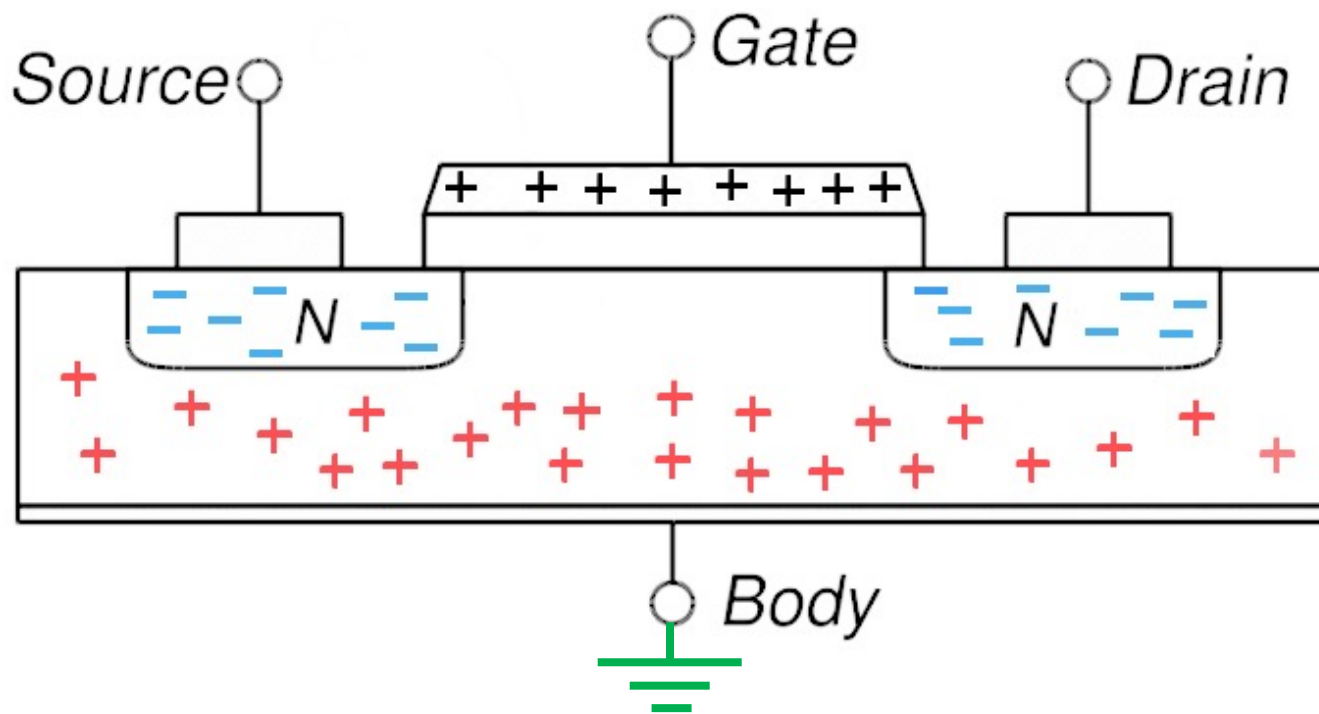- If we wish to turn device on:
 - We apply a “positive” voltage to GATE with respect to BODY
 - This positive voltage “repels” holes from under the gate
 - “depletes” the future channel region of all its holes




How we achieve this behavior...

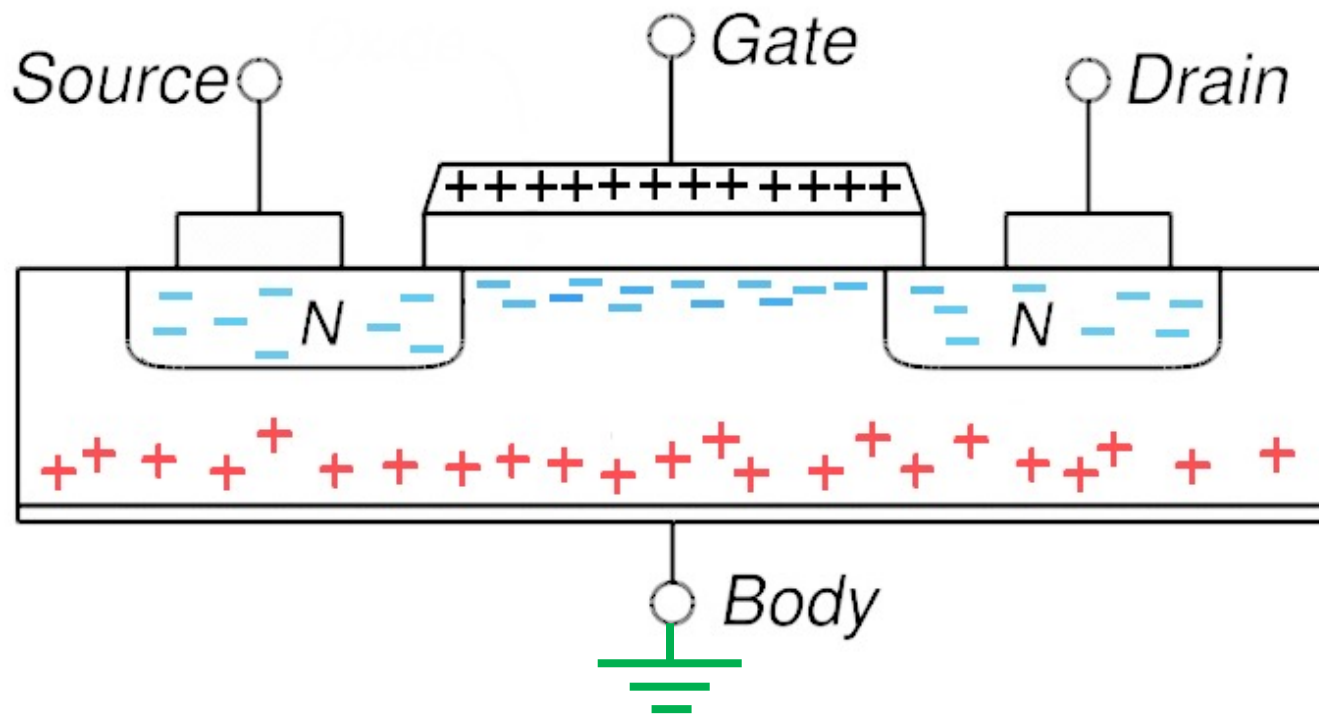- If we go further:
 - Apply a “very positive” voltage to the gate
 - Begins to attract electrons (from source & drain)
 - The channel region has been “inverted”
 - Connects (electrically) source and drain, so current can flow!




Two types of MOSFETs: nMOSFET and pMOSFET

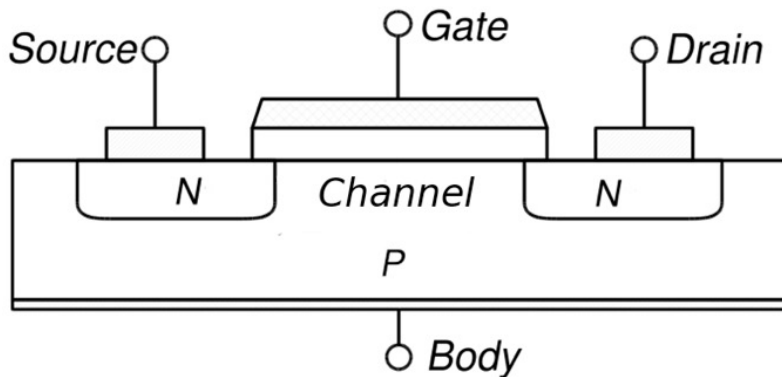- nMOSFET (nMOS): channel carries negative charges (electrons)
- pMOSFET (pMOS): channel carries positive charges (holes)




nMOSFET

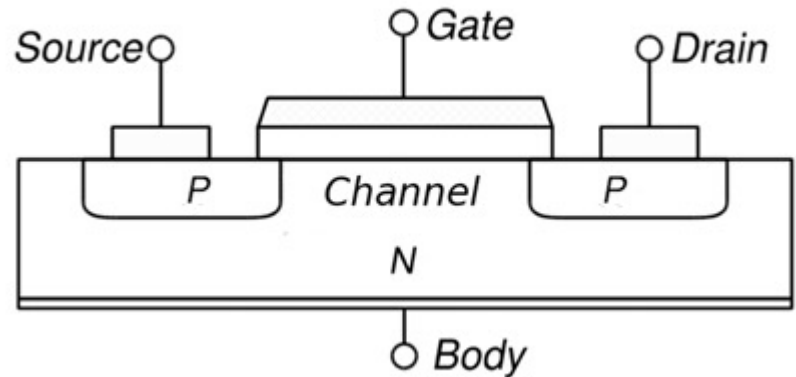


pMOSFET

Two types of MOSFETs: nMOSFET and pMOSFET

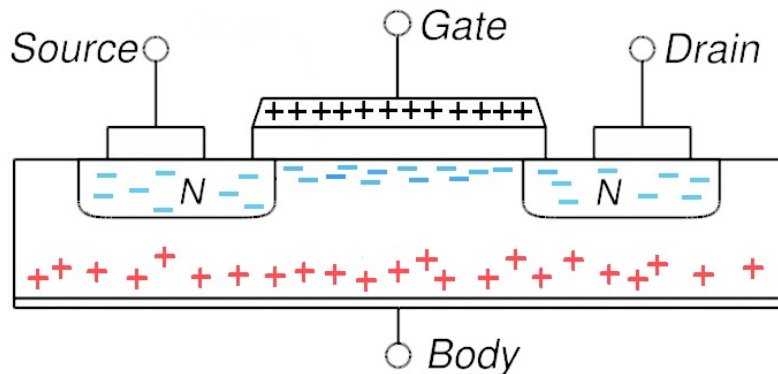- nMOSFET (nMOS): channel carries negative charges (electrons)
 - **GATE Voltage MUST BE $>$ Body, Source, Drain to be ON**
- pMOSFET (pMOS): channel carries positive charges (holes)
 - **GATE Voltage MUST BE $<$ Body, Source, Drain to be ON**




nMOSFET

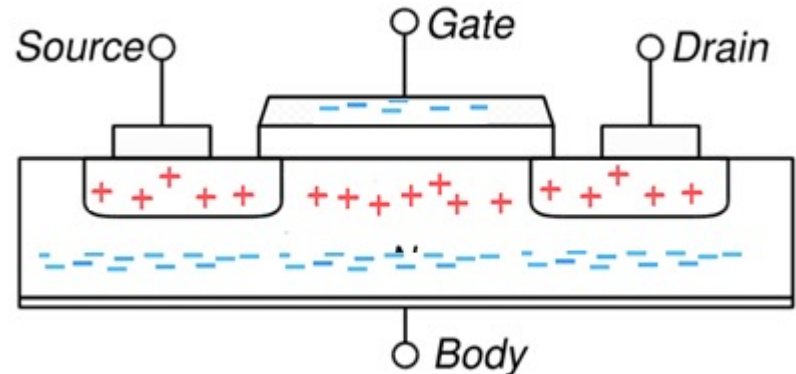


pMOSFET

Transistor Symbols

 - The circuit symbols for nmos and pmos transistors are shown below.



NMOS Transistor Symbol

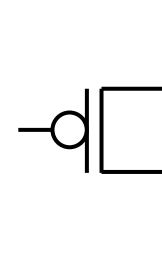


PMOS Transistor Symbol

TRANSISTORS TO LOGIC GATES

Transistor to logic device: GATE

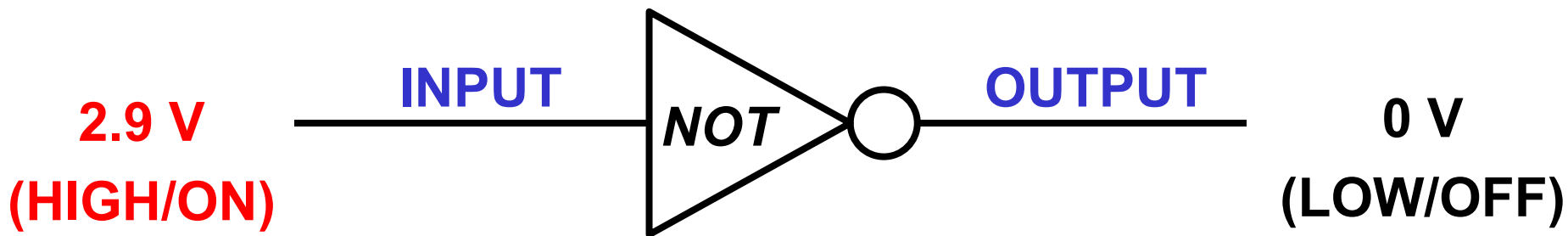Our first logic device will be an inverter:




Logical Behavior: “inverts” the incoming signal:

- Input: LOW-> output: **HIGH**
- Input: **HIGH**->output: LOW

INPUT	OUTPUT
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)

Truth Table
All possible
Combinations
Of inputs

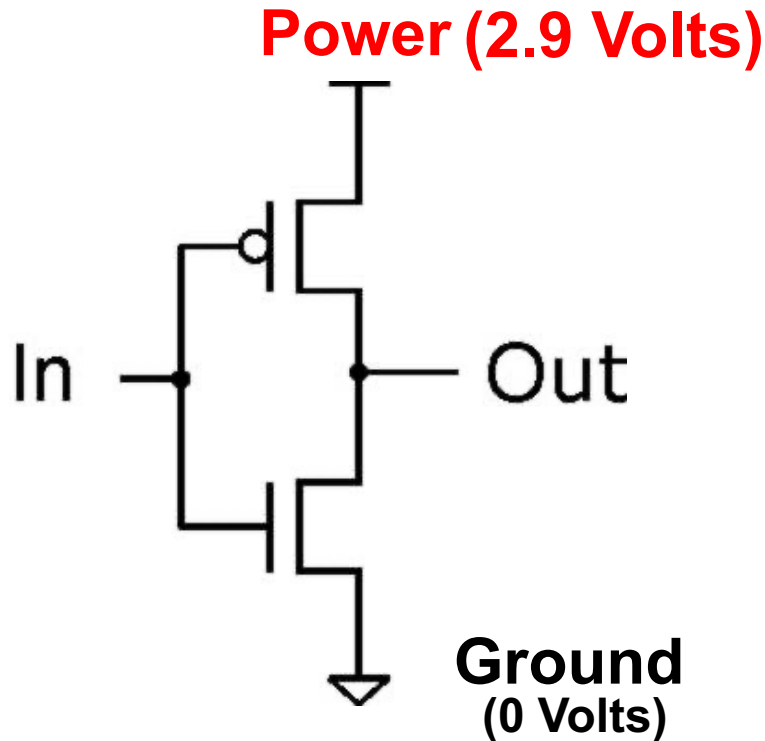How do we configure transistors to make inverter?





We take advantage of opposing nature!

-Setting $IN = 0V$ (LOW=Logic 0)


nMOS turns OFF

pMOS turns ON, connects OUT to Power

OUT=2.9V (HIGH=Logic 1 – inverse of In)

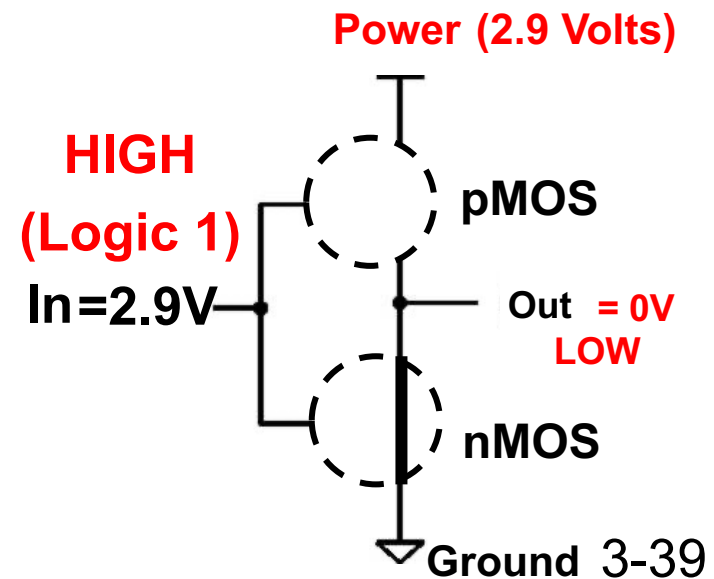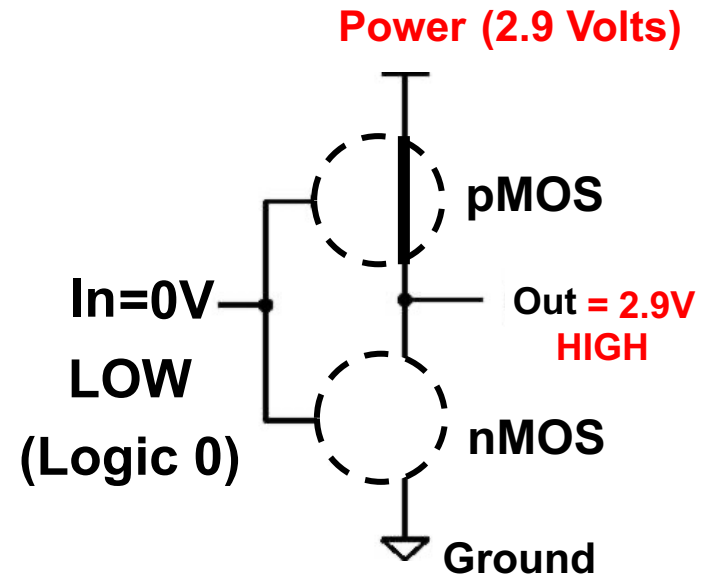

This configuration is called: CMOS

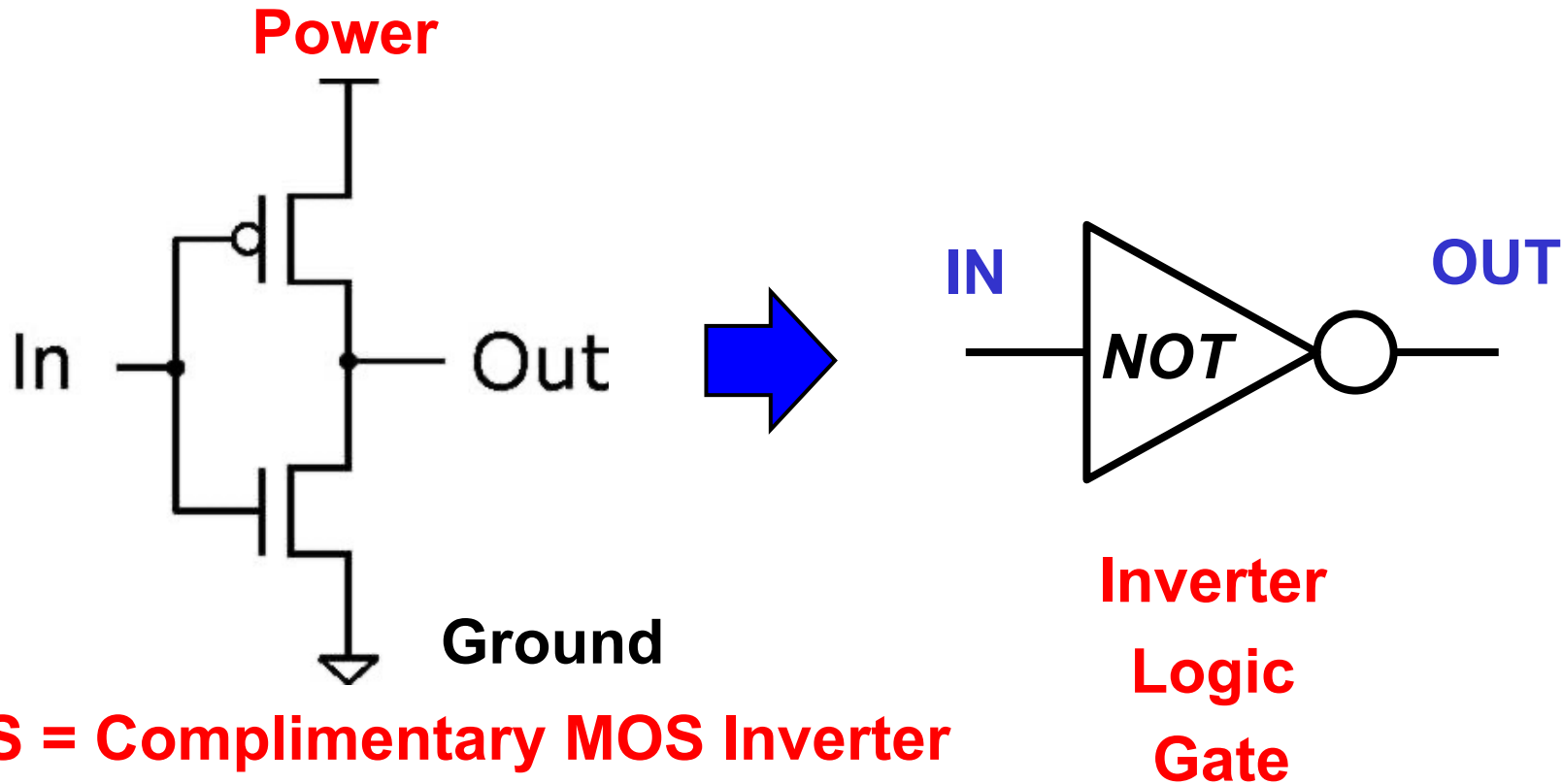

CMOS = Complimentary MOS Inverter


We have “jumped up” 1 level of abstraction

--From transistors to “gate”

--Technology inside the gate (CMOS here) isn't as crucial as its behavior

--could be: transistors, vacuum tubes, biological device, etc.

Side View of Transistors in CMOS process

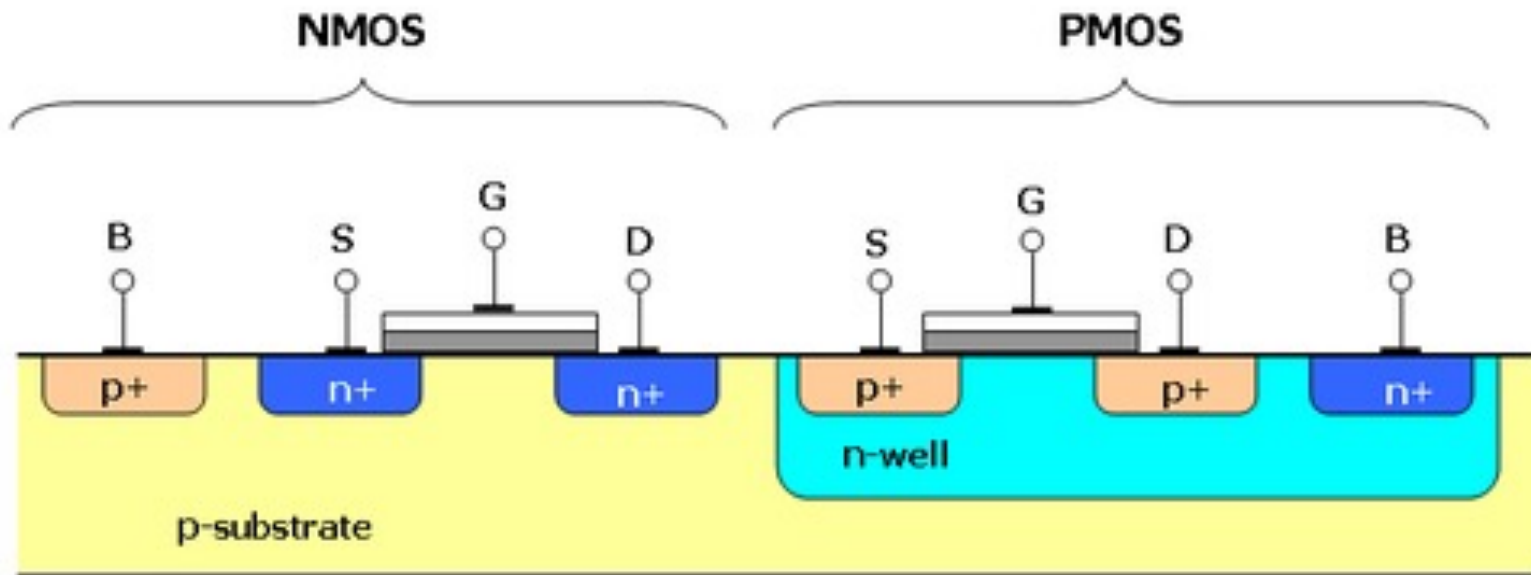

We can use the same silicon to create both types of transistors!

--The same “p-type” substrate is used to hold both NMOS/PMOS




--NMOS devices can be created right in the p-type substrate

--When a PMOS device is needed, we create an n-type *WELL*


--PMOS devices then have their own n-type “body”

--Notice the body terminal on each transistor

3-D View of CMOS Inverter in Silicon

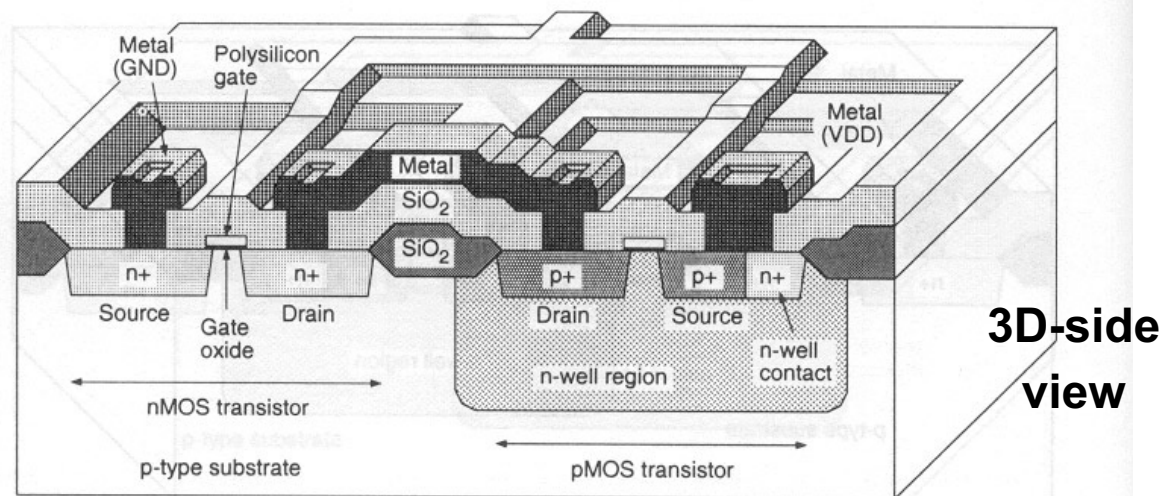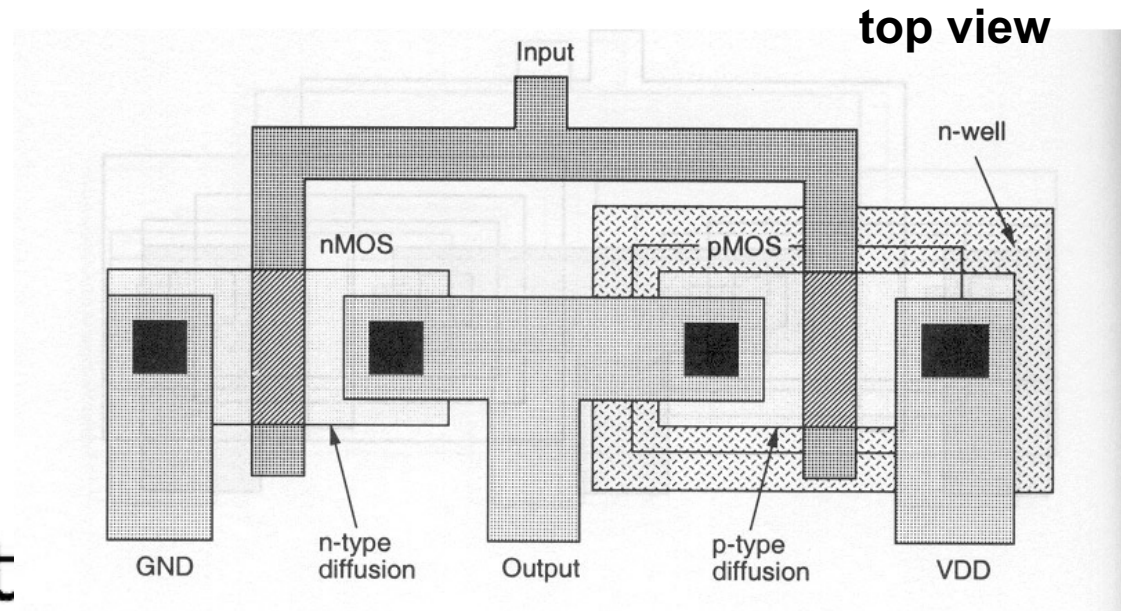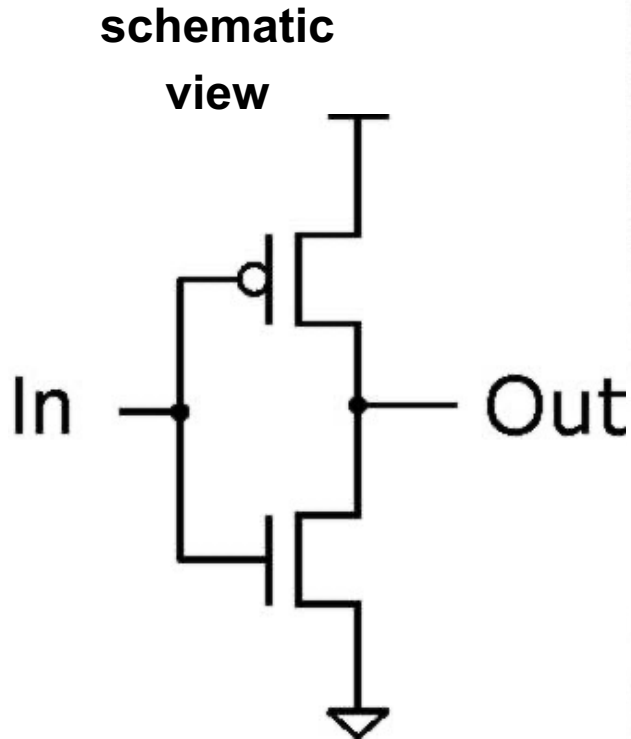

3-D of larger CMOS circuits

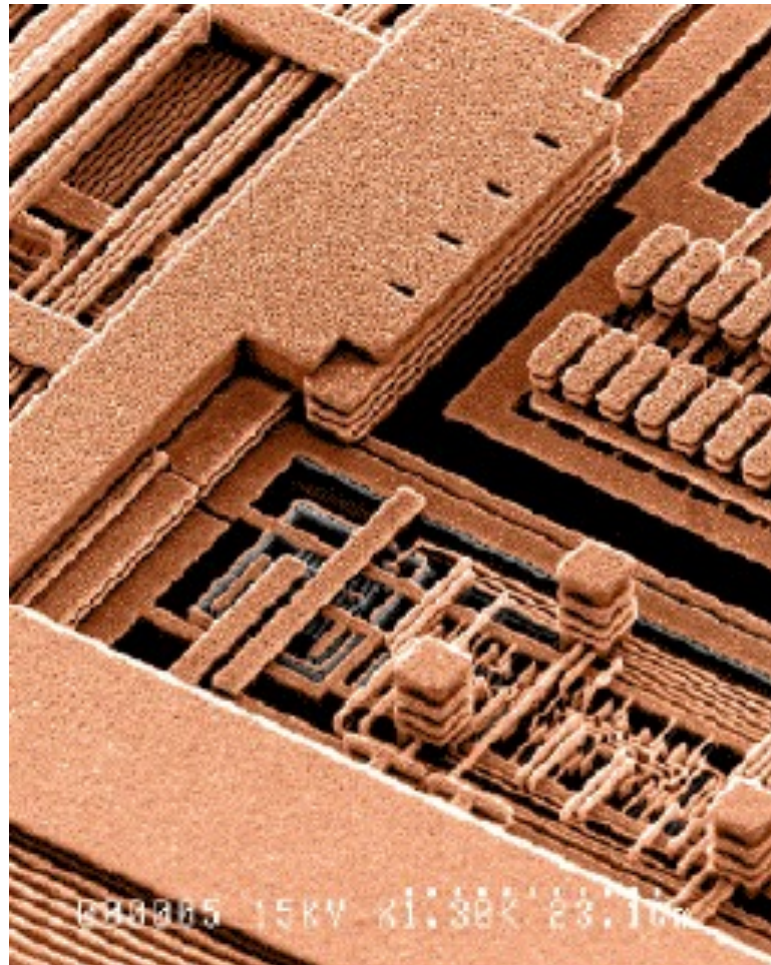

This is an SEM photo

**shows all the metal
Interconnections
On an IC**

**pMOS/nMOS are at
the very bottom**

An idea of scale

The Intel Skylake chip uses transistors that are 60 times smaller than the wavelength of light.

Skylake transistor size 14nm. Wavelength of visible light 400-700nm

An idea of scale

There are now more transistors at work in the world (15 quintillion : 15,000,000,000,000,000,000) than there are leaves on all the trees in the world

(The Perfectionists, Simon Winchester)


Limitations on CMOS transistors

- **In a digital circuit there are only two relevant voltage levels, the low voltage level, GND (0), and the high voltage level, Vdd (1).**
- **An nmos transistor is only ON when the gate voltage is higher than the source and drain voltages**
- **A pmos transistor is only ON when the gate voltage is lower than the source and drain voltages**
- **As a consequence an nmos transistor can only be used to pass a low voltage and a pmos transistor can only be used to pass a high voltage**


nMOS transistor is only on if the gate voltage is higher than the source and the drain voltages



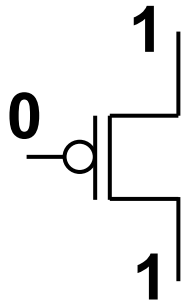
pMOS transistor is only on if the gate voltage is lower than the source and the drain voltages




Transistor ON

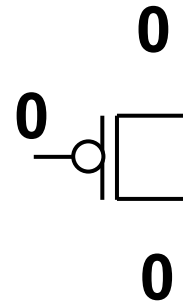

Transistor OFF

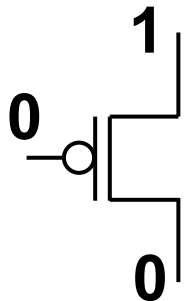

Transistor OFF

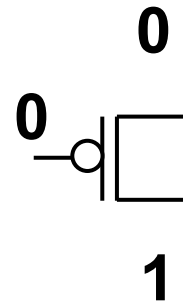


Transistor OFF

Bottom Line

- nMOS transistors can be used in switching circuits to connect circuit points to the low voltage level – GND (0). These are referred to as **Pull Down Networks**
- pMOS transistors can be used in switching circuits to connect circuit points to the high voltage level – VDD (1). These are referred to as **Pull Up Networks**

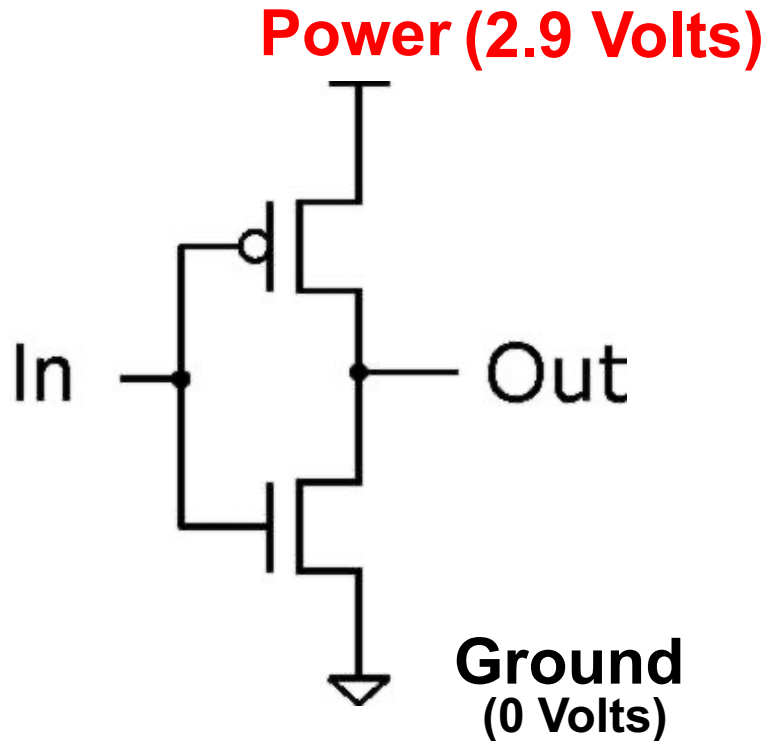How do we configure transistors to make inverter?





We take advantage of opposing nature!

-Setting $IN = 0V$ (LOW=Logic 0)

nMOS turns OFF


pMOS turns ON, connects OUT to Power

OUT=2.9V (HIGH=Logic 1 – inverse of In)

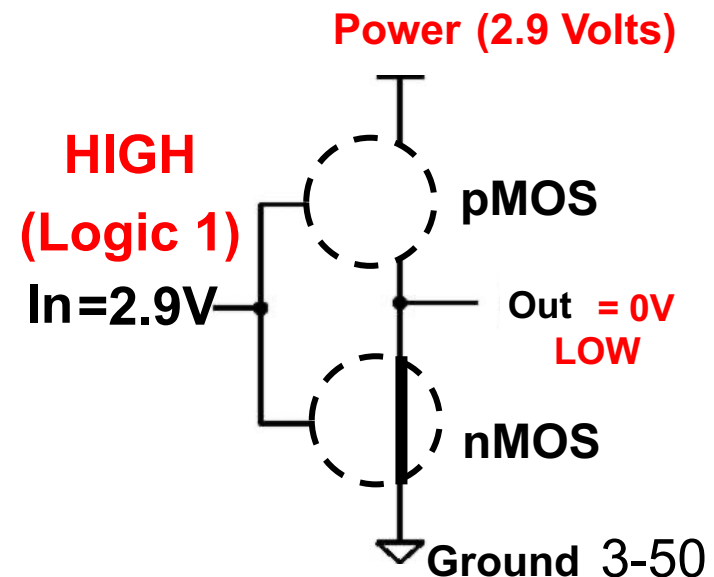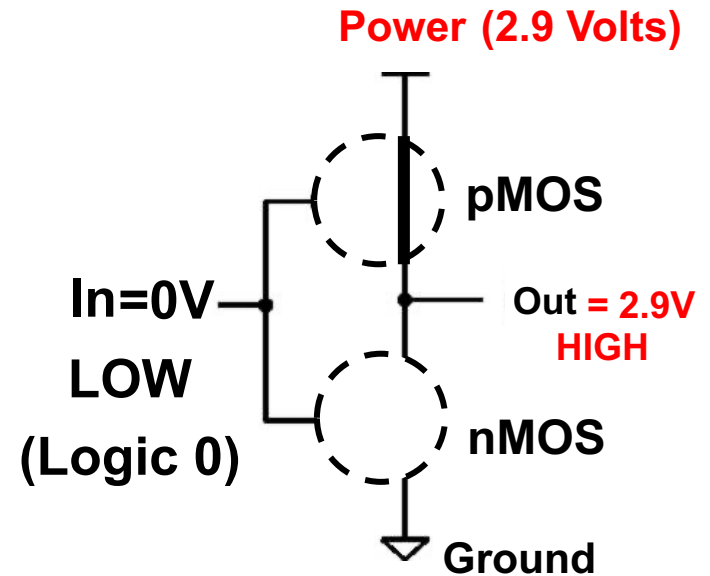

Our next “Gate”...the NAND gate

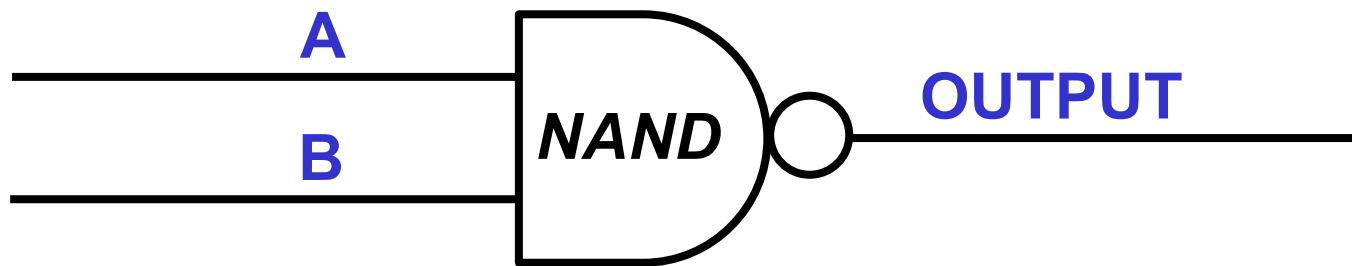We introduce a 2-input (1-output) gate called: NAND



It is an AND gate with its output INVERTED

A	B	OUT
0 (LOW)	0 (LOW)	HIGH (1)
0 (LOW)	1 (HIGH)	HIGH (1)
1 (HIGH)	0 (LOW)	HIGH (1)
1 (HIGH)	1 (HIGH)	LOW (0)

*Truth Table shows all possible combinations
Of inputs and effect on the output*

Logic Function:

OUT=NOT (A AND B)



OUT= $\neg(A \wedge B)$

OUT=(AB)'

OUT= \overline{AB}

*Different notation, but all identical
With function, we can calculate output*

NAND Gate (NOT-AND)

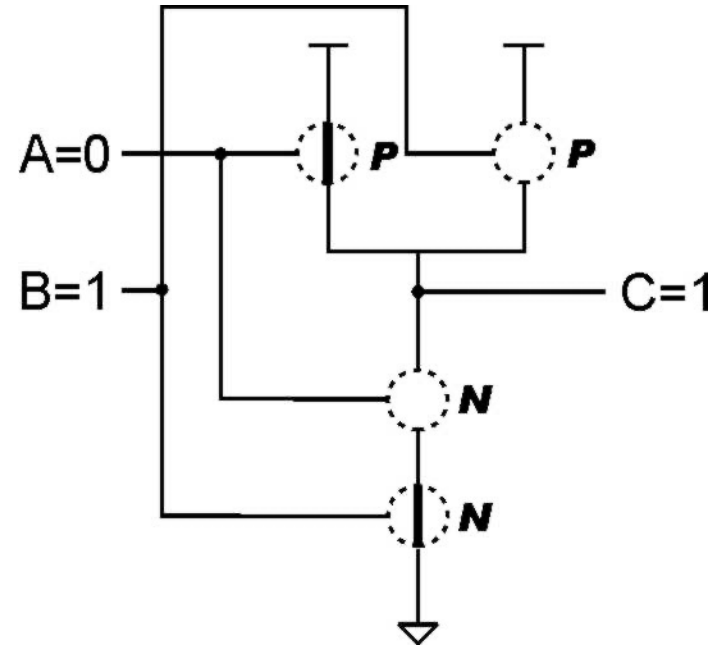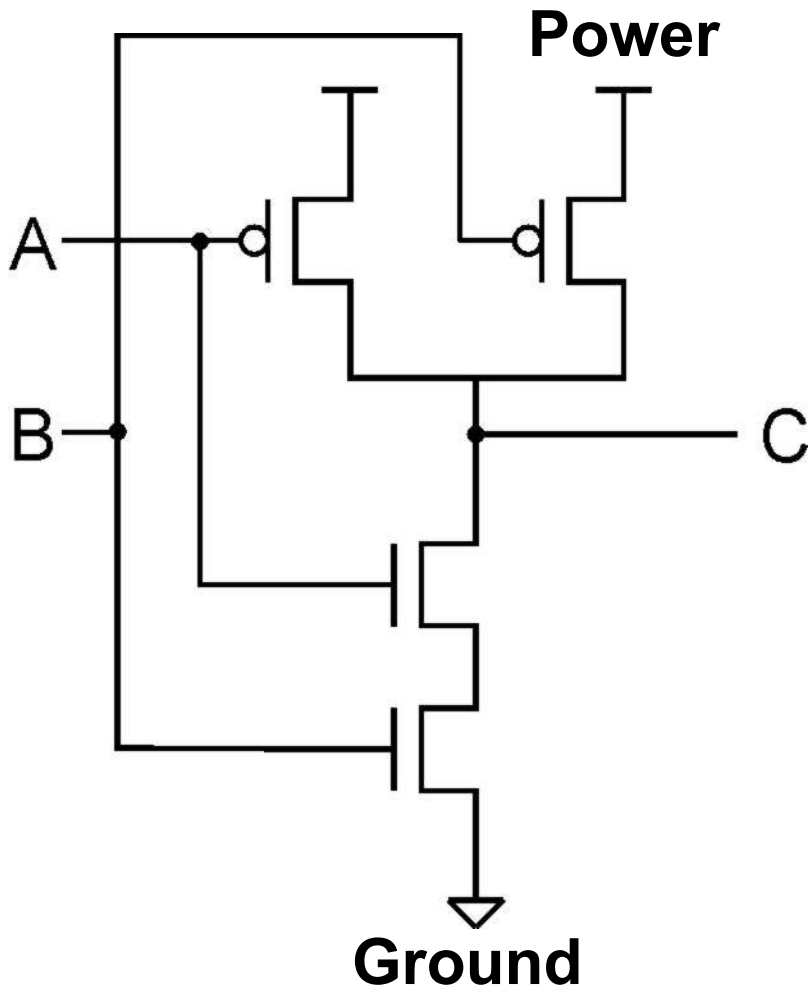

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0