

Sequential Logic

Latches, Flip Flop, Gate Delays, Clock, Timing

CIS 2400 Recitation 3



Recitation Outline

- Latches
- Clock
- Flip Flops

Latches

SR Latch

  
- Provides us a way to store a bit value (Q), used as memory
- Can store & change value with two inputs: S and R



S	R	Effect
0	0	BAD???
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Stable

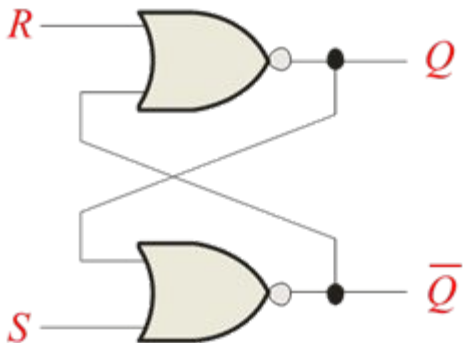Exercise: RS Latch?


- How does the behavior change if we cross-couple NOR gates instead?



S	R	Effect
0	0	Stable
0	1	$Q = 0$
1	0	$Q = 1$
1	1	Invalid


D Latch

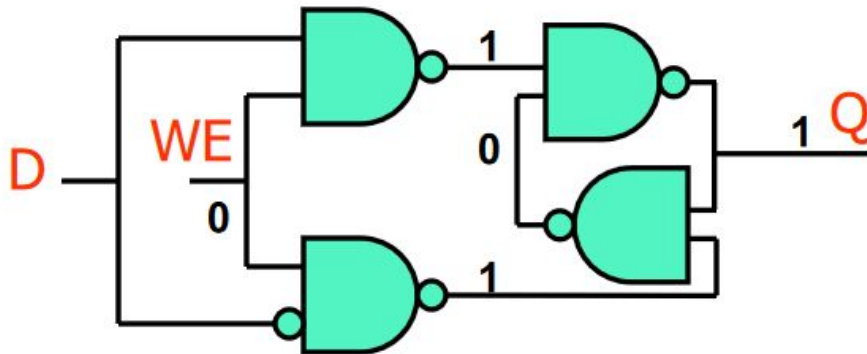- ❖ Goal: Make the RS latch understandable
 - Replace R and S with D, add WE for utility
- ❖ D the data we want to store (either 1 or 0)
- ❖ WE, whether writing (storing that bit) is enabled.
 - If not enabled, Q (the stored data) maintains current value



D Latch


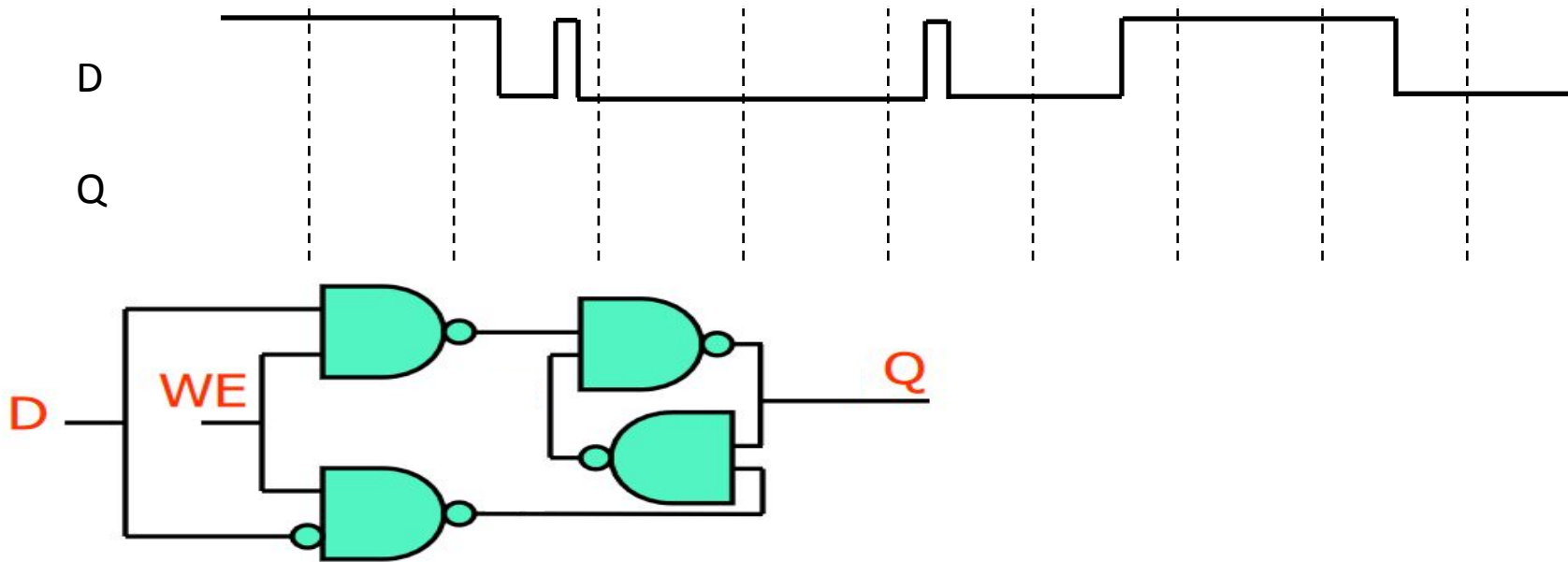
- ❖ Consider the following signal. What is the signal output (Q) of our D Latch? (Assume that WE is 1)



D Latch

- ❖ Consider the following signal. What is the signal output (Q) of our D Latch? (assume that WE is 1)


We get all the signal all the time

  

This is called "Transparent"

Transparency Issues

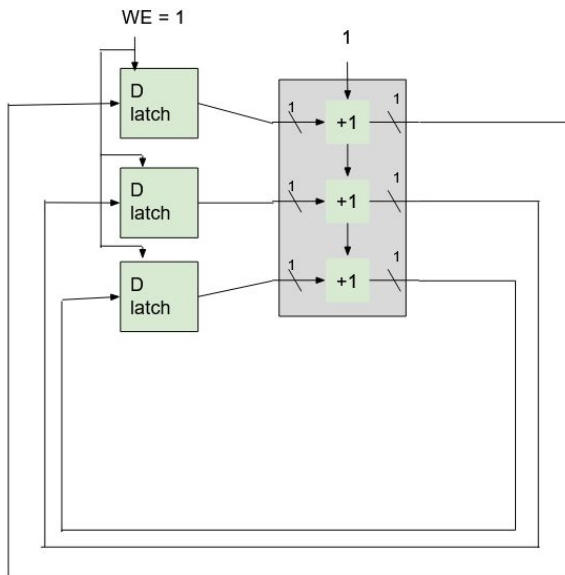- ❖ Consider that we had a 3-bit incrementer and we wanted to make a machine with 3 1-bit D-latches that went 0 -> 7 repeatedly.




Transparency Issues

Next int feeds directly back into input

- ❖ Consider that we had a 3-bit incrementer and we wanted to make a machine with 3 1-bit D-latches that went 0 -> 7 repeatedly.


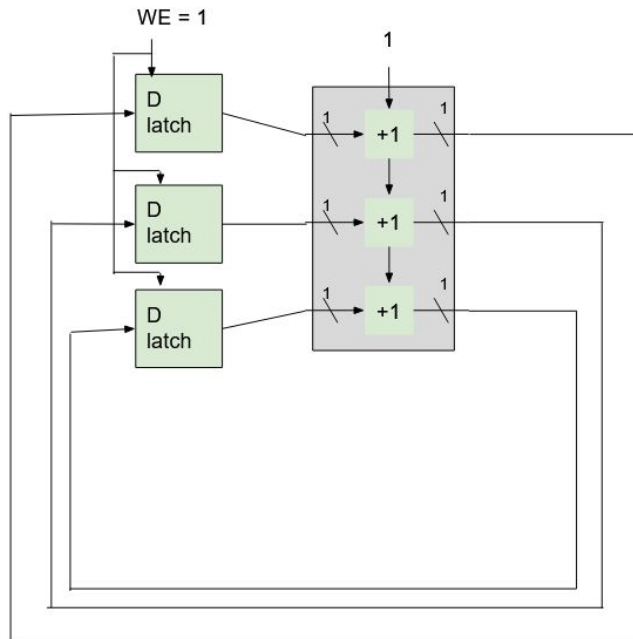
What if all three bits aren't ready at the same time?




How would we know when a value was “stable/readable”?

Delays

  - It takes time for a gate/unit to process an input.



 
- Consider our 3-bit incrementer
 - Each 'bit' incrementer depends on the carry from the previous bit incrementors
 - The LSB may be updated before the MSB



Clock

Clock Review

 - Regular up/down signal for synchronization
- Clock period?
- Clock frequency?




D-Latch with Clock

- CLK signal ANDed in



Assuming WE = 1:

 - What happens when CLK=0?
- What happens when CLK=1?





D-Latch with Clock

What's the timing diagram?

  



D-Latch with Clock

This is *semi-transparent*!

  



Thought Exercise

  What if one of the CLK input wires breaks? What's the timing diagram then? (WE = 1)



Thought Exercise

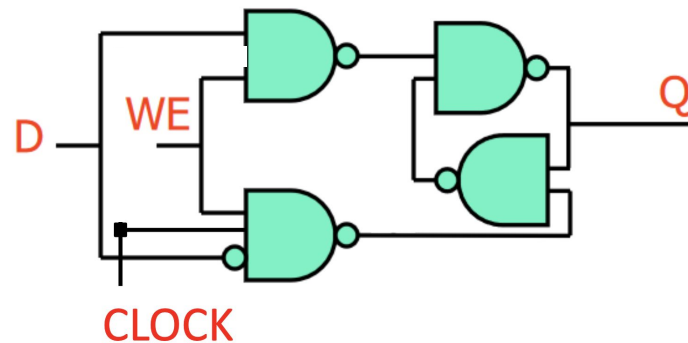 What if one of the CLK input wires breaks? What's the timing diagram then? (WE = 1)




Flip Flops

D Flip Flop



- ❖ Made by:
 - Appending a transparent-high onto a transparent-low latch
- ❖ Rules:
 - Q_{inter} is the result of passing D through a transparent-low latch
 - Q is the result of passing Q_{inter} through a transparent-high latch
 - Effectively, this makes Q only “sensitive” to the signal value at the rising edge of the clock

D Flip Flop

 


D Flip Flop Practice

  - ❖ What is Q and Q_{inter} for a D flip flop with the given clock and D signal




D Flip Flop Practice

 - ❖ What is Q and Q_{inter} for a D flip flop with the given clock and D signal



D Flip Flop Practice

 - ❖ What is Q and Q_{inter} for a D flip flop with the given clock and D signal



Q updates exactly once per clock cycle! (on a rising edge)
 Value is more “stable”

That's all we have for today!

Reminders:

- TA-lead recitations will take place on
 - Tuesdays 6:30-8:00pm in Moore 100A
 - Wednesday 12:00-1:30pm in Moore 100C
- Homework 3 is due this Friday 10/7
- **Note:** Check the course website for OH times! They may have time changes, location changes, or cancellations due to fall break.

Enjoy your fall break!! 