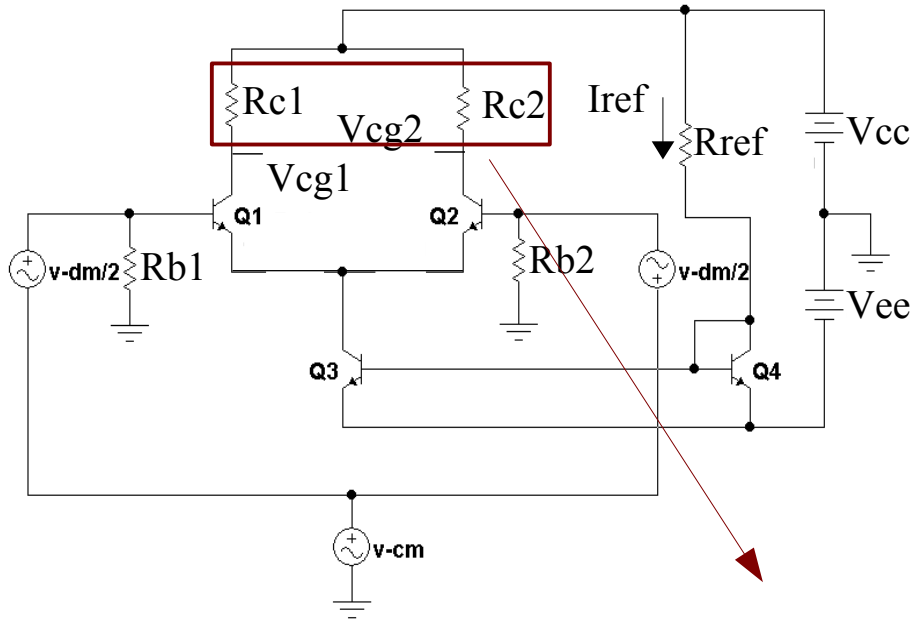




Differential Amplifier with Active Loads


- Active load basics
- PNP BJT current mirror
- Small signal model
- Design example and simulation
- Comparison of CMRR with resistive load design

Differential Amp – Active Loads Basics 1







$$R_{C2} \Rightarrow r_{o7}$$

$$R_{C1} \Rightarrow r_{o6}$$


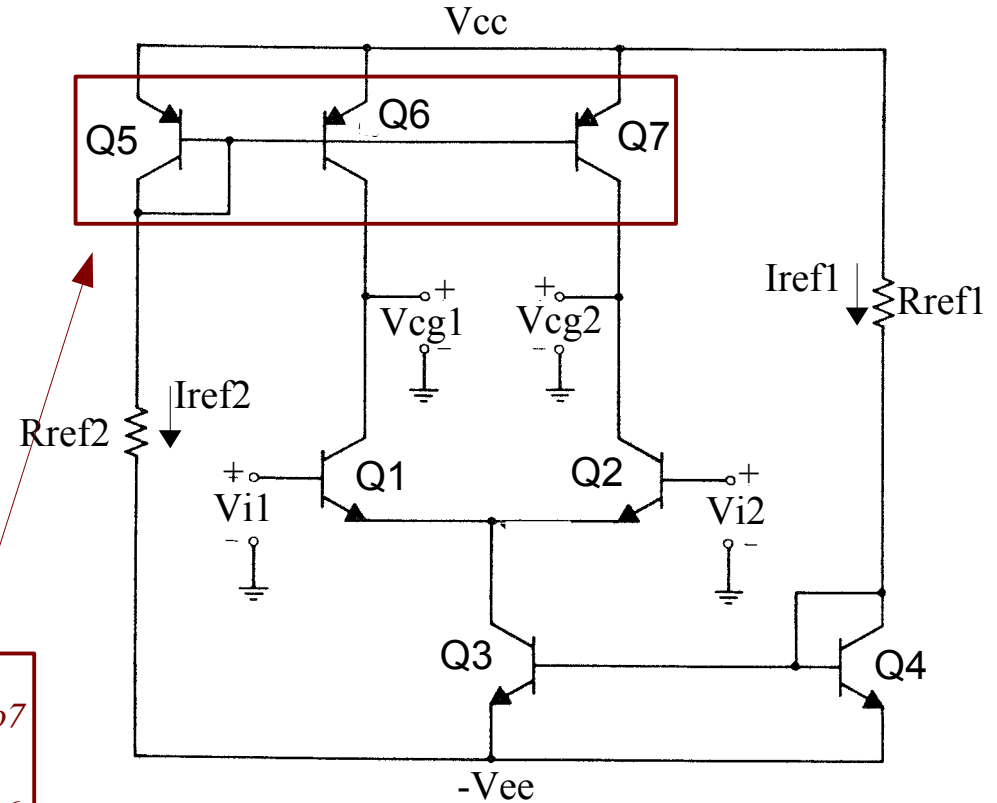


PROBLEM: Op. Pt. V_{CG1} , V_{CG2} very sensitive to mismatch $I_{ref1} \neq I_{ref2}$.

Differential Amp – Active Loads Basics 2

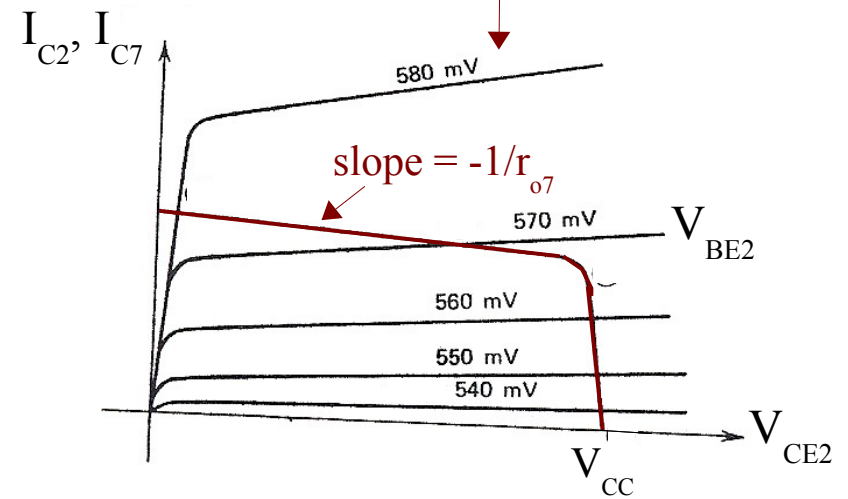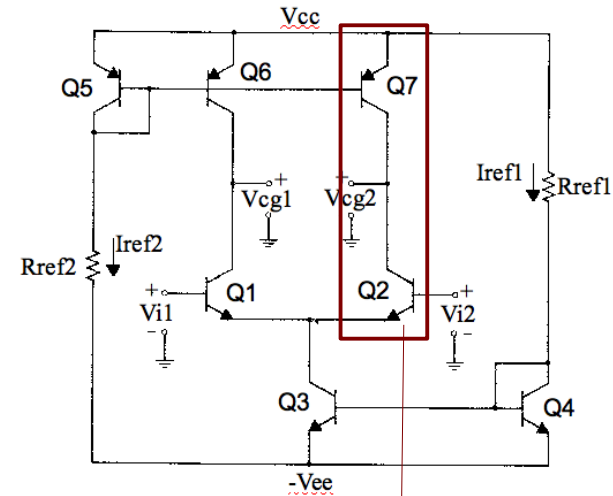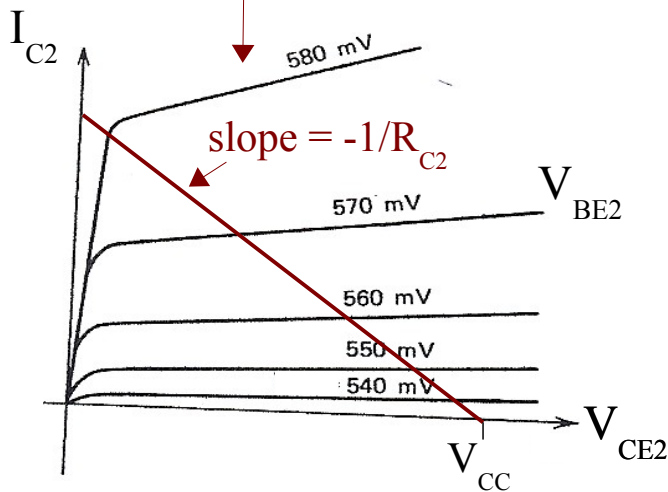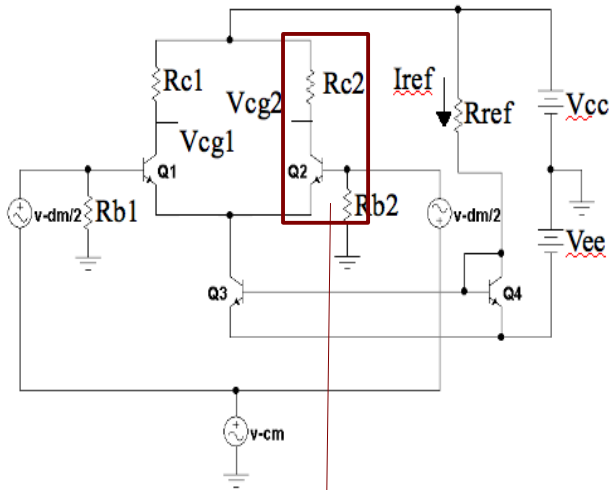

Differential Amp – Active Loads Basics 3

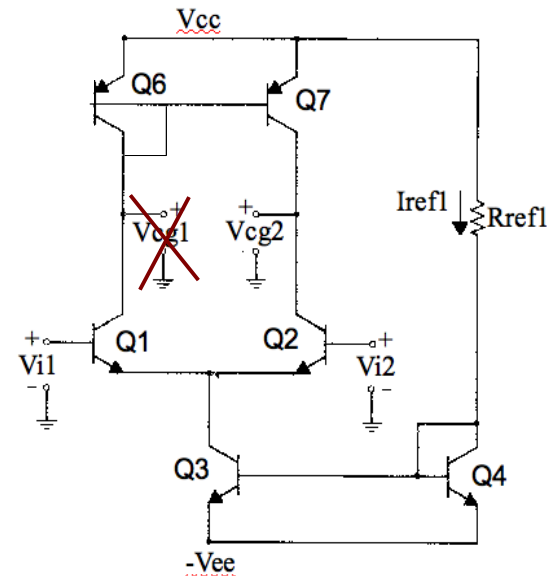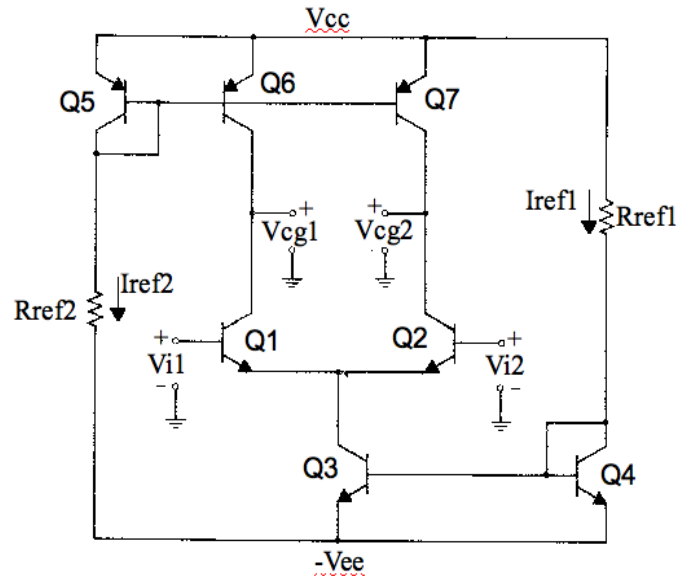


PROBLEM: Op. Pt. V_{CG1} , V_{CG2} very sensitive to mismatch $I_{ref1} \neq I_{ref2}$.

SOLUTION: all currents referenced to I_{ref1} . Op. Pt. sensitivity eliminated.

COST: output single-ended only.

GOOD NEWS: CMRR is much improved over resistive-load differential amp single-ended CMRR.

Quick Review - PNP BJT

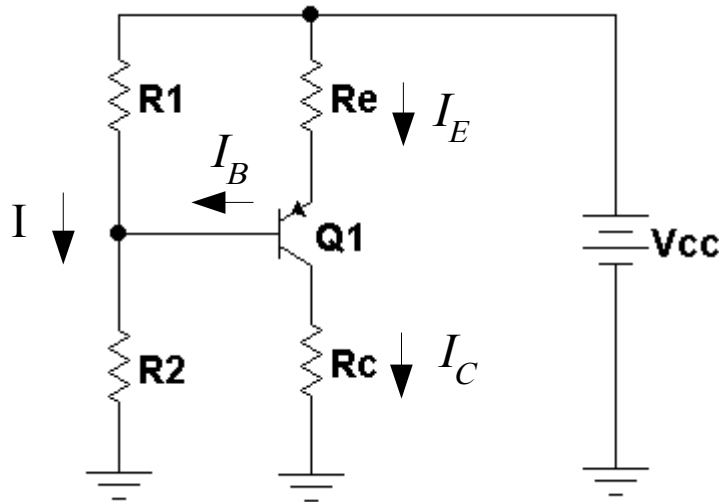

Voltage bias equations:

$$I_E = \frac{V_{CC} - (V_{BG} + 0.7)}{R_E}$$


$$I_E = \frac{(V_{CC} - V_{BG}) - 0.7}{R_E}$$

$$I_E = \frac{V_{R1} - 0.7}{R_E} = \frac{I * R_1 - 0.7}{R_E}$$

Note reference current directions!

$$I \approx \frac{I_C}{10}$$

Quick Review - PNP BJT

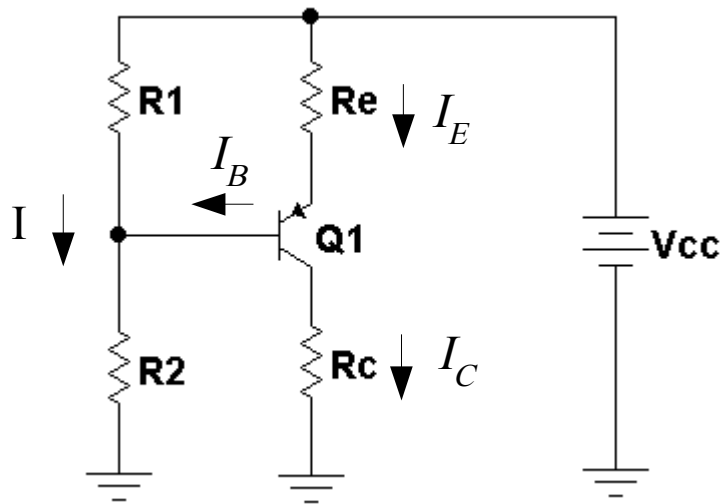




Usual Large signal equations:

$$i_C = I_S e^{\frac{V_{EB}}{V_T}}$$

$$i_B = \frac{i_C}{\beta}$$


$$i_E = i_C + i_B = \frac{(\beta + 1)}{\beta} i_C$$

$$i_C = \alpha i_E$$

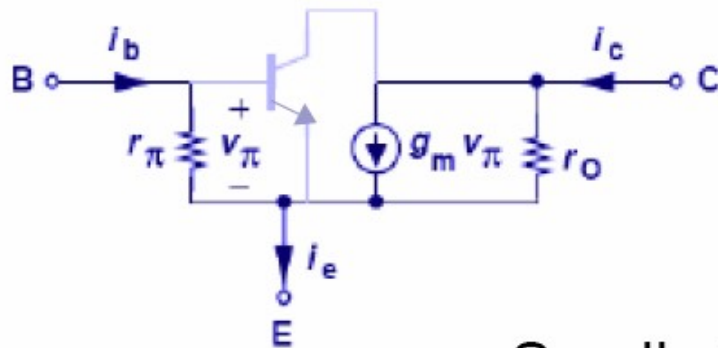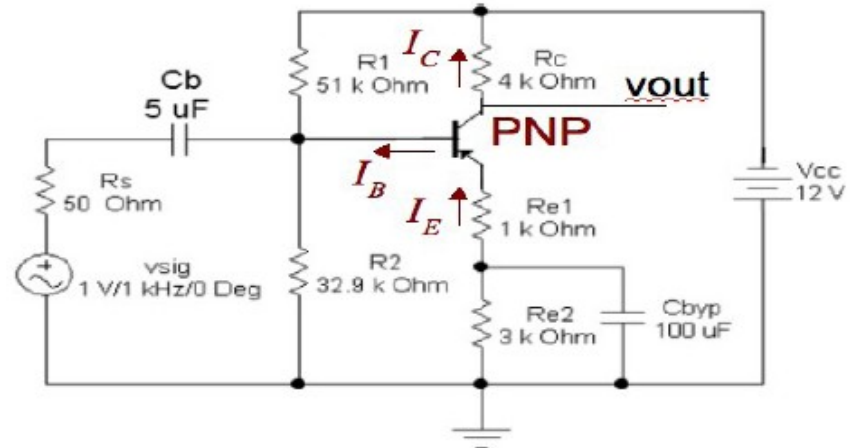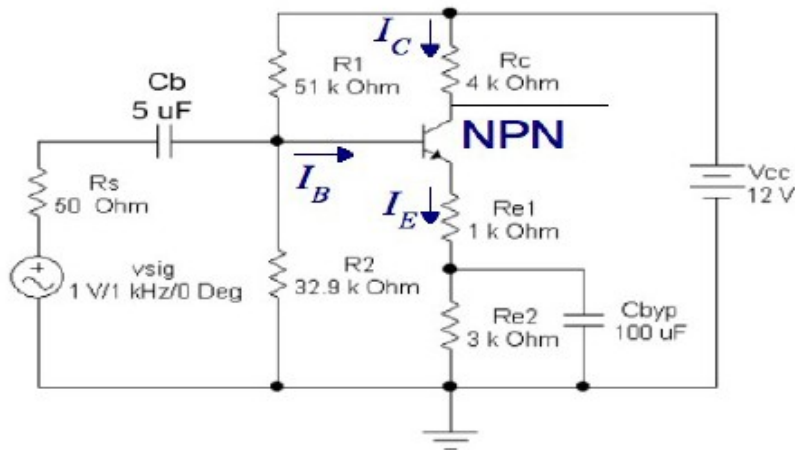

NPN: dc and ac currents in same direction

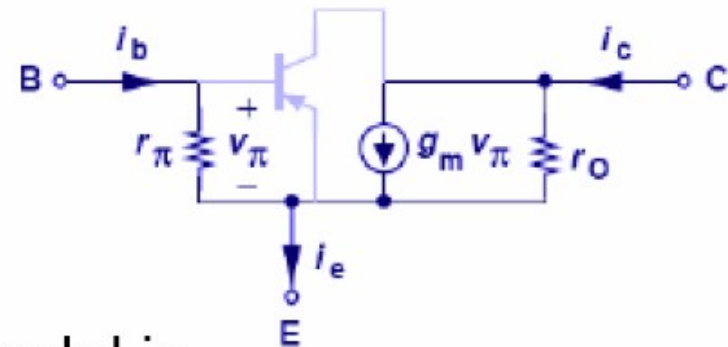
Small signal model is identical for NPN and PNP transistors!



PNP: dc and ac currents in opposite direction due to vsig polarity

PNP Mirror


Current source model Q1 = Q2:

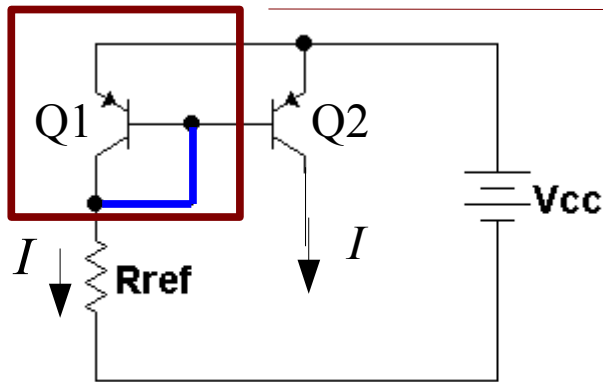

$$V_{CC} = V_{EB1} + I R_{REF}$$

$$I = \frac{V_{CC} - 0.7}{R_{REF}}$$

Small signal model:

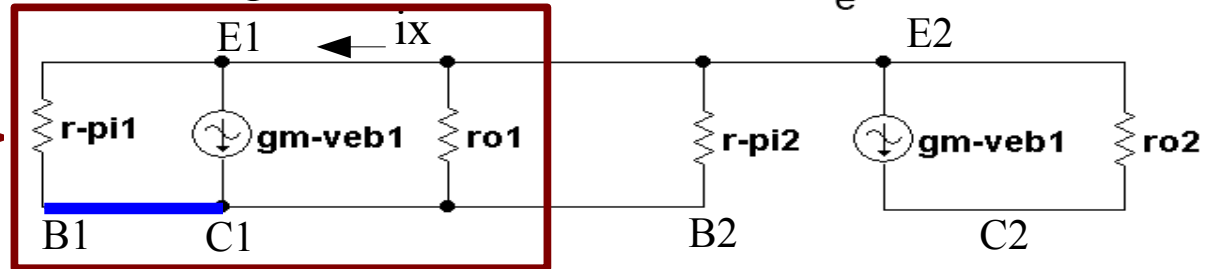

Current through r_π and $g_m v_{eb1}$:


$$i_x = \frac{V_{eb1}}{r_\pi} + g_m V_{eb1} = \left(\frac{1}{r_\pi} + g_m \right) V_{eb1}$$

$$i_x = \left(\frac{g_m}{\beta} + g_m \right) V_{eb1} = \left(\frac{\beta + 1}{\beta} \right) g_m V_{eb1} = \frac{V_{eb1}}{r_e}$$


recall

$$r_\pi = \frac{\beta}{g_m}$$

$$r_e = \frac{r_\pi}{\beta + 1}$$

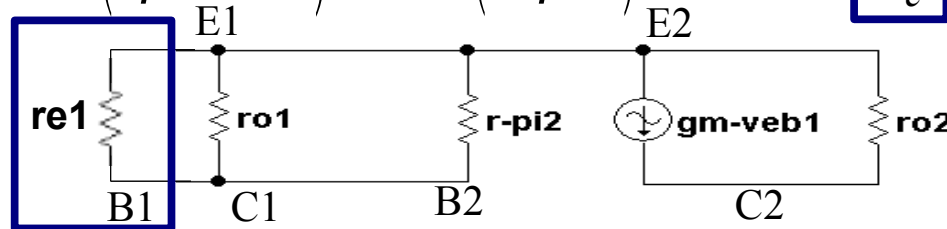

Simplified Midband DM Small Signal Model

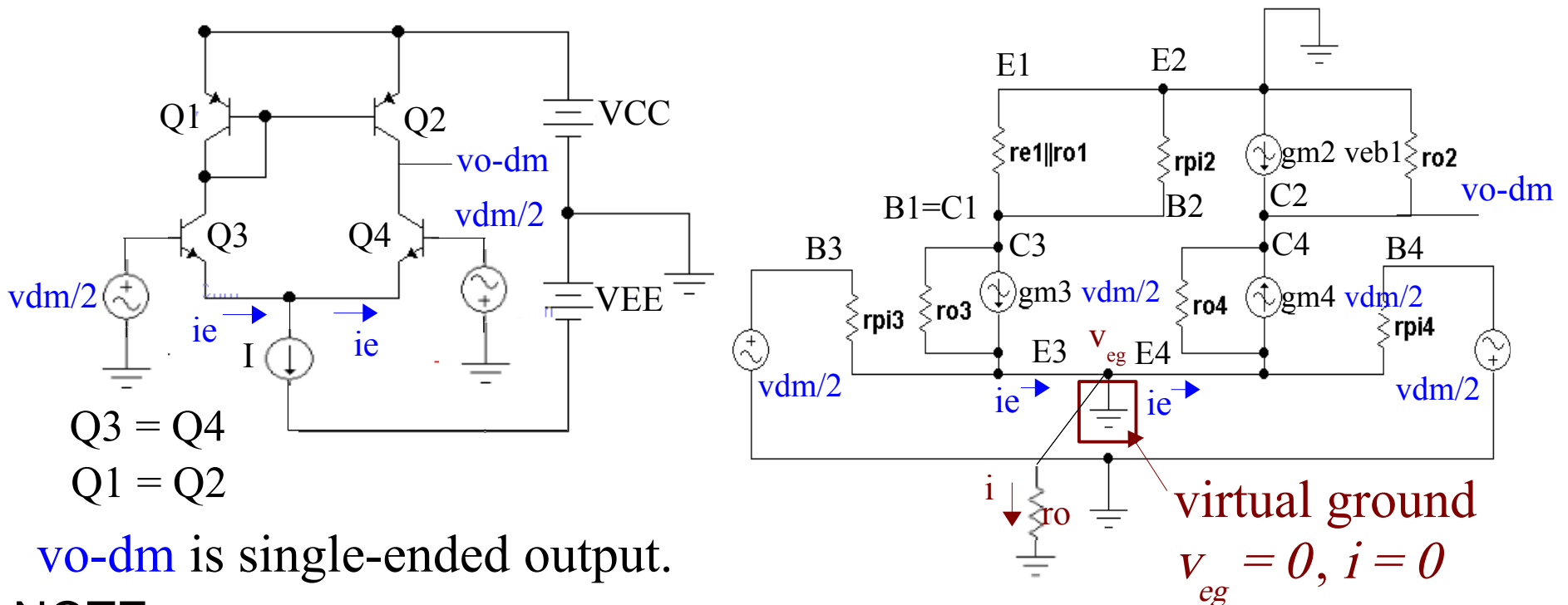



Simplified DM Small Signal Model cont.

Matched NPN: Q3 = Q4


$$g_{m3} = g_{m4} = g_{mn}$$

$$r_{e3} = r_{e4} = r_{en}$$


$$r_{\pi3} = r_{\pi4} = r_{\pi n}$$

$$r_{o3} = r_{o4} = r_{on}$$

combining parallel resistances to ground
 $r_{e1} || r_{o1} || r_{o3} || r_{\pi2} \approx r_{e1}$

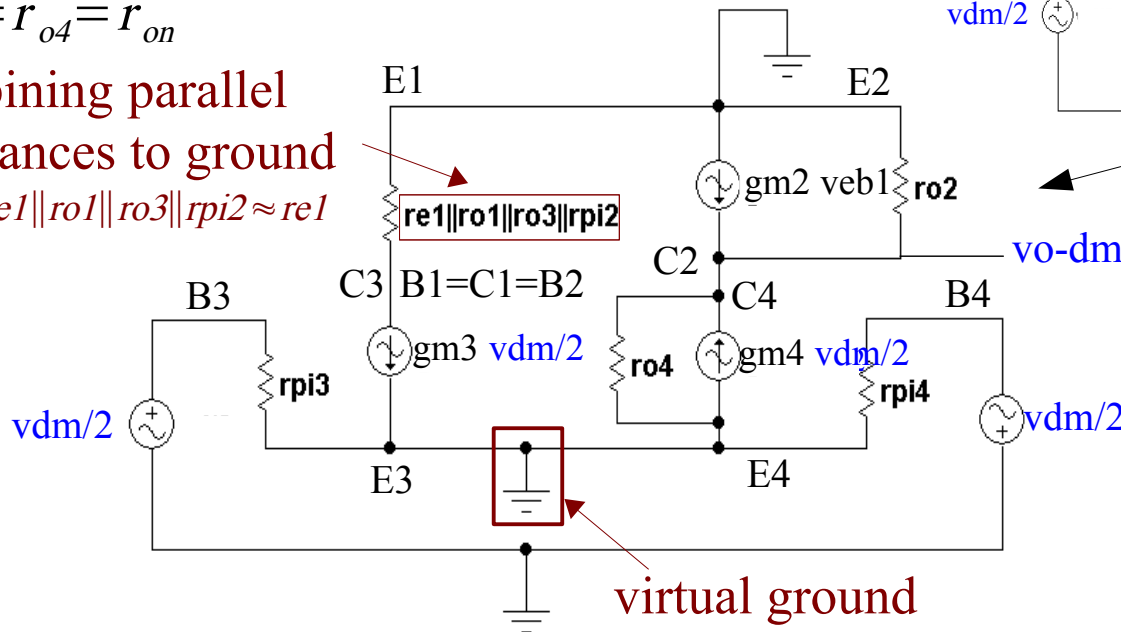

From previous slide

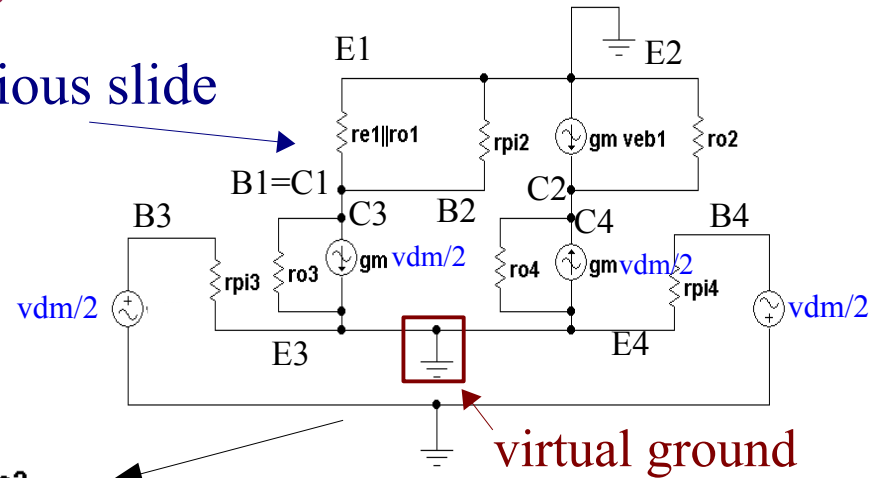

Matched PNP Q1 = Q2

$$g_{m1} = g_{m2} = g_{mp}$$

$$r_{e1} = r_{e2} = r_{ep}$$

$$r_{\pi1} = r_{\pi2} = r_{\pi p}$$


$$r_{o1} = r_{o2} = r_{op}$$

Simplified DM Small Signal Model - cont.

From previous slide with $re1 || ro1 || ro3 || rpi2 \approx re1$

Matched NPN: $Q3 = Q4$


Matched PNP: $Q1 = Q4$

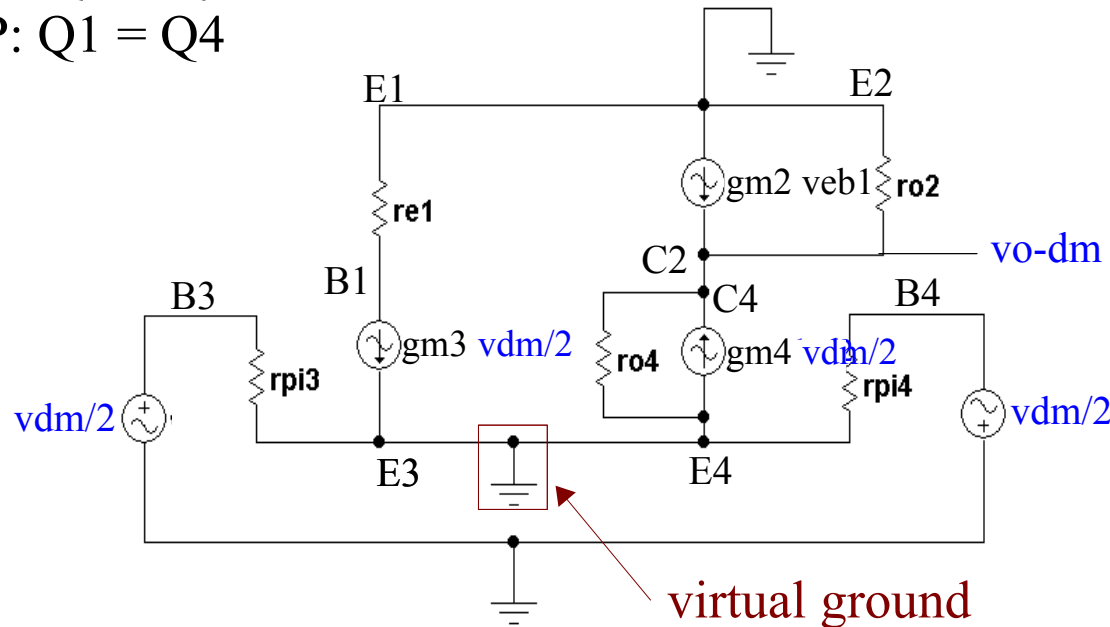

Simplified DM Small Signal Model - cont.

Matched NPN: $Q3 = Q4$

Matched PNP: $Q1 = Q2$

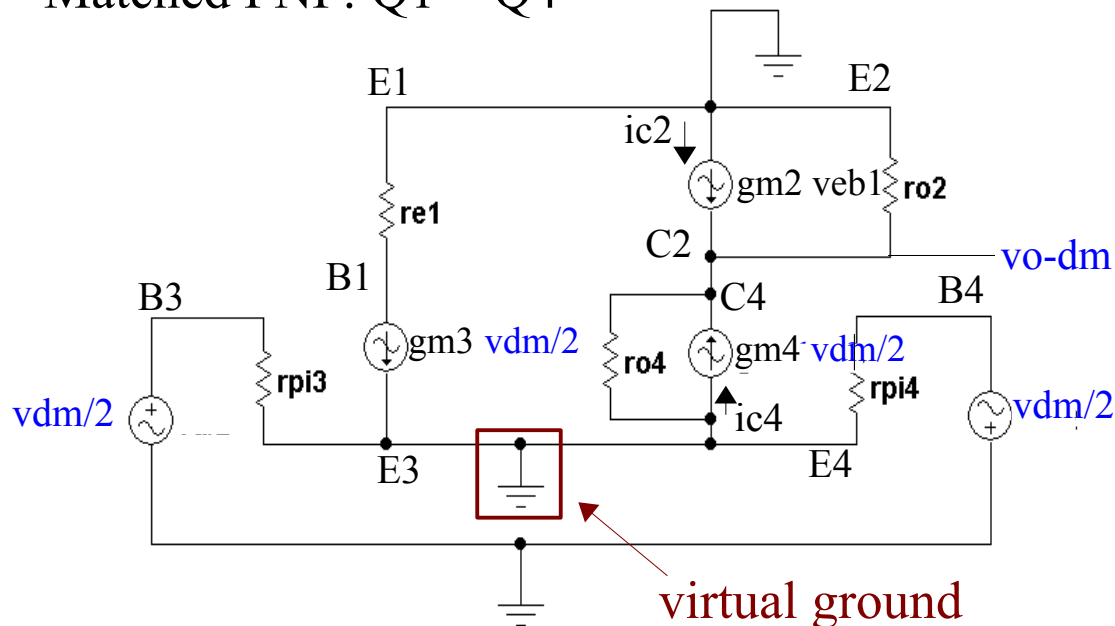

Matched transistors has been assumed throughout.

Determine i_{c2} and i_{c4} :

$$V_{eb1} \approx g_{mn} \frac{V_{dm}}{2} r_{ep}$$

$$i_{c2} = g_{mp} V_{eb1} = g_{mp} \left(g_{mn} \frac{V_{dm}}{2} r_{ep} \right)$$

where: $r_{ep} = \frac{\beta + 1}{\beta} \frac{1}{g_{mp}} \approx \frac{1}{g_{mp}}$


hence: $i_{c2} \approx g_{mn} \frac{V_{dm}}{2}$

by inspection: $i_{c4} = g_{mn} \frac{V_{dm}}{2}$

$$\Rightarrow i_{c2} \approx i_{c4}$$

Simplified DM Small Signal Model - cont.

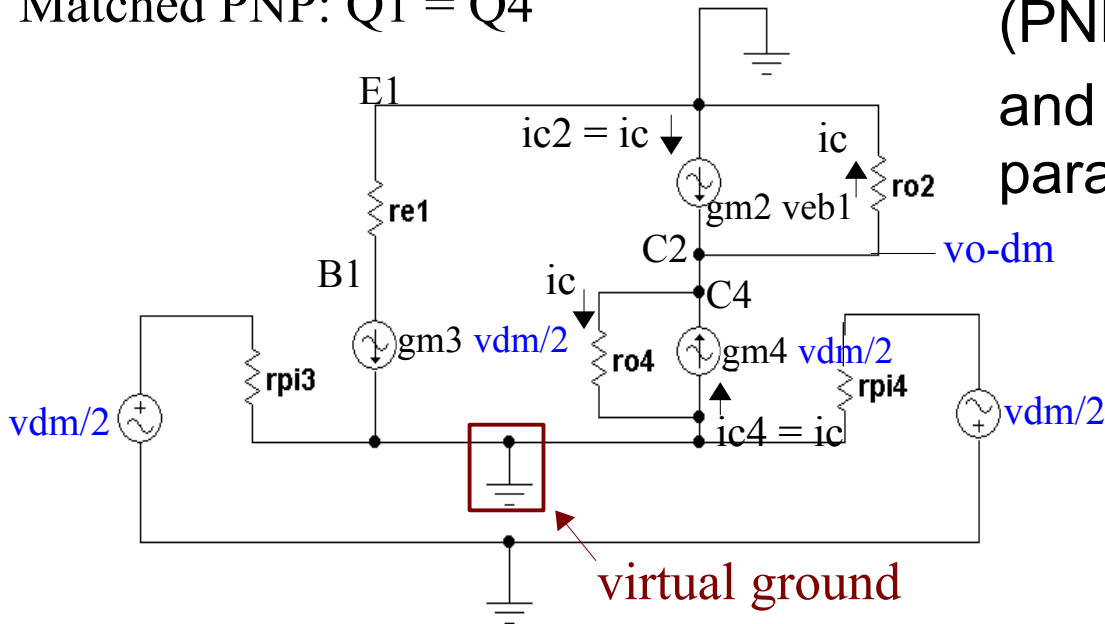Matched NPN: $Q3 = Q4$
Matched PNP: $Q1 = Q2$



Note that the Early resistors $r_{o2} = r_{op}$ (PNP) & $r_{o4} = r_{on}$ (NPN) are in parallel, and are driven by two nearly equal parallel current sources.

$$R_o = r_{op} \parallel r_{on} \approx r_o \parallel r_o = \frac{r_o}{2}$$

$$V_{o-dm} = (i_{c2} + i_{c4}) R_o = 2 \left(g_{mn} \frac{V_{dm}}{2} \right) R_o$$

$$V_{o-dm} = 2 g_{mn} R_o \frac{V_{dm}}{2}$$

$$G_{dm} = \frac{V_{o-dm}}{V_{dm}} = g_{mn} r_{op} \parallel r_{on}$$

also $G_{cm} = \frac{V_{o-cm}}{V_{cm}} = -\frac{r_{op}}{\beta_p r_o}$

From previous slide:

$$i_{c2} \approx g_{mn} \frac{V_{dm}}{2} = i_{c4}$$

Simplified Midband CM Small Signal Model

Matched NPN: Q3 = Q4

$$r_{o3} = r_{o4} = r_{on}$$

$$r_{\pi 3} = r_{\pi 4} = r_{\pi n}$$

$$r_{e3} = r_{e4} = r_{en}$$

$$g_{m3} = g_{m4} = g_{mn}$$

$$\beta_3 = \beta_4 = \beta_n$$

Matched PNP: Q1 = Q2


$$r_{o1} = r_{o2} = r_{op}$$

$$r_{\pi 1} = r_{\pi 2} = r_{\pi p}$$

$$r_{e1} = r_{e2} = r_{ep}$$

$$g_{m1} = g_{m2} = g_{mp}$$

$$\beta_1 = \beta_2 = \beta_p$$

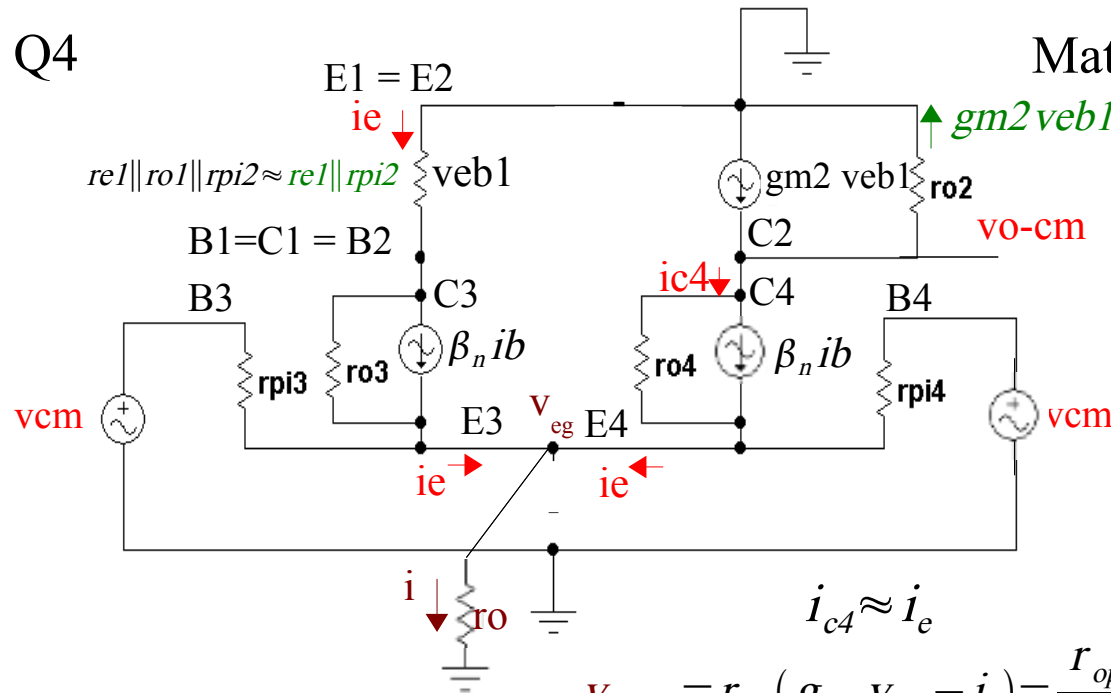


$$V_{cm} = \frac{r_{\pi n}}{\beta + 1} i_e + 2 r_o i_e \approx 2 r_o i_e \Rightarrow i_e \approx \frac{V_{cm}}{2 r_o}$$

$$V_{eb1} \approx \left(\underbrace{r_{ep} \parallel r_{\pi p}}_{re1 \parallel rpi2} \right) i_e = \frac{(r_{ep} \parallel r_{\pi p}) V_{cm}}{2 r_o}$$


$$V_{o-cm} = r_{op} (g_{mp} V_{eb1} - i_e) = \frac{r_{op}}{2 r_o} (g_{mp} (r_{ep} \parallel r_{\pi p}) - 1) V_{cm}$$

$$r_{\pi b} \parallel r_{ep} = \frac{\left(\frac{\beta_p}{g_{mp}} \right) \left(\frac{\beta_p}{g_{mp} (1 + \beta_p)} \right)}{\frac{\beta_p}{g_{mp}} + \frac{\beta_p}{g_{mp} (1 + \beta_p)}} = \frac{\beta_p}{g_{mp} (1 + \beta_p)} * \frac{1 + \beta_p}{2 + \beta_p}$$

DM Diff Amp 2N3906 PNP Active Loads

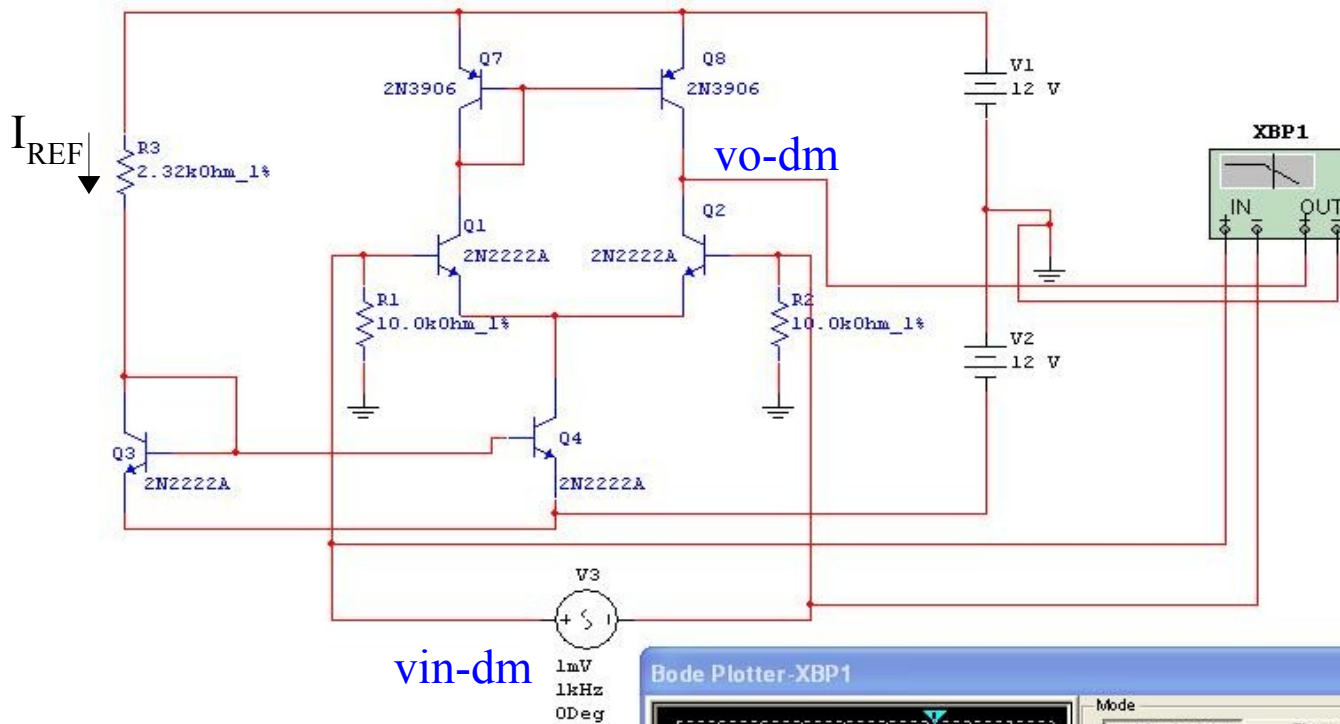

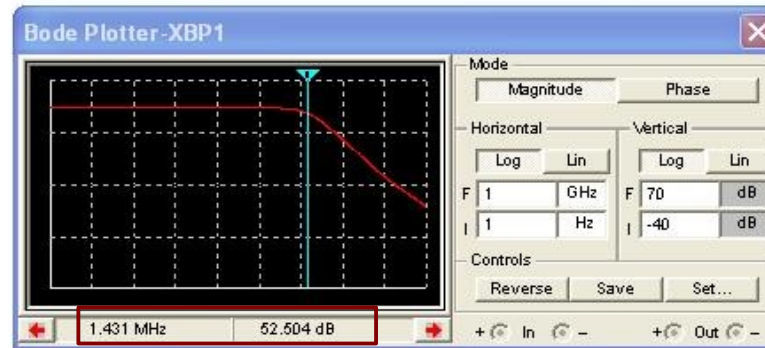Matched NPN: Q1 = Q2
 = Q3 = Q4
 Matched PNP: Q7 = Q8



Design: set R3 for
 $I_{REF} = 10 \text{ mA}$

$$R3 = \frac{23.3 \text{ V}}{10 \text{ mA}} = 2.33 \text{ k}\Omega$$


$$A_{dm} = \frac{V_{o-dm}}{V_{in-dm}} = g_m r_{o2} || r_{o8}$$

$$A_{dm} = 55.5 \text{ dB @ } 1 \text{ kHz}$$


$$= 52.5 \text{ dB @ } 1.43 \text{ MHz}$$



CM Diff Amp 2N3906 PNP Active Loads

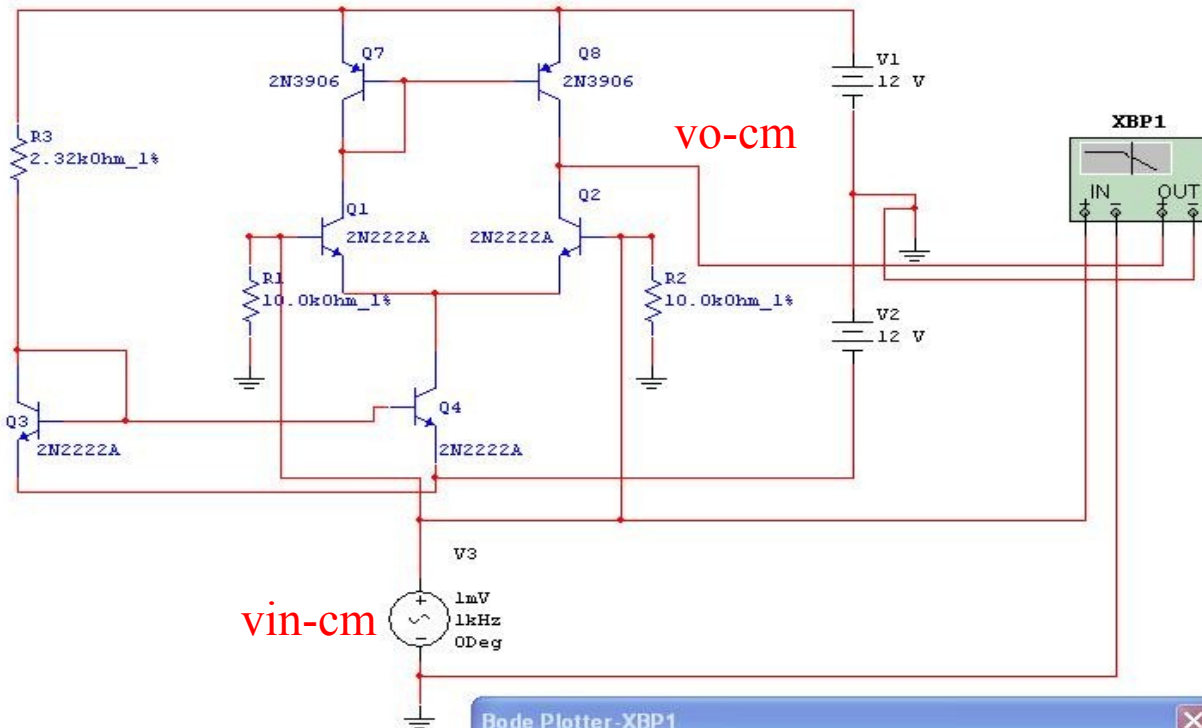

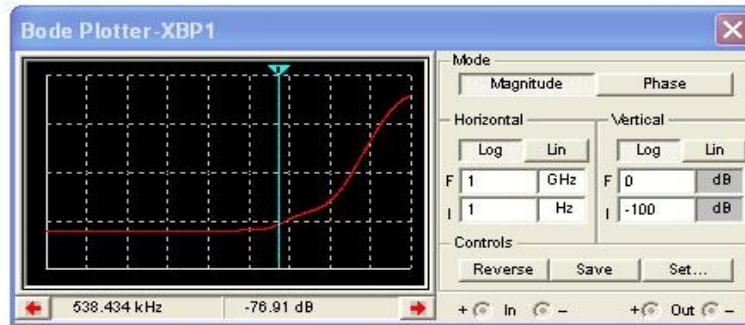Matched NPN: Q1 = Q2
 = Q3 = Q4
 Matched PNP: Q7 = Q8



$$A_{cm} = \frac{V_{o-cm}}{V_{in-cm}}$$

$$A_{cm} = -79.9 \text{ dB @ } 1 \text{ kHz}$$

$$= -76.9 \text{ dB @ } 0.54 \text{ MHz}$$


$$A_{dm} = 55.5 \text{ dB @ } 1 \text{ kHz}$$

$$CMRR = 20 \log_{10} \left(\frac{|A_{dm}|}{|A_{cm}|} \right)$$


$$= A_{dm-dB} - A_{cm-dB}$$

$$= 135.4 \text{ dB @ } 1 \text{ kHz}$$

CMRR Comparison

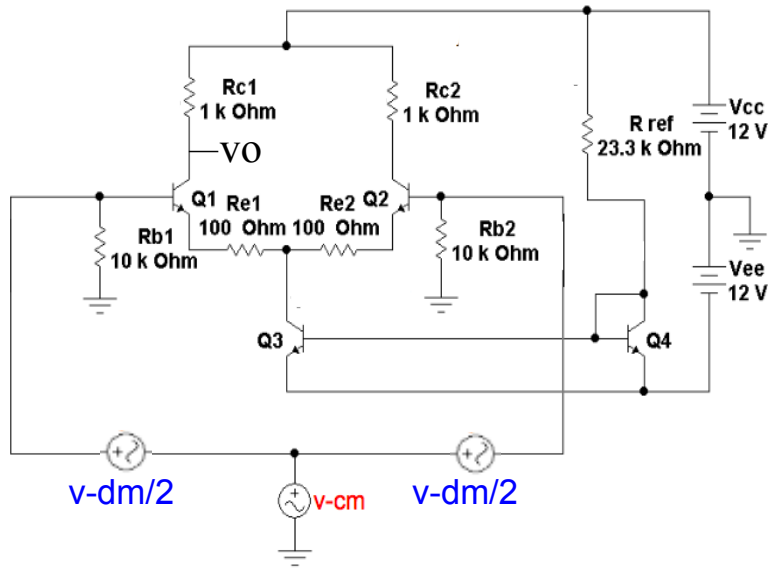

CMRR = 66 dB @ 1 kHz

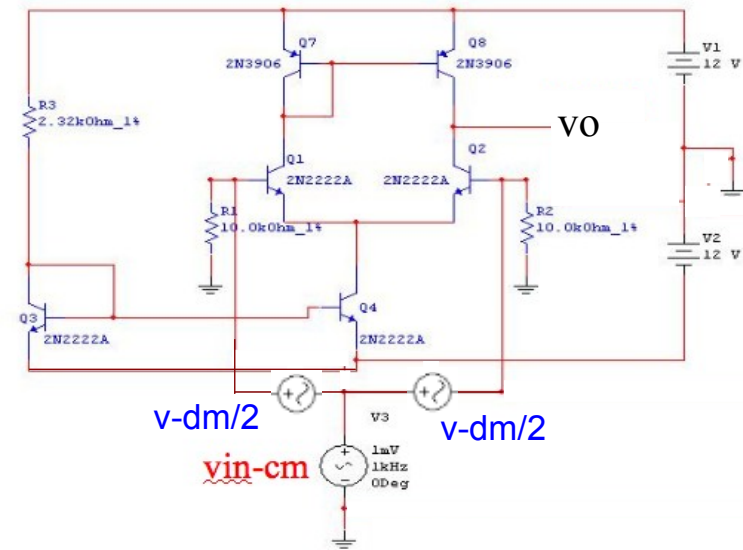

CMRR = 135 dB @ 1 kHz



Summary

Active load advantages:

1. Minimizes number of passive elements needed.
2. Can produce very high gain in one stage.
3. Much larger single-ended CMRR than single-ended CMRR for resistive load differential amplifier.
3. Inherent differential-to-single-ended conversion.

Active load disadvantages:

1. No differential output available.