

# ESE532: System-on-a-Chip Architecture

Day 7: September 24, 2018  
Pipelining -- Supplement




## Register

- On each cycle, the output of the register is the value of the input of the register on the previous cycle.

 
## Shift Register

- Illustrate operation
- Data moves through registers
- Shifts to right with each cycle
- Steady state, output at right is value input 3 cycles prior



 
## Addition

- Combinational Addition
- Two Adders
- Output is sum of 3 values



 
## Pipelined Addition

- Here we add registers to compute the addition in part of a pipeline
- Like the shift register values move through the registers over cycles
- The output is the sum of the inputs 3 cycles prior



 
## Pipelined Addition

- Note that the output is all inputs from the **same** cycle
- All the subscripts to A, B, C are the same.


 
## Retimed Add


- Now, we retime the add by applying a lag to the first adder
  - Move registers from its inputs to outputs



Penn ESE532 Fall 2018 -- DeHon

7

## Compare Behavior

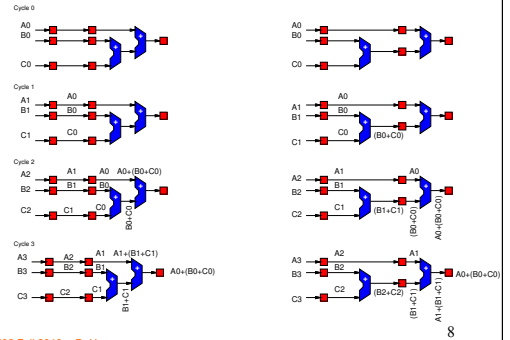


Penn ESE532 Fall 2018 -- DeHon

8
 
## Retimed Behavior

- To external behavior, the output is unchanged after the lag
  - Circuits behave identically



Penn ESE532 Fall 2018 -- DeHon

9

## Retimed Circuit Cycle Time

- Original circuit had two adder delays between registers
  - Minimum cycle time =  $2 \cdot T_{add}$
  - Throughput =  $1/(2 \cdot T_{add})$
- Retimed circuit has one adder delay between registers
  - Minimum cycle time =  $T_{add}$
  - Throughput =  $1/T_{add}$
- By performing the retiming, we doubled the throughput




Penn ESE532 Fall 2018 -- DeHon

10
 
## What-if just added a register?

- Rather than lag, what if we just added a register?




Penn ESE532 Fall 2018 -- DeHon

11
 
## Just Add Register Behavior

Note how this is different from the original (and from the retimed)

Here, final output mixes A1 with B0 and C0



Penn ESE532 Fall 2018 -- DeHon

12

## Just Add Register Function

Output takes the B and C from one input and adds it to the A that enters one cycle later.

