


University of Pennsylvania
Department of Electrical and System Engineering
Computer Organization

ESE534, Spring 2012 Assignment 2: Space-Time Multiply Monday, Jan. 23

Due: Monday, January 30, 12:00PM

We saw in lecture how to build various adders. In this problem, We're asking you to review or develop various techniques for building multipliers.

- Give latency and area in terms of the operand bitwidth, w . (we'll take asymptotic analysis, or you can use symbolic constants in terms of primitive gates such as $T_{fulladderslice}$, T_{and2} , A_{and2} , $A_{registerbit}$, A_{mux2})
 - When asked to draw an implementation, show the $w = 4$ case (except for 3(e) where we ask you to show $w = 8$). You may use hierarchical schematics.
1. Consider a spatial multiplier built out of simple, ripple-carry adders.
 - (a) Show a 4×4 multiplier.
 - (b) What is the area and latency for this multiplier? (function of w)
 2. Let's consider an alternate technique that uses the same full adder bitslice as in the previous ripple-carry adder design, but which wires up the carries differently. [This technique is known as **delayed addition**.]

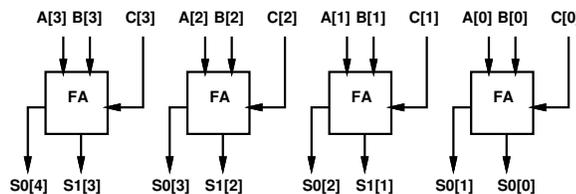

Here, A and B will be your normal two inputs to the adder. S_0 and S_1 together store the sum.

- (a) What is the latency of a single w -bit delayed addition?
- (b) How can the C input to the delayed adder be used?
- (c) Use these delayed-addition adders to build a spatial multiplier. The two input-operands to the multiplier are in standard form. Output values are represented as two numbers (*i.e.* S_0 , S_1 form shown above). Show the resulting, spatial multiplier which starts with numbers in standard form, but uses these delayed adders internally. (show $w = 4$ case.)

- (d) What do you need to do to the multiplier output to convert the result back into normal form?
- Remember, S0 and S1 jointly encode the final result. The normal form output should be a single binary-encoded word.
 - We would like this final conversion to have minimum latency. Be specific about how we implement the operation to minimize the latency it contributes.
- (e) What is the final area and latency of this multiplier? (function of w)
3. Continuing to the use full-adder bitslice used above, wire them up as an associative reduce tree to compute the result of the multiplication from all the bit-wise partial-products ($a_i \wedge b_j$).
- (a) How many partial-product bits do you start with? (function of w)
- (b) How many bits are outputs from the first stage of full-adder bitslices?
- (c) What reduction do you get with a single stage of full adders? (*e.g.* from part (a) to (b))
- (d) Continuing to use stages of full-adder bitslices to reduce the number of bits, how deep is the full reduce tree? (function of w)
- (e) Show the resulting multiplier. ($w = 8$ case)
- (f) What is the final area and latency of this multiplier? (function of w)
4. Using a datapath with only w full-adder bitslices, w AND's, multiplexers, and registers, develop an FSM to compute the product of two w -bit numbers in the least amount of total time. You may want to continue to use the basic delayed addition multiplication strategy from 3.
- (a) Identify the state registers you will need (what do they hold? how big will they be as a function of w ?).
- (b) Show the resulting multiplier:
- datapath (show $w = 4$ case)
 - how the datapath and FSM interact (control signals between them)
 - state machine diagram for the FSM
- (c) What is the latency of each cycle? (this probably demands you think about the gate-level implementation of the FSM and the datapath; can you guarantee this is **not** a function of w for any w ? (assuming delay is in the gates not the wires))
- (d) How many cycles does it take to complete the multiply? (function of w)
- (e) What is the final area and latency of this multiplier? (function of w)
5. Fill in the following table from your area/latency answers to the problems above (all functions of w):

	Design	Area	Latency
	P1: Ripple-Carry Based		
	P2: Delayed-Addition Based		
	P3: Associative Reduce Delayed-Addition		
	P4: Delayed-Addition FSM		