

Consider the computation:

```
int f(int a, int b, int c, int d, int x, int y, int z)
{
  return(a*x*x*x+b*y*y+c*z+d);
}
```

Assume:

- Multiplier (32b): Area=10, Delay=10
- Adder (32b): Area=1, Delay=1
- Multiplexer(32b): Area=1, Delay=0.1
- Register(32b): Area=0.5, Delay=0 (don't charge any extra delay)

1. How many multiplies in the computation?

2. How many adds in the computation?

3. Assuming a direct spatial implementation (like Day 15):

(a) What is the area?

(b) What is the delay?

4. How would you implement this design using only a single multiplier, a single adder along with multiplexers and registers (the number of which you pick, but should try to minimize)?

(a) What is the area?

(b) What is the delay?

5. How would you implement this design so that it had a delay within 10% of the first (fully spatial) case, but used less area? **Within 10% is more tricky than intended; Maybe only 60% slower is the easy target.**

(a) What is the area?

(b) What is the delay?