

Problem: Partition this circuit to minimize cutwidth. That is, divide the circuit into two, mutually exclusive sets of equal size (so each will have 4 of the 8 “gates”) in a way that minimizes the number of nets shared between the two sets (*e.g.* wires which would need to cross between the two sets).

