

ESE535: Electronic Design Automation

Day 8: February 13, 2008
Retiming



Today


- Retiming
 - Cycle time (clock period)
 - C-slow
 - Initial states
 - Register minimization

Task

- Move registers to:
 - Preserve semantics
 - Minimize path length between registers
 - Maximize reuse rate
 - ...while minimizing number of registers required

Example: Same Semantics

- Externally: no observable difference

 


Problem

- **Given:** clocked circuit
- **Goal:** minimize clock period without changing (observable) behavior
- *i.e.* minimize maximum delay between any pair of registers
- **Freedom:** move placement of internal registers

Other Goals

- Minimize number of registers in circuit
- Achieve target cycle time
- Minimize number of registers while achieving target cycle time
- ...start talking about minimizing cycle...

Simple Example

 


Path Length (L) = 4


Can we do better?

Legal Register Moves


- Retiming Lag/Lead

 

Canonical Graph Representation

 


Observable I/O

 


Separate arc for each path
Weight edges by number of registers
(weight nodes by delay through node)

Critical Path Length

 


Observable I/O

 

Critical Path: Length of longest path of zero weight nodes
Compute in $O(|E|)$ time by leveling network:

Topological sort, push path lengths forward until find register.

Retiming Lag/Lead

 

Retiming: Assign a lag to every vertex

$$\text{weight}(e') = \text{weight}(e) + \text{lag}(\text{head}(e)) - \text{lag}(\text{tail}(e))$$

Valid Retiming

- Retiming is valid as long as:
 - $\forall e$ in graph
 - $\text{weight}(e') = \text{weight}(e) + \text{lag}(\text{head}(e)) - \text{lag}(\text{tail}(e)) \geq 0$
- Assuming original circuit was a valid synchronous circuit, this guarantees:
 - non-negative register weights on all edges
 - no travel backward in time :-)
 - all cycles have strictly positive register counts
 - propagation delay on each vertex is non-negative (assumed 1 for today)

Retiming Task


- Move registers \equiv assign lags to nodes
 - lags define all locally legal moves
- Preserving non-negative edge weights
 - (previous slide)
 - guarantees collection of lags remains consistent globally

Penn ESE535 Spring 2008 -- DeHon

13

Retiming Transformation

 - Properties invariant to retiming
 1. number of registers around a cycle
 2. delay along a cycle
- Cycle of length P must have
 - at least P/c registers on it to be retimeable to cycle c
 - Can be computed from invariant above



Penn ESE535 Spring 2008 -- DeHon

14

Optimal Retiming

- There is a retiming of
 - graph G
 - w/ clock cycle c
 - iff $G-1/c$ has no cycles with negative edge weights
- $G-\alpha \equiv$ subtract α from each edge weight

Penn ESE535 Spring 2008 -- DeHon

15


1/c Intuition

- Want to place a register every c delay units
- Each register adds one
- Each delay subtracts $1/c$
- As long as remains more positives than negatives around all cycles
 - can move registers to accommodate
 - Captures the $\text{regs} = P/c$ constraints

Penn ESE535 Spring 2008 -- DeHon

16

$G-1/c$

 

Penn ESE535 Spring 2008 -- DeHon

17

Compute Retiming

- $\text{Lag}(v) =$ shortest path to I/O in $G-1/c$
- Compute shortest paths in $O(|V||E|)$
 - Bellman-Ford
 - also use to detect negative weight cycles when c too small

Penn ESE535 Spring 2008 -- DeHon

18


Bellman Ford

- For $k \leftarrow 0$ to N
 - $u_i \leftarrow -\infty$ (except $u_i=0$ for I/O)
- For $k \leftarrow 0$ to N
 - for $e_{ij} \in E$
 - $u_i \leftarrow \min(u_i, u_j + w(e_{ij}))$
- For $e_{ij} \in E$ //still update \rightarrow negative cycle
 - if $u_i > u_j + w(e_{ij})$
 - cycles detected

Penn ESE535 Spring 2008 -- DeHon

19


Apply to Example

 

Penn ESE535 Spring 2008 -- DeHon

20


Try $c=1$

 

Penn ESE535 Spring 2008 -- DeHon

21

Apply: Find Lags

 


Negative weight cycles?
Shortest paths?

Penn ESE535 Spring 2008 -- DeHon

22


Apply: Lags

 

Penn ESE535 Spring 2008 -- DeHon

23


Apply: Move Registers

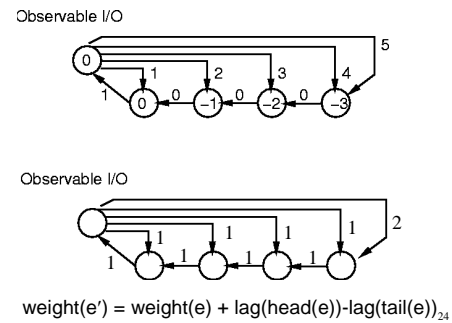


Penn ESE535 Spring 2008 -- DeHon

Apply: Retimed

Observable I/O

 

Observable I/O


 


Penn ESE535 Spring 2008 -- DeHon

25

Apply: Retimed Design


Observable I/O

  

Penn ESE535 Spring 2008 -- DeHon

26



Revise Example (fanout delay)

 

Penn ESE535 Spring 2008 -- DeHon

27



Revised: Graph

  

Penn ESE535 Spring 2008 -- DeHon

28


Revised: Graph

  

Penn ESE535 Spring 2008 -- DeHon

29


Revised: C=1?

 


Penn ESE535 Spring 2008 -- DeHon

30


Revised: C=2?

 


Revised: Lag

 



Revised: Lag

 



Take ceiling to convert to integer lags:

 



Revised: Apply Lag

  

Revised: Apply Lag

  

Revised: Retimed

  


Pipelining

- We can use this retiming to pipeline
- Assume we have enough (infinite supply) registers at edge of circuit
- Retime them into circuit

Penn ESE535 Spring 2008 -- DeHon

37


$C > 1 \implies$ Pipeline

 

Penn ESE535 Spring 2008 -- DeHon

38


Add Registers

 

Penn ESE535 Spring 2008 -- DeHon

39


Add Registers

 

Penn ESE535 Spring 2008 -- DeHon

40


Pipeline Retiming: Lag

 

Penn ESE535 Spring 2008 -- DeHon

41


Pipelined Retimed

 

Penn ESE535 Spring 2008 -- DeHon

42



Real Cycle

 

Penn ESE535 Spring 2008 -- DeHon


43

Real Cycle

  

Penn ESE535 Spring 2008 -- DeHon


Cycle C=1?

 

Penn ESE535 Spring 2008 -- DeHon

45


Cycle C=2?

 


Penn ESE535 Spring 2008 -- DeHon

46

Cycle: C-slow

 


 Cycle=c \Rightarrow C-slow network has Cycle=1



Penn ESE535 Spring 2008 -- DeHon


2-slow Cycle \Rightarrow C=1

 

Penn ESE535 Spring 2008 -- DeHon

48


2-Slow Lags

 

Penn ESE535 Spring 2008 -- DeHon

49


2-Slow Retime

 

Penn ESE535 Spring 2008 -- DeHon

50

Retimed 2-Slow Cycle

 

Penn ESE535 Spring 2008 -- DeHon

51

C-Slow applicable?


- Available parallelism
 - solve C identical, independent problems
 - e.g. process packets (blocks) separately
 - e.g. independent regions in images
- Commutative operators
 - e.g. max example

Penn ESE535 Spring 2008 -- DeHon

52

Max Example

2-Slow design:

 


X2 X2 X1 X1 X0 X0 → Y2 ? Y1 ? Y0 ?

B2 A2 B1 A1 B0 A0 → YA2 YB1 YA1 YB0 YA0 ?

Penn ESE535 Spring 2008 -- DeHon

53

Max Example

 

Computes two interleaved streams: even max, odd max

Computes final max of even and odd pairs

Penn ESE535 Spring 2008 -- DeHon


54

Note


- Algorithm/examples shown
 - for special case of unit-delay nodes
- For general delay,
 - a bit more complicated
 - still polynomial

Initial State


- What about initial state?

 

Initial State

 


Initial State

 


In general, constraints \rightarrow satisfiable?

Initial State

 

Initial State

 

Cycle1: 1
Cycle2: $!(0*in)=1$

Cycle1: /init
Cycle2: $!(/init*in)=in+init$

init=0

Cycle1: 1

Cycle2: $!(/init*in)=in$

init=1


Cycle1: 0

Cycle2: $!(/init*in)=1$

Initial State

- Cannot always get exactly the same initial state behavior on the retimed circuit
 - without additional care in the retiming transformation
 - sometimes have to modify structure of retiming to preserve initial behavior
- Only a problem for startup transient
 - if you're willing to clock to get into initial state, not a limitation

Minimize Registers

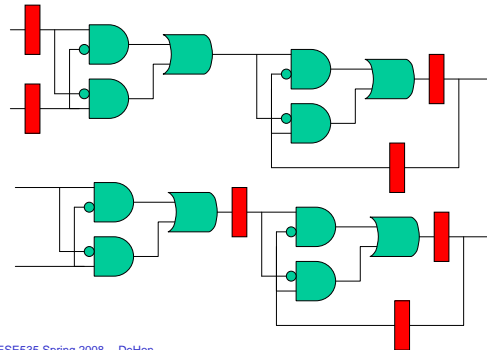

Minimize Registers

- Number of registers: $\sum w(e)$
- After retime: $\sum w(e) + \sum (F_I(v) - F_O(v)) \text{lag}(v)$
- delta only in lags
- So want to minimize: $\sum (F_I(v) - F_O(v)) \text{lag}(v)$
 - subject to earlier constraints
 - non-negative register weights, delays
 - positive cycle counts

Minimize Registers

- Can be formulated as flow problem
- Can add cycle time constraints to flow problem
- Time: $O(|V||E| \log(|V|) \log(|V|^2/|E|))$

Summary

- Can move registers to minimize cycle time
- Formulate as a lag assignment to every node
- Optimally solve cycle time in $O(|V||E|)$ time
- Also
 - Compute multithreaded computations
 - Minimize registers
- Watch out for initial values

Admin

- Homework #2 due Monday
- Reading for Monday on web

Big Ideas

- Exploit freedom
- Formulate transformations (lag assignment)
- Express legality constraints
- Technique:
 - graph algorithms
 - network flow