

# ESE535: Electronic Design Automation

Day 15: March 18, 2009  
Static Timing Analysis  
and Multi-Level Speedup




Penn ESE535 Spring 2009 -- DeHon

## Today

- Topological Worst Case
  - not adequate (too conservative)
- Sensitization Conditions
- Timed Calculus
- Delay-justified paths
  - Timed-PODEM
- Speedup

2

## Topological Worst-Case Delay

 


- Compute ASAP schedule
  - Take max of arrival times
  - Apply node Delay

Penn ESE535 Spring 2009 -- DeHon

3

## Topological Worst-Case Delay

 


- Node Delays

Penn ESE535 Spring 2009 -- DeHon

4

## Topological Worst-Case Delay

 


- Compute Delays

Penn ESE535 Spring 2009 -- DeHon

5
 
## Conservative

- Topological Worst-Case Delay can be conservative




[Fig/Examples from Logic Synthesis  
by Devadas, Gosh, Keutzer 1994]

Penn ESE535 Spring 2009 -- DeHon

## Example


- Assume each gate 1:

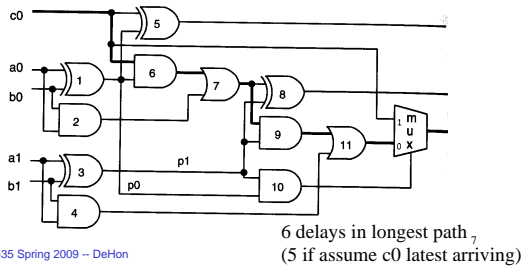

Penn ESE535 Spring 2009 -- DeHon

## Example

- Is this path possible?

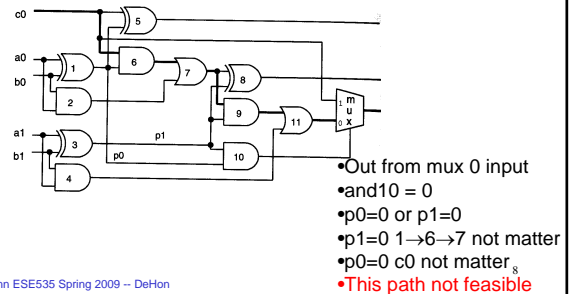

Penn ESE535 Spring 2009 -- DeHon

## False Paths

- Once consider logic for nodes
  - There are logical constraints on data values
- There are paths which cannot logically occur
  - Call them **false paths**

Penn ESE535 Spring 2009 -- DeHon

9

## What can we do?

- Need to assess what paths are real
- Brute force
  - for every pair of inputs
  - compute delay in outputs from in1→in2 input transition
  - take worst case
- Expensive:
  - $2^{2n}$  delay traces

Penn ESE535 Spring 2009 -- DeHon

10

## Alternately

- Look at single vector and determine what controls delay of circuit
  - I.e. look at values on path and determine path *sensitized* to change with input

Penn ESE535 Spring 2009 -- DeHon

11

## Controlled Inputs

- Controlled input to a gate:
  - input whose value will determine gate output
  - e.g.
    - 0 on a AND gate
    - 1 on a OR gate

Penn ESE535 Spring 2009 -- DeHon

12


## Static Sensitization

- A path is statically sensitized
  - if all the side (non-path) inputs are non-controlling
  - I.e. this path value flips with the input

Penn ESE535 Spring 2009 -- DeHon

13

## Statically Sensitized Path

 


Penn ESE535 Spring 2009 -- DeHon

14
 
## Sufficiency


- Static Sensitization is **sufficient** for a path to be a **true** path in circuit




Penn ESE535 Spring 2009 -- DeHon

15

## ...but not necessary

 

 Paths of length 3 not statically sensitizable.




But there is a true path of delay 3.

Penn ESE535 Spring 2009 -- DeHon

16
 
## Static Co-sensitization

- Each output with a controlled value
  - has a controlling value as input on path
  - (and vice-versa for non-controlled)




Penn ESE535 Spring 2009 -- DeHon

May trace multiple edges

 
## Necessary

- Static Co-sensitization is a **necessary** condition for a path to be true



Penn ESE535 Spring 2009 -- DeHon

...but not sufficient

 

Cosensitize path of length 6.  
Real delay is 5.

Penn ESE535 Spring 2009 -- DeHon

19


## Combining

- Combine these ideas into a timed-calculus for computing delays for an input vector

Penn ESE535 Spring 2009 -- DeHon

20

## Computing Delays

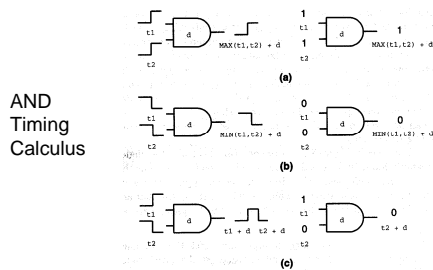

Penn ESE535 Spring 2009 -- DeHon

21


## Rules

- If gate output is at a controlling value, pick the minimum input and add gate delay
- If gate output is at a non-controlling value, pick the maximum input and add gate delay

Penn ESE535 Spring 2009 -- DeHon

22


## Example (1)

 

Penn ESE535 Spring 2009 -- DeHon

23

## Example (2)

 

Penn ESE535 Spring 2009 -- DeHon

## Now...

- We know how to get the delay of a single input condition
- Could:
  - find critical path
  - search for an input vector to sensitize
  - if fail, find next path
  - ...until find longest true path
- May be  $O(2^n)$

Penn ESE535 Spring 2009 -- DeHon

25

## Better Approach

- Ask if can justify a delay greater than T
- Search for satisfying vector
  - ...or demonstration that none exists
- Binary search to find tightest delay

Penn ESE535 Spring 2009 -- DeHon

26

## Delay Computation

- Modification of a testing routine
  - used to justify an output value for a circuit
  - similar to SAT
- PODEM
  - backtracking search to find a suitable input vector associated with some target output
  - Simply a branching search with implication pruning
    - Heuristic for smart variable ordering

Penn ESE535 Spring 2009 -- DeHon

27

## Search

- Takes two lists
  - outputs to set; inputs already set
- Propagate values and implications
- If all outputs satisfied  $\rightarrow$  succeed
- Pick next PI to set and set value
  - Search with this value set
  - If inconsistent
    - If PI not implied
      - Invert value of PI
      - Search with this value set
      - If inconsistent  $\rightarrow$  fail
      - Else succeed
    - Else fail
  - Else succeed

Penn ESE535 Spring 2009 -- DeHon

28

## Picking next variable to set


- Follow back gates w/ unknown values
  - sometimes output dictate input must be
    - (AND needing 1 output; with one input already assigned 1)
  - sometimes have to guess what to follow
    - (OR with 1 output and no inputs set)
    - Uses heuristics to decide what to follow

Penn ESE535 Spring 2009 -- DeHon


29

## Example

Try justify  $g=1$

 

(a)

 


(b)

Penn ESE535 Spring

30

## Example

 

Penn ESE535 Spring 2009 -- C

31

## For Timed Justification

- Also want to compute delay
  - on incompletely specified values
- Compute bounds on timing
  - upper bound, lower bound
  - Again, use our timed calculus
    - expanded to unknowns

Penn ESE535 Spring 2009 -- DeHon

32

## Delay Calculation

AND rules

$i_1 \rightarrow$ $i_2 \downarrow$	0	1	2
0	$0$ $MIN(l_1, l_2) + d$ $MIN(u_1, u_2) + d$	$0$ $l_2 + d$ $u_2 + d$	$0$ $MIN(l_1, l_2) + d$ $u_2 + d$
1	$0$ $l_1 + d$ $u_1 + d$	$1$ $MAX(l_1, l_2) + d$ $MAX(u_1, u_2) + d$	$2$ $l_1 + d$ $MAX(u_1, u_2) + d$
2	$0$ $MIN(l_1, l_2) + d$ $u_1 + d$	$2$ $l_2 + d$ $MAX(u_1, u_2) + d$	$2$ $MIN(l_1, l_2) + d$ $MAX(u_1, u_2) + d$

Penn ESE535 Spring 2009 -- DeHon

33

## Timed PODEM


- **Input:** value to justify and delay T
- **Goal:** find input vector which produces value and exceeds delay T
- Algorithm
  - similar
  - implications check timing as well as logic

Penn ESE535 Spring 2009 -- DeHon

34

## Example

Justify 1(3)

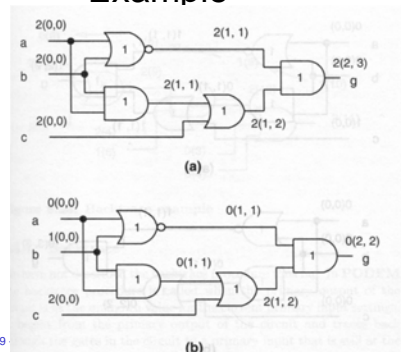


Penn ESE535 Spring 2009

## Example

Fail to justify 1(3)

Justify 0(3)

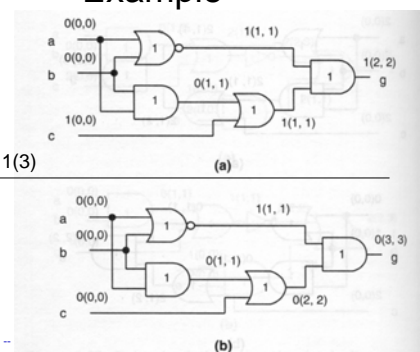

Penn ESE535 Spring 2009 --

## Search

- Less than  $2^n$ 
  - pruning due to implications
  - here saw a must be 0
    - no need to search 1xx subtree

Penn ESE535 Spring 2009 -- DeHon

37

## Questions

- On static timing analysis?

Penn ESE535 Spring 2009 -- DeHon

38

## Speed Up

(sketch flavor)

Penn ESE535 Spring 2009 -- DeHon

39

## Speed Up


- Start with area optimized network
- Know target arrival times
  - Know delay from static analysis
- Want to reduce delay of node

Penn ESE535 Spring 2009 -- DeHon

40
 
## Basic Idea

- Improve speed by:
  - Collapsing node(s)
  - Refactoring collapsed subgraph to reduce height



Penn ESE535 Spring 2009 -- DeHon

41

## Speed Up


- While (delay decreasing, timing not met)
  - Compute delay (slack)
    - Static timing analysis
  - Generate network close to critical path
    - w/in some delay  $\epsilon$ , to some distance  $d$
  - Weight nodes in network
    - Less weight = more potential to improve, prefer to cut
  - Compute **mincut** of nodes on weighted network
  - For each node in cutset
    - Partial collapse
  - For each node in cutset
    - Timing redecompose

Penn ESE535 Spring 2009 -- DeHon

42
 
## MinCut of Nodes


- Cut nodes not edges
  - Typically will need to transform to dual graph
    - All edges become nodes, nodes become edges
  - Then use maxflow/mincut



Penn ESE535 Spring 2009

## MinCut of Nodes


- What are possible cuts?

 

Penn ESE535 Spring 2009 -- DeHon

44


## MinCut of Nodes

 

Penn ESE535 Spring 2009 -- DeHon

45

## MinCut of Nodes

 

Penn ESE535 Spring 2009 -- DeHon

46

## Weighted Cut


- $W = W_t + \alpha W_a \rightarrow \alpha$  tuning parameter
- Want to minimize area expansion
  - Things in collapsed network may be duplicated
  - E.g.  $W_a$  = literals in duplicated logic
- Want to maximize likely benefit
  - Prefer nodes with varying input times to the “near critical path” network
    - Quantify: large variance in arrival times
  - Prefer nodes with critical path on longer paths

Penn ESE535 Spring 2009 -- DeHon

47
 
## Weighing Benefit

- Want to maximize likely benefit
  - Prefer nodes with varying input times to the “near critical path” network




Penn ESE535 Spring 2009 -- DeHon

48


 
## Weighing Benefit

- Want to maximize likely benefit
  - Prefer nodes with critical path on longer paths



Penn ESE535 Spring 2009 -- DeHon

49


## Timing Decomposition

- Extract area saving kernels that do not include critical inputs to node
  - $f = abcd + abce + abef$  (last time)
  - Kernels =  $\{cd + ce + ef, e + d, c + f\}$
  - $F = abe(c+f) + abcd, ab(cd+ce+ef), abc(e+d) + abef$
  - What if:
    - Critical input is  $f$ ?  $d$ ?  $a$ ?  $\{a, d\}$ ?
- When decompose (e.g. into nand2's) similarly balance with critical inputs closest to output

Penn ESE535 Spring 2009 -- DeHon

50


## Example

 

Penn ESE535 Spring 2009 -- DeHon

51


## Example

 

Penn ESE535 Spring 2009 -- DeHon

52

## Example

 

Penn ESE535 Spring 2009 -- DeHon

53

## Speed Up (review)

- While (delay decreasing, timing not met)
  - Compute delay (slack)
    - Static timing analysis
  - Generate network close to critical path
    - w/in some delay  $\epsilon$ , to some distance  $d$
  - Weight nodes in network
    - Less weight = more potential to improve, prefer to cut
  - Compute **mincut** of nodes on weighted network
  - For each node in cutset
    - Partial collapse
  - For each node in cutset
    - timing redecompose

Penn ESE535 Spring 2009 -- DeHon

54

## Admin

- Reading
  - Monday (handout today)
- Next week
  - Lecture Monday
  - No lecture Wednesday → work on assignment
  - No office hours → ask questions about problems 1 and 2 before Monday

Penn ESE535 Spring 2009 -- DeHon

55

## Big Ideas

- Topological Worst-case delays are conservative
  - Once consider logical constraints
  - may have false paths
- Necessary and sufficient conditions on true paths
- Search for paths by delay
  - or demonstrate non existence
- Search with implications
- Iterative improvement

Penn ESE535 Spring 2009 -- DeHon

56