

ESE535: Electronic Design Automation


Day 20: April 4, 2011
Static Timing Analysis
and Multi-Level Speedup



Penn ESE535 Spring 2011 -- DeHon

Today

 
- Topological Worst Case
 - not adequate (too conservative)
- Sensitization Conditions
- Timed Calculus
- Delay-justified paths
 - Timed-PODEM
- Speedup



Penn ESE535 Spring 2011 -- DeHon

2

Topological Worst-Case Delay

 


- Compute ASAP schedule
 - Take max of arrival times
 - Apply node Delay

Penn ESE535 Spring 2011 -- DeHon

3

Topological Worst-Case Delay

 


- Node Delays

Penn ESE535 Spring 2011 -- DeHon

4

Topological Worst-Case Delay

 

- Compute Delays

Penn ESE535 Spring 2011 -- DeHon

5

False Paths

- Once consider logic for nodes
 - There are logical constraints on data values
- There are paths that cannot logically occur
 - Call them **false paths**

Penn ESE535 Spring 2011 -- DeHon

6

What can we do?

- Need to assess what paths are real
- Brute force
 - for every pair of inputs
 - compute delay in outputs from $in1 \rightarrow in2$ input transition
 - take worst case
- How many such delay traces?
 - 2^{2n} delay traces

Penn ESE535 Spring 2011 -- DeHon

7

Alternately

- Look at single vector and determine what controls delay of circuit
 - I.e. look at values on path and determine path *sensitized* to change with input

Penn ESE535 Spring 2011 -- DeHon

8

Controlling Inputs

- Controlling input to a gate:
 - input whose value will determine gate output
 - e.g.
 - 0 on a AND gate
 - 1 on a OR gate

Penn ESE535 Spring 2011 -- DeHon

9


Static Sensitization

- A path is statically sensitized
 - if all the side (non-path) inputs are non-controlling
 - I.e. this path value flips with the input

Penn ESE535 Spring 2011 -- DeHon

10

Statically Sensitized Path

 


Penn ESE535 Spring 2011 -- DeHon

11

Sufficiency

 - Static Sensitization is **sufficient** for a path to be a **true** path in circuit



Penn ESE535 Spring 2011 -- DeHon

12

Static Sensitization not Necessary

Penn ESE535 Spring 2011 -- DeHon 13

Static Sensitization not Necessary

- Possible path of length 3

Penn ESE535 Spring 2011 -- DeHon 14

Static Sensitization not Necessary

- Paths of length 3 not statically sensitizable.

Penn ESE535 Spring 2011 -- DeHon 15

Static Sensitization not Necessary

- True Path of Delay 3 (simulate)

Penn ESE535 Spring 2011 -- DeHon 16

Static Co-sensitization

- Each output with a controlled value
 - has a controlling value as input on path
 - (and vice-versa for non-controlled)


May trace multiple edges 17

Necessary

- Static Co-sensitization is a **necessary** condition for a path to be true

Penn ESE535 Spring 2011 -- DeHon 18

Cosensitization not Sufficient

 


Cosensitize path of length 6.
Real delay is 5.

Combining

- Combine these ideas into a timed-calculus for computing delays for an input vector




Computing Delays

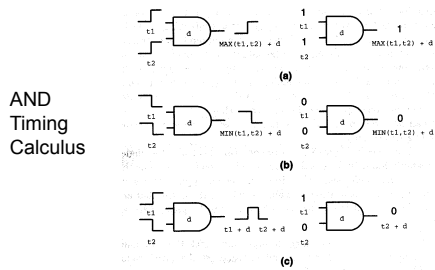


Rules

- If gate output is at a controlling value, pick the minimum input and add gate delay
- If gate output is at a non-controlling value, pick the maximum input and add gate delay


Example 1

 

Example 2

 

Example 2

 

Penn ESE535 Spring 2011 -- DeHon

25

Now...

- We know how to get the delay of a single input condition
- Could:
 - find critical path
 - search for an input vector to sensitize
 - if fail, find next path
 - ...until find longest true path
- May be $O(2^n)$

Penn ESE535 Spring 2011 -- DeHon

26

Better Approach

- Ask if can justify a delay greater than T
- Search for satisfying vector
 - ...or demonstration that none exists
- Binary search to find tightest delay

Penn ESE535 Spring 2011 -- DeHon

27

Delay Computation

- Modification of a testing routine
 - used to justify an output value for a circuit
 - similar to SAT
- PODEM (Path Oriented DEcision Making)
 - backtracking search to find a suitable input vector associated with some target output
 - branching search with implication pruning
 - Heuristic for smart variable ordering

Penn ESE535 Spring 2011 -- DeHon

28

Search

- Takes two lists
 - outputs to set; inputs already set
- Propagate values and implications
- If all outputs satisfied → succeed
- Pick next PI to set and set value
 - Search (recursive call) with this value set
 - If inconsistent
 - If PI not implied
 - Invert value of PI
 - Search with this value set
 - If inconsistent → fail
 - Else succeed
 - Else fail
 - Else succeed

Penn ESE535 Spring 2011 -- DeHon

29


Picking next variable to set

- Follow back gates w/ unknown values
 - sometimes output dictate input must be
 - (AND needing 1 output; with one input already assigned 1)
 - Implication
 - sometimes have to guess what to follow
 - (OR with 1 output and no inputs set)
 - Uses heuristics to decide what to follow

Penn ESE535 Spring 2011 -- DeHon

30


Example

 

Penn ESE535 Spring 2011 -- DeHon

31

Example (goal g=1)

 


Penn ESE535 Spring 2011 -- DeHon

32

Example (goal g=1)

- Try B=1

 


Penn ESE535 Spring 2011 -- DeHon

33

Example (goal g=1)

- Try B=0

 


Deduce any inputs?

Penn ESE535 Spring 2011 -- DeHon

34

Example (goal g=1)

- Implied A=0

 


Deduce any inputs?

Penn ESE535 Spring 2011 -- DeHon

35

Example (goal g=1)

- Implied C=1

 

Penn ESE535 Spring 2011 -- DeHon

36

For Timed Justification

- Also want to compute delay
 - on incompletely specified values
- Compute bounds on timing
 - upper bound, lower bound
 - Again, use our timed calculus
 - expanded to unknowns

Delay Calculation

AND rules


| $i_1 \rightarrow$ $i_2 \downarrow$ | 0 | 1 | ? |
|---------------------------------------|---|---|---|
| 0 | 0 $MIN(l_1, l_2) + d$ $MIN(u_1, u_2) + d$ | 0 $l_2 + d$ $u_2 + d$ | 0 $MIN(l_1, l_2) + d$ $u_2 + d$ |
| 1 | 0 $l_1 + d$ $u_1 + d$ | 1 $MAX(l_1, l_2) + d$ $MAX(u_1, u_2) + d$ | 2 $l_1 + d$ $MAX(u_1, u_2) + d$ |
| ? | 0 $MIN(l_1, l_2) + d$ $u_1 + d$ | 2 $l_2 + d$ $MAX(u_1, u_2) + d$ | 2 $MIN(l_1, l_2) + d$ $MAX(u_1, u_2) + d$ |

Unknowns force us to represent upper/lower bound on delay.

Timed PODEM


- **Input:** value to justify and delay T
- **Goal:** find input vector which produces value and exceeds delay T
- Algorithm
 - similar
 - implications check timing as well as logic

Example (goal $g=1@3$)

 


Example (goal $g=1@3$)

- Try $B=1$

 

Example (goal $g=1@3$)


- Try $B=0$

 

Deduce any inputs?

Example


- Imply A=0

 

Deduce any inputs?

Example (goal g=1@3)


- Imply C=1

 

Failed to justify 1@3

Example (goal g=0@3)

- Try C=1

 

Search

- Less than 2^n
 - pruning due to implications
 - here saw a must be 0
 - no need to search 1xx subtree

Questions

- Any questions on static timing analysis?

Speed Up

(sketch flavor)

Speed Up


- Start with area optimized network
- Know target arrival times
 - Know delay from static analysis
- Want to reduce delay of node

Penn ESE535 Spring 2011 -- DeHon

49

Basic Idea

 - Improve speed by:
 - Collapsing node(s)
 - Refactoring collapsed subgraph to reduce height



Penn ESE535 Spring 2011 -- DeHon

50

Speed Up


- While (delay decreasing, timing not met)
 - Compute delay (slack)
 - Static timing analysis
 - Generate network close to critical path
 - w in some delay ϵ , to some distance d
 - Weight nodes in network
 - Less weight = more potential to improve, prefer to cut
 - Compute **mincut** of *nodes* on weighted network
 - For each node in cutset
 - Partial collapse
 - For each node in cutset
 - Timing redecompose

Penn ESE535 Spring 2011 -- DeHon

51

MinCut of Nodes

 - Cut nodes not edges
 - Typically will need to transform to dual graph
 - All edges become nodes, nodes become edges
 - Then use maxflow/mincut




Penn ESE535 Spring 2011 -- DeHon

52

MinCut of Nodes


- What are possible cuts?

 

Penn ESE535 Spring 2011 -- DeHon

53


MinCut of Nodes

 

Penn ESE535 Spring 2011 -- DeHon

54

MinCut of Nodes

 

Penn ESE535 Spring 2011 -- DeHon

55

Weighted Cut


- $W = W_t + \alpha W_a \rightarrow \alpha$ tuning parameter
- Want to minimize area expansion (W_a)
 - Things in collapsed network may be duplicated
 - E.g. W_a = literals in duplicated logic
- Want to maximize likely benefit (W_t)
 - Prefer nodes with different input times to the “near critical path” network
 - Quantify: large difference in arrival times
 - Prefer nodes with critical path on longer paths

Penn ESE535 Spring 2011 -- DeHon

56

Weighing Benefit

 - Want to maximize likely benefit (W_t)
 - Prefer nodes with different input times to the “near critical path” network




Penn ESE535 Spring 2011 -- DeHon

57

Weighing Benefit

 - Want to maximize likely benefit (W_t)
 - Prefer nodes with critical path on longer paths



Penn ESE535 Spring 2011 -- DeHon

58

Timing Decomposition

- Extract area saving kernels that do not include critical inputs to node
 - $f = abcd + abce + abef$
 - Kernels = $\{cd + ce + ef, e + d, c + f\}$ (next time)
 - $F = abe(c+f) + abcd, ab(cd + ce + ef), abc(e+d) + abef$
 - What decomposition use (and how finish decompose)?
 - Critical input is f? e? d? $\{a, d\}$?
- When decompose (e.g. into nand2's) similarly balance with critical inputs closest to output

Penn ESE535 Spring 2011 -- DeHon

59

Delay Decompositions

- f last:
 - $abc(e+d) + abef$
 - $f*((ab)e) + ((ab)(c(e+d)))$
- e last:
 - $abe(c+f) + abcd$
 - $e*((*ab)(c+f)) + ((ab)(cd))$

Penn ESE535 Spring 2011 -- DeHon

60

Delay Decompositions

- d last:
 - $abe(c+f)+abcd$
 - $d*((ab)c)+((ab)(e(c+f)))$
- {a,d} last:
 - $abe(c+f)+abcd$
 - $a((be)(c+f)+d(bc))$

Speed Up (review)

- While (delay decreasing, timing not met)
 - Compute delay (slack)
 - Static timing analysis
 - Generate network close to critical path
 - w/in some delay ϵ , to some distance d
 - Weight nodes in network
 - Less weight = more potential to improve, prefer to cut
 - Compute **mincut** of nodes on weighted network
 - For each node in cutset
 - Partial collapse
 - For each node in cutset
 - timing redecompose

Admin

- Reading Wednesday on blackboard
- Assignment 5 graded
- Try to look at Assign 6 tonight
- Normal office hours this week (T)
- Next week office hours (4/12)
 - pushed back 5:35pm

Big Ideas

- Topological Worst-case delays are conservative
 - Once consider logical constraints
 - may have false paths
- Necessary and sufficient conditions on true paths
- Search for paths by delay
 - or demonstrate non existence
- Search with implications
- Iterative improvement