

ESE535: Electronic Design Automation

Day 24: April 18, 2011
Covering and Retiming




Previously


- Cover (map) LUTs for minimum delay
 - solve optimally for delay → flowmap
- Retiming for minimum clock period
 - solve optimally

Today

 - Solving cover/retime separately **not** optimal
- Cover+retime




Example

 








Cover with 4-LUTs

Example

 

Example: Retimed

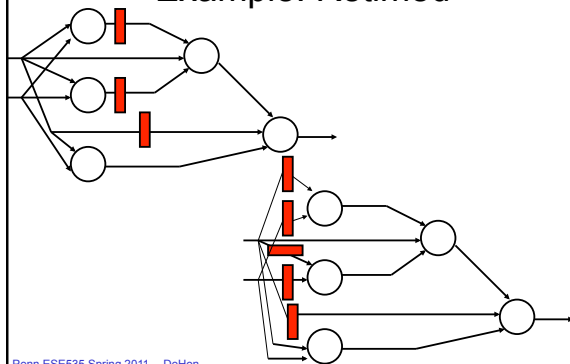

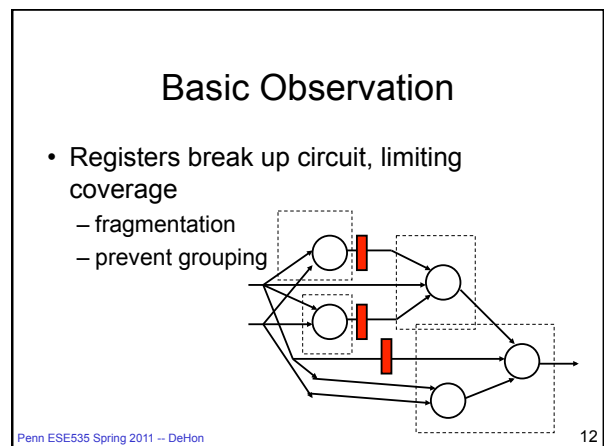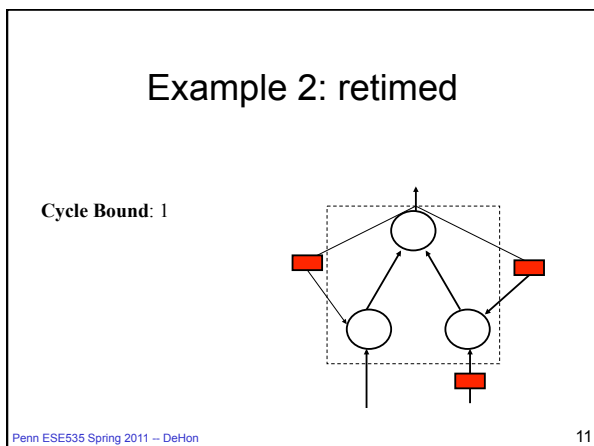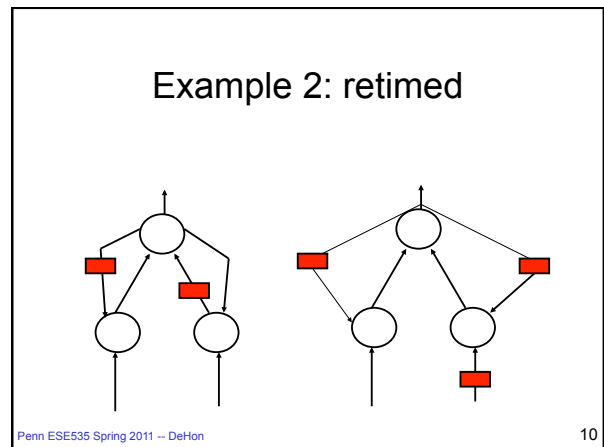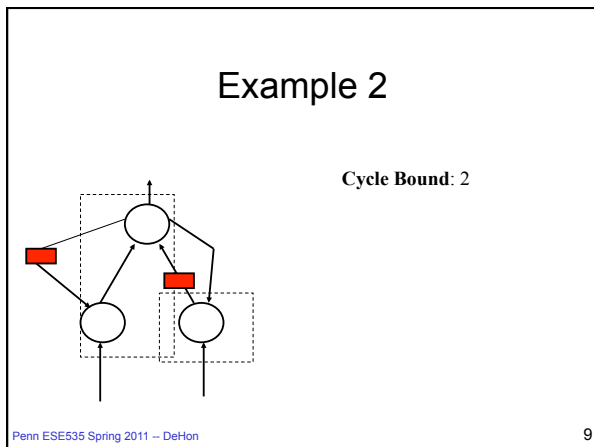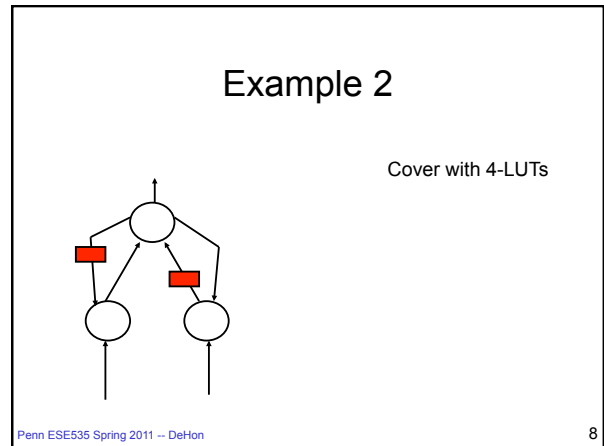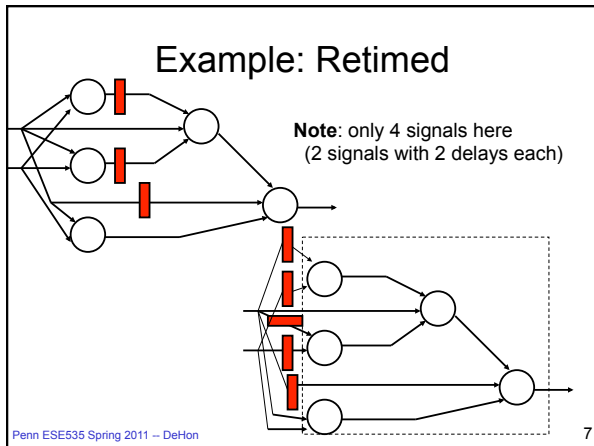

Phase Ordering Problem


- General problem
 - don't know effect of other mapping step
 - Will see this many places
- Here
 - don't know delay if retime first
 - don't know what can be packed into LUT
 - If we do not retime first
 - fragmentation: forced breaks at bad places

Penn ESE535 Spring 2011 -- DeHon

13

Observation #1

 - Retiming flops to input of (fanout free) subgraph is trivial (and always doable)



- Does not change I/O into subgraph

Penn ESE535 Spring 2011 -- DeHon

14


Observation #1: Consequence

- Can cover *ignoring* flop placement
- Then retime flops to input of gates

Penn ESE535 Spring 2011 -- DeHon

15

Fanout Problem?

 


Can we use the same trick here?

Penn ESE535 Spring 2011 -- DeHon


16

Fanout Problem?

 

Cannot retime without replicating.

Replicating increases I/O (so cut size).

 

...but I/O is what defined feasible covers for LUTs


3 cut \rightarrow 5 cut

Penn ESE535 Spring 2011 -- DeHon

17

Observation #2

 
- Retiming flops to input of a subgraph with fanout may change the subgraph I/O



Penn ESE535 Spring 2011 -- DeHon

18

Different Replication Problem

 


What does this do to I/O?

Penn ESE535 Spring 2011 -- DeHon

19


Different Replication Problem

 

Penn ESE535 Spring 2011 -- DeHon

20

Different Replication Problem

 

Can retime and cover with single 4-LUT.

Penn ESE535 Spring 2011 -- DeHon

21


Replication

- Once add registers
 - can't just grab max flow and get replication
 - (compare flowmap)
- Or, can't just ignore flop placement when have reconvergent fanout through flop

Penn ESE535 Spring 2011 -- DeHon

22

Replication

 

- Key idea:
 - represent timing paths in graph
 - differentiating based on number of registers in path
 - **new graph**: all paths from node to output have same number of flip-flops
 - label nodes u^d where d is flip-flops to output

Penn ESE535 Spring 2011 -- DeHon







23



Deal with Replication

- *Expanded Graph*:
 - start with target output node
 - for each input u^d to current expanded graph
 - grab its input edge ($x \rightarrow u$) with weight ($w(e)$)
 - add node $x^{(d+w(e))}$ to graph (if necessary)
 - add edge $x^{(d+w(e))} \rightarrow u^d$ with weight ($w(e)$)
 - continue breadth first until have enough
 - at most $k \times n$ node depth required

Penn ESE535 Spring 2011 -- DeHon

24

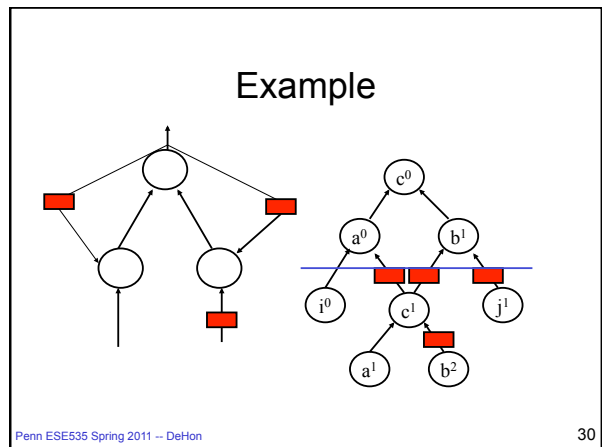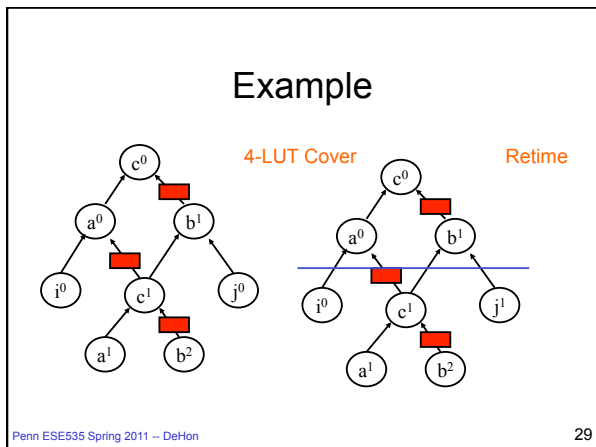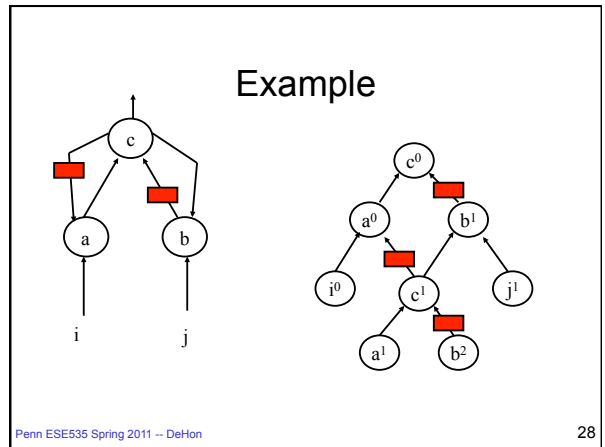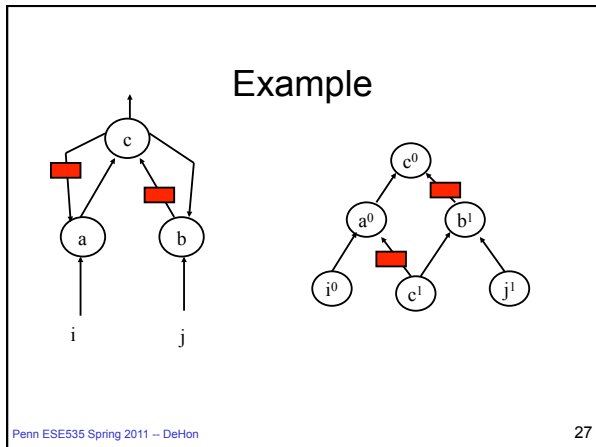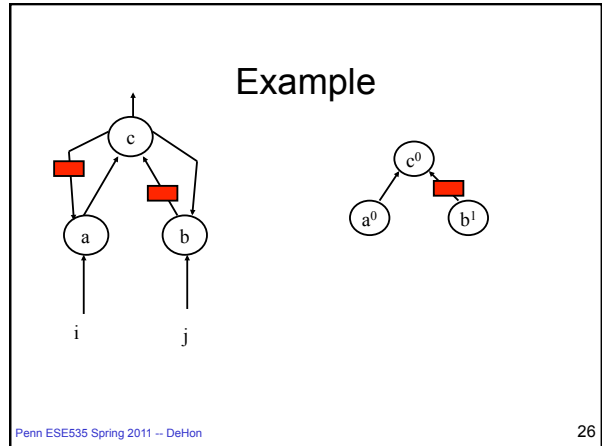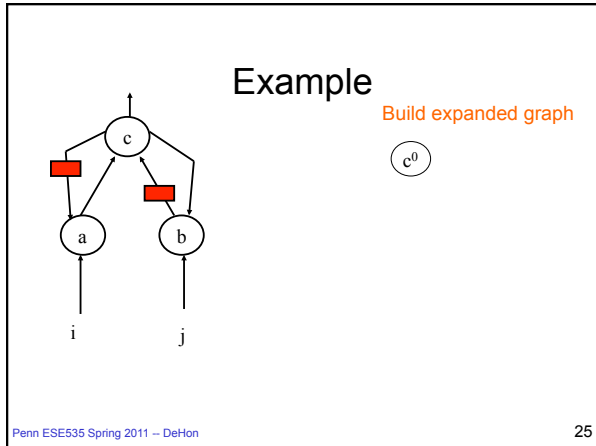

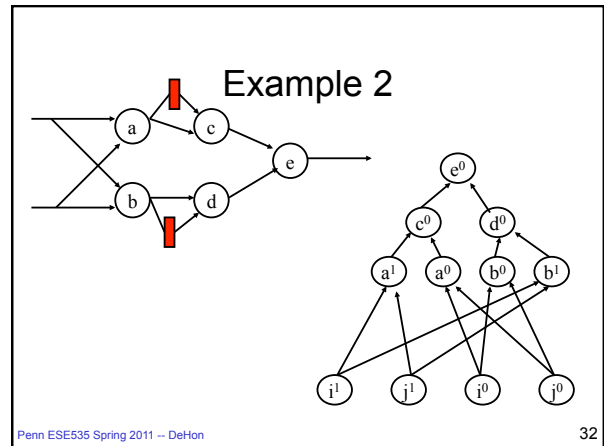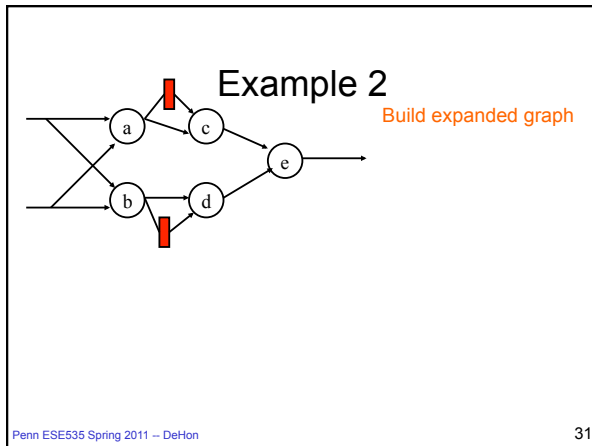

Expanded Graph

- Expanded graph does not have fanout of different flip-flop depths from the **same** node.
 - Captures IO after register retiming
- Can now cover ignoring flip-flops and trivially retime.

Penn ESE535 Spring 2011 -- DeHon 33

Labeling

- Key idea #1:
 - compute distances/delay like flowmap
 - Try collapse and compute flow cut
 - Dynamic programming to compute min delay covers
- Key idea #2:
 - count distance from register
 - like G-1/c graph

Penn ESE535 Spring 2011 -- DeHon 34

Labeling: Edge Weights

- To target clock period c
 - use graph $G-1/c$
 - paper:
 - assign weight $-c*w(e)+1$
 - (same thing scaled by c and negated)

Penn ESE535 Spring 2011 -- DeHon 35

Labeling: Edge Weight Idea

- same idea:
 - will need register ever c LUT delays
 - credit with registers as encounter
 - charge a fraction $(1/c)$ every LUT delay
 - know net distance at each point
 - if negative (delays $> c*$ registers)
 - cannot distribute to achieve c
 - otherwise
 - labeling tells where to distribute

Penn ESE535 Spring 2011 -- DeHon 36

Labeling: Flow cut

- Label node as before (flowmap)
 - $L(v) = \min\{l(u) + w(e) \mid \exists u \rightarrow v\}$
 - trivially can be $L(v) - 1/c ==$ new LUT
 - Correspond to flowmap case: $L(v) + 1$
 - note min vs. max and $-1/c$ vs. $+1$ due to rescaling to match retiming formulation and $G-1/c$ graph
 - in this formulation, a combinational circuit of depth 4 would have $L(v) = -4/c$
 - if can put this and all $L(v)$'s in one LUT
 - this can be $L(v)$
 - construct and compute flow cut to test

Penn ESE535 Spring 2011 -- DeHon

37

LUT Map and Retime

- Start with outputs
- Cover with LUT based on cut
 - move flip-flops to inputs of LUT
 - don't have meaningful labels for covered nodes
 - Know can do this by expanded graph construction
- Recursively cover inputs
- Use label to retime
 - $r(v) = \lceil l(v) \rceil - 1$

Penn ESE535 Spring 2011 -- DeHon

38

Target Clock Period c

- As before (retiming)
 - binary search to find optimal c

Penn ESE535 Spring 2011 -- DeHon

39

Summary

- Can optimally solve
 - LUT map for delay
 - retiming for minimum clock period
- But, solving separately does not give optimal solution to problem
- Can solve problems together
 - Account for registers on paths
 - Label based on register placement and (flow) cover ignoring registers
 - Labeling gives delay, covering, retiming

Penn ESE535 Spring 2011 -- DeHon

40

Admin

- Office hours pushed back this week
 - T5:30pm
- Wednesday reading online

Penn ESE535 Spring 2011 -- DeHon

41

Today's Big Ideas

- Exploit freedom
- Cost of decomposition
 - benefit of composite solution
- Technique:
 - dynamic programming
 - network flow

Penn ESE535 Spring 2011 -- DeHon

42