

ESE535: Electronic Design Automation


Day 23: April 20, 2015
Static Timing Analysis
and Multi-Level Speedup



Penn ESE535 Spring 2015 – DeHon

Delay of Preclass


- Delay?
- What transition causes?

 

2

Today

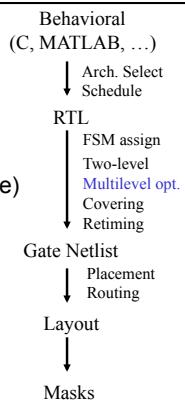
- Topological Worst Case
 - not adequate (too conservative)
- Sensitization Conditions
- Timed Calculus
- Delay-justified paths
 - Timed-PODEM
- Speedup



3

Topological Worst-Case Delay

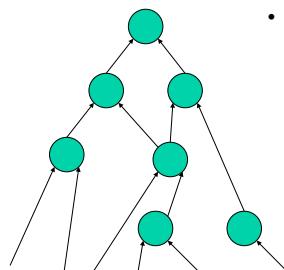
- Compute ASAP schedule
 - Take max of arrival times
 - Apply node Delay



4

Topological Worst-Case Delay

- Node Delays

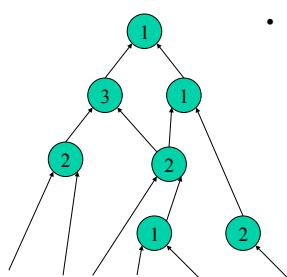


Penn ESE535 Spring 2015 – DeHon

5

Topological Worst-Case Delay

- Compute Delays

 

Penn ESE535 Spring 2015 – DeHon

6

False Paths

- Once consider logic for nodes
 - There are logical constraints on data values
- There are paths that cannot logically occur
 - Call them **false paths**

Penn ESE535 Spring 2015 – DeHon

7

What can we do?

- Need to assess what paths are real
- Brute force
 - for every pair of inputs
 - compute delay in outputs from $\text{in1} \rightarrow \text{in2}$ input transition
 - take worst case
- How many such delay traces?
 - 2^{2n} delay traces

Penn ESE535 Spring 2015 – DeHon

8

Alternately

- Look at single vector and determine what controls delay of circuit
 - I.e. look at values on path and determine path *sensitized* to change with input

Penn ESE535 Spring 2015 – DeHon

9

Controlling Inputs

- Controlling input to a gate:
 - input whose value will determine gate output
 - e.g.
 - 0 on a AND gate
 - 1 on a OR gate

Penn ESE535 Spring 2015 – DeHon

10


Static Sensitization

- A path is statically sensitized
 - if all the side (non-path) inputs are non-controlling
 - I.e. this path value flips with the input

Penn ESE535 Spring 2015 – DeHon

11

Statically Sensitized Path

 


Penn ESE535 Spring 2015 – DeHon

12

Sufficiency

 
- Static Sensitization is **sufficient** for a path to be a **true** path in circuit



Penn ESE535 Spring 2015 – DeHon

13


Static Sensitization not Necessary

 

Penn ESE535 Spring 2015 – DeHon

14


Static Sensitization not Necessary

 

Penn ESE535 Spring 2015 – DeHon

15


Static Sensitization not Necessary

 

Penn ESE535 Spring 2015 – DeHon

16


Static Sensitization not Necessary

 

Penn ESE535 Spring 2015 – DeHon

17

Static Sensitization not Necessary

 


Penn ESE535 Spring 2015 – DeHon

18

Static Sensitization not Necessary

- True Path of Delay 3 (simulate)

 


Penn ESE535 Spring 2015 – DeHon

19

Static Co-sensitization

 - Each output with a controlled value
 - has a controlling value as input on path
 - (and vice-versa for non-controlled)




Penn ESE535 Spring 2015 – DeHon

20

Necessary

 - Static Co-sensitization is a **necessary** condition for a path to be true




Penn ESE535 Spring 2015 – DeHon

21

Static Co-sensitization

 - Each output with a controlled value
 - has a controlling value as input on path
 - (and vice-versa for non-controlled)
- What is co-sensitization path length (0 output)?




Penn ESE535 Spring 2015 – DeHon

22

Static Co-sensitization

 
- Each output with a controlled value
 - has a controlling value as input on path
 - (and vice-versa for non-controlled)
- What is co-sensitization path length (1 output)?



Penn ESE535 Spring 2015 – DeHon

23


Transitions

 

Penn ESE535 Spring 2015 – DeHon

24

Cosensitization not Sufficient

 

Penn ESE535 Spring 2015 – DeHon

25

Combining

- Combine these ideas into a timed-calculus for computing delays for an input vector




Penn ESE535 Spring 2015 – DeHon

26

Computing Delays

AND
Timing
Calculus

 

Penn ESE535 Spring 2015 – DeHon

27


Rules

- If gate output is at a controlling value, pick the minimum input and add gate delay
- If gate output is at a non-controlling value, pick the maximum input and add gate delay

Penn ESE535 Spring 2015 – DeHon

28


Example 1

 

Penn ESE535 Spring 2015 – DeHon

29


Example 2

 

Penn ESE535 Spring 2015 – DeHon

30

Example 2

 

Penn ESE535 Spring 2015 – DeHon

31

Now...

- We know how to get the delay of a single input condition
- Could:
 - find “candidate” critical path
 - search for an input vector to sensitize
 - if fail, find next path
 - ...until find longest true path
- May be $O(2^n)$

Penn ESE535 Spring 2015 – DeHon

32

Better Approach

- Ask if can justify a delay greater than T
- Search for satisfying vector
 - ...or demonstration that none exists
- Binary search to find tightest delay

Penn ESE535 Spring 2015 – DeHon

33

Delay Computation

- Modification of a testing routine
 - used to justify an output value for a circuit
 - similar to SAT
- PODEM (Path Oriented DEcision Making)
 - backtracking search to find a suitable input vector associated with some target output
 - branching search with implication pruning
 - Heuristic for smart variable ordering

Penn ESE535 Spring 2015 – DeHon

34

Search

- Takes two lists
 - outputs to set; inputs already set
- Propagate values and implications
- If all outputs satisfied \rightarrow succeed
- Pick next PI to set and set value
 - Search (recursive call) with this value set
 - If inconsistent
 - If PI not implied
 - Invert value of PI
 - Search with this value set
 - If inconsistent \rightarrow fail
 - Else succeed
 - Else fail
 - Else succeed

Penn ESE535 Spring 2015 – DeHon

35


Picking next variable to set

- Follow back gates w/ unknown values
 - sometimes output dictate input must be
 - (AND needing 1 output; with one input already assigned 1)
 - Implication
 - sometimes have to guess what to follow
 - (OR with 1 output and no inputs set)
 - Uses heuristics to decide what to follow

Penn ESE535 Spring 2015 – DeHon

36


Example

 

Penn ESE535 Spring 2015 – DeHon

37

Example (goal $g=1$)

 


Penn ESE535 Spring 2015 – DeHon

38

Example (goal $g=1$)

- Try $B=1$

 


Penn ESE535 Spring 2015 – DeHon

39

Example (goal $g=1$)

- Try $B=0$

 


Penn ESE535 Spring 2015 – DeHon

40

Example (goal $g=1$)

- Implied $A=0$

 


Deduce any inputs?

Penn ESE535 Spring 2015 – DeHon

41

Example (goal $g=1$)

- Implied $C=1$

 

Penn ESE535 Spring 2015 – DeHon

42

For Timed Justification

- Also want to compute delay
 - on incompletely specified values
- Compute bounds on timing
 - upper bound, lower bound
 - Again, use our timed calculus
 - expanded to unknowns

Penn ESE535 Spring 2015 – DeHon

43

Delay Calculation

AND rules

$i_1 \rightarrow$	0	1	?
$i_2 \downarrow$			
0	0 $\text{MIN}(l_1, l_2) + d$ $\text{MIN}(u_1, u_2) + d$	0 $l_2 + d$ $u_2 + d$	0 $\text{MIN}(l_1, l_2) + d$ $u_2 + d$
1	0 $l_1 + d$ $u_1 + d$	1 $\text{MAX}(l_1, l_2) + d$ $\text{MAX}(u_1, u_2) + d$	2 $l_1 + d$ $\text{MAX}(u_1, u_2) + d$
2	0 $l_2 + d$ $u_1 + d$	2 $\text{MIN}(l_1, l_2) + d$ $\text{MAX}(u_1, u_2) + d$	2 $\text{MIN}(l_1, l_2) + d$ $\text{MAX}(u_1, u_2) + d$

Unknowns force us to represent upper/lower bound on delay.

Penn ESE535 Spring 2015 – DeHon

44

Timed PODEM


- Input:** value to justify and delay T
- Goal:** find input vector which produces value and exceeds delay T
- Algorithm
 - similar
 - implications check timing as well as logic

Penn ESE535 Spring 2015 – DeHon

45

Example (goal g=1@3)

- Work d, e, f, g

 


Penn ESE535 Spring 2015 – DeHon

46

Example (goal g=1@3)

- Try B=1 (work d, g)

 


Penn ESE535 Spring 2015 – DeHon

47

Example (goal g=1@3)

- Try B=0 (work d, e, f, g)

 


Penn ESE535 Spring 2015 – DeHon

48

Deduce any inputs?

Example

- Imply $A=0$ (work d, g)

 


Deduce any inputs?

49

Penn ESE535 Spring 2015 – DeHon

Example (goal $g=1@3$)

- Imply $C=1$ (work f, g)

 


Failed to justify $1@3$

50

Penn ESE535 Spring 2015 – DeHon

Example (goal $g=0@3$)

- Try $C=0$ (work f, g)

 

51

Penn ESE535 Spring 2015 – DeHon

Search

- Less than 2^n

- pruning due to implications
- here saw a must be 0
 - no need to search 1xx subtree

52

Penn ESE535 Spring 2015 – DeHon

Questions

- Any questions on static timing analysis?

53

Penn ESE535 Spring 2015 – DeHon

Speed Up

(sketch flavor)

54

Penn ESE535 Spring 2015 – DeHon

Speed Up


- Start with area optimized network
- Know target arrival times
 - Know delay from static analysis
- Want to reduce delay of node

Penn ESE535 Spring 2015 – DeHon

55

Basic Idea

 - Improve speed by:
 - Collapsing node(s)
 - Refactoring collapsed subgraph to reduce height



Penn ESE535 Spring 2015 – DeHon

56

Timing Decomposition

- Extract area saving kernels that do not include critical inputs to node
 - $f = abcd + abce + abef$
 - Kernels = { $cd + ce + ef, e + d, c + f$ } (last time)
 - $F = abe(c + f) + abcd, ab(cd + ce + ef), abc(e + d) + abef$
 - What decomposition use
(and how finish decompose)?
 - Critical input is e? f? d? {a,d}?
- When decompose (e.g. into nand2's) similarly balance with critical inputs closest to output

Penn ESE535 Spring 2015 – DeHon

57

Delay Decompositions

- f last:
 - $abc(e + d) + abef$
 - $f^*((ab)e) + ((ab)(c(e + d)))$
- e last:
 - $abe(c + f) + abcd$
 - $e^*((ab)(c + f)) + ((ab)(cd))$

Penn ESE535 Spring 2015 – DeHon

58

Delay Decompositions

- d last:
 - $abe(c + f) + abcd$
 - $d^*((ab)c) + ((ab)(e(c + f)))$
- $\{a, d\}$ last:
 - $abe(c + f) + abcd$
 - $a((be)(c + f) + d(bc))$

Penn ESE535 Spring 2015 – DeHon

59

Speed Up

- While (delay decreasing, timing not met)
 - Compute delay (slack)
 - Static timing analysis
 - Generate network close to critical path
 - Within some delay ϵ , to some distance d
 - Weight nodes in network
 - Less weight = more potential to improve, prefer to cut
 - Compute **mincut** of **nodes** on weighted network
 - For each node in cutset
 - Partial collapse
 - For each node in cutset
 - Timing redecompose

Penn ESE535 Spring 2015 – DeHon

60

Weighted Cut


- $W = W_t + \alpha W_a \rightarrow \alpha$ tuning parameter
- Want to minimize area expansion (W_a)
 - Things in collapsed network may be duplicated
 - E.g. W_a = literals in duplicated logic
- Want to maximize likely benefit (W_t)
 - Prefer nodes with different input times to the “near critical path” network
 - Quantify: large difference in arrival times
 - Prefer nodes with critical path on longer paths

Penn ESE535 Spring 2015 – DeHon

61

Weighing Benefit

 
- Want to maximize likely benefit (W_t)
 - Prefer nodes with different input times to the “near critical path” network



62

Weighing Benefit

 
- Want to maximize likely benefit (W_t)
 - Prefer nodes with critical path on longer paths



63

MinCut of Nodes

 
- Cut nodes not edges
 - Typically will need to transform to dual graph
 - All edges become nodes, nodes become edges
 - Then use maxflow/mincut



64

MinCut of Nodes

- MinCut given this weighting?

 

65

Speed Up (review)

- While (delay decreasing, timing not met)
 - Compute delay (slack)
 - Static timing analysis
 - Generate network close to critical path
 - w/in some delay ϵ , to some distance d
 - Weight nodes in network
 - Less weight = more potential to improve, prefer to cut
 - Compute **mincut** of **nodes** on weighted network
 - For each node in cutset
 - Partial collapse
 - For each node in cutset
 - timing recompute

Penn ESE535 Spring 2015 – DeHon

66

Big Ideas

- Topological Worst-case delays are conservative
 - Once consider logical constraints
 - may have false paths
- Necessary and sufficient conditions on true paths
- Search for paths by delay
 - or demonstrate non existence
- Search with implications
- Iterative improvement

Penn ESE535 Spring 2015 – DeHon

67

Admin

- Reading Wednesday on web

Penn ESE535 Spring 2015 – DeHon

68