

ECE 250 / CPS 250
Computer Architecture


Basics of Logic Design
ALU and Storage Elements

Benjamin Lee

Slides based on those from

Andrew Hilton (Duke), Alvy Lebeck (Duke)
Benjamin Lee (Duke), and Amir Roth (Penn)


The ALU

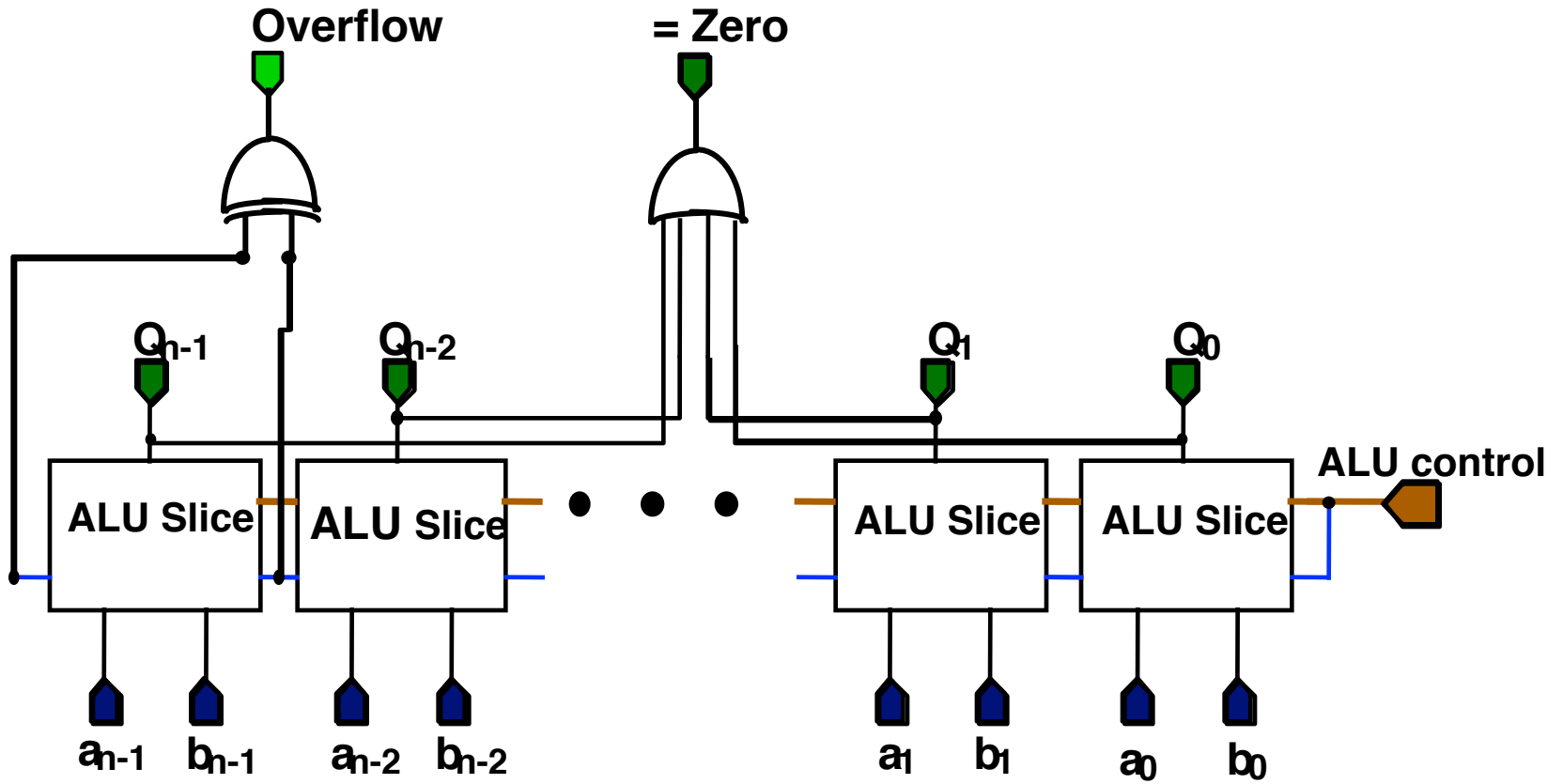

Abstraction: The ALU

- **General structure**
- **Two operand inputs**
- **Control inputs**

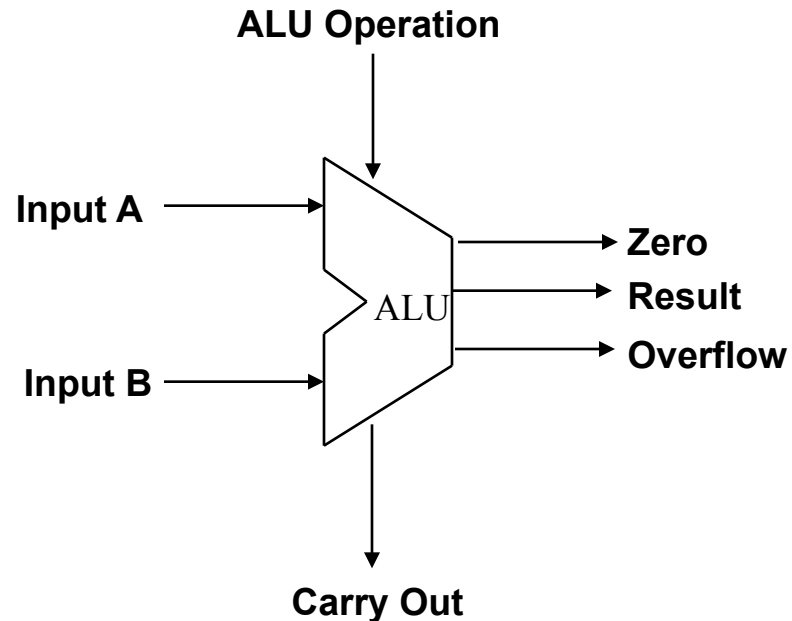- **We can build circuits for**
 - **Multiplication**
 - **Division**
 - **They are more complex**




Another Operations We Might Want: Shift

- Remember the << and >> operations?
 - Shift left/shift right?
 - How would we implement these?
- Suppose you have an 8-bit number
 $b_7b_6b_5b_4b_3b_2b_1b_0$
- And you can shift it left by a 3-bit number
 $s_2s_1s_0$
- Option 1: Truth Table?
 - $2^{11} = 2048$ rows? Yuck.


Let's simplify

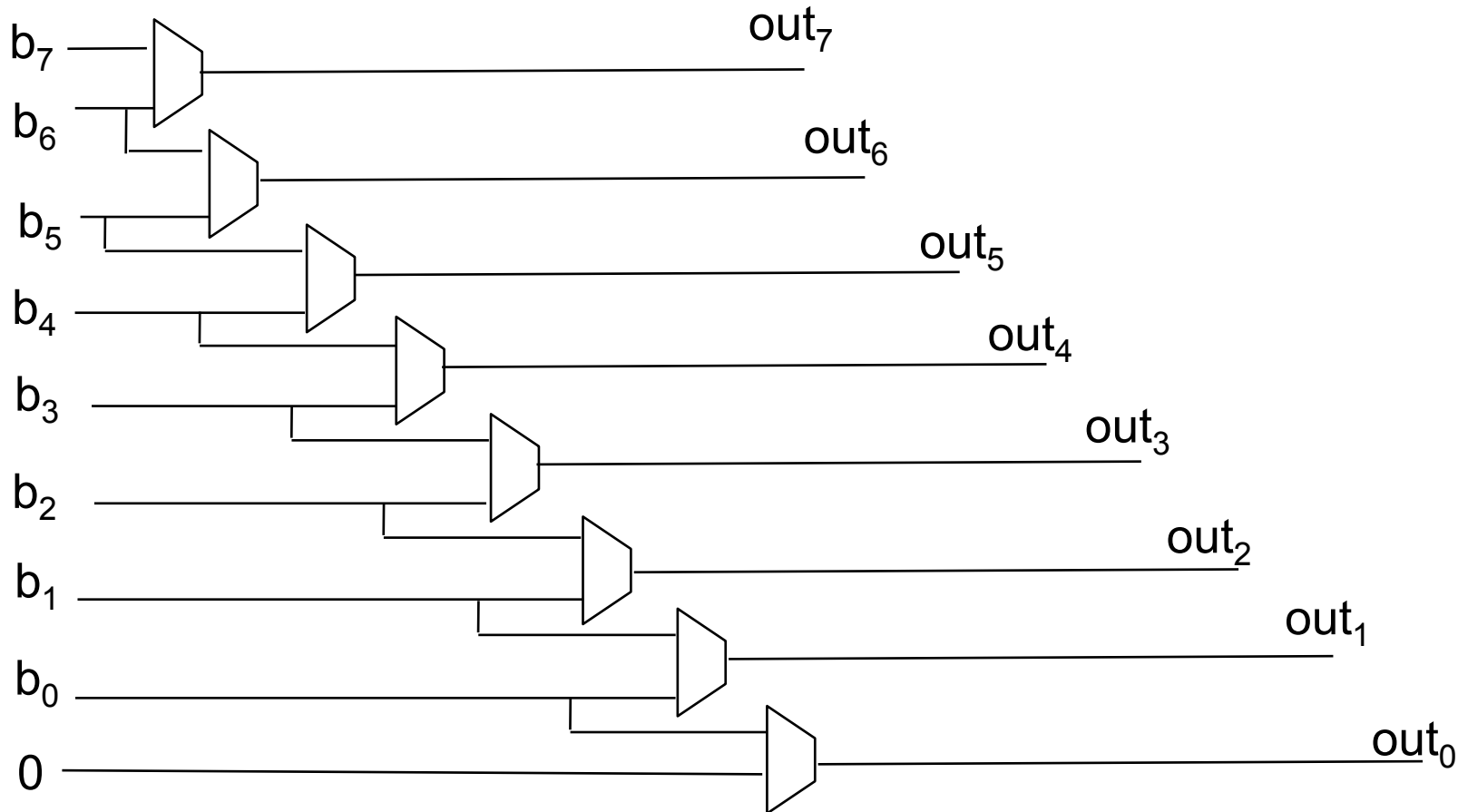- **Simpler problem: 8-bit number shifted by 1 bit number (shift amount selects each mux)**




Let's simplify

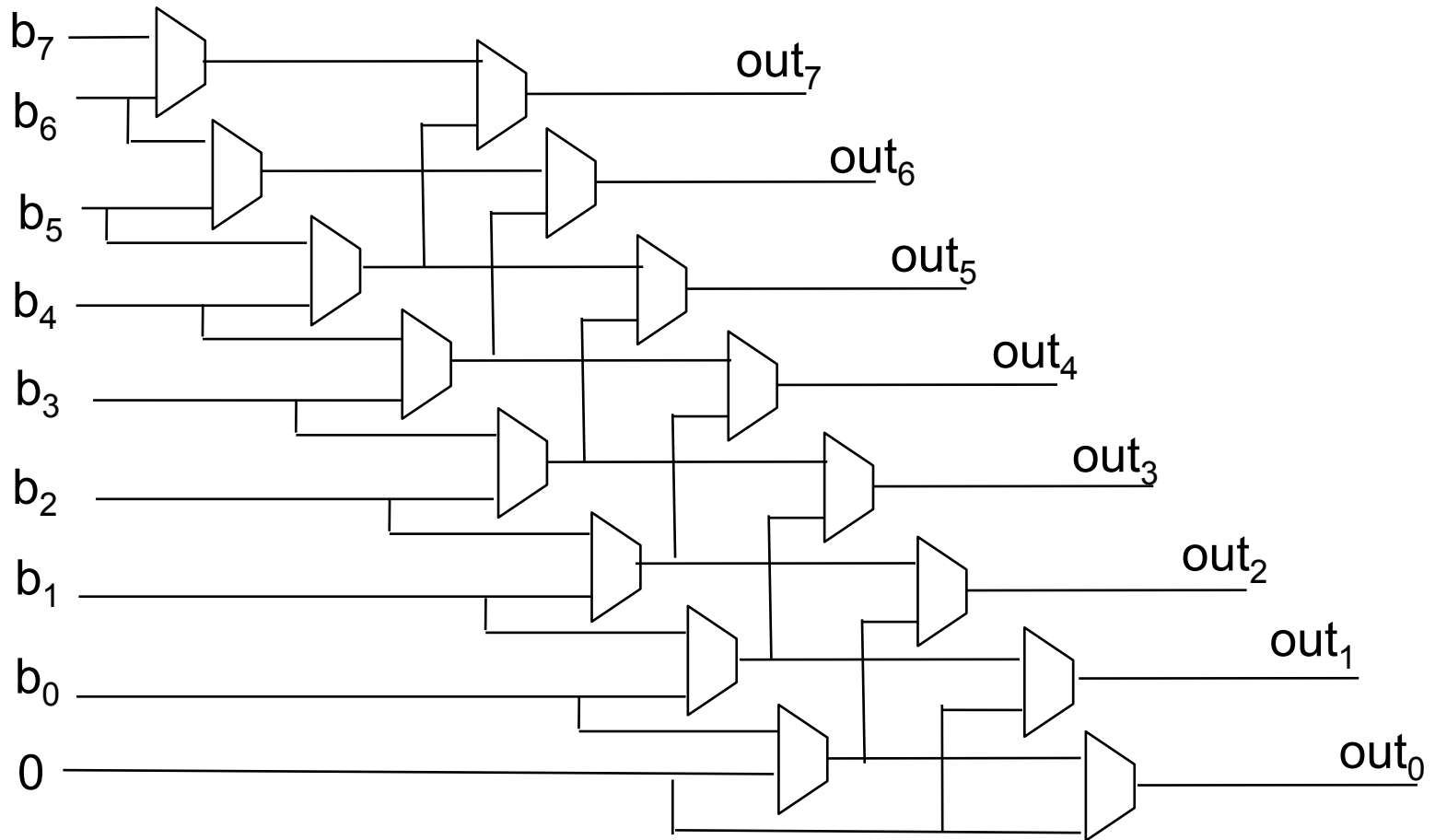- **Simpler problem: 8-bit number shifted by 2 bit number**




Now shifted by 3-bit number

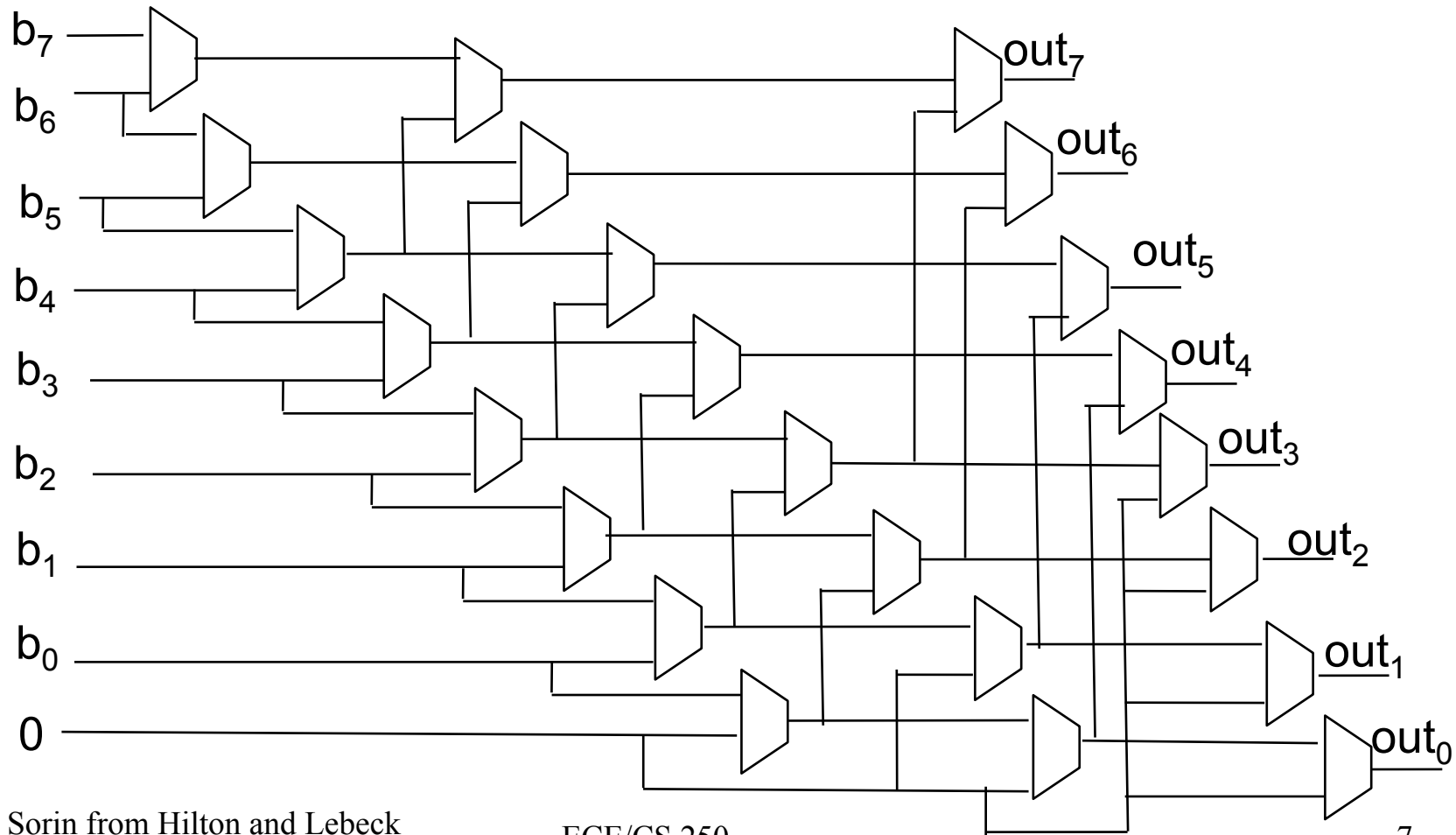- Full problem: 8-bit number shifted by 3 bit number




Now shifted by 3-bit number

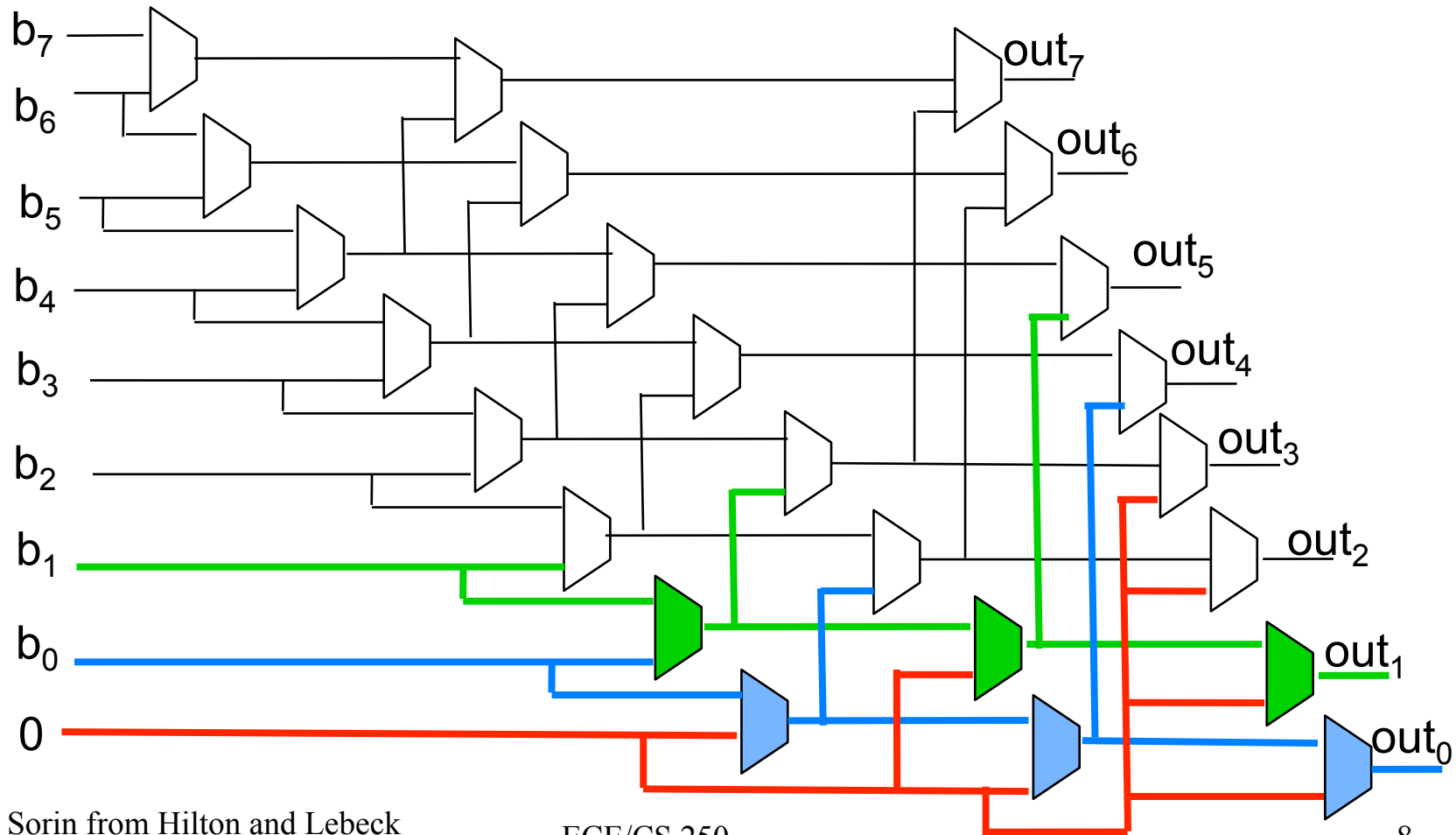- **Shifter in action: shift by 000 (all muxes have S=0)**




Now shifted by 3-bit number

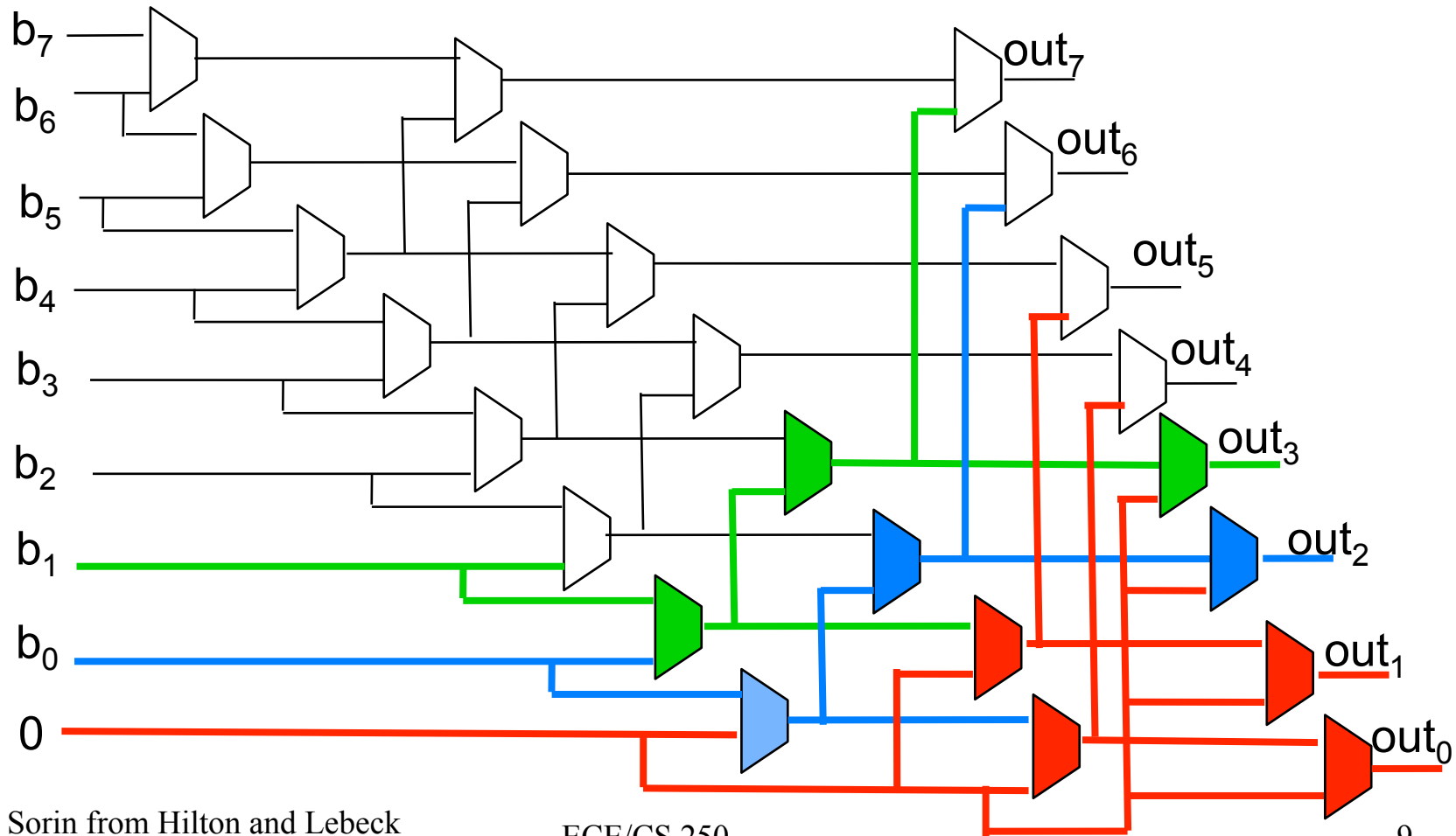- **Shifter in action: shift by 010**
 - Mux control signals from R to L: **S = 0, 1, 0**



Now shifted by 3-bit number

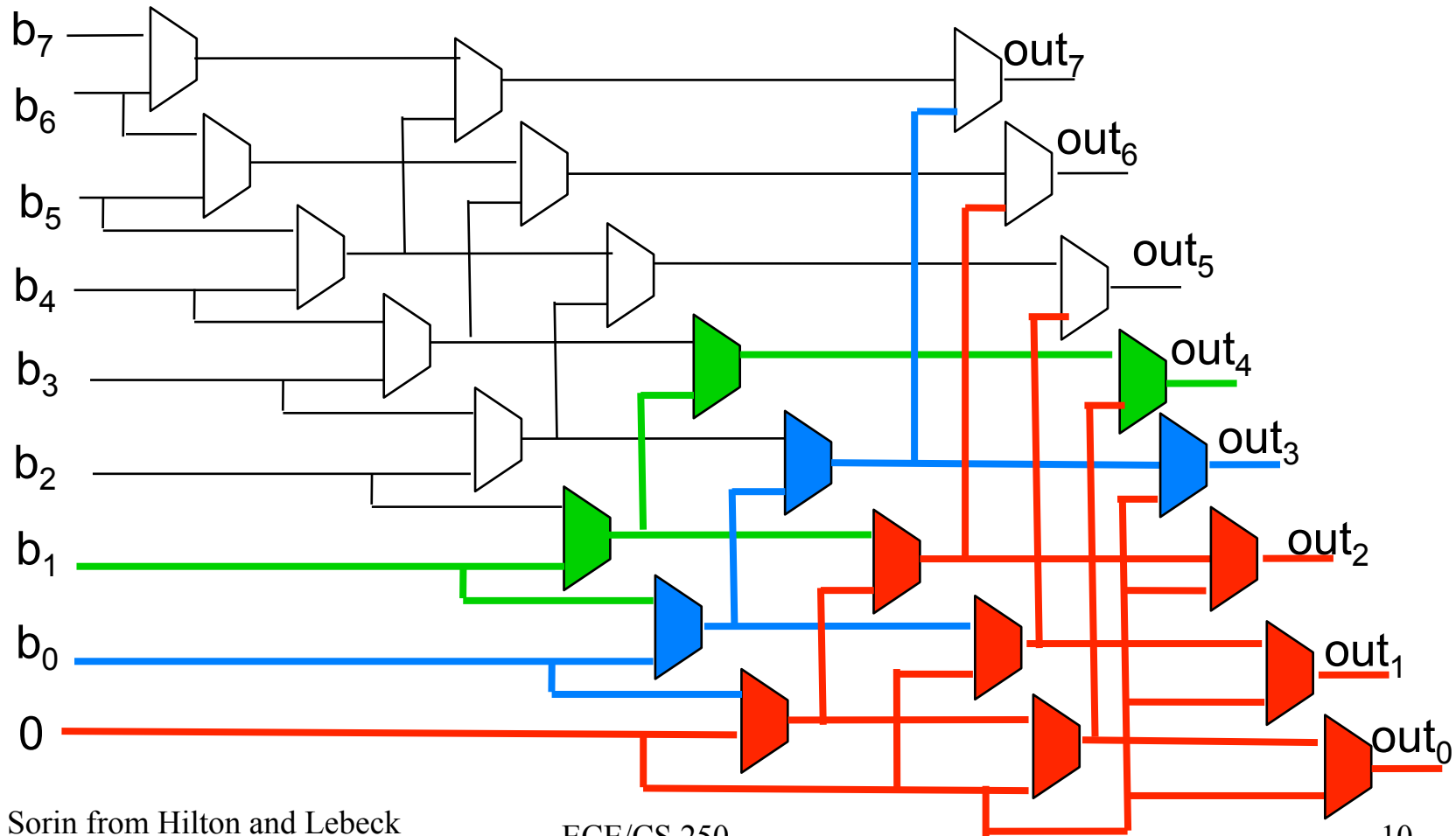- **Shifter in action: shift by 011**
 - Mux control signals from R to L: **S = 0, 1, 1**



So far...


- **We can make logic to compute “math”**
 - **Add, subtract ... and you can do mul/div in 350**
 - Assume for now that mul/div can be built
 - **Bitwise: AND, OR, NOT,...**
 - **Shifts (left or right)**
 - **Selection (MUX)**
 - **...pretty much anything**
- **But processors need state (hold value)**
 - **Registers**
 - **...**

Storage

- All the circuits we looked at so far are **combinational circuits**: the output is a Boolean function of the inputs.
- We need circuits that can remember values (registers, memory)
- The output of the circuit is a function of the input and a function of a stored value (state)
- Circuits with storage are called **sequential circuits**
- Key to storage: feedback loops from outputs to inputs



Ideal Storage – Where We’re Headed

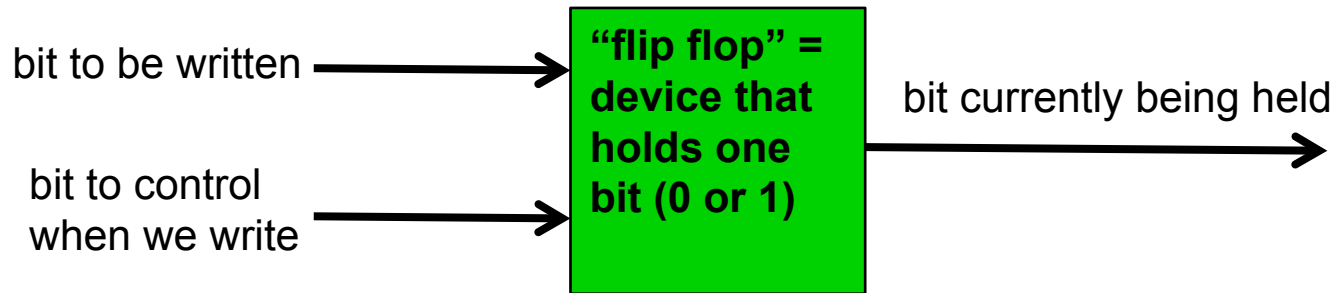- **We want something that can hold 1 bit**
- **We want to control when it is re-written**



- **We’re going to dig a bit into the box**




FF Step #1: Set-Reset (SR) Latch

  




R	S	Q
0	0	Q
0	1	1
1	0	0
1	1	-

Don't set both S & R to 1.
Seriously, don't do it.




Set-Reset Latch (Continued)

   




Set-Reset Latch (Continued)

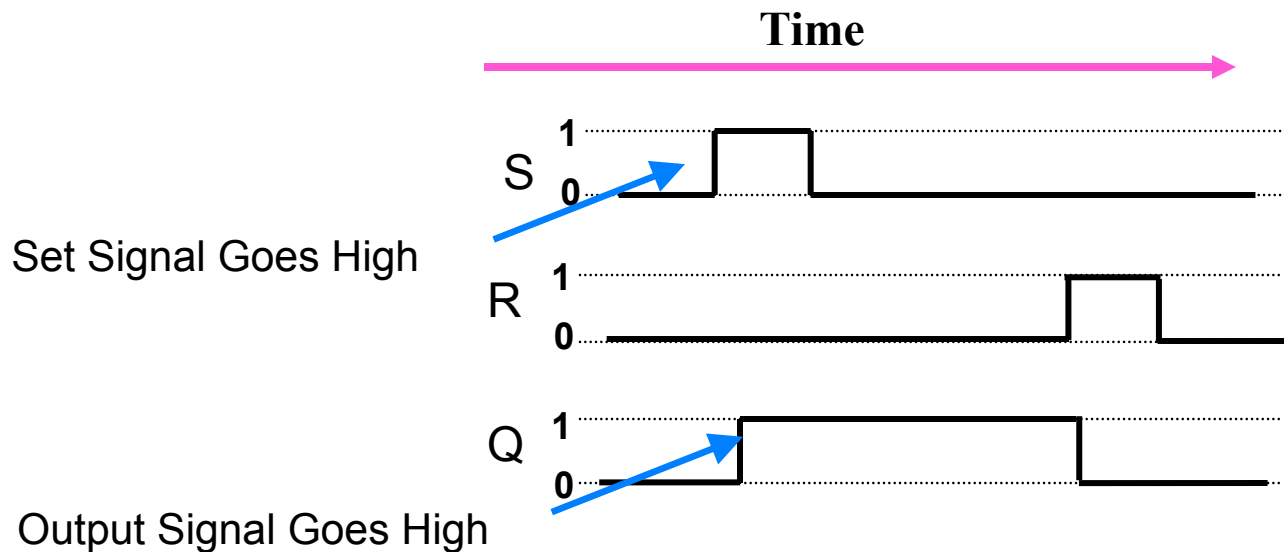  

Set-Reset Latch (Continued)

   


Set-Reset Latch (Continued)

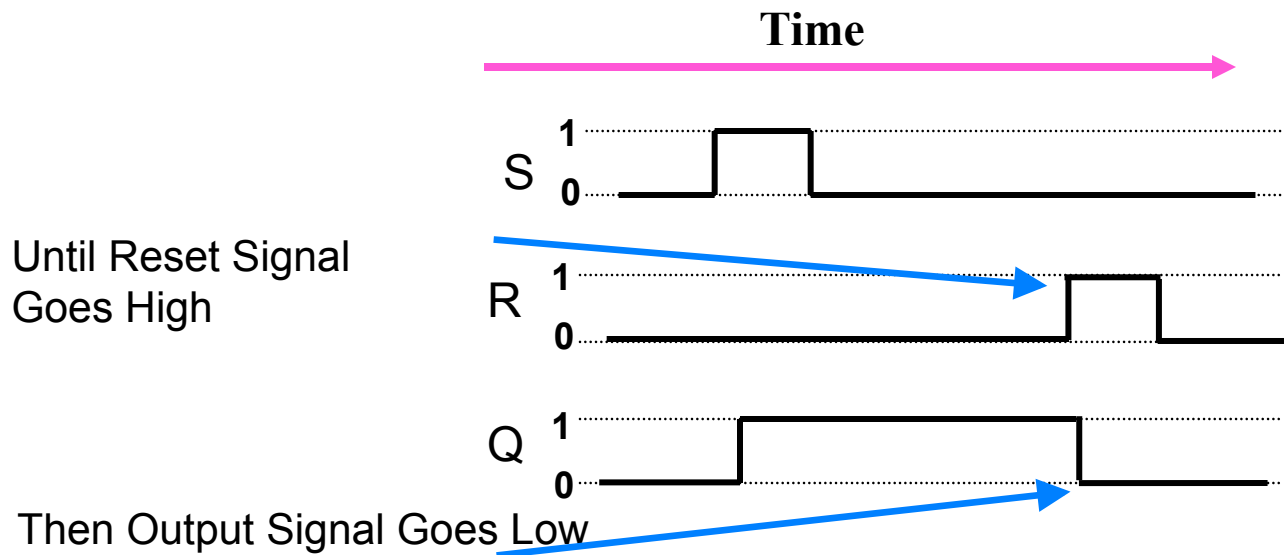  

SR Latch


- **Downside: S and R at once = chaos**
- **Downside: Bad interface**
- **So let's build on it to do better**

FF Step #2: Data Latch (“D Latch”)

 

Starting with SR Latch

Data Latch (D Latch)

 


Starting with SR Latch

Change interface to
Data + Enable (D + E)

If $E=0$, then $R=S=0$.


If $E=1$, then $S=D$ and $R=!D$

Data Latch (D Latch)

 


D	E	Q
0	1	0
1	1	1
-	0	Q


Time

 


Data Latch (D Latch)

 

D	E	Q
0	1	0
1	1	1
-	0	Q

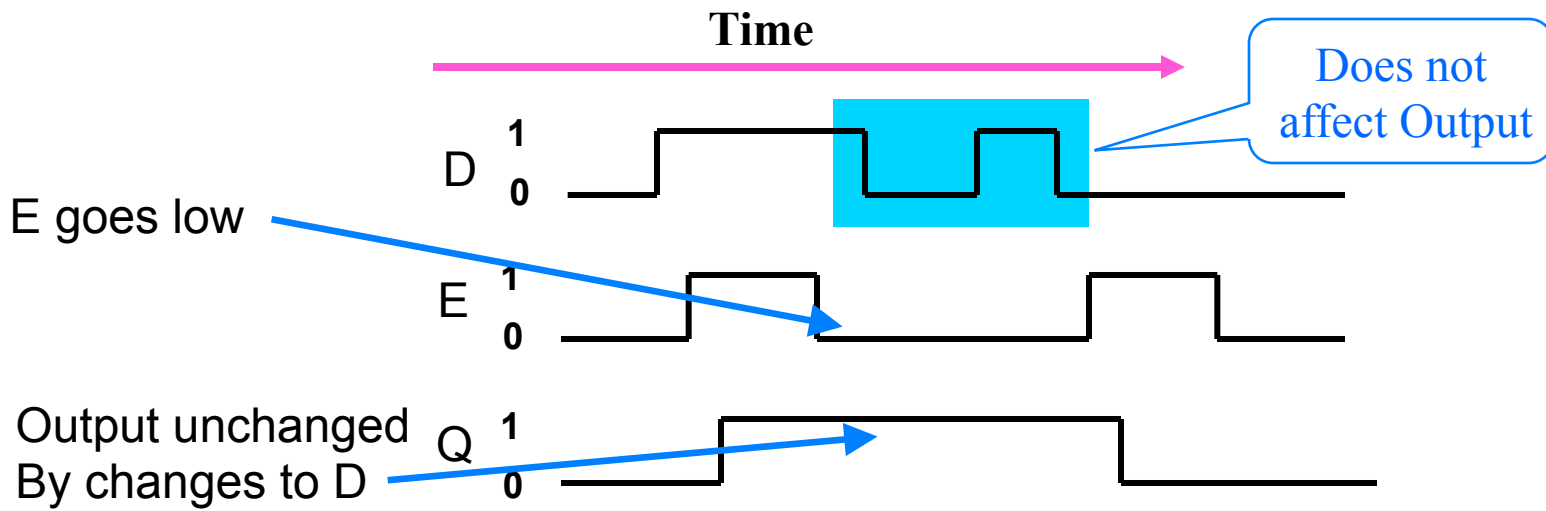


Data Latch (D Latch)

 


D	E	Q
0	1	0
1	1	1
-	0	Q

Time

 


Data Latch (D Latch)

 

D	E	Q
0	1	0
1	1	1
-	0	Q

Time

 


Logic Takes Time

- **Logic takes time:**
 - **Gate delays: delay to switch each gate**
 - **Wire delays: delay for signal to travel down wire**
 - **Other factors (not going into them here)**
- **Need to make sure that signals timing is right**
 - **Don't want to have races or wacky conditions..**

Clocks

 
- **Processors have a clock:**
 - Alternates 0 1 0 1
 - Like the processor's internal metronome
 - Latch → logic → latch in one clock cycle



– **3 GHz processor = 3 Billion clock cycles/sec**


FF Step #3: Using Level-Triggered D Latches

 - **First thoughts: Level Triggered**
 - Latch captures new value when clock is high
 - Latch holds existing value when clock is low




Strawman: Level Triggered

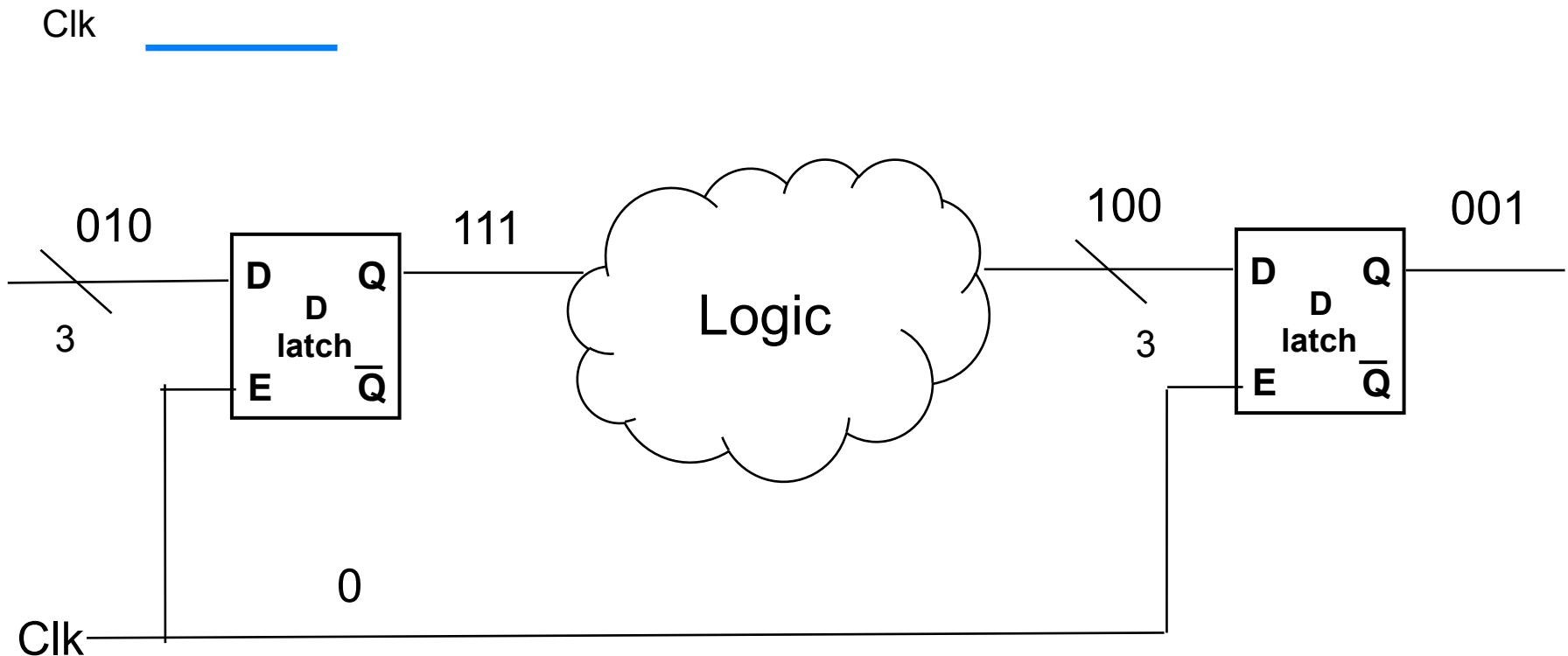- How we'd like this to work
 - Clock is low, all values stable




Strawman: Level Triggered

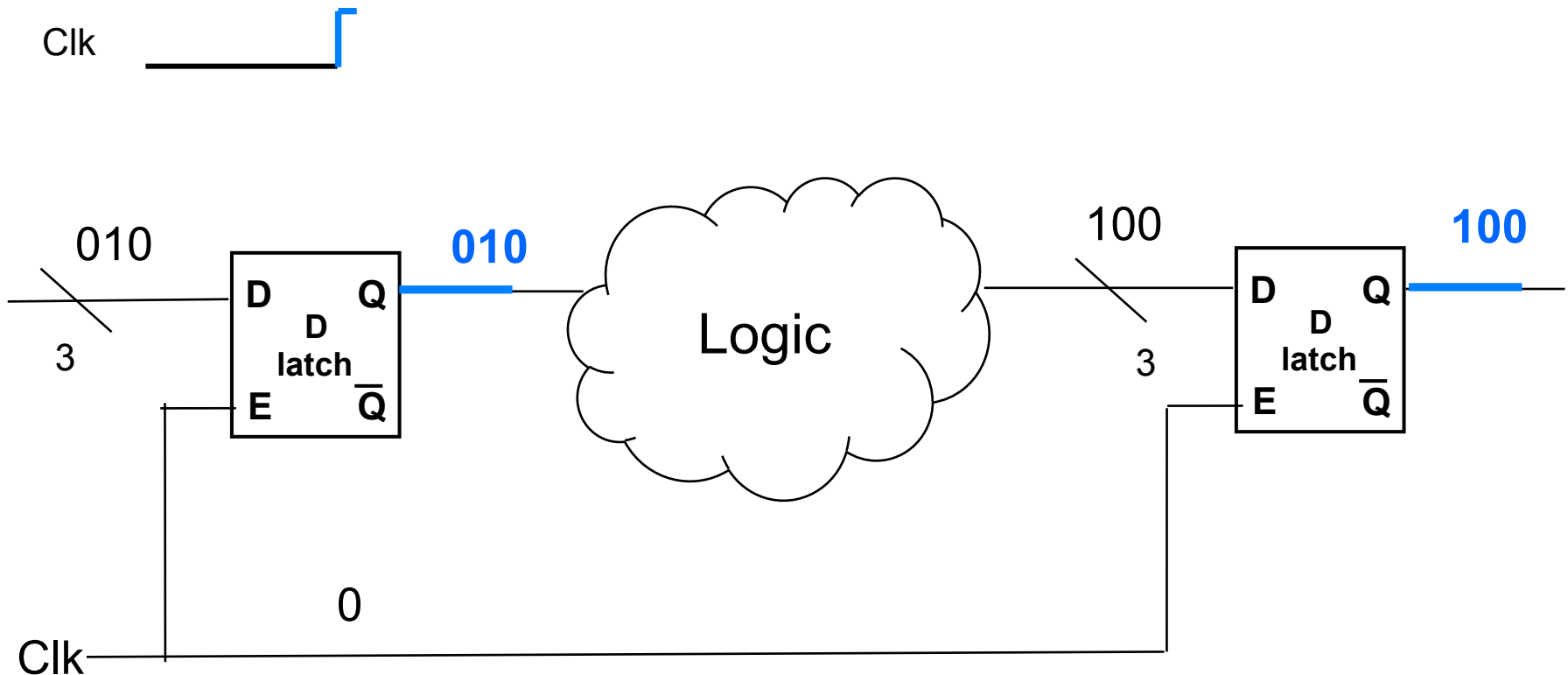- How we'd like this to work
 - Clock goes high, latches capture and xmit new val




Strawman: Level Triggered

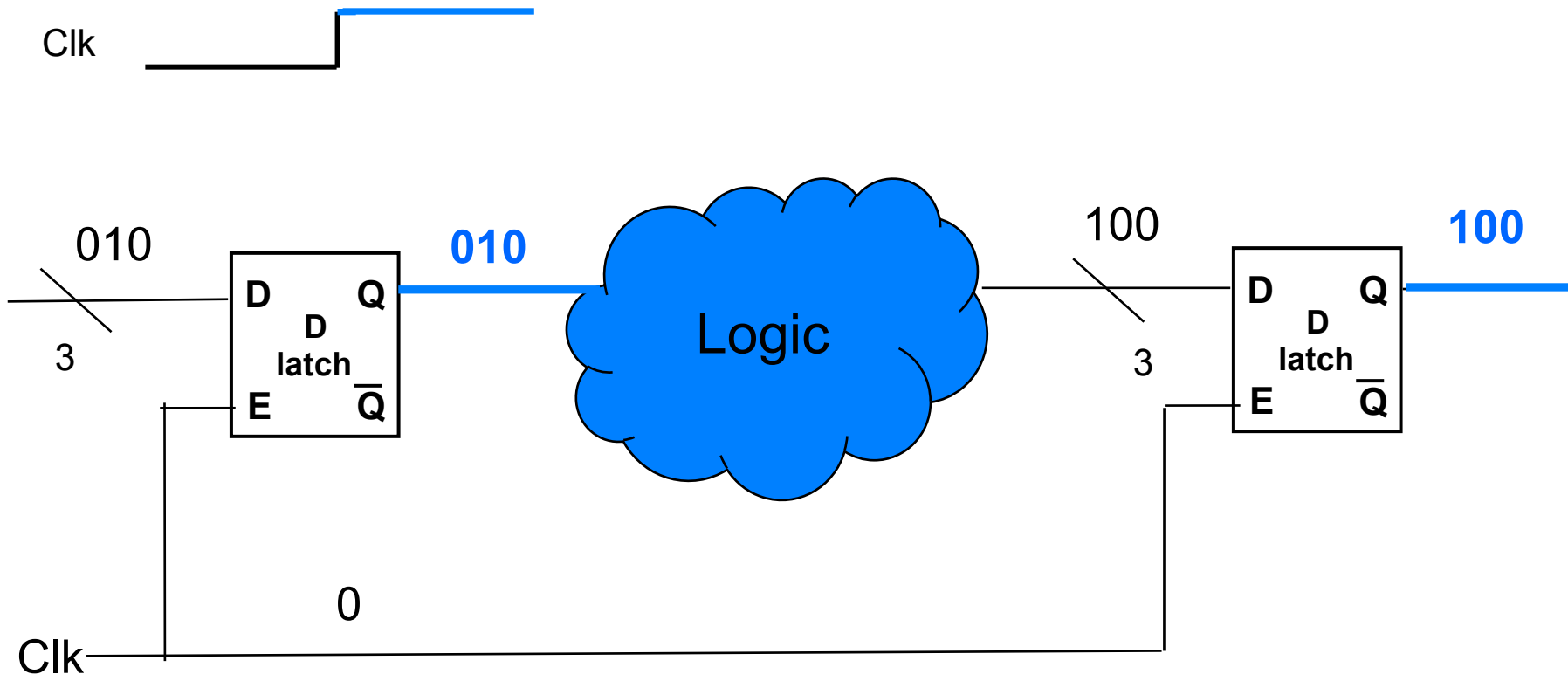- How we'd like this to work
 - Signals work their way through logic w/ high clk




Strawman: Level Triggered

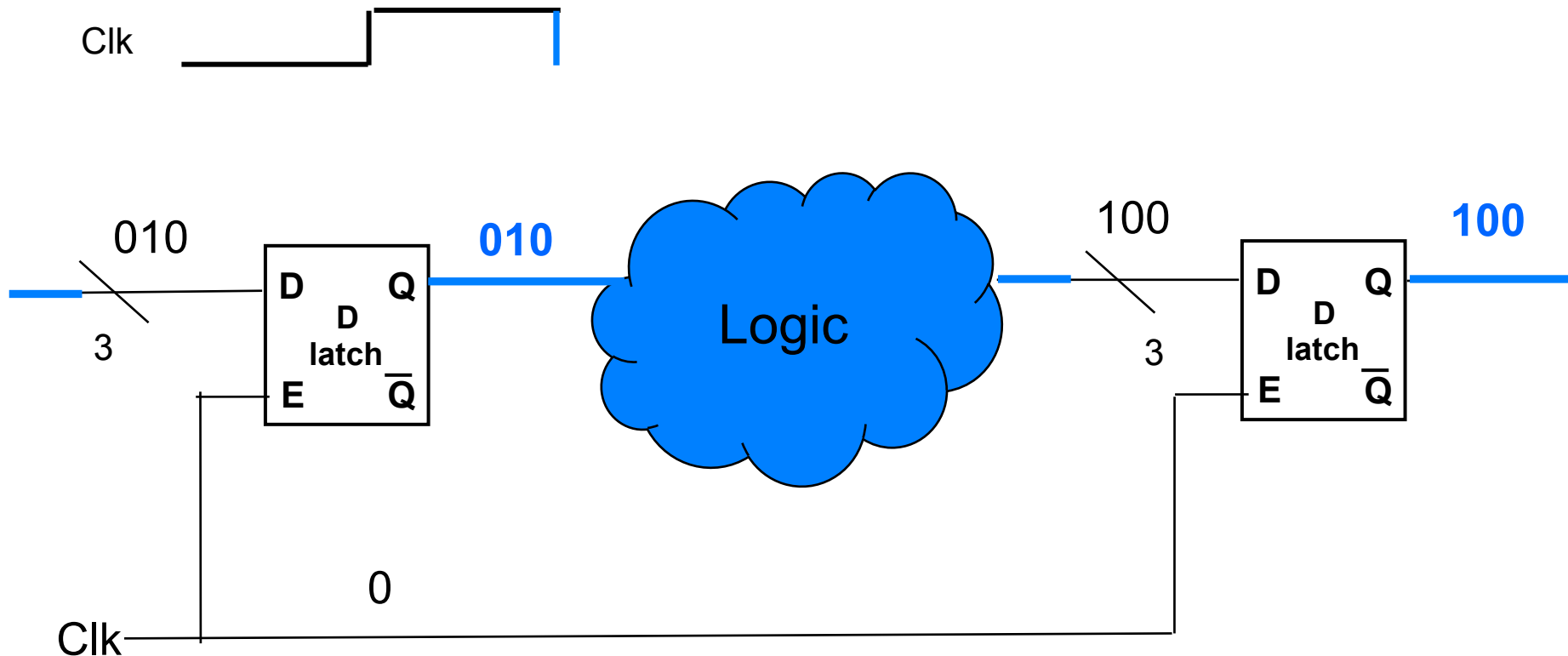- How we'd like this to work
 - Clock goes low before signals reach next latch




Strawman: Level Triggered

 - How we'd like this to work
 - Clock goes low before signals reach next latch




Strawman: Level Triggered

 - How we'd like this to work
 - Everything stable before clk goes high




Strawman: Level Triggered

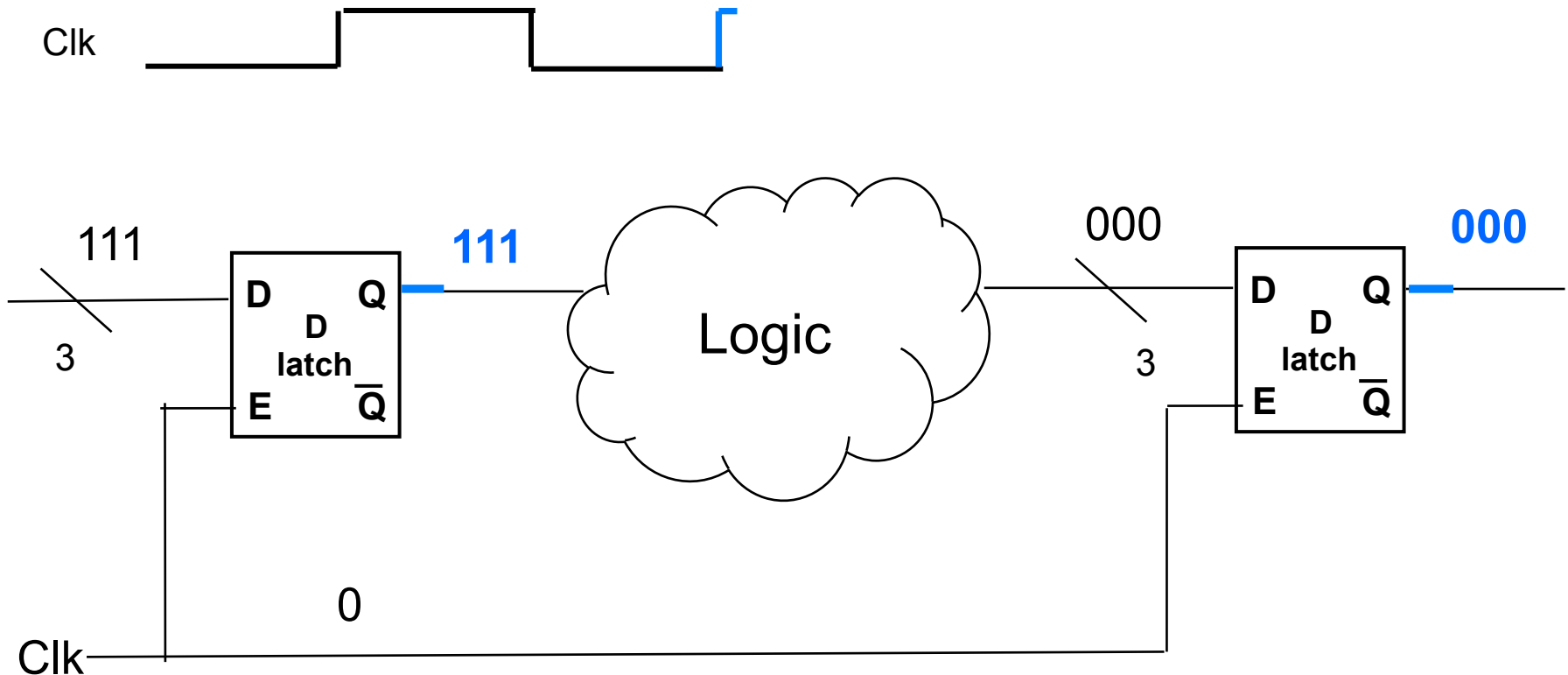- How we'd like this to work
 - Clk goes high again, repeat




Strawman: Level Triggered

 - **Problem: What if signal reaches latch too early?**
–I.e., while clk is still high



Strawman: Level Triggered

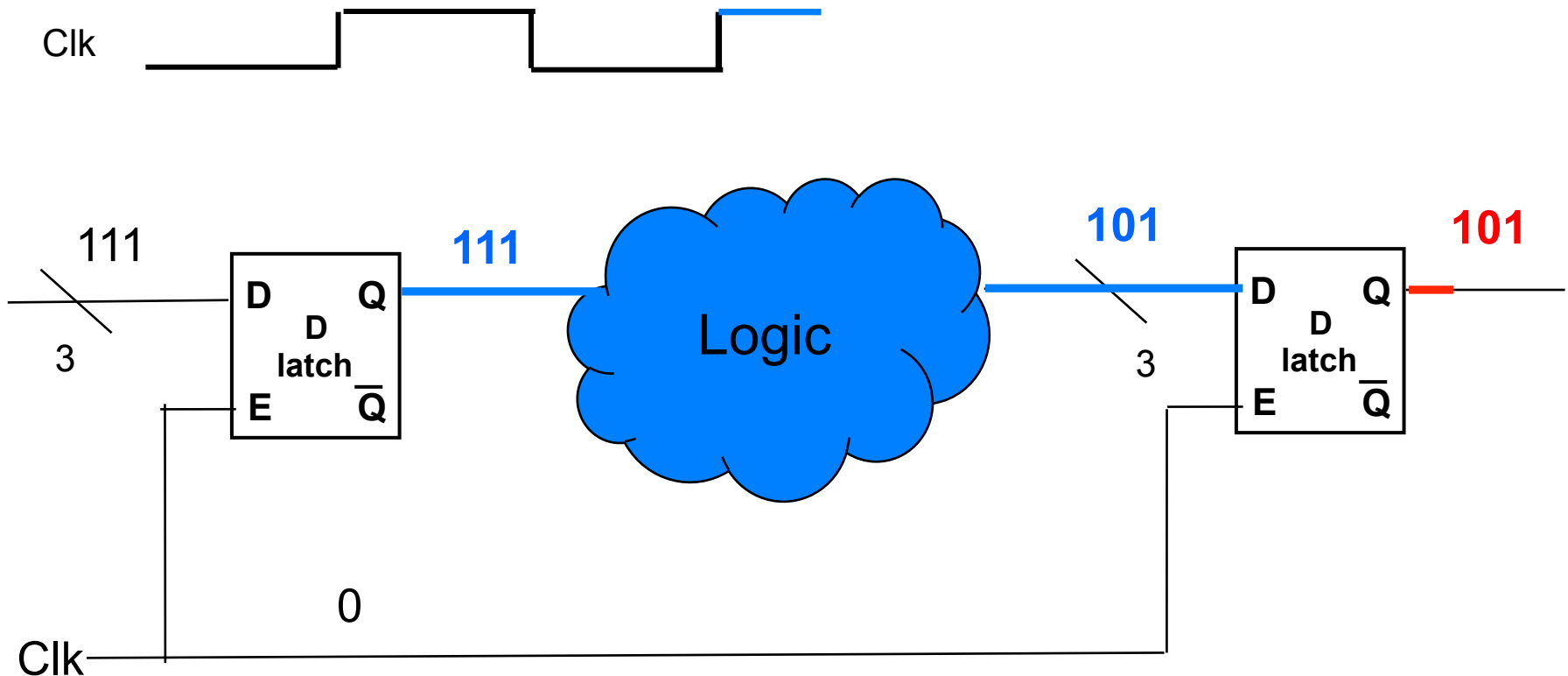- **Problem: What if signal reaches latch too early?**
 - **Signal goes right through latch, into next stage..**




That would be bad...

- **Getting into a stage too early is bad**
 - **Something else is going on there → corrupted**
 - **Also may be a loop with one latch**

FF Step #4: Edge Triggered


- Instead of level triggered
 - Latch a new value at a clock level (high or low)
- We use edge triggered
 - Latch a value at an clock edge (rising or falling)

Rising Edges

 


Falling Edges

Our Ultimate Goal: D Flip-Flop

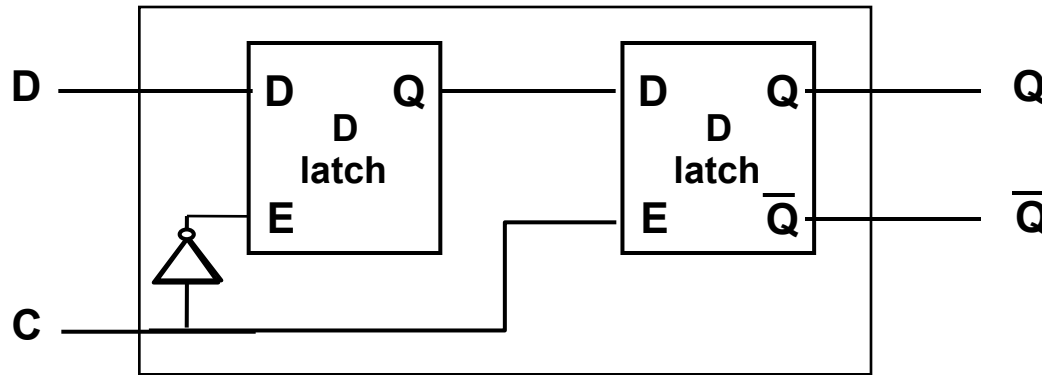


- **Rising edge triggered D Flip-flop**
 - **Two D Latches w/ opposite clking of enables**

D Flip-Flop

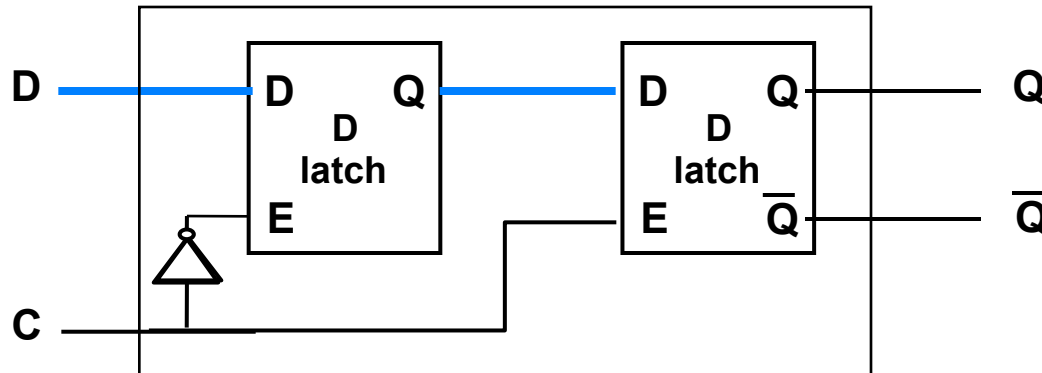


- **Rising edge triggered D Flip-flop**
 - **Two D Latches w/ opposite clking of enables**
 - **On Low Clk, first latch enabled (propagates value)**
 - **Second not enabled, maintains value**

D Flip-Flop

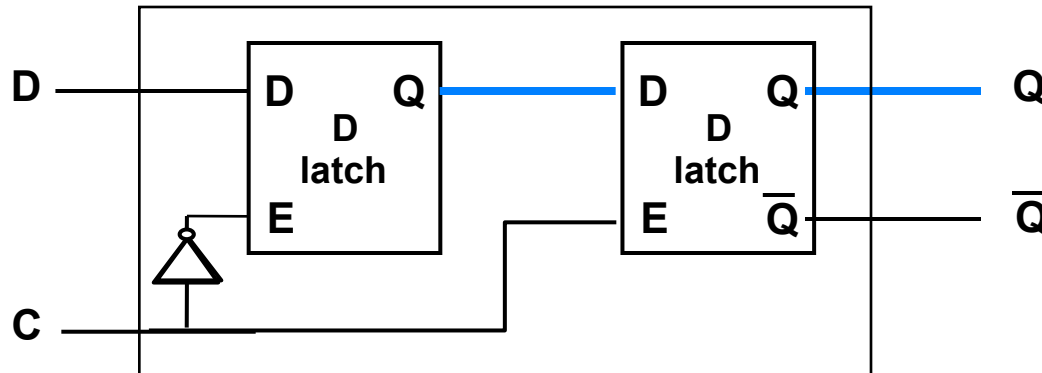

- **Rising edge triggered D Flip-flop**
 - **Two D Latches w/ opposite clking of enables**
 - **On Low Clk, first latch enabled (propagates value)**
 - **Second not enabled, maintains value**
 - **On High Clk, second latch enabled**
 - **First latch not enabled, maintains value**

D Flip-Flop

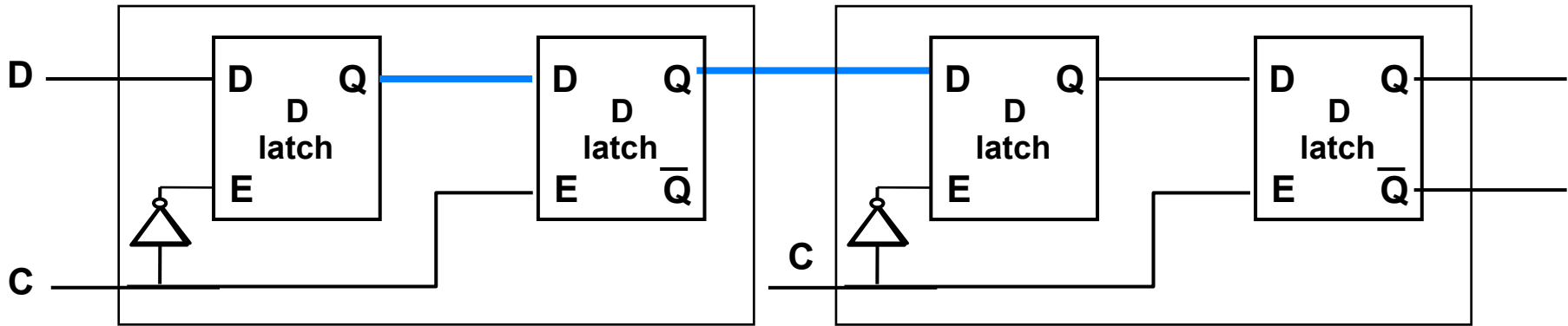

- **No possibility of “races” anymore**
 - Even if I put 2 DFFs back-to-back...
 - By the time signal gets through 2nd latch of 1st DFF 1st latch of 2nd DFF is disabled
- **Still must ensure signals reach DFF before clk rises**
 - Important concern in logic design “**making timing**”


D Flip-Flop

- **Could also trigger on falling edge**
 - **Switch which latch has NOT on clk**



- **D Flip-flop is ubiquitous**
 - **Typically people just say “latch” and mean DFF**
 - **Which edge: doesn't matter**
 - **As long as consistent in entire design**
 - **We'll use rising edge**

D flip flops

 - **Generally don't draw clk input**
 - Have one global clk, assume it goes there
 - Often see \triangleright as symbol meaning clk



  - **Maybe have explicit enable**
 - Might not want to write every cycle
 - If no enable signal shown, implies always enabled




- **Get output and NOT(output) for “free”**

More Storage Than a D-FF: Register File

- A MIPS register can be made with 32 flip flops
- One register can store one 32-bit value
- So do we just replicate this 32 times to get the 32 registers for a MIPS processor?
 - Not exactly
- **Register File** (the physical storage for the regs)
 - MIPS register file has 32 32-bit registers
- How do we build a Register File using D Flip-Flops?
- What other components do we need?


Register File Design

 - Use a mux to pick read ?
 - 32-input mux = slow
 - (other regs not pictured)




Register File Design

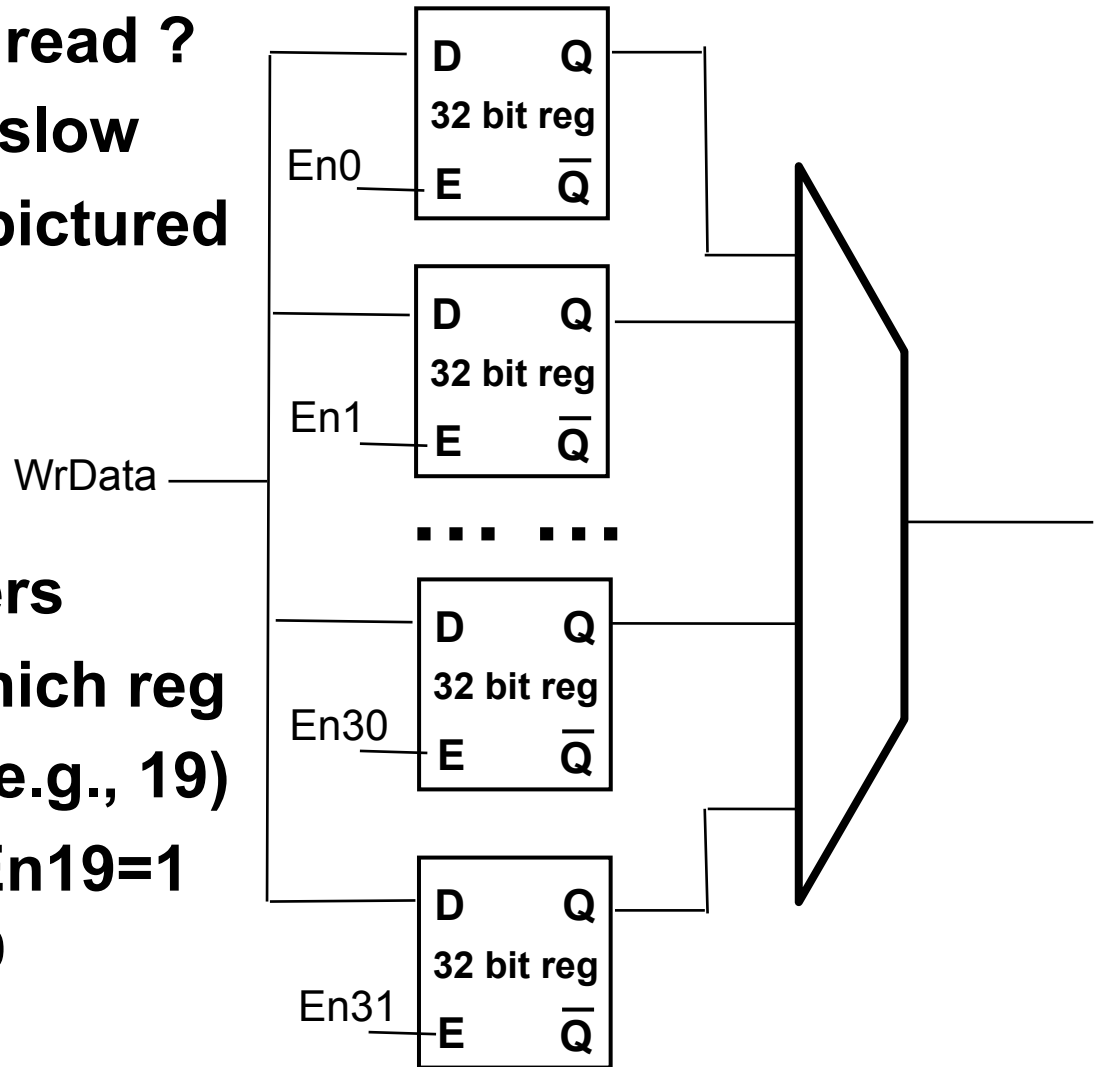- Use a mux to pick read ?
 - 32 input mux = slow
 - other regs not pictured
- Writing the registers
 - Need to pick which reg
 - Have reg num (e.g., 19)
 - Need to make $En_{19}=1$
 - $En_0, En_1, \dots = 0$




First: A Decoder

 - **First task: convert binary number to “one hot”**
 - N bits in
 - 2^N bits out
 - $2^N - 1$ bits are 0, 1 bit (matching the input) is 1



Decoder Logic

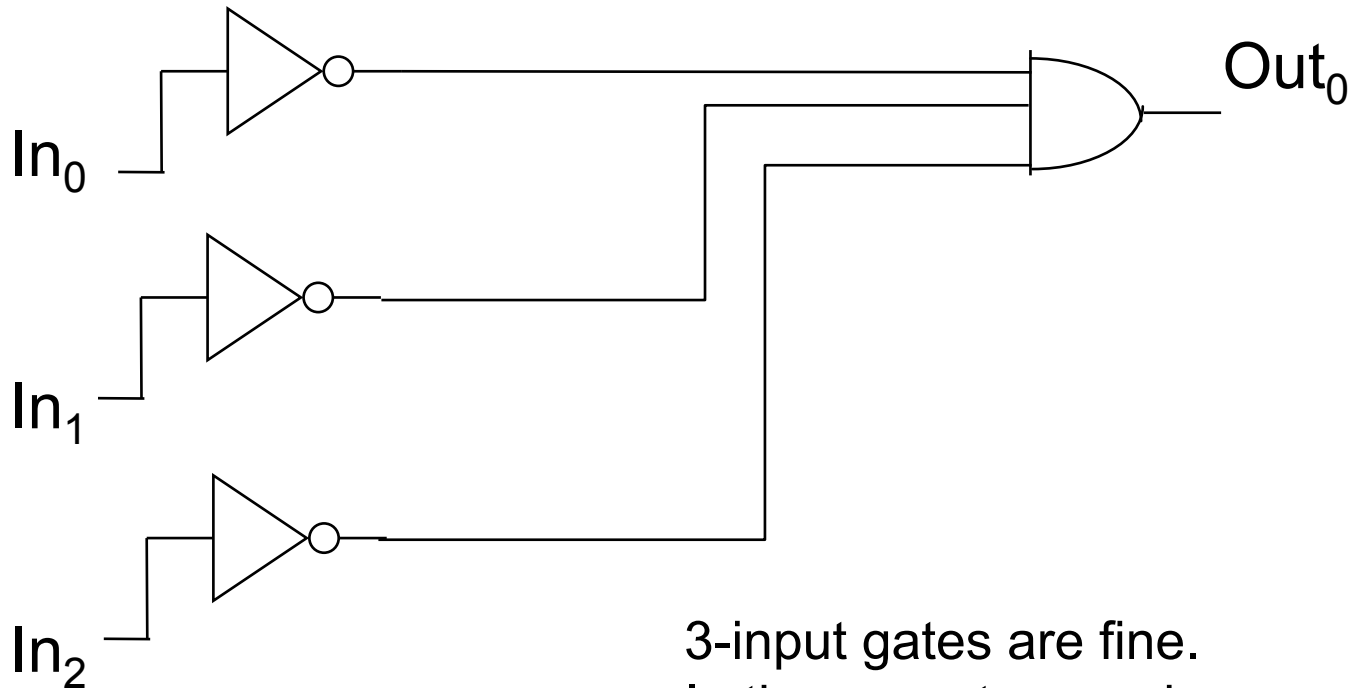- Decoder comprised of AND gates for each output:
 - $\text{Out}_0 = 1$ only if input 000




3-input gates are fine.

In theory, gates can have any # of inputs
In practice >4 converted to multiple gates

Decoder Logic

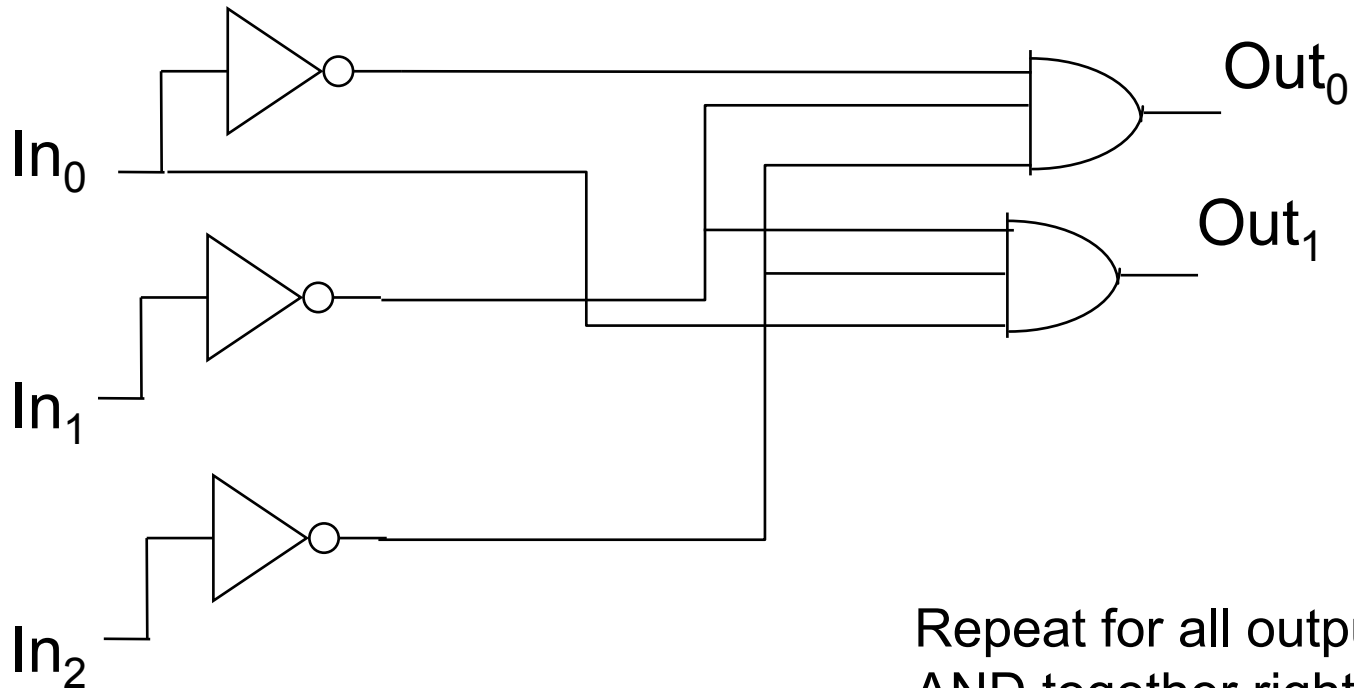- Decoder comprised of AND gates for each output:
 - $\text{Out}_1 = 1$ only if input 001




Repeat for all outputs:
AND together right bits
(gets messy fast on a slide)

Register File

- **Now we know how to write:**
 - **Use decoder to convert reg # to one hot**
 - **Send write data to all regs**
 - **Use one hot encoding of reg # to enable right reg**
- **How do we read?**
 - **32-input mux is not realistic**
 - **To do this: expand our world from {0, 1} to {0, 1, Z}**

Kind of like water in a pipe...

 - To understand Z , let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - This wire is 0 (it has no water)



Kind of like water in a pipe...

- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - This wire is 1 (it is full of water)




Kind of like water in a pipe...

- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose a gate drives a 0 onto this wire
 - Think of it as sucking the water out




Kind of like water in a pipe...

 - To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose a gate drives a 0 onto this wire
 - Think of it as sucking the water out



Kind of like water in a pipe...

 - To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose a gate drives a 0 onto this wire
 - Think of it as sucking the water out




Kind of like water in a pipe...

- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose a gate drives a 0 onto this wire
 - Think of it as sucking the water out



Kind of like water in a pipe...

 - To understand Z , let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose the gate now drives a 1
 - Think of it as pumping water in



Kind of like water in a pipe...

- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose the gate now drives a 1
 - Think of it as pumping water in




Kind of like water in a pipe...

- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose the gate now drives a 1
 - Think of it as pumping water in



Remember this rule?

 
- Remember I told you not to connect two outputs?



- If one gate tries to drive a 1 and the other drives a 0
 - One pumps water in.. The other sucks it out
 - Except it's electric charge, not water
 - “Short circuit” → lots of current → lots of heat

So this third option: Z

 - There is a third possibility: Z (“high impedance”)
 - Neither pushing water in, nor sucking it out
 - Simply prevents water flow with no effect on pipe
 - Prevents electricity from flowing through
- Gate that gives us {0,1,Z} : **Tri-state**




D	E	Q
0	1	0
1	1	1
-	0	Z

We've had this rule one day... and you break it


It's ok to connect multiple outputs together
Under one circumstance:

 All but one must be outputting Z at any time



Mux, implemented with tri-states

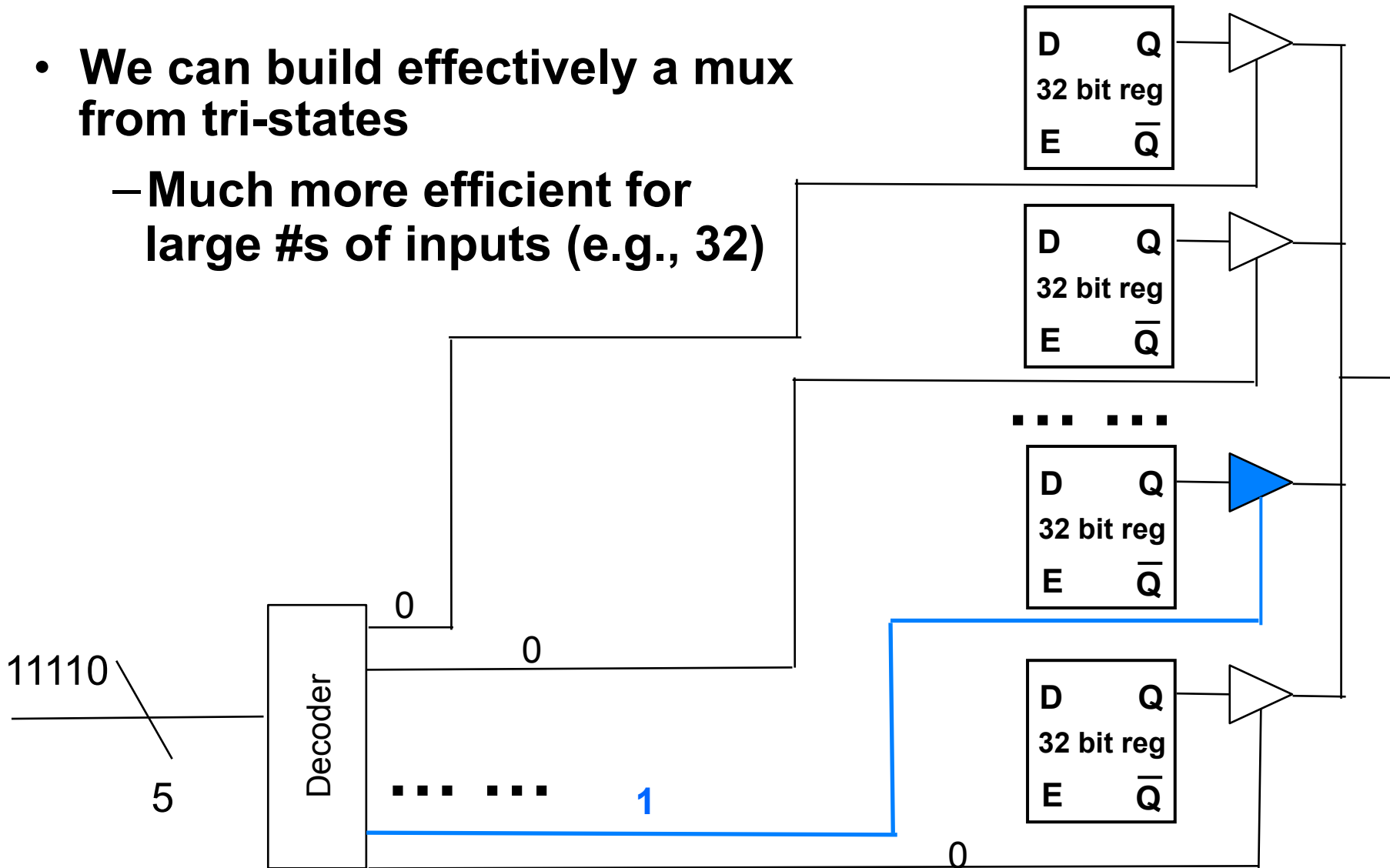- We can build effectively a mux from tri-states
 - Much more efficient for large #s of inputs (e.g., 32)



Ports

- **Read Port(s)**
 - **Ability to do one read per clock cycle**
 - **Adding a read port**
 - **Another decoder**
 - **Another set of tri-states**
 - **Another output bus (wire connecting the tri-states)**
 - **Read 2 source registers per instr?**
 - **Maybe even more if we do many instrs at once**
- **Write Port**
 - **Ability to do one write per cycle**
 - **Adding a write port**
 - **Add muxes to select write values**

Minor Detail

- **FYI: This is not how a register file is implemented**
 - **(Though it is how other things are implemented)**
 - **Actually done with SRAM**
 - **We'll see that later this semester...**

Summary

Can layout logic to compute things

Add, subtract,...

Now can store things

D flip-flops

Registers

Also understand clocks

Just about ready to make a datapath!