

ECE 250 / CPS 250
Computer Architecture

Basics of Logic Design
Finite State Machines

Benjamin Lee


Slides based on those from

Andrew Hilton (Duke), Alvy Lebeck (Duke)
Benjamin Lee (Duke), and Amir Roth (Penn)

Finite State Machine (FSM)


- FSM = States + Transitions
 - Next state = function (current state, inputs)
 - Outputs = function (current state, inputs)
- What you do depends on what state you're in
 - Think of a calculator ... if you type "+3=", the result depends on what you did before, i.e., the state of the calculator
- Canonical Example: Combination Lock
 - Must enter 3 8 4 to unlock

Finite State Machines: Example

 


- Combination Lock Example:
 - Need to enter 3 8 4 to unlock
- Initial State called "start": no valid piece of combo seen
 - All FSMs get reset to their start state

Finite State Machines: Example

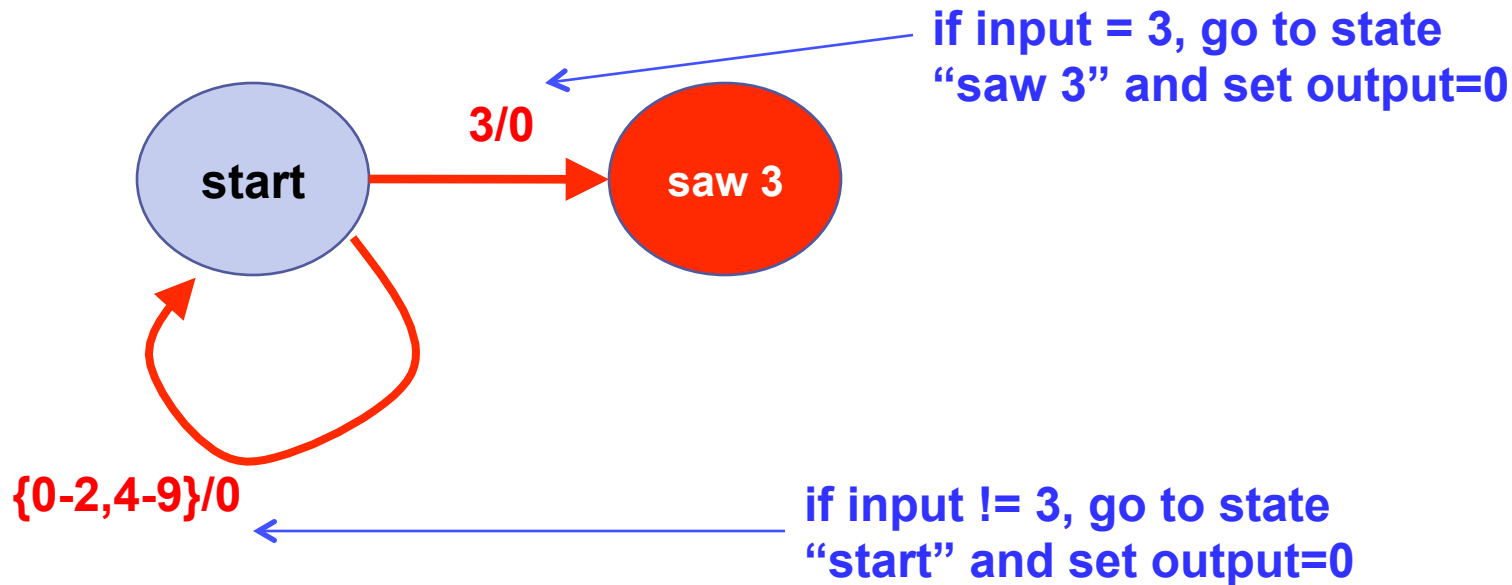


- Combination Lock Example:
 - Need to enter **3 8 4** to unlock
- Input of 3: transition to new state, output=0
- Any other input: stay in same state, output=0

Finite State Machines: Example

 


- Combination Lock Example:
 - Need to enter **3 8 4** to unlock
- If in state "saw 3":
 - Input = 8? Goto state "saw 38" and output=0

Finite State Machines: Example

 


- Combination Lock Example:
 - Need to enter **3 8 4** to unlock
- If in state "saw 38":
 - Input = 4? Goto state "saw 384" and set output=1 → Unlock!

Finite State Machines: Example

 

- Combination Lock Example:
 - Need to enter **3 8 4** to unlock
- If in state "saw 384":
 - Stay in this state forever and output=1

Finite State Machines: Example

 

In this picture, the circles are **states**.

The arcs between the states are **transitions**.

The figure is a **state transition diagram**, and it's the first thing you make when designing a finite state machine (FSM).

Finite State Machines: Caveats


Do NOT assume all FSMs are like this one!

- **A finite state machine (FSM) has at least two states, but can have many, many more. There's nothing sacred about 4 states (as in this example). Design your FSMs to have the appropriate number of states for the problem they're solving.**
 - **Question: how many states would we need to detect sequence 384384?**
- **Most FSMs don't have state from which they can't escape.**

FSM Types: Moore and Mealy


- Recall: FSM = States + Transitions
 - Next state = function (current state, inputs)
 - **Outputs = function (current state, inputs)**
- This is the most general case
 - Called a “Mealy Machine”
 - We will assume Mealy Machines from now on
- A more restrictive FSM type is a “Moore Machine”
 - **Outputs = function (current state)**

State Transition Diagram → Truth Table

 

Current State	Input	Next state	Output
Start	3	Saw 3	0 (closed)
Start	Not 3	Start	0
Saw 3	8	Saw 38	0
Saw 3	3	Saw 3	0
Saw 3	Not 8 or 3	Start	0
Saw 38	4	Saw 384	1 (open)
Saw 38	3	Saw 3	0
Saw 38	Not 4 or 3	Start	0
Saw 384	Any	Saw 3	1

State Transition Diagram → Truth Table

 

Digital logic → must represent everything in binary, including state names. But mapping is arbitrary!

We'll use this mapping:

start = 00

saw 3 = 01

saw 38 = 10

saw 384 = 11

State Transition Diagram → Truth Table

Current State	Input	Next state	Output
00 (start)	3	01	0 (closed)
00	Not 3	00	0
01	8	10	0
01	3	01	0
01	Not 8 or 3	00	0
10	4	11	1 (open)
10	3	01	0
10	Not 4 or 3	00	0
11	Any	11	1

4 states → 2 flip-flops to hold the current state of the FSM

Next state given by inputs to flip-flops are D_1D_0

Current state given by outputs of flip-flops: Q_1Q_0

State Transition Diagram → Truth Table

Q1	Q0	Input	D1	D0	Output
0	0	3	0	1	0 (closed)
0	0	Not 3	0	0	0
0	1	8	1	0	0
0	1	3	0	1	0
0	1	Not 8 or 3	0	0	0
1	0	4	1	1	1 (open)
1	0	3	0	1	0
1	0	Not 4 or 3	0	0	0
1	1	Any	1	1	1

Input can be 0-9 → requires 4 bits
input bits are in3, in2, in1, in0

State Transition Diagram → Truth Table

Q1	Q0	In3	In2	In1	In0	D1	D0	Output
0	0	0	0	1	1	0	1	0
0	0	Not 3				0	0	0
0	1	1	0	0	0	1	0	0
0	1	0	0	1	1	0	1	0
0	1	Not 8 or 3				0	0	0
1	0	0	1	0	0	1	1	1
1	0	0	0	1	1	0	1	0
1	0	Not 4 or 3				0	0	0
1	1	Any				1	1	1

**From here, it's just like combinational logic design!
Write out product-of-sums equations, optimize, and build.**

State Transition Diagram → Truth Table




Q1	Q0	In3	In2	In1	In0	D1	D0	Output
0	0	0	0	1	1	0	1	0
0	0	Not 3				0	0	0
0	1	1	0	0	0	1	0	0
0	1	0	0	1	1	0	1	0
0	1	Not 8 or 3				0	0	0
1	0	0	1	0	0	1	1	1
1	0	0	0	1	1	0	1	0
1	0	Not 4 or 3				0	0	0
1	1	Any				1	1	1

$$\text{Output} = (Q1 \cdot \neg Q0 \cdot \neg \text{In3} \cdot \text{In2} \cdot \neg \text{In1} \cdot \neg \text{In0}) + (Q1 \cdot Q0)$$

$$D1 = (\neg Q1 \cdot Q0 \cdot \text{In3} \cdot \neg \text{In2} \cdot \neg \text{In1} \cdot \neg \text{In0}) + (Q1 \cdot \neg Q0 \cdot \neg \text{In3} \cdot \text{In2} \cdot \neg \text{In1} \cdot \neg \text{In0}) + Q1 \cdot Q0$$


D0 = do the same thing

Truth Table → Sequential Circuit

   


**Start with 2 FFs and 4 input bits. FFs hold current state of FSM.
(not showing clock/enable inputs on flip flops)**

Truth Table → Sequential Circuit

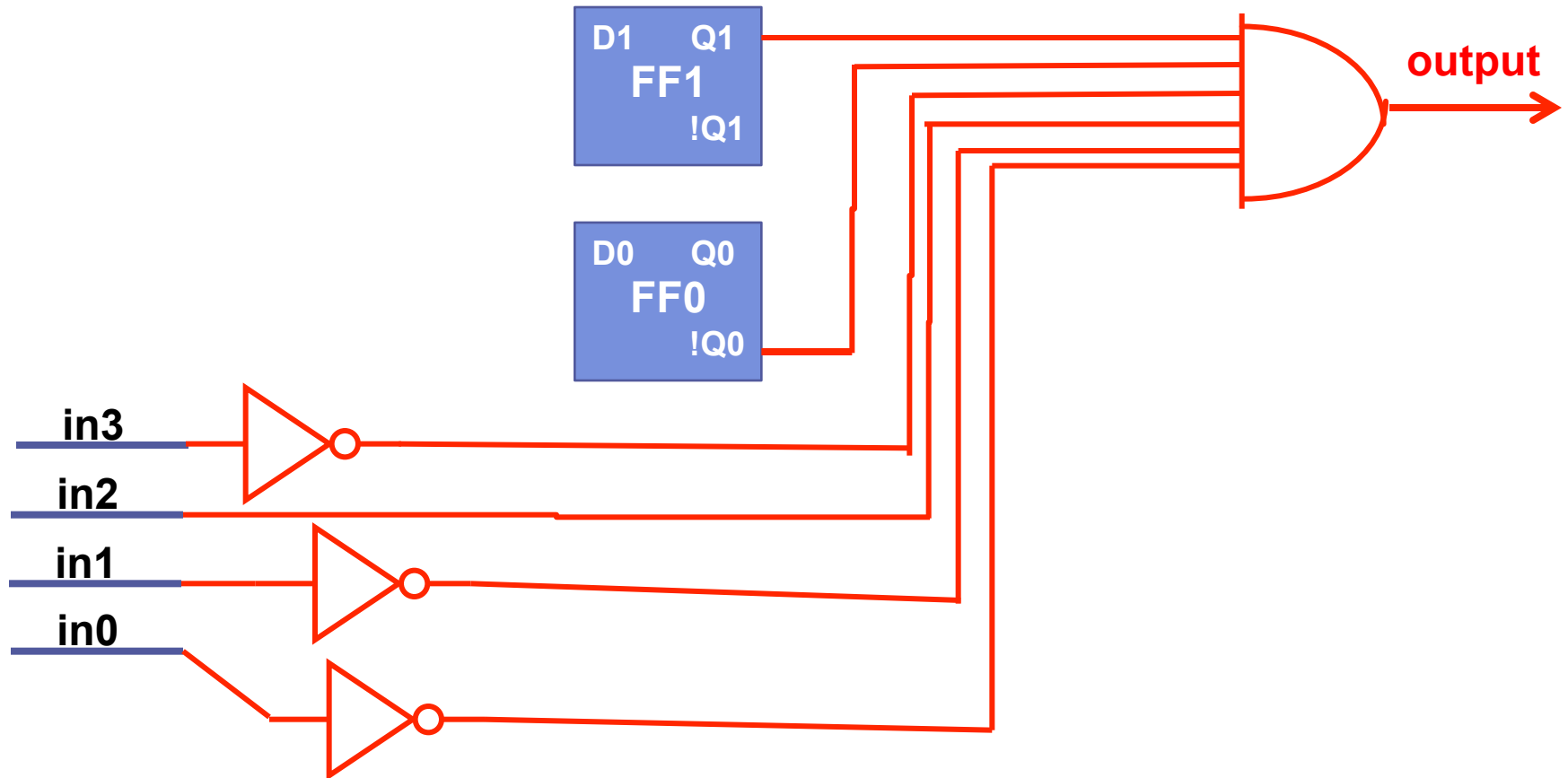


$$\text{output} = (Q1 \cdot !Q0 \cdot !In3 \cdot In2 \cdot !In1 \cdot !In0) + Q1 \cdot Q0$$

Truth Table → Sequential Circuit

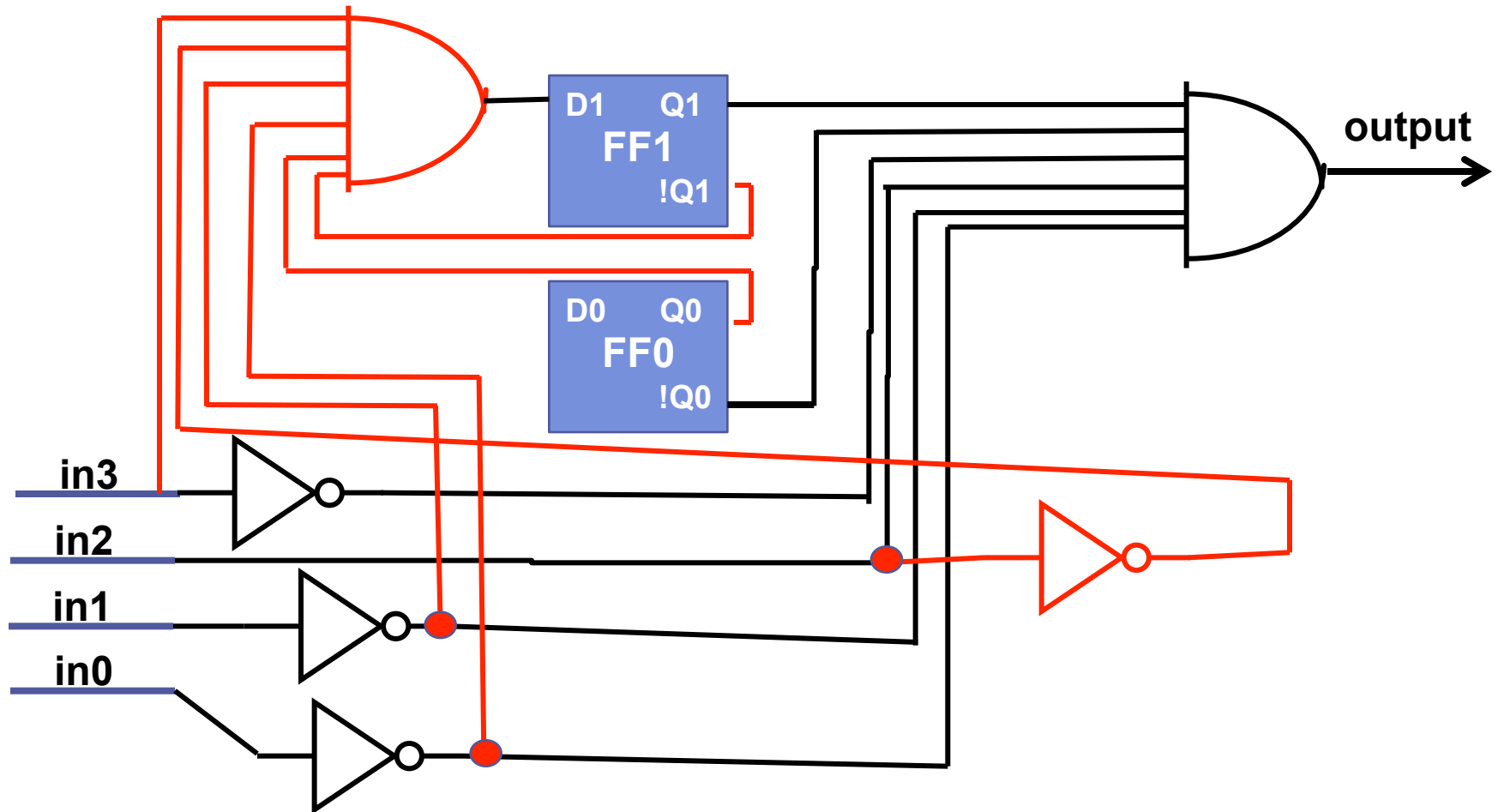

$$D1 = (!Q1 \cdot Q0 \cdot in3 \cdot !in2 \cdot !in1 \cdot !in0) + (Q1 \cdot !Q0 \cdot !in3 \cdot in2 \cdot !in1 \cdot !in0) + Q1 \cdot Q0$$

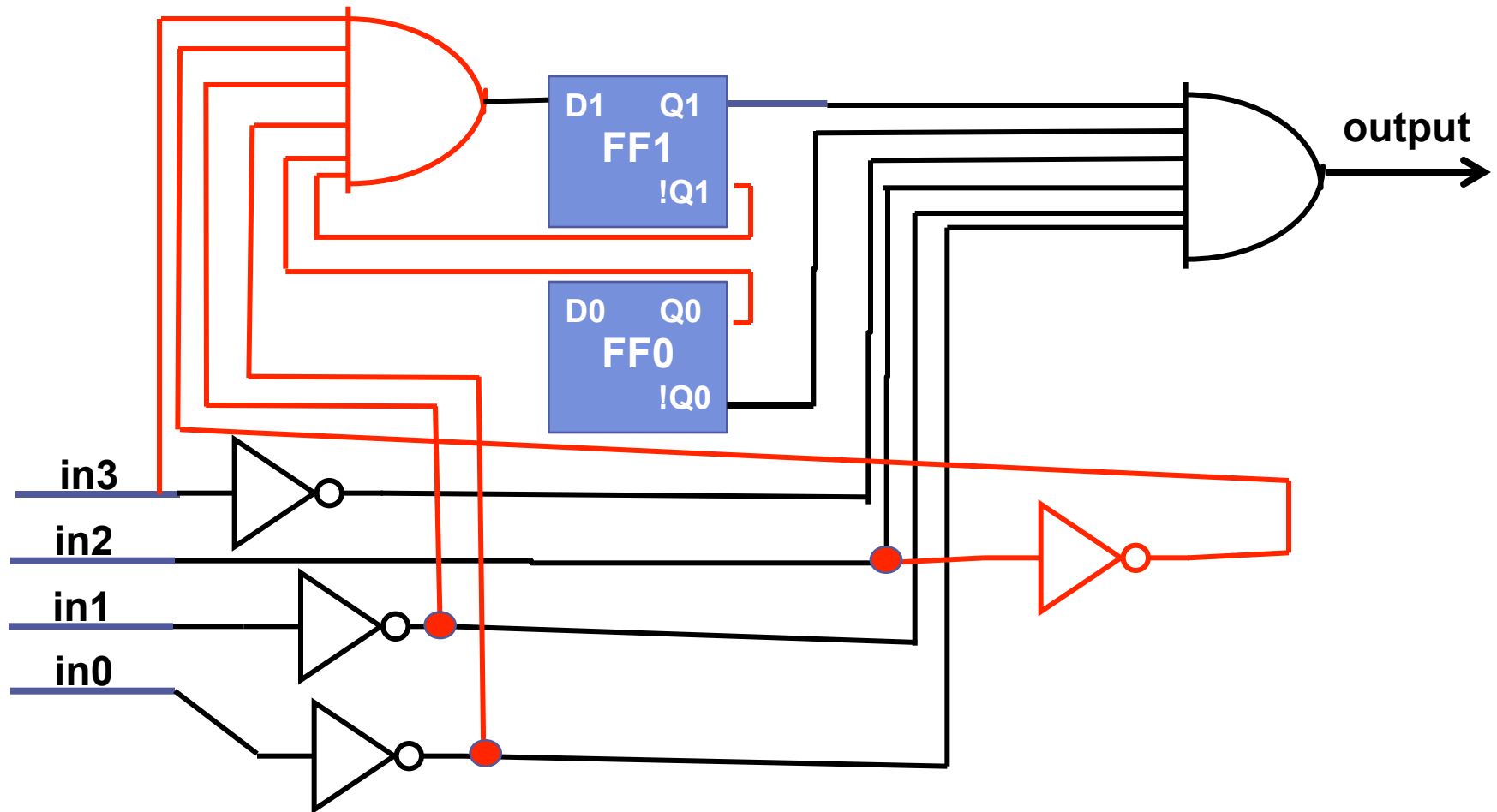Truth Table \rightarrow Sequential Circuit



D0 = ?? Fill this in and do it at home.

FSM Design Principles

- Systematic approach that always works:
 - Start with state transition diagram
 - Make truth table
 - Write out product-of-sums logic equations
 - Optimize logic equations (optional)
 - Implement logic in circuit
- Sometimes can do something non-systematic
 - Requires cleverness, but tough to do in general
- Do not do the following!
 - Use clock as an input (D input of FF)
 - Perform logic on clock signal