ECE/CS 250: Computer Architecture

Basics of Logic Design: Boolean Algebra, Logic Gates

Benjamin Lee

Slides based on those from Alvin Lebeck, Daniel Sorin, Andrew Hilton, Amir Roth, Gershon Kedem

Admin

- Resource: Pragmatic Logic by William Eccles
 - In Sakai Resources and linked off web page.
 - Skim for what you need, way too much in there
- This material is covered in MUCH greater depth in ECE/CS 350 please take ECE/CS 350 if you want to learn enough digital design to build your own processor
- Download Logisim before Friday's recitation
 - http://ozark.hendrix.edu/~burch/logisim/download.html

What We've Done, Where We're Going



(Almost) Bottom UP to CPU

Computer = Machine That Manipulates Bits

- Everything is in binary (bunches of 0s and 1s)

 Instructions, numbers, memory locations, etc.
- Computer is a machine that operates on bits
- Computers physically made of transistors

 Electrically controlled switches
- We can use transistors to build logic
 - E.g., if this bit is a 0 and that bit is a 1, then set some other bit to be a 1
 - E.g., if the first 5 bits of the instruction are 10010 then set this other bit to 1 (to tell the adder to subtract instead of add)

How Many Transistors Are We Talking About?

Pentium III

- Processor Core 9.5 Million Transistors
- Total: 28 Million Transistors

Pentium 4

Total: 42 Million Transistors

Core2 Duo (two processor cores)

- Total: 290 Million Transistors
- Core2 Duo Extreme (4 processor cores, 8MB cache)
- Total: 590 Million Transistors

Core i7 with 6-cores

• Total: 2.27 Billion Transistors

How do they design such a thing? Carefully!

Abstraction!

- Use of abstraction (key to design of any large system)
 - Put a few (2-8) transistors into a logic gate (or, and, xor, ...)
 - Combine gates into logical functions (add, select,....)
 - Combine adders, shifters, etc., together into modules
 Units with well-defined interfaces for large tasks: e.g., decode
 - Combine a dozen of those into a core...
 - Stick 4 cores on a chip...

You are here:

Use of abstraction (key to design of any large system)

- Put a few (2-8) transistors into a logic gate

- Combine gates into logical functions (add, select,....)

- Combine adders, muxes, etc together into modules Units with well-defined interfaces for large tasks: e.g., decode
- Combine a dozen of those into a core...
- Stick 4 cores on a chip...

Boolean Algebra

- First step to logic: Boolean Algebra
 - Formal apporoach for manipulating of True / False (1/0)
 - After all: everything is just 1s and 0s
- Boolean Functions:
 - Given inputs (variables): A, B, C, P, Q...
 - Compute outputs using logic operators, such as:
- NOT: !A (= ~A = Ā = A')
- **AND:** A&B (= A·B = A*B = AB = A∧B) = A&&B in C/Java
- **OR:** $A | B (= A+B = A \lor B) = A || B in C/Java$
- **XOR:** A ^ B (= A ⊕ B)
- NAND, NOR, XNOR, Etc.

• Can represent as Truth Table: shows outputs for all inputs

a	NOT(a)
0	1
1	0

• Can represent as truth table: shows outputs for all inputs

a	NOT(a)
0	1
1	0

a	b	AND(a,b)
0	0	0
0	1	0
1	0	0
1	1	1

• Can represent as truth table: shows outputs for all inputs

a	NOT (a)
0	1
1	0

a	b	AND(a,b)
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR(a,b)
0	0	0
0	1	1
1	0	1
1	1	1

• Can represent as truth table: shows outputs for all inputs

[a	NOT(a)		a	b	AND	(a,b)		a	b	0	R(a	,b)	
ſ	0	1		0	0	(0		0	0		0		
	1	0		0	1	0			0	1		1		
			:	1	0		C		1	0		1		
				1	1		1		1	1		1		
а	ı b	XOR (a	,b)		a	b	XNOR	.(a,	b)		a	b	NOR	(a,b)
0	0	0			0	0	1				0	0		1
0) 1	1			0	1	0				0	1		0
1	. 0				1	0	0				1	0		0
1	. 1	0			1	1	1				1	1		0

Boolean Gates (More Later)

 Gates are electronic devices that implement simple Boolean functions (building blocks of hardware)
 <u>Examples</u>



© Alvin R. Lebeck from Hilton and Sorin

CS/ECE 250

Any Inputs, Any Outputs

- Can have any # of inputs, any # of outputs
- Can have arbitrary functions:

a	b	С	$\mathbf{f}_1\mathbf{f}_2$
0	0	0	01
0	0	1	1 1
0	1	0	1 0
0	1	1	0 0
1	0	0	1 0
1	1	0	01
1	1	1	1 1

• Example: (A & B) | !C

Start with Empty TT

Column Per Input Column Per Output



• Example: (A & B) | !C

Start with Empty TT

Column Per Input Column Per Output

Fill in Inputs Counting in Binary

Α	В	С	Output
0	0	0	

• Example: (A & B) | !C

Start with Empty TT

Column Per Input Column Per Output

Fill in Inputs Counting in Binary



• Example: (A & B) | !C

Start with Empty TT

Column Per Input Column Per Output

Fill in Inputs

Row per set of input values Counting in Binary

Α	В	С	Output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 Example: (A & B) | !C

Start with Empty TT

Column Per Input Column Per Output

Fill in Inputs

Row per set of input values Counting in Binary

Compute Output for reach row (0 & 0) | !0 = 0 | 1 = 1

Α	В	С	Output
0	0	0	1
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 Example: (A & B) | !C

Start with Empty TT

Column Per Input Column Per Output

Fill in Inputs

Row per set of input values Counting in Binary

Compute Output for each row (0 & 0) | !1 = 0 | 0 = 0

Α	В	С	Output
0	0	0	1
0	0	1	0
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 Example: (A & B) | !C

Start with Empty TT

Column Per Input Column Per Output

Fill in Inputs

Row per set of input values Counting in Binary

Compute Output for each row (0 & 1) | !0 = 0 | 1 = 1

Α	В	С	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

• Example: (A & B) | !C

Start with Empty TT

Column Per Input Column Per Output

Fill in Inputs

Row per set of input values Counting in Binary

Compute Output for each row

Α	В	С	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



 Try one yourself: (!A | B) & !C

You try one...

 Try one yourself: (!A | B) & !C

Answer:

Α	В	С	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

© Alvin R. Lebeck from Hilton and Sorin

CS/ECE 250

• Given a Truth Table, find the formula?

Hmmm..

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

• Given a Truth Table, find the formula?

Hmmm ... Could write down every "true" case Then OR together:

```
(!A & !B & !C) |
(!A & !B & C) |
(!A & B & !C) |
(A & B & !C) |
(A & B & C)
```

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

• Given a Truth Table, find the formula?

Hmmm.. Could write down every "true" case Then OR together:

```
(!A & !B & !C) |
(!A & !B & C) |
(!A & B & !C) |
(A & B & !C) |
(A & B & & C)
```

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

• Given a Truth Table, find the formula?

Hmmm.. Could write down every "true" case Then OR together:

```
(!A & !B & !C) |
(!A & !B & C) |
(!A & B & !C) |
(A & B & !C) |
(A & B & & !C) |
```

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Works every time
- Result is right...
- But really ugly

```
(!A & !B & !C) |
(!A & !B & C) |
(!A & B & !C) |
(A & B & !C) |
(A & B & C)
```

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- -Works every time
- Result is right...
- But really ugly

```
(!A & !B & !C) |
(!A & !B & C) |
(!A & B & !C) |
(A & B & !C) |
(A & B & C)
Could just be (A & B) here ?
```

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- -Works every time
- Result is right...
- But really ugly

```
(!A & !B & !C) |
(!A & !B & C) |
(!A & B & !C) |
(A&B)
```

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

This approach: "sum of products"

- Works every time
- Result is right...
- But really ugly

```
(!A & !B & !C) |
(!A & !B & C) |
(!A & B & !C) |
(A&B)
```

Could just be (!A & !B) here

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- -Works every time
- Result is right...
- But really ugly

```
(!A & !B) |
(!A & B & !C) |
(A&B)
```

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

This approach: "sum of products"

- -Works every time
- Result is right...
- But really ugly
- (!A & !B) | (!A & B & !C) | (A&B)

Looks nicer... Can we do better?

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

This approach: "sum of products"

- -Works every time
- Result is right...
- But really ugly
- (!A & !B) | (!A & B & !C) | (A&B)

This has a lot in common: !A & (something)

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

This approach: "sum of products"

- -Works every time
- Result is right...
- But really ugly

(!A & ! (B & C)) |

(A & B)

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Just did some of these by intuition.. but

- Somewhat intuitive approach to simplifying
- This is math, so there are formal rules
 - Just like "regular" algebra

Boolean Function Simplification

- Boolean expressions can be simplified by using the following rules (bitwise logical):
 - -A & A = A A | A = A

 -A & 0 = 0 A | 0 = A

 -A & 1 = A A | 1 = 1

 -A & !A = 0 A | !A = 1

$$-!!A = A$$

- & and | are both commutative and associative
- & and | can be distributed: A & (B | C) = (A & B) | (A & C)
- & and | can be subsumed: A | (A & B) = A

DeMorgan's Laws

Two (less obvious) Laws of Boolean Algebra:
 – Let's push negations inside, flipping & and |

! (A & B) = (!A) | (!B)

! (A | B) = (!A) & (!B)

– You should try this at home – build truth tables for both the left and right sides and see that they're the same

• One more simplification on early example:

```
(!A & ! (B & C)) |
(A & B)
=
(!A & (!B | !C)) |
(A & B)
```

Α	В	С	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Another Simplification Example

! (!A | ! (A & (B | C)))

! (!A | !(A & (B | C))) DeMorgan's !!A & !! (A & (B | C))

```
! (!A | ! (A & (B | C)))
                    DeMorgan's
!!A & !! (A & (B | C))
            Double Negation Elimination
A & (A & (B | C))
                 Associativity of &
(A & A) & (B | C)
                     A = A & A = A
A & (B | C)
```

Come up with a formula for this Truth Table Simplify as much as possible

Α	В	С	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

© Alvin R. Lebeck from Hilton and Sorin

CS/ECE 250

Come up with a formula for this Truth Table Simplify as much as possible

Sum of Products:

(A & B & C)

Α	В	С	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Simplify first two terms:
 (!A & !B & !C) | (!A & B & !C)

Simplify: (!A & !B & !C) | (!A & B & !C) Regroup (associative/commutative): ((!A & !C) & !B) | ((!A & !C) & B)

Simplify: (!A & !B & !C) | (!A & B & !C) Regroup (associative/commutative): ((!A & !C) & !B) | ((!A & !C) & B) Un-distribute (pull out common factor): (!A & !C) & (!B | B)

```
Simplify:
   (!A & !B & !C) | (!A & B & !C)
Regroup (associative/commutative):
   ((!A & !C) & !B) | ((!A & !C) & B)
Un-distribute:
   (!A & !C) & (!B | B)
OR identities:
   (!A & !C) & true = (!A & !C)
```

Come up with a formula for this Truth Table Simplify as much as possible

Sum of Products:

- (!A & !C) |
- (A & !B & C) |
- (A & B & C)

Α	В	С	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Come up with a formula for this Truth Table Simplify as much as possible

Sum of Products:

- (!A & !C)|
- (A & C)

Α	В	С	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Applying the Theory

- Lots of good theory
- Can reason about complex Boolean expressions
 - Can design software to minimize
- But why is this useful?

Boolean Gates

 Gates are electronic devices that implement simple Boolean functions (building blocks of hardware)
 <u>Examples</u>



© Alvin R. Lebeck from Hilton and Sorin

CS/ECE 250

Guide to Remembering your Gates

- This one looks like it just points its input where to go
 - It just produces its input as its output
 - Called a buffer



Guide to Remembering your Gates

- This one looks like it just points its input where to go
 - It just produces its input as its output
 - Called a buffer



A circle always means negate



Brief Interlude: Building An Inverter



Guide to Remembering Your Gates

• AND Gates have a straight edge, like an A (in AND)



OR Gates have a curved edge, like an O (in OR)



Guide to Remembering Your Gates

If we stick a circle on them...



We get NAND (NOT-AND) and NOR (NOT-OR)
 – NAND(a,b) = NOT(AND(a,b))

Guide to Remembering Your Gates

- XOR looks like OR (curved line)
 - But has two lines (like an X does)

$$\begin{array}{c} \mathbf{a} \\ \mathbf{b} \\ \mathbf{b} \\ \mathbf{b} \\ \mathbf{b} \\ \mathbf{b} \\ \mathbf{b} \\ \mathbf{c} \\ \mathbf{$$

- Can put a dot for XNOR
 - XNOR is 1-bit "equals" by the way



Boolean Functions, Gates and Circuits

• Circuits are made from a network of gates.

```
(!A & !C) | (A & C)
```



© Alvin R. Lebeck from Hilton and Sorin

CS/ECE 250

A few more words about gates

Gates have inputs and outputs

If you try to hook up two outputs, bad things happen
 (your processor catches fire)



 If you don't hook up an input, it behaves kind of randomly (also not good, but not set-your-chip-on-fire bad)

- Pick between 2 inputs (called 2-to-1 MUX)
 - Short for multiplexor
- What might we do first?

- Pick between 2 inputs (called 2-to-1 MUX)
 - Short for multiplexor
- What might we do first?
 - Make a truth table?
 - S is selector:
 - S=0, pick A
 - S=1, pick B

Α	В	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Pick between 2 inputs (called 2-to-1 MUX)
 - Short for multiplexor
- What might we do first?
 - Make a truth table?
 - S is selector:
 - S=0, pick A
 - S=1, pick B
- Next: sum-of-products

(!A & B & S) | (A & !B & !S) | (A & B & !S) | (A & B & S)

Α	В	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Pick between 2 inputs (called 2-to-1 MUX)
 - Short for multiplexor
- What might we do first?
 - Make a truth table?
 - S is selector:
 - S=0, pick A
 - S=1, pick B
- Next: sum-of-products
- Simplify
 - (A & !S) |
 - (B & S)

Α	В	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Circuit Example: 2x1 MUX

Draw it in gates:



MUX(A, B, S) = (A & !S) | (B & S)

So common, we give it its own symbol:



© Alvin R. Lebeck from Hilton and Sorin

CS/ECE 250

Example 4x1 MUX





© Alvin R. Lebeck from Hilton and Sorin

CS/ECE 250

Arithmetic and Logical Operations in ISA

- What operations are there?
- How do we implement them?
 - Consider a 1-bit Adder

Summary

- Boolean Algebra & functions
- Logic gates (AND, OR, NOT, etc)
- Multiplexors
- Download Logisim for Recitation

- http://ozark.hendrix.edu/~burch/logisim/download.html