 


# CIS 371 Computer Organization and Design

## Unit 2: Digital Logic & Hardware Description

Based on slides by Prof. Amir Roth & Prof. Milo Martin

## This Unit: Digital Logic & Hdw Description




- Transistors & fabrication
- Digital logic basics
  - Focus on useful components
- Hardware design methods
  - Introduction to Verilog

## Readings


- Digital logic
  - P&H, Appendix C
- Manufacturing
  - P&H, Section 1.7
- See webpage for Verilog HDL resources

## Motivation: Implementing a Datapath

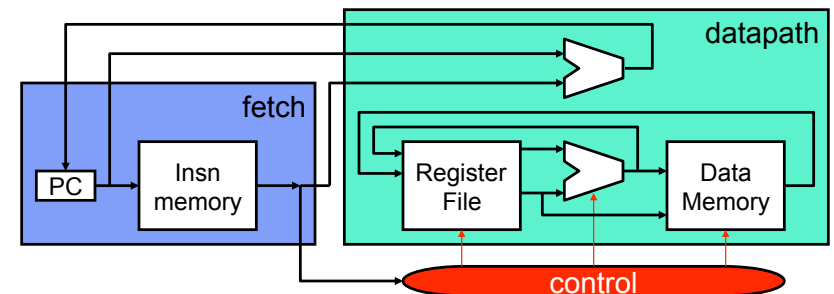



- **Datapath**: performs computation (registers, ALUs, etc.)
  - ISA specific: can implement every insn (single-cycle: in one pass!)
- **Control**: determines which computation is performed
  - Routes data through datapath (which regs, which ALU op)
- **Fetch**: get insn, translate opcode into control
- **Fetch** → **Decode** → **Execute** "cycle"

## Two Types of Components

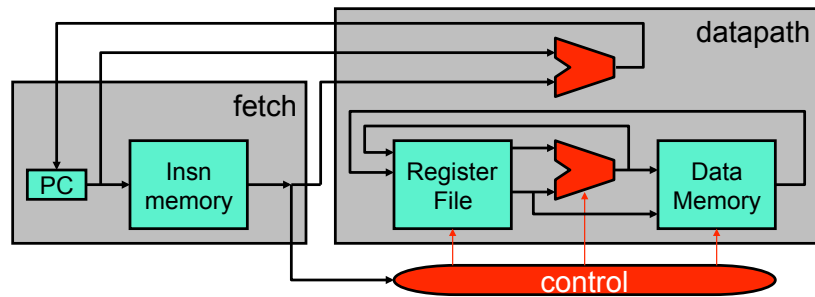


- **Purely combinational:** stateless computation
  - ALUs, muxes, control
  - Arbitrary Boolean functions
- **Combinational/sequential:** storage
  - PC, insn/data memories, register file
  - Internally contain some combinational components

## Example LC4 Datapath

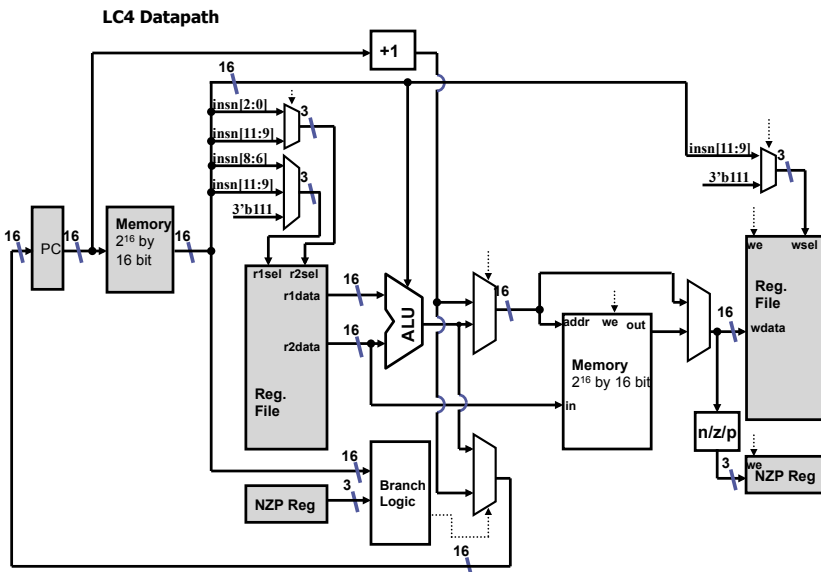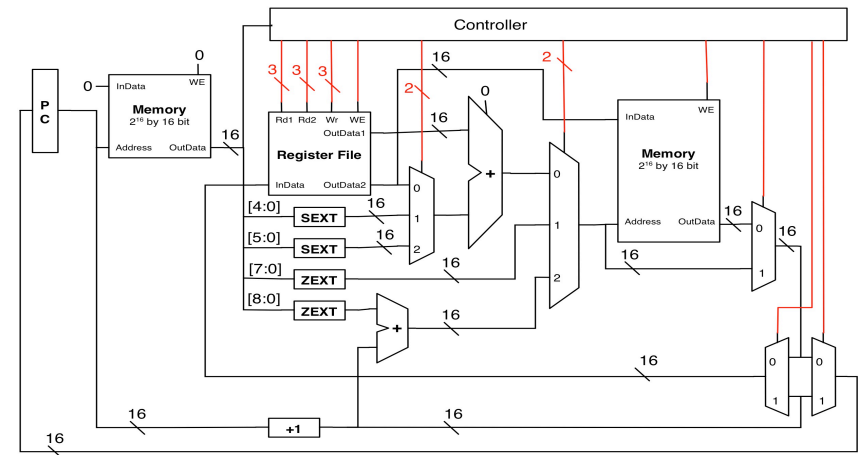


## Transistors & Fabrication

 


Intel Pentium M Wafer

## Semiconductor Technology

 


- Basic technology element: **MOSFET**
  - Solid-state component acts like electrical switch
  - **MOS**: metal-oxide-semiconductor
    - Conductor, insulator, semi-conductor
- **FET**: field-effect transistor
  - Channel conducts source→drain only when voltage applied to gate
- **Channel length**: characteristic parameter (short → fast)
  - Aka "feature size" or "technology"
  - Currently: 0.022 micron ( $\mu\text{m}$ ), 22 nanometers (nm)
  - Continued miniaturization (scaling) known as "**Moore's Law**"
    - Won't last forever, physical limits approaching (or are they?)

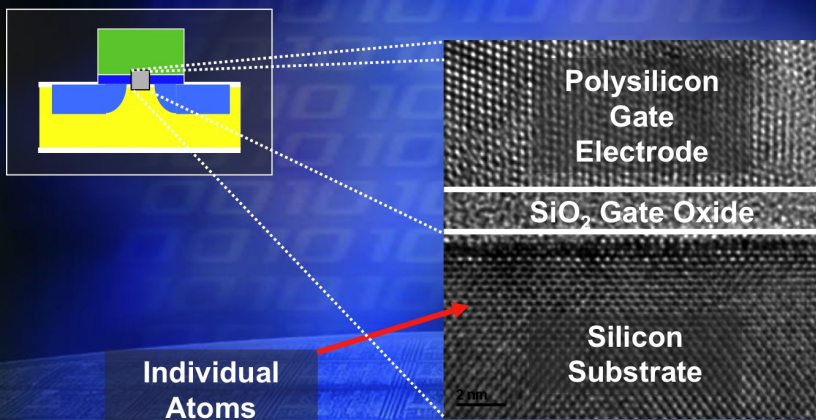
## Gate dielectric today is only a few molecular layers thick



## Transistors

 


## Transistor Geometry: Length & Scaling

 


- **Transistor length:** characteristic of “process generation”
  - “22nm” refers to the transistor gate length
- Each process generation shrinks transistor length by 1.4x
  - “Moore’s law” -> roughly 2x improvement transistor density
  - Roughly linear improvement in switching speeds (lower resistance)

## Manufacturing Steps

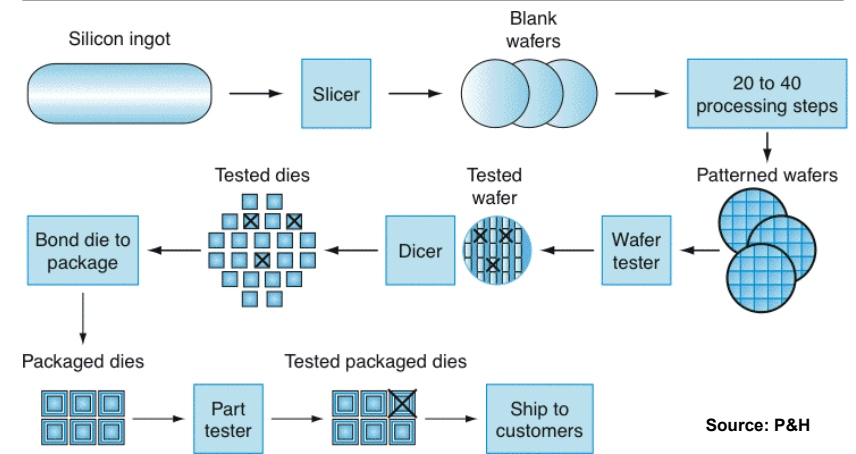


 
## Manufacturing Steps

- Multi-step photo-/electro-chemical process
  - More steps, higher unit cost
- + Fixed cost mass production (\$1 million+ for “mask set”)


  
## Integrated Circuit (IC) Costs

- Chips built in multi-step chemical processes on **wafers**
  - Cost / wafer is constant, f(wafer size, number of steps)
- Chip (die) cost is related to **area**
  - Larger chips means fewer of them
- Cost is more than linear in area
  - Why? random defects
  - Larger chips means fewer working ones
  - Chip cost  $\sim$  chip area $^\alpha$ 
    - $\alpha = 2$  to  $3$
- **Wafer yield:** % wafer that is chips
- **Die yield:** % chips that work
- Yield is increasingly non-binary - fast vs slow chips




## Manufacturing Defects

Correct:



Defective:

 

Defective:




Slow:




- Defects can arise
  - Under-/over-doping
  - Over-/under-dissolved insulator
  - Mask mis-alignment
  - Particle contaminants
- Try to minimize defects
  - Process margins
  - Design rules
    - Minimal transistor size, separation
- Or, tolerate defects
  - Redundant or "spare" memory cells
  - Can substantially improve yield

## Wires

 


- Transistors 1-dimensional for design purposes: **width**
- Wires 4-dimensional: **length, width, height, "pitch"**
  - Longer wires have more "resistance" (slower)
  - "Thinner" wires have more "resistance" (slower)
  - Closer wire spacing ("pitch") increases "capacitance" (slower)

## Transistors and Wires

 

 
## Complementary MOS (CMOS)

- Voltages as values
  - Power ( $V_{DD}$ ) = "1", Ground = "0"
- Two kinds of MOSFETs
  - **N-transistors**
    - Conduct when gate voltage is 1
    - Good at passing 0s
  - **P-transistors**
    - Conduct when gate voltage is 0
    - Good at passing 1s
- **CMOS**
  - Complementary n-/p- networks form boolean logic (i.e., gates)
  - And some non-gate elements too (important example: RAMs)


 
## Basic CMOS Logic Gate


- **Inverter:** NOT gate
  - One p-transistor, one n-transistor
  - Basic operation
  - Input = 0
    - P-transistor closed, n-transistor open
    - Power charges output (1)
  - Input = 1
    - P-transistor open, n-transistor closed
    - Output discharges to ground (0)



 
## Another CMOS Gate Example

- What is this? Look at **truth table**

- 0, 0 → 1
- 0, 1 → 1
- 1, 0 → 1
- 1, 1 → 0
- Result: **NAND** (NOT AND)
- NAND is "universal"




- What function is this?

 

 
## Digital Building Blocks: Logic Gates

- **Logic gates:** implement Boolean functions
  - Basic gates: NOT, NAND, NOR
    - Underlying CMOS transistors are naturally inverting (● = NOT)




- NAND, NOR are "Boolean complete"

 

## Alternative to Fabrication: FPGA

- We'll use **FPGAs (Field Programmable Gate Array)**
  - Also called Programmable Logic Devices (PLDs)
- An FPGA is a special type of programmable chip
  - Conceptually, contains a grid of gates
  - The wiring connecting them can be reconfigured electrically
    - Using more transistors as switches
  - Once configured, the FPGA can emulate any digital logic design
  - Tool converts **gate-level design** to configuration
- Uses
  - **Hardware prototyping** (what "we" are doing)
  - Low-volume special-purpose hardware
  - New: computational offload

## In Our Lab: Digilent XUP-V2P Boards

 

Program FPGA to run LC4

- "The project"
- Hook up keyboard
- And VGA
- Game on!

Boards have many features


Use some for debugging

- LEDs, switches
- Other features
- Ethernet, flash reader
- 256MB SDRAM, audio in/out
- Can boot Linux


## Digital Logic Review
 
## Digital Building Blocks: Logic Gates

- **Logic gates:** implement Boolean functions
  - Basic gates: NOT, NAND, NOR
  - Underlying CMOS transistors are naturally inverting (● = NOT)



- NAND, NOR are "Boolean complete"

 

## Boolean Functions and Truth Tables

- Any Boolean function can be represented as a truth table
  - **Truth table:** point-wise input  $\rightarrow$  output mapping
  - Function is disjunction of all rows in which "Out" is 1

A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


- Example above:  $Out = AB'C + ABC' + ABC$

## Truth Tables and PLAs

- Implement Boolean function by implementing its truth table
  - Takes two levels of logic
    - Assumes inputs and inverses of inputs are available (usually are)
  - First level: ANDs (product terms)
  - Second level: ORs (sums of product terms)
- **PLA (programmable logic array)**
  - Flexible circuit for doing this
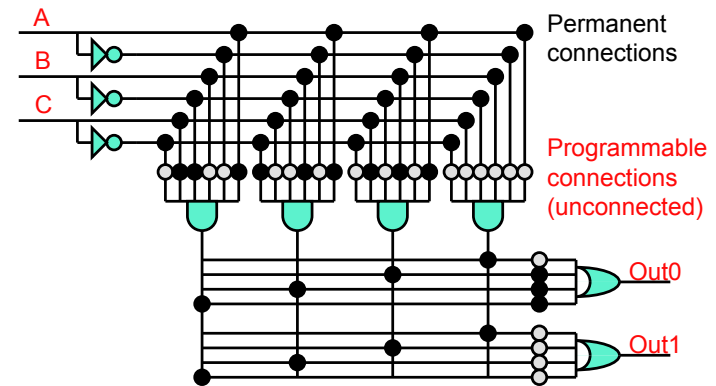
## PLA Example

- PLA with 3 inputs, 2 outputs, and 4 product terms
  - $Out0 = AB'C + ABC' + ABC$



## Boolean Algebra

- **Boolean Algebra:** rules for rewriting Boolean functions
  - Useful for simplifying Boolean functions
    - Simplifying = reducing gate count, reducing gate "levels"
  - Rules: similar to logic (0/1 = F/T)
    - **Identity:**  $A1 = A, A+0 = A$
    - **0/1:**  $A0 = 0, A+1 = 1$
    - **Inverses:**  $(A')' = A$
    - **Idempotency:**  $AA = A, A+A = A$
    - **Tautology:**  $AA' = 0, A+A' = 1$
    - **Commutativity:**  $AB = BA, A+B = B+A$
    - **Associativity:**  $A(BC) = (AB)C, A+(B+C) = (A+B)+C$
    - **Distributivity:**  $A(B+C) = AB+AC, A+(BC) = (A+B)(A+C)$
    - **DeMorgan's:**  $(AB)' = A'+B', (A+B)' = A'B'$

## Logic Minimization

- **Logic minimization**
  - Iterative application of rules to reduce function to simplest form
  - **Design tools do this automatically**

```

Out = AB'C + ABC' + ABC
Out = A(B'C + BC' + BC) // distributivity
Out = A(B'C + (BC' + BC)) // associativity
Out = A(B'C + B(C'+C)) // distributivity (on B)
Out = A(B'C + B1) // tautology
Out = A(B'C + B) // 0/1
Out = A((B'+B)(C+B)) // distributivity (on +B)
Out = A(1(B+C)) // tautology
Out = A(B+C) // 0/1
    
```




## Non-Arbitrary Boolean Functions

- PLAs implement Boolean functions point-wise
  - E.g., represent  $f(X) = X+5$  as  $[0 \rightarrow 5, 1 \rightarrow 6, 2 \rightarrow 7, 3 \rightarrow 8, \dots]$
  - Mainly useful for "arbitrary" functions, no compact representation
- Many useful Boolean functions are not arbitrary
  - Have a compact implementation
  - Examples
    - Multiplexer
    - Adder
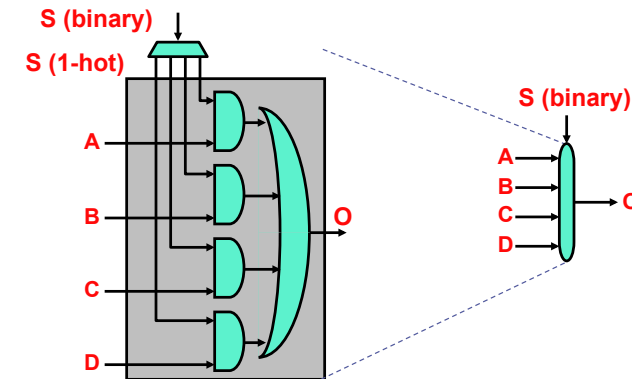
## Multiplexer (Mux)

- **Multiplexer (mux)**: selects output from N inputs
  - Example: 1-bit 4-to-1 mux
  - Not shown: N-bit 4-to-1 mux = N 1-bit 4-to-1 muxes + 1 decoder




## Adder

- **Adder**: adds/subtracts two 2C binary integers
  - **Half adder**: adds two 1-bit "integers", no carry-in
  - **Full adder**: adds three 1-bit "integers", includes carry-in
  - **Ripple-carry adder**: N chained full adders add 2 N-bit integers
  - **To subtract**: negate B input, set bit 0 carry-in to 1

## Full Adder


- What is the logic for a full adder?
  - Look at truth table

CI	A	B	→	CO	S
0	0	0	→	0	0
0	0	1	→	0	1
0	1	0	→	0	1
0	1	1	→	1	0
1	0	0	→	0	1
1	0	1	→	1	0
1	1	0	→	1	0
1	1	1	→	1	1

 

- $S = C'A'B + C'AB' + CA'B' + CAB = C \wedge A \wedge B$
- $CO = C'AB + CA'B + CAB' + CAB = CA + CB + AB$

## N-bit Adder/Subtractor

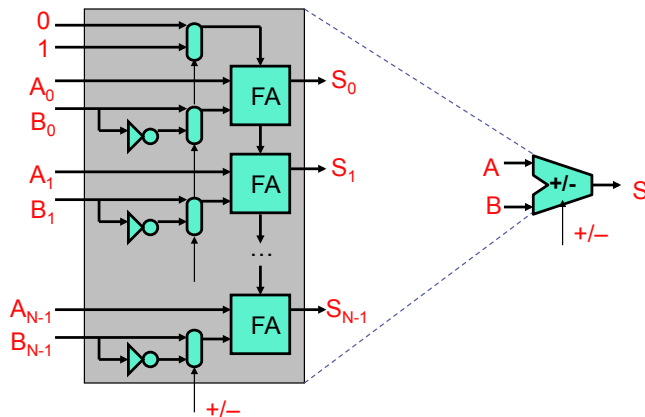

- More later when we cover arithmetic

## Hardware Design Methods


## Hardware Design Methodologies

- Fabricating a chip requires a detailed layout
  - All transistors & wires
- How does a hardware designer describe such design?
  - (Bad) Option #1: draw all the masks "by hand"
    - All 1 billion transistors? Umm...
  - Option #2: use computer-aided design (CAD) tools to help
    - Layout done by engineers with CAD tools or automatically
- Design levels – uses **abstraction**
  - **Transistor-level** design – designer specifies transistors (not layout)
  - **Gate-level** design – designer specifies gates, wires (not transistors)
  - **Higher-level** design – designer uses higher-level building blocks
    - Adders, memories, etc.
    - Or logic in terms of and/or/not, and tools translates into gate

## Describing Hardware

- Two general options
- Schematics
  - Pictures of gates & wires
- Hardware description languages
  - Use textual descriptions to specify hardware
- Translation process called "synthesis"
  - Textual description -> gates -> full layout
    - Tries to minimize the delay and/or number of gates
  - Much like process of compilation of software

# Schematics

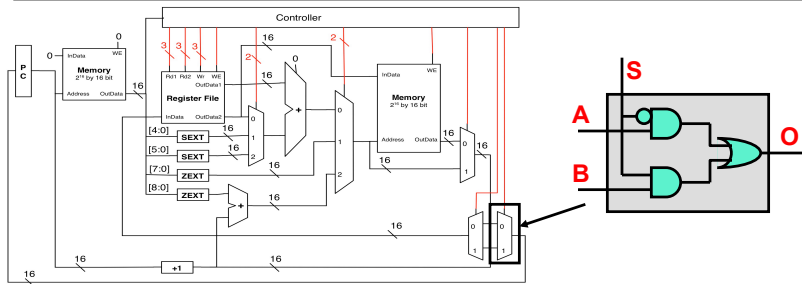

- Draw pictures
  - Use a schematic entry program to draw wires, logic blocks, gates
  - Support hierarchical design (arbitrary nesting)
  - + Good match for hardware which is inherently spatial, purty
  - Time consuming, "non-scalable" (large designs are unreadable)
  - Rarely used in practice ("real-world" designs are big)


# Hardware Description Languages (HDLs)

- Write "code" to describe hardware
  - HDL vs. SDL
  - Specify wires, gates, modules (also hierarchical)
  - + Easier to create, edit, modify, scales well
  - Disconnect: must still "think" visually (gets easier with practice)

```

module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;
  wire S_, AnS_, BnS_;

   not (S_, S);
  and (AnS_, A, S_);
  and (BnS_, B, S);
  or (Out, AnS_, BnS);
endmodule
    
```




# (Hierarchical) HDL Example

- Build up more complex modules using simpler modules
  - Example: 4-bit wide mux from four 1-bit muxes

```

module mux2to1_4(S, A, B, Out);
  input [3:0] A;
  input [3:0] B;
  input S;
  output [3:0] Out;

   mux2to1 mux0 (S, A[0], B[0], Out[0]);
  mux2to1 mux1 (S, A[1], B[1], Out[1]);
  mux2to1 mux2 (S, A[2], B[2], Out[2]);
  mux2to1 mux3 (S, A[3], B[3], Out[3]);
endmodule
    
```



# Verilog HDL

- **Verilog**: HDL we will be using
  - Syntactically similar to C (by design)
  - ± Ease of syntax hides fact that this isn't C (or any SDL)
  - We will use a few lectures to learn Verilog

```

module mux2to1_4(S, A, B, Out);
  input [3:0] A;
  input [3:0] B;
  input S;
  output [3:0] Out;

  mux2to1 mux0 (S, A[0], B[0], Out[0]);
  mux2to1 mux1 (S, A[1], B[1], Out[1]);
  mux2to1 mux2 (S, A[2], B[2], Out[2]);
  mux2to1 mux3 (S, A[3], B[3], Out[3]);
endmodule
    
```

← These aren't variables

← These aren't function calls

## HDLs are not “SDLs” (PLs)

---

- Similar in some (intentional) ways ...
  - Syntax
    - Named entities, constants, scoping, etc.
  - Tool chain: synthesis tool analogous to compiler
    - Multiple levels of representation
    - “Optimization”
    - Multiple targets (portability)
  - “Software” engineering
    - Modular structure and parameterization
    - Libraries and code repositories
- ... but different in many others
  - One of the most difficult conceptual leaps of this course

## Hardware is not Software

---

- Just two different beasts (or two parts of the same beast)
  - Things that make sense in hardware, don’t in software, vice versa
  - One of the main themes of 371
- **Software is sequential**
  - Hardware is inherently parallel, at multiple levels
  - Have to work to get hardware to *not* do things in parallel
- Software atoms are purely functional (“digital”)
  - Hardware atoms have quantitative (“analog”) properties too
  - Including correctness properties!
- Software mostly about quality (“functionality”)
  - Hardware mostly about quantity: performance, area, power, etc.
- One reason that HDLs are not SDLs

## HDL: Behavioral Constructs

---

- HDLs have **low-level structural** constructs
  - Specify hardware structures directly
  - Transistors, gates (**and**, **not**) and wires, hierarchy via modules
- Also have **mid-level behavioral** constructs
  - Specify operations, not hardware to perform them
  - Low-to-medium-level: **&**, **~**, **+**, **\***
- Also **higher-level behavioral** constructs
  - High-level: **if-then-else**, **for** loops
  - Some of these are synthesizable (some are not)
    - Tools try to guess what you want, often highly inefficient
    - Higher-level → more difficult to know what it will synthesize to!
- HDLs are both high- and low-level languages in one!
  - And the boundary is not clear!

## HDL: Simulation

---

- Another use of HDL: simulating & testing a hardware design
  - Cheaper & faster turnaround (no need to fabricate)
  - More visibility into design (“debugger” interface)
- **HDLs have features just for simulation**
  - Higher level data types: integers, FP-numbers, timestamps
  - Higher level control structures: for-loops, conditionals
  - Routines for I/O: error messages, file operations
  - Obviously, **these cannot be synthesized into circuits**
- Also another reason for HDL/SDL confusion
  - HDLs have “SDL” features for simulation

---

## Verilog HDL

---

## Verilog HDL

- Verilog is a (surprisingly) big language
  - Structural constructs at both gate and transistor level
  - Facilities for specifying memories
  - Precise timing specification and simulation
  - Lots of “behavioral” constructs
  - C-style procedural variables, including arrays
  - A pre-processor
  - VPI: Verilog programming interface
  - ...

---

## HDL History

- 1970s:
  - First HDLs
- Late 1970s: VHDL
  - VHDL = VHSIC HDL = Very High Speed Integrated Circuit HDL
  - VHDL inspired by programming languages of the day (Ada)
- 1980s:
  - Verilog first introduced
  - Verilog inspired by the C programming language
  - VHDL standardized
- 1990s:
  - Verilog standardized (Verilog-1995 standard)
- 2000s:
  - Continued evolution (Verilog-2001 standard)
- Both VHDL and Verilog evolving, still in use today

---

## 371 Verilog HDL

- **We’re going to learn a focused *subset* of Verilog**
  - Focus on synthesizable constructs
  - Focus on avoiding subtle synthesis errors
  - Use as an educational tool
- For synthesis
  - Structural constructs at gate-level only
  - A few behavioral constructs
- Some testing and debugging features

**Rule 1: if you haven’t seen it in lecture, you can’t use it!**

**Rule 1a: when in doubt, ask!**

## Basic Verilog Syntax

- Have already seen basic syntax, looks like C
  - C/C++/Java style comments
  - Names are case sensitive, and can use \_ (underscore)
  - Avoid: clock, clk, power, pwr, ground, gnd, vdd, vcc, init, reset, rst
    - Some of these are "special" and will silently cause errors

```

/* this is a module */
module mux2to1(S, A, B, Out);
    input S, A, B;
    output Out;
    wire S_, AnS_, BnS;
    // these are gates
    not (S_, S);
    and (AnS_, A, S_);
    and (BnS_, B, S);
    or (Out, AnS_, BnS);
endmodule
    
```


## (Gate-Level) Structural Verilog

- Primitive "data type": **wire**
  - Have to declare it
 
### Structural

```

module mux2to1(S, A, B, Out);
    input S, A, B;
    output Out;
    wire S_, AnS_, BnS;
    not (S_, S);
    and (AnS_, A, S_);
    and (BnS_, B, S);
    or (Out, AnS_, BnS);
endmodule
    
```




## (Gate-Level) Structural Verilog

- Primitive "operators": gates
  - Specifically: **and, or, xor, nand, nor, xnor, not, buf**
  - Can be multi-input: e.g., **or (C, A, B, D)** (C = A+B+D)
  - "Operator" **buf** just repeats input signal (may amplify it)
 
### Structural

```

module mux2to1(S, A, B, Out);
    input S, A, B;
    output Out;
    wire S_, AnS_, BnS;
    not (S_, S);
    and (AnS_, A, S_);
    and (BnS_, B, S);
    or (Out, AnS_, BnS);
endmodule
    
```




## (Gate-Level) Behavioral Verilog

- Primitive "operators": boolean operators
  - Specifically: **&, |, ^, ~**
  - Can be combined into expressions
  - Can be mixed with structural Verilog

### "Behavioral" (Synthesizable)

```

module mux2to1(S, A, B, Out);
    input S, A, B;
    output Out;
    wire S_, AnS_, BnS;
    assign S_ = ~S;
    assign AnS_ = A & S_;
    assign BnS_ = B & S;
    assign Out = AnS_ | BnS;
endmodule
    
```

 


## Wire Assignment

- **Wire assignment:**
  - Connect combinational logic block or other wire to wire input
  - **Order of statements not important**, executed totally in parallel
  - When right-hand-side changes, it is re-evaluated and re-assigned
  - Designated by the keyword **assign**

### “Behavioral” (Synthesizable)

```
module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;
  wire S_, AnS_, BnS;
  assign S_ = ~S;
  assign AnS_ = A & S_;
  assign BnS = B & S;
  assign Out = AnS_ | BnS;
endmodule
```

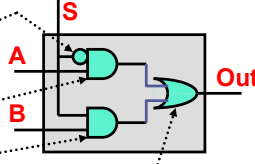

## Wire Assignment


- Assignment can be combined with declaration

```
wire c = a | b;
```

### “Behavioral” (Synthesizable)

```
module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;

  wire S_ = ~S;
  wire AnS_ = A & S_;
  wire BnS = B & S;
  assign Out = AnS_ | BnS;
endmodule
```

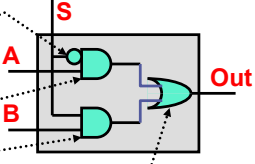


## (Gate-Level) Behavioral Verilog

- Primitive “operators”: boolean operators
  - Specifically: **&**, **|**, **^**, **~**
  - **Can be combined into expressions**
  - Can be mixed with structural Verilog

### “Behavioral” (Synthesizable)

```
module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;

  assign Out = (~S & A) | (S & B);
endmodule
```

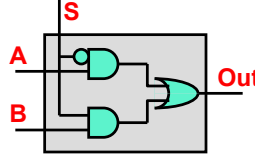


## Easiest Way to do a Mux?

- Verilog supports **?:** conditional assignment operator
  - Much more useful (and common) in Verilog than in C/Java

### “Behavioral” (Synthesizable)

```
module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;

  assign Out = S ? B : A;
endmodule
```

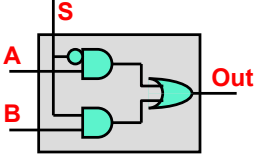

## Wires Are Not C-like Variables!

- Order of assignment doesn't matter

```
• This works fine
module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;
  wire S_, AnS_, BnS;
  assign Out = AnS_ | BnS;
  assign BnS = B & S;
  assign AnS_ = A & S_;
  assign S_ = ~S;
endmodule
```

- Can't "reuse" a wire

```
assign temp = a & b;
assign temp = a | b;
```

- Actually, you can; but doesn't do what you think it does

## Wire Vectors

- Wire vectors: also called "arrays" or "buses"

```
wire [7:0] w1; // 8 bits, w1[7] is most significant bit
wire [0:7] w2; // 8 bits, w2[0] is most significant bit
```

- Example:

```
module 8bit_mux2to1 (S, A, B, Out);
  input S;
  input [7:0] A, B;
  output [7:0] Out;
  assign Out = S ? B : A;
endmodule
```

Unlike C, array range is part of type, not variable!

- Operations

- Bit select: `vec[3]`
- Range select: `vec[3:2]`
- Concatenate: `assign vec = {x, y, z};`

## Repeated Signals

- Concatenation

```
wire vec[2:0] = {x, y, z};
```

- Can also repeat a signal n times

```
wire vec[15:0] = {16{x}}; // 16 copies of x
```

- Example uses (what does this do?):

```
wire [7:0] out;
wire [3:0] A;
assign out = {4{1'd0}}, A[3:0];
```

- What about this?

```
assign out = {4{A[3]}}, A[3:0];
```

## Gate-Level Vector Operators

- Verilog also supports behavioral vector operators

- Logical bitwise and reduction:** `~, &, |, ^`

```
wire [7:0] vec1, vec2;
wire [7:0] vec3 = vec1 & vec2; // bitwise AND
wire w1 = ~|vec1; // NOR reduction
```

- Integer arithmetic comparison:** `+, -, *, /, %, ==, !=, <, >`

```
wire [7:0] vec4 = vec1 + vec2; // vec1 + vec2
```

- Important: all arithmetic is unsigned, want signed? "roll your own"
- Good: in signed/unsigned integers: `+, -, *` produces same output
  - Just a matter of interpretation
- Bad: in signed/unsigned integers: `/, %` is not the same
- Ugly: Xilinx will not synthesize `/, %` anyway
  - Need to implement divider for LC4's DIV and MOD instructions



## Why Use a High-Level Operator?

- Abstraction
  - Why write assembly, when you can write C? (not a great example)
- Take advantage of built-in high level implementation
  - Virtex-IIPro FPGAs have integer multipliers on them
  - Xilinx will use these rather than synthesizing a multiplier from gates
    - Much faster and more efficient
  - How hard is it for Xilinx to figure out you were doing a multiply?
    - If you use `*`: easy
    - If you "roll your own" using gates: nearly impossible
- Why *not* use high-level operators?
  - Less certain what they will synthesize to
  - Or even if it will synthesize at all: e.g., /, %

## Wire and Wire Vector Constants

- ```
wire [3:0] w = 4'b0101;
```
- The "4" is the number of bits
  - The "b" means "binary" - "h" for hex, "o" for octal, "d" for decimal
  - The "0101" are the digits (in binary in this case)
- ```
wire [3:0] w = 4'd5; // same thing, effectively
```
- Here is a single wire constant
- ```
wire w = 1'b0;
```
- A useful example of wire-vector constants:
- ```
module mux4to1(Sel, A, B, C, D, Out);
  input [1:0] Sel;
  input A, B, C, D;
  output Out = (Sel == 2'd0) ? A :
               (Sel == 2'd1) ? B :
               (Sel == 2'd2) ? C : D;
endmodule
```

## Hierarchical Design using Modules

- Interface specification

```
module mux2to1(Sel, A, B, Out);
  input Sel, A, B;
  output Out;
```

  - Can also have `inout`: bidirectional wire (we will not need)
- Alternative: Verilog 2001 interface specification

```
module mux2to1(input Sel, A, B, output Out);
```
- Declarations
  - Internal wires, i.e., "locals"
  - Wires also known as "nets" or "signals"


```
wire S_, AnS_, BnS;
```
- Implementation: primitive and module instantiations

```
and (AnS_, A, S_);
and (BnS_, B, S_);
or (O, AnS_, BnS_);
```
 
## Verilog Module Example

```
module mux2to1(S, A, B, O);
  input S, A, B;
  output O;
  wire S_, AnS_, BnS;

  not (S_, S);
  and (AnS_, A, S_);
  and (BnS_, B, S);
  or (O, AnS_, BnS);
endmodule
```



- Instantiation: `mux2to1 mux0 (cond, in1, in2, out);`
  - Non-primitive module instances must be named (helps debugging)
- Operators and expressions can be used with modules
  - `mux2to1 mux0 (cond1 & cond2, in1, in2, out);`

## Hierarchical Verilog Example

- Build up more complex modules using simpler modules
- Example: 4-bit wide mux from four 1-bit muxes
  - Again, just “drawing” boxes and wires

```
module mux2to1_4(Sel, A, B, O);
    input [3:0] A;
    input [3:0] B;
    input Sel;
    output [3:0] O;

    mux2to1 mux0 (Sel, A[0], B[0], O[0]);
    mux2to1 mux1 (Sel, A[1], B[1], O[1]);
    mux2to1 mux2 (Sel, A[2], B[2], O[2]);
    mux2to1 mux3 (Sel, A[3], B[3], O[3]);
endmodule
```

## Connections by Name

- Can (should?) specify module connections by name
  - Helps keep the bugs away
  - Example
  - Also, then order doesn't matter

```
mux2to1 mux0 (.S(Sel), .A(A[0]), .B(B[0]), .O(O[0]));
mux2to1 mux1 (.A(A[1]), .B(B[1]), .O(O[1]), .S(Sel));
```

## Per-Instance Module Parameters

- Module parameters: useful for defines varying bus widths
  - But for widths, not “types” (in HDL “width” == “type”)

```
module Nbit_mux2to1 (Sel, A, B, Out);
    parameter N = 1;
    input [N-1:0] A, B;
    input Sel;
    output [N-1:0] Out;
    assign Out = Sel ? B : A;
endmodule
```

- Two ways to instantiate: implicit

```
Nbit_mux2to1 #(4) mux1 (S, in1, in2, out);
```
- And explicit


```
Nbit_mux2to1 mux1 (S, in1, in2, out);
defparam mux1.N = 4;
```
- Multiple parameters per module allowed

## Verilog Pre-Processor

- Like the C pre-processor
  - But uses ` (back-tick) instead of #
  - Constants: ``define`
    - No parameterized macros
    - Use ` before expanding constant macro
  - ``define letter_A 8'h41`  
`wire w[7:0] = `letter_A;`
  - Conditional compilation: ``ifdef`, ``endif`
  - File inclusion: ``include`
- Parameter vs ``define`
  - Parameter only for “per instance” constants
  - ``define` for “global” constants

## Sequential Logic
 
## Sequential Logic & Synchronous Systems




- Processors are complex fine state machines (FSMs)
  - Combinational (compute) blocks separated by storage elements
    - State storage: memories, registers, etc.
- Synchronous systems**
  - Clock:** global signal acts as write enable for all storage elements
    - Typically marked as triangle
  - All state elements write together, values move forward in lock-step
    - + Simplifies design: design combinational blocks independently
- Aside: asynchronous systems
  - Same thing, but ... no clock
  - Values move forward using explicit handshaking
    - ± May have some advantages, but difficult to design

## Two Types of Digital Circuits

- Combinational Logic**
  - Logic **without state** variables
  - Examples: adders, multiplexers, decoders, encoders
  - No clock involved**
- Sequential Logic**
  - Logic **with state** variables
  - State variables: latches, flip-flops, registers, memories
  - Clocked**
  - State machines, multi-cycle arithmetic, processors
- Sequential Logic in Verilog**
  - Special idioms using behavioral constructs that synthesize into latches, memories


## Datapath Storage Elements

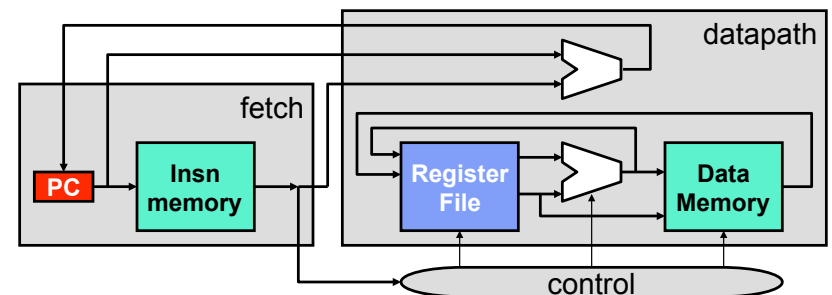

- Three main types of storage elements
  - Singleton registers:** PC
  - Register files:** ISA registers
  - Memories:** insn/data memory
 
## Cross-Coupled Inverters (CCIs)

- **Cross-coupled inverters (CCIs)**
  - Primitive "storage element" for storing state
  - Most storage arrays (regfile, caches) implemented this way
  - Where is the input and where is the output?




## S-R Latch

- **S-R (set-reset) latch**

- Cross-coupled NOR gates
- Distinct inputs/outputs

S, R	Q
0, 0	old Q
0, 1	0
1, 0	1
1, 1	0

 

- S=0, R=0? circuit degenerates to cross-coupled INVs
- S=1, R=1? not very useful
- Not really used ... except as component in something else

## D Latch

- **D latch:** S-R latch + ...

- control that makes S=R=1 impossible


E, D	Q
0, 0	old Q
0, 1	old Q
1, 0	0
1, 1	1

- In other words

0, D	old Q
1, D	D


- In words

 - When E is 1, Q gets D
- When E is 0, Q retains old value



 
## Timing Diagrams

- Voltage {0,1} diagrams for different nodes in system
  - "Digitally stylized": changes are vertical lines (instantaneous?)
  - Reality is analog, changes are continuous and smooth
- Timing diagram for a D latch



## Triggering: Level vs. Edge


 


- The D-latch is **level-triggered**
  - The latch is open for writing as long as E is 1
  - If D changes continuously, so does Q
    - May not be the functionality we want
- Often easier to reason about an **edge-triggered** latch
  - The latch is open for writing only on E transition ( $0 \rightarrow 1$  or  $1 \rightarrow 0$ )
    - + Don't need to worry about fluctuations in value of D

## D Flip-Flop

  
### • D Flip-Flop:

- Sequential D-latches
- Enabled by inverse signals
- First latch open when  $E = 0$
- Second latch open when  $E = 1$
- Overall effect?
  - D flipflop latches D on  $0 \rightarrow 1$  transition
- E is the "clock" signal input



 
## FF<sub>WE</sub>: FF with Separate Write Enable

- **FF<sub>WE</sub>**: FF with separate write enable
  - FF D(ata) input is MUX of D and Q, WE selects



- Bad idea: why not just AND the CLK and WE?
  - + Fewer gates
  - Creates timing problems
    - Do not try to do logic on CLK in Verilog
    - No, really. Never do this.

## N-bit Register

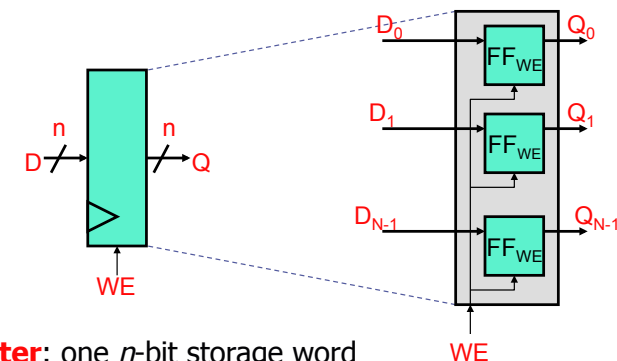


- **Register**: one  $n$ -bit storage word
  - Non-multiplexed input/output: data buses write/read same word
- Implementation: FF<sub>WE</sub> array with shared write-enable (WE)
  - FFs written on CLK edge if WE is 1 (or if there is no WE)

## Sequential Logic in Verilog
 
## Designing Sequential Logic

- CIS371 design rule: separate combinational logic from sequential state elements
  - Not enforced by Verilog, but a very good idea
  - Possible exceptions: counters, shift registers
- We'll give you a flip-flop module (see next slide)
  - Edge-triggered, not a transparent latch
  - Parameterized to create a  $n$ -bit register
- Example use: state machine



## Sequential Logic In Verilog


- How are state-holding variables specified in Verilog?
  - First instinct: structurally
  - After all, real latches and flip-flops are made from gates...

```

module latch(out, in, we);
  output out; input in, we;
  wire not_out = ~(out | (we & ~in));
  assign out = ~(not_out | (we & in));
endmodule

```

 - This should work, right? RIGHT?
  - Logically, yes... in practice, no
    - Storage elements are highly analog
    - FPGAs have dedicated storage



## Verilog Flipflop (Behavioral Magic)

- How do we specify state-holding constructs in Verilog?

```
module dff (out, in, wen, rst, clk);
```

```

  output out;
  input in;
  input wen, rst, clk;

  wen = write enable
  rst = reset
  clk = clock

```

```

reg out;
always @(posedge clk)
begin
  if (rst)
    out = 0;
  else if (wen)
    out = in;
end

```

- **reg**: interface-less storage bit
- **always @ ( )**: synthesizable behavioral sequential Verilog
  - Tricky: hard to know exactly what it will synthesize to
  - **We will give this to you, don't write your own**
  - "Creativity is a poor substitute for knowing what you're doing"

```
endmodule
```

## Verilog Register (Behavioral Magic)

- How do we specify state-holding constructs in Verilog?

```
module register (out, in, wen, rst, clk);  
    parameter n = 1;                wen = write enable  
    output [n-1:0] out;              rst = reset  
    input [n-1:0] in;                clk = clock  
    input wen, rst, clk;
```

```
    reg [n-1:0] out;  
    always @(posedge clk) reg: interface-less storage bit  
    begin always @ ( ): synthesizable behavioral sequential Verilog  
        if (rst)   
            out = 0;  
        else if (wen)   
            out = in;  
    end
```


endmodule

## Clocks Signals

- Clocks & reset signals are **not** normal signals
- Travel on dedicated "clock" wires
  - Reach all parts of the chip
  - Special "low-skew" routing
- Ramifications:
  - Never do logic operations on the clocks
  - If you want to add a "write enable" to a flip-flop:
    - Use a mux to route the old value back into it
    - (or use the flip-flop with write enable we give you!)
    - Do not just "and" the write-enable signal with the clock!
- Messing with the clock can cause a errors
  - Often can only be found using detail low-level simulation
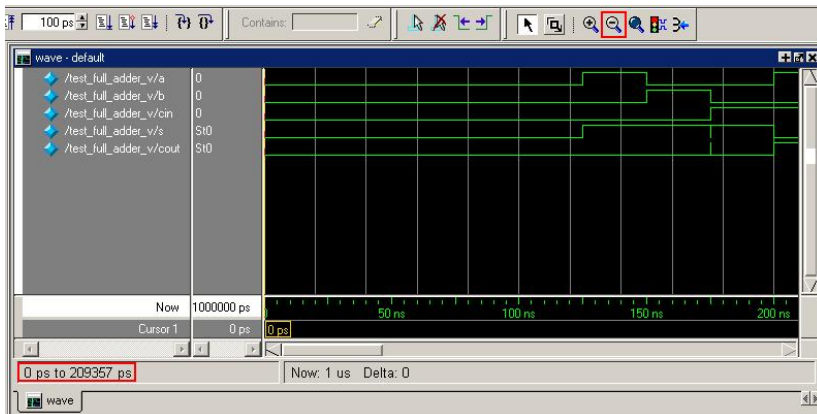
## Simulation

- One way to test and debug designs
- Graphical output via waveforms



## Testbenches

- A more effective way to test & debug designs
- In C/Java?
  - Write test code in C/Java to test C/Java
  - "Test harness", "unit testing"
- For Verilog/VHDL?
  - Write test code in Verilog to test Verilog
  - Verilog has advanced "behavioral" commands to facilitate this:
    - Delay for  $n$  units of time
    - Full high-level constructs: if, while, sequential assignment, ints
    - Input/output: file I/O, output to display, etc.

## Common Errors

---

- Tools are from a less gentle time
  - More like C, less like Java
  - Assume that you mean what you say
- Common errors:
  - Not assigning a wire a value
  - Assigning a wire a value more than once
  - Implicit wire declarations (default to type "wire" 1-bit wide)
- Avoid names such as:
  - clock, clk, power, pwr, ground, gnd, vdd, vcc, init, reset, rst
  - Some of these are "special" and will silently cause errors


## Additional Verilog Resources

---

- Elements of Logic Design Style by Shing Kong, 2001
  - Dos, do-nots, tips
  - <http://www.cis.upenn.edu/~milom/elements-of-logic-design-style/>
- Verilog HDL Synthesis: A Practical Primer
  - By J. Bhasker, 1998
  - To the point (<200 pages)
- Advanced Digital Design with the Verilog HDL
  - By Michael D. Ciletti, 2003
  - Verilog plus lots of digital logic design (~1000 pages)
- Verilog tutorial from textbook (posted on course web page)

## Summary

---

 

- Transistors & fabrication
- Digital logic basics
  - Focus on useful components
- Hardware design methods
  - Introduction to Verilog
- Next unit: single-cycle datapath