

ESE534: Computer Organization

Day 21: April 12, 2010
Retiming



Penn ESE534 Spring2010 -- DeHon

Today

- Retiming Demand
 - Folded Computation
 - Logical Pipelining
 - Physical Pipelining
- Retiming Supply
 - Technology
 - Structures
 - Hierarchy

Penn ESE534 Spring2010 -- DeHon

2

Retiming Demand

Penn ESE534 Spring2010 -- DeHon

3

Image Processing

- Many operations can be described in terms of 2D window filters
 - Compute value as a weighted sum of the neighborhood
 - $Out[x][y]=in[x][y]*c[1][1]+in[x-1][y]c[0][1]+in[x][y-1]*c[1][0]+in[x+1][y]*c[2][1]+in[x][y+1]*c[1][2]....$
- Blurring, edge and feature detection, object recognition and tracking, motion estimation, VLSI design rule checking

Penn ESE534 Spring2010 -- DeHon

4

Preclass 2

- Describes window computation:
 - 1: for x=0 to N-1
 - 2: for y=0 to N-1
 - 3: out[x][y]=0;
 - 4: for wx=0 to W-1
 - 5: for wy=0 to W-1
 - 6: out[x][y]+=in[x+wx][y+wy]*c[wx][wy]

Penn ESE534 Spring2010 -- DeHon

5

Preclass 2

- How many times is each $in[x][y]$ used?
 - 1: for x=0 to N-1
 - 2: for y=0 to N-1
 - 3: out[x][y]=0;
 - 4: for wx=0 to W-1
 - 5: for wy=0 to W-1
 - 6: out[x][y]+=in[x+wx][y+wy]*c[wx][wy]

Penn ESE534 Spring2010 -- DeHon

6

Preclass 2

- Sequentialized on one multiplier,
 - Distance between $\text{in}[x][y]$ uses?


```

1: for x=0 to N-1
2:   for y=0 to N-1
3:     out[x][y]=0;
4:     for wx=0 to W-1
5:       for wy=0 to W-1
6:         out[x][y]+=in[x+wx][y+wy]*c[wx][wy]
    
```

Penn ESE534 Spring2010 -- DeHon

7

Window

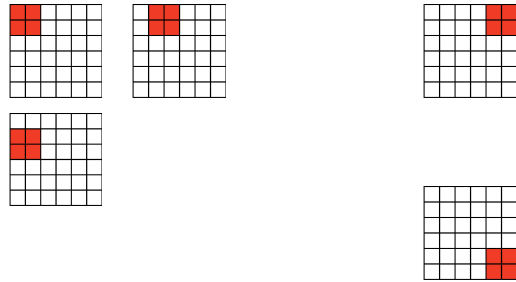


Penn ESE534 Spring2010 -- DeHon

8

Parallel Scaling/Spatial Sum

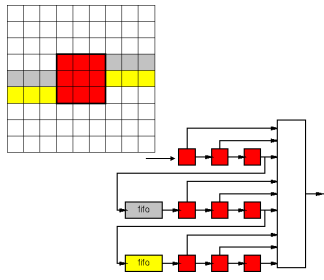- Compute entire window at once
 - More hardware, fewer cycles



Penn ESE534 Spring2010 -- DeHon

Preclass 2

- Unroll inner loop,
 - Distance between $\text{in}[x][y]$ uses?

```

1: for x=0 to N-1
2:   for y=0 to N-1
3:     out[x][y]=0;
4:     for wx=0 to W-1
5:       for wy=0 to W-1
6:         out[x][y]+=in[x+wx][y+wy]*c[wx][wy]
    
```

Penn ESE534 Spring2010 -- DeHon

10

Fully Spatial


- What if we gave each pixel its own processor?

Penn ESE534 Spring2010 -- DeHon

11

Preclass 1

- How many registers on each link?

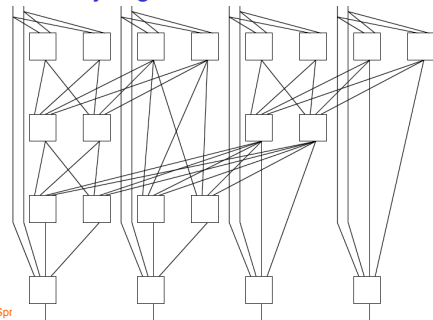

Penn ESE534 Spr

12

Flop Experiment #1

- Pipeline/C-slow/retime to single LUT delay per cycle
 - MCNC benchmarks to 256 4-LUTs
 - **no interconnect accounting**

Number of Registers	1	2	3	4	5	6	7	8	9	10
Percentage	72	16	4.5	2.2	1.3	0.96	1.2	0.46	0.12	0.11



- average 1.7 registers/LUT (some circuits 2--7)

Penn ESE534 Spring2010 -- DeHon

13

Long Interconnect Path

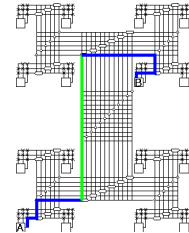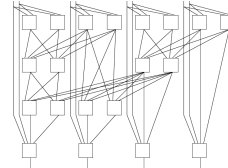- What happens if one of these links ends up on a long interconnect path?





Penn ESE680-002 Fall2007 -- DeHon

14

Pipeline Interconnect Path

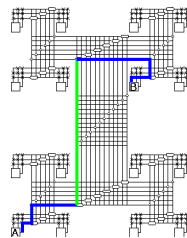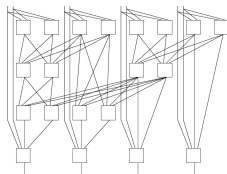- To avoid cycle being limited by longest interconnect
 - Pipeline network



Penn ESE680-002 Fall2007 -- DeHon

15

Chips >> Cycles


- Chips growing
- Gate delays shrinking
- Wire delays aren't scaling down
- → Will take many cycles to cross chip

DeHon Dagstuhl 06361

16

Clock Cycle Radius


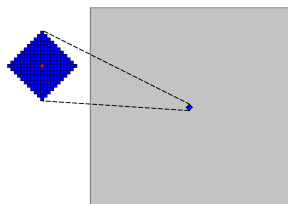
- Radius of logic can reach in one cycle (45 nm)
 - Radius 10 (preclass 20: $L_{seg}=5 \rightarrow 50ps$)
 - Few hundred PEs
 - Chip side 600-700 PE
 - 400-500 thousand PEs
 - 100s of cycles to cross



DeHon Dagstuhl 06361

Pipelined Interconnect

- In what cases is this convenient?

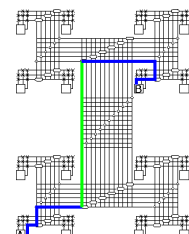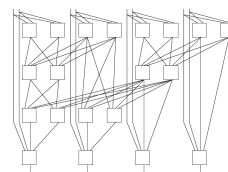


Penn ESE680-002 Fall2007 -- DeHon

18

Pipelined Interconnect

- When might it pose a challenge?

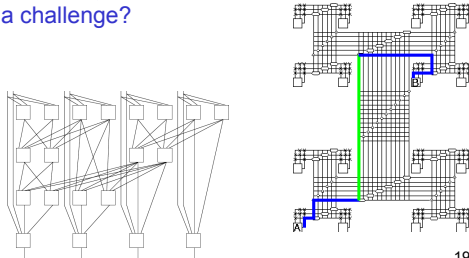


Penn ESE680-002 Fall2007 -- DeHon

19

Long Interconnect Path

- What happens here?

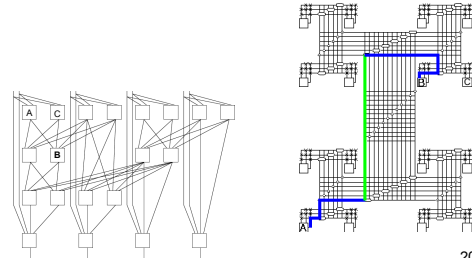


Penn ESE680-002 Fall2007 -- DeHon

20

Long Interconnect Path

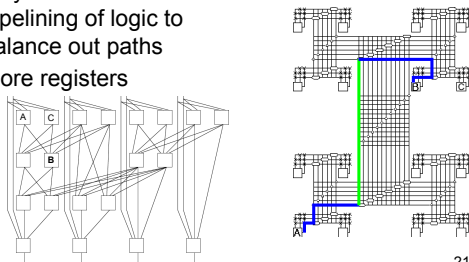- Adds pipeline delays
- May force further pipelining of logic to balance out paths
- More registers



Penn ESE680-002 Fall2007 -- DeHon

21

Reminder

Flop Experiment #1

- Pipeline/C-slow/retime to single LUT delay per cycle
 - MCNC benchmarks to 256 4-LUTs
 - no interconnect accounting

Number of Registers	1	2	3	4	5	6	7	8	9	10
Percentage	72	16	4.5	2.2	1.3	0.96	1.2	0.46	0.12	0.11

– average 1.7 registers/LUT (some circuits 2--7)

Penn ESE534 Spring2010 -- DeHon

22

Flop Experiment #2

- Pipeline and retime to HSRA cycle
 - place on HSRA
 - single LUT or interconnect timing domain
 - same MCNC benchmarks

Number of Registers	1	2	3	4	5	6	7	8	9	10	>10
Percentage	60	6.9	5.9	3.8	4.3	2.7	2.6	1.9	1.5	1.2	9.2

– average 4.7 registers/LUT

Penn ESE534 Spring2010 -- DeHon

[Tsu et al., FPGA 1999]

23

Retiming Requirements

- Retiming requirement depends on parallelism and performance
- Even with a given amount of parallelism
 - Will have a distribution of retiming requirements
 - May differ from task to task
 - May vary **independently** from compute/interconnect requirements
 - Another balance issue to watch
 - Balance with compute, interconnect
 - Need a canonical way to measure
 - Like Rent?


Penn ESE534 Spring2010 -- DeHon

24

Retiming Supply

Optional Output

- Flip-flop (optionally) on output

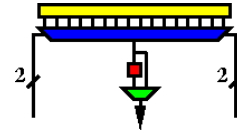

- flip-flop: $4-5K\lambda^2$
- Switch to select: $\sim 5K\lambda^2$
- Area: 1 LUT ($800K \rightarrow 1M\lambda^2/\text{LUT}$)
- Bandwidth: 1b/cycle


Output

- Single Output
 - Ok, if don't need other timings of signal
- Multiple Output
 - more routing



Input

- More registers ($K\times$)
 - $7-10K\lambda^2/\text{register+mux}$
 - $4\text{-LUT} \Rightarrow 30-40K\lambda^2/\text{depth}$
- No more interconnect than unretimed
 - **open**: compare savings to additional reg. cost
 - Area: 1 LUT ($1M+d*40K\lambda^2$) get Kd regs
 - $d=4, 1.2M\lambda^2$
 - Bandwidth: K/cycle
 - $1/d$ th capacity

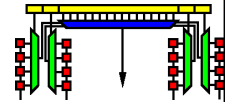

Preclass 3

Diagram	Description	Area per Block	Blocks Needed	Total Area	Best?
	4-LUT with single optional flip-flop on output	$1.01M\lambda^2$			
	4-LUT with configurable depth output register with maximum depth 4	$1.04M\lambda^2$			
	4-LUT with configurable depth input registers with maximum depth 4	$1.16M\lambda^2$			

Day 5

Some Numbers (memory)

- Unit of area = λ^2 ($F=2\lambda$)
 - [more next week]
- Register as stand-alone element $\approx 4K\lambda^2$
 - e.g. as needed/used last lecture
- Static RAM cell $\approx 1K\lambda^2$
 - SRAM Memory (single ported)
- Dynamic RAM cell (DRAM process) $\approx 100\lambda^2$
- Dynamic RAM cell (SRAM process) $\approx 300\lambda^2$

Retiming Density

- LUT+interconnect $\approx 1M\lambda^2$
- Register as stand-alone element $\approx 4K\lambda^2$
- Static RAM cell $\approx 1K\lambda^2$
 - SRAM Memory (single ported)
- Dynamic RAM cell (DRAM process) $\approx 100\lambda^2$
- Dynamic RAM cell (SRAM process) $\approx 300\lambda^2$
- Can have much more retiming memory per chip if put it in large arrays
 - ...but then cannot get to it as frequently

Penn ESE534 Spring2010 -- DeHon

31

Retiming Structure Concerns

- Area: λ^2/bit
- Throughput: bandwidth (bits/time)
- Energy

Penn ESE534 Spring2010 -- DeHon


32

Just Logic Blocks

- Most primitive

– build flip-flop out of logic blocks

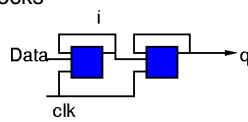- $I \leftarrow D^*/\text{Clk} + I^*\text{Clk}$
- $Q \leftarrow Q^*/\text{Clk} + I^*\text{Clk}$



- Area: 2 LUTs (800K \rightarrow $1M\lambda^2/\text{LUT}$ each)
- Bandwidth: 1b/cycle

Penn ESE534 Spring2010 -- DeHon


33

Separate Flip-Flops

- Network flip flop w/ own interconnect

- + can deploy where needed
- requires more interconnect

- + Vary LUT/FF ratio
 - Arch. Parameter

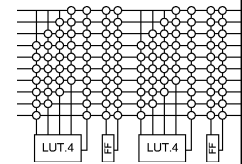

- Assume routing \propto inputs
 - 1/4 size of LUT
- Area: $200K\lambda^2$ each
- Bandwidth: 1b/cycle

Penn ESE534 Spring2010 -- DeHon

34

Virtex SRL16

- Xilinx Virtex 4-LUT
 - Use as 16b shiftreg

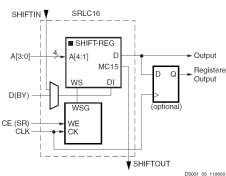



Figure 21: Shift Register Configurations

- Area: $\sim 1M\lambda^2/16 \approx 60K\lambda^2/\text{bit}$
 - Does not need CLBs to control
- Bandwidth: 1b/2 cycle (1/2 CLB)
 - 1/16 th capacity

Penn ESE534 Spring2010 -- DeHon

35

Register File Memory Bank

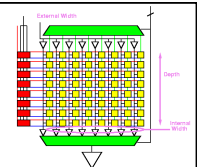


- From MIPS-X
 - $1K\lambda^2/\text{bit} + 500\lambda^2/\text{port}$
 - $\text{Area}(\text{RF}) = (d+6)(W+6)(1K\lambda^2 + \text{ports} * 500\lambda^2)$
- $w \gg 6, d \gg 6 \quad l+o=2 \Rightarrow 2K\lambda^2/\text{bit}$
- $w=1, d \gg 6 \quad l+o=4 \Rightarrow 35K\lambda^2/\text{bit}$
 - comparable to input chain
- More efficient for wide-word cases

Penn ESE534 Spring2010 -- DeHon

36

Xilinx CLB

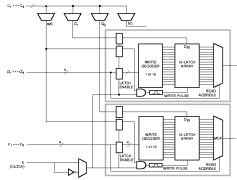- Xilinx 4K CLB
 - as memory
 - works like RF
- Area: $1/2$ CLB ($640K\lambda^2$)/ $16 \approx 40K\lambda^2/\text{bit}$
 - but need 4 CLBs to control
- Bandwidth: $1b/2$ cycle ($1/2$ CLB)
 - $1/16$ th capacity




Memory Blocks

- SRAM bit $\approx 1200\lambda^2$ (large arrays)
- DRAM bit $\approx 100\lambda^2$ (large arrays)
- Bandwidth: W bits / 2 cycles
 - usually single read/write
 - $1/2^A$ th capacity

Dual-Ported Block RAMs

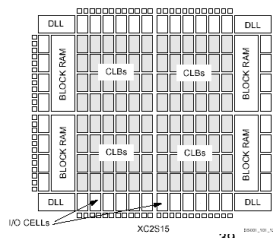- Virtex-6 Series 36Kb memories
- Stratix-4
 - 640b, 9Kb, 144Kb
- Can put $1M/1K \approx 1K$ bits in space of 4-LUT
 - Trade few 4-LUTs for considerable memory



Hierarchy/Structure Summary

- “Memory Hierarchy” arises from area/ bandwidth tradeoffs
 - Smaller/cheaper to store words/blocks
 - (saves routing and control)
 - Smaller/cheaper to handle long retiming in larger arrays (reduce interconnect)
 - High bandwidth out of shallow memories
 - Applications have mix of retiming needs

λ^2	DRAM	SRAM	RF bit	FF/RF	RF×1	XC	In FF	net FF	FF/LUT
	100	1200	2K	5K	40K	40K	75K	200K	800K
bw/cap.	$1/10^7$	$1/10^5-10^3$		$1/100$	$1/100$	$1/16$	$1/4$	$1/1$	$1/1$

Modern FPGAs

- Output Flop (depth 1)
- Use LUT as Shift Register (16)
- Embedded RAMs (9Kb,36Kb)
- Interface off-chip DRAM ($\sim 0.1-1$ Gb)
- No retiming in interconnect
 -yet

Modern Processors

- DSPs have accumulator (depth 1)
- Inter-stage pipelines (depth 1)
 - Lots of pipelining in memory path...
- Reorder Buffer (4—32)
- Architected RF (16, 32, 128)
- Actual RF (256, 512...)
- L1 Cache (~ 64 Kb)
- L2 Cache (~ 1 Mb)
- L3 Cache (10-100Mb)
- Main Memory in DRAM ($\sim 10-100$ Gb)

Admin

- Final Exercise
 - Basic statement out
 - Will continue to refine and detail
 - One arch. Desc. to add by next Monday
- No new homework grading
- Reading for Wednesday on web

Penn ESE534 Spring2010 -- DeHon

43

Big Ideas [MSB Ideas]

- Tasks have a wide variety of retiming distances (depths)
 - Within design, among tasks
- Retiming requirements vary independently of compute, interconnect requirements (balance)
- Wide variety of retiming costs
 - $100 \lambda^2 \rightarrow 1M\lambda^2$
- Routing and I/O bandwidth
 - big factors in costs
- Gives rise to memory (retiming) hierarchy 44

Penn ESE534 Spring2010 -- DeHon